

Report from Turin on Front-End design


Ennio Monteil - Angelo Rivetti - Luca Pacher

Turin, 27/08/2013


monteil@to.infn.it

Charge Sensitive Amplifier

 - Single-ended common source amplifier with a cascoded input
- Simulation of the **noise contribution** due to the electronics
- Comparison with the **EKV model**
- Gain can be increased using a **regulated cascode** for the PMOS




CSA Noise analysis: results (1)

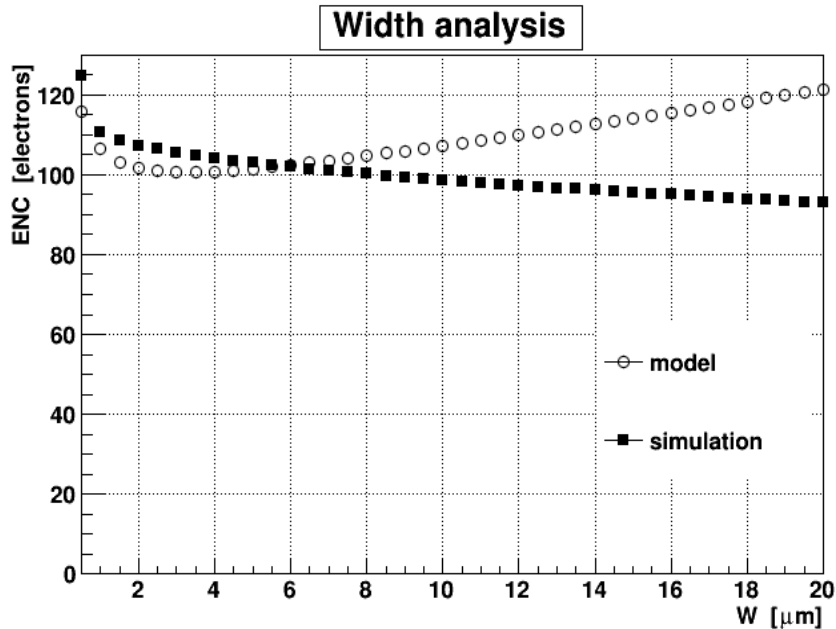

Constraints:

- $L = 130 \text{ nm}$
- Peaking time $T_p = 12.5 \text{ ns}$
- $C_{\text{detector}} = 100 \text{ fF}$
- $I = 1.6 \mu\text{A}$

 Good agreement with the EKV model (within 10%)





Constraints:

- $W = 8 \mu\text{m}$
- $L = 130 \text{ nm}$
- Peaking time $T_p = 12.5 \text{ ns}$
- $C_{\text{detector}} = 100 \text{ fF}$

Noise increases reducing power consumption: need to find the best compromise

CSA Noise analysis: results (2)

 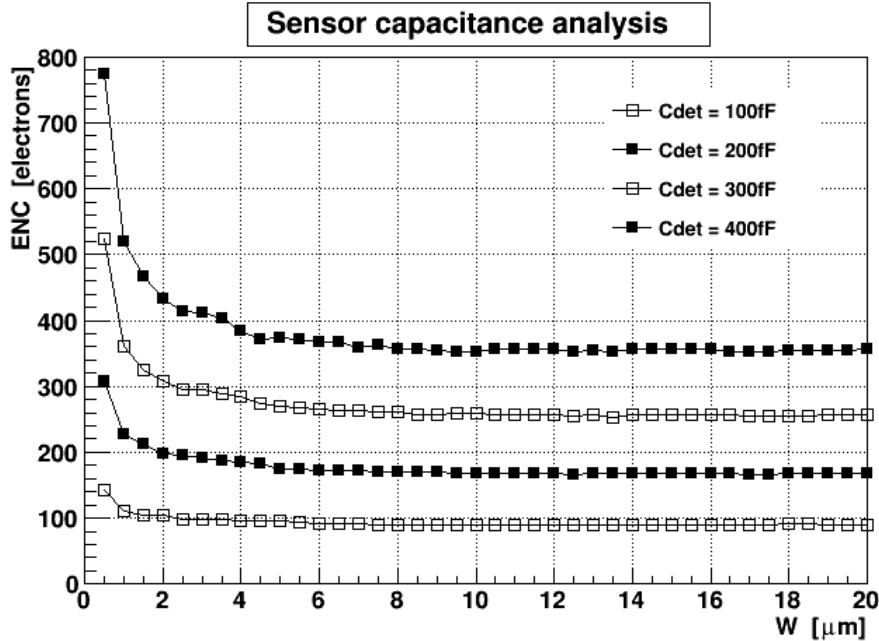


Constraints:

- $L = 130\text{nm}$
- Peaking time $T_p = 12\text{ ns}$
- $I = 1.6\ \mu\text{A}$



ENC linearly dependent on C_{detector}

CSA Noise analysis: results (3)

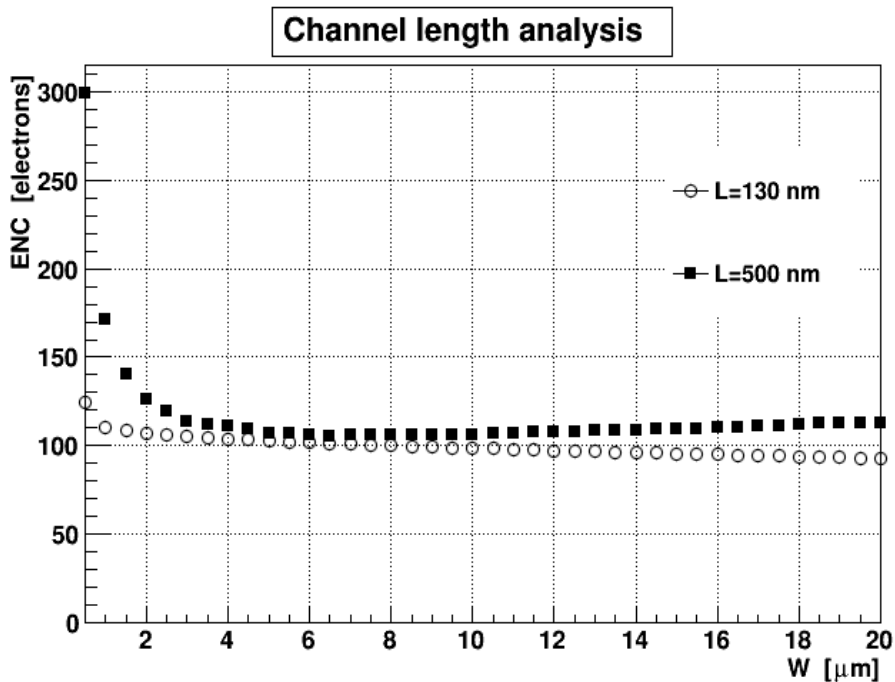

Constraints:

- Peaking time $T_p = 12.5$ ns
- $I = 1.6$ μA
- $C_{\text{detector}} = 100$ fF

Noise **does not increase sensibly** with the channel length

Next steps

- Study of the **feedback network schematic** (bipolar architecture based on the Krummenacher scheme)
- Study of the **gain linearity**
- **Mismatch analysis**: MC simulation of the variation of the transistors parameters due to manufacturing fluctuations
- Simulation of the **power consumption**
- Implementation of the **leakage compensation** circuit
- Connection of this stage with the **comparator**



Comparator design (1)

- build a full-featured front-end analog chain → complete VFE with ***synchronous binary readout***


- go ahead with ***discrete time*** comparators and ***autozeroing*** studies

- try to keep the design as simple as possible

 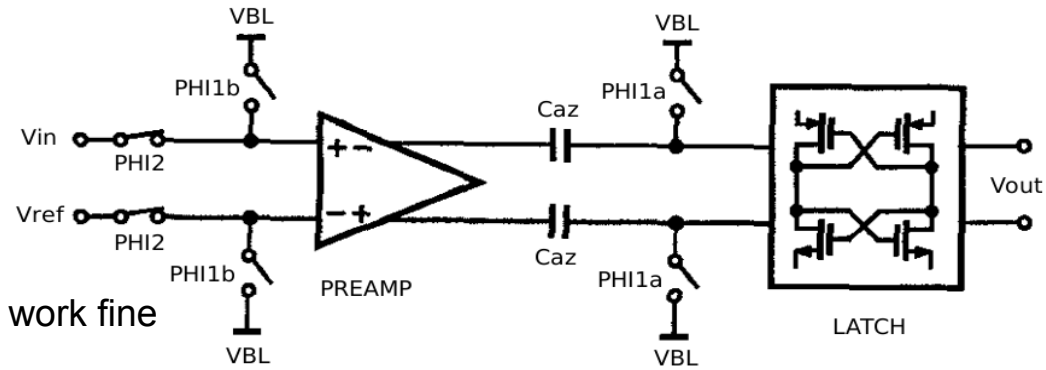→ ***one stage PREAMP + LATCH + OOS*** work fine



Comparator design (2)

 


- at present, offset compensation performed **each BX** (maybe redundant ?)
- realistic analog pulses coming from the VFE fed to the comparator
- **1000 electrons** minimum detectable signal constraint fulfilled
- 100% hit efficiency verified in **MC mismatches** simulations (no missing/fake hits due to offsets)
- 'ad hoc' **control signals**, move to a **logic FSM algorithm** for a more realistic design indeed

Thanks for your
attention

Backup

Charge Sensitive Amplifier

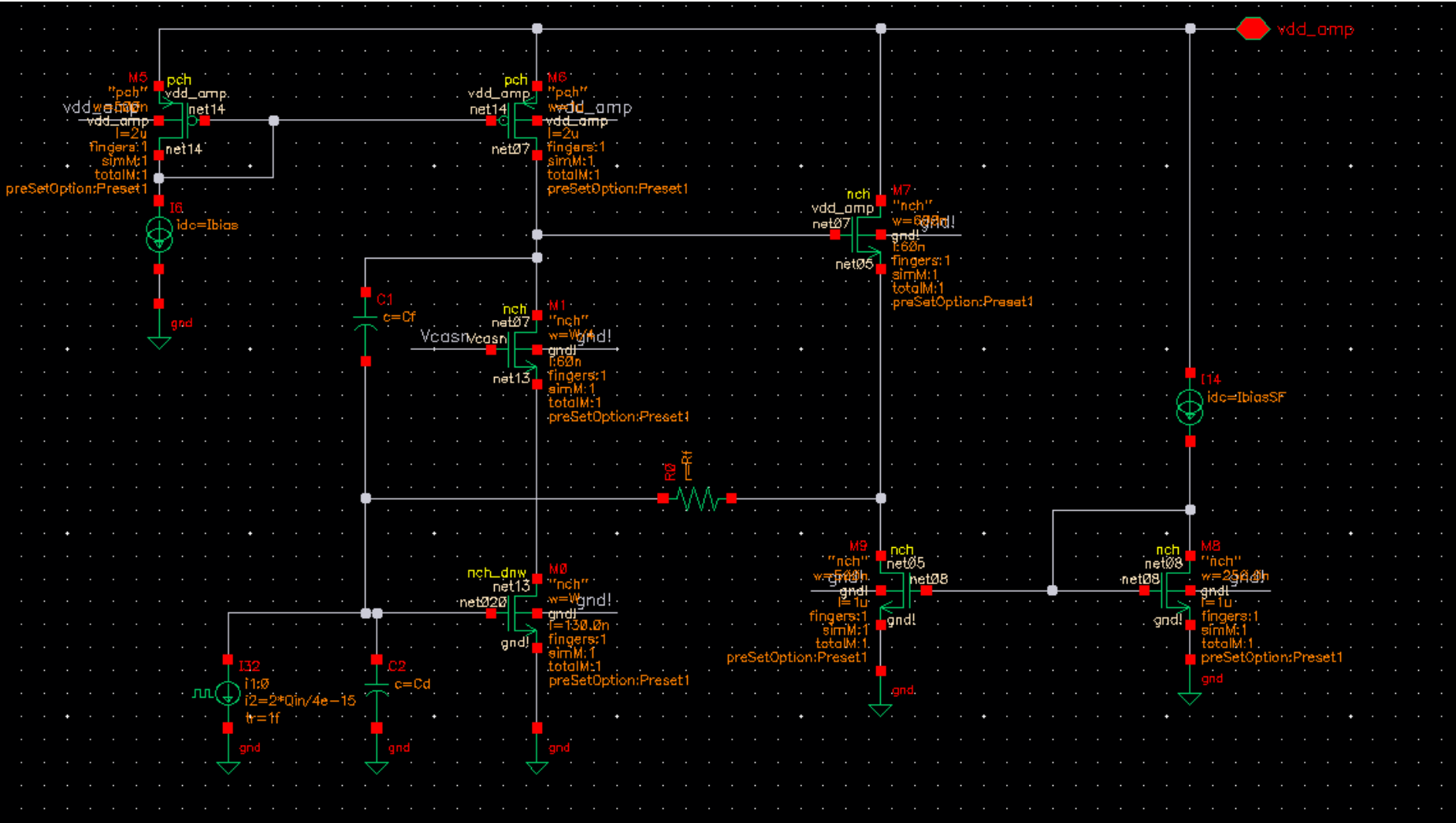

Comparator - PREAMP schematic

