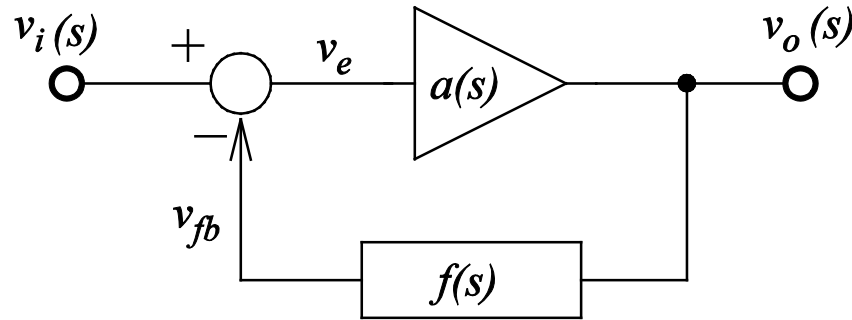


# Evaluation of stability in Charge Sensitive Amplifiers (CSA)

Jan Kaplon

CERN PH-ESE/ME

# Negative feedback - why?




$$T(j\omega) = \frac{v_o(s)}{v_i(s)} = \frac{a(j\omega)}{1 + a(j\omega)f(j\omega)} \approx \frac{1}{f(j\omega)} \quad \text{if } a(j\omega) \gg 1$$

Using negative feedback provides:

- Stabilisation of gain (process variation, temperature)
- Improvement of PSRR and distortion
- Bandwidth-gain trading
- Negative feedback can be used to change the input or output impedances (allows for low input impedance CSA)**

# Feedback amplifier - descriptions

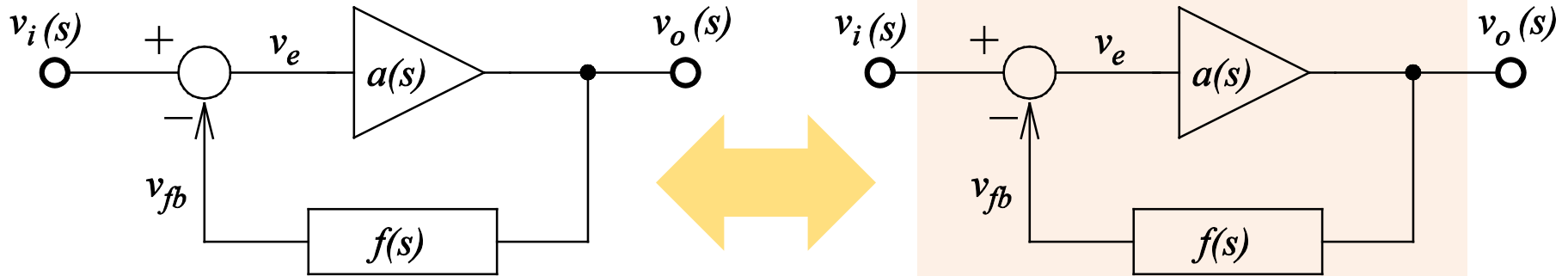


$$T(j\omega) = \frac{v_o(s)}{v_i(s)} = \frac{a(j\omega)}{1 + a(j\omega)f(j\omega)}$$

Feedback amplifier described by amplifier and feedback network functions in frequency domain

$$T(s) = \frac{v_o(s)}{v_i(s)} = H \frac{b_0 s^n + b_1 s^{n-1} + \dots + b_{n-1} s + b_n}{c_0 s^n + c_1 s^{n-1} + \dots + c_{n-1} s + c_n}$$

Network function in Laplace domain
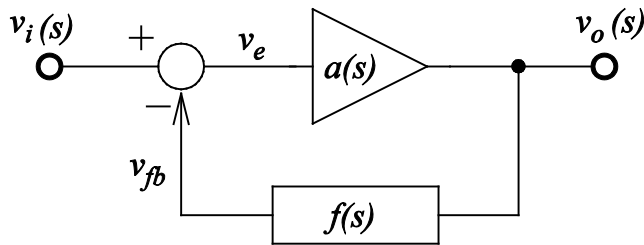
# Stability criterion for open loop analysis




$$T(j\omega) = \frac{v_o(s)}{v_i(s)} = \frac{a(j\omega)}{1 + a(j\omega)f(j\omega)}$$

Assumption that  $a(j\omega) \gg 1$  valid for frequencies below bandwidth limitation, at high frequency when loop gain approaches 1 we have to check the phase to prevent denominator becomes 0!

Barkhausen stability criterion  $\rightarrow a(j\omega)f(j\omega) \neq -1$


Check amplitude and phase of the loop gain ( $a \cdot f$ )
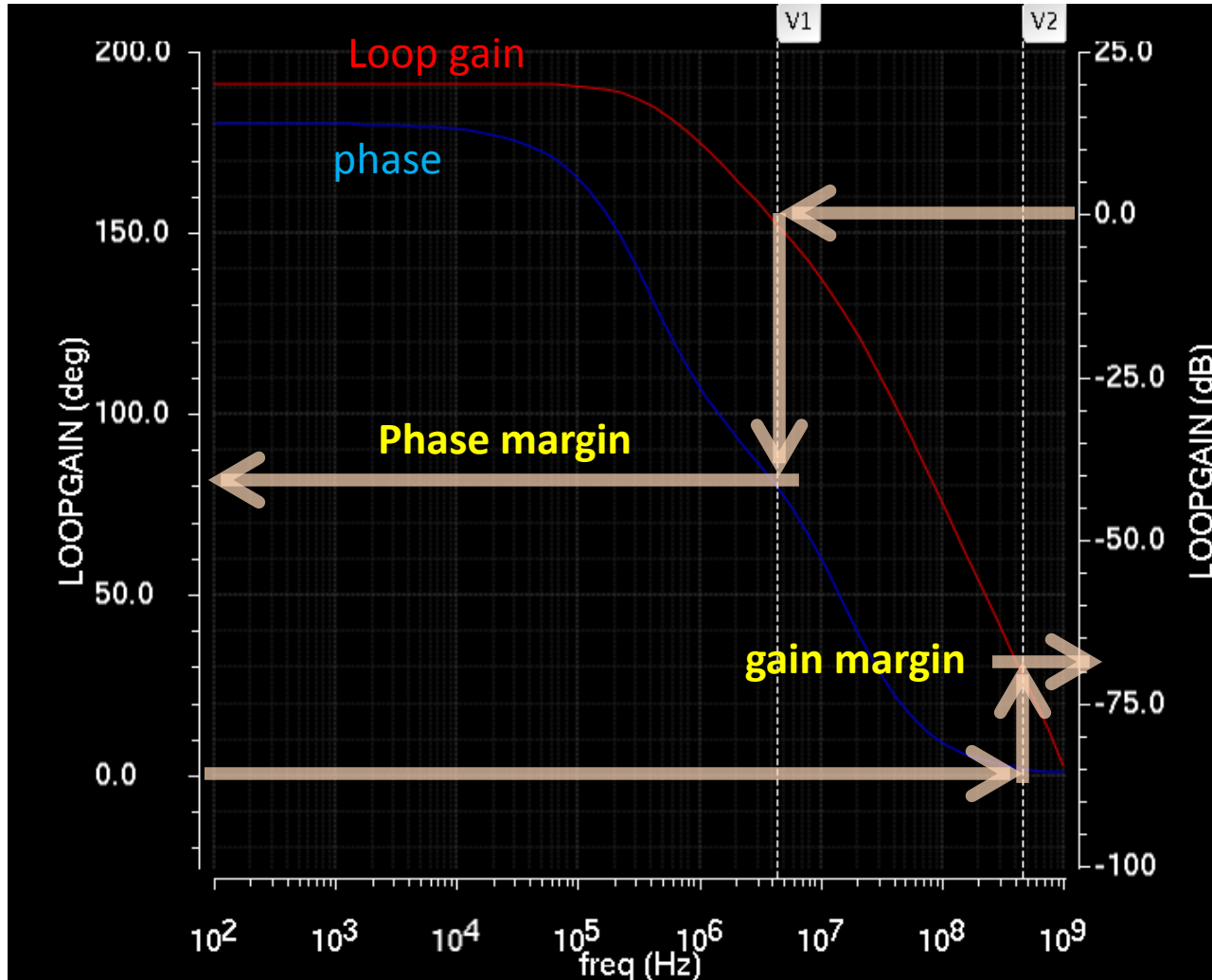
# Stability measure for open loop analysis: phase and gain margins



Loop gain amplitude and phase of two pole system


# CAD simulation for open loop analysis

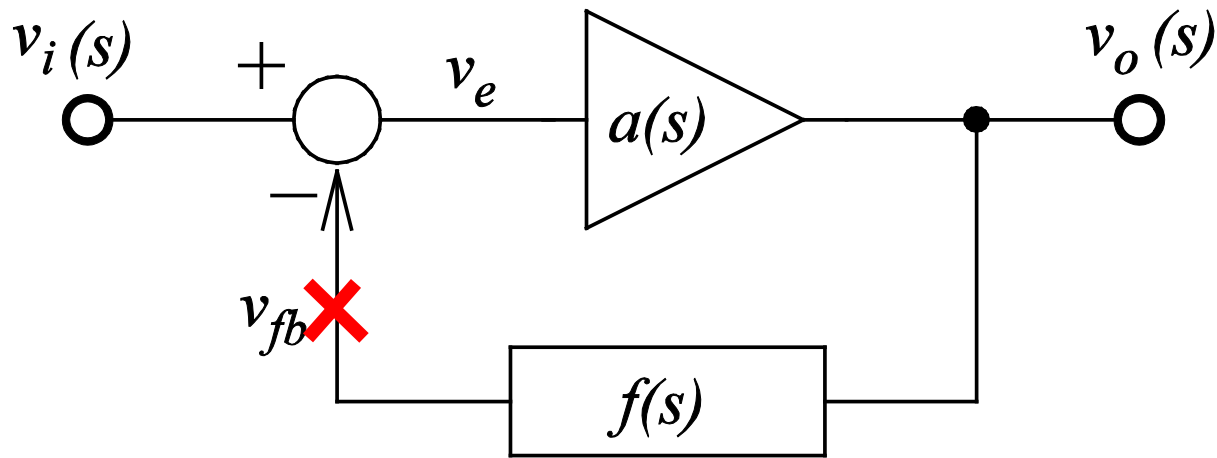

## Test loop gain amplitude and phase:

- AC simulation of open loop circuit (sensing signal at the output of the open loop)
- STB simulation of closed loop circuit in Spectre (method based on Middlebrook double injection method)
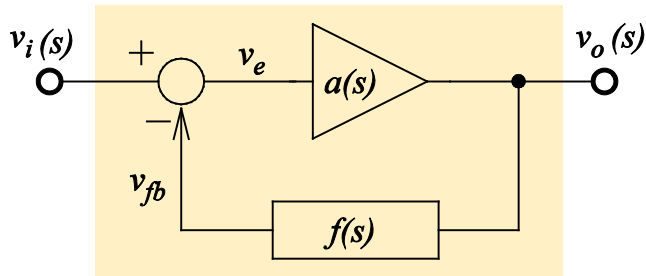
# Stability criteria for close loop analysis



$$T(s) = \frac{v_o(s)}{v_i(s)} = H \frac{b_0 s^n + b_1 s^{n-1} + \dots + b_{n-1} s + b_n}{c_0 s^n + c_1 s^{n-1} + \dots + c_{n-1} s + c_n} = K \frac{(s - z_n)(s - z_{n-1}) \dots (s - z_2)(s - z_1)}{(s - p_n)(s - p_{n-1}) \dots (s - p_2)(s - p_1)}$$

After factorization

Zeroes (reals or conjugated complex pairs)


Poles (reals or conjugated complex pairs)

**Time response bounded (stable system) → all poles with negative real parts (all poles on the left half s-plane)**

Checking of pole locations for polynomial which are not factorized (rough results of analytical calculations):

- ❑ Routh-Hurwitz criterion (checking coefficients of Ruth array – tedious algorithm for simplified circuits only)
- ❑ Run PZ (pole zero) analysis in Spectre or HSpice for full or simplified circuit
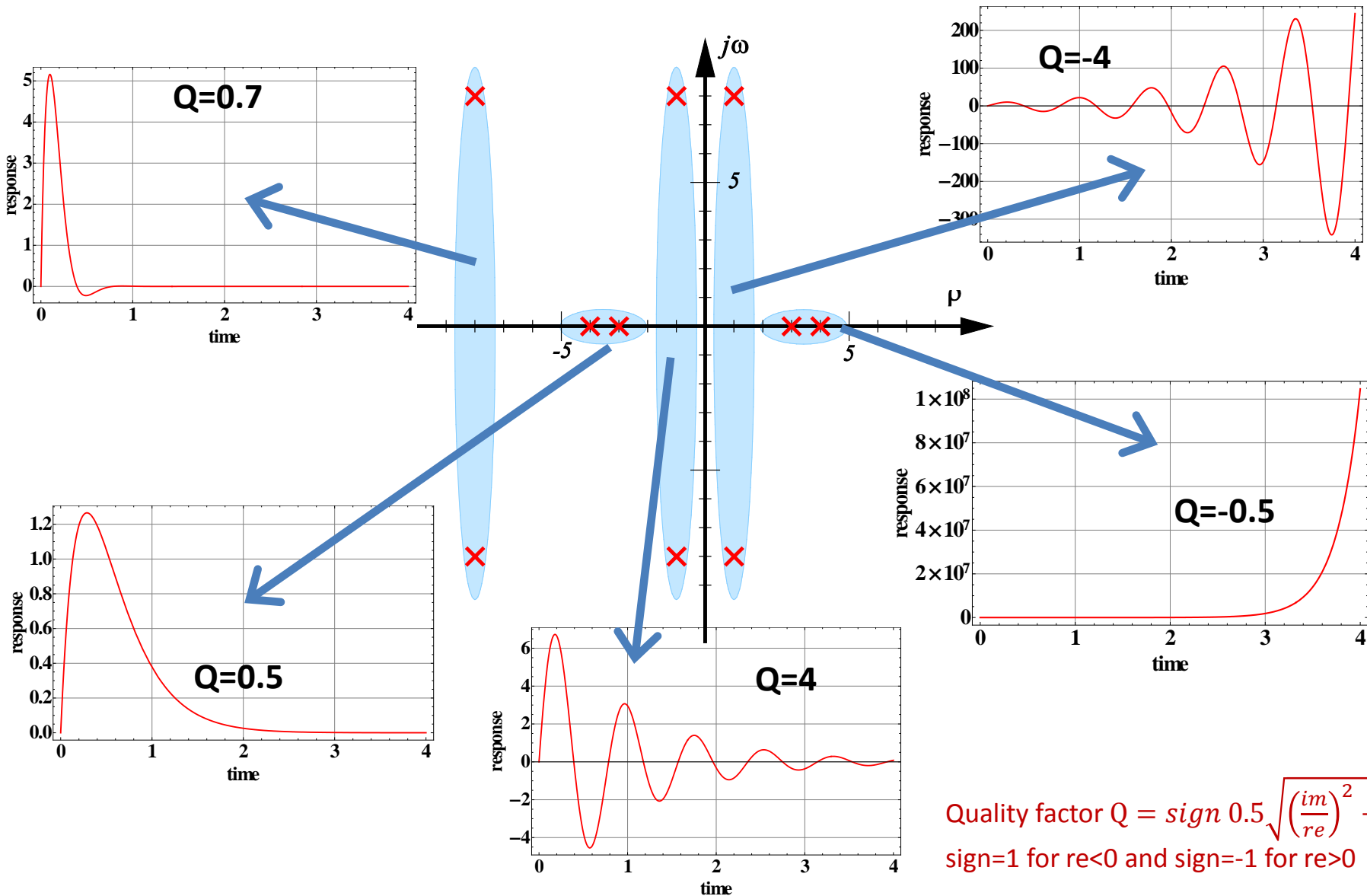
# Time responses of two-pole system, s-plane



Quality factor  $Q = \text{sign} \cdot 0.5 \sqrt{\left(\frac{im}{re}\right)^2 + 1}$   
 sign=1 for  $re < 0$  and sign=-1 for  $re > 0$



# Close loop analysis

## Analysis of the location of poles:

- ❑ Analytical analysis of the simplified circuits
- ❑ PZ analysis in HSpice or Spectre (list of poles and zeroes in the circuit)

Analytical analysis :

- ❑ Simplifying the circuit
- ❑ Finding network function (building and solving equations)
- ❑ Factorization of denominator (poles) and numerator (zeroes) of network function based on the assumption that all poles and zeroes are well separated (and are on the left half plane – circuit is stable)

$$\left(1 + \frac{s}{P_1}\right) \left(1 + \frac{s}{P_2}\right) \left(1 + \frac{s}{P_3}\right) \approx 1 + \frac{s}{P_1} + \frac{s^2}{P_1 P_2} + \frac{s^3}{P_1 P_2 P_3} \quad \text{if } P_1 \ll P_2 \ll P_3$$

# Open loop analysis versus close loop analysis (phase margin PM versus pole quality Q)


**Q=0.5 (two real poles/asymptotic response) → phase margin from  $\sim 83^\circ$  and above (\*)**

**Q=0.7 (pair of complex poles, response with  $\sim 5\%$  undershoot) → phase margin  $\sim 70^\circ$**

(\*) The conversion between pole quality and phase margin is really ambiguous (one can find system with  $PM=85^\circ$  and  $Q=0.55$ ).

- ❑ Phase margin depends on position of poles as well as type of feedback.
- ❑ Time response depends on location of zeroes and poles not on phase margin
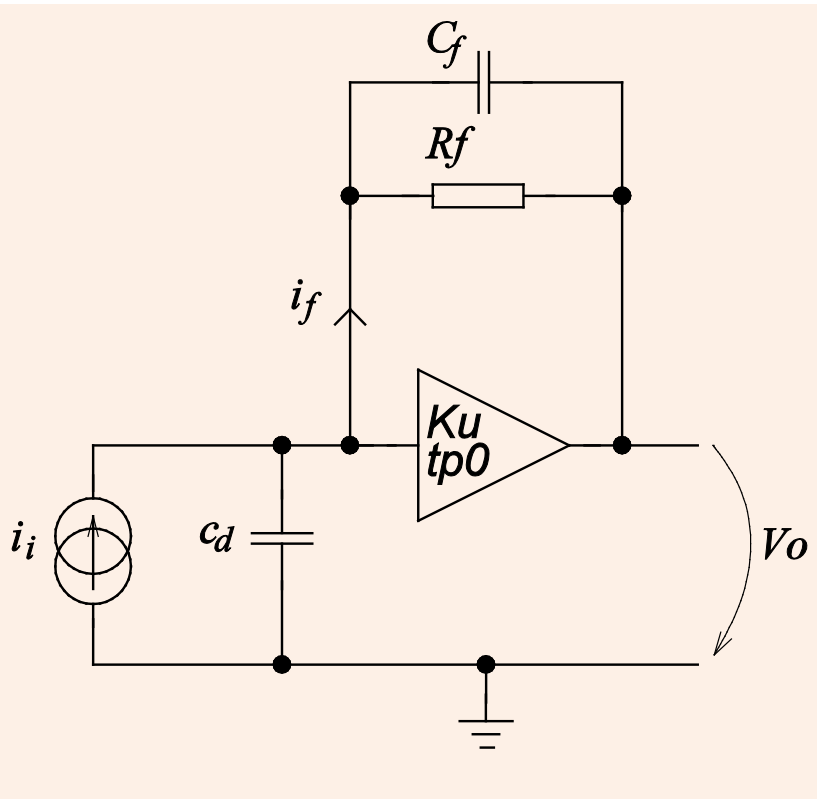
# Ideal CSA (single pole amplifier, ideal output buffer) – closed loop analysis – analytical approach



$$T(s) = \frac{V_o}{i_i} = \frac{K_{us} Z_f Z_i}{Z_f + Z_i + K_{us} Z_i}$$

$$P1 \cong \frac{1}{R_f C_f}$$

$$P2 \cong \frac{K_u}{\frac{cd}{C_f} tp0}$$

**GBP**


Stable circuit → finding parameters of the feedback for which  $P1 \ll P2$  (real and well separated poles)

$$Z_i = \frac{1}{s c_d} \quad K_{us} = \frac{K_u}{1 + s tp0} \quad Z_f = \frac{R_f}{1 + s tf} \quad tf = R_f C_f$$

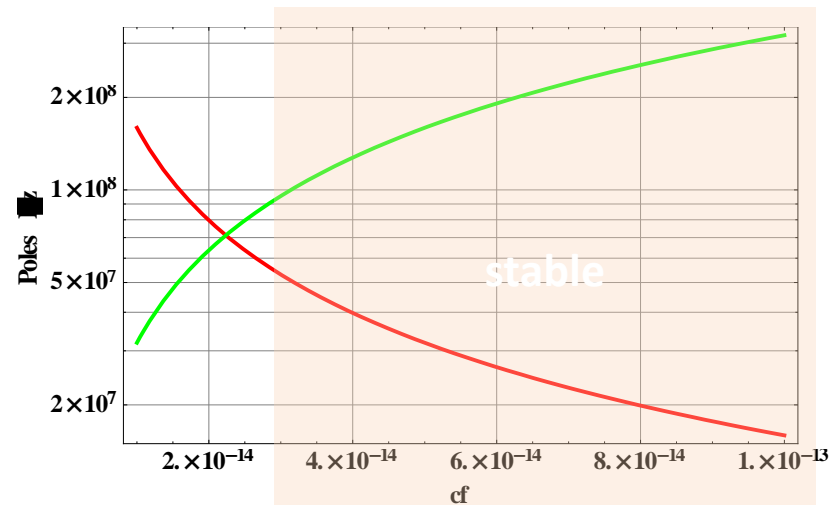
# Ideal CSA (2 pole system)

For good phase margin  $P1 \ll P2$  ( $P1$  and  $P2$  real)

$$P1 \cong \frac{1}{Rf Cf} \quad P2 \cong \frac{GBP}{\frac{cd}{Cf}}$$





$Cd=1pF$

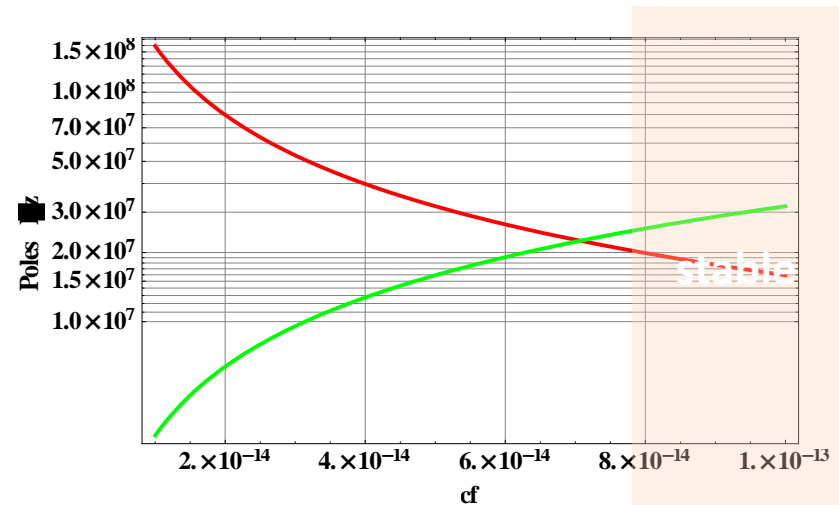

$Cd=10pF$


$Rf=100k$ ,  $tp0=50ns$ ,  $Ku=60dB$  ( $GBP \sim 2GHz$ )

# Spectre PZ analysis of ideal CSA

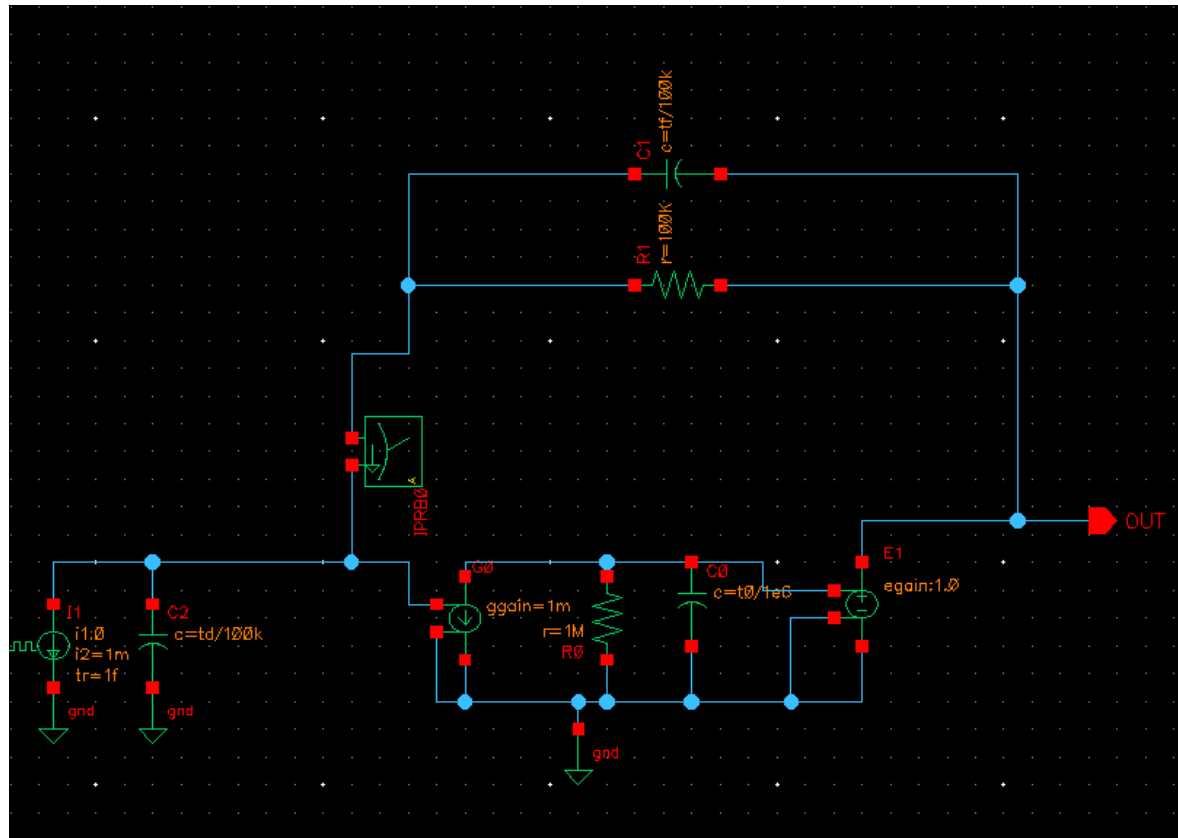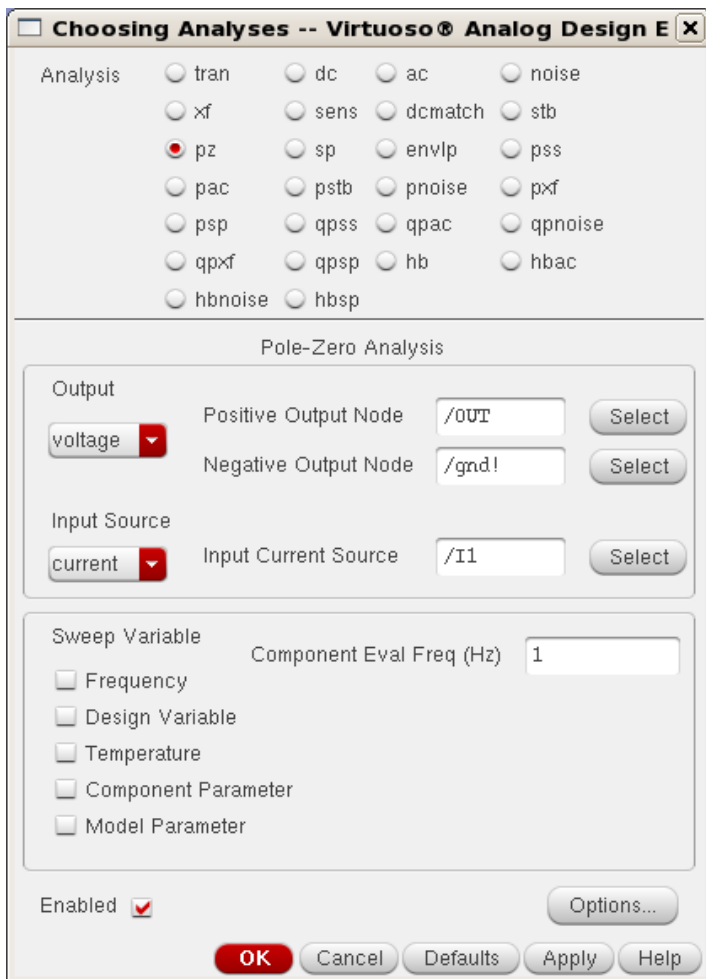

- Circuit in close loop configuration
- Definition of input and output nodes

# Spectre PZ analysis of ideal CSA

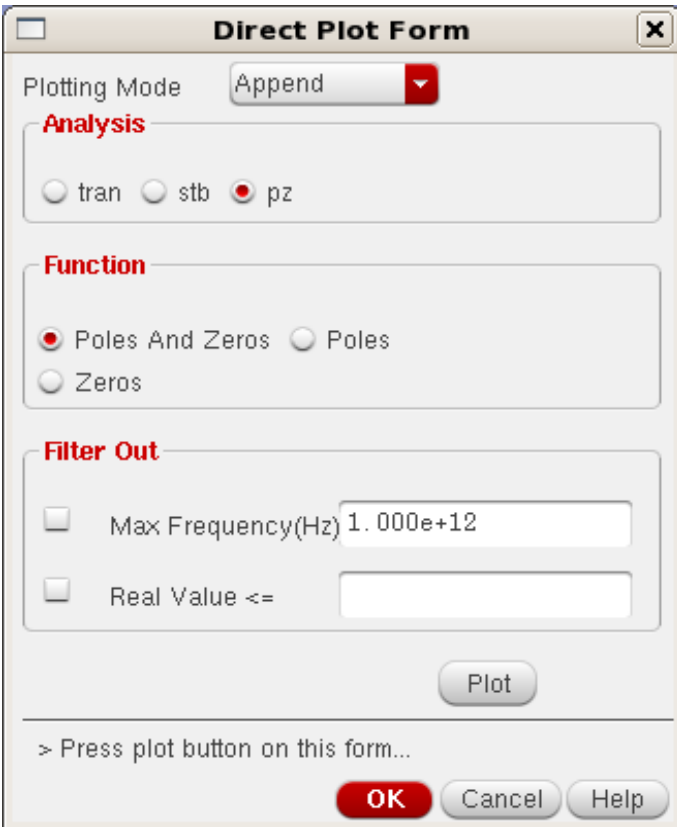

**Direct Plot Form**

Plotting Mode: Append

**Analysis**

tran  stb  pz

**Function**

Poles And Zeros  Poles  
 Zeros

**Filter Out**


Max Frequency(Hz) 1.000e+12

Real Value <=

Plot

> Press plot button on this form...

OK Cancel Help

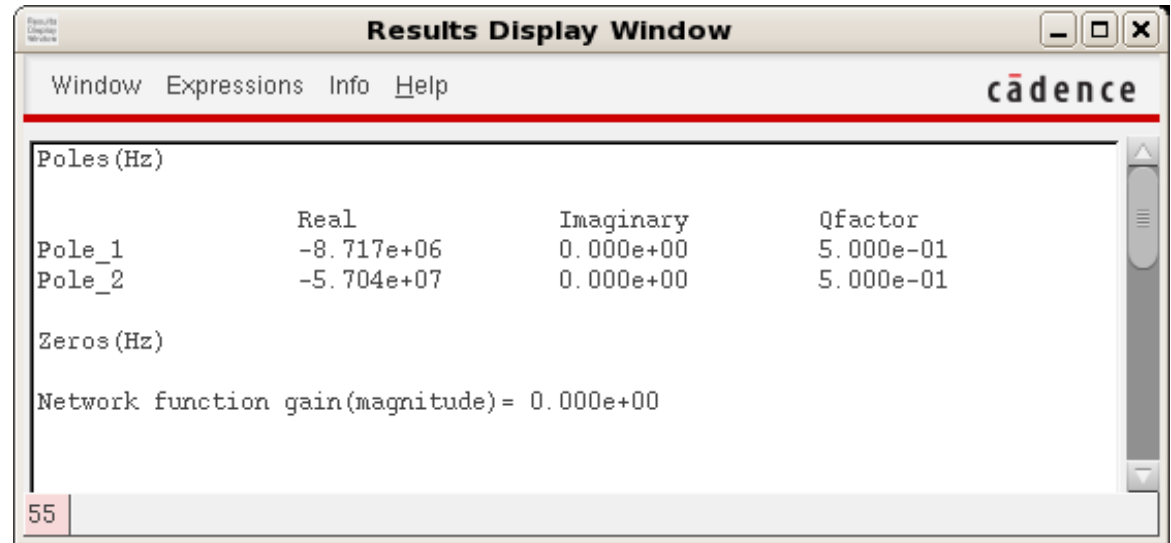

**Results Display Window**

Window Expressions Info Help cadence

Poles (Hz)

	Real	Imaginary	Qfactor
Pole_1	-8.717e+06	0.000e+00	5.000e-01
Pole_2	-5.704e+07	0.000e+00	5.000e-01

Zeros (Hz)


Network function gain(magnitude) = 0.000e+00

55

Access to results through direct plot form or print summary

Ideal CSA with  $R_f=100k$ ,  $t_{p0}=50ns$ ,  $K_u=60dB$  (GBP  $\sim 2GHz$ ),  $t_f=20ns$ ,  $c_d=10p$ ,  $PM=86^\circ$
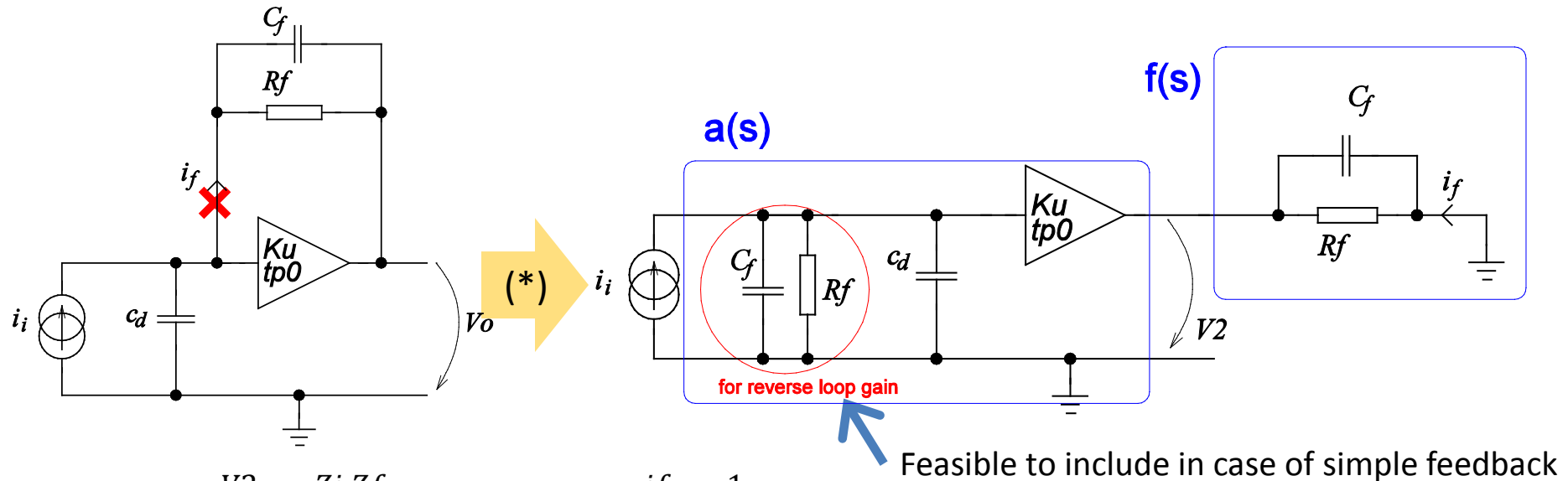
# CSA; shunt-shunt feedback type. Open loop analysis.




$$a(s) = \frac{V_2}{i_i} = \frac{Z_i Z_f}{Z_i + Z_f} K_{us} \quad f(s) = \frac{i_f}{V_2} = \frac{1}{Z_f}$$

$$A_{closed\ loop}(s) = \frac{a(s)}{1 + a(s)f(s)} = T(s) = \frac{K_{us} Z_f Z_i}{Z_f + Z_i + K_{us} Z_i}$$


Loop gain: ratio of  $i_f/i_i \rightarrow$  amplitude and phase of  $i_f$  (for  $i_i=1$ )

(\*) Grey, Meyer, Analysis and Design of Analog Integrated Circuits, chapter 8.5.1


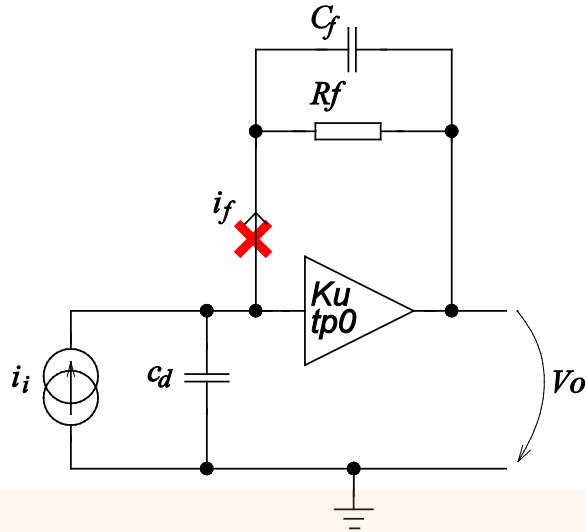
# Open loop analysis of ideal CSA – examples of loop gain phase behaviour


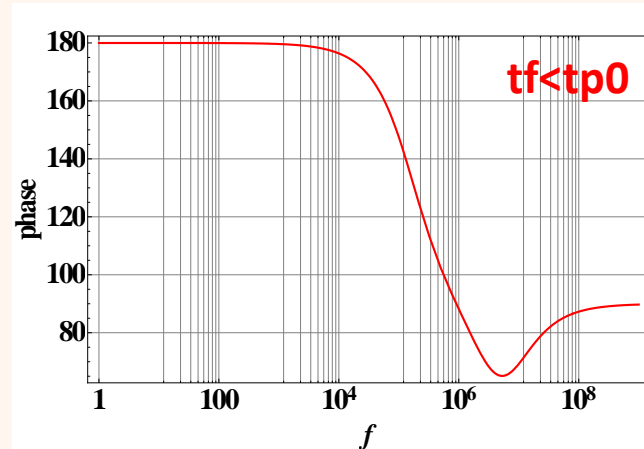
$$\text{Loop Gain} = Ku \frac{1 + s tf}{(1 + s (tf + Rf cd))(1 + s tp0)}$$




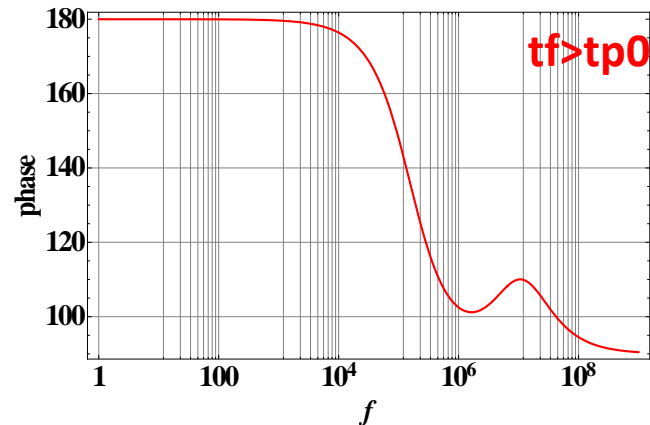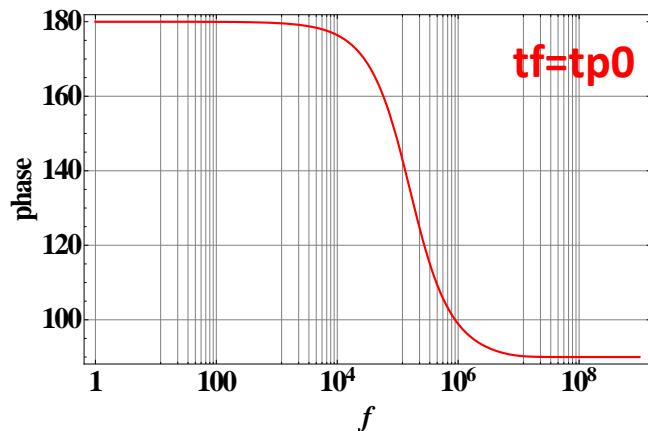$Rf=100k$ ,  $tp0=50ns$ ,  $Ku=60dB$  (GBP  $\sim 2GHz$ ),  $tf=20ns$ ,  $cd=10p$





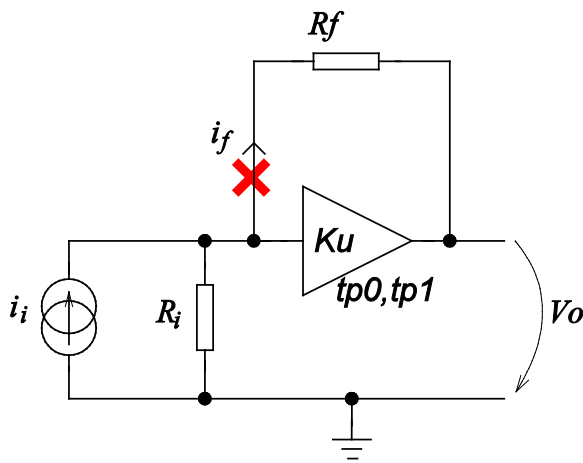
# Loop gain phase of shunt-shunt feedback amplifier (for comparison) – always monotonic



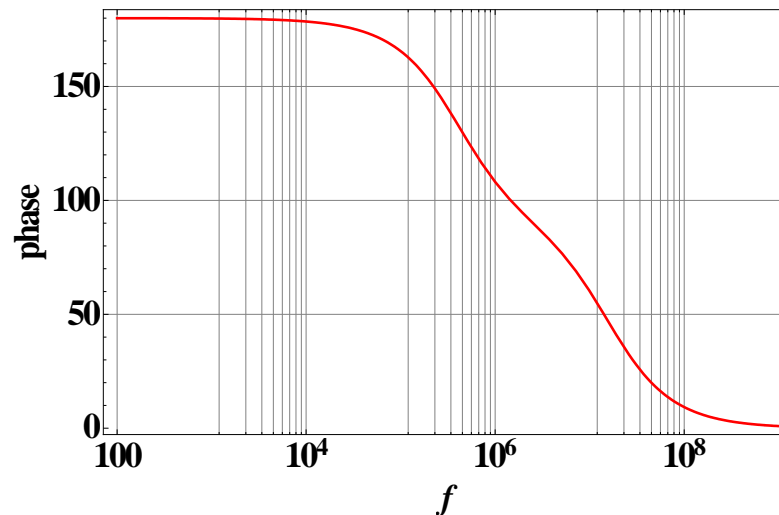
$$\text{Loop Gain} = Ku \frac{R_i}{R_i + R_f} \frac{1}{(1 + s tp_0)(1 + s tp_1)}$$



$R_f=1\text{M}, R_i=10\text{k}, tp_0=10\text{ns}, tp_1=400\text{ns}, Ku=60\text{dB}$

# CSA- loop partially open

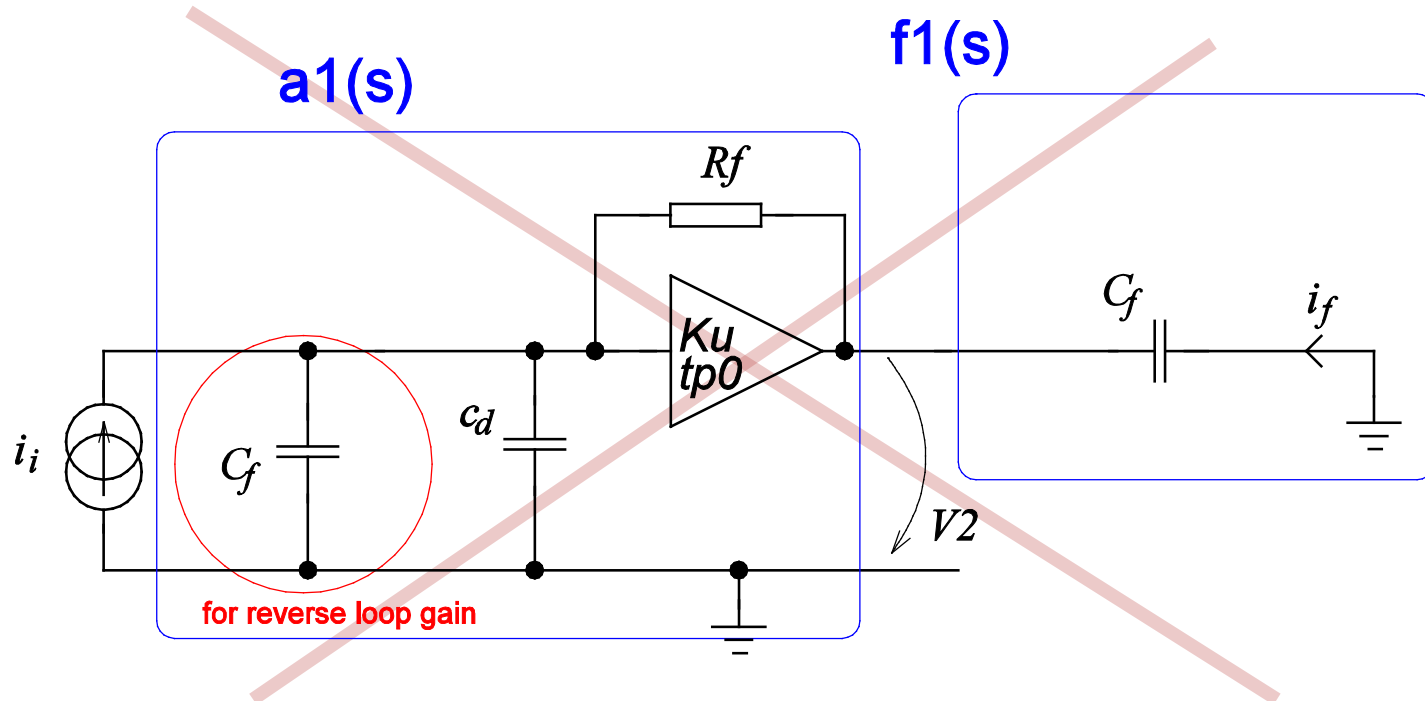

$$A_{closed\ loop}(s) = \frac{a1(s)}{1 + a1(s)f1(s)} = T(s) = \frac{Kus\ Zf\ Zi}{Zf + Zi + Kus\ Zi}$$

The loop is not fully open – the loop gain and its phase is not significant for the stability estimation


# Open loop analysis

## Physical opening of the loop has some drawbacks:

- ❑ Problems with DC operating point of the circuits → necessity of use replicas for generation of bias voltages, tricks for compensation of leakage (gate or base) currents, creation of special schematics (not the same as used for final circuit) etc.
- ❑ Taking into account the reverse loop gain is difficult for active feedbacks
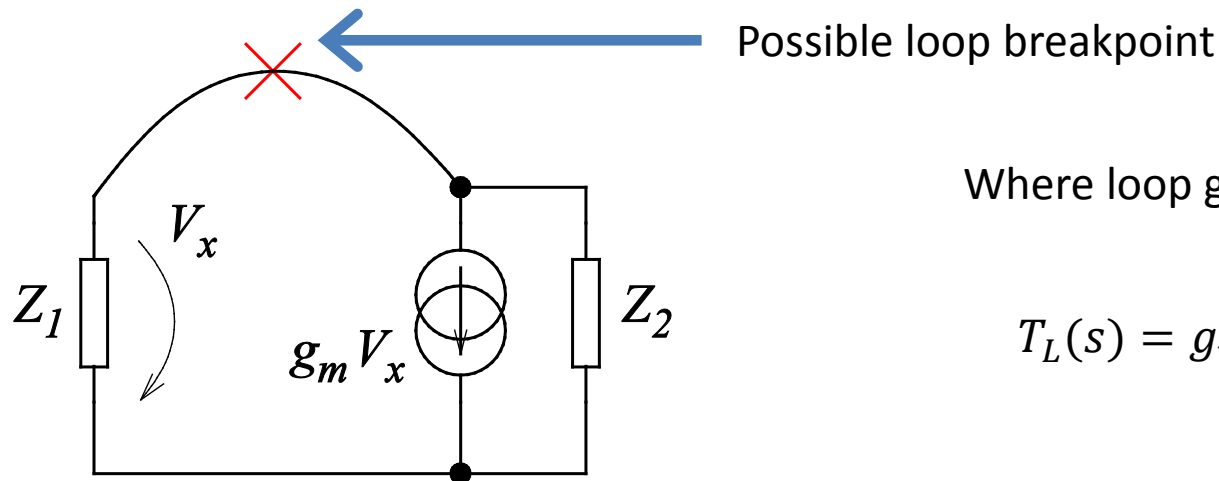
# Calculation (or measurement) of loop gain using Middlebrook Double Injection method – principles

Any single loop feedback circuit can be represented by following scheme:



Where loop gain  $T_L(s)$  is


$$T_L(s) = g_m \frac{Z_1 Z_2}{Z_1 + Z_2}$$

R.D. Middlebrook, *Measurement of loop gain in feedback systems*, Int.J.Electronics, 1975, Vol.38, No.4, 485-512

P.J. Hurst, *Determination of Stability Using Return Ratios in Balanced Fully Differential Feedback Circuits*, IEEE Trans. on Circ. and Systems, Vol.42, No.12, Dec. 1995

Sol Rosenstark, *Feedback amplifier principles*, Macmillan Publishing Company New York, 1985, ISBN 0-02-947810-3


# Middlebrook Double Injection method

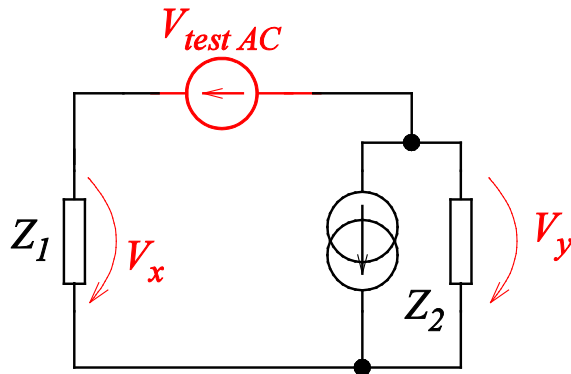

$$\frac{V_y}{V_x} \equiv T_V = g_m Z_2 + \frac{Z_2}{Z_1}$$

Loop Gain:  $T_L = g_m \frac{Z_1 Z_2}{Z_1 + Z_2}$


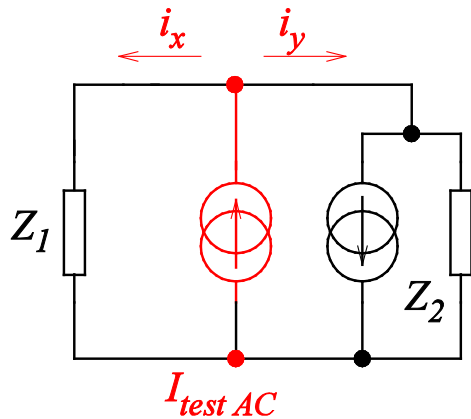
$$T_L = \frac{T_V T_i - 1}{T_V + T_i + 2}$$



$$\frac{i_y}{i_x} \equiv T_i = g_m Z_1 + \frac{Z_1}{Z_2}$$

- ❑ No DC break in the loop, all loading effects included
- ❑ Measure/calculate  $T_V$  and  $T_i$ , then calculate  $T_L$

# Spectre STB analysis of ideal CSA

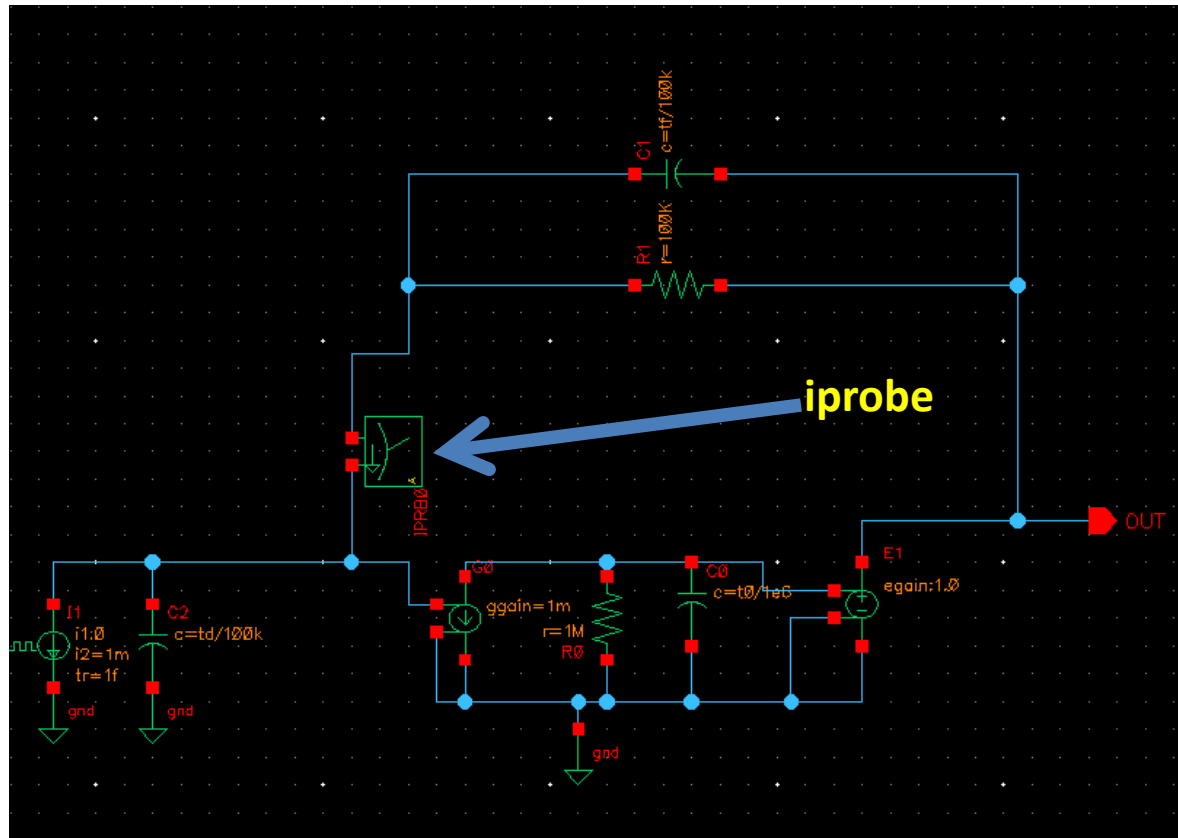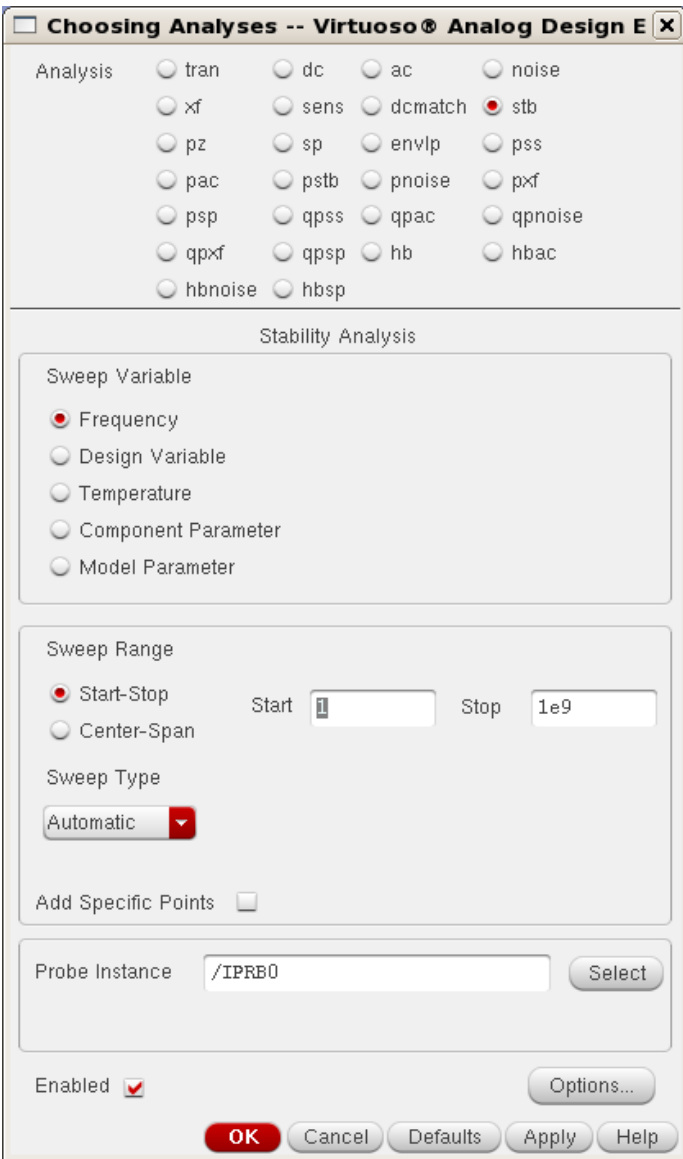

Based on Middlebrook double injection method

- Circuit in close loop configuration
- iprobe component from analogLib defining the loop breakpoint

# Spectre STB analysis of ideal CSA

**Direct Plot Form** [X]

Plotting Mode: Append [v]

**Analysis**

tran  stb  pz

**Function**

Loop Gain  Stability Summary  
 Phase Margin  Gain Margin  
 PM Frequency  GM Frequency

**Modifier**

Magnitude  Phase  Magnitude and Phase


**Magnitude Modifier**

None  dB10  dB20

Add To Outputs  Plot

> Press plot button on this form...


OK Cancel Help

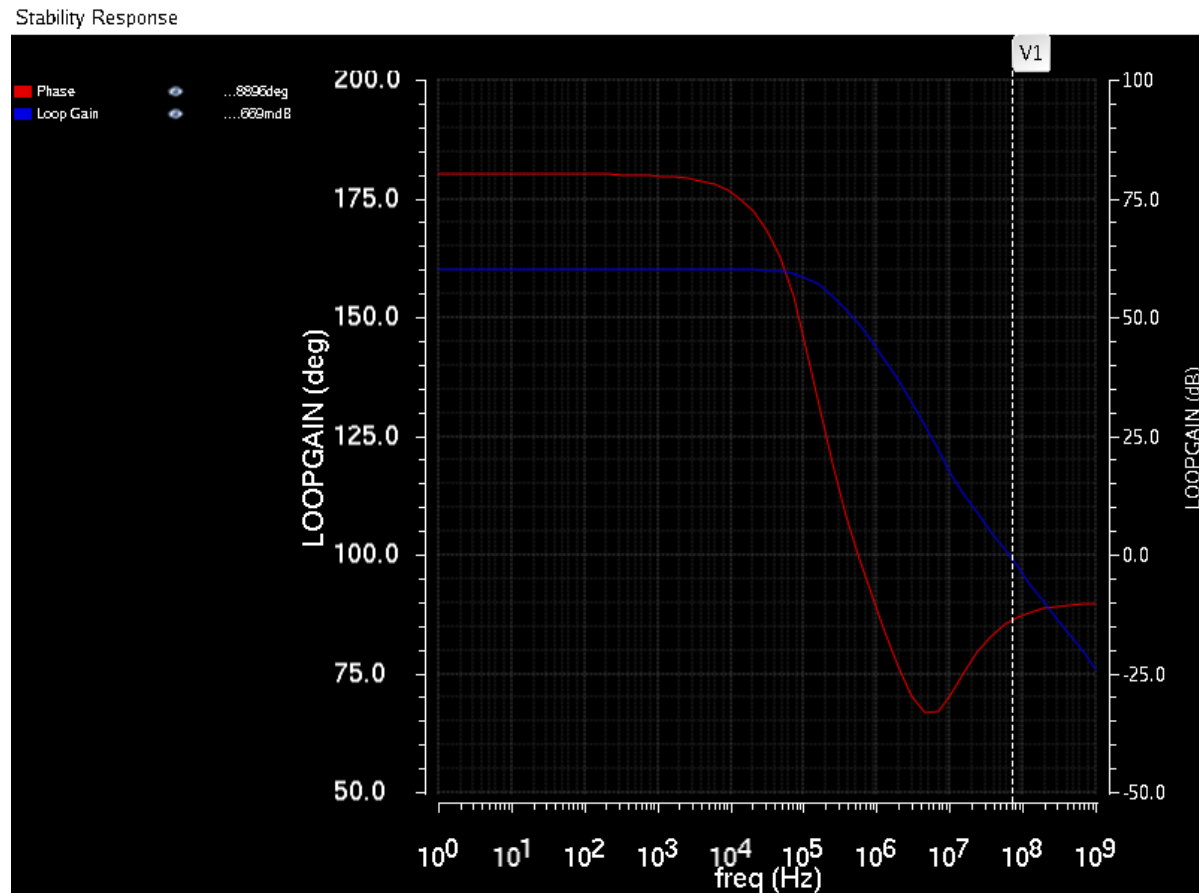

Access to results through direct plot form or print summary

Ideal CSA with  $R_f=100k$ ,  $t_{p0}=50ns$ ,  $K_u=60dB$  (GBP  $\sim 2GHz$ ),  $t_f=20ns$ ,  $c_d=10p$ ,  $PM=86^\circ$ , two real poles
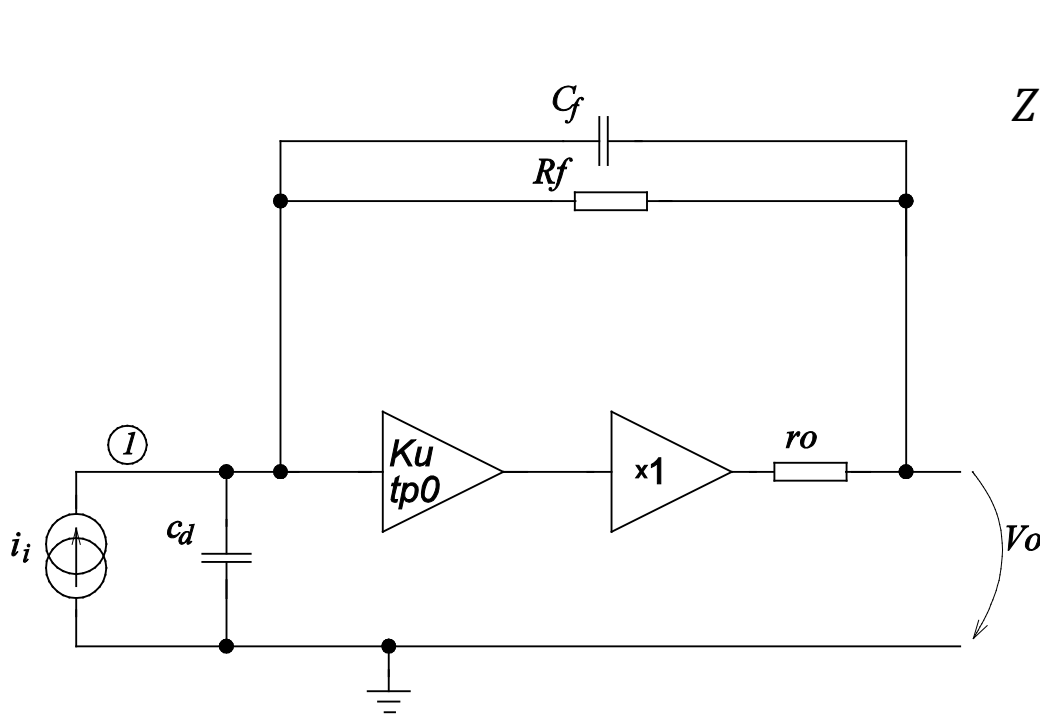
# CSA with finite impedance output buffer – close loop analysis



$$Z_{1,2} \cong \mp \sqrt{\frac{K_u}{r_o C_f t_{p0}}} \quad \text{GBP}$$

$$P1 \cong \frac{1}{R_f C_f}$$


$$P2 \cong \frac{K_u}{\left(\frac{c_d}{C_f} + 1\right) t_{p0}} \quad \text{GBP}$$

$$P3 \cong \frac{1}{C_f r_o}$$



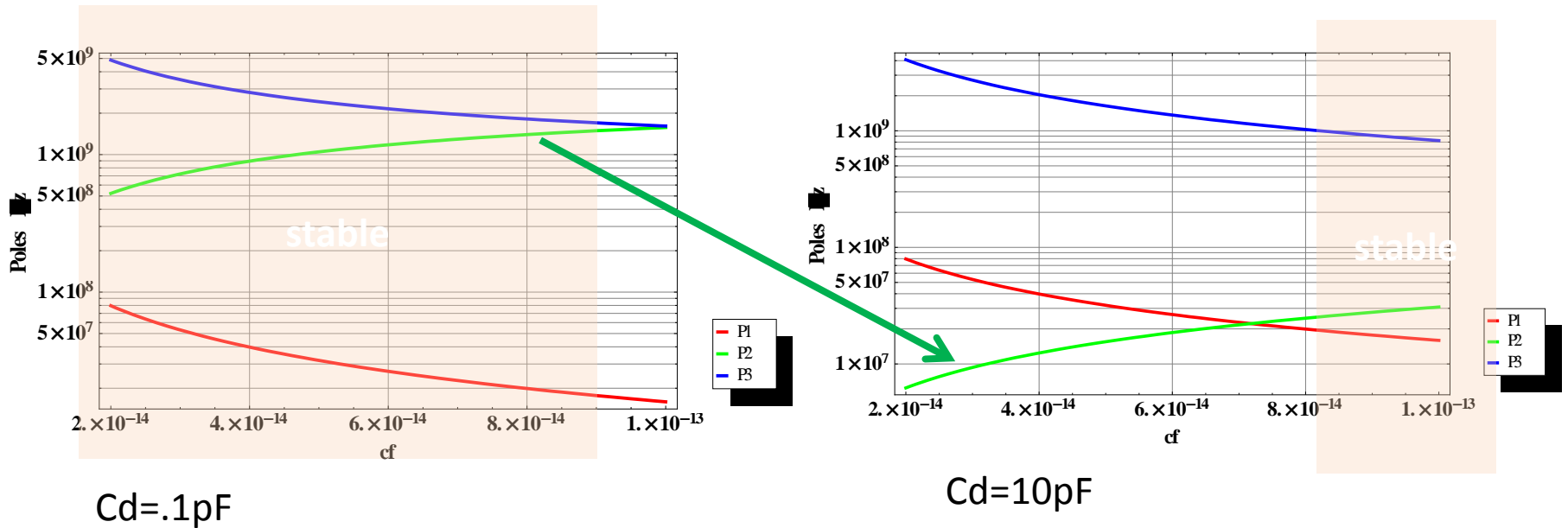
# CSA with finite impedance output buffer – close loop analysis

$$P1 \cong \frac{1}{R_f C_f} \quad P2 \cong \frac{GBP}{\left(\frac{cd}{C_f} + 1\right)} \quad P3 \cong \frac{1}{C_f r_o}$$



$R_f = 100\text{k}$ ,  $t_{p0} = 50\text{ns}$ ,  $K_u = 60\text{dB}$  (GBP  $\sim 2\text{GHz}$ ),  $r_o = 2\text{k}$
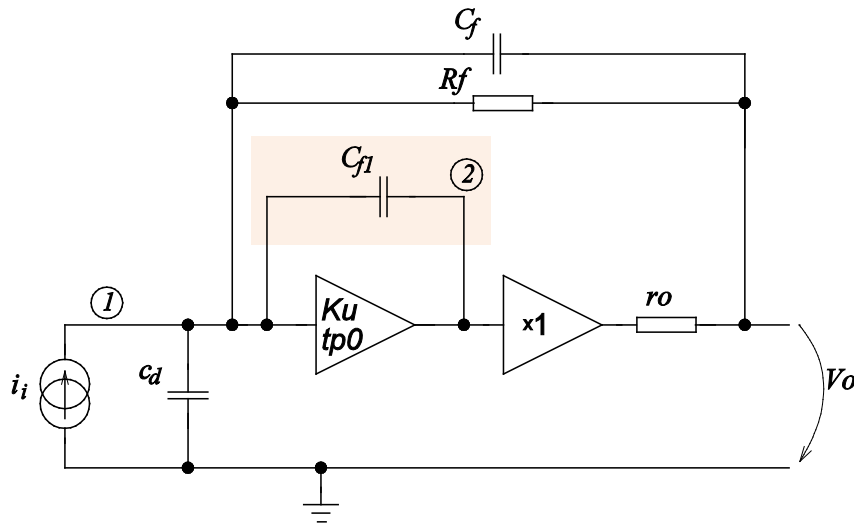
# CSA with finite impedance output buffer and compensation – close loop analysis



$$Z_{1,2} \cong -\frac{Cf1}{2 ro Cf (Cf1 + cl)} \mp \sqrt{\frac{GBP_{mod}}{ro Cf}}$$

Zeros in LFP and RHP asymmetric – visible undershoot

$$GBP = \frac{gm}{cl}, \quad GBP_{mod} = \frac{gm}{cl + Cf1}$$


$$P_1 \approx \frac{1}{Rf (Cf + Cf1)} \quad \rightarrow \text{unchanged (*)}$$

$$P_2 \approx \frac{GBP_{mod}}{\frac{cd}{Cf + Cf1} + \frac{Cf Cf1}{Cf + Cf1} GBP_{mod} ro} \quad \rightarrow \text{moved down with Cf1}$$


$$P_3 \sim \frac{1}{Cf ro} \quad \rightarrow \text{moved up (Cf now is a fraction of Cf')}$$

(\*) assumed effective value of  $Cf' = Cf + Cf1$
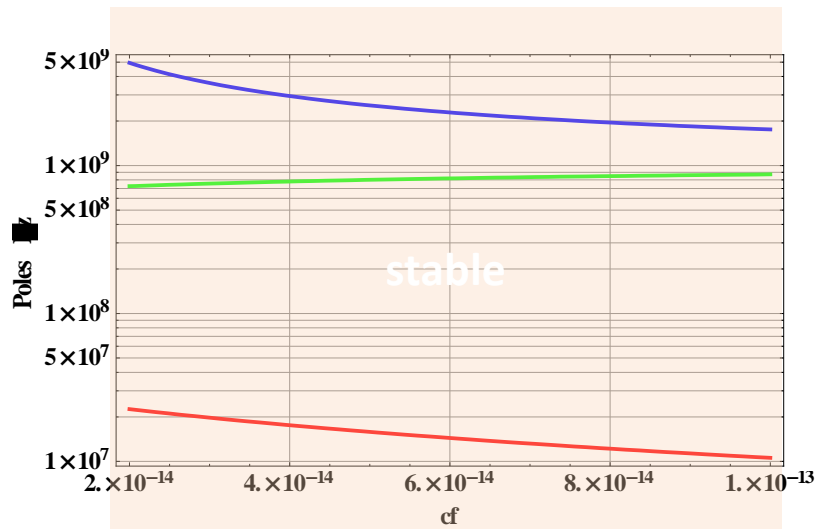
# CSA with finite impedance output buffer and compensation – close loop analysis



$C_d = 0.1 \text{ pF}$

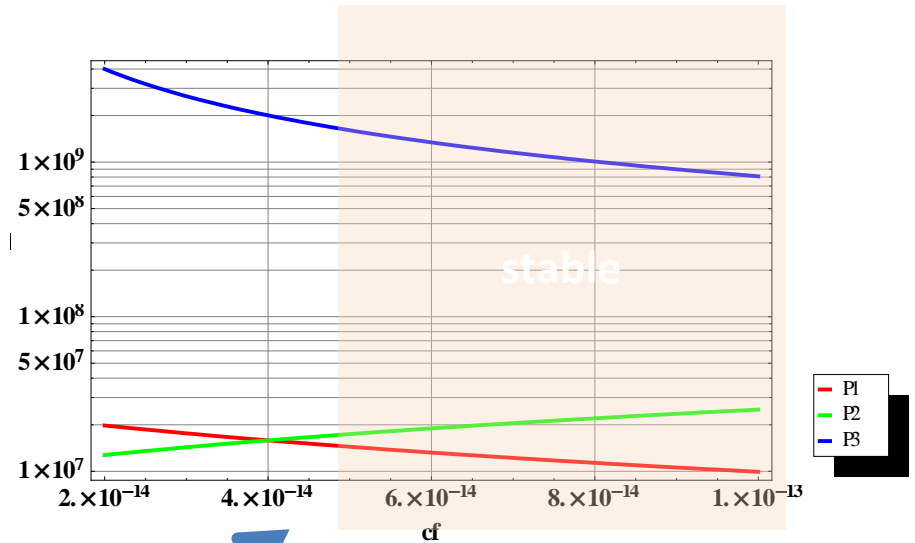


$C_d = 10 \text{ pF}$


Stable range of  $C_f$  starts lower due to the fact that effective feedback capacitance is now  $C_f + C_{f1}$

$R_f = 100 \text{ k}$ ,  $t_{p0} = 50 \text{ ns}$ ,  $K_u = 60 \text{ dB}$  (GBP  $\sim 2 \text{ GHz}$ ),  $r_o = 2 \text{ k}$ ,  $C_{f1} = 50 \text{ f}$
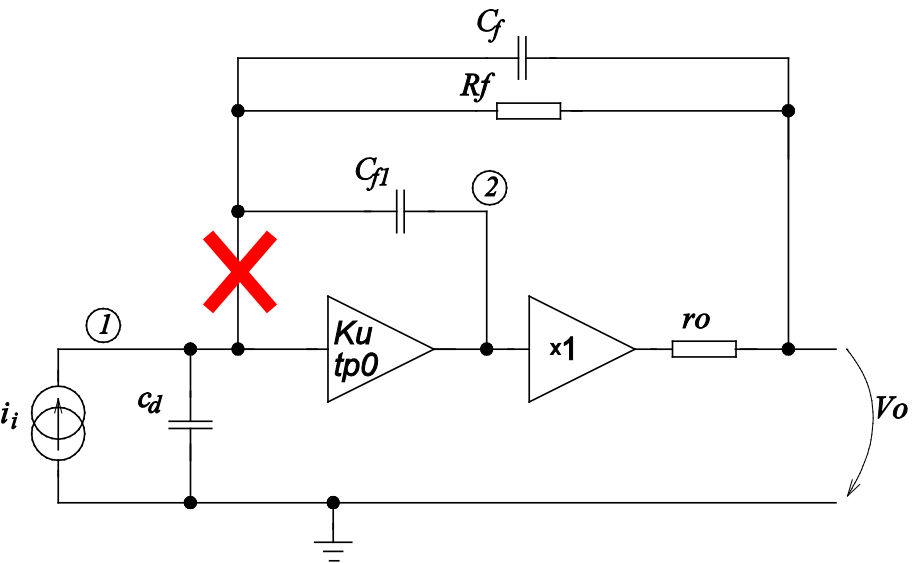
# CSA with finite impedance output buffer and compensation – open loop analysis: where to open the loop?




or

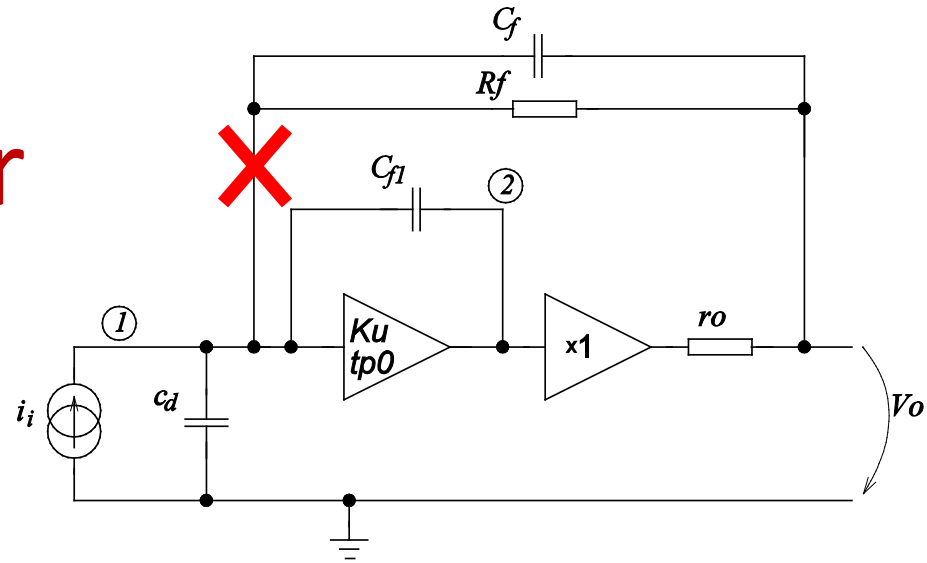

Criterion:


- loop fully open
- calculate amplifier and feedback transmittances ( $a$  and  $f$ ) and  $T=a/(1+af)$  and compare it to transmittance of circuit in close loop configuration
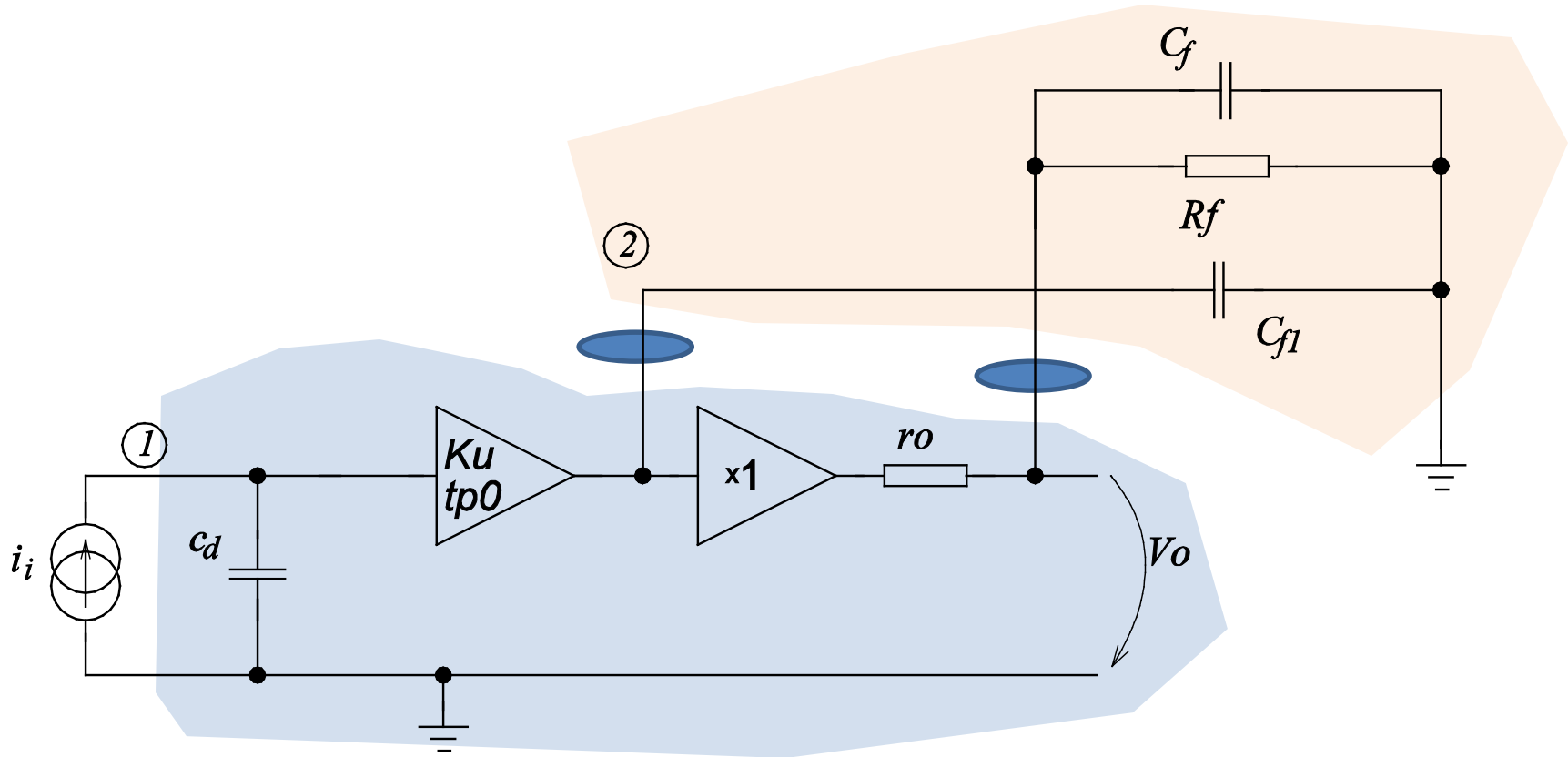
# CSA with finite impedance output buffer and compensation – open loop analysis: where to open the loop?




- ❑  $a$  and  $f$  not two-port devices  $\rightarrow$  not possible to calculate transmittances:  $a$ ,  $f$  and  $a \cdot f$
- ❑  $C_{f1}$  acts as internal compensation (acts on P2 only)  $\rightarrow$  after opening of  $C_{f1}$  the  $a$  changes significantly  $\rightarrow$  errors in estimation of PM up to 50%
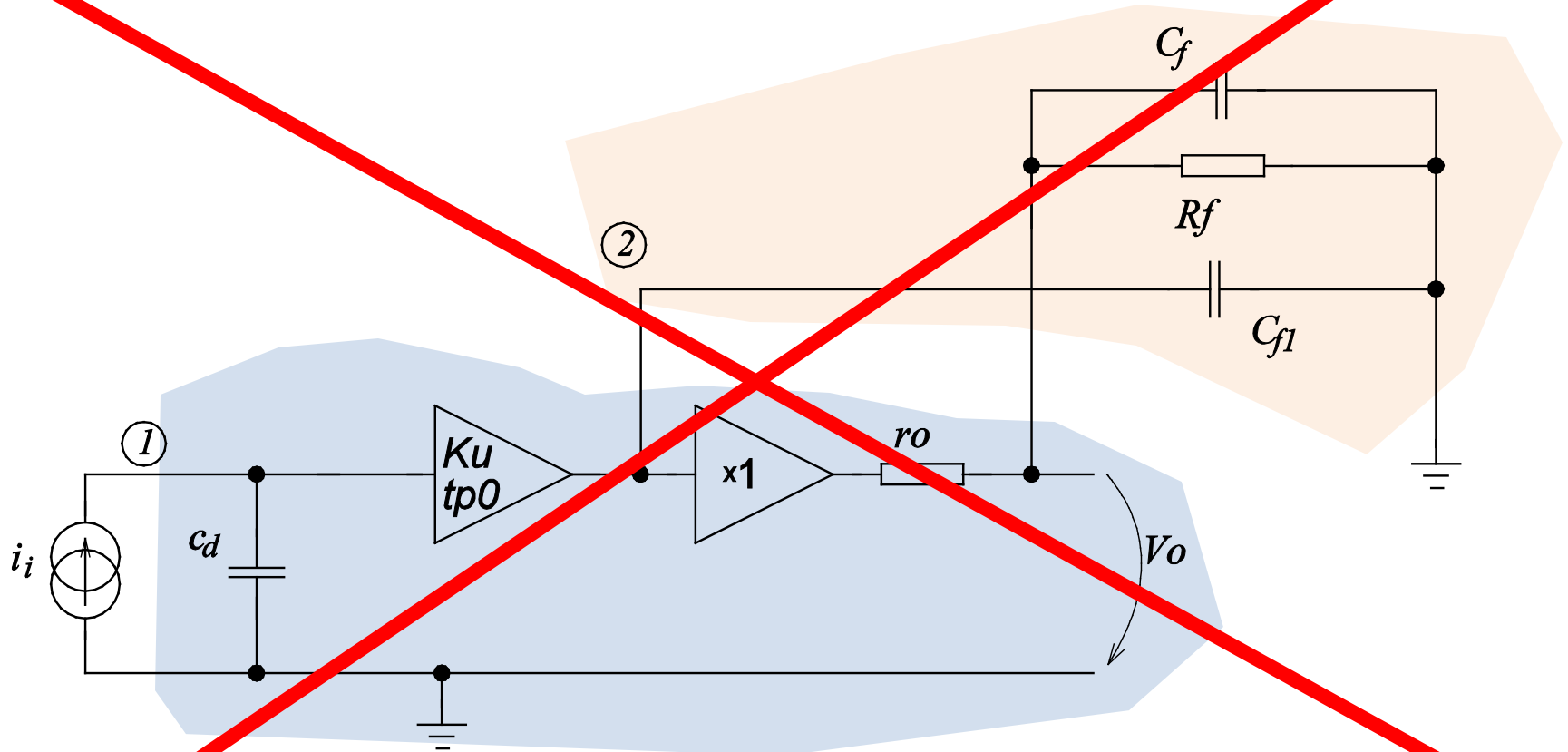
# CSA with finite impedance output buffer and compensation – open loop analysis: where to open the loop?



We should not open loop in this place

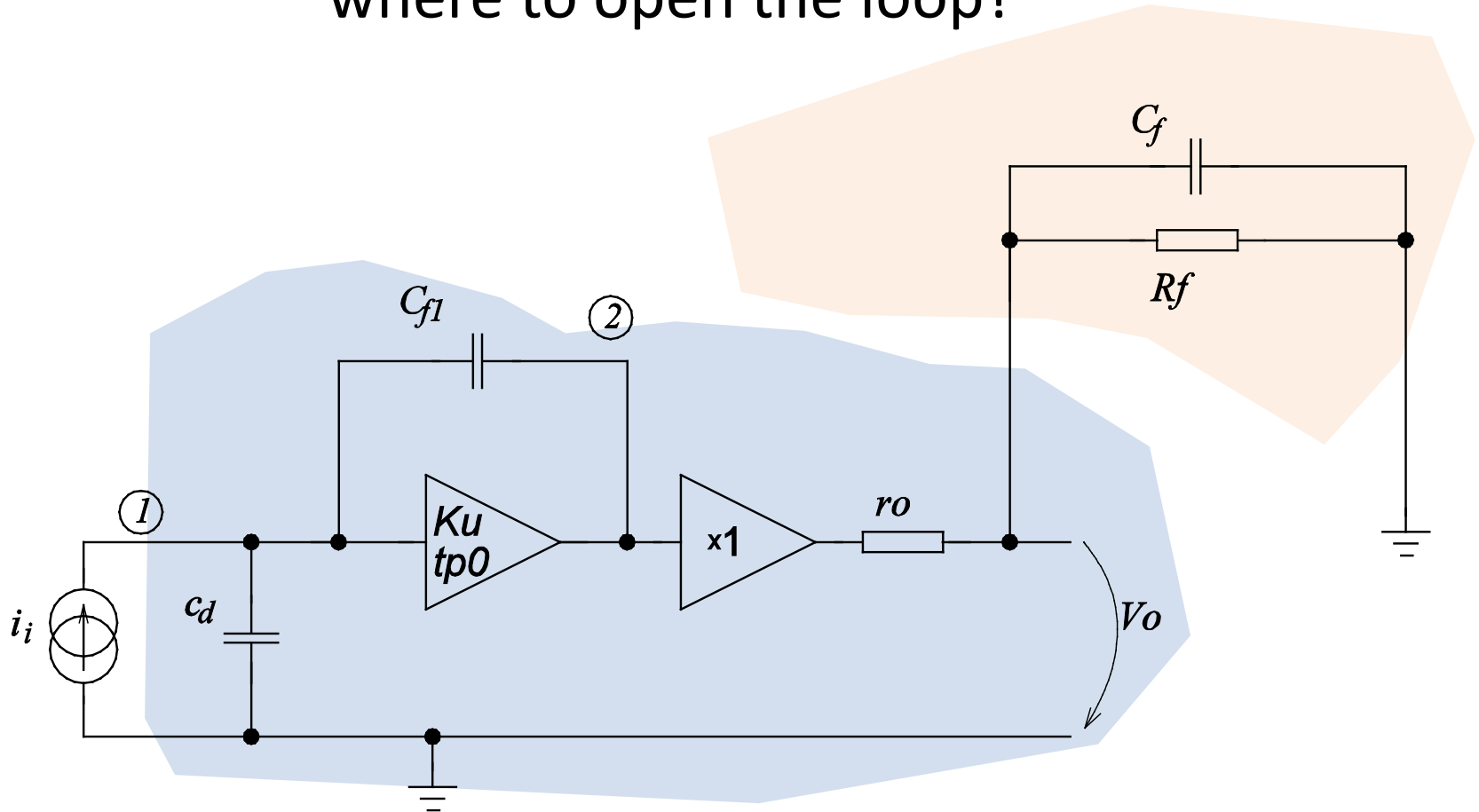
# CSA with finite impedance output buffer and compensation – open loop analysis: where to open the loop?



$a$  and  $f$  well defined, transmittance  $t=a/(1+af)$  the same as transmittance of circuit in close loop configuration → proper breakpoint for the loop
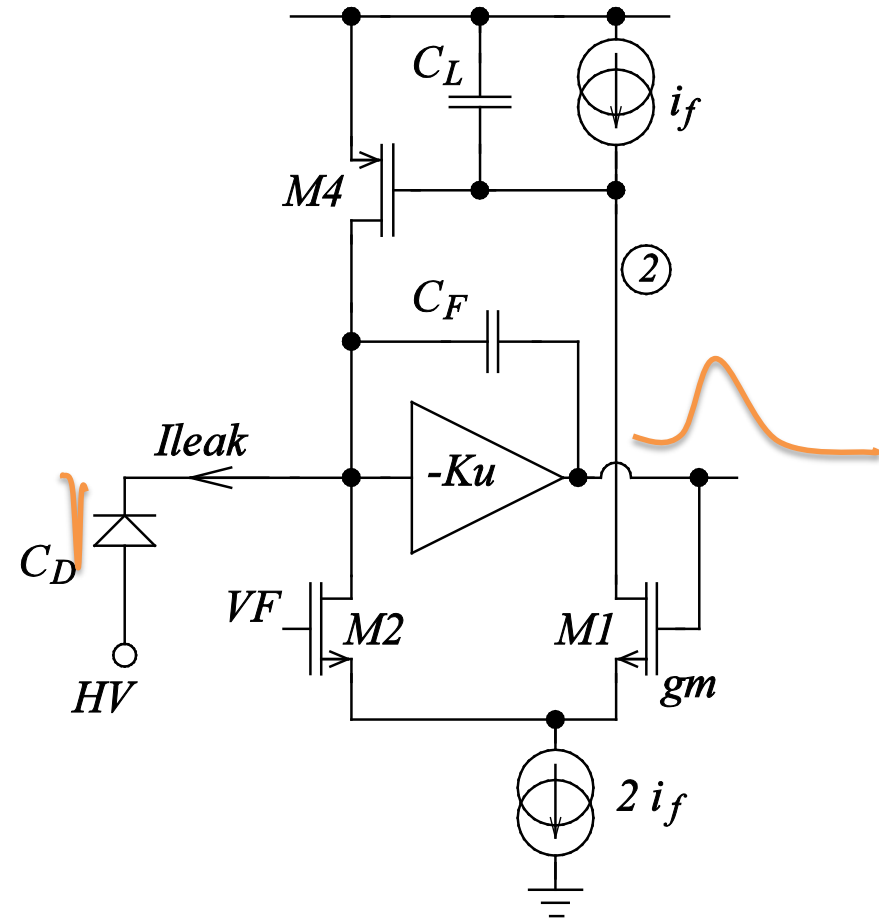
# Krummenacher feedback – dual branch active feedback example

- ❑ Fast feedback (signal discharge); M1 biased with  $i_f$  equivalent to feedback resistor of value  $1/g_m$  and feedback capacitor  $C_F$
- ❑ Slow feedback (leakage compensation); excess current from M1 generated by leakage attempting to flow from M2 causes lowering potential on N2 what in consequence increase the current through M4 (variation of voltage is filtered by  $C_F$ )
  - ❑ slow feedback is forcing detector leakage to flow through M4
  - ❑ VF control voltage is restored at the output






# Krummenacher feedback – close loop analysis

$$Z_1 = \frac{g_{ds1} + g_{ds3}}{C_l}$$

$$Z_2 = 2 \frac{g_{m12}}{C_5}$$

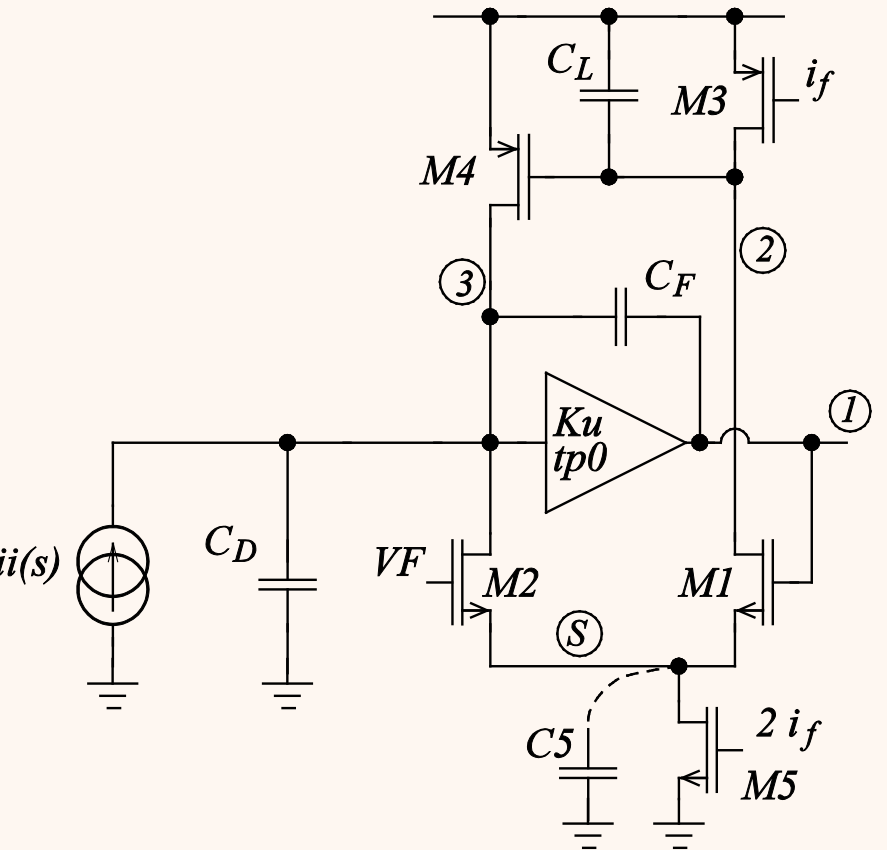

$$P_1 \approx \frac{2 g_{m4}}{C_l}$$

Very low frequency pole related to leakage compensation filtering (for  $g_{m1}=g_{m2}=g_{m12}$ )

$$P_2 \approx \frac{g_{m12}}{2 C_f}$$

Low frequency pole related to fast feedback:  $2/g_{m12} \sim R_f$

$$P_3 \approx 2 \frac{g_{m12}}{C_5}$$

Med. frequency pole related to parasitic on node S  $\rightarrow C_5$  should be minimized:  $C_5 \ll C_f$  !!


$$P_4 \approx \frac{C_f K_u}{C_d \tau_{P0}} = \frac{C_f}{C_d} GBP$$

High frequency pole related to dominant pole of amplifier  $\rightarrow$  GBP should be maximized

Good stability provided for well separated poles:  $P_1 \ll P_2 \ll P_3 \ll P_4$

Critical points: separation of  $P_2$  and  $P_3$  by minimizing  $C_5$  (or increase of  $C_f$ ), separation of  $P_1$  and  $P_2$  if  $g_{m4} \gg g_{m1}$  (high leakage) by proper value of  $C_l$  ( $C_l \gg C_f$ )
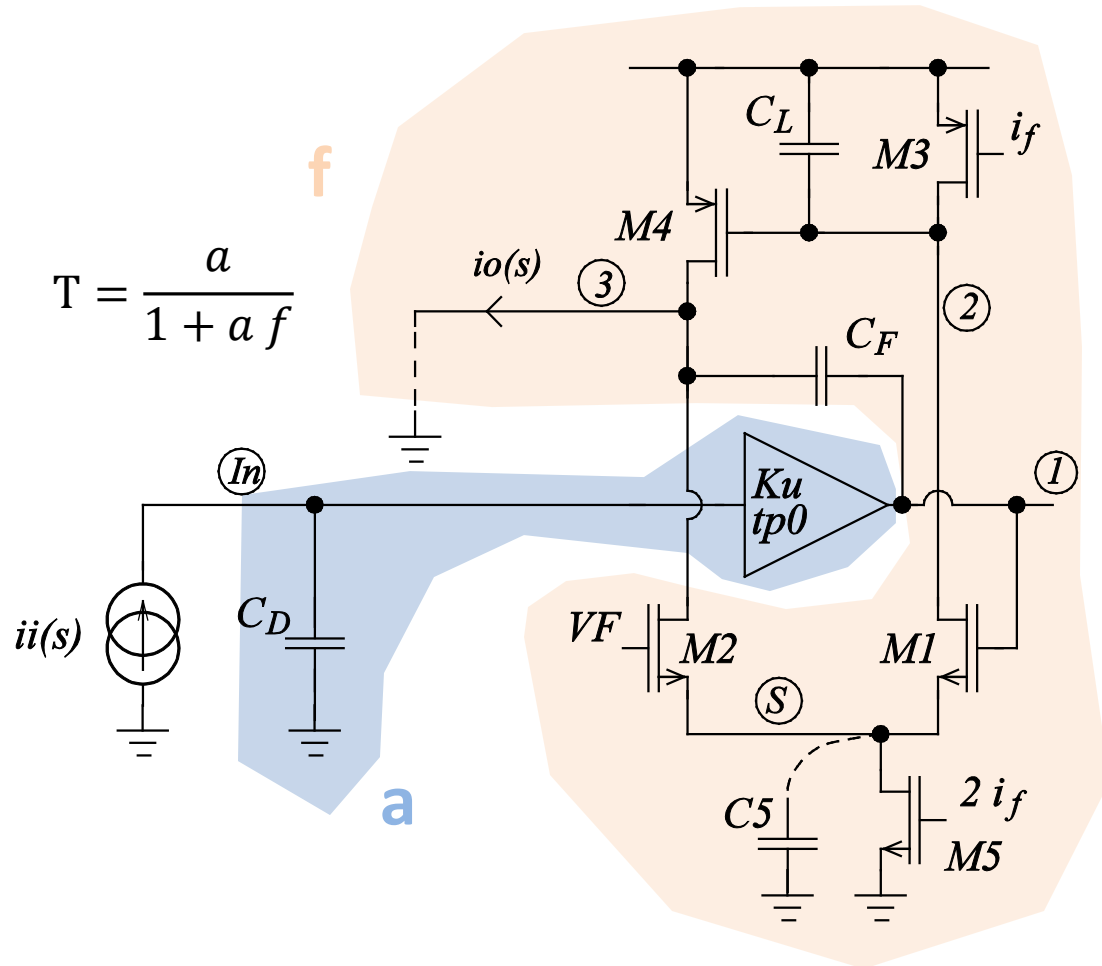
# Krummenacher feedback – open loop analysis



- ❑ Breaking loop at common point of two feedbacks at the input
- ❑ After calculation of  $a$ ,  $f$  and  $T = a / (1 + a f)$  the position of zeroes and poles are the same as in the close loop analysis →  $a$  and  $f$  are unaffected after opening the loop → classical or STB open loop gain analysis can be performed

# Krummenacher open loop: comparison of classical (no reverse loop gain) and STB approach

Poles and zeroes of the loop gain (a f):

$$gm1 = gm2 = gm12$$



$$Z_1 = \frac{gm4}{Cl} \quad Z_2 = \frac{gm12}{2 Cf} \quad Z_3 = 2 \frac{gm12}{C5}$$

$$P_1 \approx 0 \text{ or } P_1 \approx P_2 \text{ (STB)} \quad P_2 \approx \frac{gds1 + 2 gds3}{2 Cl} \quad P_3 \approx 2 \frac{gm12}{C5} \quad P_4 \approx \frac{1}{\tau_{P0}}$$



Differences only for low frequencies → PM measurement not affected
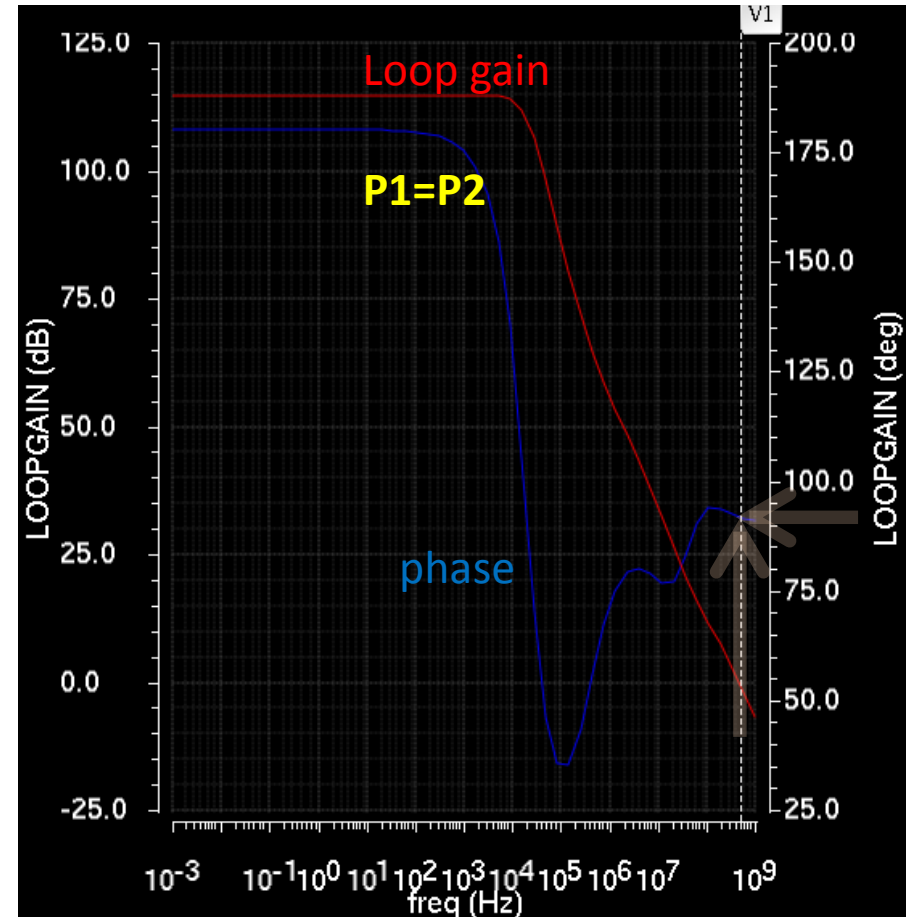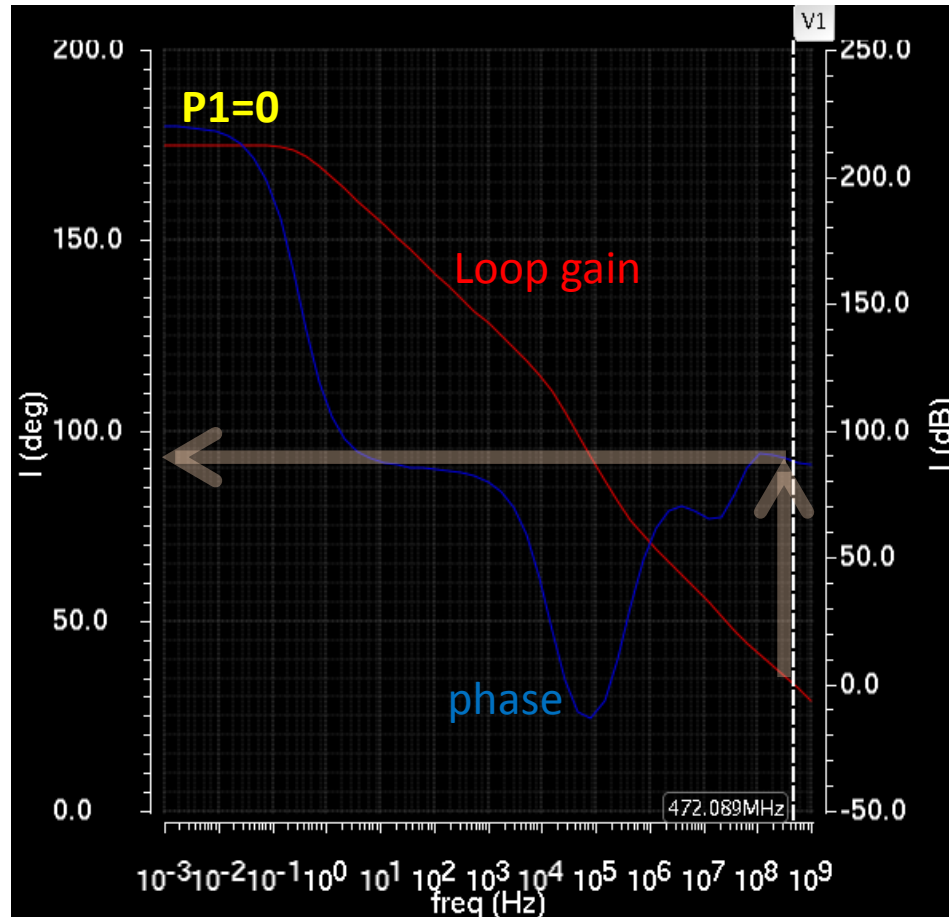
# Krummenacher open loop: AC open loop vs. STB

65nm design for CMS CTPix ASIC, simplified circuit (all transistors and amplifier built with VCCS)



# CTPix preamp: STB and PZ analysis

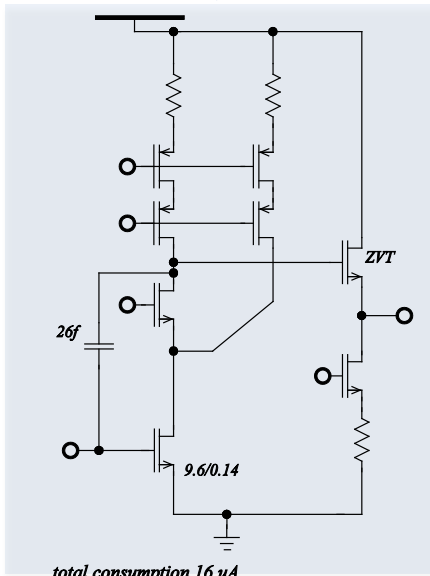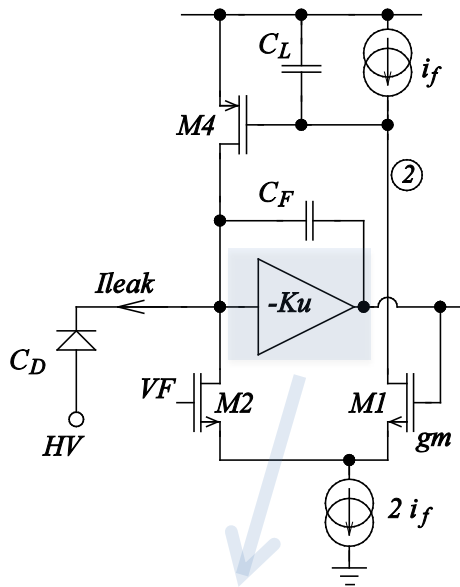

total consumption 16 uA

## Input stage:

Designed for long pixels (1500x100um),  
cd=280fF

Telescopic cascode with degenerated PMOS  
sources

Input transistor: NMOS 9.6um/140nm

$C_f=6.4\text{fF}$ ,  $C_{f1}=26\text{fF}$


Consumption: 16uA (12uA input transistor)

Open loop gain: ~54dB

GBP: 2GHz (for compensated cascode)

Krummenacher feedback (leakage  
compensation for n+ on p- detectors,  
 $I_f=80\text{nA}$ )

# CTPix preamp: STB analysis

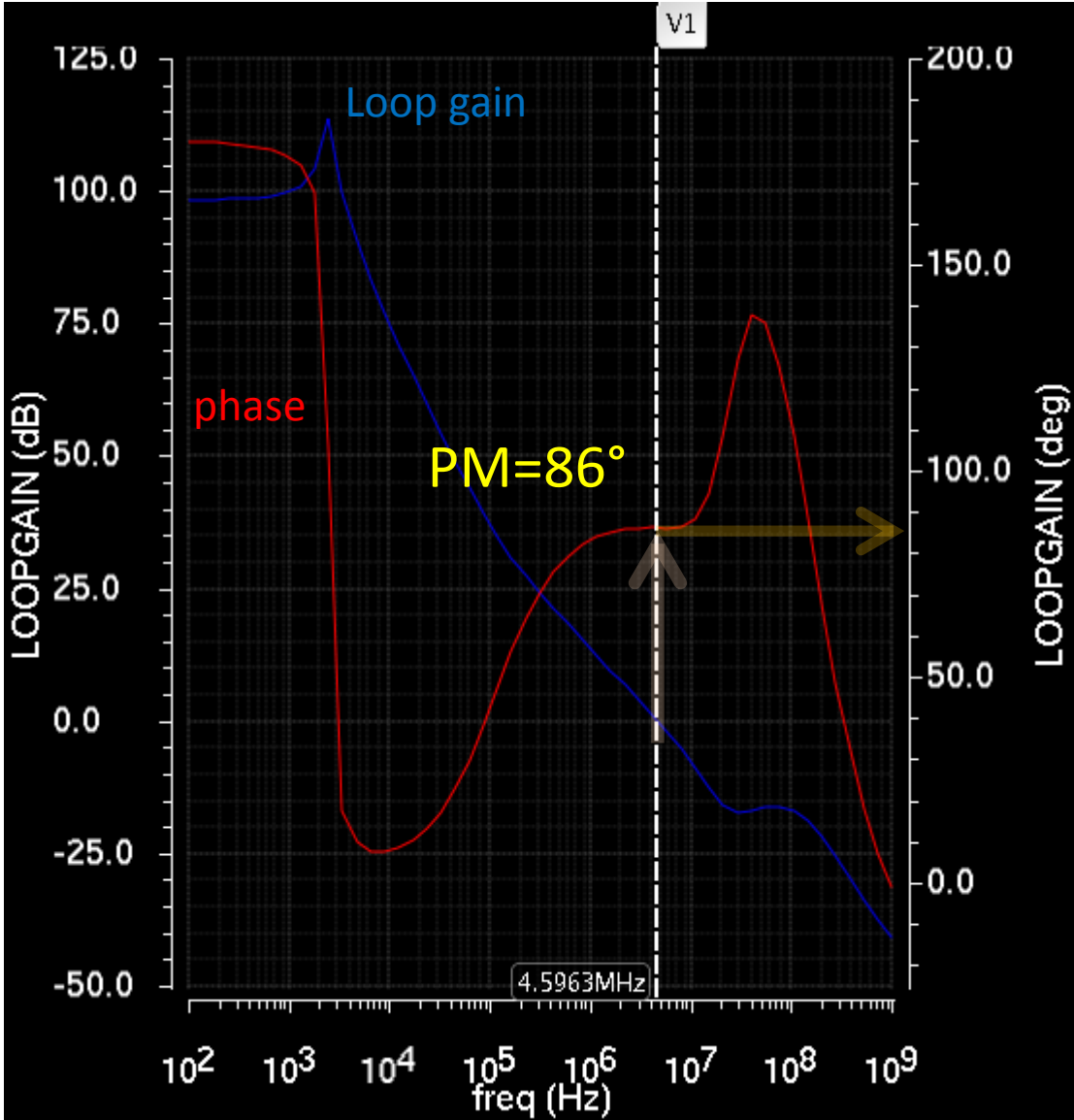

# CTPix preamp: PZ analysis

Dominant poles → reals  
Three high freq. complex pairs at 150MHz, 200MHz and 2GHz with  $Q < 0.6$

Poles (Hz)			
	Real	Imaginary	Qfactor
Pole_1	-1.140e+05	0.000e+00	5.000e-01
Pole_2	-5.375e+06	0.000e+00	5.000e-01
Pole_3	-1.493e+07	0.000e+00	5.000e-01
Pole_4	-4.268e+07	0.000e+00	5.000e-01
Pole_5	-4.877e+07	0.000e+00	5.000e-01
Pole_6	-1.219e+08	0.000e+00	5.000e-01
Pole_7	-1.329e+08	0.000e+00	5.000e-01
Pole_8	-1.436e+08	8.149e+07	5.749e-01
Pole_9	-1.436e+08	-8.149e+07	5.749e-01
Pole_10	-2.088e+08	2.734e+06	5.000e-01
Pole_11	-2.088e+08	-2.734e+06	5.000e-01
Pole_12	-2.882e+08	0.000e+00	5.000e-01
Pole_13	-3.124e+08	0.000e+00	5.000e-01
Pole_14	-3.124e+08	0.000e+00	5.000e-01
Pole_15	-3.918e+08	0.000e+00	5.000e-01
Pole_16	-5.041e+08	0.000e+00	5.000e-01
Pole_17	-5.689e+08	0.000e+00	5.000e-01
Pole_18	-6.013e+08	0.000e+00	5.000e-01
Pole_19	-8.141e+08	0.000e+00	5.000e-01
Pole_20	-1.012e+09	0.000e+00	5.000e-01
Pole_21	-1.206e+09	0.000e+00	5.000e-01
Pole_22	-1.415e+09	0.000e+00	5.000e-01
Pole_23	-1.665e+09	0.000e+00	5.000e-01
Pole_24	-2.008e+09	5.199e+08	5.165e-01
Pole_25	-2.008e+09	-5.199e+08	5.165e-01
Pole_26	-2.293e+09	0.000e+00	5.000e-01
Pole_27	-4.331e+09	0.000e+00	5.000e-01
Pole_28	-4.331e+09	0.000e+00	5.000e-01
Pole_29	-9.056e+11	0.000e+00	5.000e-01
Pole_30	-9.690e+11	0.000e+00	5.000e-01

Zeros (Hz)			
	Real	Imaginary	Qfactor
Zero_1	-3.243e+02	0.000e+00	5.000e-01
Zero_2	-1.912e+07	0.000e+00	5.000e-01
Zero_3	-4.208e+07	0.000e+00	5.000e-01
Zero_4	-5.876e+07	0.000e+00	5.000e-01
Zero_5	-1.330e+08	0.000e+00	5.000e-01
Zero_6	-1.975e+08	0.000e+00	5.000e-01
Zero_7	-2.086e+08	0.000e+00	5.000e-01
Zero_8	-3.876e+08	0.000e+00	5.000e-01
Zero_9	-5.043e+08	0.000e+00	5.000e-01
Zero_10	-5.656e+08	0.000e+00	5.000e-01
Zero_11	-6.002e+08	0.000e+00	5.000e-01
Zero_12	7.045e+08	0.000e+00	-5.000e-01
Zero_13	-8.124e+08	0.000e+00	5.000e-01
Zero_14	-1.012e+09	0.000e+00	5.000e-01

# Summary

- ❑ Open loop gain analysis (classical or STB) and close loop analysis should be both used for establish the stability margins of the design
- ❑ Time response (asymptotic or oscillatory) defined by position of poles and zeroes not phase margin → keep in mind ambiguities between quality of the poles and phase margin!
- ❑ Stable design should have all poles on LHP with quality below 0.7 and phase margin above 70°
  - ❑ lower pole quality and higher phase margin are very welcome!
  - ❑ higher quality poles at frequencies  $\sim f_t$  and above probably acceptable (if inevitable)
- ❑ Open loop gain analysis and STB check only the feedback under test (do not check feedbacks related to internal amplifier architecture like regulated cascode, more exact transistor models etc.) → PZ analysis has big advantage from this viewpoint
- ❑ We discussed only single ended feedbacks → differential feedbacks possible to analyse in STB however the differential iprobe does not exist in analogLib → PZ analysis more straightforward for differential circuits