

QIE10-11 Readout Chip Development

T. Zimmerman

Fermi National Accelerator Laboratory

FEE 2014


Argonne National Laboratory

May 20, 2014


Overview of multi-decade QIE development

- The QIE [Charge (**Q**) Integrator and **E**ncoder] is a custom ASIC designed to **digitize wide dynamic range charge signals** from photo-detectors (PMTs, SiPMs), with approximately constant resolution and **no deadtime**
- A short history:
 - 1989: Originally conceived by Bill Foster for **SDC @ SSC**
 - 1995: 1st fully-functional chip designed by Tom Zimmerman for the **KTeV experiment @ FNAL (QIE5)**
 - 2 μm Orbit “Bi-CMOS”, 3000 ch.
 - 1996: Front-end for calorimeters of **CDF @ FNAL (QIE6)**
 - 2 μm Orbit “Bi-CMOS”, 10,000 ch.
 - 2002: Front-end for **MINOS Near Detector @ FNAL (QIE7)**
 - 2 μm Orbit “Bi-CMOS”, 10,000 ch.
 - 2003: Front-end for **CMS HCAL @ CERN (QIE8)**
 - 0.8 μm AMS BiCMOS, 10,000 ch. .
 - 2004: Front-end for **BTEV @ FNAL (cancelled) (QIE9)**
 - 0.8 μm AMS BiCMOS
 - 2013-14: Front-end for **CMS forward calorimeter (QIE10)**
Barrel and endcap calorimeters **(QIE11)**
 - 0.35 μm AMS SiGe BiCMOS

SSC

 

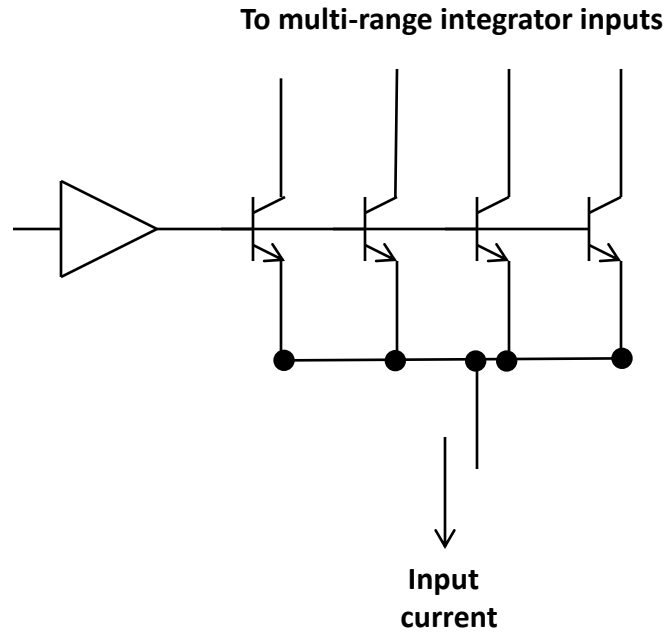All QIE chips are based on the NPN bipolar current splitter concept:




The current split ratios are determined by NPN emitter area ratios (using multiples of a unit transistor).

Split ratios remain constant over a big dynamic range, even in the presence of mismatch (not true for MOS)!

Therefore, all QIE chips are realized using a BiCMOS process.

Overview of QIE10


- The newest design (**QIE10**) features:
 - Dead-timeless operation @ 40 MHz, using 4-phase operation (same as all previous QIEs)
 - High dynamic range: 3 fC – 330 pC (~17 bits). 6-bit mantissa, 4 Ranges → 256 codes (10X the range of QIE8)
 - Logarithmic response - ~1% measurement across dynamic range
 - Controlled impedance input over full dynamic range (5 meter input cable from PMT)
 - 6 bit TDC (0.5 ns) with programmable threshold (first QIE with a TDC)
 - Serial download of programmable parameters (new feature)
 - True LVDS outputs
 - On-chip test charge injection
 - Low power: 320 mW
 - +5V @ 40 mA analog
 - +3.3V @ 35 mA digital
 - 350 nm AMS SiGe process (first QIE to use this process)

 

Overview of QIE11

- Similar to QIE10 with the following differences:
 - Intended for SiPM readout
 - Programmable input current shunt to achieve scaling factors of:
 - x1, x1.5, x2, x3, x4, x6, x8, x12 (in order to accommodate higher than anticipated SiPM gain)
 - Lowest possible input impedance (not constant, impedance naturally goes down as signal magnitude goes up)

- How the QIE10 works:
 - ★ Receives charge (current) from PMT Anode
 - ★ “Splits” current into four weighted **Ranges**
 - ★ Gates and integrates current fractions onto separate capacitors
 - ★ Based on the signal magnitude, 1 of the 4 Ranges is selected to be digitized
 - Ranges are logarithmically weighted (X8)
 - ★ Digitizes the analog voltage from the selected Range
 - 6-bit FADC with *logarithmic* response (bin width 1, 2, 4, 8) → “Mantissa”
 - ★ Outputs 2-bit code for the Range digitized (0 - 3) → “Exponent”
- ⇒ **Produces floating-point output codes**
- ⇒ **Response is approximately logarithmic...**

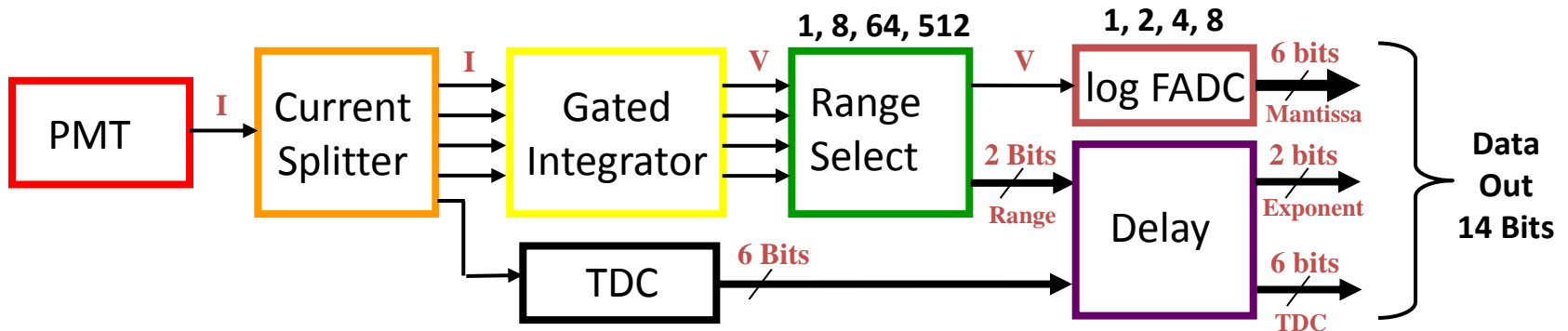


In reality, 4 sets of integrators (4 phases A-D) are used to achieve dead-timeless operation:

- Operations are pipelined at 40 MHz using 4-phase circuits ⇒ *Produces a code representing the current integrated in each and every 25 ns period and never stops*
- Data includes 2-bit **CapID** to indicate phase

4 pipelined phases:

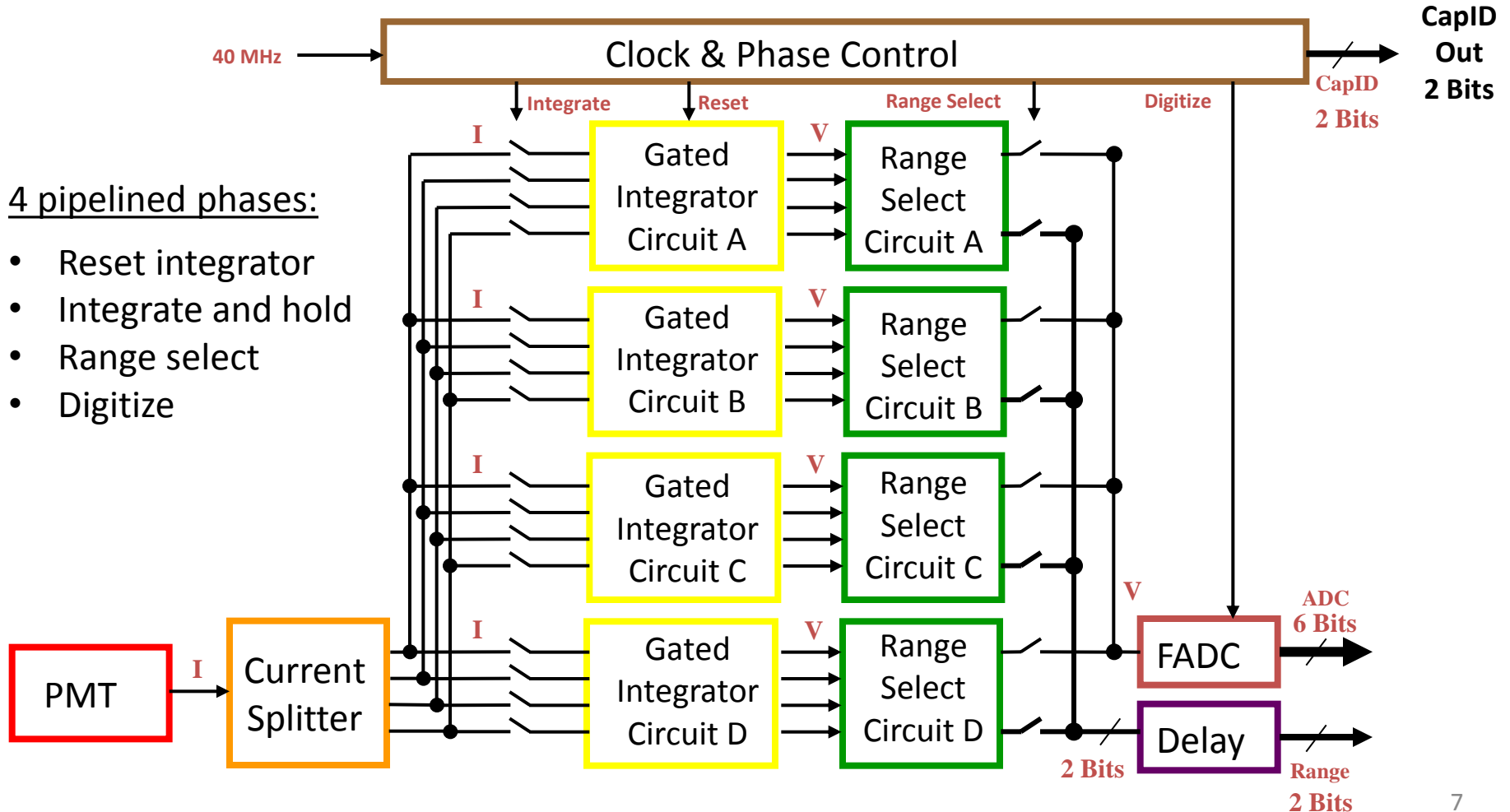- Reset integrator
- Integrate and hold
- Range select
- Digitize




- **Splitter/integrator implementation:**



- 24 identical NPN transistors, arranged in groups: x16, x4, x2, x1, x1
- Integrator capacitor ratios: 1, 2, 8, 32
- Results in 4 integration ranges, each scaled by X8
- Selected integrator feeds a 4-section ADC with binary weighted bin widths
- Results in effectively 16 ranges, scaled by x2

Simplified diagram:

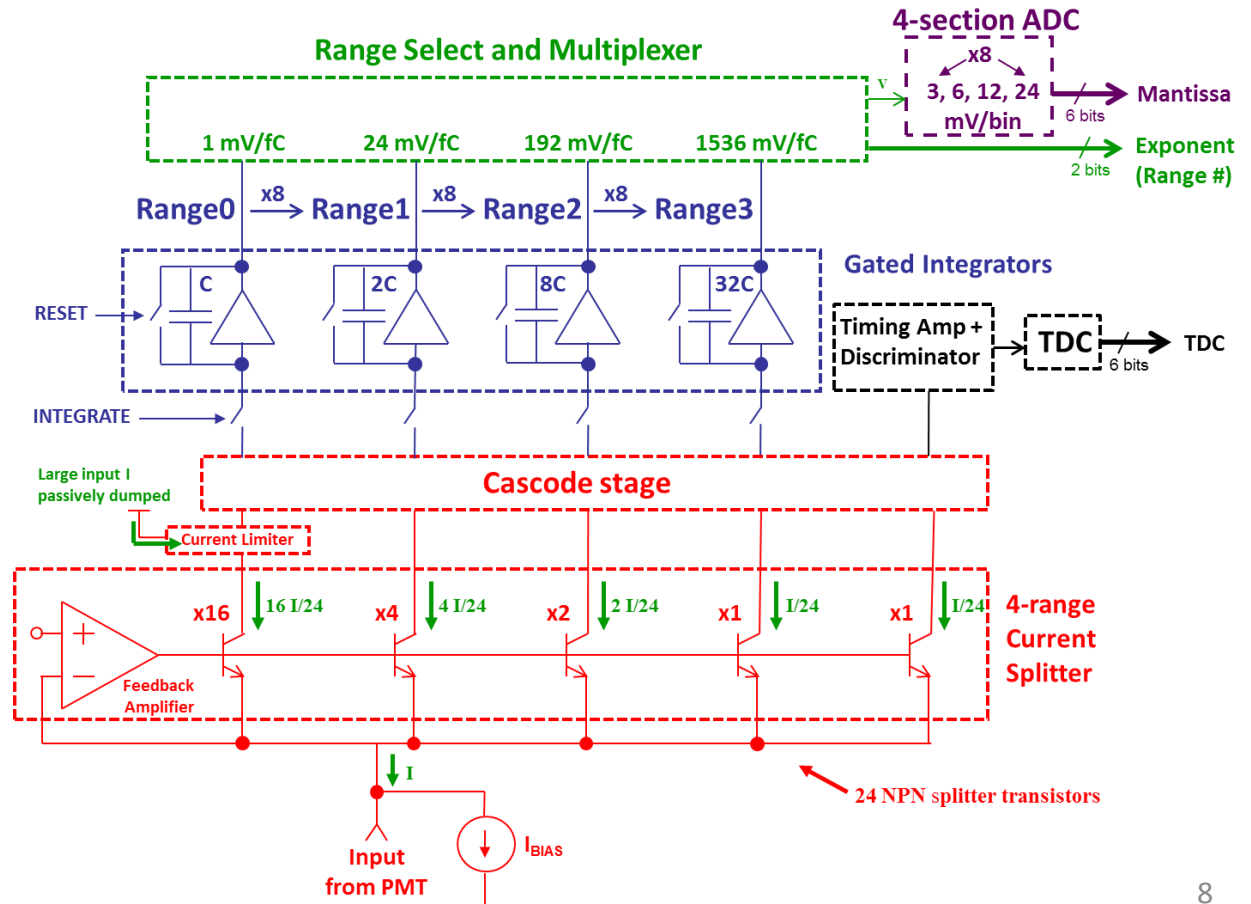- Only 1 of 4 integration phases shown
- Shown as single-ended implementation, actually done in pseudo-differential form (shown later)



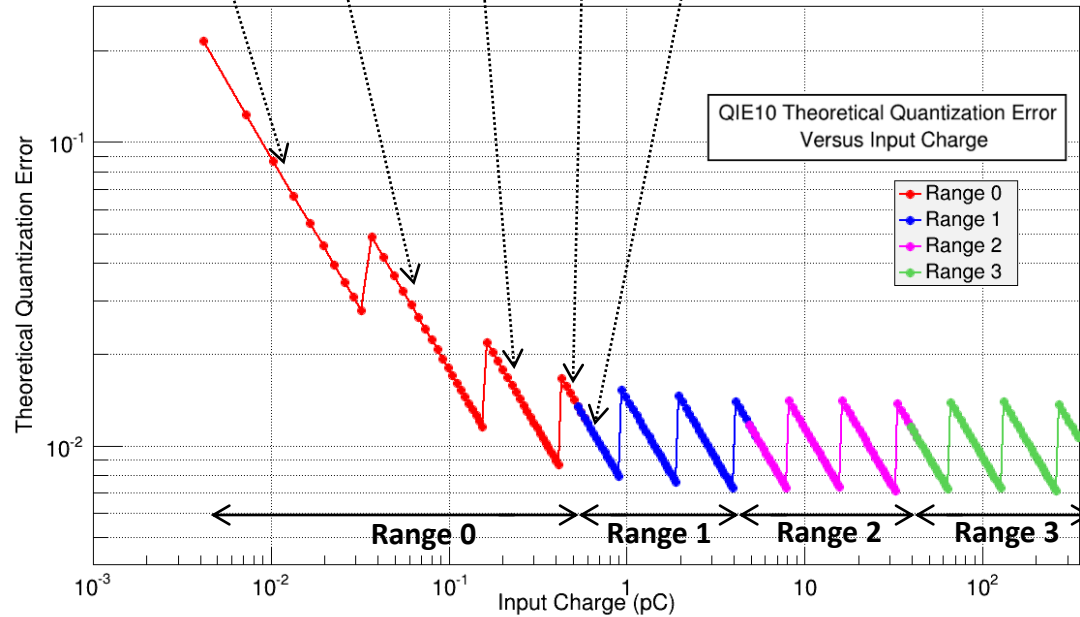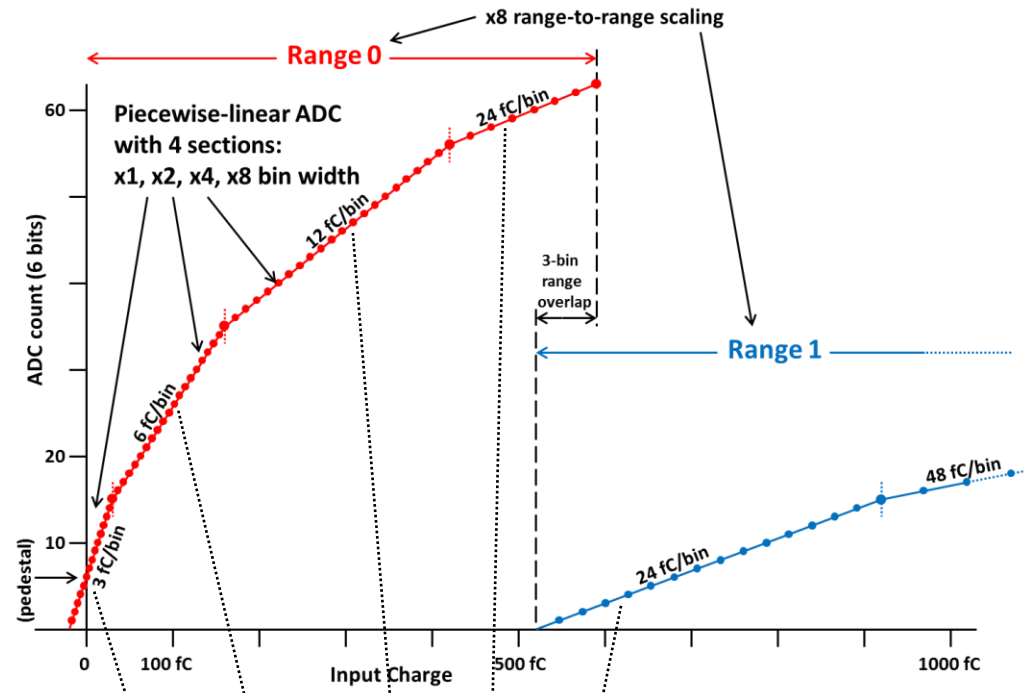
The combination of x8 range scaling and a 4-section piecewise-linear ADC give "16-range" floating-point response:



Controlled impedance input amplifier/splitter design challenges

- Constant split ratio over wide dynamic range: NPN splitter required (not NMOS)
- Small DC input bias current (< 20 uA)
- Constant impedance input for 0 – 60 mA input current: *requires novel feedback amp approach*


Basic approach:

 

Stabilize the open-loop gain:
replace R with I source and Q₃



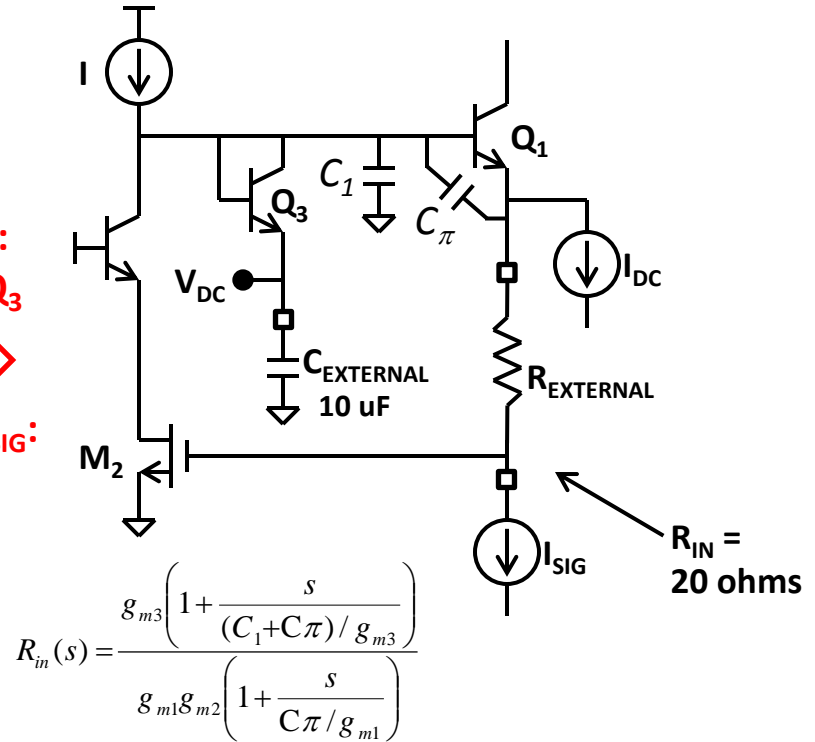Both g_{m1} and g_{m3} go up with I_{SIG} :
 R_{IN} remains constant!



Arrange the value of C1 so the pole cancels the zero:
resistive input to very high frequency!

For the biggest signals (>> 1mA), M₂ is debiased, and
Q₁ functions as an open-loop common base amp,
with input resistance set by R_{EXTERNAL}.

Tune V_{DC} and R_{EXTERNAL} for R_{IN} = 20 ohms. 10

Small signal analysis

$$R_{in}(s) = \frac{1 + \frac{s}{R(C_1 + C_\pi)}}{g_{m1} g_{m2} R \left(1 + \frac{s}{C_\pi / g_{m1}} \right)}$$


But $I_{SIG} \gg I_{DC}$ so
NOT small signal!

g_{m1} goes up with I_{SIG} , so open-loop
gain and R_{IN} changes with I_{SIG} !


A crucial QIE strategy: Implement all analog circuits in pseudo-differential form: 2 “identical” inputs -- signal source connects to the *SIG* input, and the *REF* input floats

RESULT: *excellent stability and common-mode rejection*

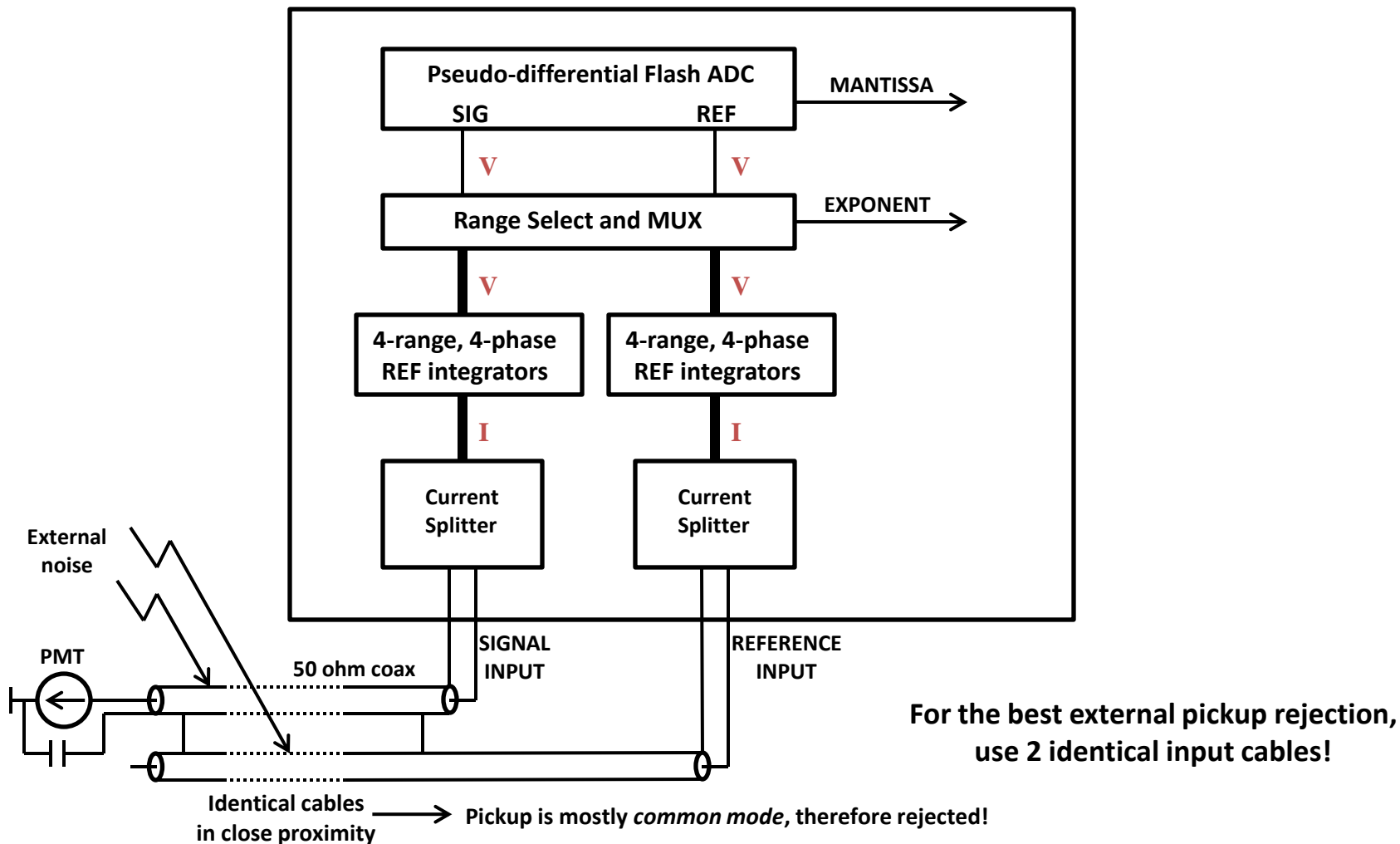
(relatively immune to shifts in bias levels, supply voltage, clock frequency, temperature, etc.)




Pseudo-differential TDC implementation

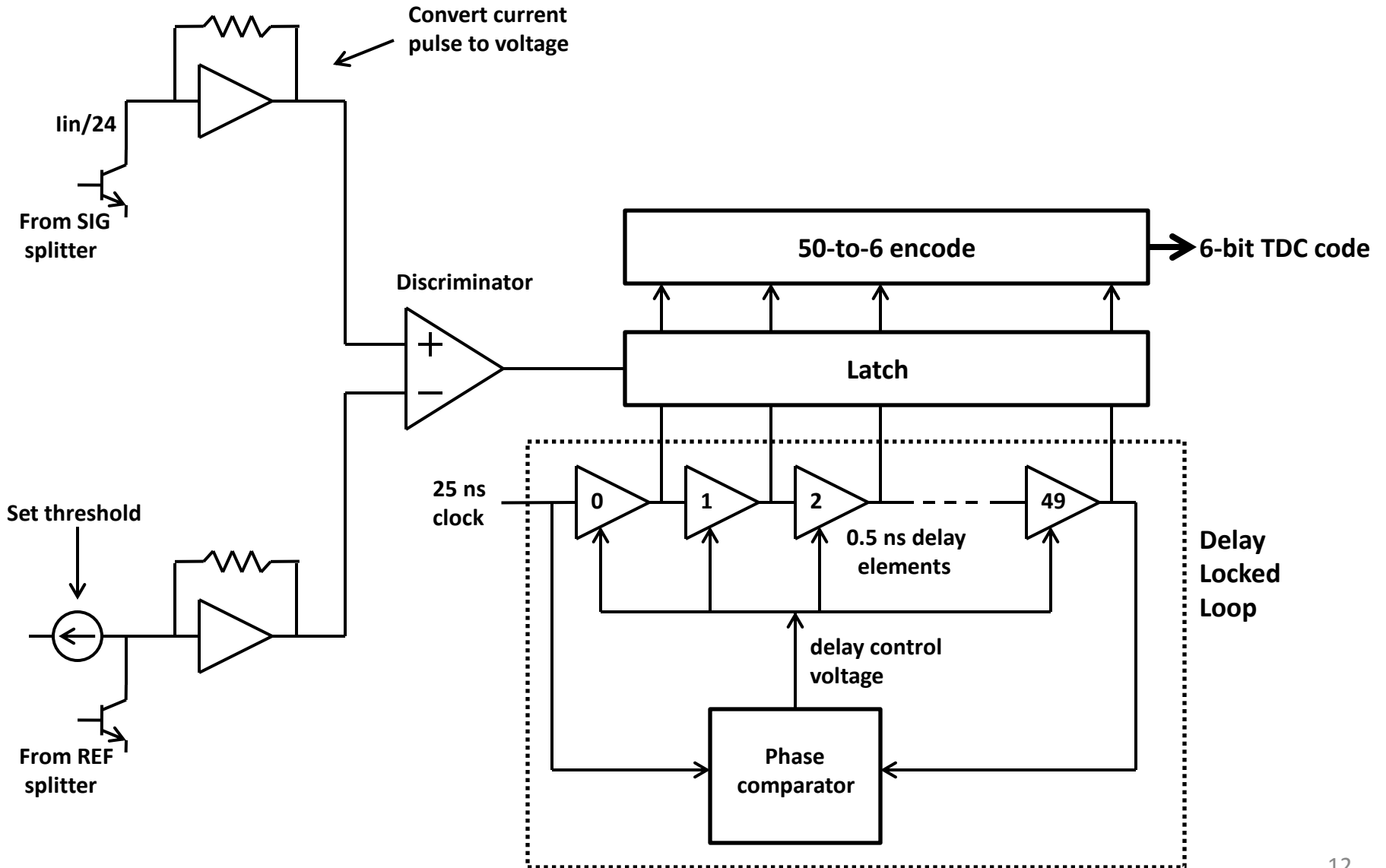

 
Pseudo-differential Flash ADC implementation



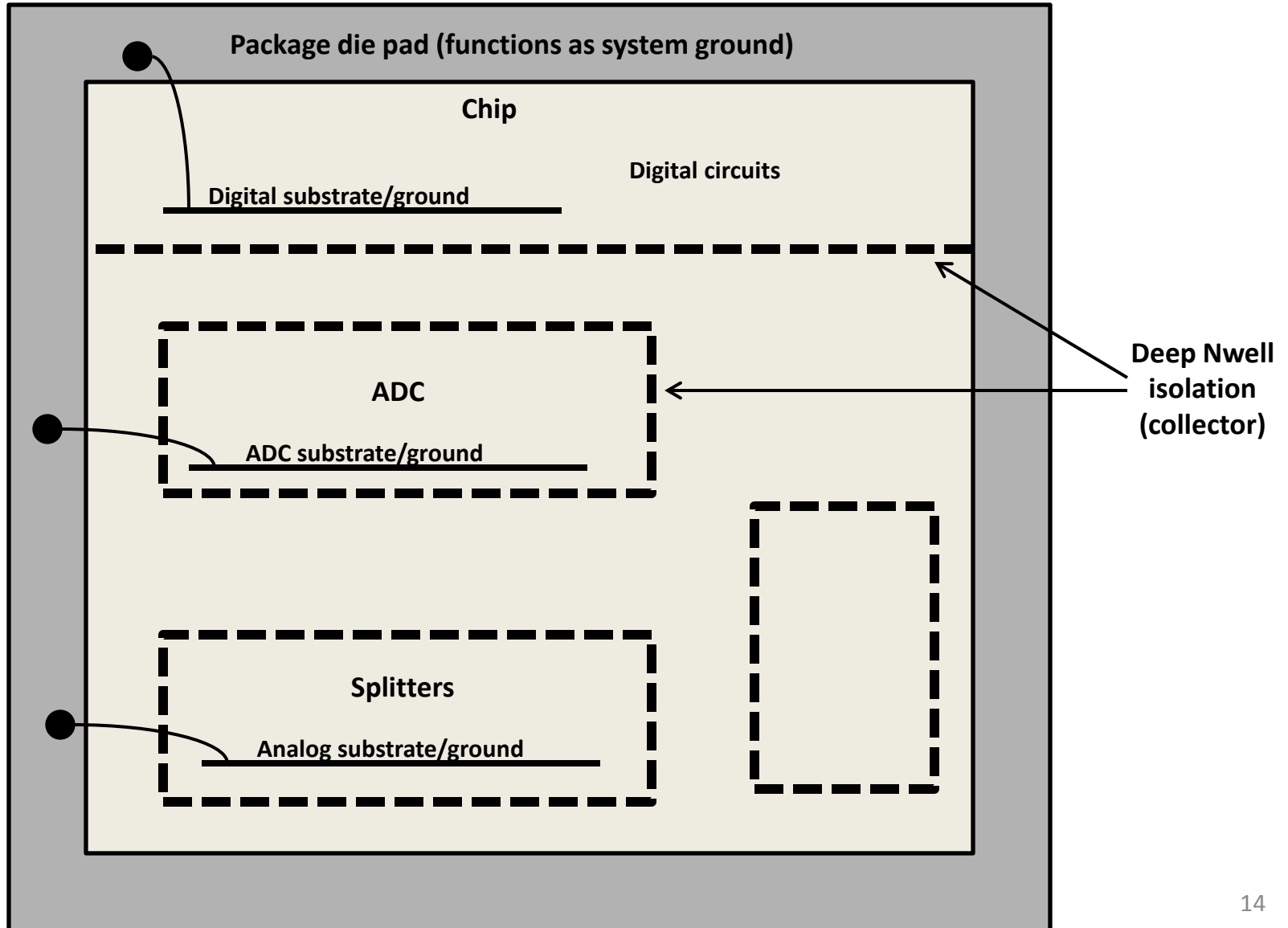Another crucial QIE strategy: Create isolated substrate areas on the same chip. Reference them all to the die pad (“system ground”). This greatly reduces digital-to-analog coupling!




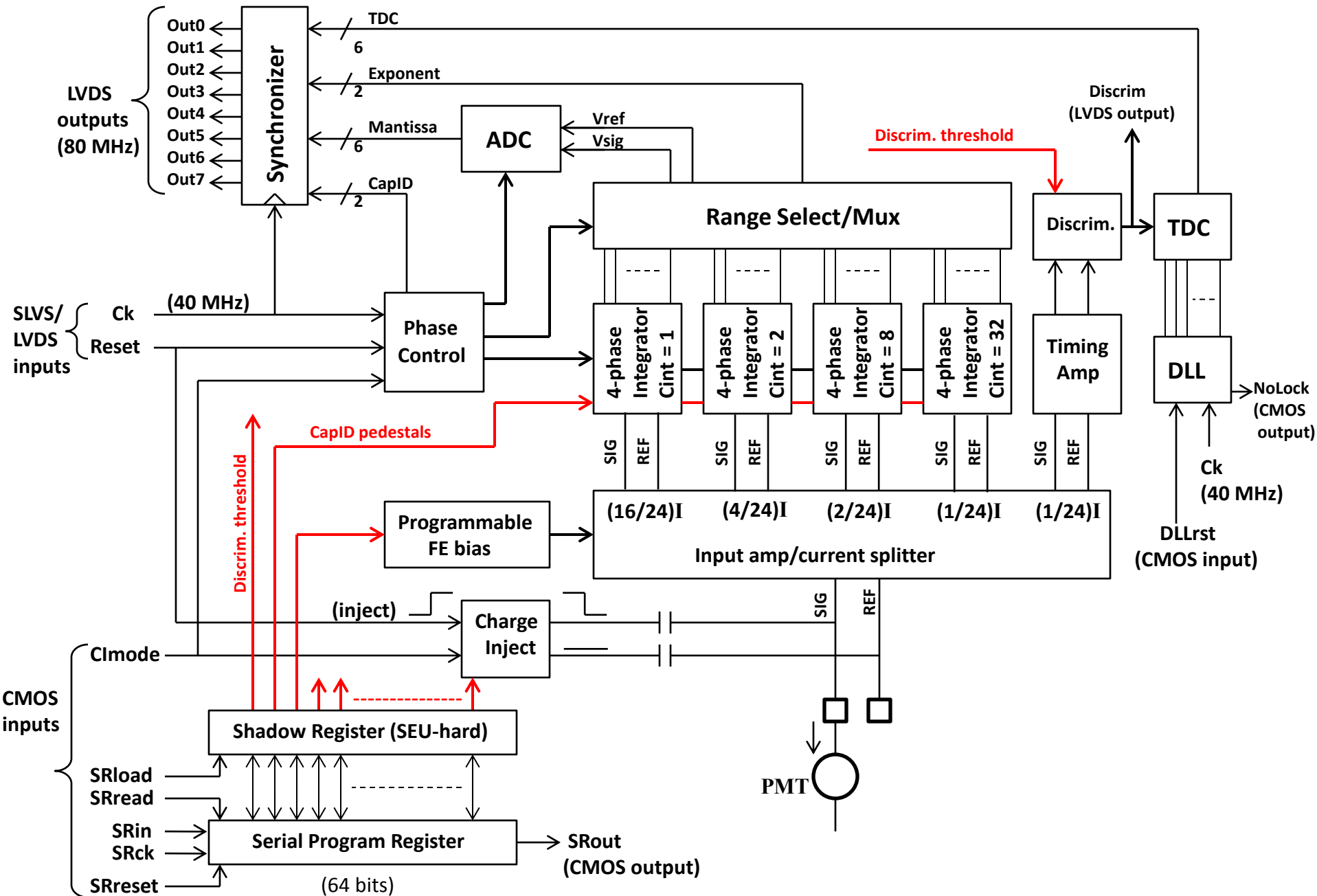Put it all together: QIE10 full chip block diagram




QIE10 Test Results

 - **LSB = 3 fC (as expected)**
- **Input impedance stable over complete dynamic range**
- **Noise with 5 meter RG58 input cables: 1.8 fC (input referred)**
- **Noise with short (0.2 meter) RC58 input cables: 0.6 fC**
- **No change in pedestals or noise after 50 KRad TID (Cs-137 source)**
- **No SEUs in shadow register holding programmed values after 6E12 p/cm² (230 MeV proton beam)**



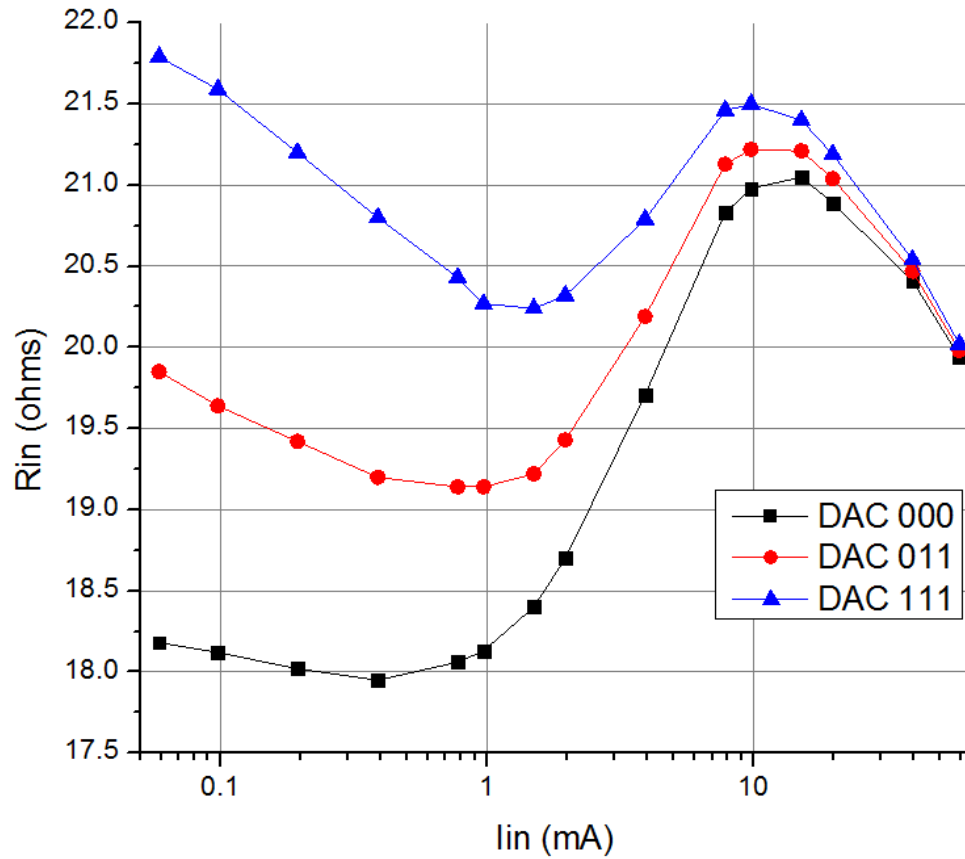
Measured QIE10 input resistance over full dynamic range




(DAC provided for tweaking of input resistance at low end)

Study ADC response
on a single range:

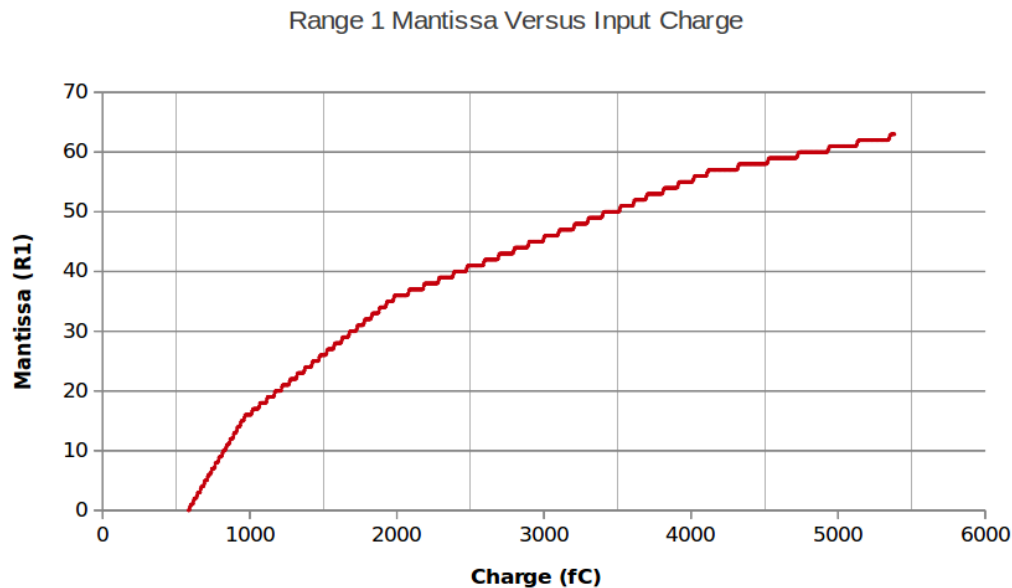⇒ *Response as expected –
See all 4 ADC sections*



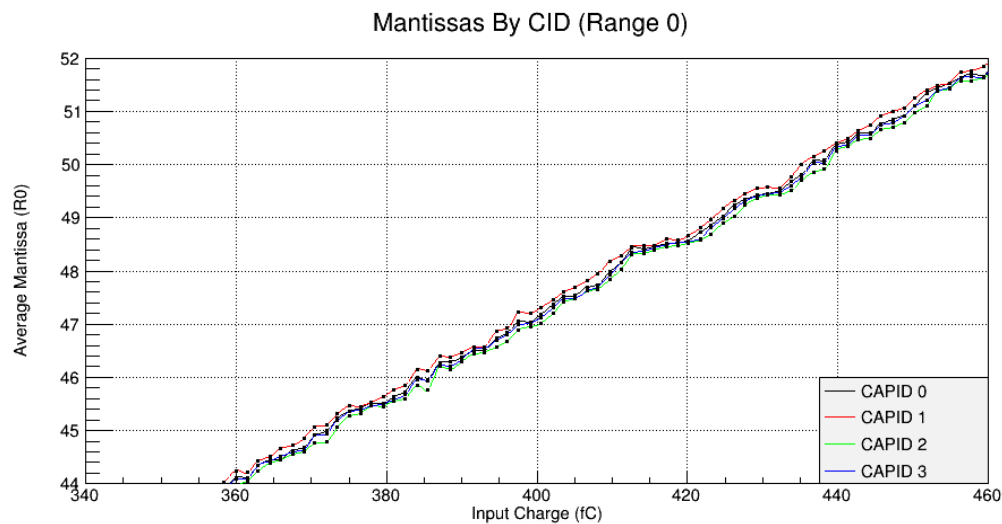
Look at uniformity across
all 4 capIDs (phases)
(one ADC section shown):



⇒ *Response as expected*

⇒ *Note: Uses capID pedestal adjust feature to make pedestals uniform*

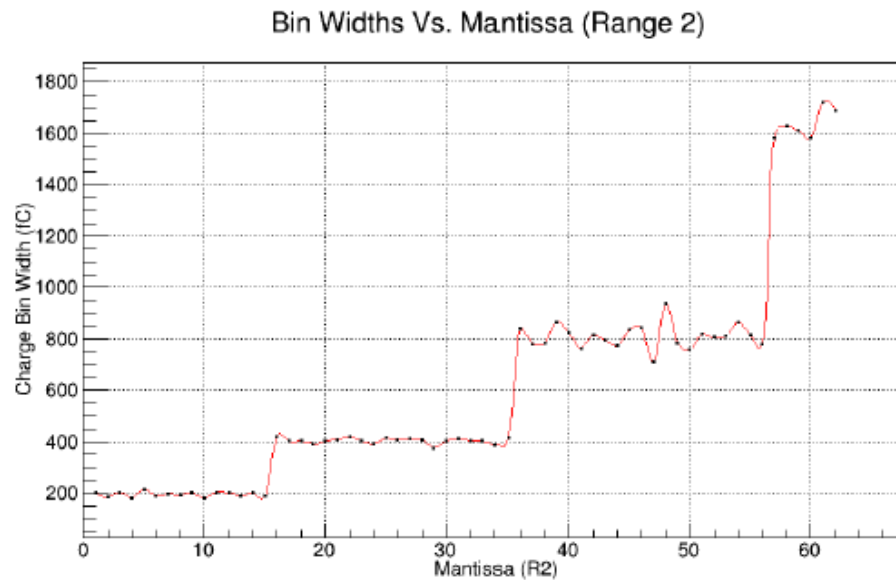Study of bin widths in the 4-section ADC:





- ⇒ **See nice uniform bin widths**
- ⇒ **Bin width variation minimized in bottom 2 sections by design (small bin size requires less variation than large bin to achieve the same DNL)**

- **Timing Studies - TDC Response**

- Apply external input pulse (well above TDC threshold).
- Step pulse delay by 50 ps, average 100 data points per setting

TDC Code Versus Pulse Delay For Chip X

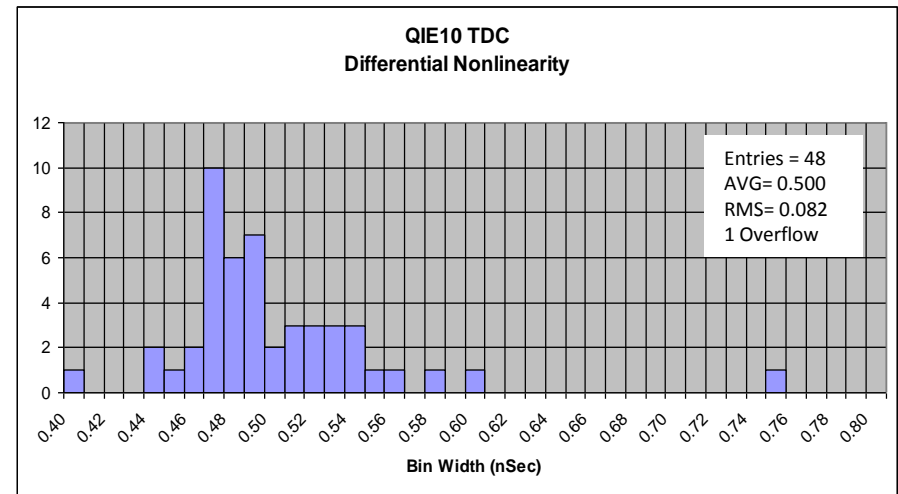 


Data from Fermilab

⇒ **See nice linear response**

⇒ **Bin width uniformity is good: average width = 0.50 ns, DNL < 0.1 ns**

QIE11 (SiPM readout chip)

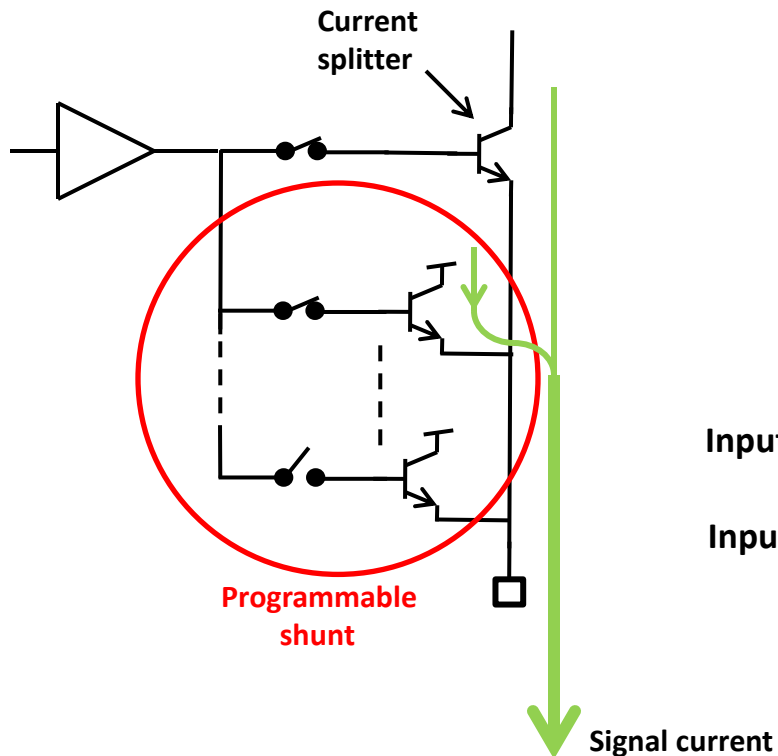- Non-inverting input (same as QIE10)
- Current shunt provides programmable gain to accommodate big SiPM signals
- Low input impedance for big signals (remove constant impedance circuit)
- Full-chip prototype works well (x5 shunt) with only a couple of small bugs



Input resistance ~ 15 ohms for small signal, no shunt

Input resistance ~ 1 ohm for largest signal, big shunt

QIE: a success story over 25 years!

Future QIE work this year:

- **Modification of QIE11 for ATLAS: add another bit of resolution (7-bit mantissa)**
- **Quad QIE (4 per package)??**