



AGH UNIVERSITY OF SCIENCE  
AND TECHNOLOGY



# AIDA IP blocks activities at AGH-UST

**Marek Idzik** AGH-UST

Faculty of Physics and Applied Computer Science  
AGH University of Science and Technology


AIDA 3<sup>rd</sup> Annual Meeting, Vienna 26-28 March 2014

## Outline and Status of IP blocks at AGH-UST

- Design Kit for 65 nm not yet released by CERN
  - We are still waiting to start design in 65 nm. We hope for submission this year...
- At the beginning of AIDA AGH-UST proposed to develop some blocks in IBM 130 nm
  - Fast (>40 Msps) 6-bit
  - Fast 10-bit SAR ADC
  - Variable frequency PLL
  - SLVS interface
- All above blocks were designed in IBM 130 nm, 1<sup>st</sup> prototypes were produced, the result are summarized in next slides...


# IP blocks needed for multichannel readout

## Example: SALT chip architecture

 

- Readout of silicon strip detectors in LHCb Upgrade or LumiCal detector in future ILC will contain front-end and ADC in each channel, and fast serialization of output data.
- Among the key blocks in these readouts, which can be also used as IP cores, are ADC, PLL, SLVS
- First prototypes of these blocks are available – the performed measurements are discussed in this talk
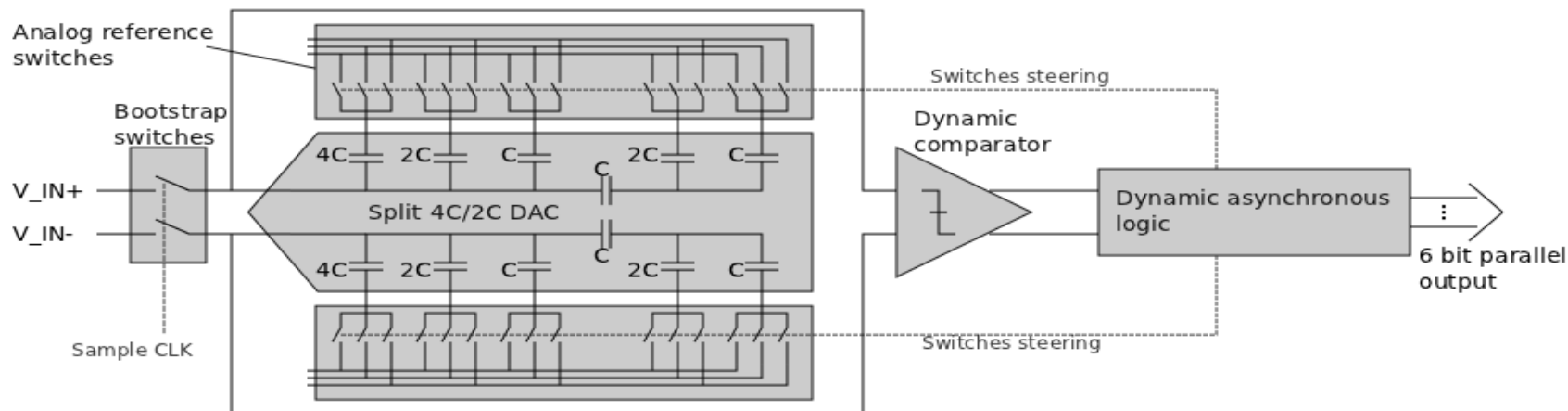
# 6-bit SAR ADC for SALT chip in LHCb Upgrade Architecture & Design considerations



## Architecture of ADC:

- Differential segmented/split DAC with MCS switching scheme – **ultra low power**
- Dynamic comparator – **no static power consumption, power pulsing for free**
- Asynchronous logic – no clock tree – **power saving, allows asynchronous sampling**
- Dynamic SAR logic – **much faster than conventional static logic**




## Design considerations:

- Resolution 6 bits
- Variable sampling frequency up to ~80 MS/s
- Power consumption at 40 MS/s 0.35 mW
- pitch, ready for multichannel integration 40  $\mu\text{m}$

K. Świentek, M. Firlej, T. Fiutowski, M. Idzik, J. Moroń, T. Szumlak "SALT – new silicon strip readout chip for the LHCb Upgrade", TWEPP2013 23-27 September 2013, Perugia Italy

# 6-bit SAR ADC


## Post-layout simulations

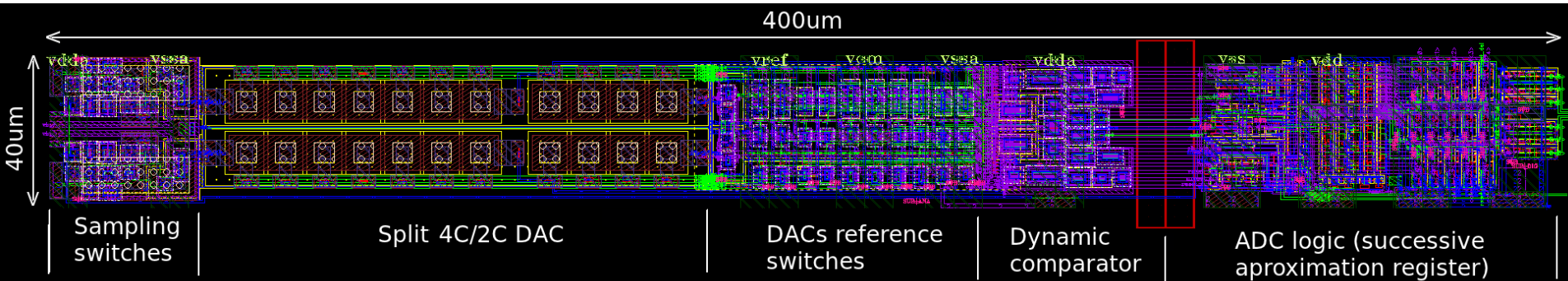 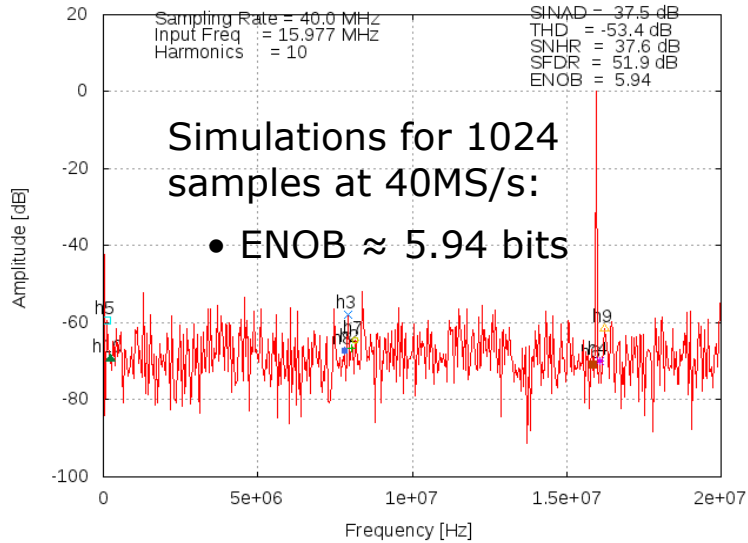


# 6-bit SAR ADC

## Static tests – linearity (@50 MS/s)

Transfer function

 

INL/DNL measurements

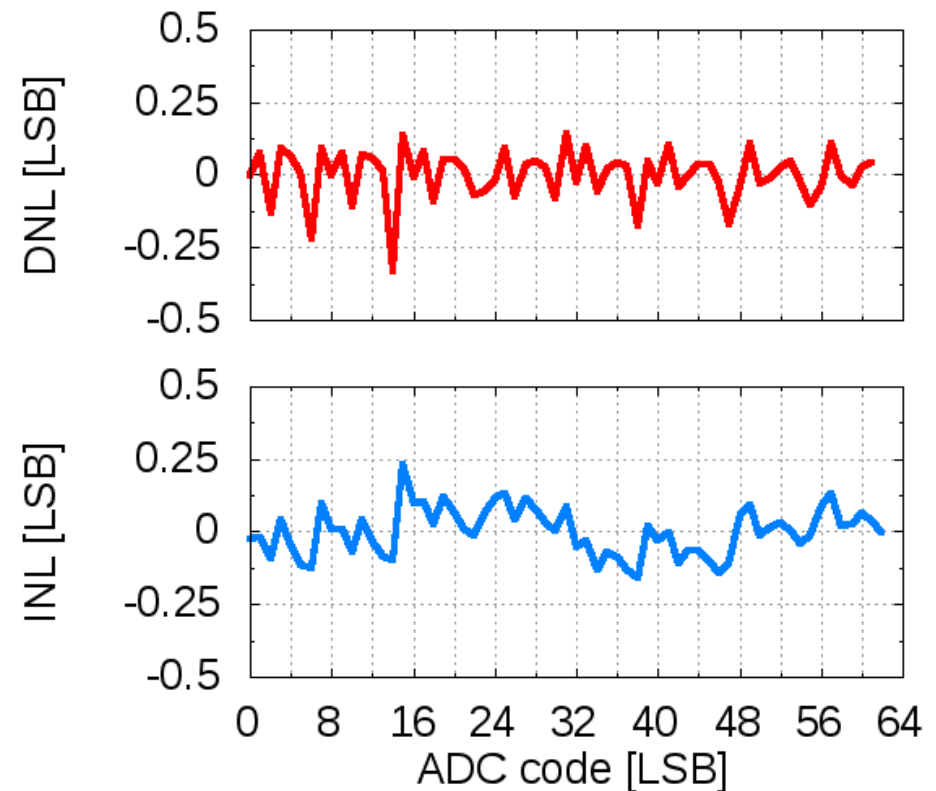


- Measurements show that ADC works very well
- At 50MHz sampling frequency good linearity INL,  $DNL < 0.4$  is seen


# 6-bit SAR ADC

## Dynamic tests – ENOB effective resolution

Example DFT Spectrum @50MS/s

 


Sampling frequency sweep

 

- Measurements show very good dynamic behaviour.
- Measured ENOB is between 5.7 – 5.9 bits
- ADC works well for sampling frequencies beyond 80 MHz
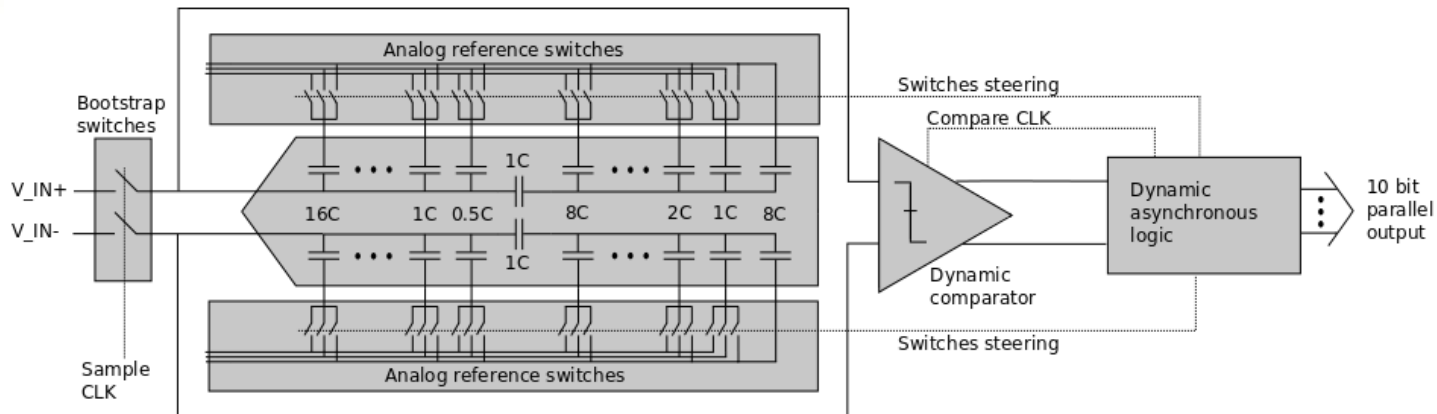
# 10-bit SAR ADC for LumiCal at ILC Architecture & Design considerations



## Architecture of ADC:

- Differential segmented/split DAC with MCS switching scheme – **ultra low power**
- Dynamic comparator – **no static power consumption, power pulsing for free**
- Asynchronous logic – no clock tree – **power saving, allows asynchronous sampling**
- Dynamic SAR logic – **much faster than conventional static logic**


## Design considerations:

- Resolution 10 bits
- Variable sampling frequency up to ~50 MS/s
- Power consumption at 40 MS/s ~1 mW
- pitch, ready for multichannel integration 146  $\mu\text{m}$

J. Moron, M. Firlej, T. Fiutowski, M. Idzik, Sz. Kulis, K. Swientek. “Development of variable sampling rate low power 10-bit SAR ADC in IBM 130 nm technology”, TWEPP2013 23-27 September 2013, Perugia Italy




# 10-bit SAR ADC for Lumical

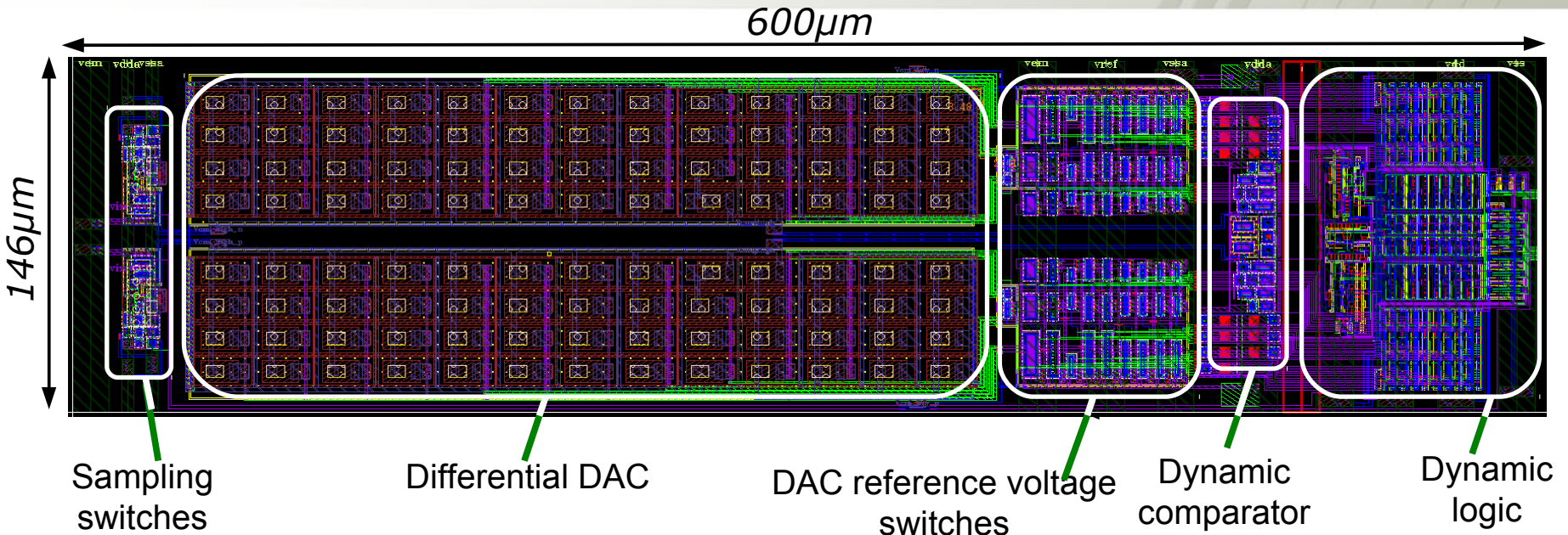
 
## Simulated performance of 10 bit ADC:


- Simulated ENOB ~ **9.5-9.7 bits**
- Maximum sampling rate ~ **50 MS/s**
- Power consumption ~ **1mW @ 40 MS/s**




# 10-bit SAR ADC for LumiCal

## Static measurement results

Transfer function

 

INL/DNL measurements

 

- ADC works well in the whole input signal range
- Generally, good linearity is measured, although for a few codes improvement is still needed


# 10-bit SAR ADC for LumiCal

## Dynamic measurement results (@20 MS/s)

 
### Example DFT Spectrum

Sampling Rate = 10.0 MHz  
 Input Freq = 158.691 kHz  
 Harmonics = 10

SINAD = 56.9 dB  
 THD = -71.2 dB  
 SNHR = 57.1 dB  
 SFDR = 72.5 dB



### Input frequency sweep

 

**ENOB ~ 9.3** up to Nyquist input frequency for  $f_{\text{sample}} \sim 20\text{MHz}$


ADC works for  $f_{\text{sample}}$  beyond 40 MS/s, but above 20 MS/s ENOB start to decrease.  
 Problem with jitter above 20 MS/s found..., will be fixed in next submission.

# Prototypes of SAR ADC vs State-of-the-Art Performance of first prototypes

## Main features:



	LHCb	LumiCal
• Resolution [bits]	6	10
• Sampling frequency [MS/s]	>80	20 (50*)
• Power cons. [mW] @ 40 MS/s	0.35	1
• Size [mm <sup>2</sup> ] Dim. [μm]	0.016 40 x 400	0.087 146x600
• DNL/INL [LSB]	<0.4	~1.0
• SINAD@40MS/s [dB] ENOB [bits]	37.5 5.8	>56 9.3
• FOM [fJ/conv]	~150	~50

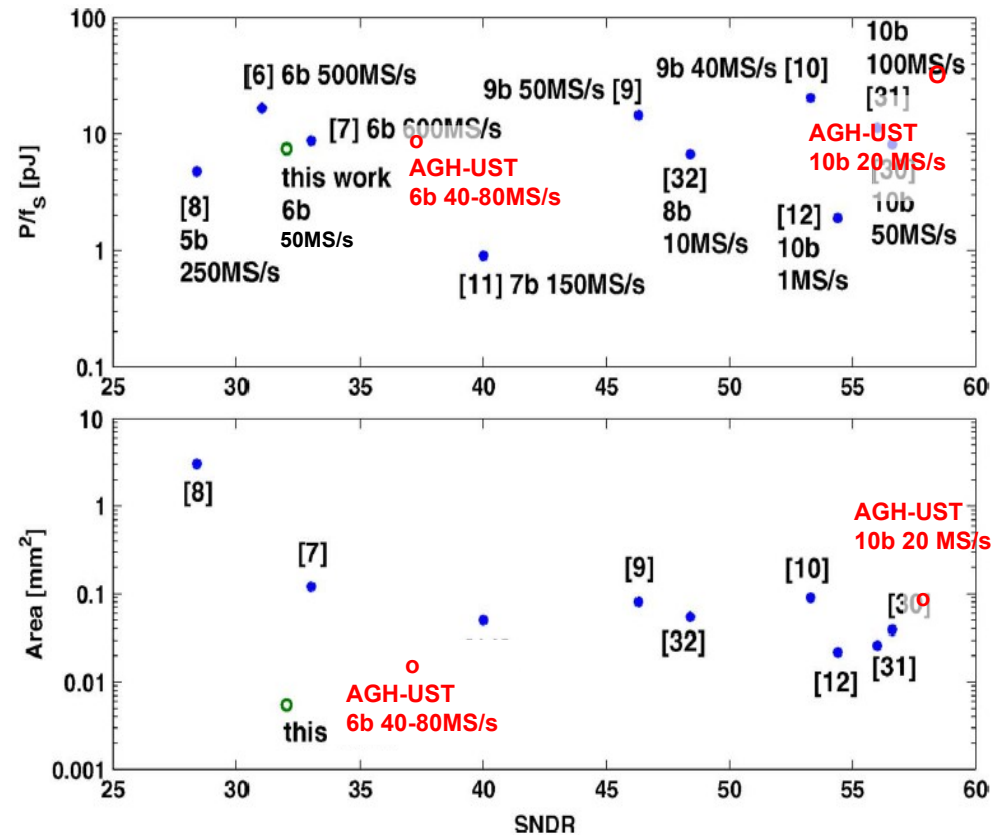Performance of our ADCs  
is similar to  
State-of-the-Art designs



AGH-UST data were added to Table taken from “this work” :  
P.Nuzzo, C. Nani, at el., “A 6-Bit 50-MS/s Threshold Configuring SAR ADC in 90-nm Digital CMOS”,  
IEEE Trans. On Circuits and Systems I vol.59 pp.80-92 January 2012
 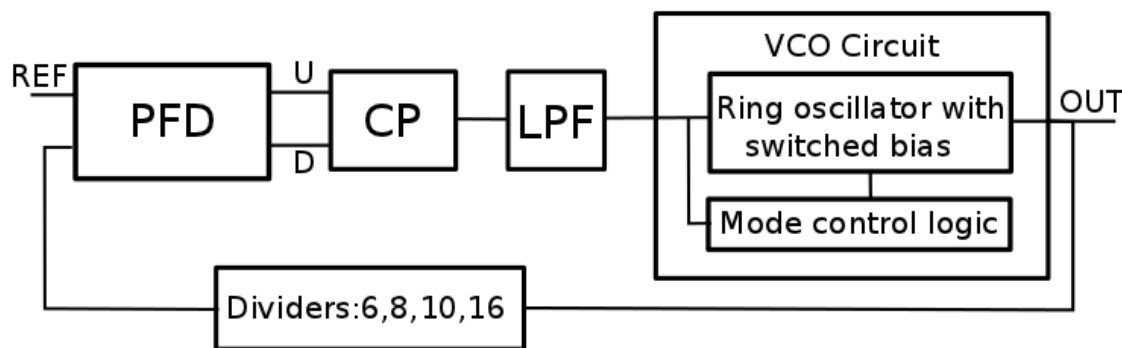
# Low power PLL in 130 nm CMOS Architecture and specifications




300 x 300  $\mu\text{m}$



## PLL features:

- General purpose PLL block
- Very wide output frequency range (10MHz - 3.5GHz)
- 16 VCO modes - Automatically (or manually) changed
- Power consumption  $\sim 0.6\text{mW}@1\text{GHz}$
- Different loop division factors: 6, 8, 10 and 16
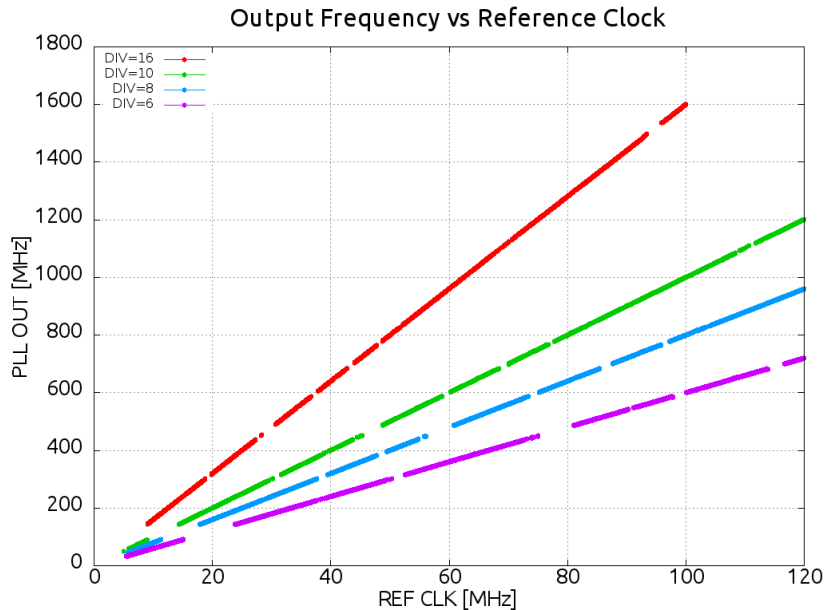
# Low power PLL in 130 nm CMOS Measurements



 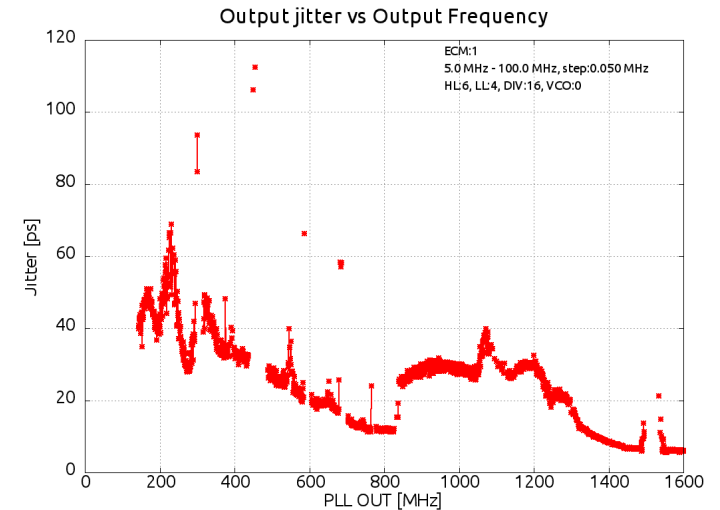- Measurements confirm proper circuit operation in frequency range 20MHz-1.6GHz
- All four division factors work properly
- Power consumption scales linearly with PLL clock frequency (two rings → two curves)
- Gaps in frequency and Jitter need to be improved




# Multichannel ADC aspects

## Design of SLVS interface

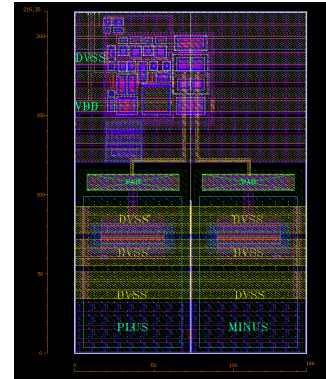
### Specifications:

- Architecture
  - Driver – based on Boni paper
  - Receiver – based on self-biased amplifier (Bazes paper)
- Technology – CMOS 130 nm
- Maximum frequency  $\sim 1\text{GHz}$
- Pitch matched to pads. Driver/receiver integrated with 2 pads (146 $\mu\text{m}$  pitch)


Functionality verified during ADC and PLL test up to  $\sim 1.5\text{ GHz}$ . Dedicated quantitative tests not yet done (waiting in line...)



Driver

 

Receiver

 

## Summary

- Two low power ADCs (6-bit, 10-bit), general purpose PLL and SLVS interface were designed in 130 nm, fabricated and tested.
- All blocks are fully functional, quantitative tests show excellent results for 6-bit ADC and good results for 10-bit ADC and PLL.
- Improved versions were submitted in February 2014



*Thank you for attention*




# Multichannel SAR ADC with serialization Architecture
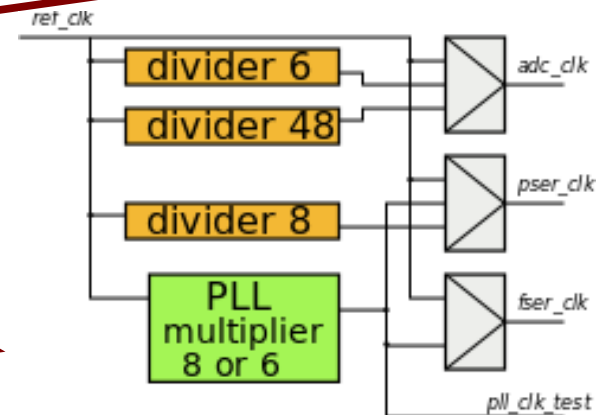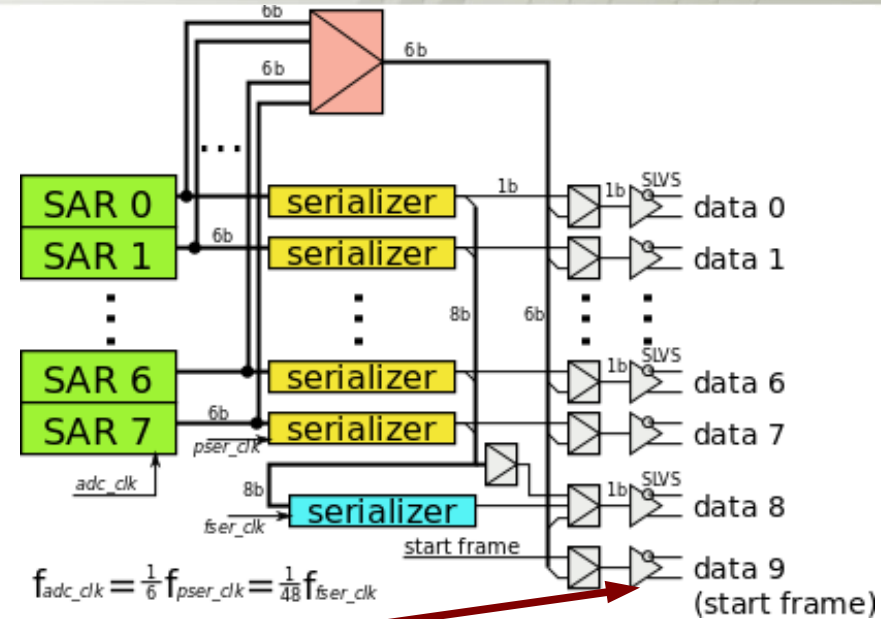
## Specifications & implementation issues:

- 8 channels of 6-bit SAR ADC
- Technology 130 nm CMOS
- Multimode digital multiplexer/serializer:
  - Full serialization: one data link per all channels (external clk division or PLL clk generation)
  - Partial serialization: one data link per channel (external clk division or PLL clk generation)
  - Test mode: single channel output (max fsmp ~50 Msps)
- High speed SLVS interface (>1GHz)
- Multiple clock generation schemes (with or without PLL)
- PLL for data serialization
- Power pulsing



# 6-bit SAR ADC Layout of prototype ASIC

 

2340um x 1380um

ADC prototype contains:

- 8 channels of 6-bit SAR ADC in 40um pitch
- Multiplexing&Serialization circuitry
- PLL prototype (discussed later...)
- SLVS I/O circuitry (discussed later...)
- Staggered pads

Prototypes were fabricated in 2012. FPGA based test setup was developed. Measurements of ADC performance have been completed...

# ADC testing Measurement setup

DFT and data analysis –  
custom software

Differential function  
generator – Agilent 81160A



Power supply



Input  
sine

Sample  
clock


Results

Sampled data  
(low bitrate)

Sampled data  
(high bitrate)

Sampling Rate = 40.0 MHz  
input freq = 3.916 MHz  
Harmonics = 10

 SINAD = 57.0 dB  
THD = -69.6 dB  
SNR = 57.3 dB  
SFDR = 74.6 dB



DAQ – receives fast transmission from ADC  
(up to 500 Mb/s), captures the data and sends  
to PC via Ethernet for offline analysis