

# Chip Development Progress

Andreu Montiel, Raimon Casanova, Oscar Alonso, Eva Vilella and Angel Diéguez

Systems Instrumentation and Communications (SIC)  
Department of Electronics, University of Barcelona (UB)  
C/ Martí i Franquès 1, 08028 – Barcelona, Spain

[evilella@el.ub.edu](mailto:evilella@el.ub.edu)




## ➤ Outline

- 1. Reminder of the general structure of the readout system**
- 2. Shaper design**
  - MOSFET based solution
  - Noise comparison
- 3. ADC design**
  - Problem of typical Wilkinson ADCs
  - Incremental data converters
  - Comparison


# 1. General structure of the readout circuit.

Different options for shaper resistor →

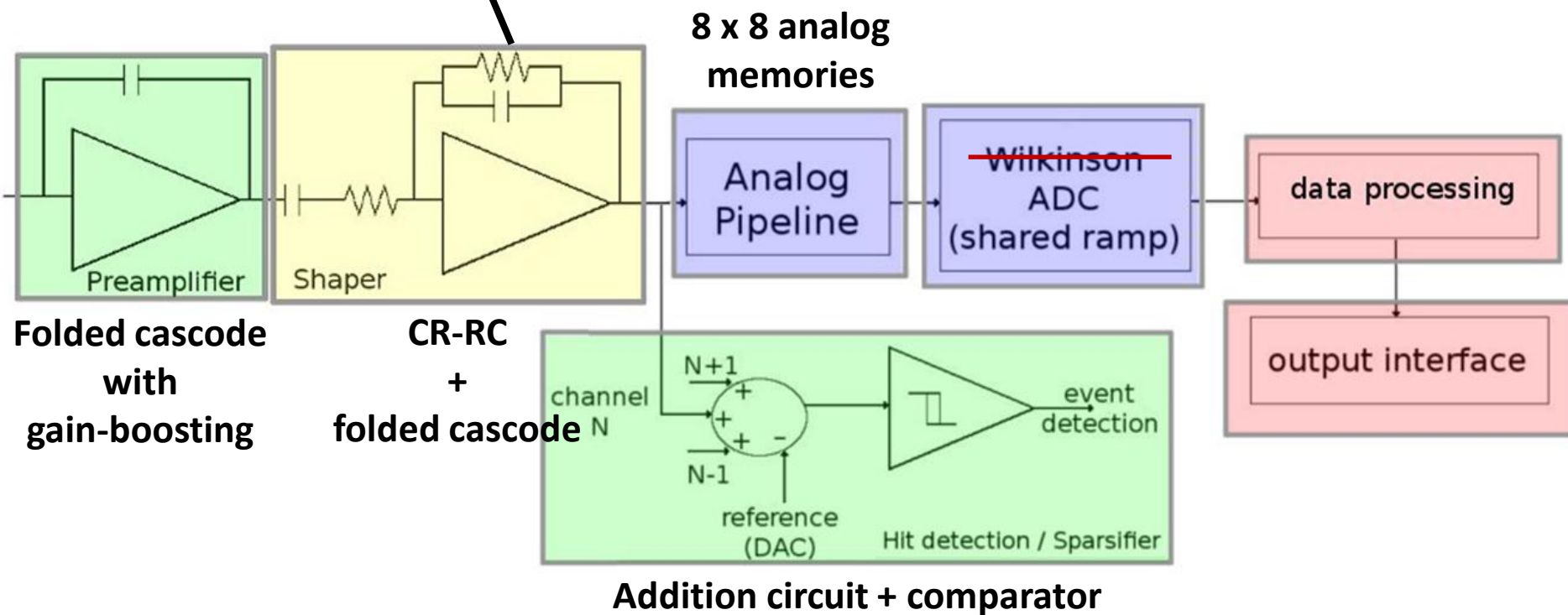
- a) Polysilicon resistor (large area, discarded)
- b) Active resistor (current mirror based, explored and finally discarded)
- c) Single MOSFET (presented today)




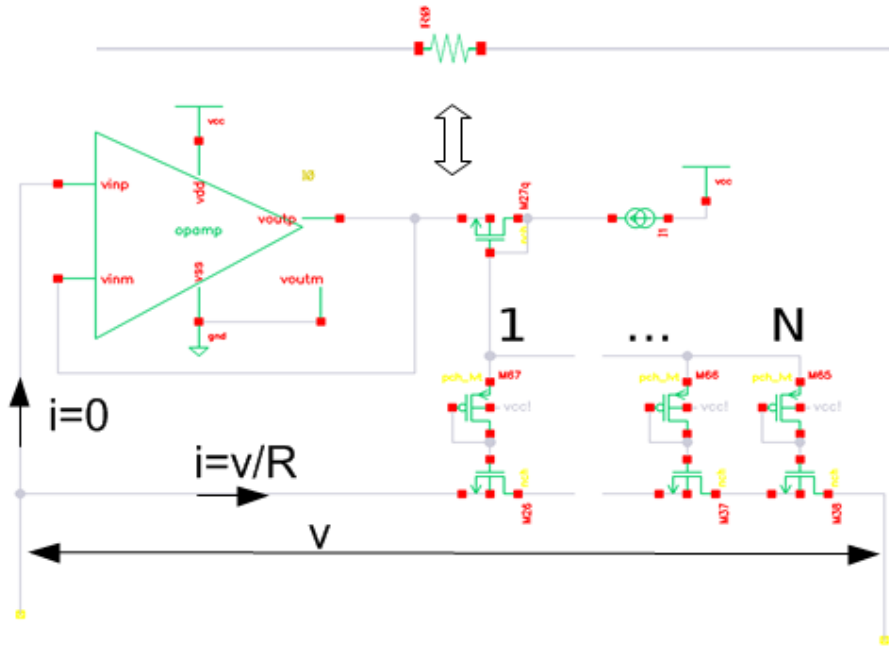
## 2. Shaper design. MOSFET based solution.



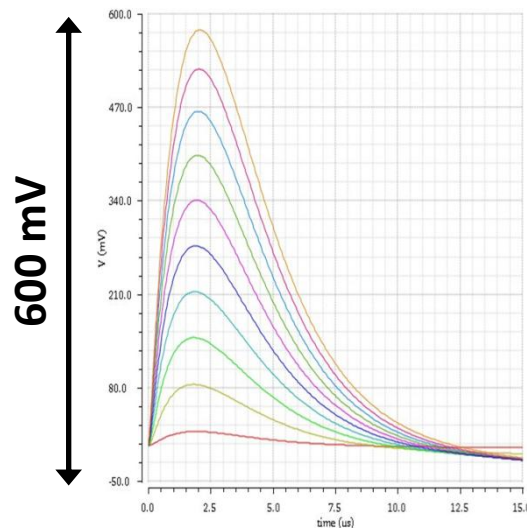- $V_{GATE}$  is referenced to  $V_{SOURCE}$  of the first transistor with a follower. Regulated with a programmable current.
- The voltage in the resistor is divided with  $N$  transistors.
- $\sim G\Omega$  equivalent resistor.
- Quasi-floating gate transistor
- $V_{GATE} \sim \text{constant}$  (gate is capacity-coupled to source)



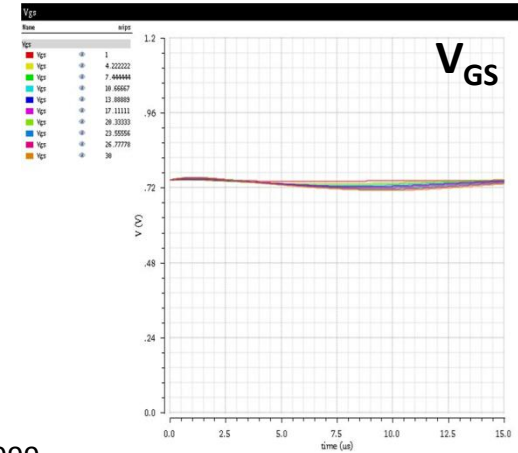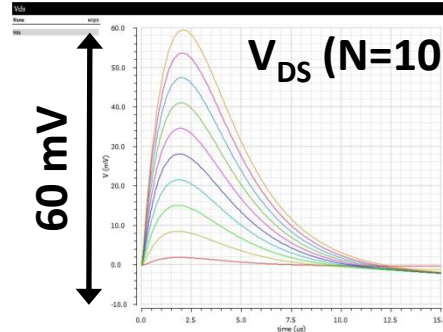- Very low  $V_{DS}$  variations due to multiple transistors in series (linearity  $\uparrow\uparrow$ )



- 1) E. Özalevli, P.E. Hasler, IEEE Trans. Circuits Syst. 55 (2008) 999.
- 2) J. Ramírez-Angulo et al., Electron. Lett. 41 (2005) 511.

## 2. Shaper design. Noise comparison.

### - Noise comparison:

$$\text{ENC} = A + B \cdot C_d$$

- A, B = noise parameters

-  $C_d$  = detector capacity

### - Simulation conditions:

- Dynamic range: 30 MIPs

- Different sensor thickness

- 2  $\mu$ s of peaking time

### - Comparison with other front-ends:

	sensor thickness	A	B	Noise at 20pF
Poly. resistors	300 $\mu$ m	260e-	4.9e-/pF	350e-
	200 $\mu$ m	188e-	4.5e-/pF	272e-
Current mirror based	300 $\mu$ m	180e-	7.7e-/pF	326e-
	200 $\mu$ m	228e-	7.7e-/pF	374e-
MOSFET based	300 $\mu$ m	148e-	6.3e-/pF	266e-
	200 $\mu$ m	129e-	5.5e-/pF	233.1e-


Front-end	A (e-)	B(e-/pF)	Shaping time
APV25	246	36	50 ns
MX6	340	20	
VA1	200	8	1 $\mu$ s
Beetle	303	33,6	25 ns
KPix	300	35	
This des., polysilicon	260	4.9	2 $\mu$ s
This des., current scaling	180	7,7	2 $\mu$ s
This des., quasi-floating gate	148	6,3	2 $\mu$ s

Simulated data →

### 3. ADC design. Problem of typical Wilkinson ADCs.

- **Preferred ADC option** → multi-channel parallel **Wilkinson ADC**.
- Problem → sensitive to parameter spread in nm technologies + limited speed (**time=2<sup>nbits</sup> clock cycles**).
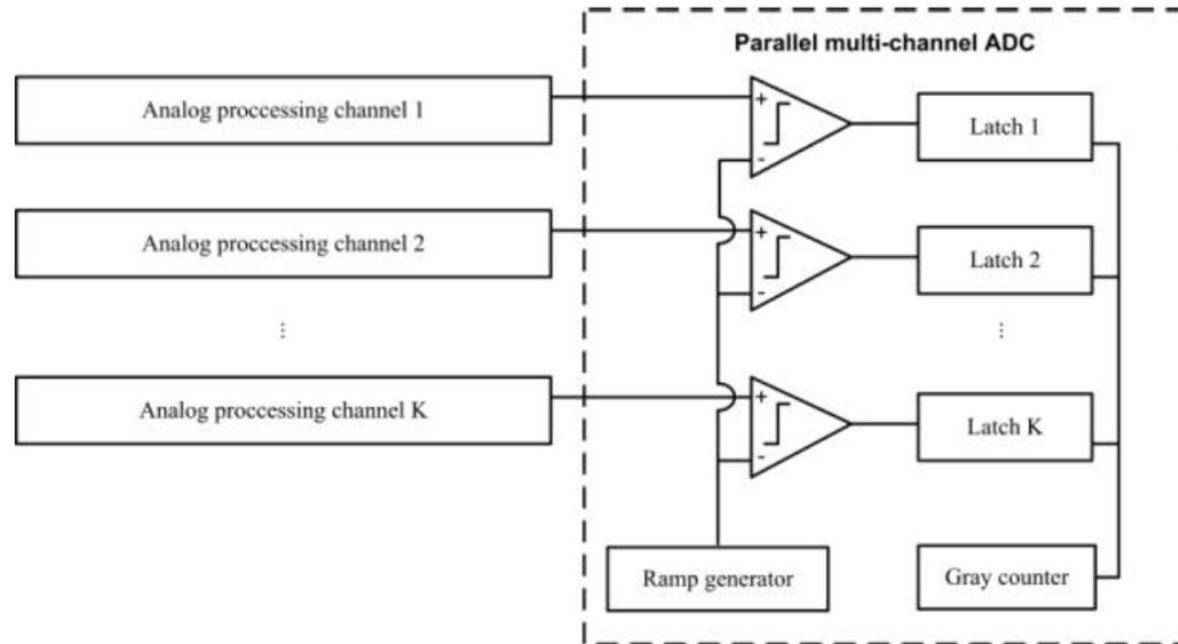
#### Multi-channel parallel Wilkinson ADC




- **Proposed solution** → **Incremental data converter (IDC)**.
  - Sigma-delta converter with stop/reset (to fit ILC timeline).
  - **Insensitive to parameter spread**.
    - Highly digital circuits.
  - **Higher operating frequencies** (1 order of magnitude faster than Wilkinson ADCs).
    - Possibility to multiplex several channels per ADC + reduction of area.

### 3. ADC design. Incremental data converters.

- Possible architectures:

- First order (1 integrator + 1 comparator) → long conversion times of  $2^{n_{bits}}$  clock cycles
- **Second and higher orders by cascading integrators (Cascaded-Integrators Feed-Forward or CIFF)**

2nd order  
CIFF  
architecture

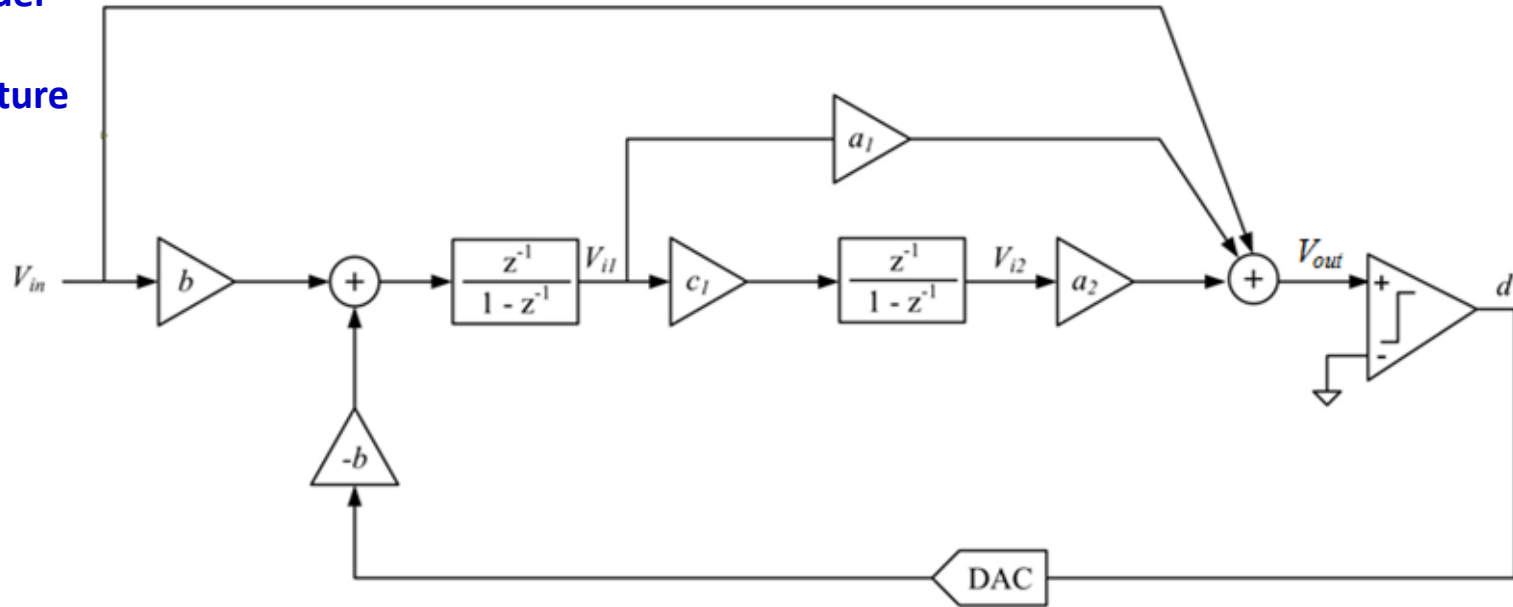

- Advantages of CIFF architectures:


- **Short conversion times** →  $\sqrt{\frac{2^{n_{bits}+1}}{c_1 \cdot b}}$  clock cycles (2nd order),  $\sqrt[3]{\frac{3 \cdot 2^{n_{bits}+1}}{c_2 \cdot c_1 \cdot b}}$  clock cycles (3rd order)
- Less sensitive to non-linearities.
- Less voltage swing.
- 1 DAC only (less matching problems).

### 3. ADC design. Comparison.

- Number of clock cycles or n (assuming  $b, c_1$  and  $c_2 = 1$ ):

nbits	n		
	Wilkinson	second order	third order
8	256	23	12
9	512	32	15
10	1024	45	19
11	2048	64	23
12	4096	91	29
13	8192	128	37
14	16384	181	47

Ratio

 

- Inputs:

- 256 channels
- 8 hits per strip (expected)
- 8 samples to reconstruct each hit
- 12 bits of resolution (n bits)
- 40 MHz of clock frequency

Results per channel:

6.5 ms (256 channels parallel Wilkinson ADC)

$$8 \frac{\text{hits}}{\text{stripe}} \cdot 8 \frac{\text{samples}}{\text{hit}} \cdot n \cdot \frac{1}{\text{clock frequency}} = 0.14 \text{ ms (2nd order IDC)} \rightarrow 45 \text{ times faster! (area } \downarrow \text{)}$$

0.046 ms (3rd order IDC) → 141 times faster! (area ↓↓)



### 3. ADC design. Comparison.

- Number of clock cycles or n (exact value of b, c<sub>1</sub>, c<sub>2</sub>, a<sub>1</sub> and a<sub>2</sub>?):

order	b	c <sub>1</sub>	c <sub>2</sub>	a <sub>1</sub>	a <sub>2</sub>	n
2	0.7	0.6	-	1.107	0.515	139
3	0.35	0.5	0.65			60

- The coefficients must be set below 1 to avoid the saturation of the integrators  
 - Coefficients simulated with Matlab (Sigma Delta Toolbox)

#### Results :

6.5 ms (256 channels parallel Wilkinson ADC)

$$8 \frac{\text{hits}}{\text{stripe}} \cdot 8 \frac{\text{samples}}{\text{hit}} \cdot n \cdot \frac{1}{\text{clock frequency}} = 0.22 \text{ ms (2nd order IDC)} \rightarrow 0.056 \text{ s per 256 channels}$$

0.096 ms (3rd order IDC) → 0.024 s per 256 channels

- IDCs offer higher conversion rates than Wilkinson ADCs (at the same clock frequency)  
 - In IDCs, it is possible to multiplex several channels per ADC (area ↓, same conversion time):

- 256 channels parallel Wilkinson ADC
- 2nd order IDC → **9 IDCs (9 ADCs)** for a conversion time of ≈ 6.5 ms (28 channels per ADC)
- 3rd order IDC → **4 IDCs (4 ADCs)** for a conversion time of ≈ 6.5 ms (64 channels per ADC)



**Thank you for your attention**