



MAX

MYRRHA ACCELERATOR eXPERIMENT
RESEARCH & DEVELOPMENT PROGRAMME



Development of 700 MHz SS Amplifiers


EuCARD-2 Accelerator for ADS
CERN 20/ 21 March 2014

S.Sierra/ B.Darges

THALES



For the record: RF needs along the Linac

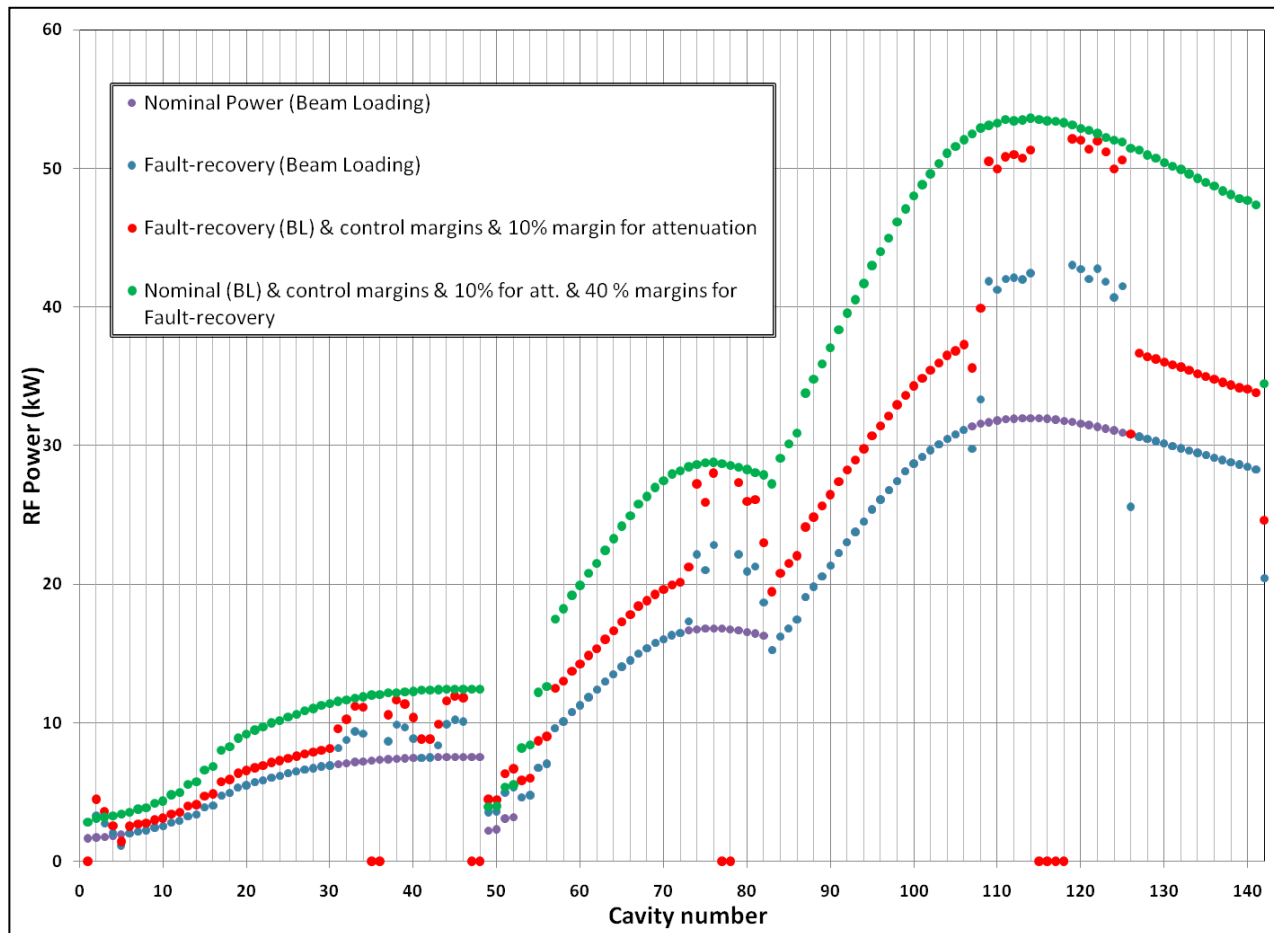

See F Bouly presentation



- Major requirements:

- 94 cavities have to be fed with RF @ 704MHz and in CW
- Reliability of the RF amplifier & ancillaries has to be optimized (> 50 000h)
- Fast beam recovery procedures using neighboring cavities in case of failure is foreseen.

- The recovery procedure (neighboring cavities) is not thinkable with a power distribution through several cavities
- It's always better to independently phased cavities
- Power distribution through the linac is not constant (from 18 to 55 kW cw)
- The RF power need for each cavity is rather low (few tens of kilowatts)



MAX

MYRRHA ACCELERATOR eXPERIMENT
RESEARCH & DEVELOPMENT PROGRAMME



- **In this particular case, SSPA is foreseen for RF amplifiers**

Advantages:

- No High Voltage (few tens of V)
- Power adjustments configuration possible at the installation :
 - A common design of cabinets could be foreseen with cabinets receiving individuals modules adapted to the position along the linac
- Sufficient space is necessary
- Due to the relative low power the balance efficiency between recombination losses/ SS efficiency is acceptable
- One single module fault RF is still available

But:

- Special attention must be done on the design and protection of individual modules and power supplies (including redundancies of these PS)
- with all protective devices, redundancies on the power supplies and architecture this solution is quite expensive.



MAX

MYRRHA ACCELERATOR eXPERIMENT
RESEARCH & DEVELOPMENT PROGRAMME




SSPA architecture

From individual modules up to the final amplifier


With individual fault operation consequencey



RF base Module 850CW @ 700MHz

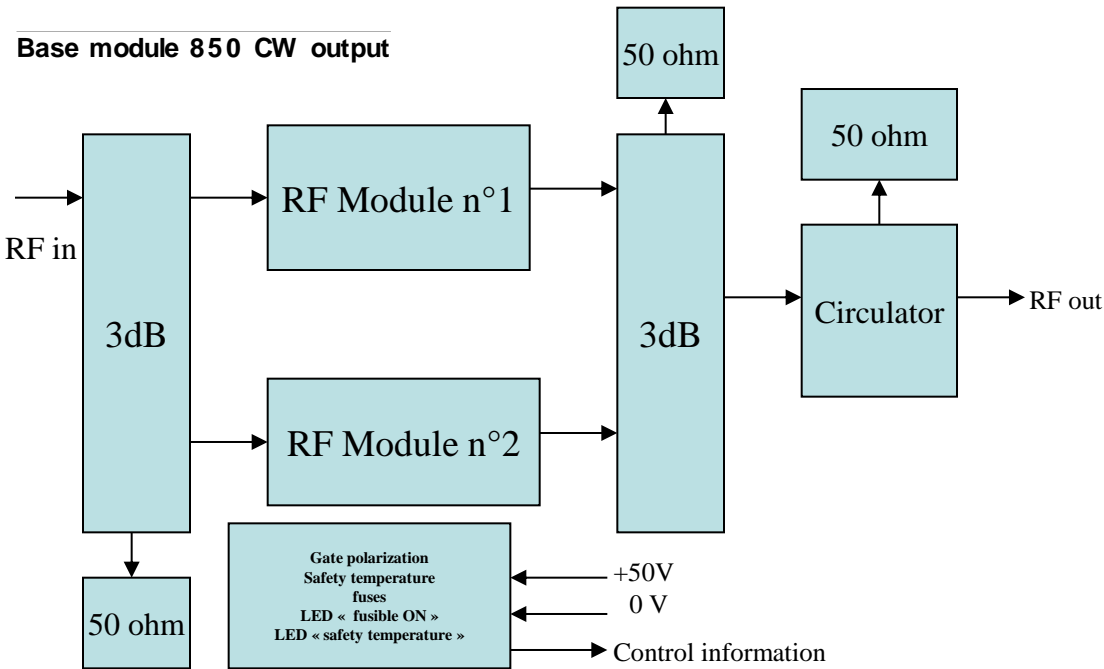



Example RF base module 300W@500MHz

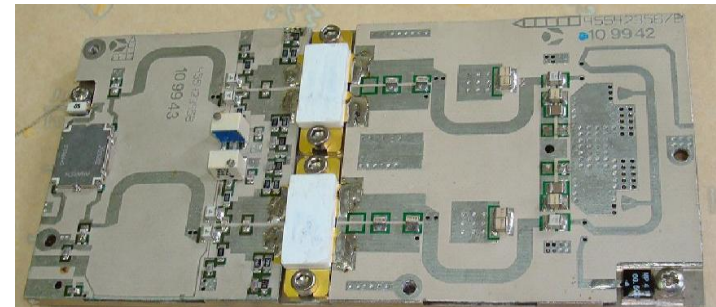

- None adjusting RF
- 90% CMS devices
- Last generation Technologies Transistors
- RoHS compliant



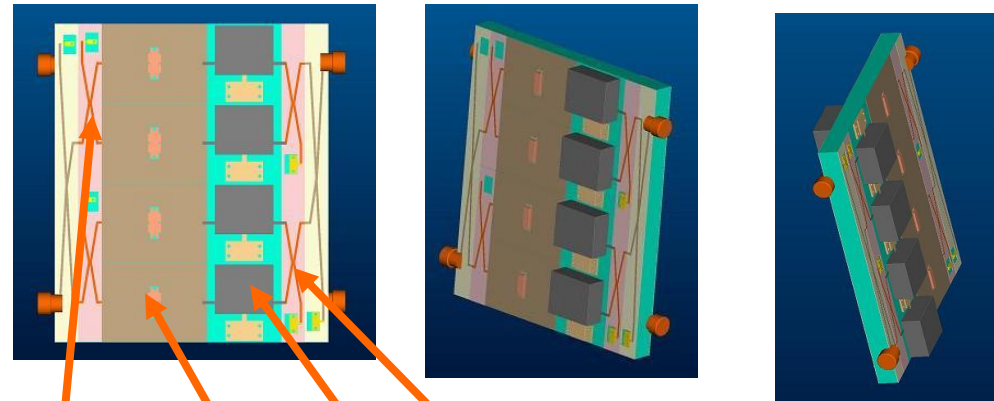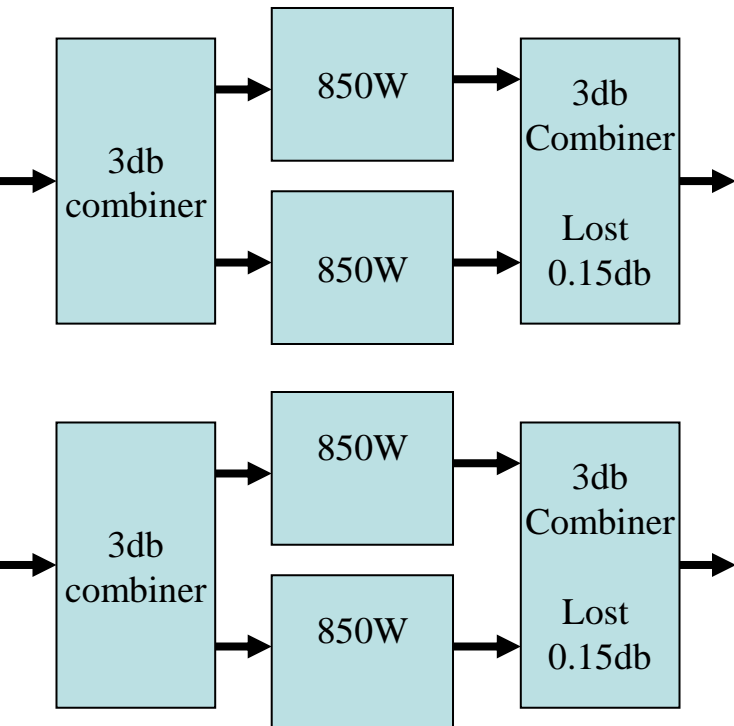2 x 1.6 kW CW @ 700MHz base block (two sides)



3 x splitters

4 x Base modules


3 x combiners

4 x isolators



Calculation on lost config. N°1


Place	Base power	Transistors OFF	Output Power (W)	db
A	1600	0	1600	0,0
B	1600	1	900	-2,5
C	1600	2	400	-9,0
D	1600	3	100	-12,0
E	1600	4	0	

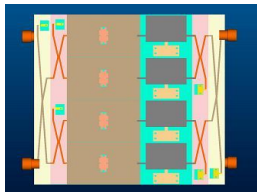


A




B

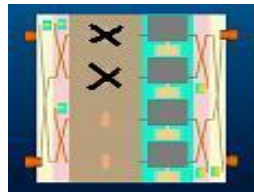


C

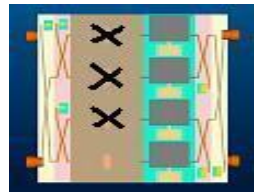

D

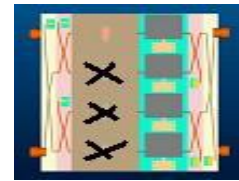

D

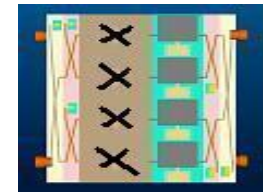

E





MAX

MYRRHA ACCELERATOR eXPERIMENT
RESEARCH & DEVELOPMENT PROGRAMME



16 kW CW @ 700 MHz base block

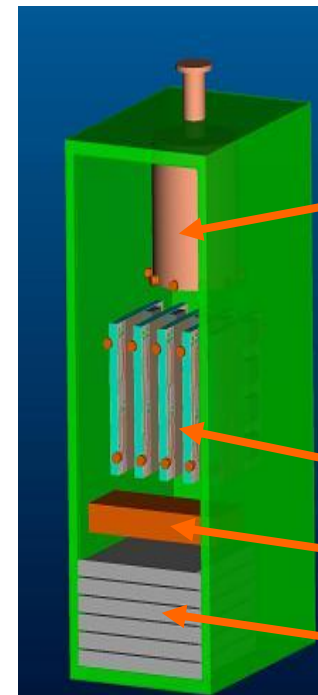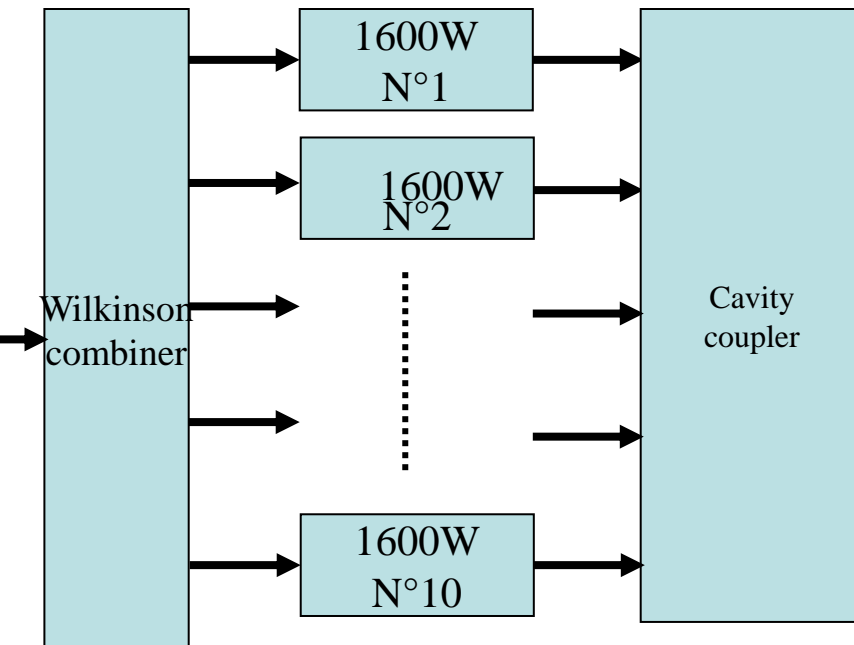

Cavity combiner

5 amplifiers

driver

6 x Power supply



Evaluation Output Power=F(Transistors ON/ OFF)

Cavity coupler (example → 4 inputs)
(Thales Patent)



Cavity 10 inputs		
N	Lost	Pout
0	0db	16Kw
1	0,2db	15,3Kw
2	0,45db	14,4Kw
3	0,67db	13,7Kw
4	0,9db	13Kw



Evaluation Output Power=F(modules ON/ OFF)

Cavity coupler (example → 4 inputs)
(Thales Patent)




3.2Kw fail

Cavity coupler 10 inputs N (fail ==> Nx1,6Kw)	perte	Pout
0	0db	16Kw
1	0,9db	13Kw
2	1,7db	11Kw
3	2,5db	9Kw



Pout \approx 32 kW CW @ 700MHz cabinet

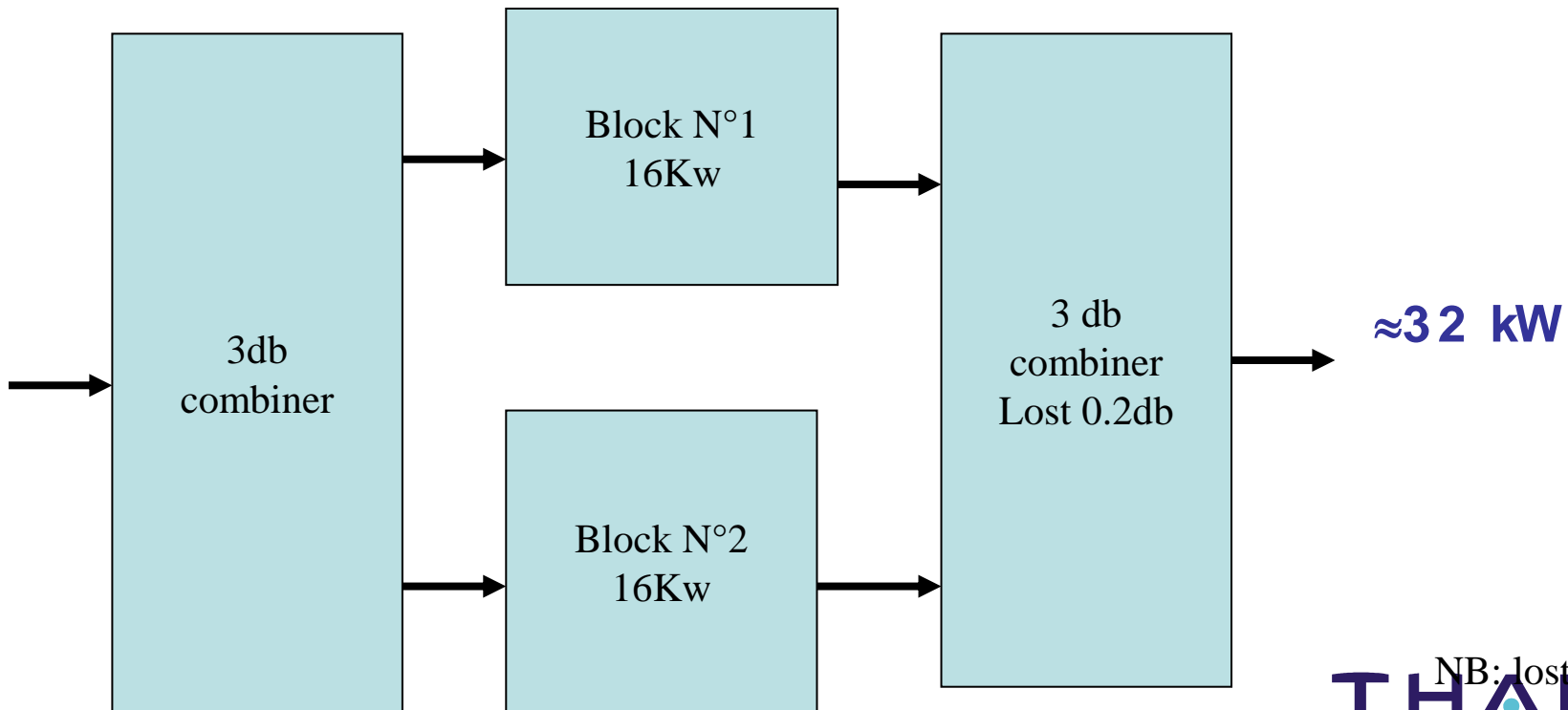



Evaluation Output Power =F(transistors ON/ OFF)

$$P_{out} = \frac{P_1 + P_2 + 2\sqrt{P_1}\sqrt{P_2}}{2}$$

Transistors fail	Pout cabinet 1	Pout cabinet 2	total Pout	Lost
0	16Kw	16Kw	32KW	0db
1	15,3Kw	16Kw	31,3KW	0,1dB
2	14,4Kw	16Kw	30,4KW	0,22dB
3	13,7Kw	16Kw	29,6KW	0,34dB
4	13Kw	16Kw	28.9KW	0,45dB



1.6Kw fail



Evaluation Output Power =F(modules 1.6Kw ON/ OFF)

$$P_{out} = \frac{P_1 + P_2 + 2\sqrt{P_1}\sqrt{P_2}}{2}$$



3.2KW fail




1.6 KW fail

P1	P2	Pout
16Kw	16Kw	32Kw
13Kw	16Kw	28,9Kw
11Kw	16Kw	26,8Kw
9Kw	16Kw	19,5Kw



Pout ≈ 32 kW CW @ 700 MHz Cabinet

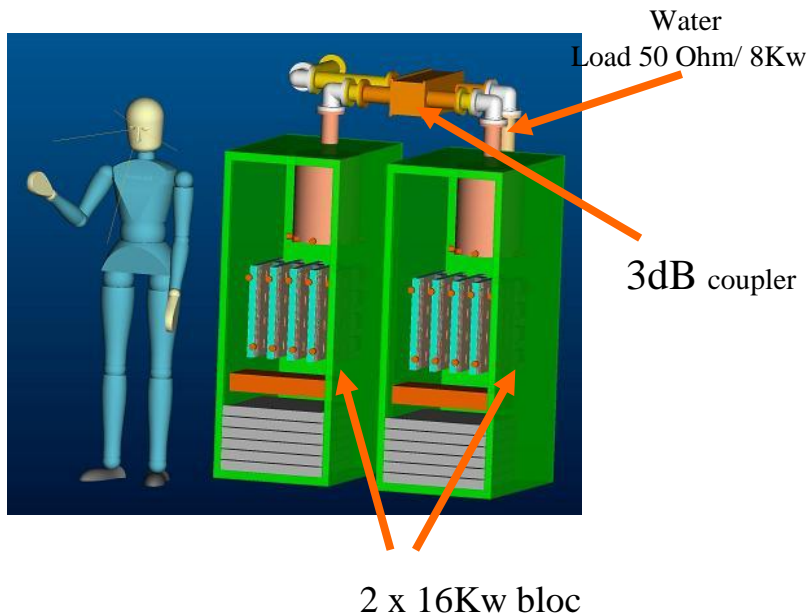

What could be proposed for the linac:

3 kinds of cabinets:

- One family of 16 kW (11 kW with 3.2 kW off)
- Another one at 32 kW (28kW with 3.2 kW off)
- Last at 64 kW (60kW with 3.2 kW off)



MAX

MYRRHA ACCELERATOR eXPERIMENT
RESEARCH & DEVELOPMENT PROGRAMME



Prototyping and results



BLF888A → NXP

1. Product profile

1.1 General description

A 600 W LDMOS RF power transistor for broadcast transmitter applications and industrial applications. The excellent ruggedness of this device makes it ideal for digital and analog transmitter applications.

Table 1. Application information


RF performance at $V_{DS} = 50$ V unless otherwise specified.

Mode of operation	f (MHz)	$P_{L(AV)}$ (W)	$P_{L(M)}$ (W)	G_p (dB)	η_D (%)	IMD3 (dBc)	IMD _{shldr} (dBc)	PAR (dB)
RF performance in a common source 860 MHz narrowband test circuit								
2-tone, class-AB	$f_1 = 860$; $f_2 = 860.1$	250	-	21	46	-32	-	-
pulsed, class-AB [1]	860	-	600	20	58	-	-	-



Load pull measurement

RF base Module 400 CW @ 700 MHz

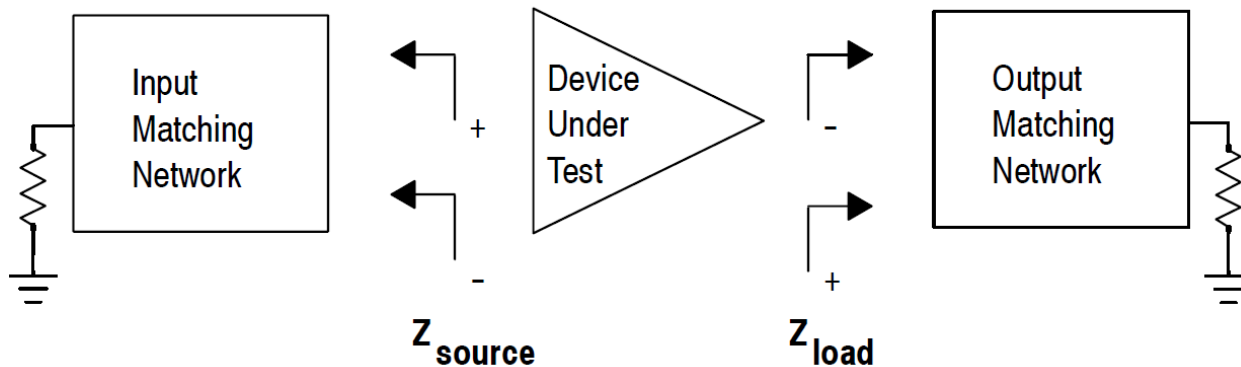

Z_{source} = Test circuit impedance as measured from gate to gate, balanced configuration.

Z_{load} = Test circuit impedance as measured from drain to drain, balanced configuration.



MAX

Measurement

MYRRHA ACCELERATOR eXPERIMENT
RESEARCH & DEVELOPMENT PROGRAMME



Frequency	Zsource (ohm)	Zload(ohm)
700	$2,2+J0,1$	$5,6+J1,2$

Gain	Pout	Compression	efficiency
19dB	575 pulse (duty 20%)	1 db	55%

Gain	Pout	Compression	efficiency
20dB	400 W CW	0,1dB	55%



MAX


Physique measurement

MYRRHA ACCELERATOR eXPERIMENT

RESEARCH & DEVELOPMENT PROGRAMME



Load 50Ohm
1KW

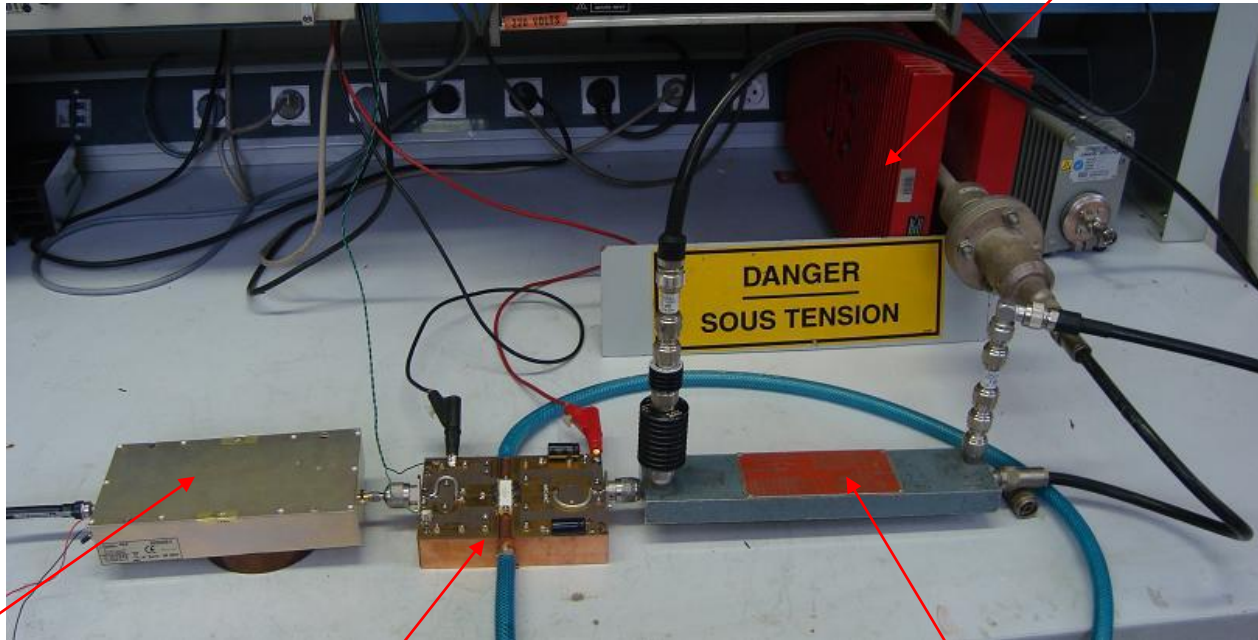

driver

amplifier

Measurement coupler

THALES




MAX

MYRRHA ACCELERATOR eXPERIMENT
RESEARCH & DEVELOPMENT PROGRAMME




RF module V2

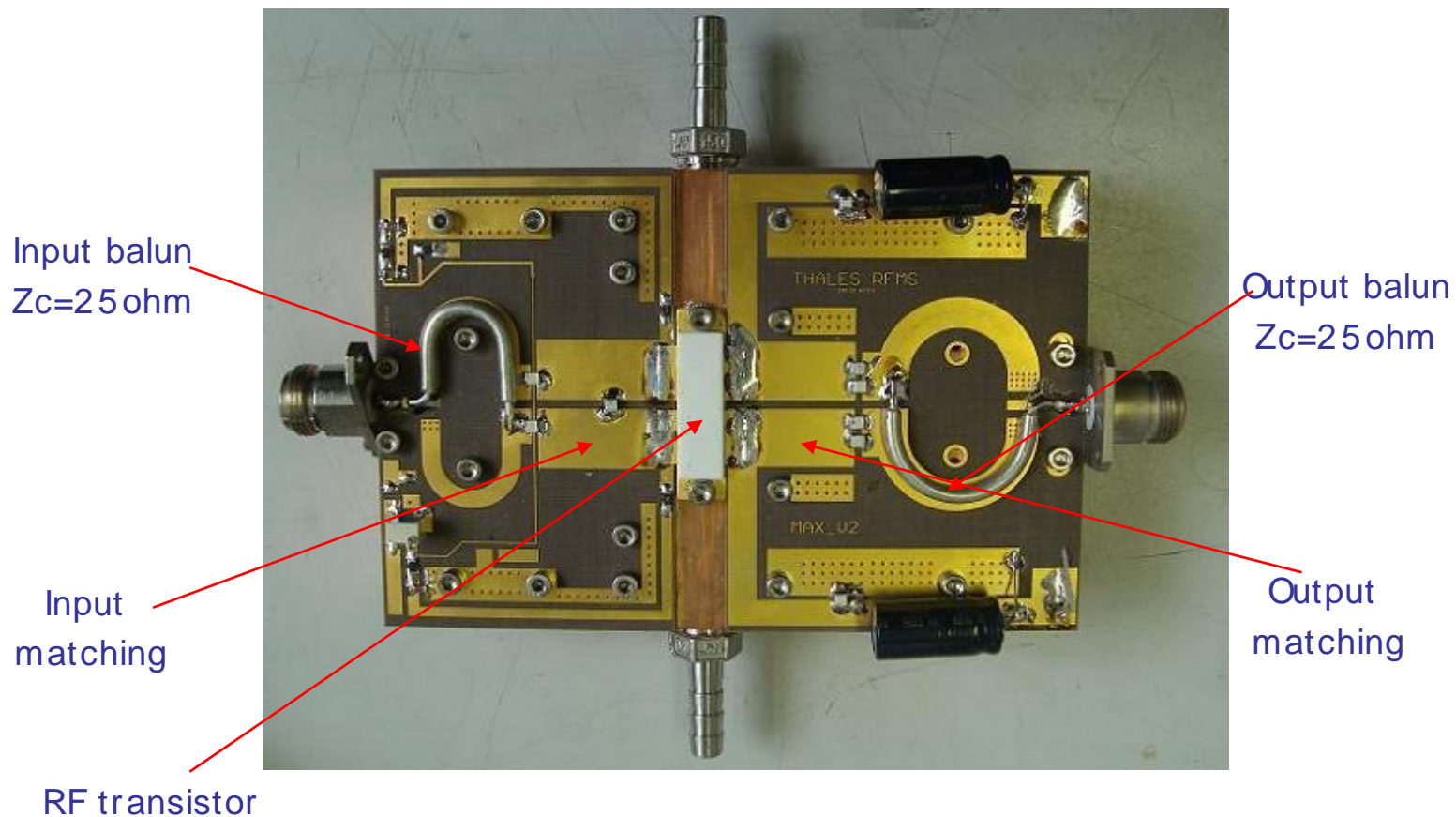



RF base Module 2x 400 CW @ 700MHz

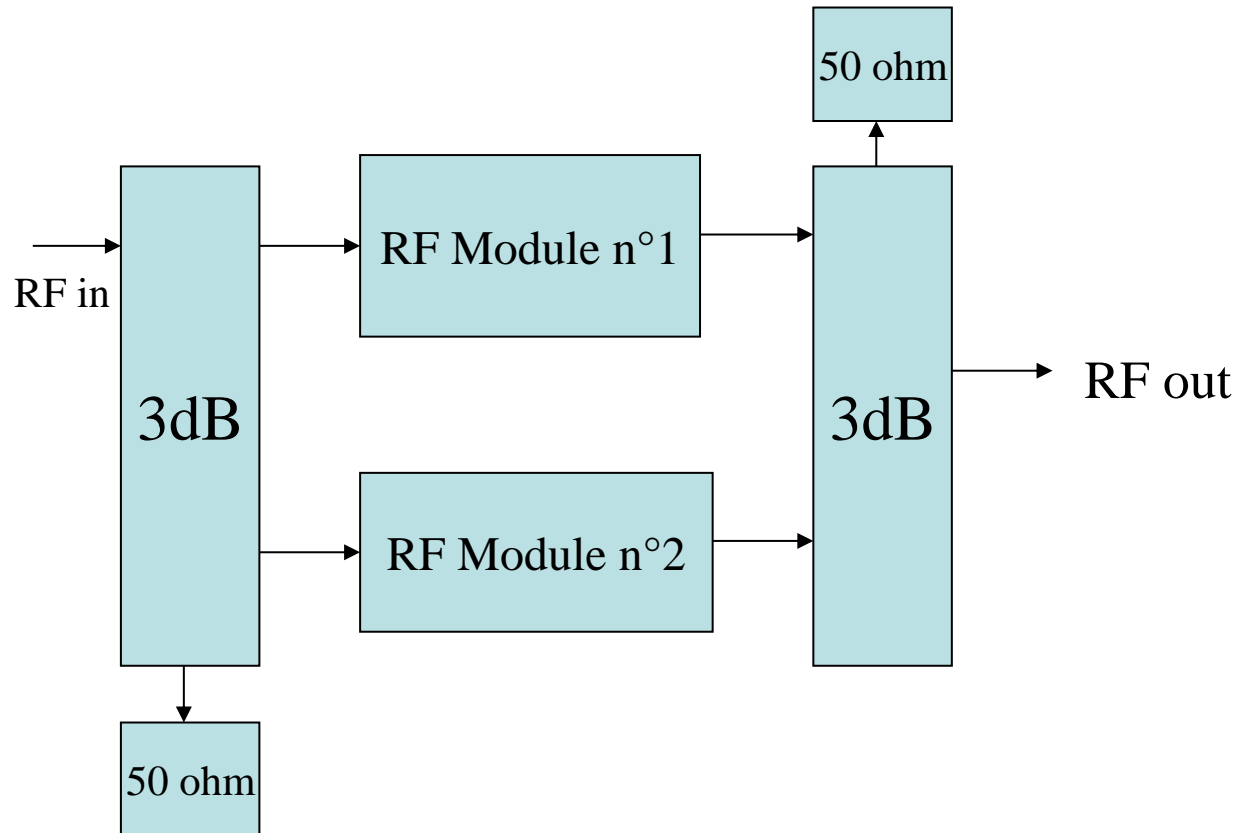



3 db micro-strip (prototype)



lost(S23,S13)	coupling (S23,S13)	Adaptation(S11,S22,S33,S44)	isolation (S12)
-0,23dB	-3,2dB	> -18 dB	>-20dB




MAX

MYRRHA ACCELERATOR eXPERIMENT
RESEARCH & DEVELOPMENT PROGRAMME



2 RF modules coupled (prototype)

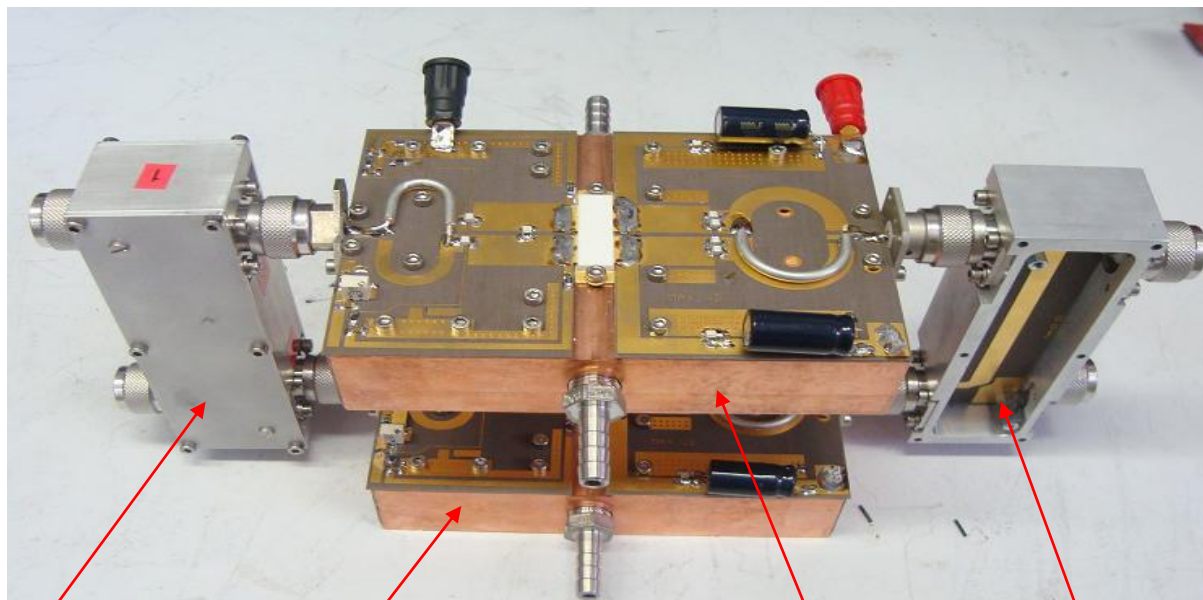

3dB coupler
Input printed

Amplifier N°1

Amplifier N°2

3dB coupler
Output printed




MAX

MYRRHA ACCELERATOR eXPERIMENT
RESEARCH & DEVELOPMENT PROGRAMME



Gain	Pout	Compression	efficiency
19,7dB	880 W pulse (duty 20%)	0,1 db	49%
19,7dB	800 W CW	0,3db	51%

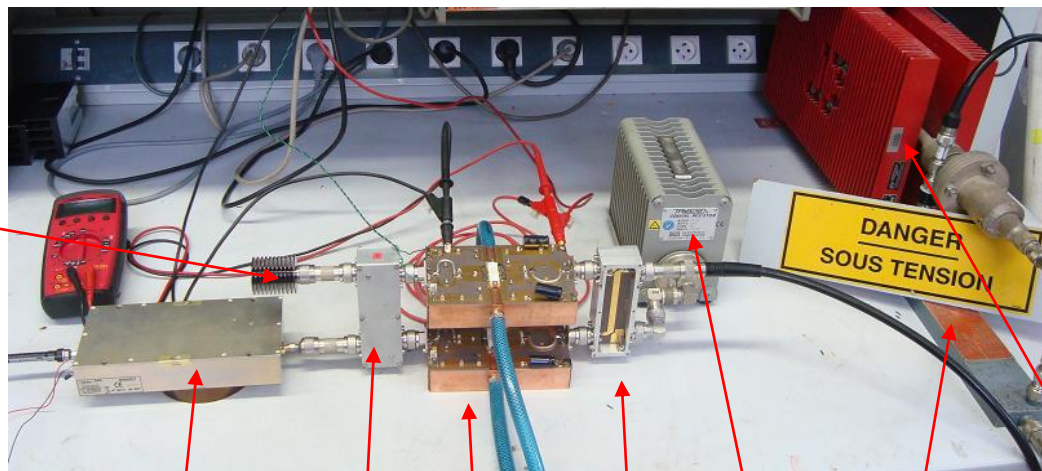

50ohm
10W

Driver

3dB coupler
Input

2x 400W
Output
amplifier

3dB coupler
Output

50ohm
500 W

Measurement
coupler

50ohm
1KW

Measurement

THALES



MAX

MYRRHA ACCELERATOR eXPERIMENT
RESEARCH & DEVELOPMENT PROGRAMME



Next possible steps

THALES




MAX

MYRRHA ACCELERATOR eXPERIMENT
RESEARCH & DEVELOPMENT PROGRAMME



Step N° 1

2 x 1.6 kW CW @ 700MHz base block

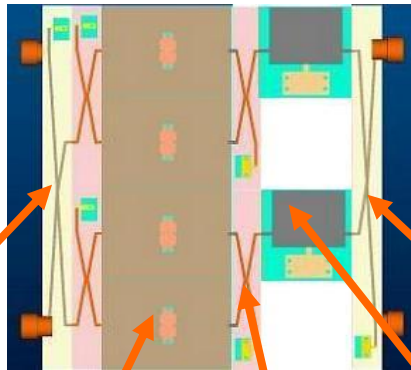

3 x splitters


4 x Base modules

1x combiner

2 x isolators

2 x « 3dB coupler »

450mm

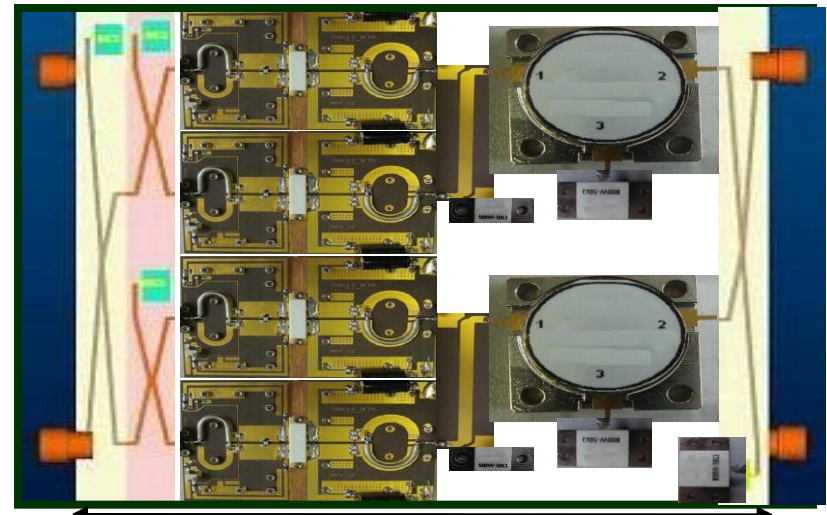

500mm

THALES




MAX

MYRRHA ACCELERATOR eXPERIMENT
RESEARCH & DEVELOPMENT PROGRAMME



Step N°2


16 kW CW @ 700 MHz base block

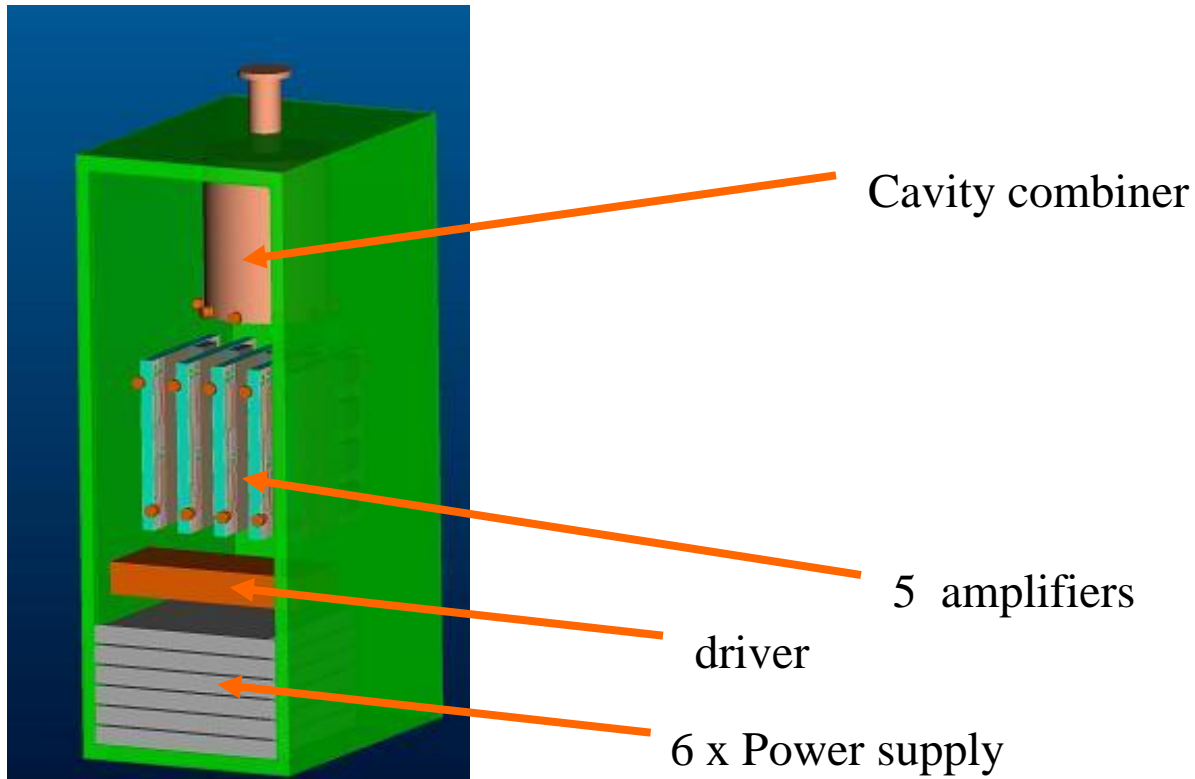



Step N°3

Pout \approx 32 kW CW @ 700 MHz

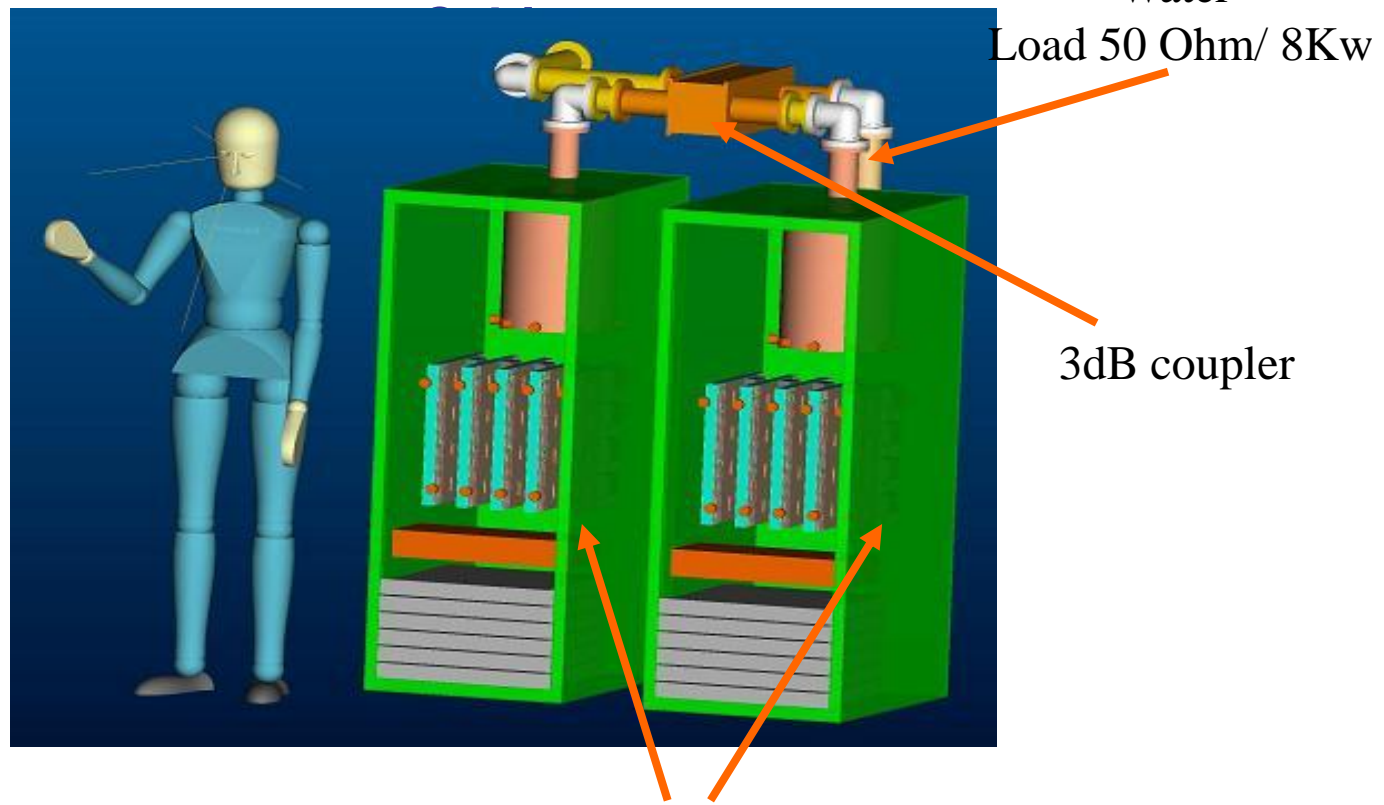



MAX

MYRRHA ACCELERATOR EXPERIMENT
RESEARCH & DEVELOPMENT PROGRAMME




Similar realizations




MAX

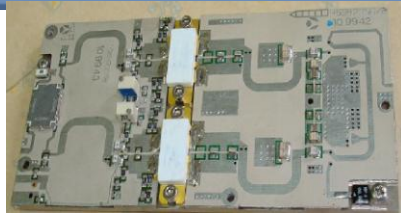MYRRHA ACCELERATOR eXPERIMENT
RESEARCH & DEVELOPMENT PROGRAMME



Individual module @ 500MHz to 800 MHz

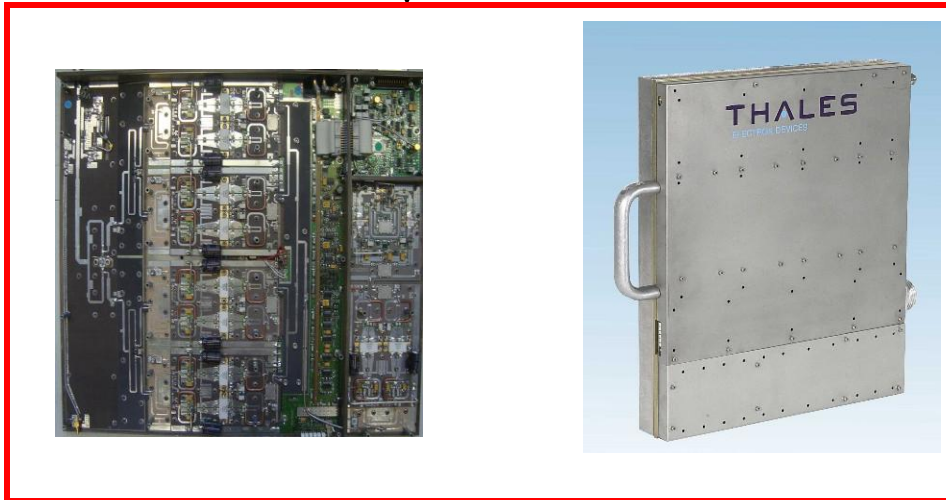

Core module 500MHz up to 800 MHz



Complete amplifier 500MHz à 800 MHz
(10KW à 30Kw)

THALES



MAX


MYRRHA ACCELERATOR eXPERIMENT
RESEARCH & DEVELOPMENT PROGRAMME



Cavity coupler



Bloc 16Kw to 32Kw

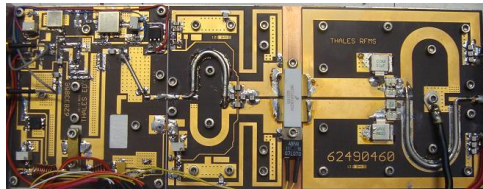

RF bloc 1Kw @ 352MHz
(RF generator integrated)



50 kW cabinet





MAX


MYRRHA ACCELERATOR eXPERIMENT
RESEARCH & DEVELOPMENT PROGRAMME



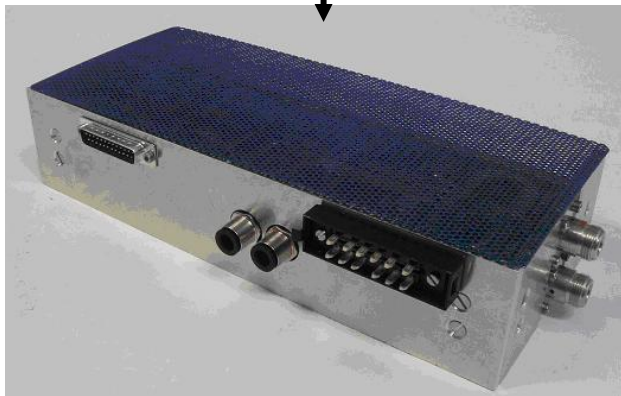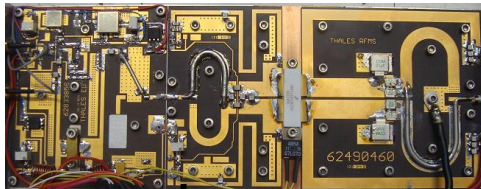
RF module 1kW @ 352MHz
Rf generator integrated



Rf module 2 x 1Kw @ 352MHz

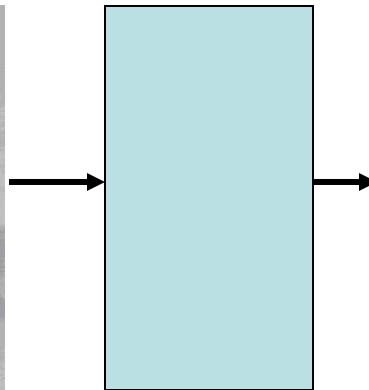

2 x 10 channels
repartition

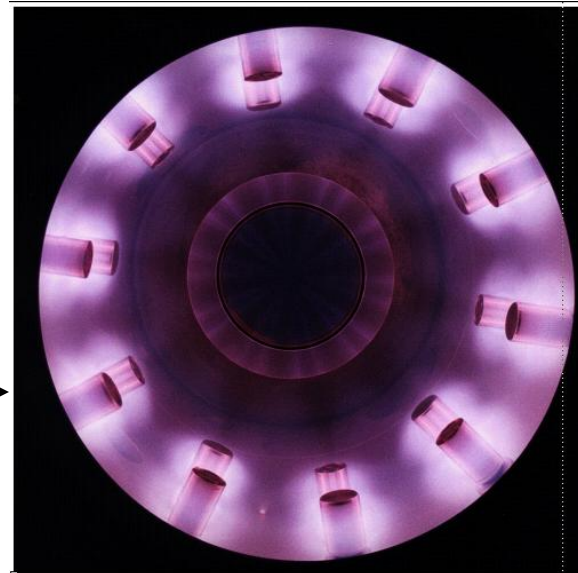

2x10 applications

THALES



MAX

MYRRHA ACCELERATOR EXPERIMENT
RESEARCH & DEVELOPMENT PROGRAMME



Thank You

THALES