



---

# Introduction to analog integrated circuit design: from schematic to layout

Patrick Pittet, Francis Calmon, Laurent Quiquerez, Rémy Cellier

2nd International Summer School on INtelligent Signal Processing for FrontIER Research and Industry

July 14th-25th, 2014, Paris Diderot University, Paris


# Introduction

---

 **Level 0: IC chip (die)**

 **Level 1: Packaged chip**

 **Level 2: Printed circuit board**


 **Level 3: Card-on-board  
(backplane)**

**Level 4: Cabinet** 


**Level 4: System** 
 
# Introduction


This lab is focused on the methodology and design flow for the design of CMOS analog integrated circuits (Full custom design).



*Schematic*

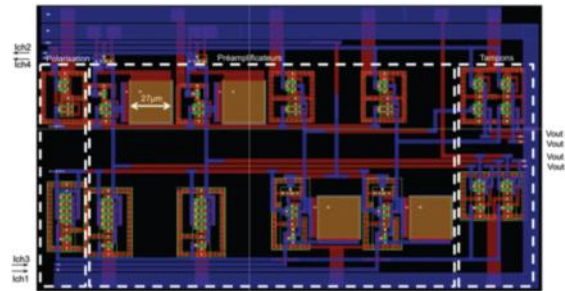



*Layout*

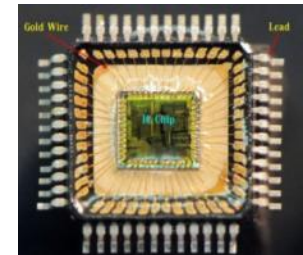

*Packaged IC*

This class implements Cadence CAD-Tools.

# Analog cell and CMOS technology

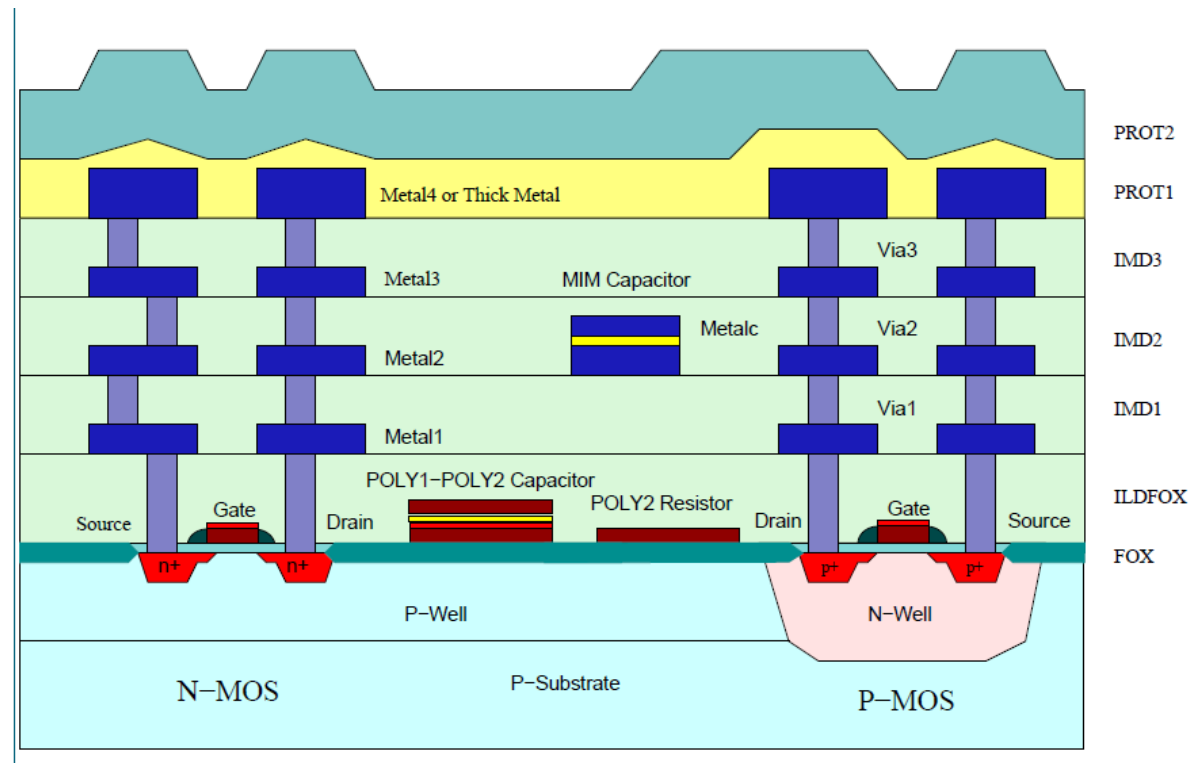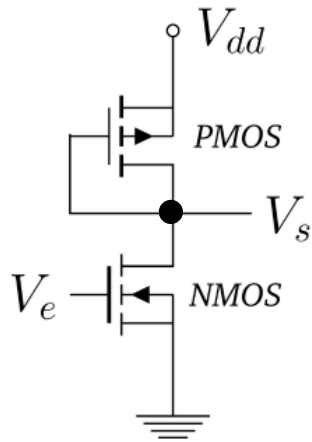


Analog cell  
(inverter)

Austriamicrosystems (AMS) 0.35  $\mu\text{m}$  CMOS

([http://cmp.imag.fr/aboutus/slides/slides2007/03\\_KT\\_AMS.pdf](http://cmp.imag.fr/aboutus/slides/slides2007/03_KT_AMS.pdf))

# IC design flows

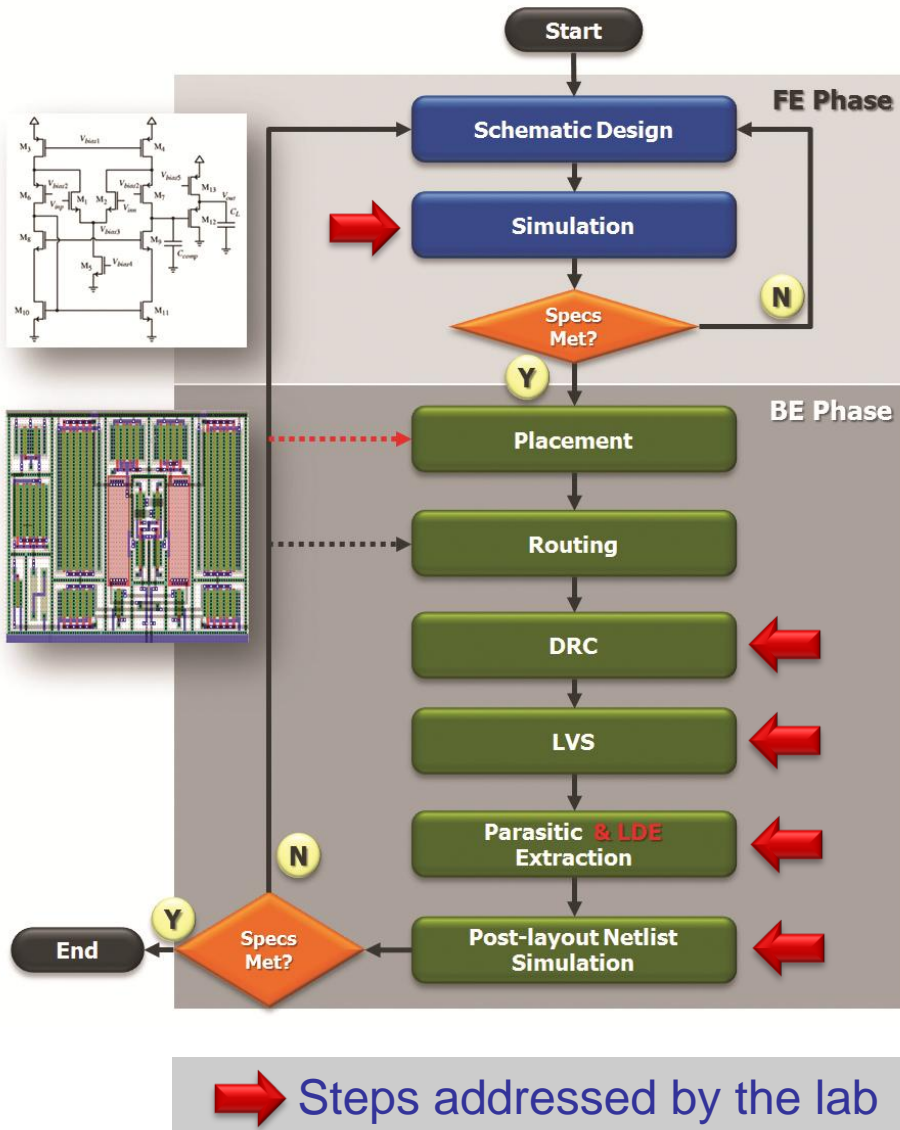

## Schematic:

- Basics design computations
- Parametric study based on static, transient, small signal simulations and noise analysis

## Layout:

- Design Rule check
- Layout versus Schematic verification
- Parasitic components extraction
- Post-layout simulation

# Design calculations

Design calculations.xlsx - Microsoft Excel

Mise en page Formules Données Révision Affichage Compléments

Calibri 11 A A

Revenir à la ligne automatiquement Standard

G I S Police Alignement Nombre

Mise en forme conditionnelle

fx

A B C D E F G H

11

12

13

14 **In the saturation region ( $|V_{GS}| > V_T$  and  $|V_{DS}| > |V_{DS,sat}|$ ):**

15

16

17

18

19

20

21

22

23

24

25

26

27

28

29

30

31

32

33

34

35

36

37

38

39

40


41

42

43

44

45

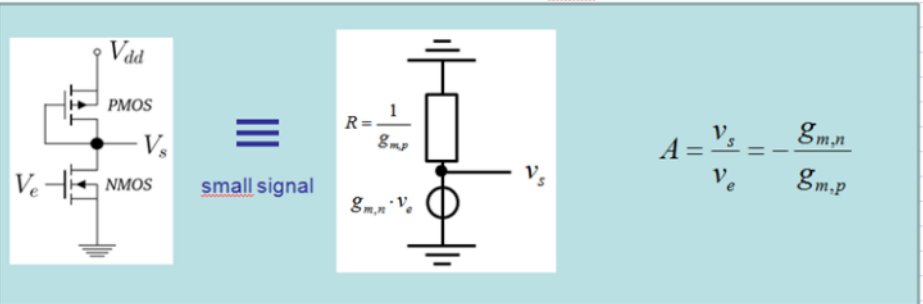

**small signal**

$$R = \frac{1}{g_{m,p}}$$

$$A = \frac{v_s}{v_e} = -\frac{g_{m,n}}{g_{m,p}}$$

$$|I_{d_p}| = \frac{K_p W_p}{2 L_p} (V_{GS_p} - V_{T_p})^2$$

$$g_{m,n} = \sqrt{2 \times K_n \times \frac{W_n}{L_n} \times I_d}$$

$$|A| = \left| \frac{v_s}{v_e} \right| = \sqrt{\frac{K_n W_n L_p}{K_p W_p L_n}}$$



$$I_{d_n} = \frac{K_n W_n}{2 L_n} (V_{GS_n} - V_{T_n})^2$$

$$g_{m,p} = \sqrt{2 \times K_p \times \frac{W_p}{L_p} \times I_d}$$



**Transistor sizes are chosen for DC bias point and AC gain achievements**

Typical Technological parameters @3.3V			
Vdd	3,3	Ve (V)	0,55
Kp	58	Vs (V)	2,6
Vtp	0,65	Ln (μm)	0,35
Kn (μA/V <sup>2</sup> )	170	Wn (μm)	10
Vtn (V)	0,5	Lp (μm)	0,35
		Wp (μm)	29
		Idp (μA)	6,1
		Idn (μA)	6,1
		Gain	-1


# Simulations

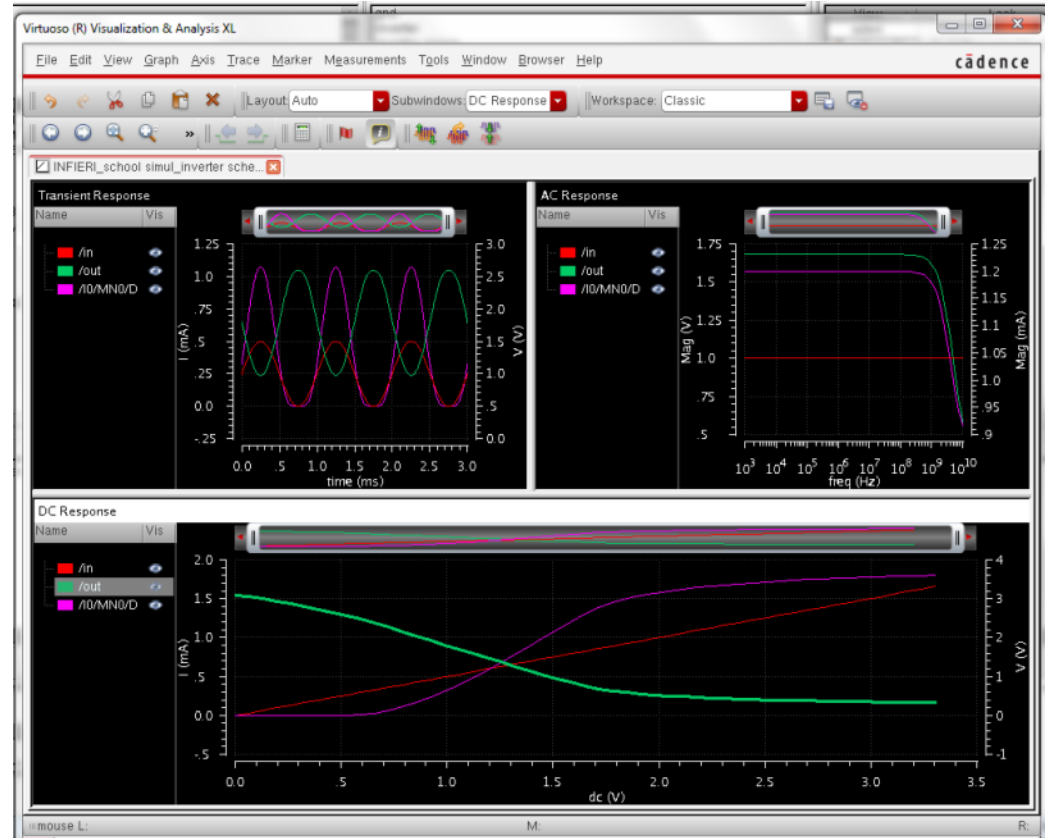 

# Layout

  


(a) Transistor NMOS

 



 
# Process and Mismatch simulations

- Wafer production will always show some variation of technological parameter



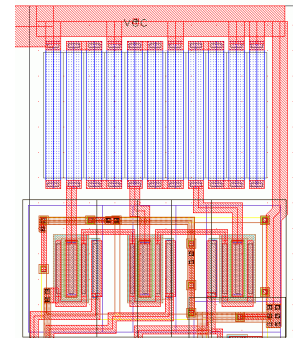- Mismatch on design parameters components



=> Monte-Carlo Process and Mismatch simulations will be run

