



Design and Measurements of the Inductive Adder Pulser

J. Holma

CERN TE/ABT, Geneva, Switzerland

Acknowledgement M.J. Barnes
CERN



Overview

➤ Background

- CLIC Layout with Damping Ring (DR) kickers
- Specifications for CLIC DR Extraction Kicker System
- Challenges and Issues


➤ Inductive Adder Design

- Schematic
- Contributors to the Droop of the Output Waveform
- Compensation of Droop and Ripple
- Specifications for the First Prototype Inductive Adder



➤ Measurements on the Prototype Inductive Adder

- 3.5 kV Pulses w/o Modulation
- Passive Droop Compensation
- Active Droop Compensation
- Active Compensation of Droop and Ripple

➤ Summary and Future Work

 


Ideal stripline current for 1 GHz option

  



CLIC General Layout

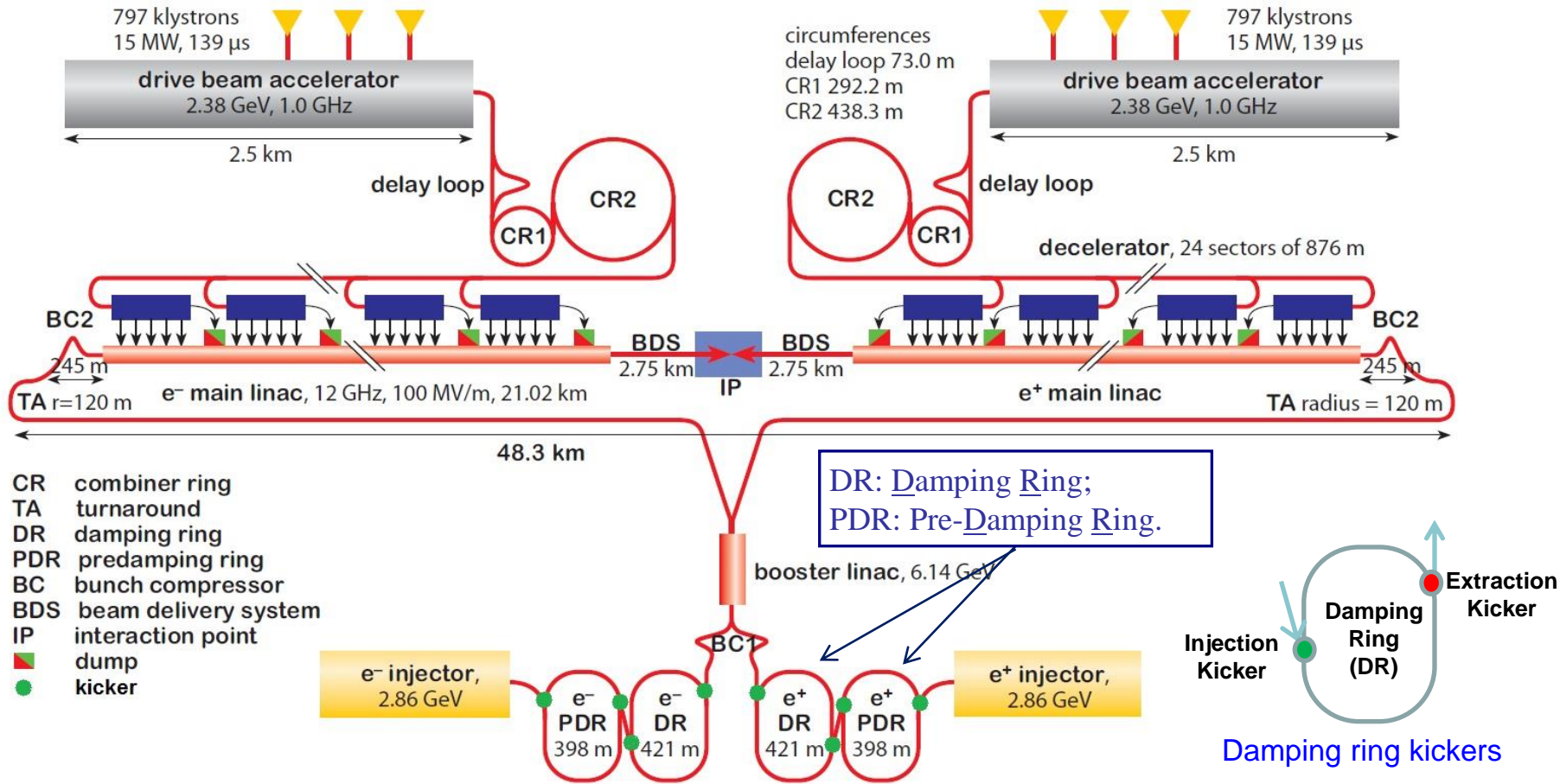

PDR & DR Kickers (●):

- One injection and extraction system per ring and per beam (8 systems);
- Damping rings reduce beam emittance; hence kickers must be high stability (low ripple);
- Low beam coupling impedance and good field homogeneity are required (talk by C. Belver-Aguilar).





Specifications for the CLIC DR Extraction Kicker Systems


	CLIC DR (1 GHz 2 GHz)
Pulse voltage (kV) (per Stripline)	± 12.5
Stripline pulse current [50 Ω load] (A)	± 250
Repetition rate (Hz)	50
Pulse flat-top duration (ns)	~ 160 ~ 900
Flat-top reproducibility	$\pm 1 \times 10^{-4}$ (± 0.01 %)
Flat-top stability [inc. droop], (Inj.) per Kicker SYSTEM (Ext.)	$\pm 2 \times 10^{-3}$ (± 0.2 %) $\pm 2 \times 10^{-4}$ (± 0.02 %)
Field rise time (ns)	1000
Field fall time (ns)	1000
Beam energy (GeV)	2.86
Total kick deflection angle (mrad)	1.5 (0.09 deg)
Aperture (mm)	20
Effective length (m)	1.7
Field inhomogeneity (%) [3.5mm radius] [1mm radius]	± 0.1 (Inj.) ± 0.01 (Ext.)

NOTE:

  
- For rise/fall times, ≤ 100 ns desired!
- Close to 0 V intra-pulse (off-time) voltage required!



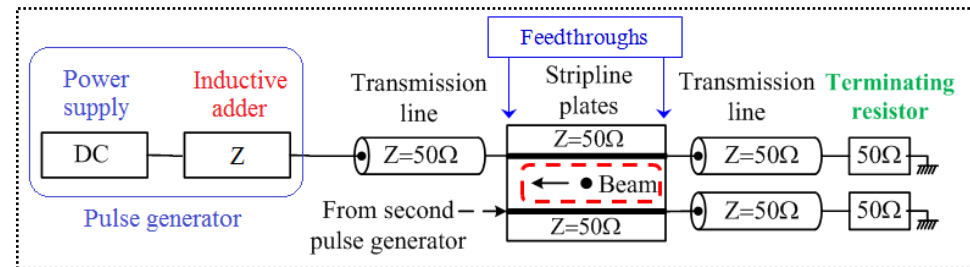Drawing of the CLIC DR extraction kicker
(Courtesy of C. Belver-Aguilar)




Schematic of a kicker system

 


CLIC DR kicker pulse definition

Challenges and Issues

 


CLIC DR kicker pulse definition

 

Schematic of a kicker system


- **$\pm 0.02\%$ ($\pm 2.5\text{ V}$) requirement for the flat-top stability of $\pm 12.5\text{ kV}$, 160 to $\sim 900\text{ ns}$ pulse is an extremely demanding specification!**
 - **An order of magnitude better than in any existing kicker systems!**
 - **Compensation of droop and ripple of the output voltage is required.**
- Adequate impedance matching to minimize duration of settling time:
 - Impedance (and field homogeneity) of the stripline kicker has been optimized: unfortunately the impedance cannot be $50\ \Omega$ for both power-off (even) and power-on (odd) operation modes!
 - Odd-mode impedance of the striplines is $\sim 41\ \Omega$ (see talk by C. Belver-Aguilar), which causes settling time to be $\sim 100\text{ ns}$. Therefore **the pulse flat-top duration is at least $\sim 260\text{ ns}$ (2 GHz option)**
- Suitable high precision measurements of the pulse in the laboratory:
 - better relative precision than $\pm 2.5\text{ V}$ in 12.5 kV required!**

 




Inductive Adder

- Many primary “layers”, each with solid-state switches
- The output voltage is approximately the sum of the voltages of the primary constant voltage layers
- + Control electronics referenced to ground
- + No electronics referenced to high voltage despite the high voltage output of the adder
- + The output voltage can be modulated during the pulse with an analogue modulation layer
- + Modularity: the same design can potentially be used for kickers with different specifications (CLIC PDR & DR kicker modulators)
- + Redundancy and machine safety: if one switch or layer fails, the adder still gives full voltage or a significant portion of the required output pulse
- + Possibility to generate positive or negative output pulses with the same adder: the polarity of the pulse can be changed by grounding the other end of the output of the adder

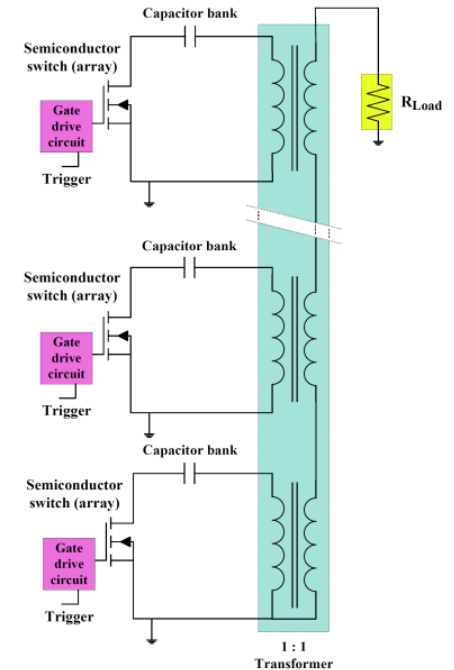


Schematic of an inductive adder

 


A prototype inductive adder

Contributors to the Droop of the Output Waveform of an Inductive Adder


- The droop of the output pulse of an inductive adder is caused by:
 - The small voltage droop of the storage capacitor (C_s) as it supplies charge during the pulse
 - The resistive losses in the primary switch and in the primary circuit (R_{sw}), which depends on the current through the magnetizing inductance (L_m).
- **Only the voltage droop of the capacitors can be compensated by adding more capacitance per layer!**
- **The only methods to effectively decrease the droop, caused by a combination of resistive losses and magnetizing inductance of the transformer core, is to apply either passive or active analogue modulation (or both) for the output pulse.**
- **These methods are necessary to reach very low droop ($\ll 1\%$).**

 

 Simplified schematic of a constant voltage layer of an inductive adder



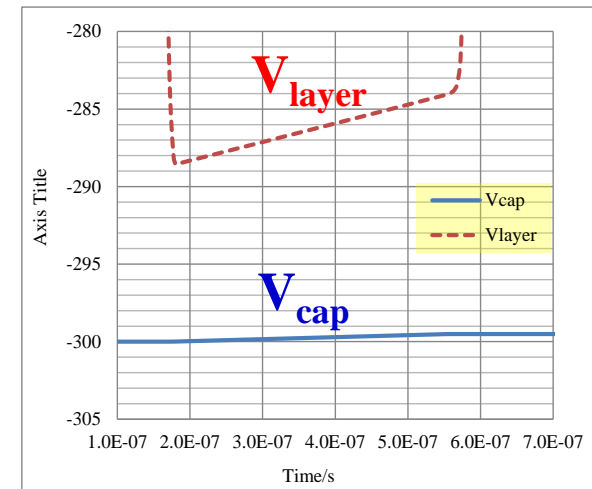Simplified model of a layer of an inductive adder during the pulse




Capacitor voltage V_{cap} and voltage of a layer V_{layer} during a pulse. $C_s = 24 \mu F$, $R_{sw} = 0.34 \Omega$ and $R_{load}/N = 10 \Omega$.

Compensation of Droop and Ripple

- In analogue modulation layer, there is no storage capacitor but there is resistor R_a
- Resistor R_a is effectively in series with the load
- Load voltage during the flat-top:


$$V_{Load} \approx \frac{R_{Load}}{R_{Load} + R_a} V_{Max}$$

- V_{Max} is the sum of the voltages over the layers except the analogue modulation layer: $V_{Load} \leq V_{Max}$!
- Resistor R_a is in parallel with magnetizing inductance L_m
- Compensation modes:
 - **PASSIVE MODE:** During the pulse, current through L_m increases, which causes current through R_a to decrease. Therefore, voltage over R_a decreases, which causes V_{Load} to increase. This voltage change is reverse in comparison with voltage droop caused by storage capacitors in other layers.
 - **ACTIVE MODE:** A linear RF power transistor provides a shunt path for the current through resistor R_a . Therefore, the voltage over R_a can be controlled by controlling the current through the RF power transistor.

 




Compensation of Droop and Ripple

 

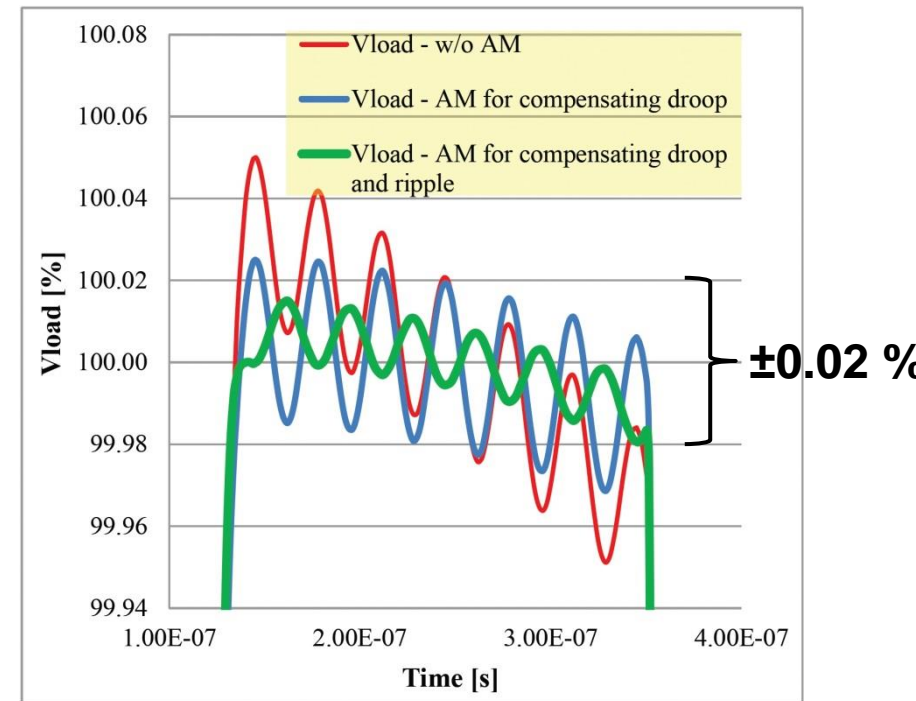Simulated droop compensation with passive analogue modulation



Simulated droop and ripple compensation with active analogue modulation

- **Passive analogue modulation – partial droop compensation**
- **Active analogue modulation – partial droop and ripple compensation**
- **For the CLIC DR kicker modulator, both PASSIVE and ACTIVE modulation methods will be applied!**




A 5-Layer Prototype Inductive Adder

- The purpose of the prototype inductive adder has been:
 - To verify experimentally design steps for the high precision inductive adder
 - To test both passive and active analogue modulation
 - To approach the required ± 0.02 % flat-top stability for the output pulse, as specified for the CLIC DR extraction kicker modulator


Design Parameter	Prototype Inductive Adder	CLIC DR Extraction Kicker Modulator
Output Voltage (kV)	3.5	12.5
Output Current [50 Ω load] (A)	70 (250)	250
Voltage per layer	700	700
Number of layers	5	20
Pulse flat-top duration (ns)	*350 (900)	160 – 900
Pulse rise time [0.1-99.9 %] (ns)	100	< 1000
Pulse fall time [0.1-99.9 %] (ns)	100	< 1000
Flat-top stability (for 160 ns)	± 0.02 %	± 0.02 %
Repetition rate (Hz)	50	50

 * limited by transformer cores, design value 900 ns




The prototype inductive adder with two half-layers inserted

 Measurements on the 5-Layer Prototype Inductive Adder




The prototype inductive adder with the measurement setup

 Measurements on the 5-Layer Prototype Inductive Adder



**CURRENT
TRANSFORMER**

 The prototype inductive adder with a current transformer and a load



**In initial measurements,
only one branch per
half-layer PCB was
powered!
2 branches per layer.**




Measurements: 3.5 kV Output Pulse - No Modulation

■ Setup for the measurement:

- The prototype adder with 5 layers
- 1 branch powered per half-layer PCB, 2 branches per layer
- Capacitors ($24 \mu\text{F}/\text{layer}$) charged initially to 750 V
- 50Ω , 18 kV load by Diconex
- No modulation applied.

■ Output pulse parameters



 
- Output voltage: 3.5 kV
- Rise time (0.1...99.99 %) 160 ns
- Droop: $\sim 3.4 \%$ (120 V) for 170 ns flat-top duration
- Small intra-pulse voltage ($\sim 10 \text{ V}$).



Measurements: Passive Compensation of Droop and Active Compensation of Droop and Ripple


■ Setup for the measurement:

 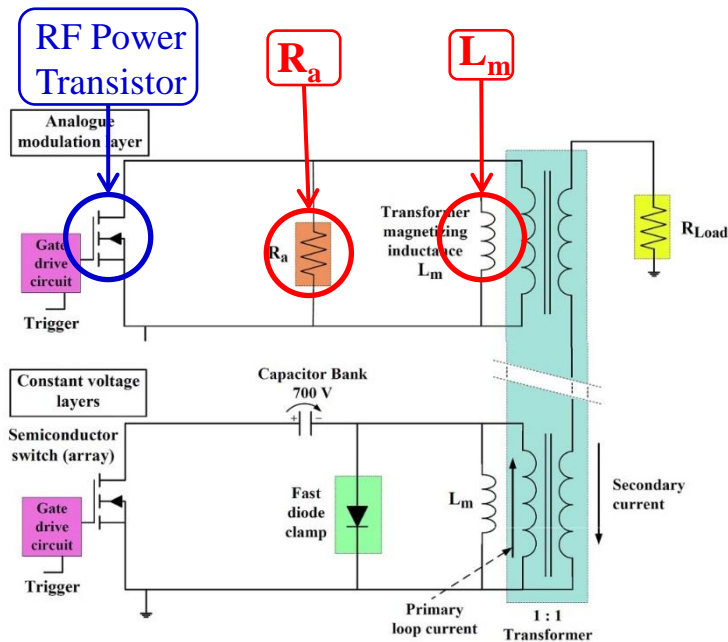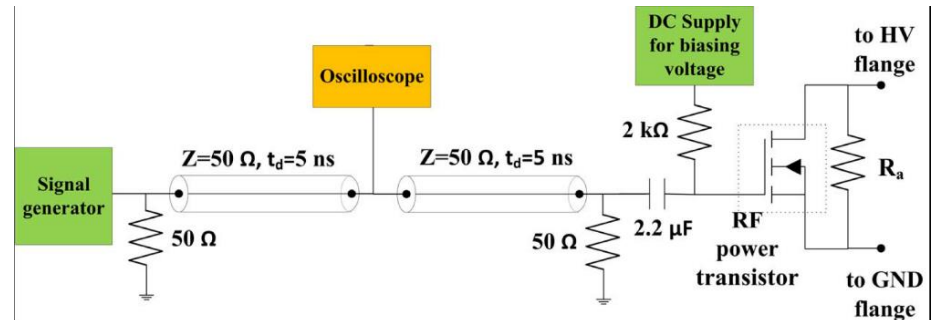- The prototype adder with 4 constant voltage layers and an analogue modulation layer
- 1 branch powered per half-layer PCB, 2 branches per layer
- Capacitors (24 $\mu\text{F}/\text{layer}$) charged initially to 350...553 V.
- Passive or active analogue modulation applied



Schematic and layout of the active analogue modulation layer

Measurements: Passive Droop Compensation

 


Setup for the measurement:

- 4 constant voltage layers and a passive analogue modulation layer
- 1 branch powered per half-layer PCB, 2 branches per layer
- Capacitors ($24 \mu\text{F}/\text{layer}$) initially charged to 350 V ($R_a = 7.9 \Omega$)

Notes:

- Tektronix scope used (DPO 5034) has a nominal vertical resolution of 8 bits ($< \pm 0.4\%$) – can be improved with oversampling and averaging
- The curve is an average of 1000 measured pulses
- **The optimal combination of R_a & L_m depends on the output voltage!**

Measurements: Active Droop Compensation

 


Setup for the measurement:

- 4 constant voltage layers and a passive analogue modulation layer
- 1 branch powered per half-layer PCB, 2 branches per layer
- Capacitors ($24 \mu\text{F}/\text{layer}$) initially charged to 551 V ($R_a = 7.9 \Omega$)
- Active droop compensation with piece-wise linear ramp function

Notes:

- The curve is average of 1000 measured pulses
- Repeat of the measurement with averaging of 4000 pulses resulted in $\pm 1.17 \text{ V}$ ($\pm 0.06 \%$)!

Measurements: Active Ripple Generation

 

Setup for the measurement:

- 4 constant voltage layers and a passive analogue modulation layer
- 1 branch powered per half-layer PCB, 2 branches per layer
- Capacitors ($24 \mu F/\text{layer}$) initially charged to 200 V ($R_a = 7.9 \Omega$)
- Active ripple generation with a **positive ramp (blue)** and **2 MHz (red)**, **10 MHz (purple)** and **30 MHz (green)** sine waves.



Note:

- **Modulation range: ~10 % of the maximum output voltage**




Measurements: Active Ripple Compensation

- **Setup for the measurement:**
 - The prototype adder with 5 layers
 - 1 branch powered per half-layer PCB, 2 branches per layer
 - Capacitors (24 μF /layer) charged initially to 551 V
 - Active analogue modulation layer
 - Modulation signal: a ramp + a sine wave with a frequency of 5...25 MHz.
- **Steps for active ripple compensation**
 - Gain and phase responses for the injected compensation signal from the signal generator to the load voltage were measured
 - Correction factor were defined for compensation signal
 - Load voltage was measured
 - Fast Fourier Transformor (FFT) was applied to define the most significant ripple components
 - A compensation signal, consisting of ramp to compensate the droop and a sine wave to compensate the most significant ripple component was created.
 - The compensation signal was applied and the load voltage was measured.

 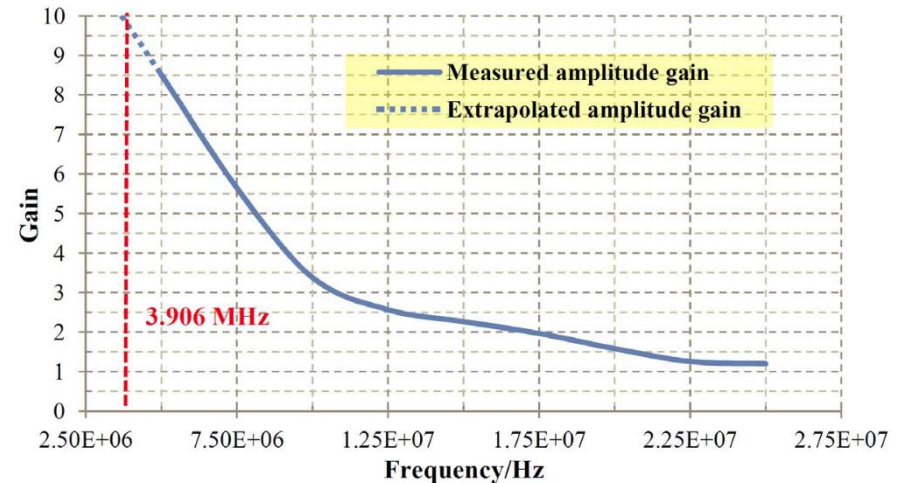

Measurements: Active Ripple Compensation

 

Setup for the measurement:

- 4 constant voltage layers and a passive analogue modulation layer
- 1 branch powered per half-layer PCB, 2 branches per layer
- Capacitors (24 μF /layer) initially charged to 551 V ($R_a = 7.9 \Omega$)
- Active droop and ripple compensation

Notes:

- The curve is an average of 1000 measured pulses
- Repeat of the measurement with averaging of 4000 pulses resulted in $\pm 1.02 V$ ($\pm 0.06\%$)!




Evaluation of Accuracy of the Measurements

- The effective bit length of a 8-bit ADC is 6-7 bits.
- The effective bith length of the oscilloscope can be increased with the following means
 - Oversampling (OS)
 - Ensemble averaging (EA)
 - **Both these methods were applied**
- **Accuracy of the measurements**
 - **Active droop compensation:**
 - The best measurements: **$\pm 0.06 \%$ ($\pm 1.17 \text{ V}$)**
 - The effective number of bits of the ADC: **6** (effective length of bits) + **1** (OS,4x) + **6** (EA,4k) = **13**
 - Absolute precision: **0.37 V** (in the range of 3 kV)
 - **Active droop and ripple compensation:**
 - The best measurements : **$\pm 0.05 \%$ ($\pm 0.96 \text{ V}$)**
 - The effective number of bits: **6** + **1** (OS,4x) + **5** (EA,1k) = **12**
 - Absolute precision: **0.73 V** (in range of 3 kV).
 - With EA of 4k, the numbers were $\pm 0.06 \%$ ($\pm 1.02 \text{ V}$), 13 bits and 0.37 V.


Mod. method	PM (d)	AM (d)	AM (d&r)
$\Delta U_{d+r} (\%)$	± 0.16	± 0.07 (1k) ± 0.06 (4k)	± 0.05 (1k) ± 0.06 (4k)
$\Delta U_{d+r} (\text{V})$	± 1.9	± 1.23 (1k) ± 1.17 (4k)	± 0.96 (1k) ± 1.02 (4k)
$\text{Res}_{\text{Enh,OS}}$ (bits)	0	1 1	1 1
Averaging (n)	100	1000 4000	1000 4000
$\text{Res}_{\text{Enh,EA}}$ (bits)	3.3	5 (1k) 6 (4k)	5 (1k) 6 (4k)
$V_{r,\text{ADC}} (\text{V})$	2000	3000 (1k) 3000 (4k)	3000 (1k) 3000 (1k)
$\text{Res}_{\text{Rel}} (\%)$	0.16	0.024 (1k) 0.012 (4k)	0.024 (1k) 0.012 (4k)
$\text{Res}_{\text{Abs}} (\text{V})$	3.2	0.73 0.37	0.73 0.37

ΔU_{d+r} = combined droop and ripple (flat-top instability), $\text{Res}_{\text{Enh,OS}}$ = resolution enhancement by oversampling (averaging of samples), $\text{Res}_{\text{Enh,EA}}$ = resolution enhancement by ensemble averaging (averaging of pulses), V_r = voltage range of a measurement channel, Res_{Rel} = relative accuracy, Res_{Abs} = absolute accuracy

- Two 5-layer, 3.5 kV prototype inductive adders have been built and tested at CERN
- Both passive and active analogue modulation methods tested to improve the flat-top stability of the output pulses
- The best measured flat-top stability for 160 ns pulse flat-top has been $\pm 0.05\%$ ($\pm 0.96\text{ V}$) at 1.8 kV, which was reached by applying active droop and ripple compensation.
- The final goal is to reach the stability requirement for the CLIC DR extraction kicker modulator ($\pm 0.02\%$)
- **The full-size 12.5 kV, 250 A, CLIC DR kicker prototype inductive adders are currently being designed at CERN**
- The design of 12.5 kV inductive adders is based on the design of the two 5-layer prototype inductive adders.

 










- Improve the precision of the active analogue modulation, to meet ± 0.02 % requirement for the combined droop and ripple:
 - Measurements with new magnetic cores, pulse duration up to 900 ns
 - A new active analogue modulation layer with improved precision of ripple compensation (an RF amplifier between the RF MOSFET and a signal generator)
 - Measurements with a 16-bit oscilloscope
- Measurements of two 12.5 kV inductive adders with a stripline kicker installed in a beamline in an accelerator test facility
- Other possible applications for inductive adder technology at CERN:
 - FCC kicker systems (20 kV, 3.6 kA, 2.5 μ s)
 - PS KFA kicker system (40 kV, 1.5 kA, 2.6 μ s)

 

3D model of a future inductive adder at CERN (Courtesy of P. Faure)



Questions & Comments?

         



References and Bibliography

1. Holma J., Barnes M.J.: "The Prototype Inductive Adder With Droop Compensation for the CLIC Kicker Systems.", IEEE Trans. Plasma Sci., Vol. 42, No. 10, Oct. 2014.
2. Holma J., Barnes M.J., Belver-Aguilar C.: "Measurements on a Prototype Inductive Adders with Ultra-flat-top Output Pulses for CLIC Kicker Systems", Proc. IPAC'14, Dresden, Germany, June 15-20, 2014.
3. Holma J., Barnes M.J.: "Initial Measurements on a Prototype Inductive Adder for the CLIC Kicker Systems", Proc. of PPC'13, San Francisco, CA, USA, June 16-21, 2013.
4. Holma J., Barnes M.J., Ovaska S.J.: "Modelling of Parasitic Inductances of a High Precision Inductive Adder for CLIC", Proc. of IPAC'13, Shanghai, China, May 12-17, 2013.
5. Holma J., Barnes M.J.: "Sensitivity Analysis for the CLIC Damping Ring Inductive Adder", Proc. of Int. Power Modulators and High Voltage Conference, San Diego, CA, USA, Jun. 3-7, 2012.
6. Holma J., Barnes M.J.: "Evaluation of Components for the High Precision Inductive Adder for the CLIC Damping Rings", Proc. of IPAC 2012, New Orleans, USA, May 20-26, 2012.
7. Holma J., Barnes M.J.: "Pulse Power Modulator Development for the CLIC Damping Ring Kickers", CLIC-Note-938, CERN, Geneva, Switzerland, April 27, 2012.



Spare Slides



Demonstration of Active Ripple Compensation in Time and Frequency Domains

Time domain

- Original waveform: load voltage with ramp compensation applied (blue)
- Compensated waveform (green): the droop and the most significant ripple frequency has been compensated
- A ripple component deliberately amplified (red): the most significant ripple component has been amplified (phase shift of the ripple component -180 degrees in comparison with the green curve)

Frequency domain

- Magnitudes of FFTs of the original load voltage (blue), ripple compensation applied (green) and a ripple component amplified (red).
- FFT of original waveform: load voltage with ramp compensation applied (blue)
- FFT of compensated waveform (green): the droop and the most significant ripple frequency has been compensated
- FFT of a the waveform in which a ripple component has been amplified (red): phase shift of a ripple component -180 degrees in comparison with the green curve

