




Computer-based Modelling and Experimental Optimization of Power Supplies




Agenda

TOPICS:

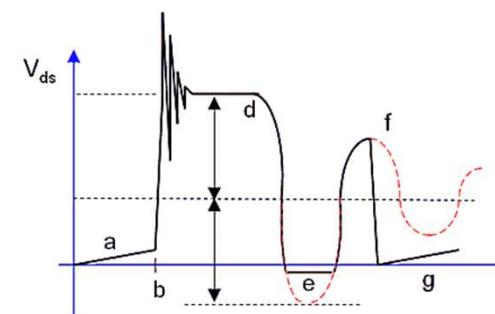


ref. 1

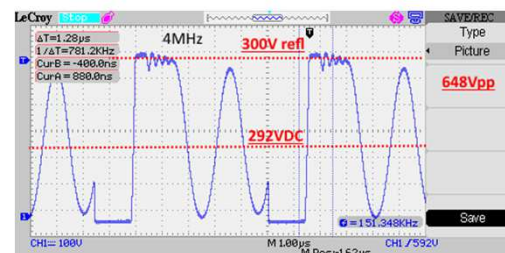



Everything Looks Better But

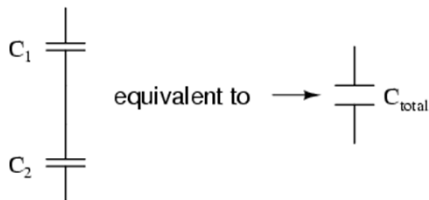- ❑ 30 kV OEM cap. charger
- ❑ Prototype evaluation
- ❑ Safe background
- ❑ Auxiliary PSU
- ❑ 1T Forward Converter
- ❑ Reflected impedance by N^2





Series Capacitances

$$C_{total} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}}$$

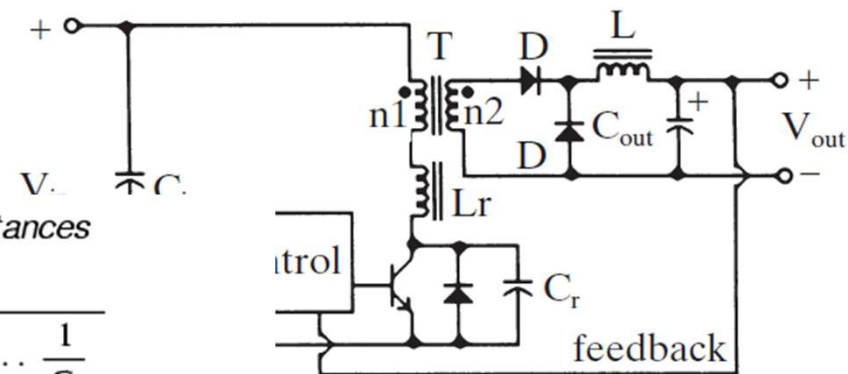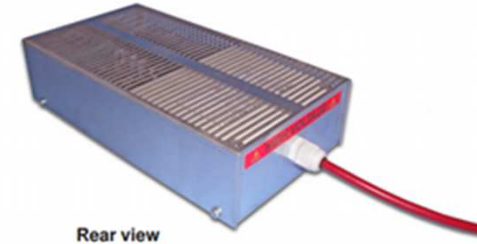


ref. 2

Linear Power Supply Design

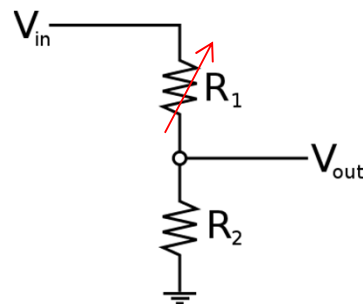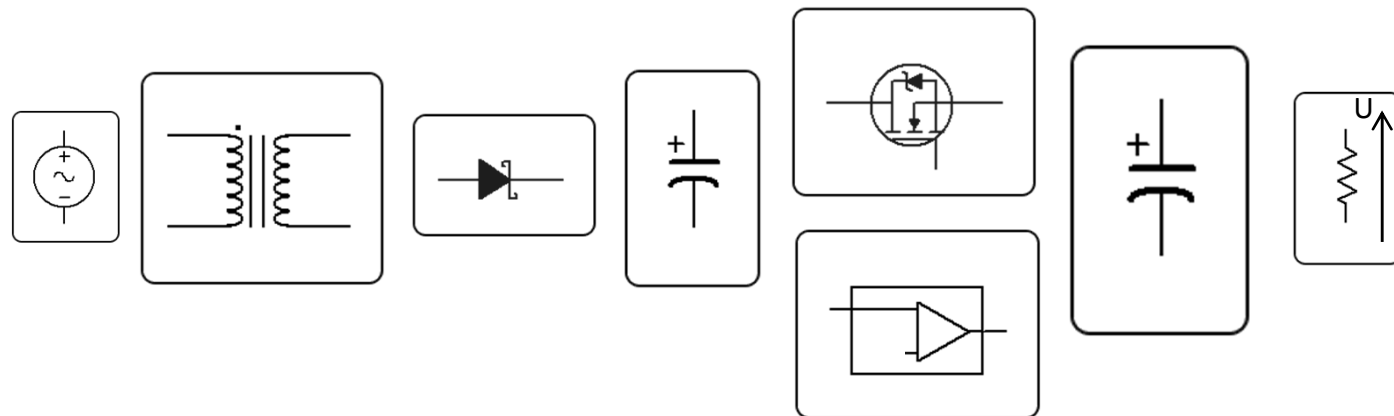

WHY DO WE WANT TO BUILD A SWITCHING POWER SUPPLY

Switching Power Supply Design

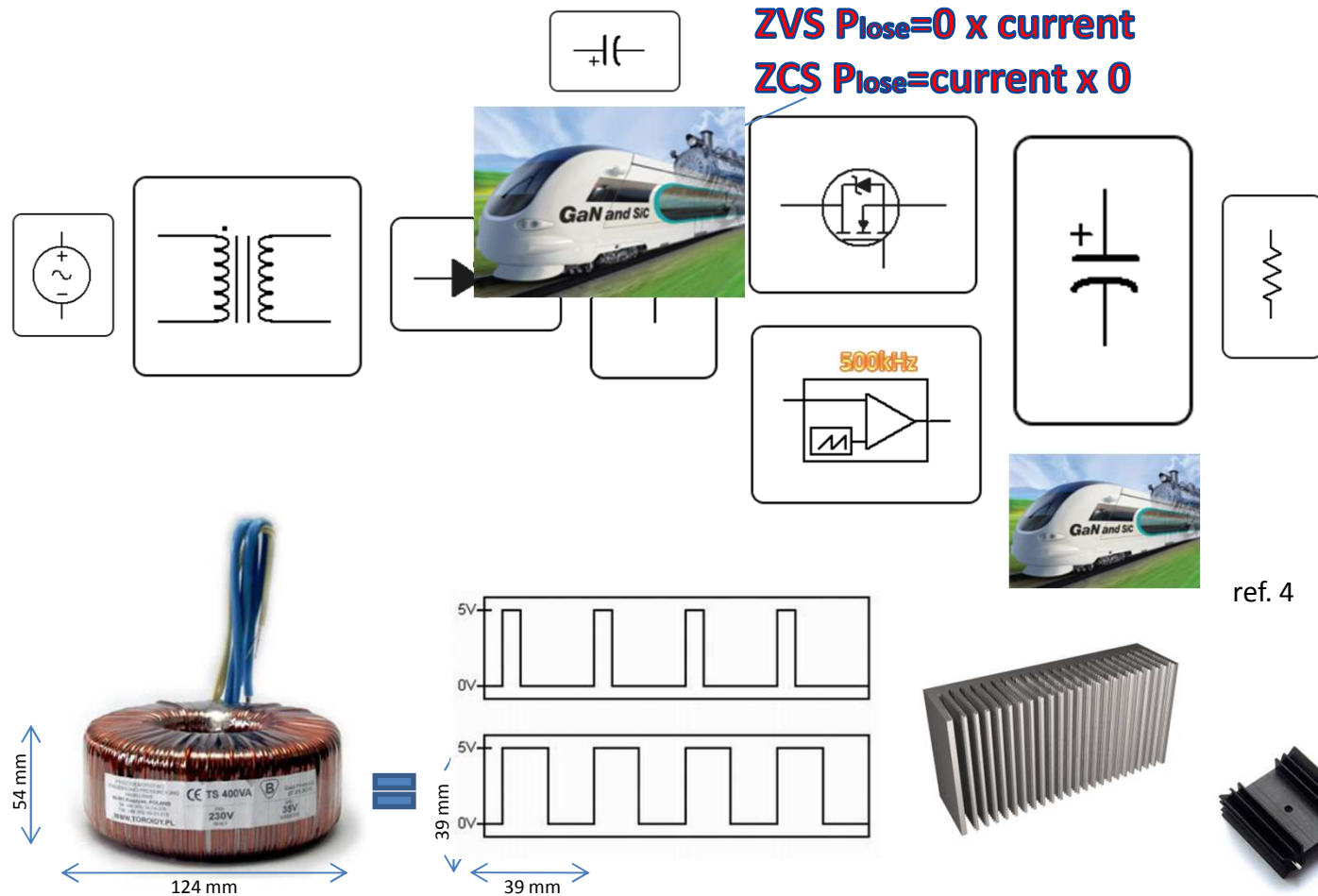

Everything Looks Better But


- ❑ Reliability
- ❑ Safety
- ❑ Development Time
- ❑ Custom Magnetic
- ❑ EMI
- ❑ Testing and Qualification
- ❑ Required Design Expertise.




ref. 5

Linear or Switching Supply?

- ❑ **Linear:** Low ripple and noise specification
- ❑ **Linear:** fast transient response
- ❑ **Linear:** inefficient and generates heat
- ❑ **SMPS:** Efficient, can generate noise
 - ❑ SMPS: noise V_{pp} from 20Hz to 20MHz
- ❑ **QR SMPS:** ZVS improves ripple and noise
- ❑ **QR SMPS:** Higher power density and flexible.

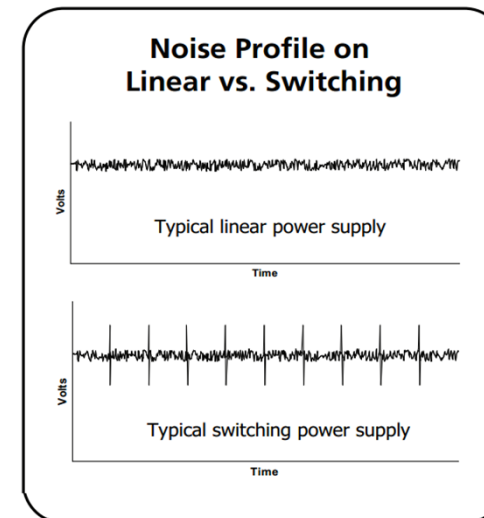


ref. 6

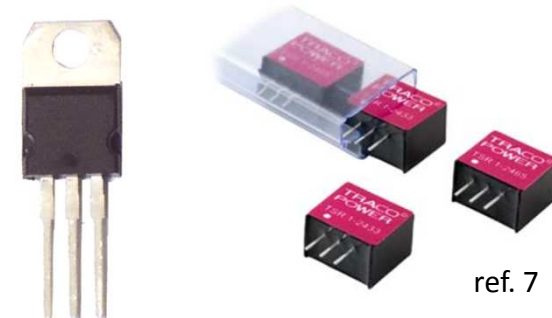


ref. 7

More Than Voltage and Current


□ Line Regulation

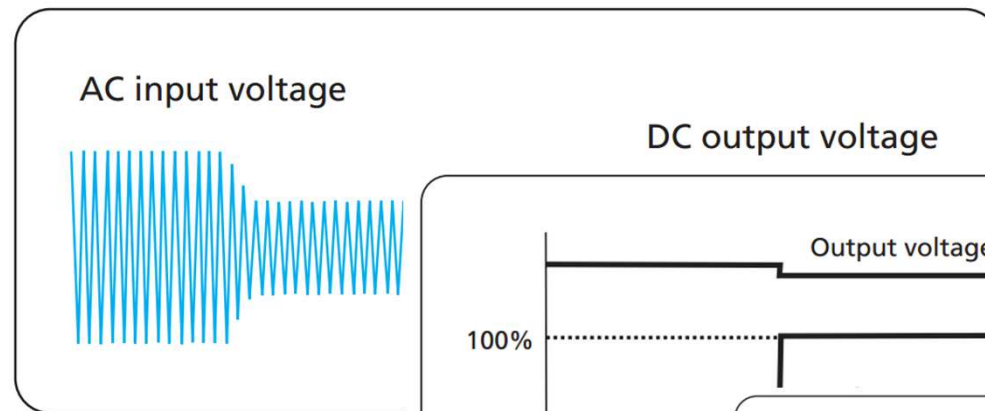

□ Load Regulation

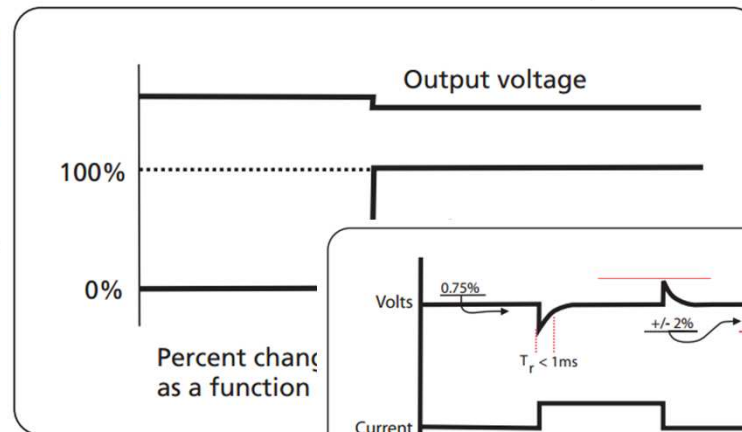


□ Transient Response

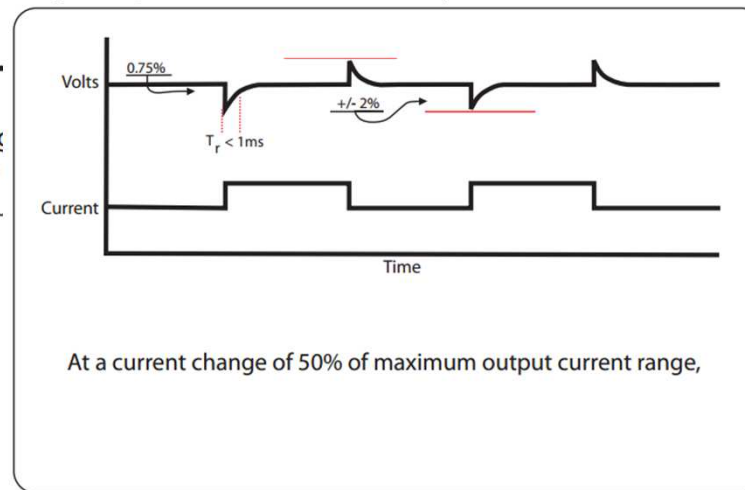

ref. 6

More Than Voltage and Current

❑ Slew Rate (60% of the I_o)

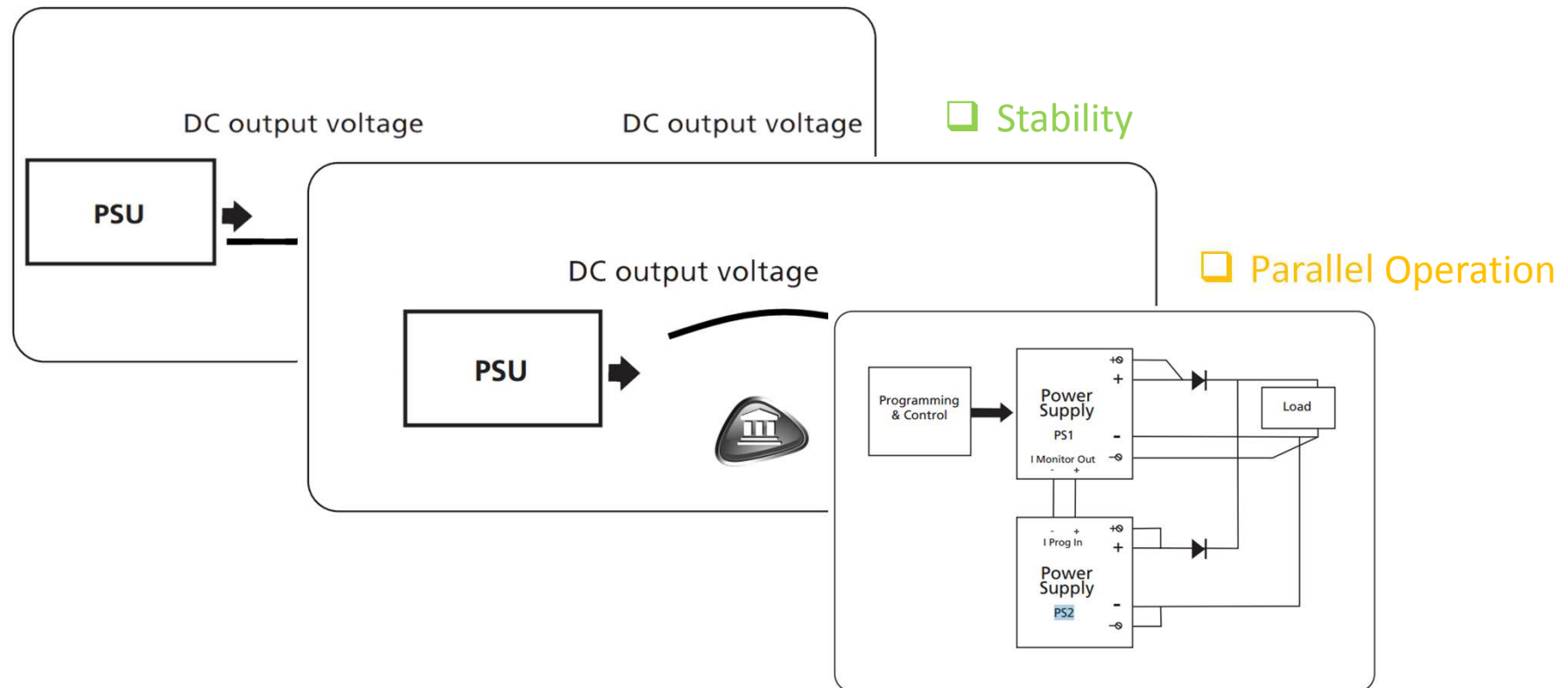



ref. 6

Control Loop

□ Stability and Phase Margin

□ Keep phase shift from less than 360 degrees before the loop gain falls below unity

□ Power supply should be silent

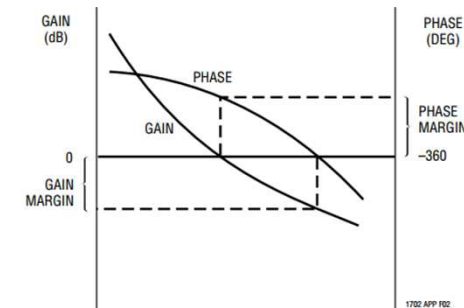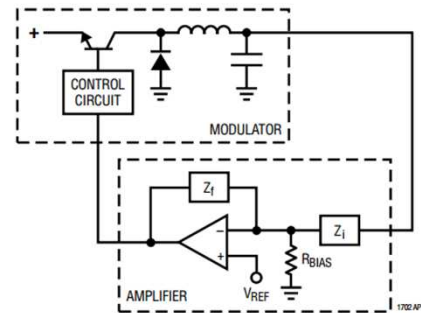

Closed Loop Circuit

Figure A2. Stability Criteria

ref. 8

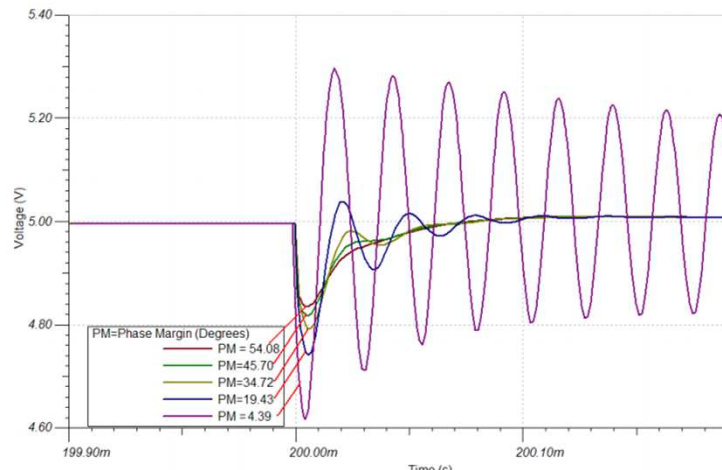


Table 1. Phase Margin vs Ringing in Load-Step Response

Phase Margin (Degrees)	Ringing (Bumps)
80.88	0
60.75	0
57.64	0
54.08	0
50.16	1
45.7	1.5
40.61	2
34.72	3
27.78	4
19.43	6
9.09	17

ref. 9

Good PSU Specification

Table 2. Performance Specification Summary

Specification	Test Conditions	Min	Typ	Max	Unit
V_{IN} voltage range		8	12	24	V
No Load Input Current	$I_{OUT} = 0A$, $V_{IN} = 12V$		6.3		mA
Output voltage set point					
Line regulation					
Operating frequency					
Output current range					
Output over current limit ⁽¹⁾	$V_{IN} =$				
Output over current limit ⁽¹⁾	$V_{IN} =$				
Load regulation					
Load transient response					
Loop bandwidth	$I_{OUT} = 2.5A$, $V_{IN} = 12V$		7.8		kHz
Phase margin	$I_{OUT} = 2.5A$, $V_{IN} = 12V$		56		°
Output ripple voltage	$I_{OUT} = 2.5A$, $V_{IN} = 12V$		75		mVpp
Peak efficiency	$I_{OUT} = 0.9A$, $V_{IN} = 12V$		87.9		%
Output current DCM threshold	$V_{IN} = 12V$		340		mA

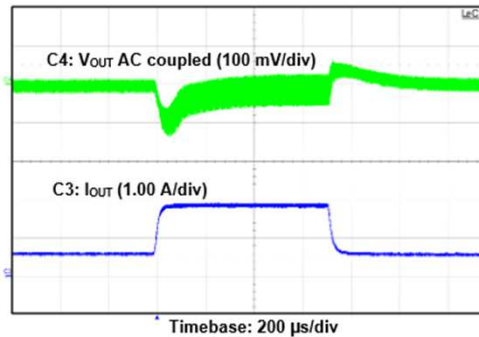


Figure 5. Load Transient Response

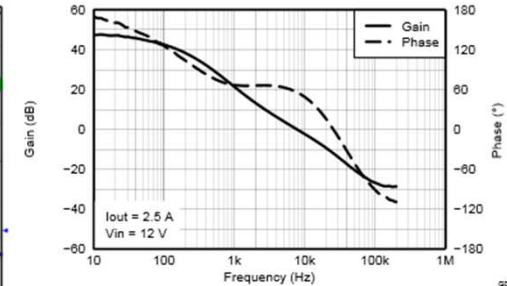



Figure 6. Loop Response

ref. 9

Agenda


TOPICS:

Power Supply Specification

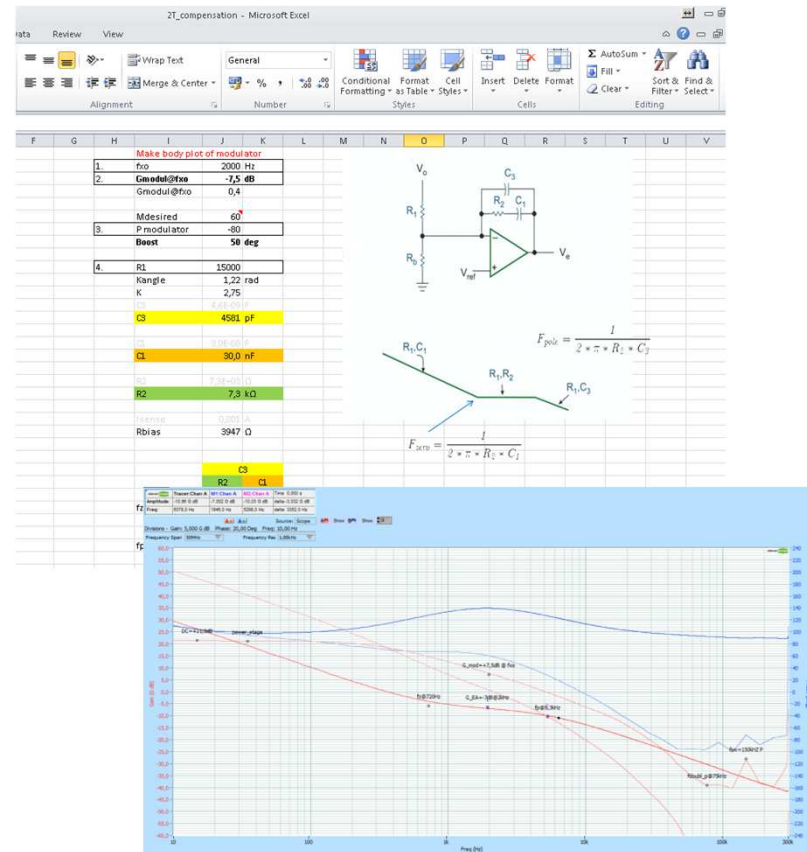

Modelling Power Supplies

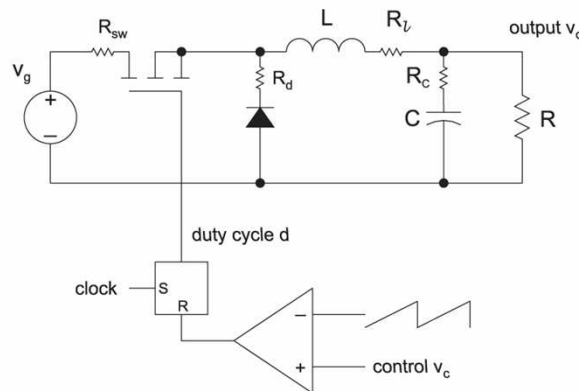- ❑ The power electronics field is supposedly simple



- ❑ Christophe Basso Switch-Mode Power Supply book
 - 1300 equations to cover the basics of operation

$$\frac{\hat{v}_o}{\hat{d}} = V_g \frac{1 + sCR_c}{1 + \frac{s}{\omega_o Q} + \frac{s^2}{\omega_o^2}}$$

$$\omega_o = \frac{1}{\sqrt{LC}}$$



$$Q = \frac{1}{\frac{Z_o}{R} + \frac{DR_{sw} + D'R_d + R_c + R_l}{Z_o}}$$

$$Z_o = \sqrt{\frac{L}{C}}$$


ref. 10

Small-Signal Model


Linear Regulator

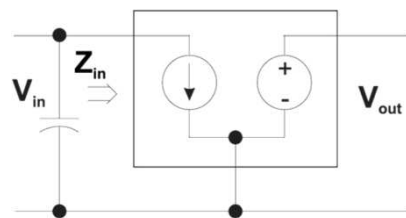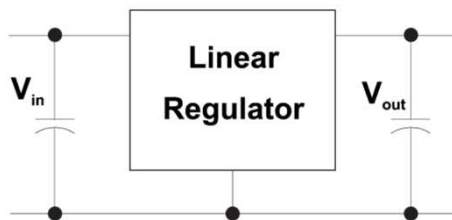

Switching Mode Power Supply

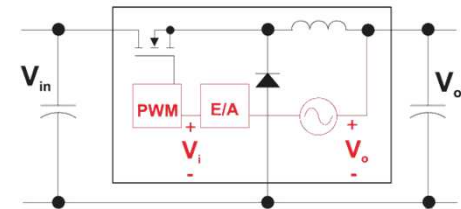


Negative input impedance of SMPS

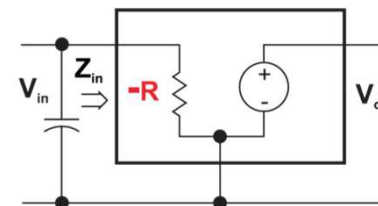

ref. 10


Simulation Tools

❑ Multisim - NI Instrument

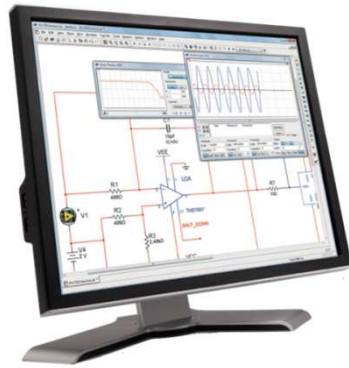


ref. 11


❑ Simplis - Simetrix Technologies

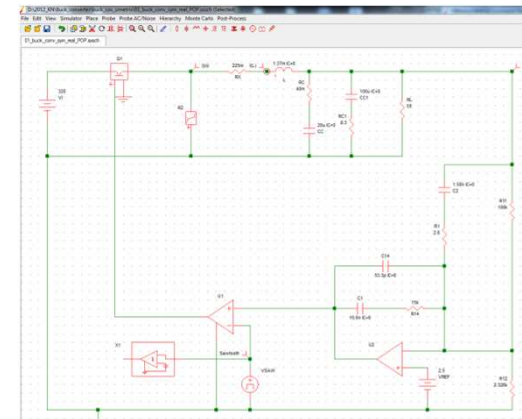

❑ LTspice - Linear Technology

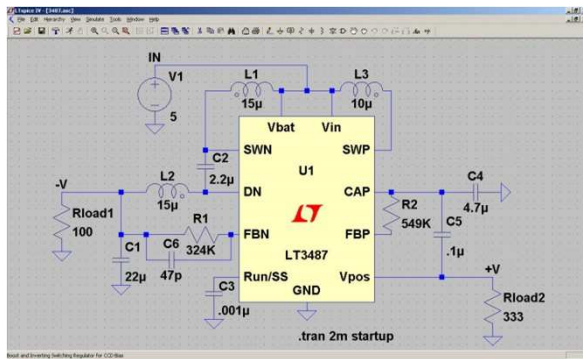


❑ Power 456 – Ridley Engineering

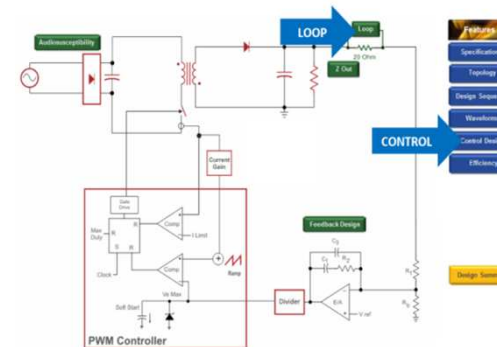

ref. 10

Modelling Approaches

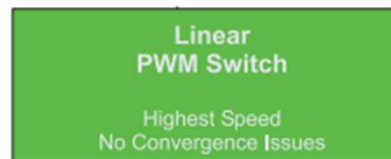- ❑ Four different ways to simulate power supplies




Analytical Power Stage Transfer Functions
Power Stage Transfer Function Bode Plots

ref. 10

Design Tools from Linear Tech.


LTpower CAD

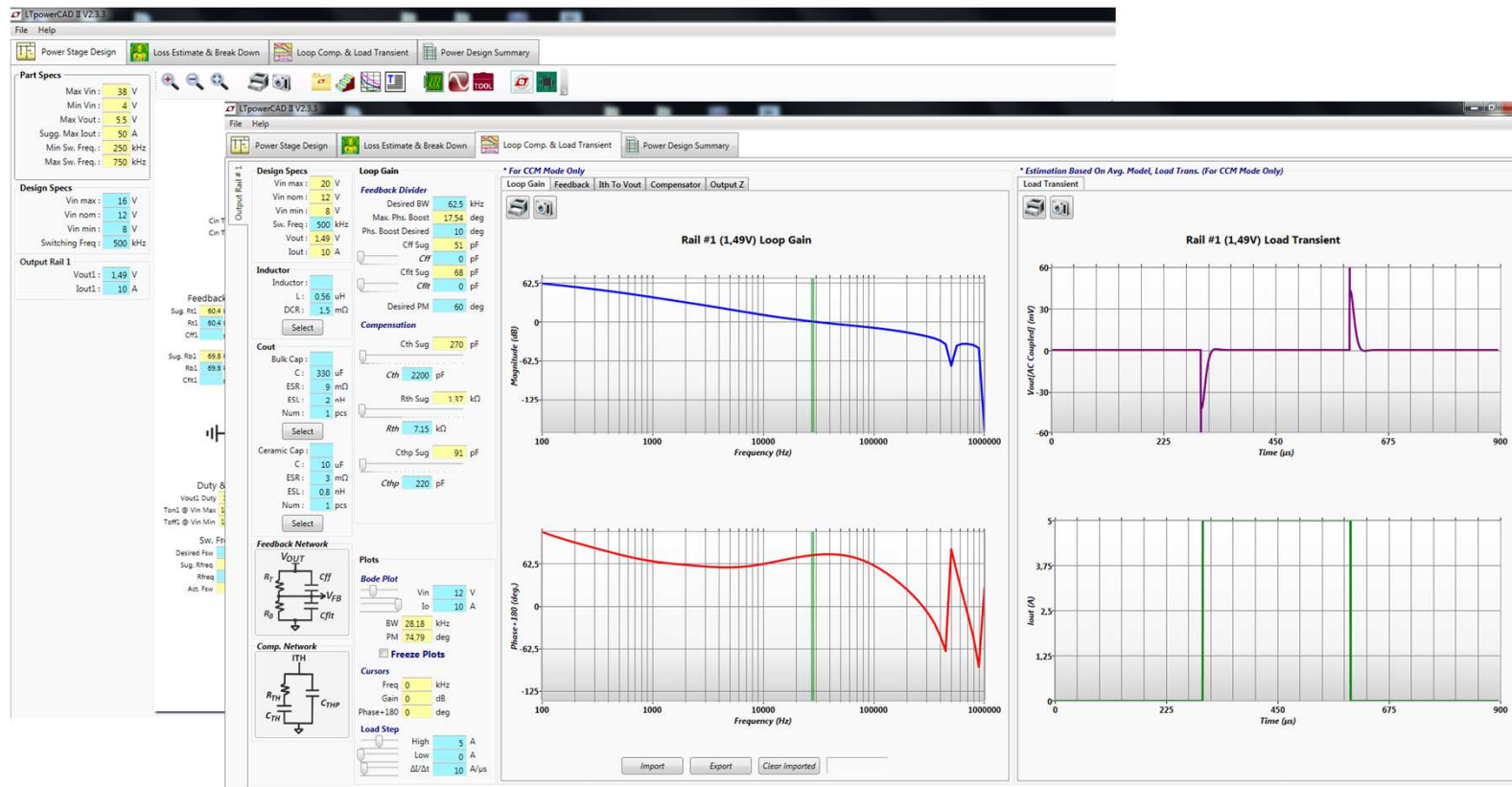

ref. 12

Design Tools from Texas Instr.

TI WebBench

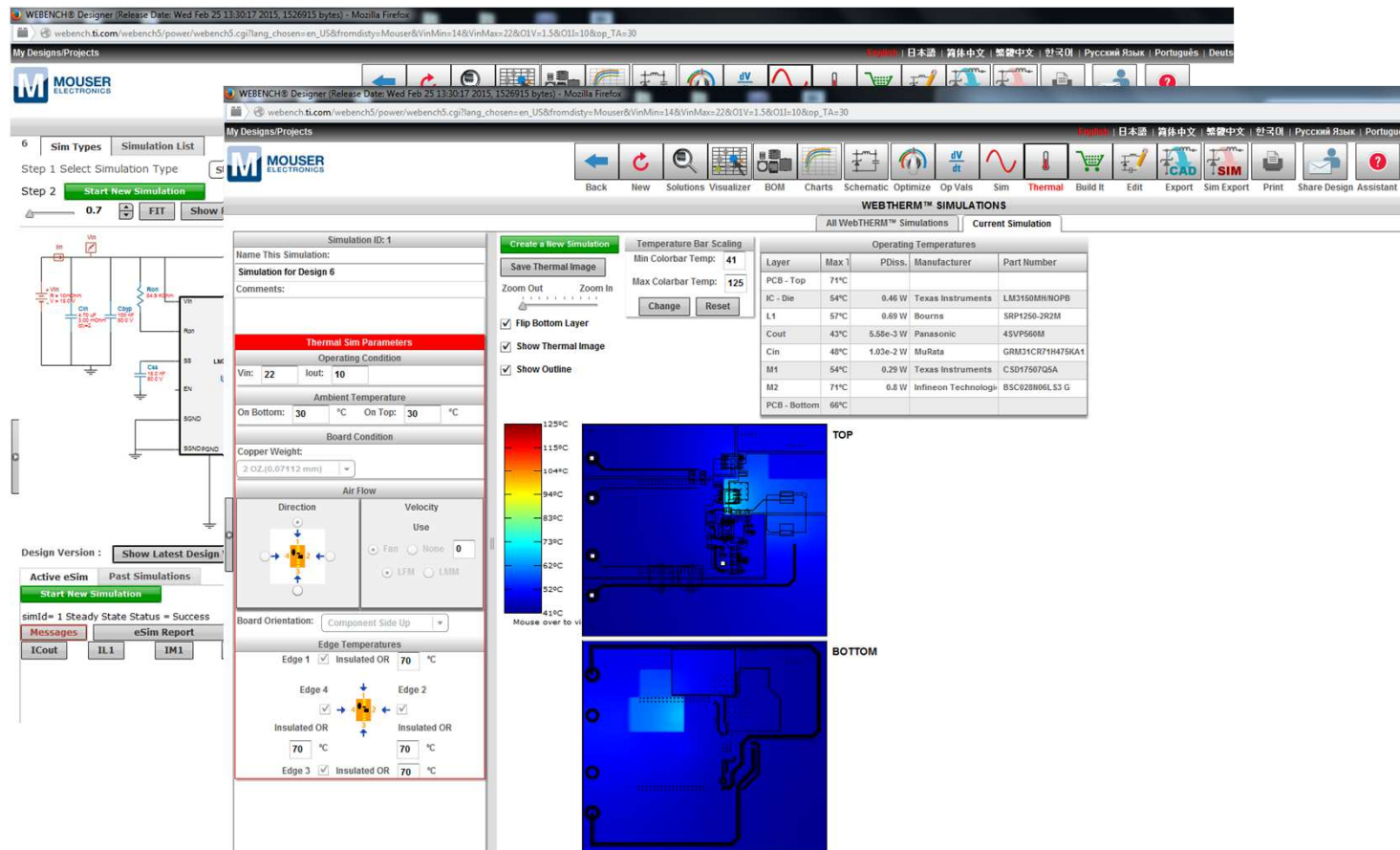

ref. 9

References

❑ List of references

Ref: 01 <http://www.dos4ever.com/flyback/flyback.html>

Ref: 02 Power Supply Cookbook – Marty Brown

Ref: 03 <http://www.toroidy.pl/>

Ref: 04 Gallium Nitride GaN Technology Overview A.Lidow

Ref: 05 <http://farnell.com/>

Ref: 06 Considerations When Specifying a DC Power Supply B. Martin

Ref: 07 <http://www.tracopower.com/>

Ref: 08 A NEW MATHEMATICAL TOOL FOR STABILITY ANALYSIS AND SYNTHESIS H. Venable

Ref: 09 <http://www.ti.com/>

Ref: 10 <http://www.ridleyengineering.com/design-center.html>

Ref: 11 <http://www.ni.com/multisim/>

Ref: 12 <http://www.linear.com/solutions/LTPowerCAD>

