

# FPGA tutorial

## Lecture 3

Wednesday 09.09.2015 – 14:00

Jochen Steinmann

**BND SCHOOL**

Belgian Dutch German graduate school in particle physics



**XILINX**®



Physics  
Institute III B

**RWTHAACHEN**  
UNIVERSITY

# 3<sup>rd</sup> Project - Summary

- Counter
  - CLK      Clock input
  - DIR      Up / Down
  - EN      enable
  - RST      Reset (synchronous)  
will be executed on next clock event
  - VAL      16bit wide **register** for counting value




# 3<sup>rd</sup> – Project – Solution

- In the skeleton I used switches for everything
  - also for clock!
  - gives opportunity to see, what happens when



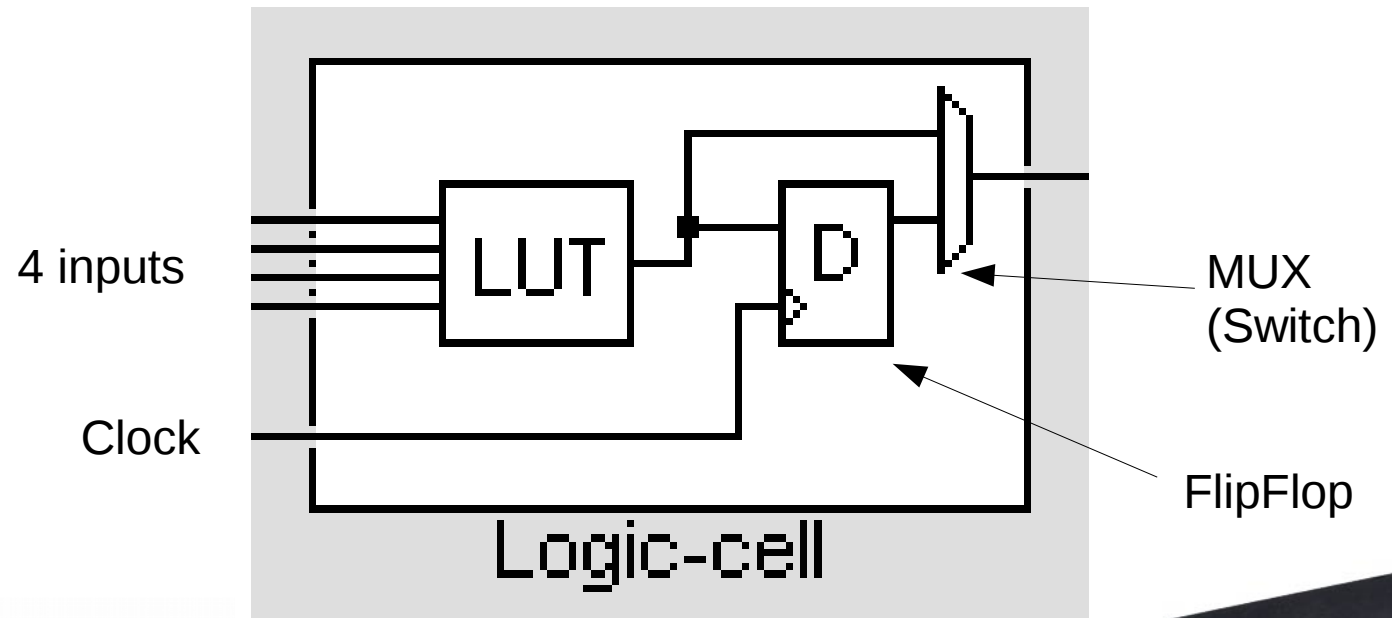
# FPGA – Implemented Logic

- Almost all logic can be reduced to use ANDs, ORs and FlipFlops
- FPGA uses “logic cells” for implementation
- Up to 4 / 6 inputs can go to one cell



 
# FPGA – Implemented Logic

- logic cells can be connected within each other
- inputs and content of LUT is generated by configuration  
→ VIVADO
- FPGA on BASYS3
  - 33k logic cells


 
# FPGA – input / output


- IO – cells have
  - FlipFlops
  - Pull – Up / Pull Down
  - Input and Output Driver


 
# FPGA – Output Levels


- Slow Signals
  - Single ended
    - LVCMOS, LVTTTL (0 - 3V3)
- Fast Signals
  - Differential Signals
    - LVDS (CM 1V25 AC 400mV)  
sometimes using current source

Distortions affect only the common mode  
Voltage difference is unaffected  
Mostly using twisted pairs


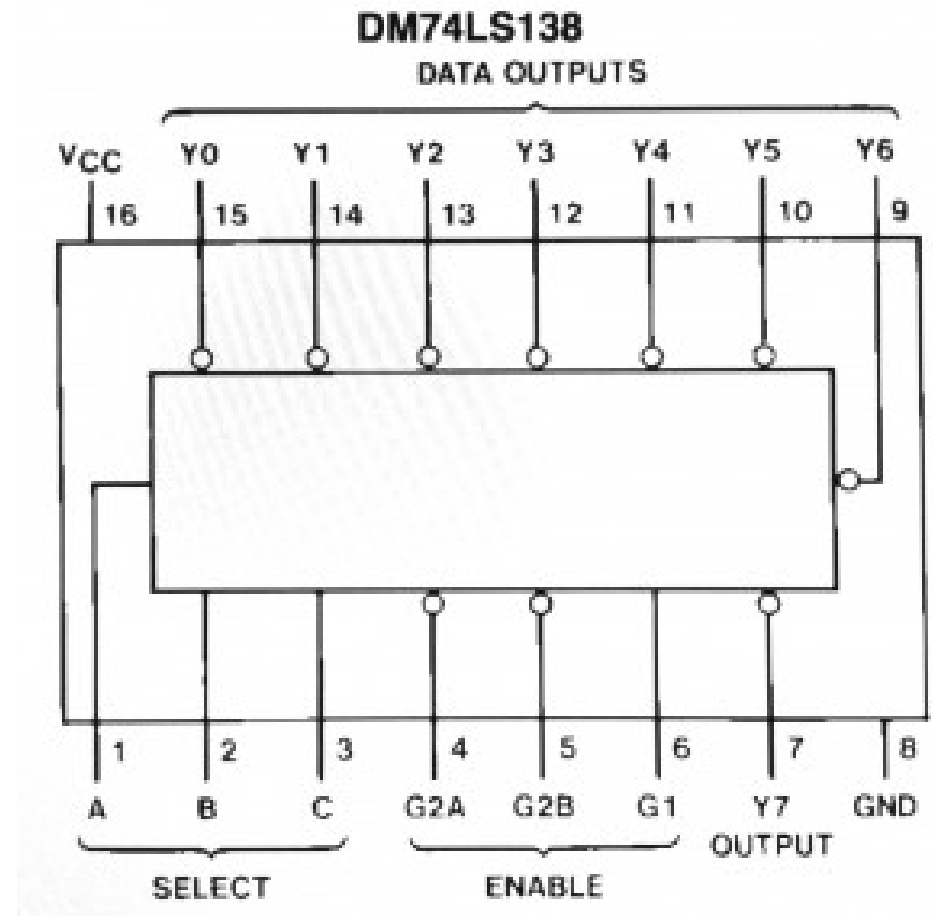
# Talking to many devices

- Address decoder
- selects only one device  
3 out of 8
- 2 different types
  - one hot (1)
  - one cold (0)
- all others inverted  
logic level



one famous type:  
74 HC 138






# Logic table of 74HC138

FUNCTION TABLE

ENABLE INPUTS			SELECT INPUTS			OUTPUTS							
G1	$\overline{G2A}$	$\overline{G2B}$	C	B	A	Y0	Y1	Y2	Y3	Y4	Y5	Y6	Y7
X	H	X	X	X	X	H	H	H	H	H	H	H	H
X	X	H	X	X	X	H	H	H	H	H	H	H	H
L	X	X	X	X	X	H	H	H	H	H	H	H	H
H	L	L	L	L	L	L	H	H	H	H	H	H	H
H	L	L	L	L	H	H	L	H	H	H	H	H	H
H	L	L	L	H	L	H	H	L	H	H	H	H	H
H	L	L	L	H	H	H	H	H	L	H	H	H	H
H	L	L	H	L	L	H	H	H	H	L	H	H	H
H	L	L	H	H	L	H	H	H	H	H	L	H	H
H	L	L	H	H	H	H	H	H	H	H	H	H	L

disabled

 

# Need of an address decoder?

- Independent:
  - outside FPGA
  - inside FPGA
- Different logic blocks (chips) have to be addressed.
  - ensure that only one is active and talks with the master
  - if multiple devices (slave) are active, may cause short circuits and lot of trouble



# 4<sup>th</sup> – Project

- Address encoder
  - if talking to multiple chips, you have to ensure, that only one is selected at the same time!
  - Two options
    - one hot → selected chip 1, others 0
    - one cold → selected chip 0, others 1
  - Input
    - 2 bit (0-3)
  - Output
    - 4 bit

**Hint:**

you can use a bus to access elements of a bus

$a[b]$  → will access the bit  $b$  of  $a$



# Output to humans


- There are many ways how an FPGA device can communicate with the “operator”
  - High energy physik
    - mostly remote access → e.g. Network etc.
  - Consumer devices
    - need graphical menues
      - LEDs → easy
      - **7-Segment displays** → **more complex, but still simple**
      - LCDs → too complex for this course



# Difference

- Humans use **decimal** system
- FPGAs and computers use **binary** system
- Need to convert between different worlds
  - $1001 \rightarrow 9$

 **1<sup>st</sup> 7 segment lookup table**




# 5<sup>th</sup> - Project


- Heading forwards to display numbers on the 7-segement display
- Lookup table for 7 segment display
  - 7 segments can display 10 values 0 – 9
  - depending on the input different outputs have to be switched on
- Inputs 4 Bit → sw3 – sw0
- Outputs 8 Bit → 7 Segments



# 5<sup>th</sup> – Project

 

 An un-illuminated seven-segment display, and nine illumination patterns corresponding to decimal digits





one Bus  
segments = 'b0000011;  
A + B on



# 5<sup>th</sup> - Project

Pin 1

  



# Verilog – CASE

- simple case structure

```
reg [1:0] address;  
case (address)  
    2'b00 : begin  
        statement1;  
    end  
    2'b01, 2'b10 : statement2;  
    default : statement3;  
endcase
```

either you implement all possible combination, or you use a default  
Otherwise the logic is not fully determined.



# 6<sup>th</sup> - Project

- Problem:

- FPGA uses binary notation
- Human uses decimal notation
- have to split our number into digits

- ones
- tens
- hundrets


**use 8 bit input → 0 ... 255**

**Binary Coded Decimal  
4 Bit for each digit**



# BCD

- Example:

 

# BCD Algorithm

1. If any column (1000's, 100's, 10's, 1's) is 5 or greater add 3 to that column
2. Shift all #'s to the left 1 position
3. If 8 shifts are done, it's finished.  
Evaluate each column for the BCD values
4. Go to step 1.

<http://www.eng.utah.edu/~nmcdonal/Tutorials/BCDTutorial/BCDConversion.html>



# BCD – Pseudo Code

```
for(i=0; i<8; i++) {  
    //check all columns for >= 5  
    for each column {  
        if (column >= 5)  
            column += 3;  
  
        //shift all binary digits left 1  
        Hundreds <<= 1;  
        Hundreds[0] = Tens[3];  
        Tens << = 1;  
        Tens[0] = Ones[3];  
        Ones << = 1;  
        Ones[0] = Binary[7];  
        Binary <<= 1;  
    }  
}
```



100's	10's	1's	Binary	Operation
			1010 0010	
		1	010 0010	<< #1
		10	10 0010	<< #2
		101	0 0010	<< #3
		1000		add 3
	1	0000	0010	<< #4
	10	0000	010	<< #5
	100	0000	10	<< #6
	1000	0001	0	<< #7
	1011			add 3
1	0110	0010		<< #8

162

1

6

2



# Verilog – for loop

- define somewhere an integer i  
for(i=start; i<=stop; i=i+1) begin  
end
- Difference to C/C++ or PCs
  - due to synthesis loops runtime is zero
  - **loops don't need a clock!**
  - just to make the source code look a bit nicer :-)



# Verilog - shift

- Multiply and divide by 2
  - value  $\ll$  position  $\rightarrow$  shift to left  $\rightarrow * 2$
  - value  $\gg$  position  $\rightarrow$  shift to right  $\rightarrow / 2$
- if you shift out of memory, the bit is lost





# ToDo

- 4) address decoder  
(de-) select one bit of 8  
3 bit input  
3 to 8 (one cold)
- 5) 7 segment lookup table  
map 4 input bits to the 7 segments, which  
should light up
- 6) Binary coded decimal  
display 4 bits as 0 ... 9 on the 7 segments

