

FPGA tutorial


Lecture 4

Thursday 10.09.2015 – 14:00

Jochen Steinmann

BND SCHOOL

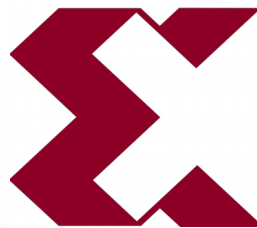Belgian Dutch German graduate school in particle physics



XILINX®



Physics
Institute III B





RWTHAACHEN
UNIVERSITY

Putting all together ...

- Final Exercise
 - 8-bit decimal counter (0 – 255)
 - 7 segment display
 - Enable
 - Up / Down
 - driven by ~ 10 Hz



What do we need?

- all the things we programmed before
 - 7segment lookup 
 - address decoder (1 cold) 
 - several counter 
 - BCD encoder 



How to generate a slow clock?

- It is always nice to have a clock with
 - dutycycle of 50% (50% low, 50% high)
 - defined phase with respect to the master clock
- use a counter
 - count up and down → this ensures 50% duty cycle



Clock divider

- divider is set via maxCNT

Clock divider I provide!

always running up down counter
no enable, no reset
you might use your counter with
by setting .RST(0) .EN(1)

On every clock change

we use CLKout as the direction!

```
counter mycnt( .dir(CLKout),  
               .CLK(CLKIn),  
               .cnt(cnt_reg) );
```

```
always @( cnt_reg ) begin  
    if( (cnt_reg == maxCNT) ) begin  
        CLKout = 1; // count down  
    end  
    if( (cnt_reg == 0 ) ) begin  
        CLKout = 0; // count up  
    end  
end  
end
```




7th - Project

- I provide you all the modules needed.
- Use them!
- Just connect them in the right way.
- You just have to write the top module
 - in BND_07skel part of the top module is already filled.
 - If you like to, you can delete this and start from scratch
 - If you are not that familiar with FPGAs, just connect the modules with each other



7th – Project

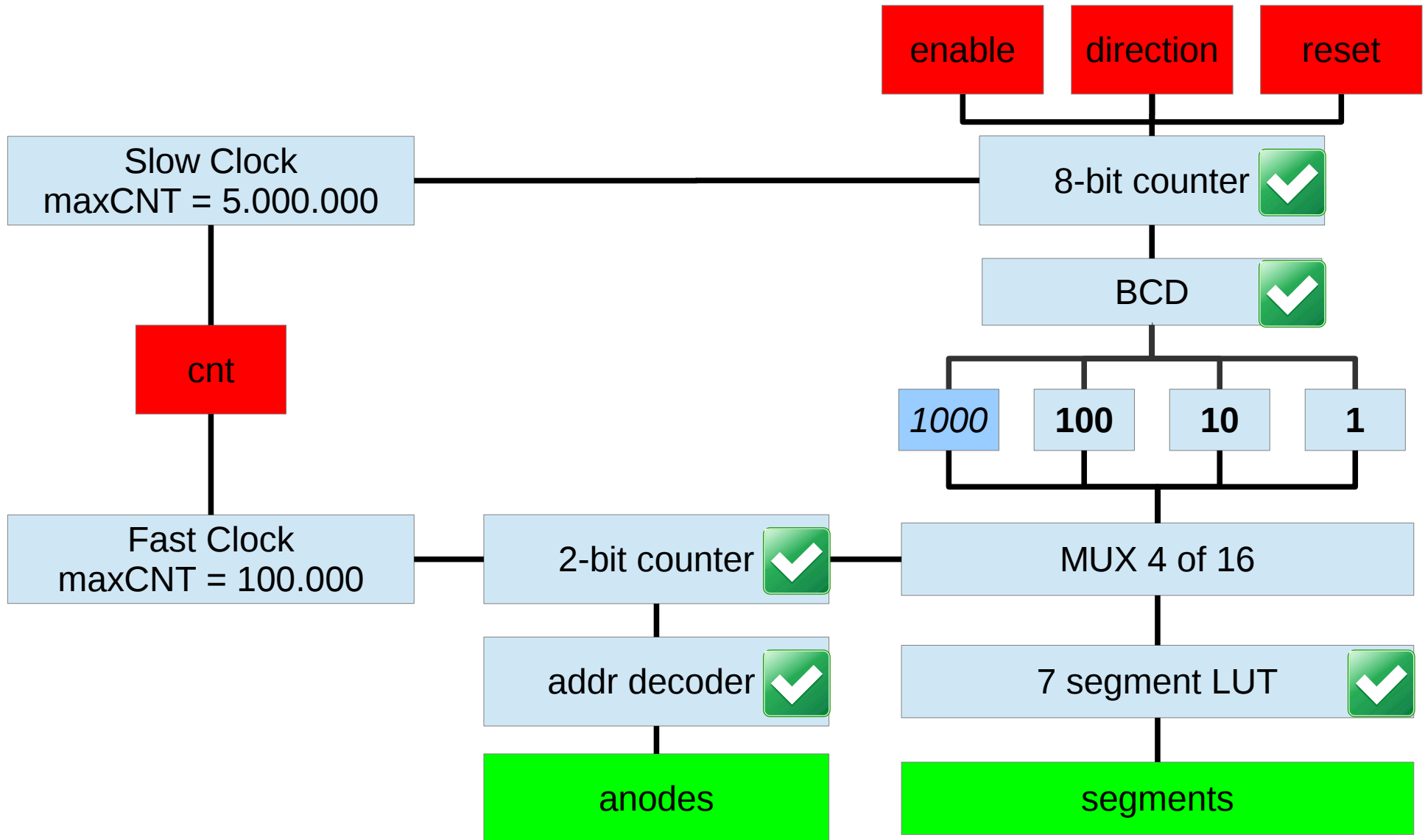

If there is time...

- Try to modify the working solution
 - add a real stop watch behaviour
 - one button for start / stop



At the end of the lecture ...

- Please return the Laptops to the right box
 - they have a number written on top
 - each box has a number, please match them

