



# Front-end electronics dedicated to the next generation of linear collider calorimeter

---

## CALICE COLLABORATION

LPC Clermont

**Samuel MANEN**

G rard BOHNER

Jacques LECOQ

LAL Orsay

Julien FLEURY

Christophe de la TAILLE

Gis le MARTIN




# OUTLINE

---

- o Requirements for ECAL
- o Electronics synoptic
- o Low noise preamplifier
- o Shaper
- o Pipeline analog to digital converter
  - o Gain 2 amplifier.
  - o The comparator.
- o Conclusion and schedule.

 
# Requirements for ECAL

- ECAL : **Barrel with sandwich silicon-tungsten** structure composed of 40 layers of reading with diodes of  $1\text{cm}^2$ .
- 34 Millions channels **very low consumption**
  - Pulsed power supply.
- **Large dynamic range** typically 14-15 bits and accuracy about 8bits.
  - Multi-gain system.
- Train = 3000 Bunch-crossing every 200ms.  
BX = between 150ns-300ns.
  - Slow system.




# Electronics integration

- Chip embedded in detector.

 

- Reduce line capacitance → reduce preamplifier consumption to obtain a noise less than 1/10 MIP (MIP= 40,000 e-).
- Reduce crosstalk.
- Electromagnetic shower on chip???
- Cooling issues.
- Sensor (diode) is a wafer 6cm\*6cm so 1 chip for 36 channels.
  - 34 Millions channels → 950,000 chips.
  - 34 Millions channels → 3,400 m<sup>2</sup> silicon.

# Electronics synoptic

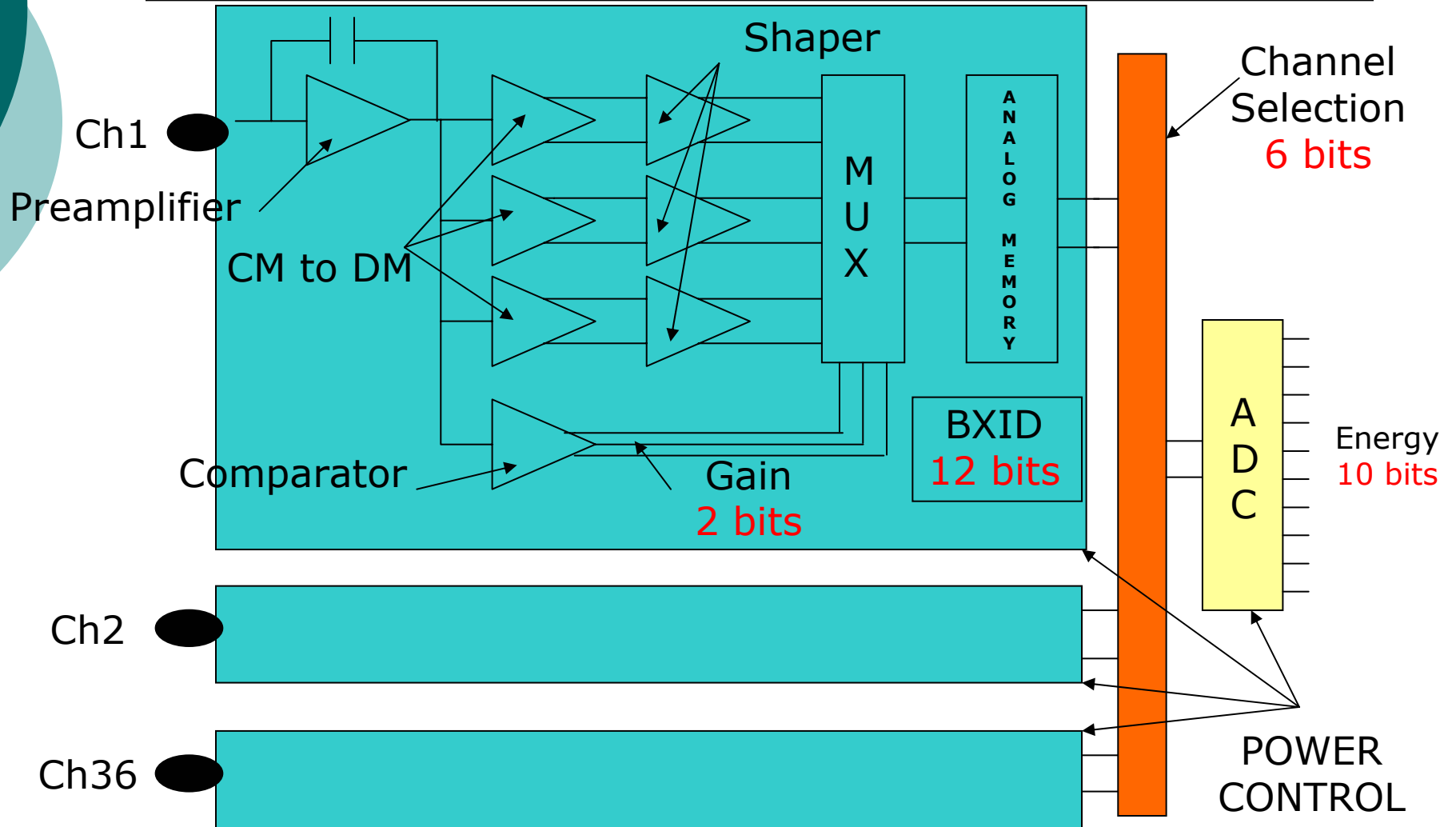




# Technology choice for R&D

---

- **The electronics for front-end will be mixed**
  - Need good digital performance.
  - Need good analog performance.
  - As cheap as possible.
- **Our choice AMS 0.35 $\mu$ m CMOS (c35b4)**
  - Perennity because used by car industry.
  - Two transistors type.
    - Transistor 3.3V for digital block.
    - Transistor 5V for analog block.

# THE PREAMPLIFIER

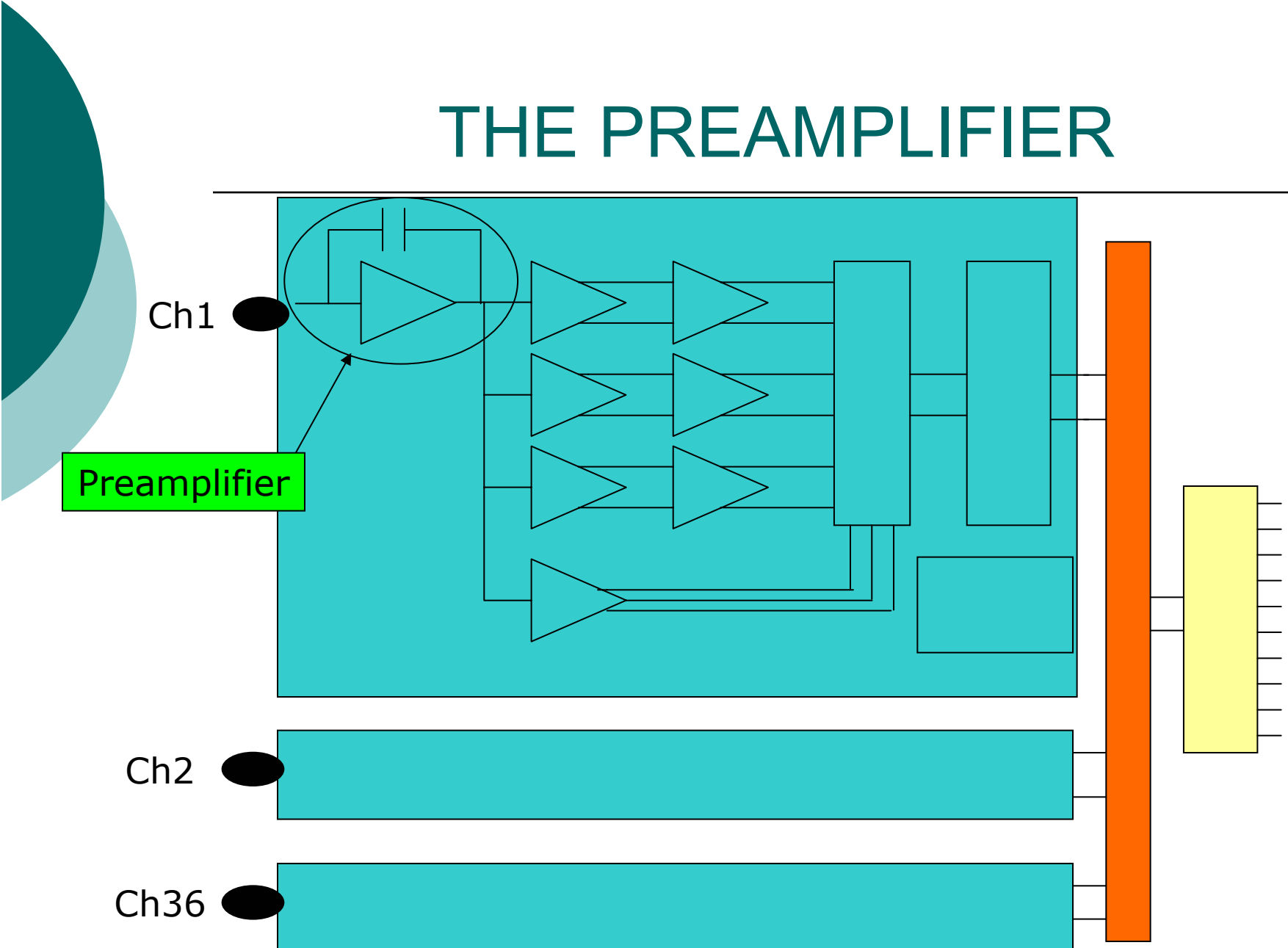

Preamplifier

Ch1

Ch2

Ch36



# Low noise preamplifier

---

- MIP is fixed by silicon wafer depth: 500 $\mu$ m so 40,000e-
- **Noise is defined as MIP/10 so 4000e-**.

- Two types of noise :

- **Serial noise** :

$$e_n^2 = \frac{8 \times k \times T}{3 \times g_m} + \frac{A_f}{f}$$

The noise 1/f is neglected because we have a transistor Pmos in input.

- **Parallel noise** :


$$i_n^2 = 2 \times q \times I_g + \frac{4 \times k \times T}{R_f}$$

- **Use a big transistor Pmos** to have important  $g_m$ .
  - Large W 2000 $\mu$ m.
  - Small L 0,5 $\mu$ m.
  - Need current  $I_{ds}=200\mu$ A (power limited 1mW for preamplifier).


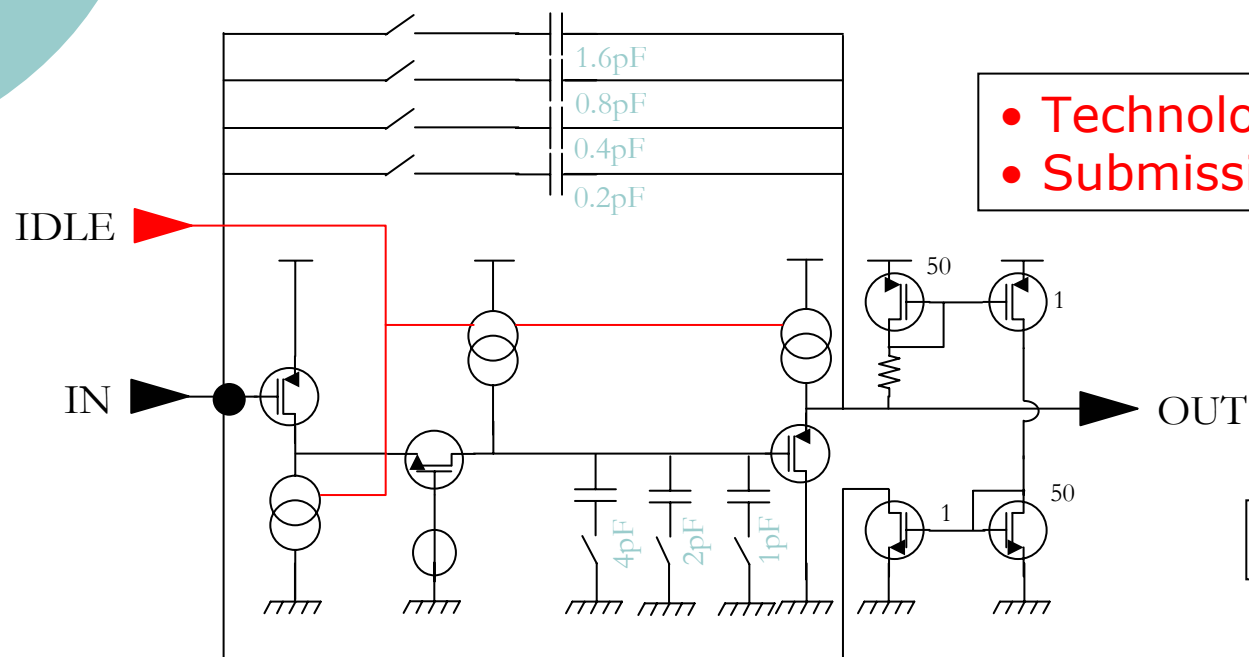
# Schematic of the preamplifier


- o Standard charge preamplifier
- o Low consumption: below 1mW
- o Low noise: about  $1\text{nV}/\sqrt{\text{Hz}}$



- Technology: AMS CMOS  $0.35\mu\text{m}$
- Submission: April 19<sup>th</sup> 2004

LAL Orsay (J.Fleury)


# Electronics synoptic

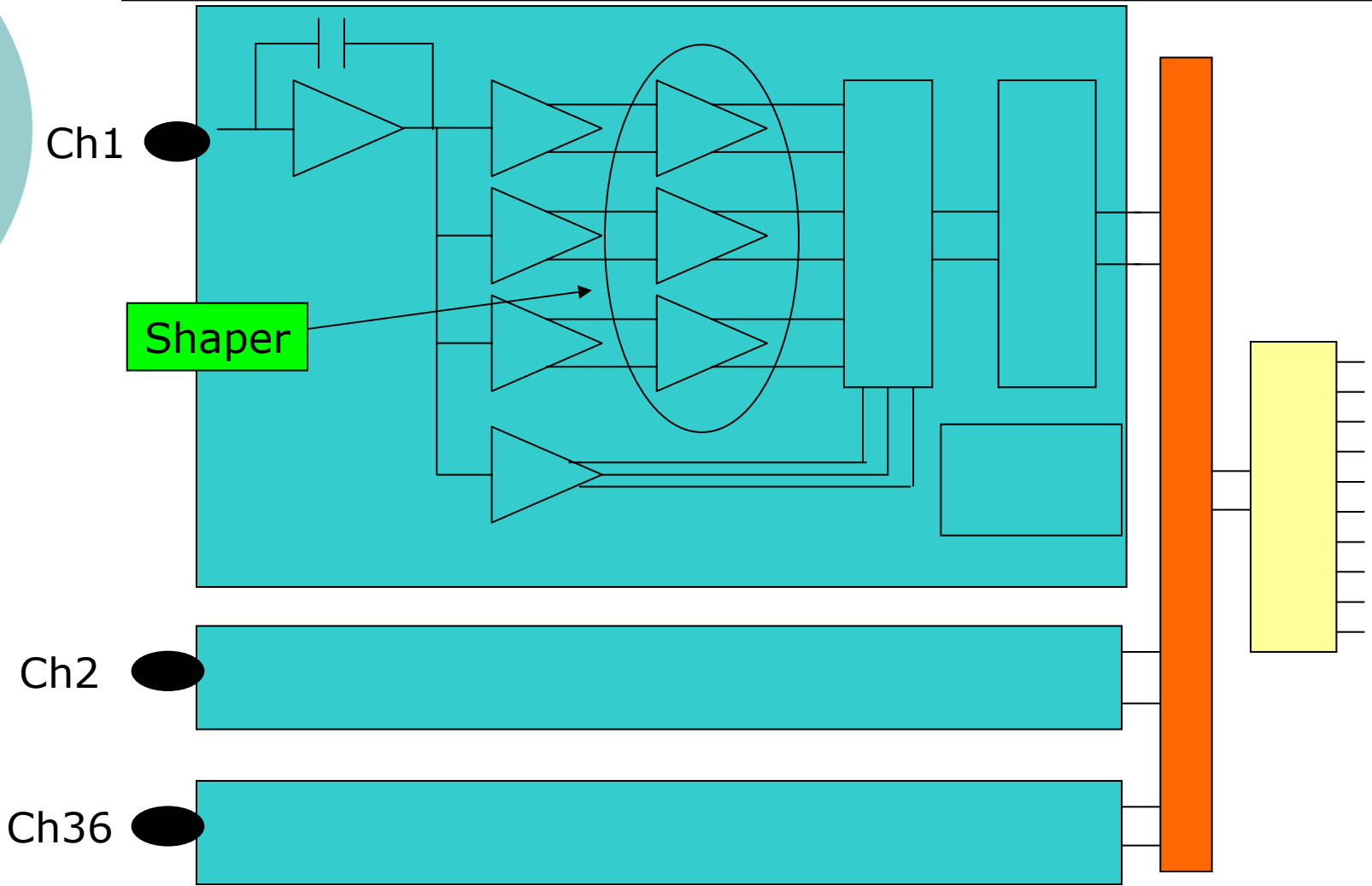

# Two alternatives of filtering
 
## ○ Shaper CRRC<sup>2</sup>


- $g_m = 10 \text{ mA/V} \rightarrow e_n = 1.1 \text{ nV}/\sqrt{\text{Hz}}$
- $I_g = 30 \text{ nA} \rightarrow i_n = 100 \text{ fA}/\sqrt{\text{Hz}}$



- ENC=1,430e-
- Advantage:
  - System well known
- Inconvenient:
  - Takes a large place with resistances
  - Slow reset, probably pile-up.

## ○ Switched integrator

- Same conditions

 

- ENC=1,660e-
- Advantage:
  - Good integration of switch
  - No pile-up
- Note:
  - Need a command signal




# Amplifier of the shaper


---

- Development of an amplifier in two technologies :
  - Shaper is built with an amplifier used as integrator in  $0.8\mu\text{m}$  BiCMOS.
  - Gain 100 amplifier in  $0.35\mu\text{m}$  CMOS to define offset.
- Mixing of two schematics
  - An amplifier with resistive common mode feedback.
  - A differential amplifier with input and output rail to rail.

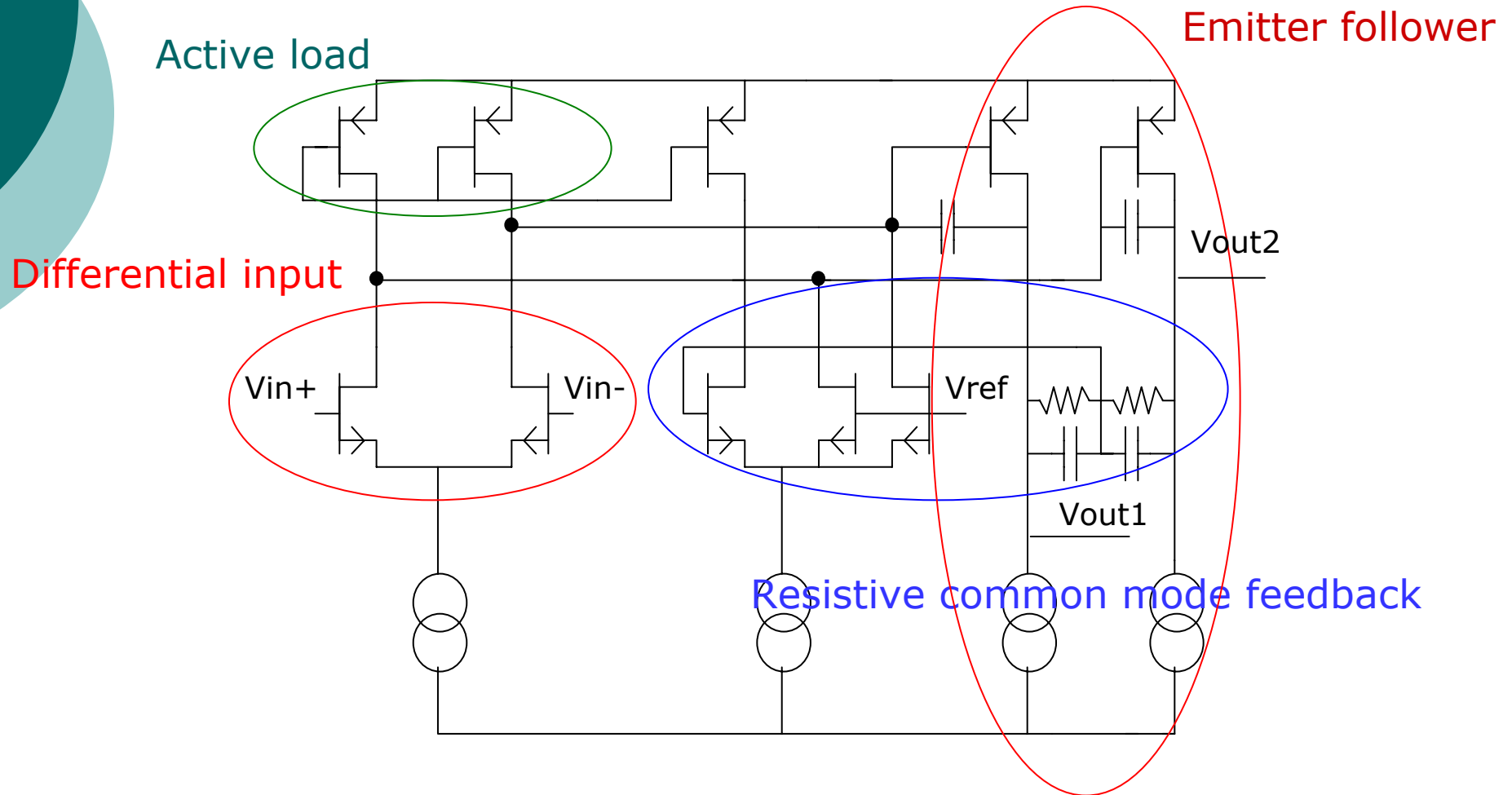
# Differential amplifier with resistive common mode feedback


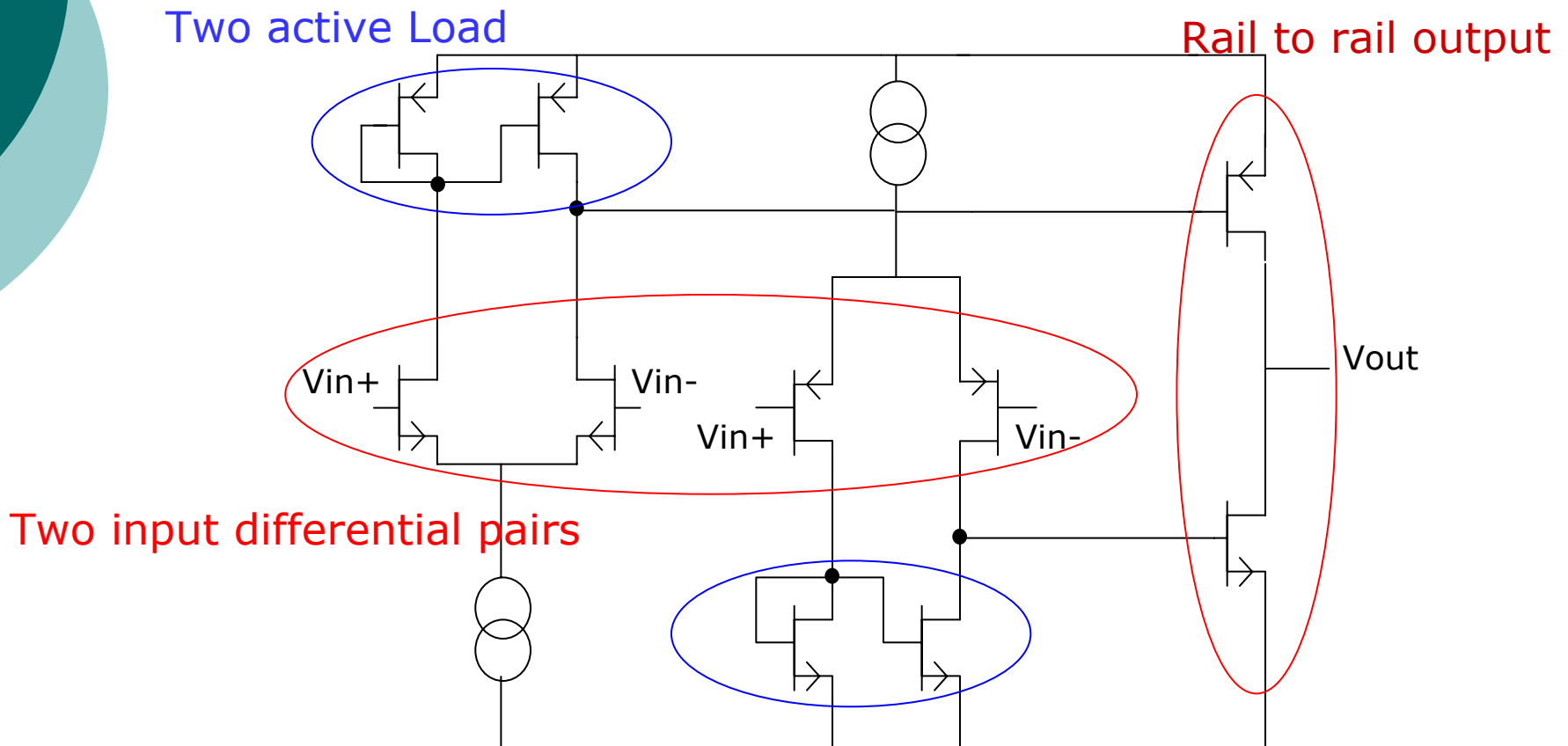
# Differential amplifier with rail to rail input output




# Amplifier CMOS

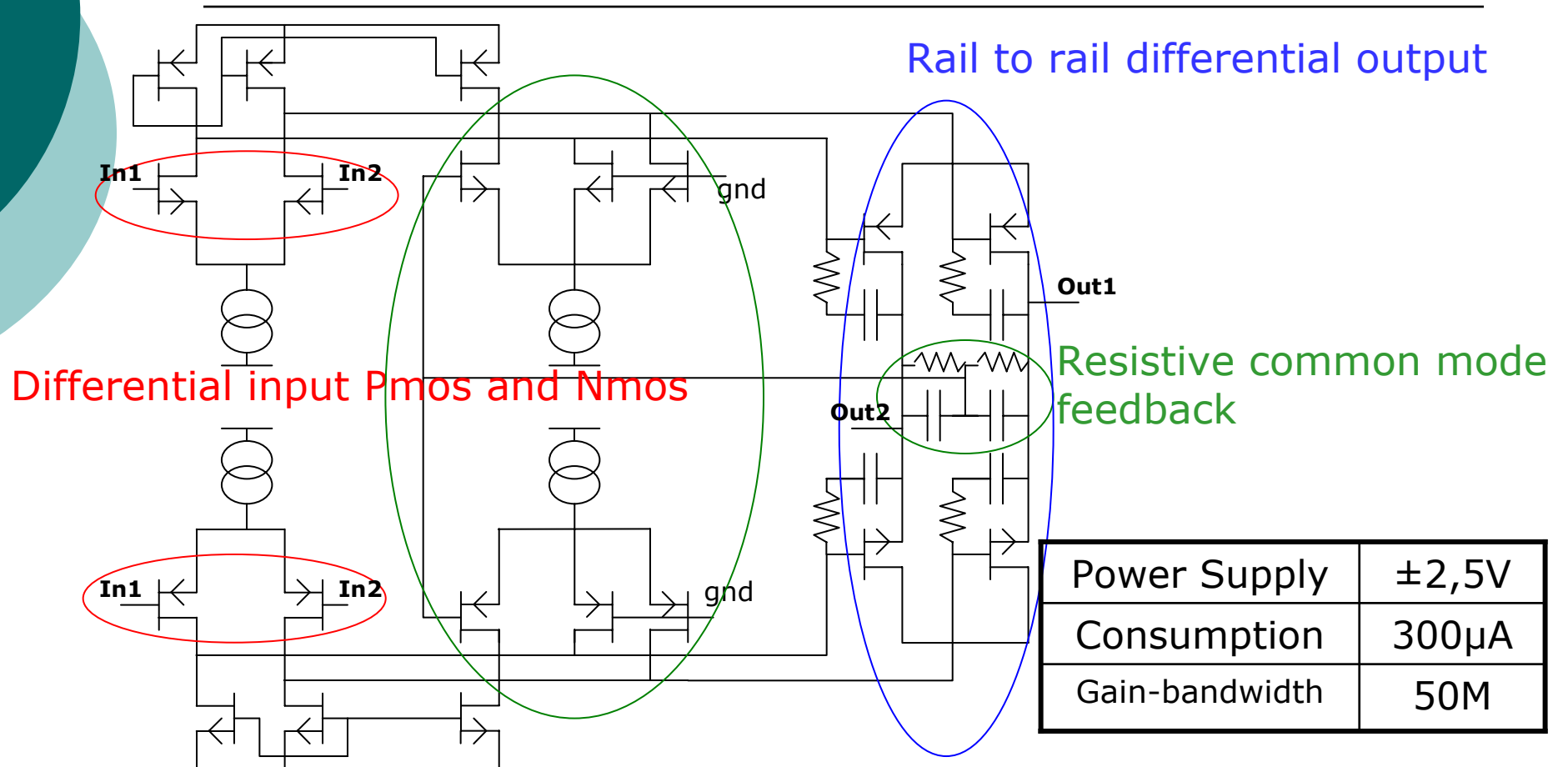
 
# Amplifier: some tests results


- Two versions of amplifier
  - One in  $0.8\mu\text{m}$  with the amplifier in integrator. OK.



- One in  $0.35\mu\text{m}$  with the gain 100 amplifier :
  - Offset measured =  $1\text{mV}$ , so good matching.




# Electronics synoptic

 

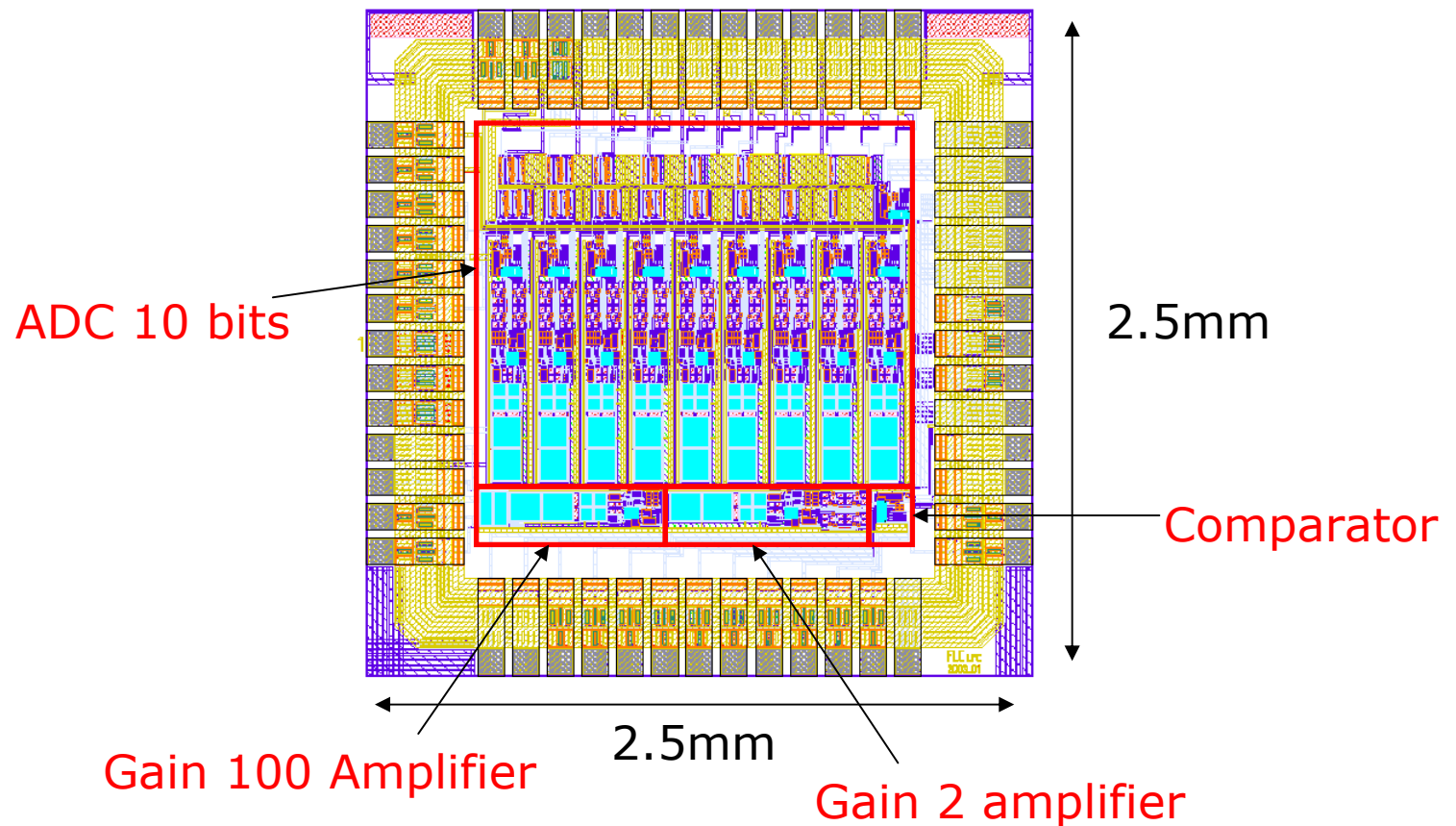
# The chip in technology 0.35 $\mu\text{m}$ CSI

Chip developed and tested in 2003. Area 6.25 mm<sup>2</sup>.



# ADC pipeline schematic principle

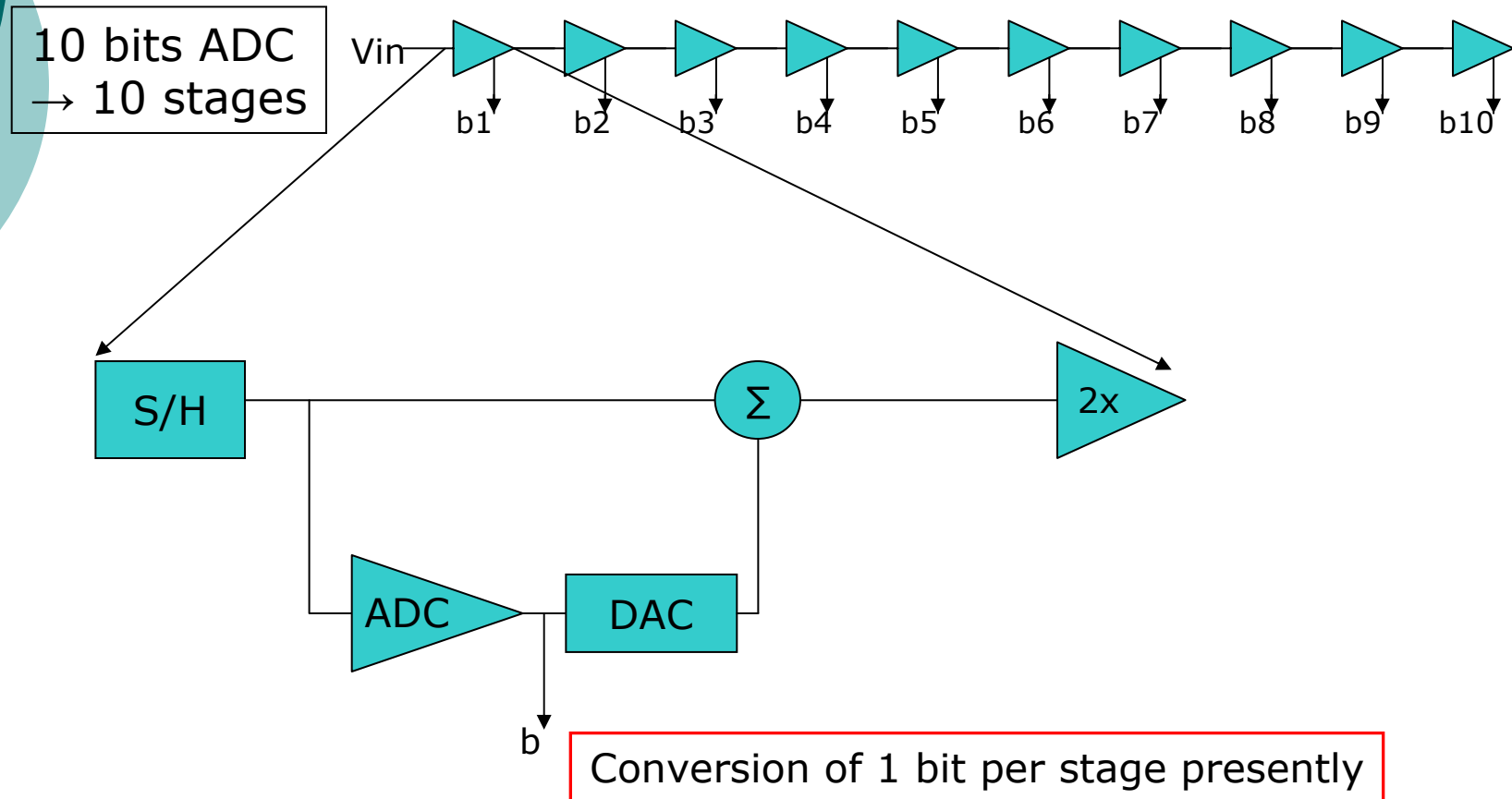

# ADC equivalent scheme

Two cases :

□ If  $V_{in} > V_{ref}$


→ Bit N out = 1 and  $V_{in(N+1)} = (V_{in} - V_{ref}) * 2$

□ If  $V_{in} < V_{ref}$

→ Bit N out = 0 and  $V_{in(N+1)} = V_{in} * 2$



What we need:

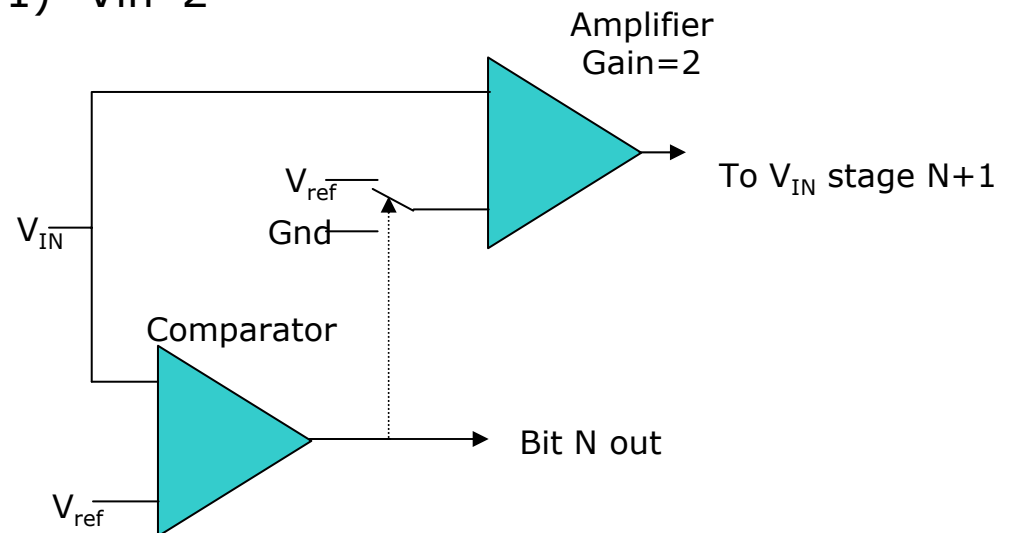- An amplifier in gain 2.
- A comparator.


 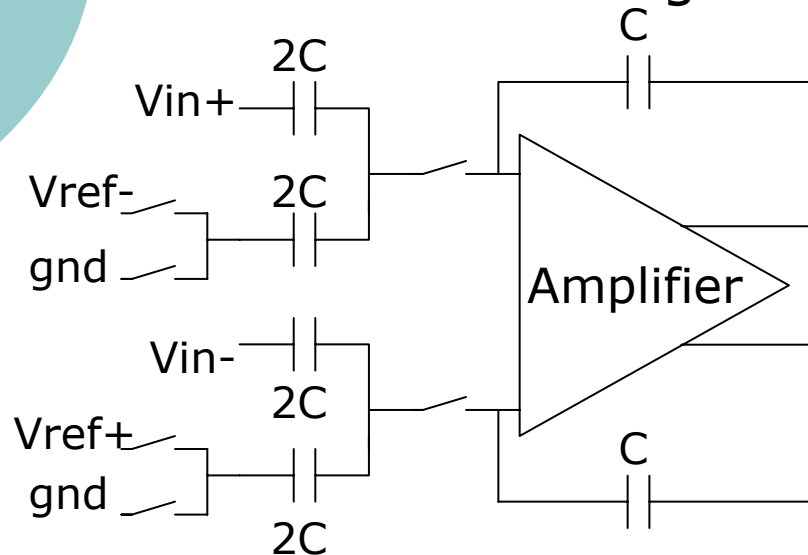
# Gain 2 amplifier

- Gain 2 amplifier is identical to the shaper one.
- Hard to do a gain 2 to obtain 10 bits.




Layout capacitance with  $C=300\text{fF}$  ( $18.5 \times 18.5\mu\text{m}$ )

## Tests results:

- Average gain= $2.01 \pm 0.02$
- Average offset= $-4 \pm 4\text{mV}$

# Comparator CMOS

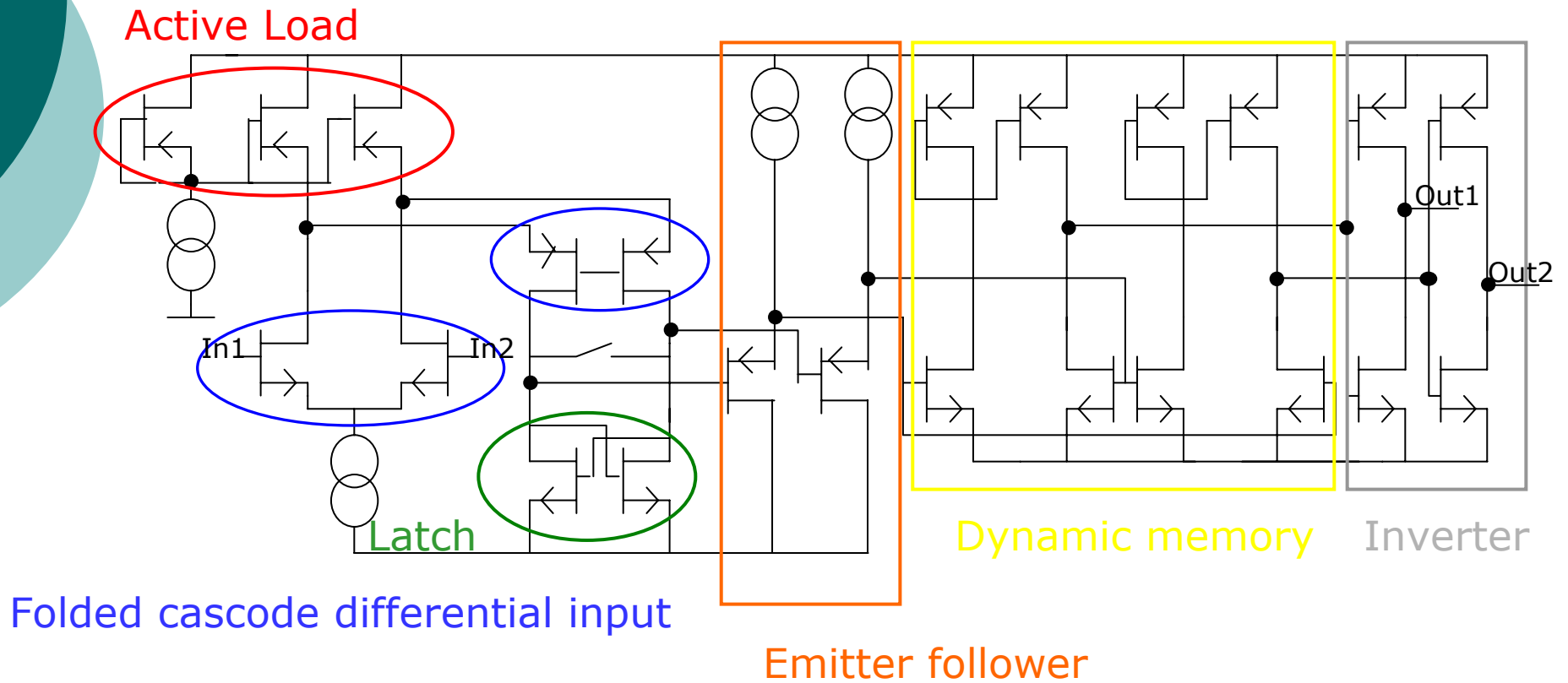

Comparator is used in other IN2P3 laboratories.

# Comparator tests and simulation results

Power Supply	$\pm 2,5V$
Consumption	100 $\mu A$
Clock frequency	5MHz
Sensitivity	300nV
Offset	9mV

Simulation parasitic results

Noise	
Sensitivity	300 $\mu V$
Offset average	11mV

Tests results

## CONCLUSIONS:

- Very good modelisation.
- Must improve offset due to parasitic capacitance.
- Sensitivity in test correspond to the noise of system.



# Simulations and tests results for ADC

---

- First simulation results successful but in fact this simulation was done without parasitic capacitance...!!!
- **TESTS:**
  - Functionality verified.
  - 5 first bits are obtained.


Power supply	$\pm 2,5V$
Dissipation	20mW
Input	$\pm 1V$
Clock	5MHz

- **SIMULATION with parasitic:**
  - Problems of stability with amplifier.
  - Very important error on output code.


 
# New ADC pipeline 10 bits in 0.35 $\mu$ m C35B4


Chip send in July 2004. Area 4.17 mm<sup>2</sup>.


 
# Improvements done for ADC

---

- Polysilicium high resistivity permits to draw big resistance
  - Occupy less place on silicon.
- **AMPLIFIER:**
  - Amplifier stabilization with higher RC on rail to rail output.
  - New layout for gain 2: more compact to obtain better matching.



- **COMPARATOR:**
  - Offset improvement.
- More important power supply decoupling.
- Simulation results with parasitic this time
  - 10 bits obtained, wait and see for tests in October 2004.



# Conclusion

---

- One possible global scheme of the FE electronic exists.
- Two possibilities of filtering OK.
  - Shaper CRRC<sup>2</sup>
  - Switched integrator
- Charge preamplifier, a shaper and a comparator CMOS exist.



# Schedule

---

- News improvements for ADC:
  - 1.5 bit per stage for consumption.
  - Not exactly the same block for 10 stages.
  - To reduce consumption only one master current for all amplifiers and comparators.
  - Perhaps, need digital correction. Not realized for the moment.
  - Offset correction for amplifier?...