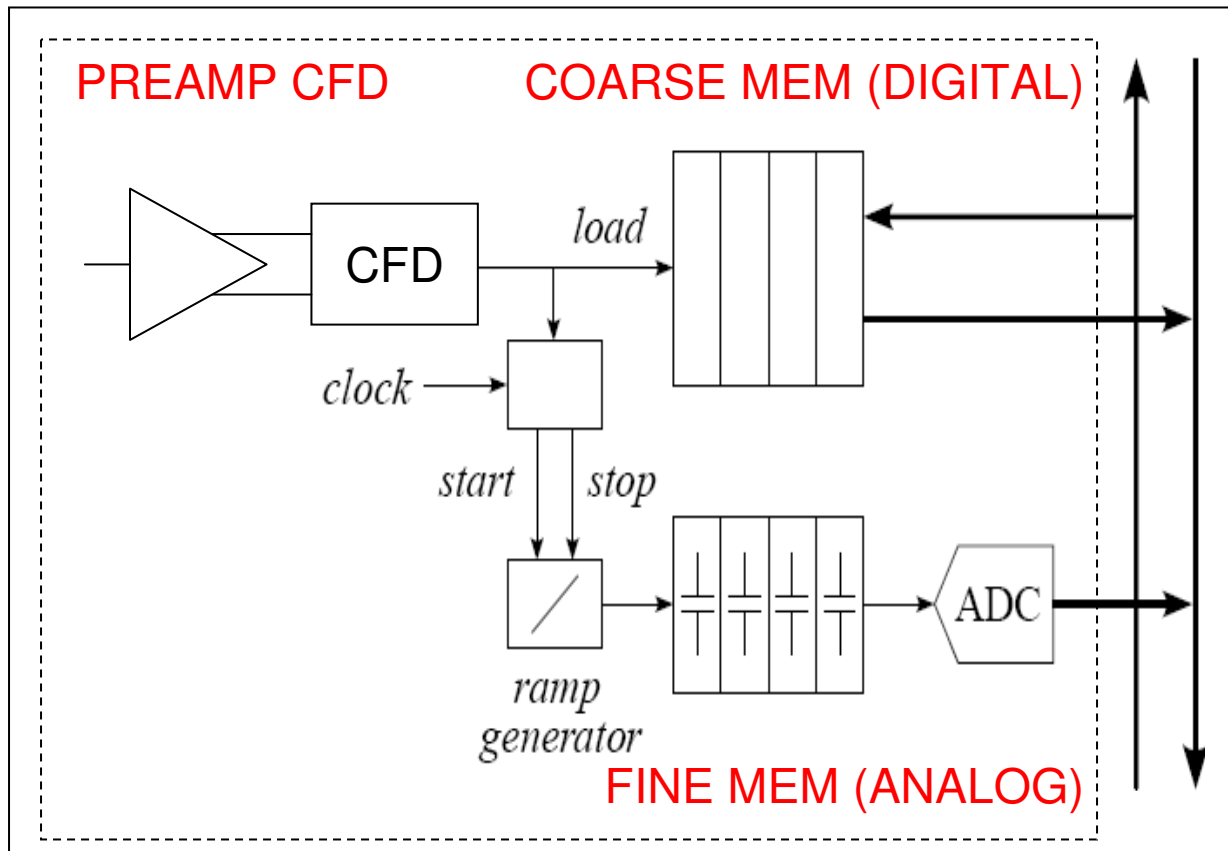


# NA62 CFD Design Review

Sorin Martoiu, INFN, Torino

# CFD-FE Overview




- Efficient de-randomization
- Efficient use of space
- Reduce end-of-column complexity


# CFD-FE Overview

- Extract 100ps accurate information
- De-randomize
- Convert to digital


# Prototype

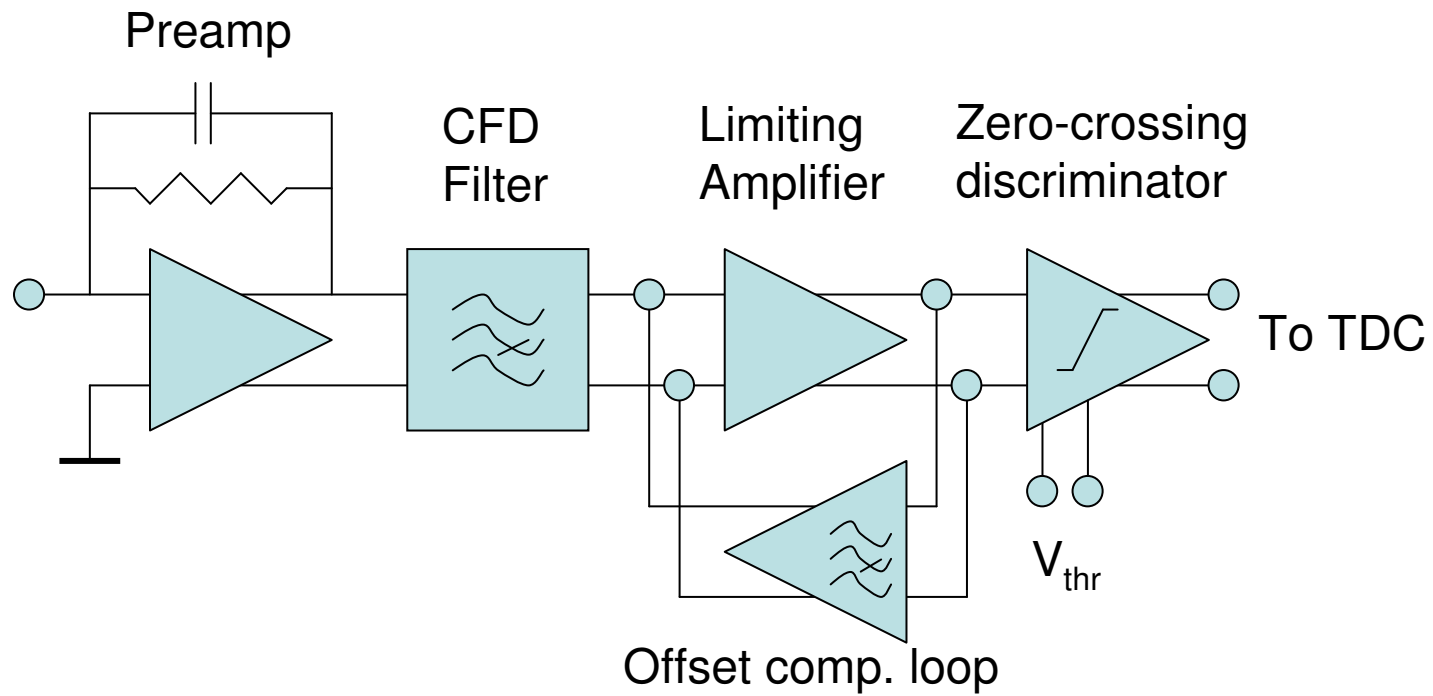

# “CMOS” Differential Implementation


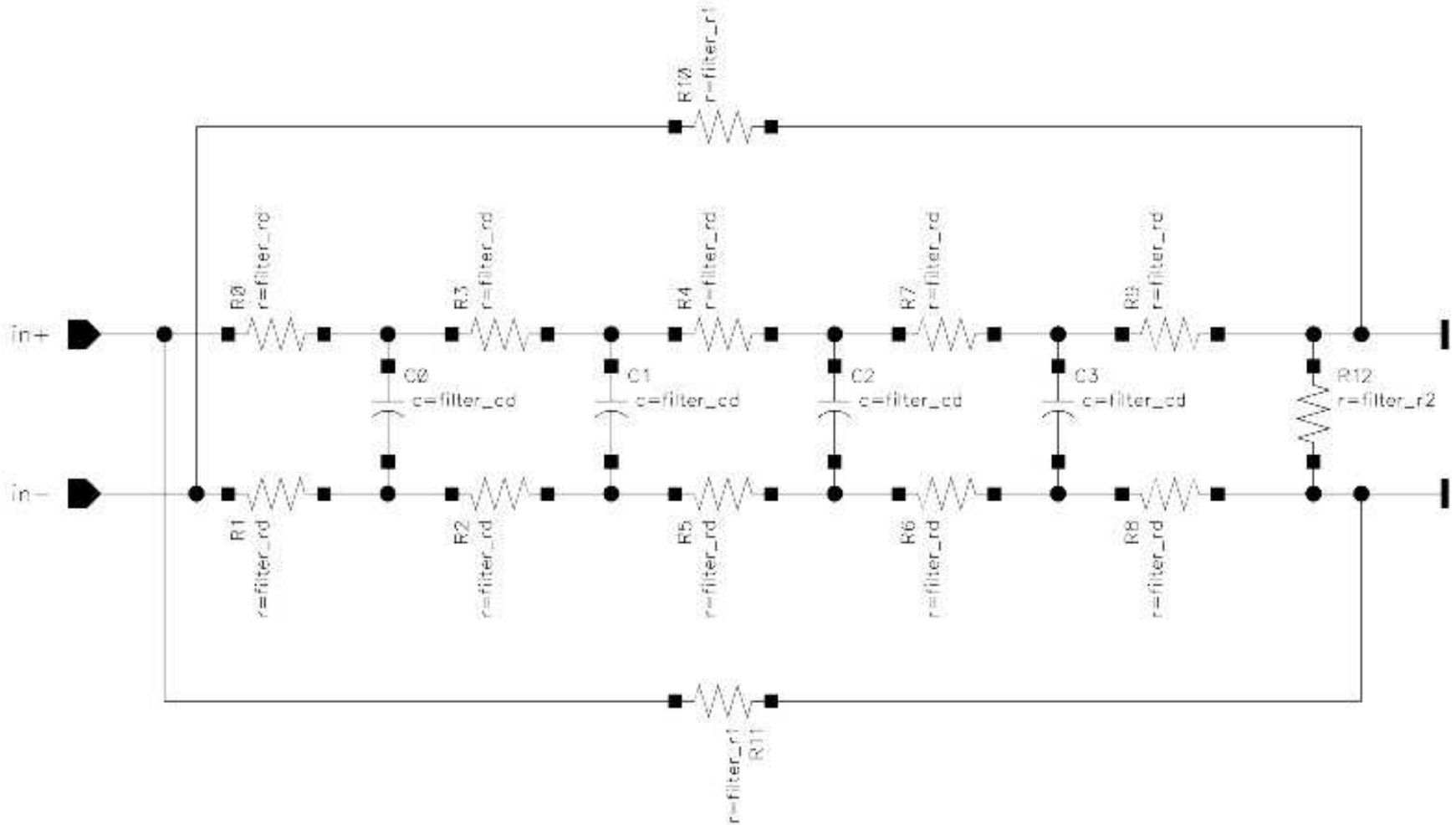


# Dynamic Offset Compensation

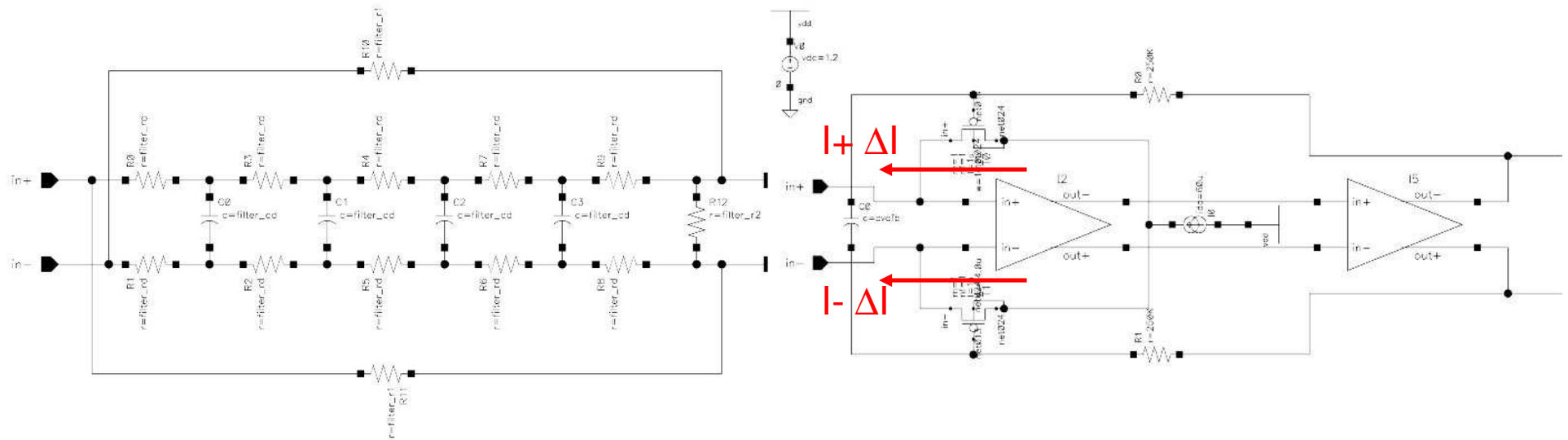


- Offset cancellation
- Low-pass feedback  $\Rightarrow$  high-pass overall transfer  $\Rightarrow$  reduce low-frequency noise (1/f noise)

# Dynamic Offset Compensation

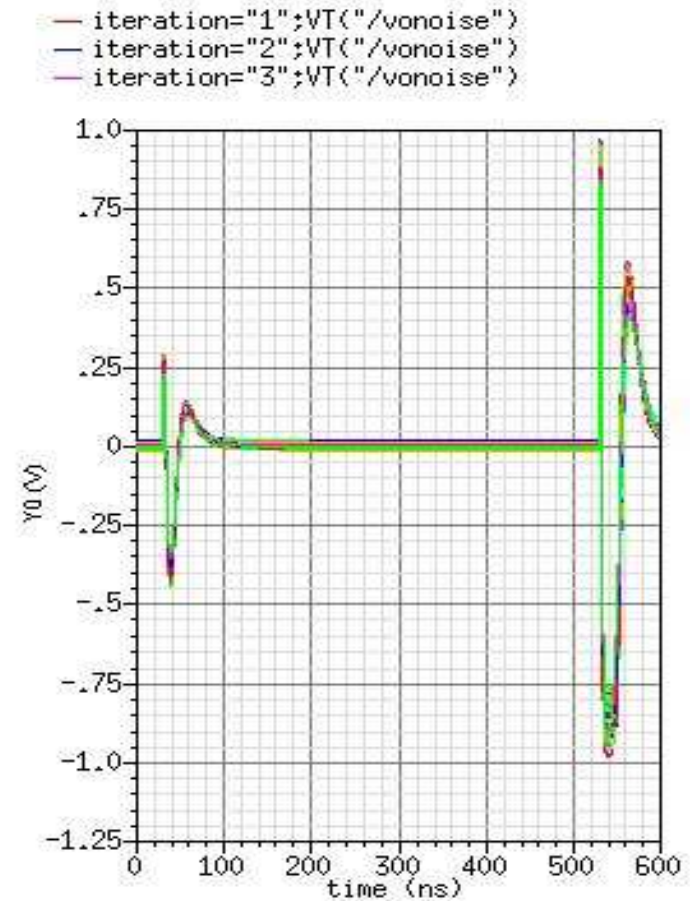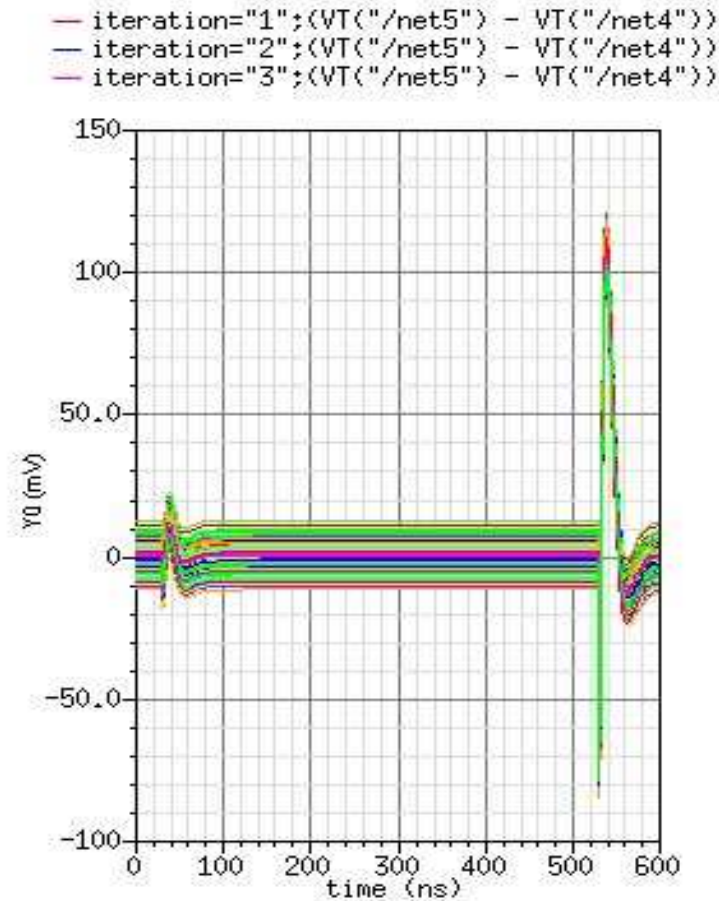


# Coincidence discriminator

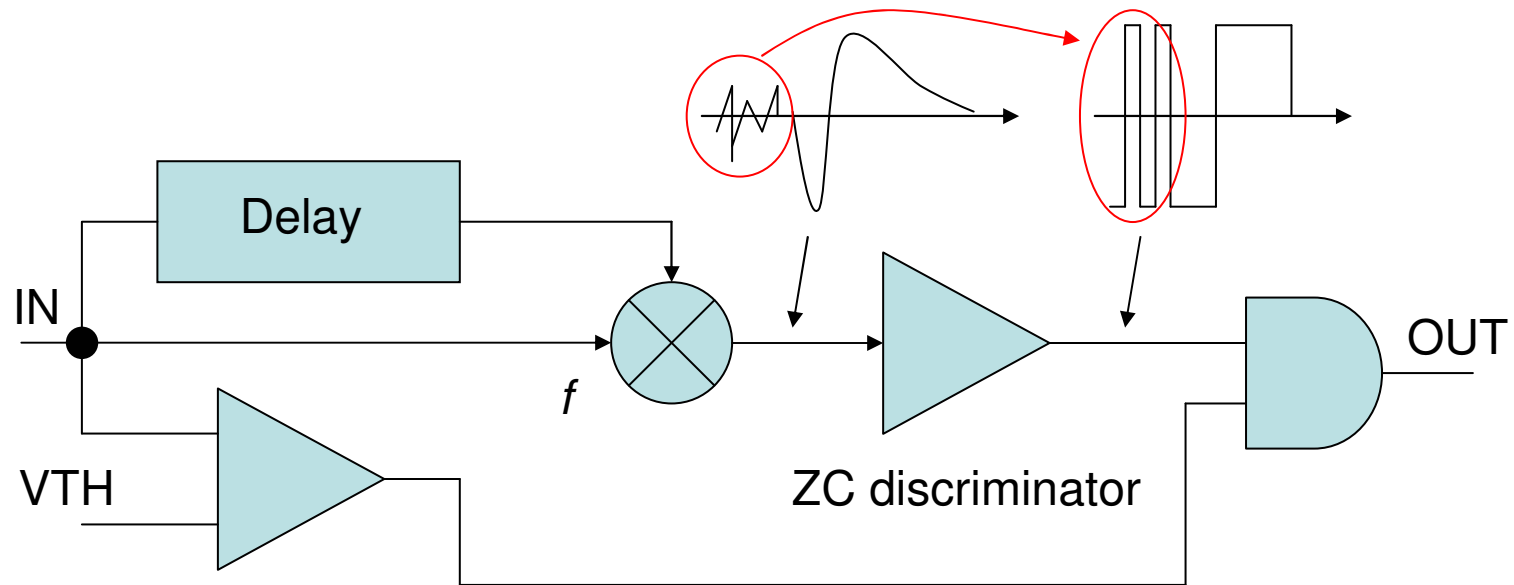


- Noise produces inherent noise switching at output of ZCD
- Need parallel leading-edge discriminator to mask noise switching
- Noise switching is not eliminated



# ZCD w/ hysteresis

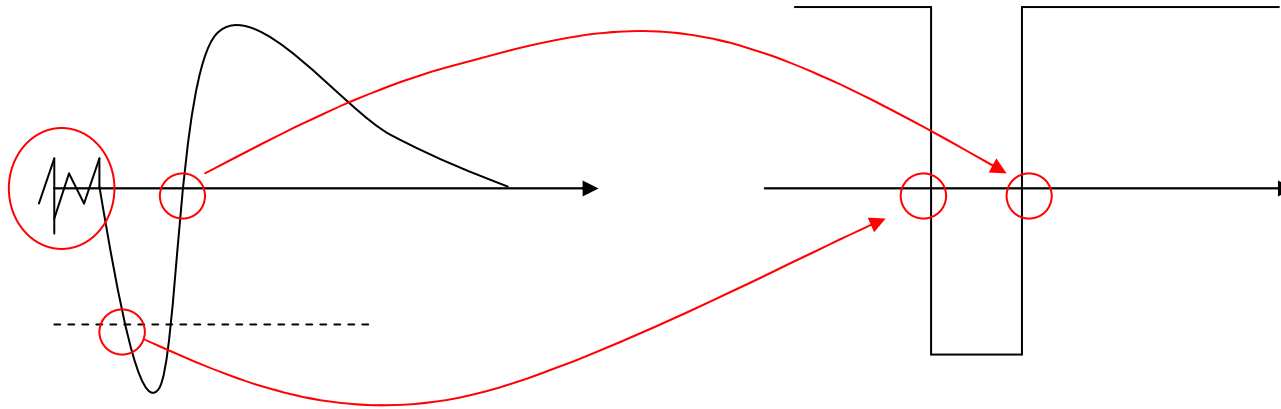

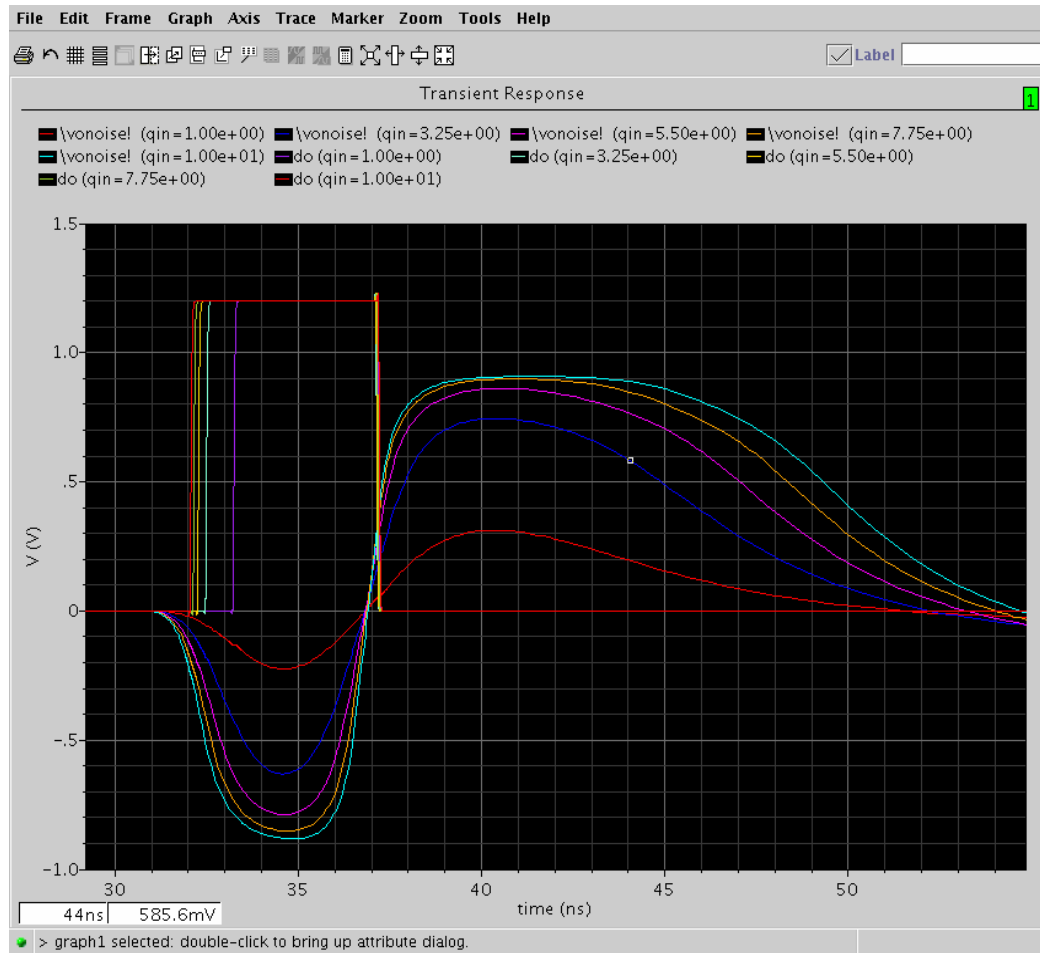- ZCD “arms” when the bipolar signal crosses a certain threshold
- Switching noise is eliminated
- Additional fast block w/o offset compensation => may introduce some time walk





8/10/08

NA62 CFD - Sorin Martoiu





10

# Measurements

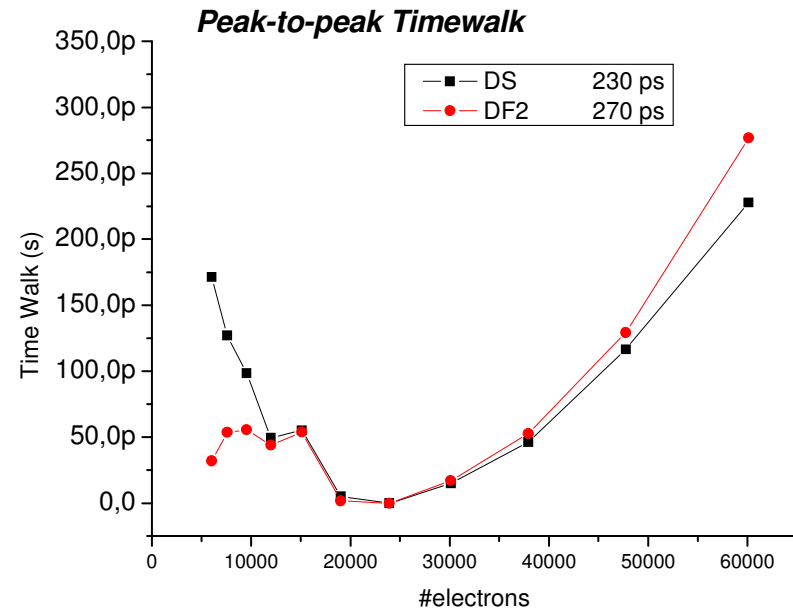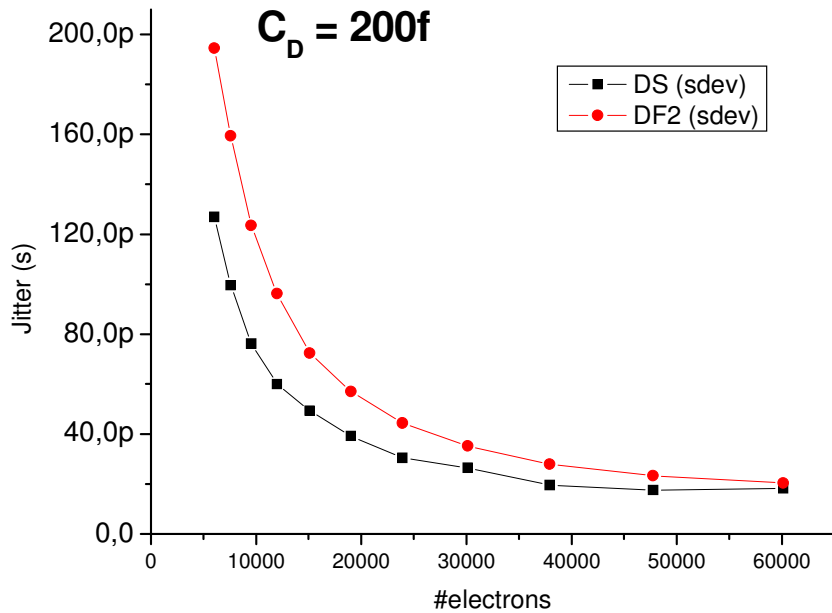

	Jitter @14ke (ps)	Jitter @6ke (ps)	TW(p-p) (ps)	LandauStd @22ke (ps)	LandauStd @14ke (ps)
DF1	73	195	277	92	93,7
DS	50	127	228	73,5	75,02


# Landau Correction 14ke<sup>-</sup>

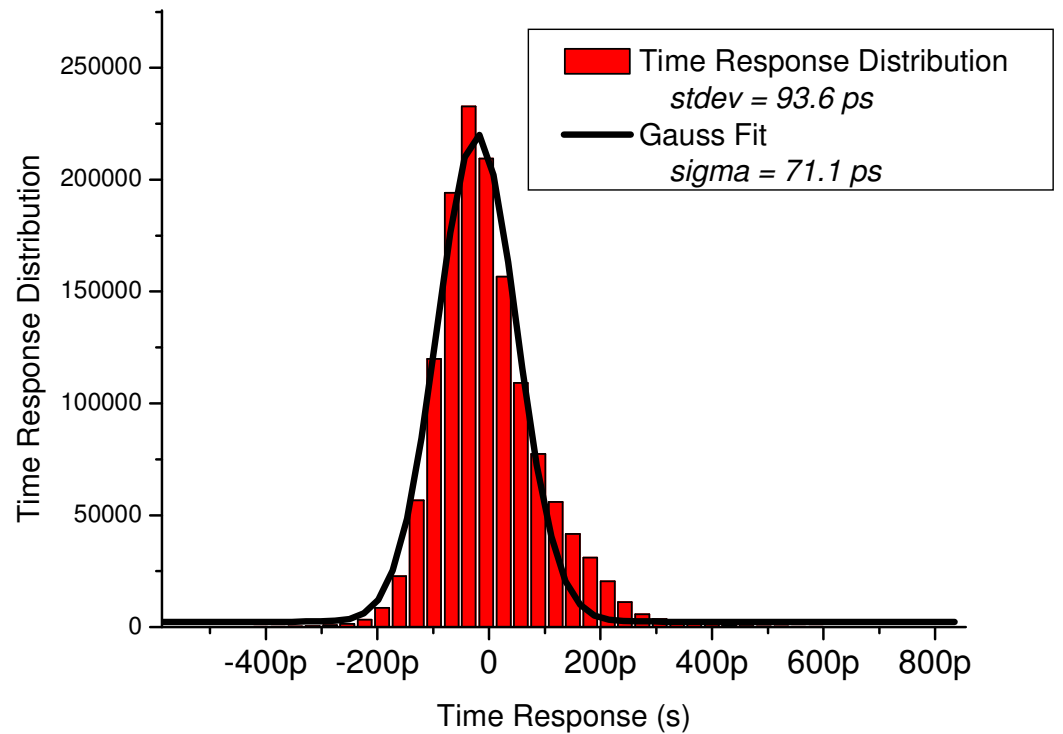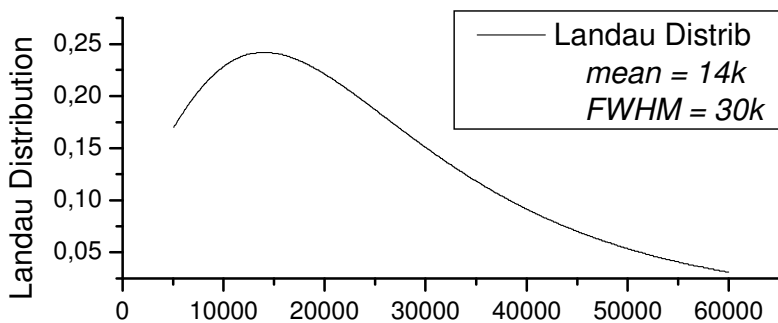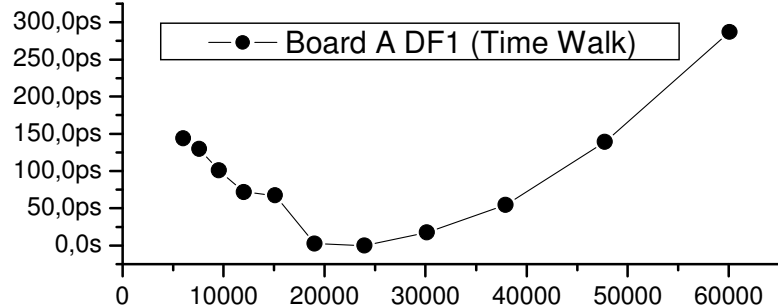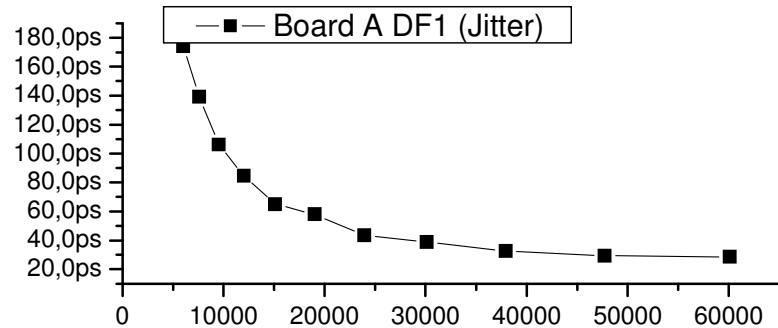


# New Prototype

- LP input transistor
  - Bipolarity
  - Noise penalty
- Fully differential preamplifier
- Leakage current compensation


# SE Preamp I

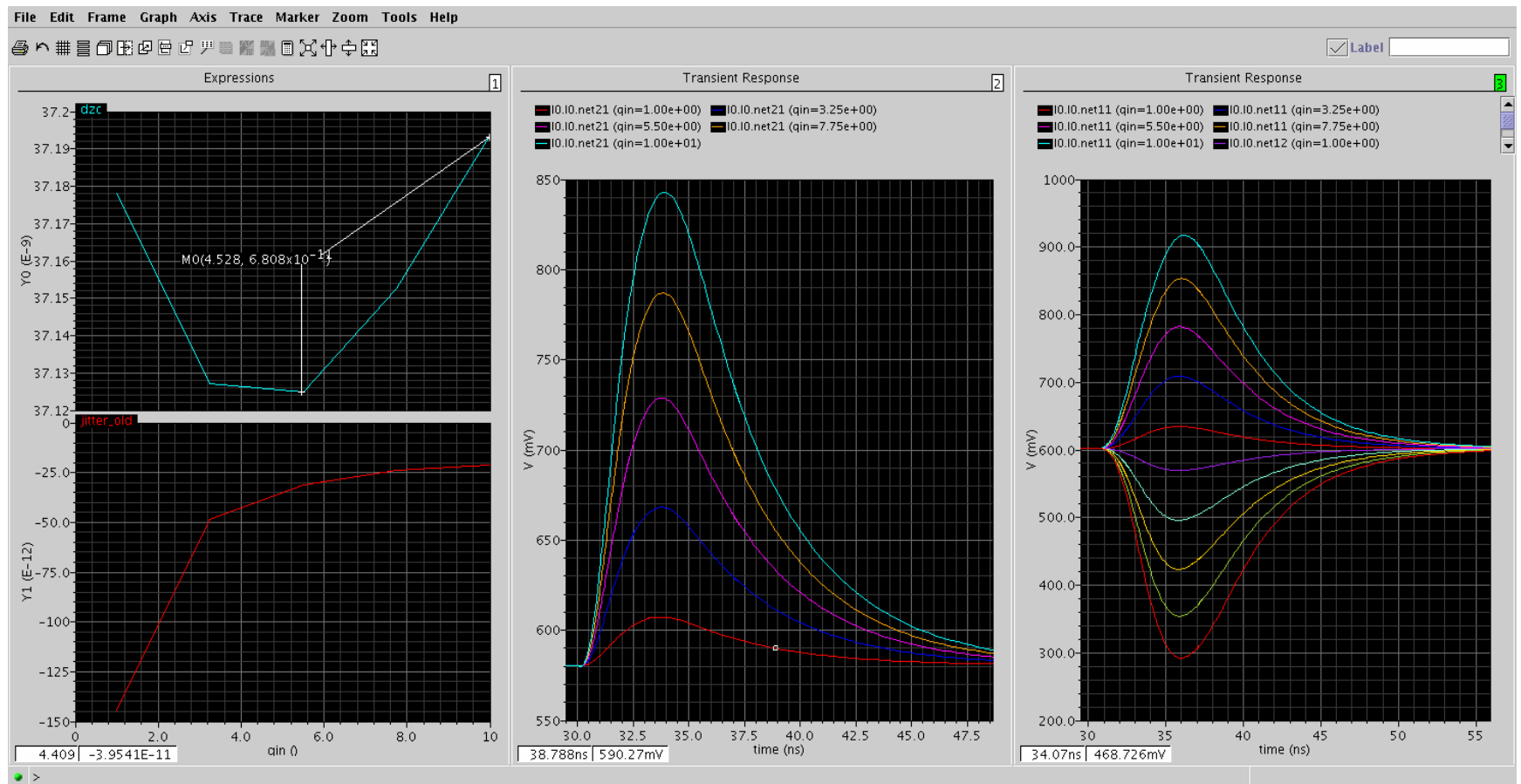

# SE Preamp II

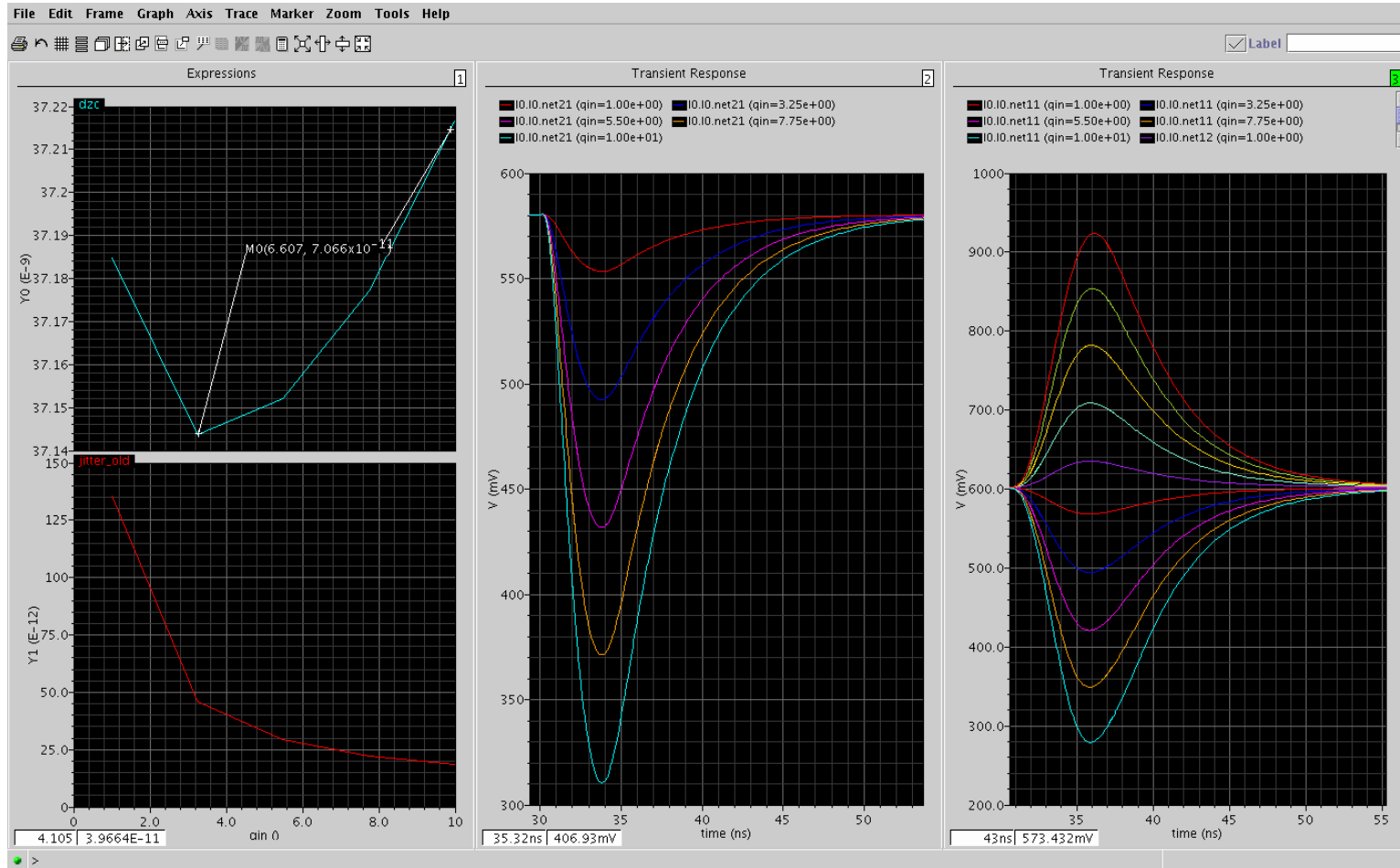

# Differential Preamp

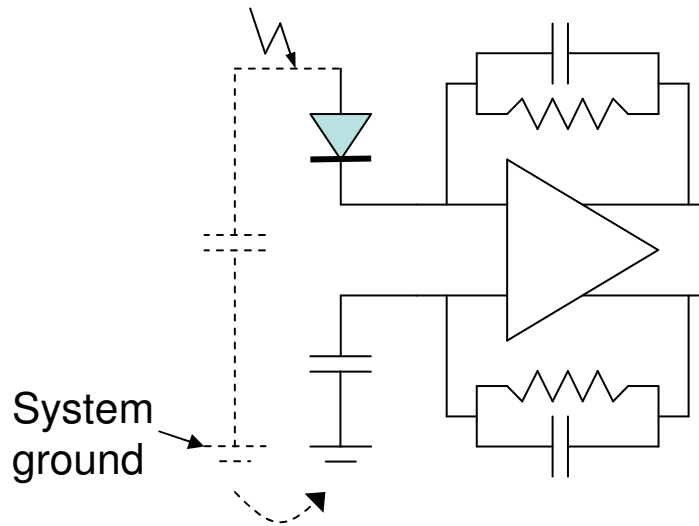


2 possible grounding schemes:

a) System ground

- Local spur-noise injection
- HV separation

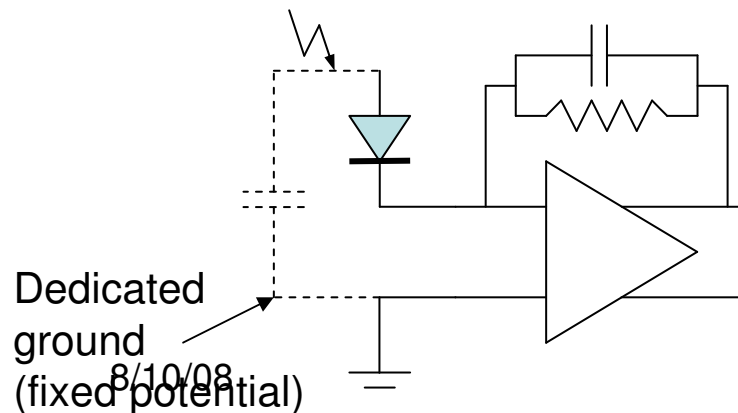b) Dedicated ground

- Potential HV risk
- Better performance (speed and noise)







# Differential Preamp

- Under-compensated
  - Still stable without detector
- Class-AB
- Low CMFB phase margin (40 - 50 deg)
- Leakage compensation slow servo-loop


# Differential Preamp

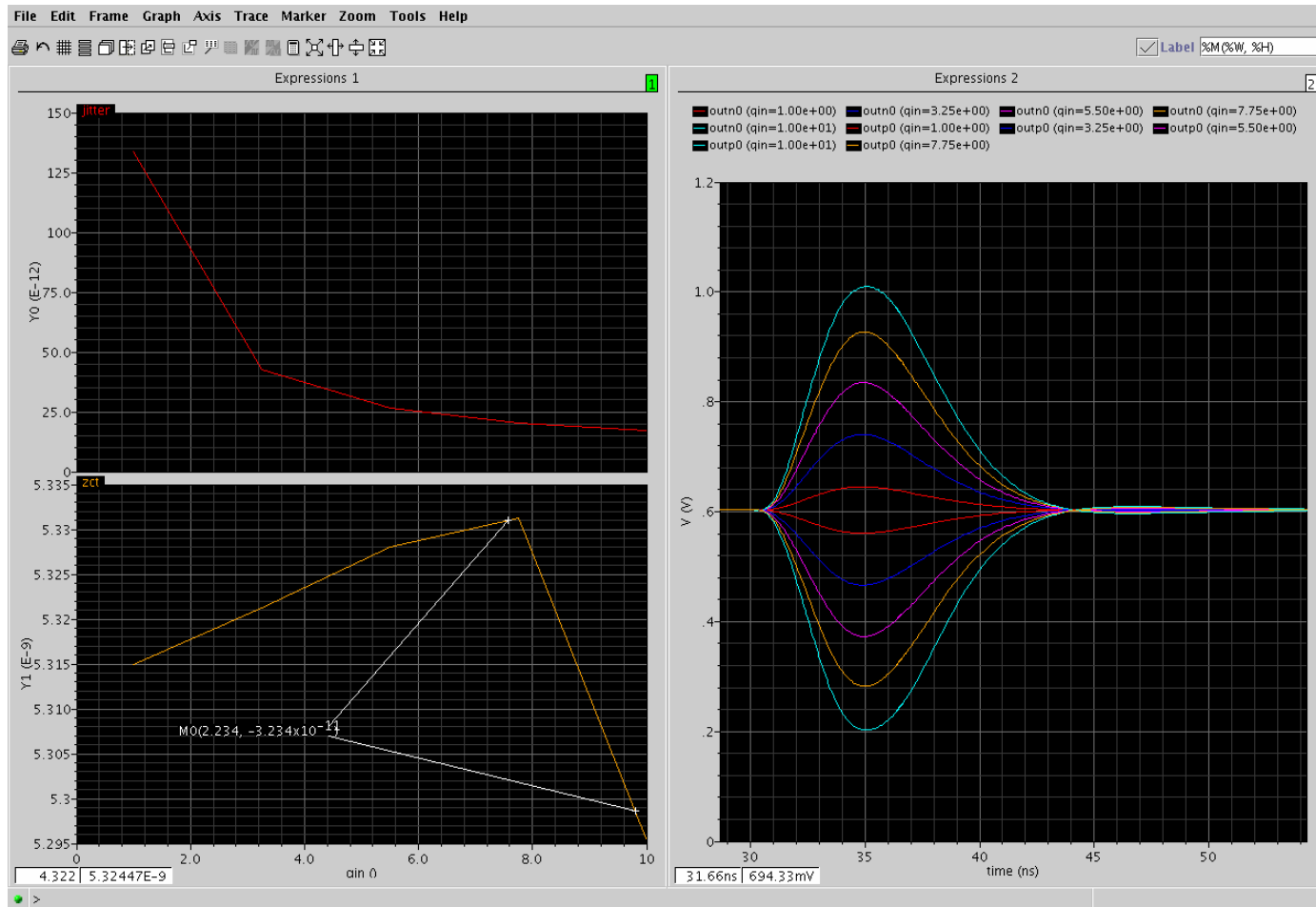


# Tail Cancellation

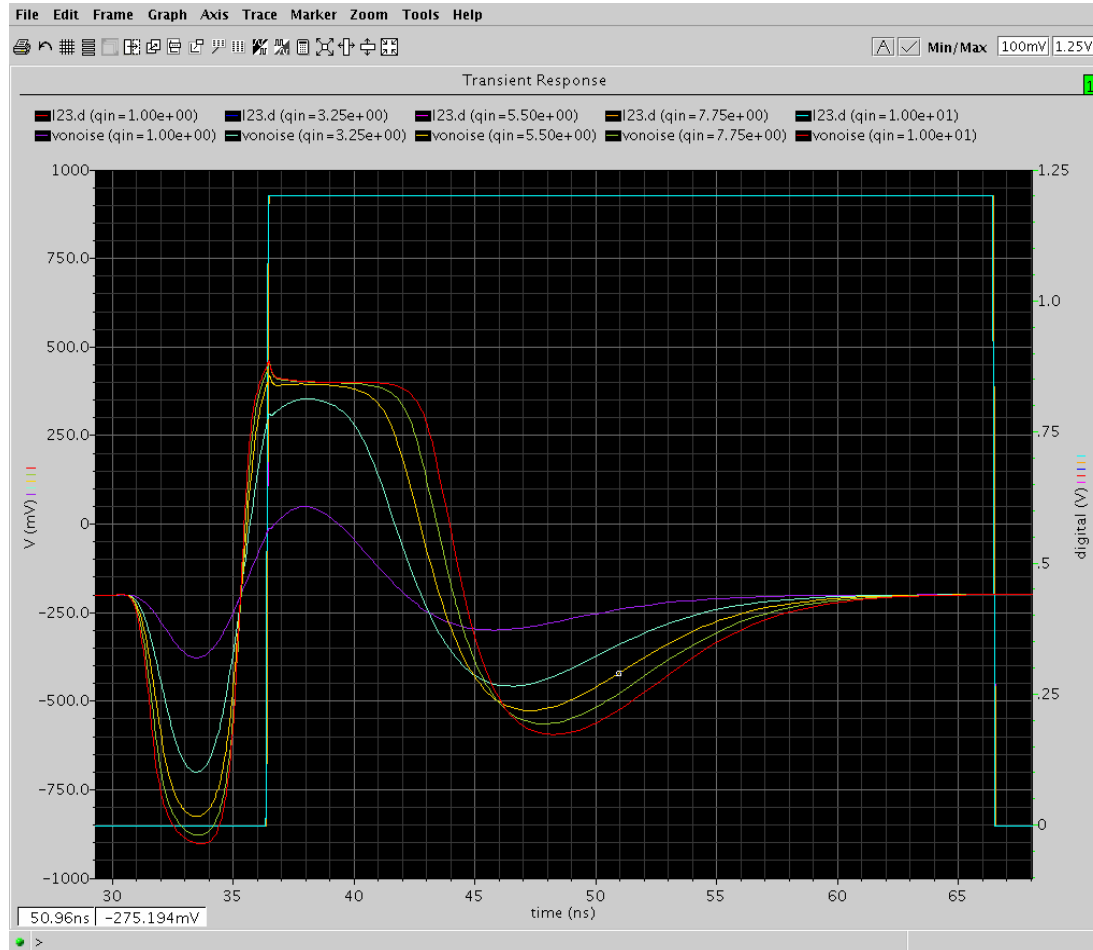


# Wilkinson TDC

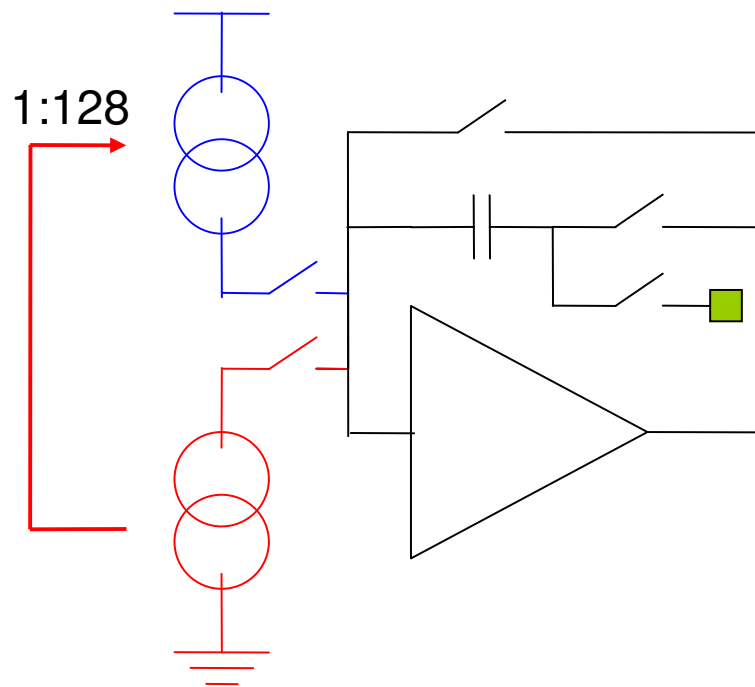

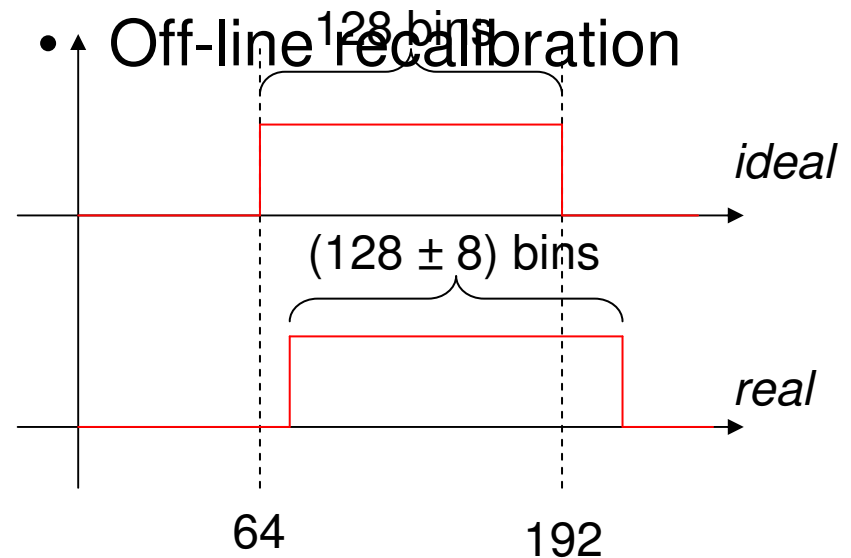- ~16 LSB range mismatch (p-p)
- 4-5 bit calibration DAC
- Off-line recalibration



# TDC

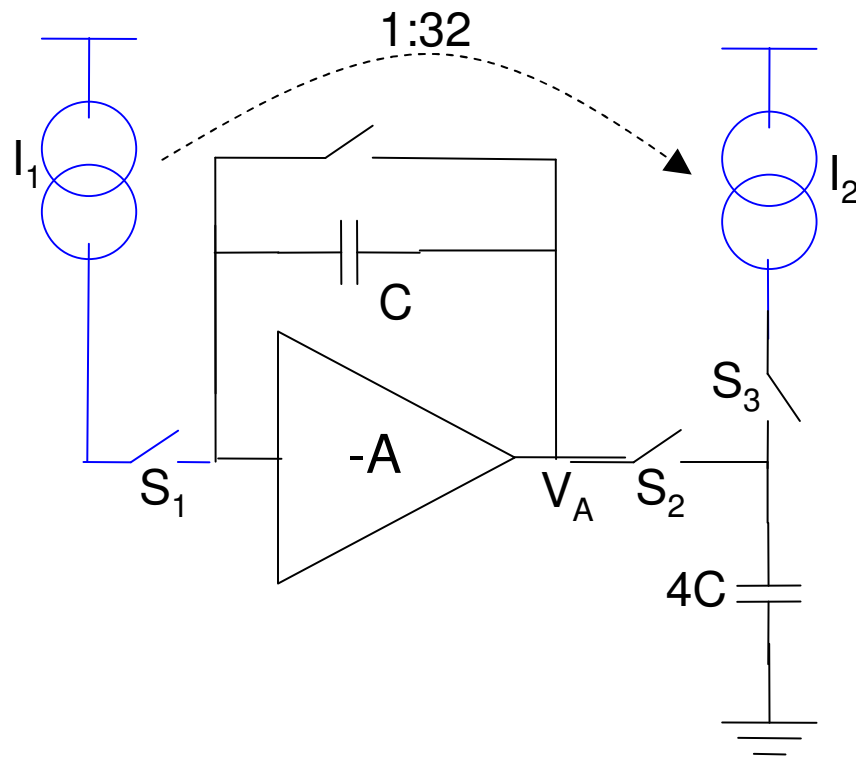

## Modified Wilkinson TDC:

1.  $S_1$ :  $I_1$  charges  $C$  for  $t_x$
2.  $S_2$ :  $V_A$  potential transferred to  $4C$  (charge transferred to  $4C$  is 4 times the charge stored on  $C$ )
3.  $S_3$ :  $I_2$  charges  $4C$  to the initial voltage

## Advantages:

- Current ratio is reduced by the capacitor ratio
- Better matching of same polarity current sources

# Power Consumption

	$I_{DD}$	Power
Preamp	360 $\mu$ A	430 $\mu$ W
CFD + Limiting Amp + ZCD	120 $\mu$ A	144 $\mu$ W
TDC	80 $\mu$ A	100 $\mu$ W
Total	560 $\mu$ A	0.67 mW