



TDC per pixel option: architecture description

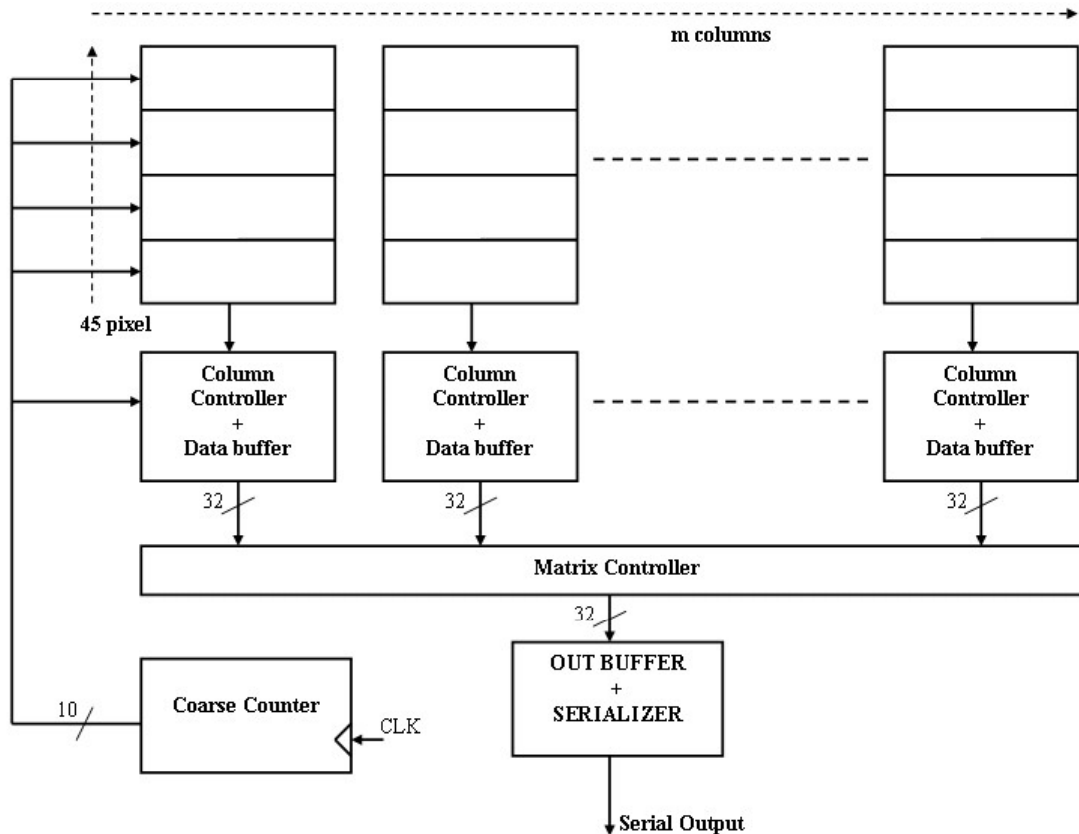
A. Rivetti




Basic features



- The time walk correction:
 - Done inside the pixel with a **Constant Fraction Discriminator (CFD)**.
- Time digitization:
 - Coarse time: **Gray counter** distributed to the pixels.
 - Fine measurement: **Time to Amplitude (TAC)** converter in each pixel
- Data derandomization and transmission:
 - **Four-level buffer** inside the pixel and **high-speed serial links** for off-chip transmission



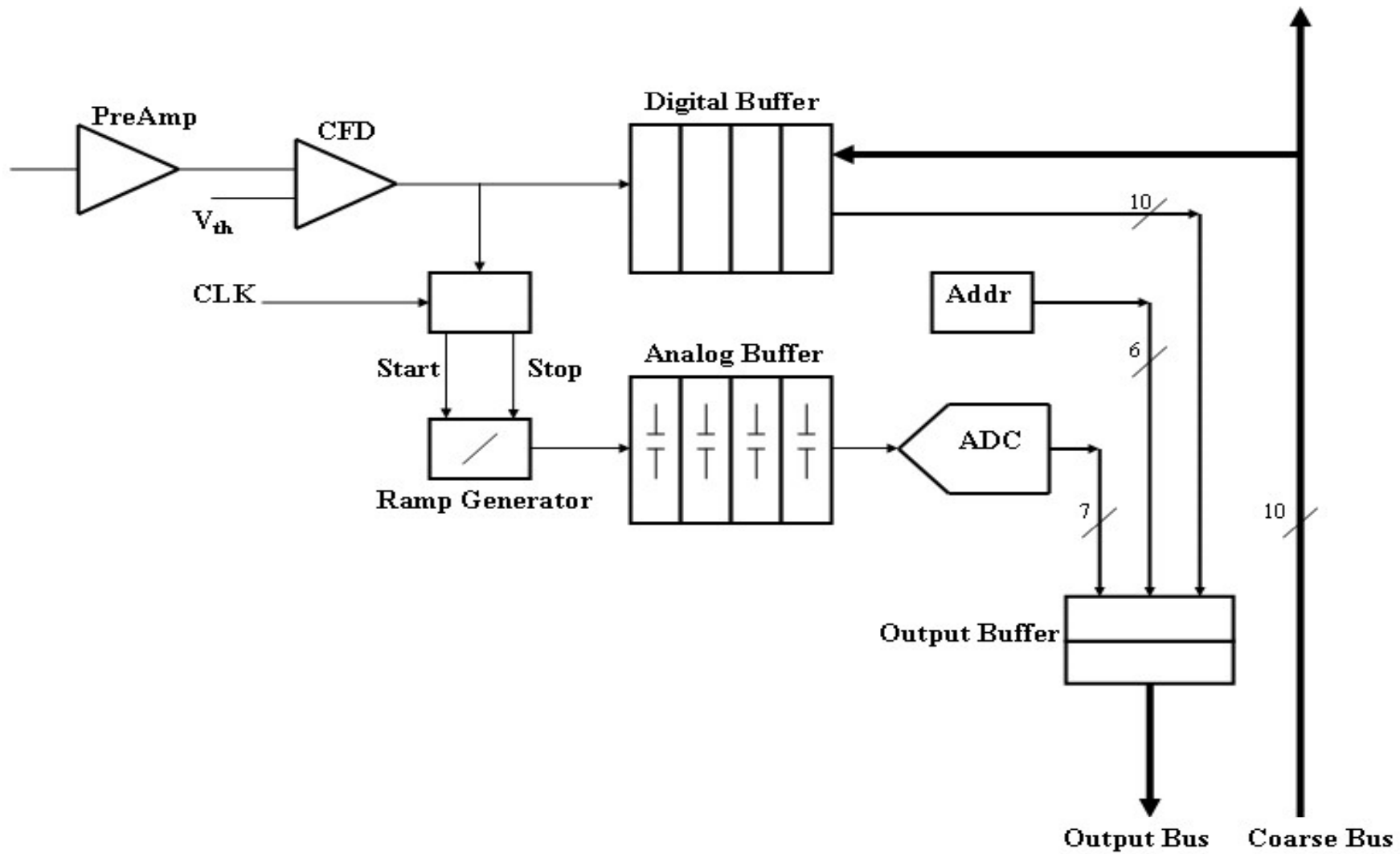- System Clock: **160 MHz**
- Global coarse counter (**10 bits**)
- Each column of 45 pixels is read-out by its own controller (**End-of-Column controller**)
- Only **digital buses** between pixels and EoC controller
- The Matrix controller will merge data coming from m columns (where m depend on the link speed)
- Derandomization done inside the pixel. **Token-based read-out scheme.**






Pixel operation





- A coarse counter counts the 160 MHz clock. The word is **Gray-encoded** and distributed to the pixels.
- The value of the coarse counter is latched into **local pixel registers** when the CFD fires.
- At the same time a constant current source starts **charging-up a capacitor**.
- The charging process is stopped at the first leading edge following a trailing edge of the master clock.
- The analogue value stored in the capacitor is digitized with a **Wilkinson ADC** to provide the **fine-time** measurement.
- The range of the TDC spans three master clock cycles to guarantee adequate analogue measurement and accommodate time mismatch between the coarse and fine counter
- TDC time bin: **97.6 ps**




Timing waveforms

 

How many buffers?

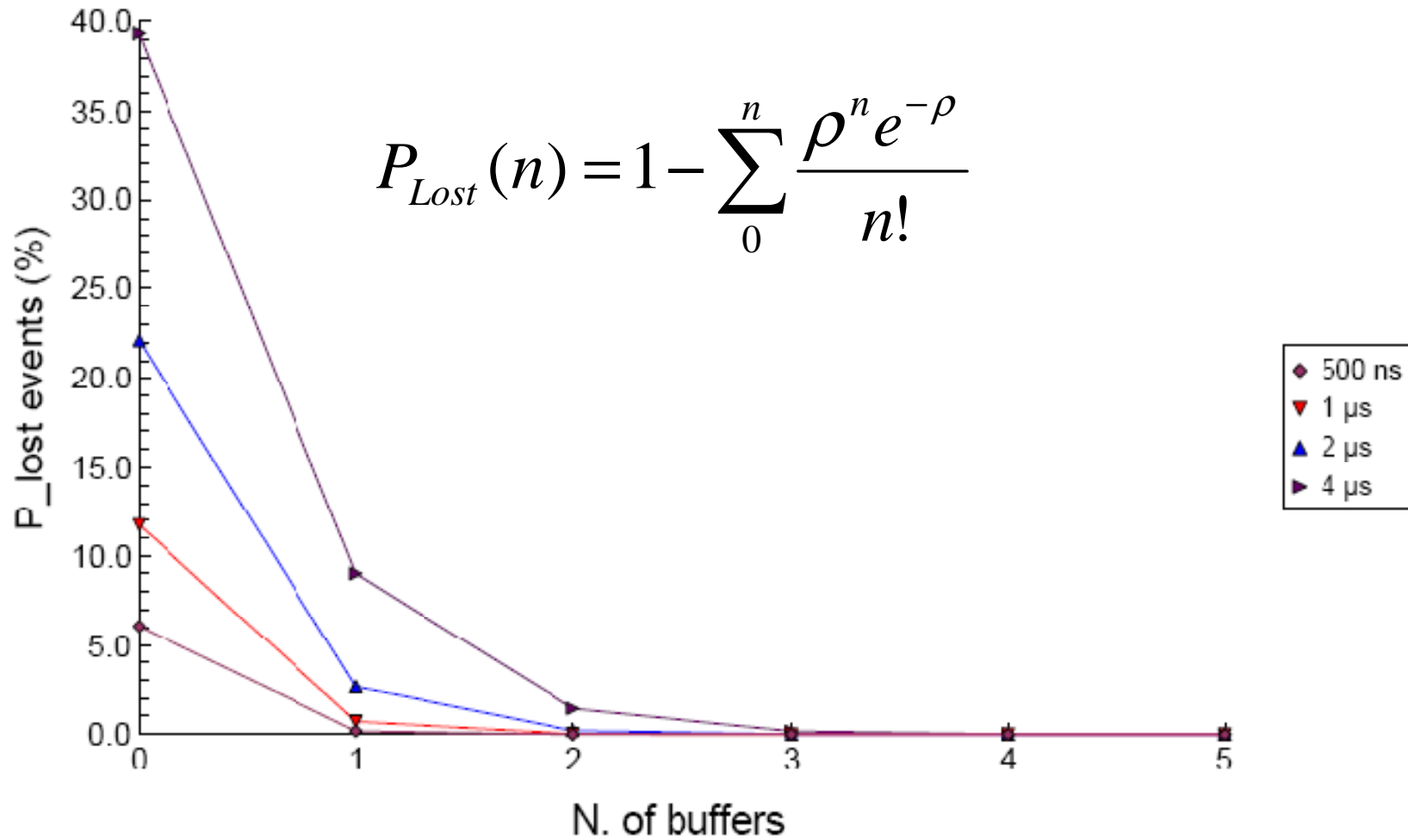 

How many buffers?

 





Advantages and drawback






- Optimal usage of **pixel area** (300 μm x 300 μm).
- **Simplified** read-out scheme.
- **No analogue signal** propagation **outside** the pixel...
- Lower system clock (160 MHz vs 320 MHz.)

But...

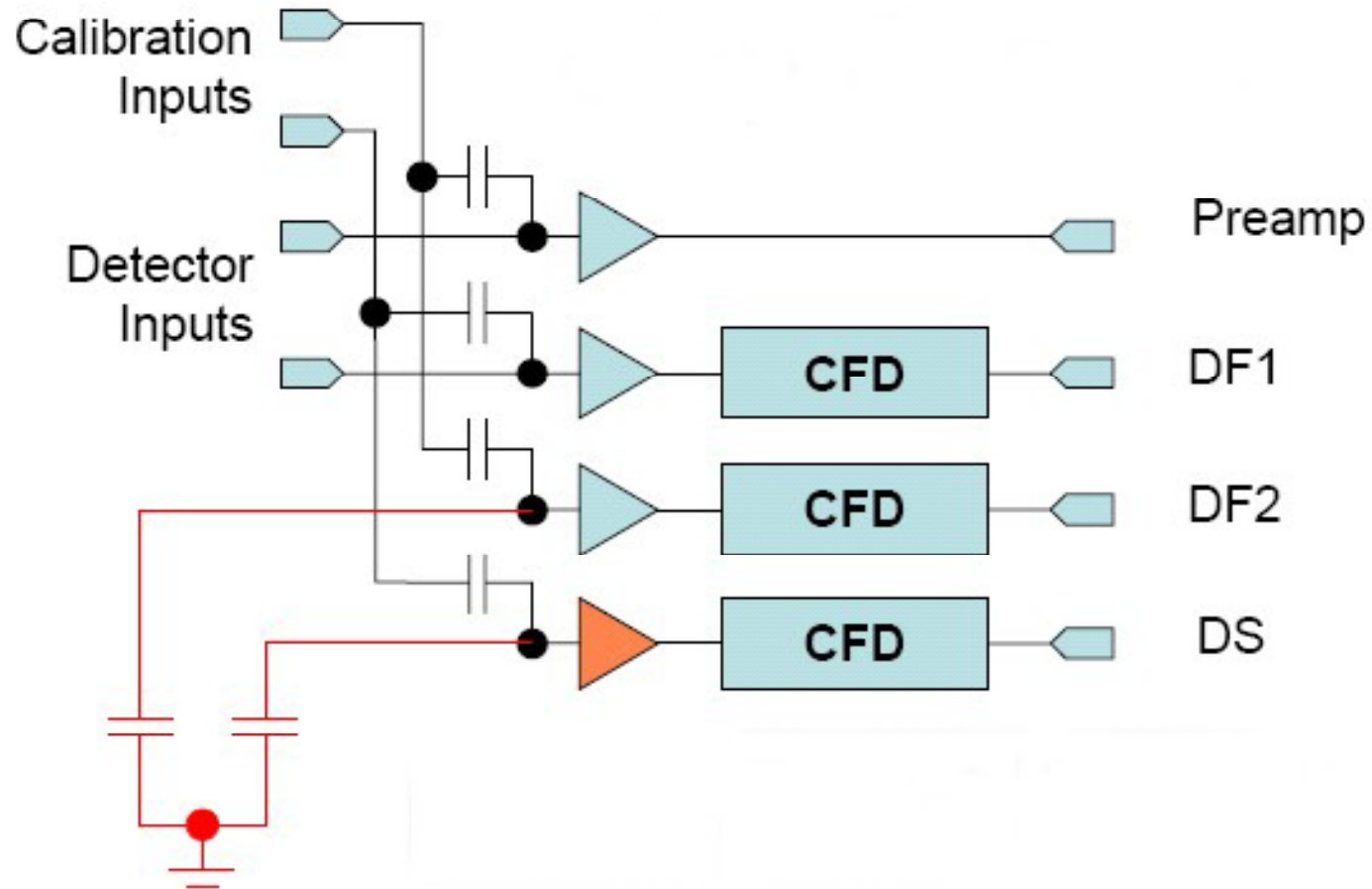 - More **digital activity** close to the front-end.
- More digital logic in critical area => **SEU tolerance** required.
- Needs careful **clock distribution over** the whole matrix.



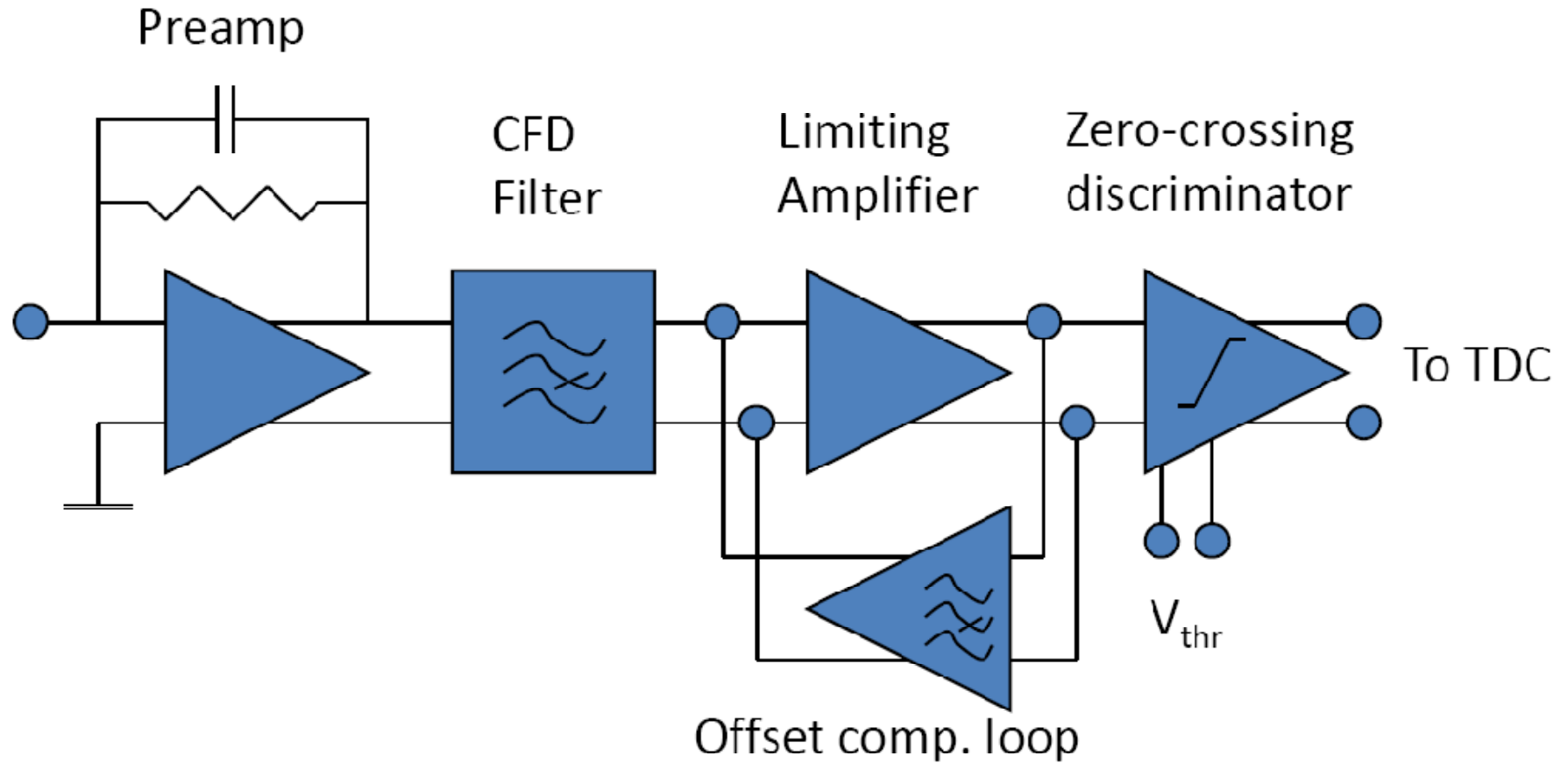 

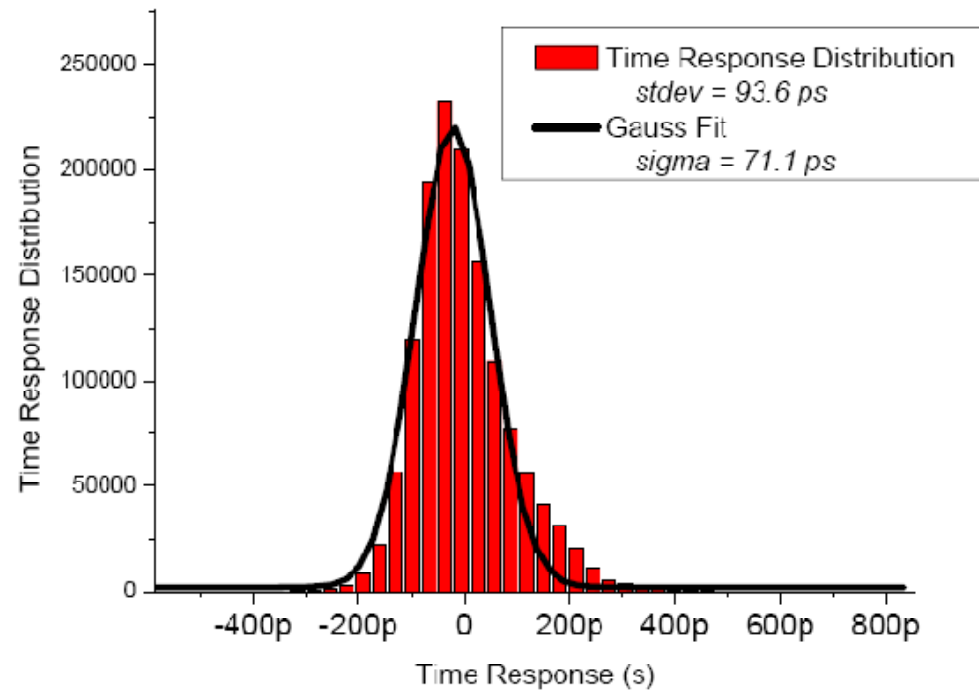

- Total resolution calculated through Monte-Carlo based on the jitter and residual walk measurements of the first prototype.



demonstrator chip: key points



- Full pixel design.
- Two full columns with 45 pixels each.
- One spare column with 15 pixels.
- Final End of Column logic
- Not final data transmission scheme



TDC on pixel demo chip

