

# NA62 front end for end of column demonstrator

Jan Kaplon/Pierre Jarron


# Architecture

Preamp; buffered cascode (NMOS input transistor), resistive feedback (200k)

Gain; 70mV/fC (27mV/fC at preamp output)

Preamplifier AC coupled to shaper and discriminator stages

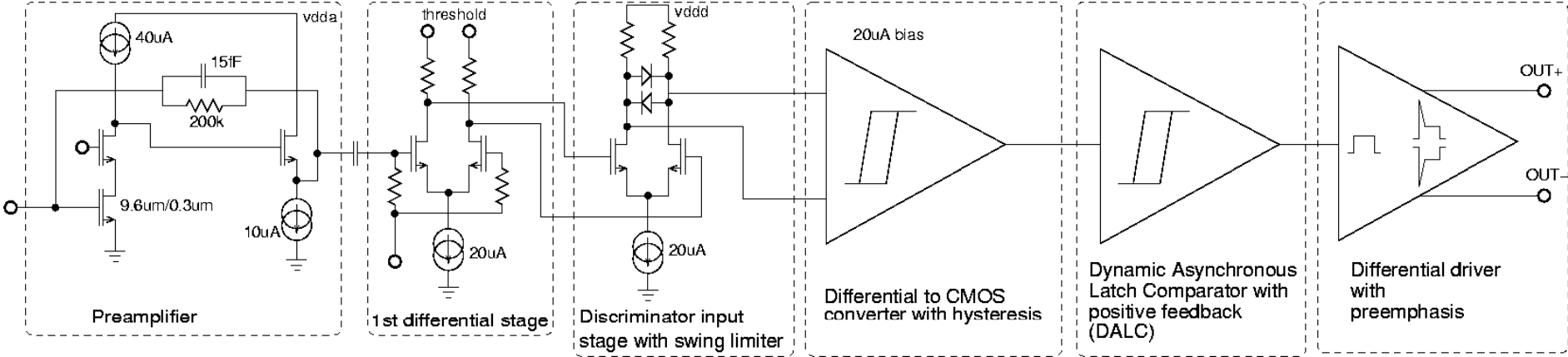Consumption (without transmission line driver) ; 120uA/pixel




Feedback ;

Cf=14 fF

Rf= 200k

Input transistor; NMOS 9.6/0.3um, 40uA bias


# Noise

 

5ns peaking time CR-RC<sup>2</sup>  
Input transistor bias; 40uA, Feedback resistor 200k $\Omega$   
Detector leakage; 20nA

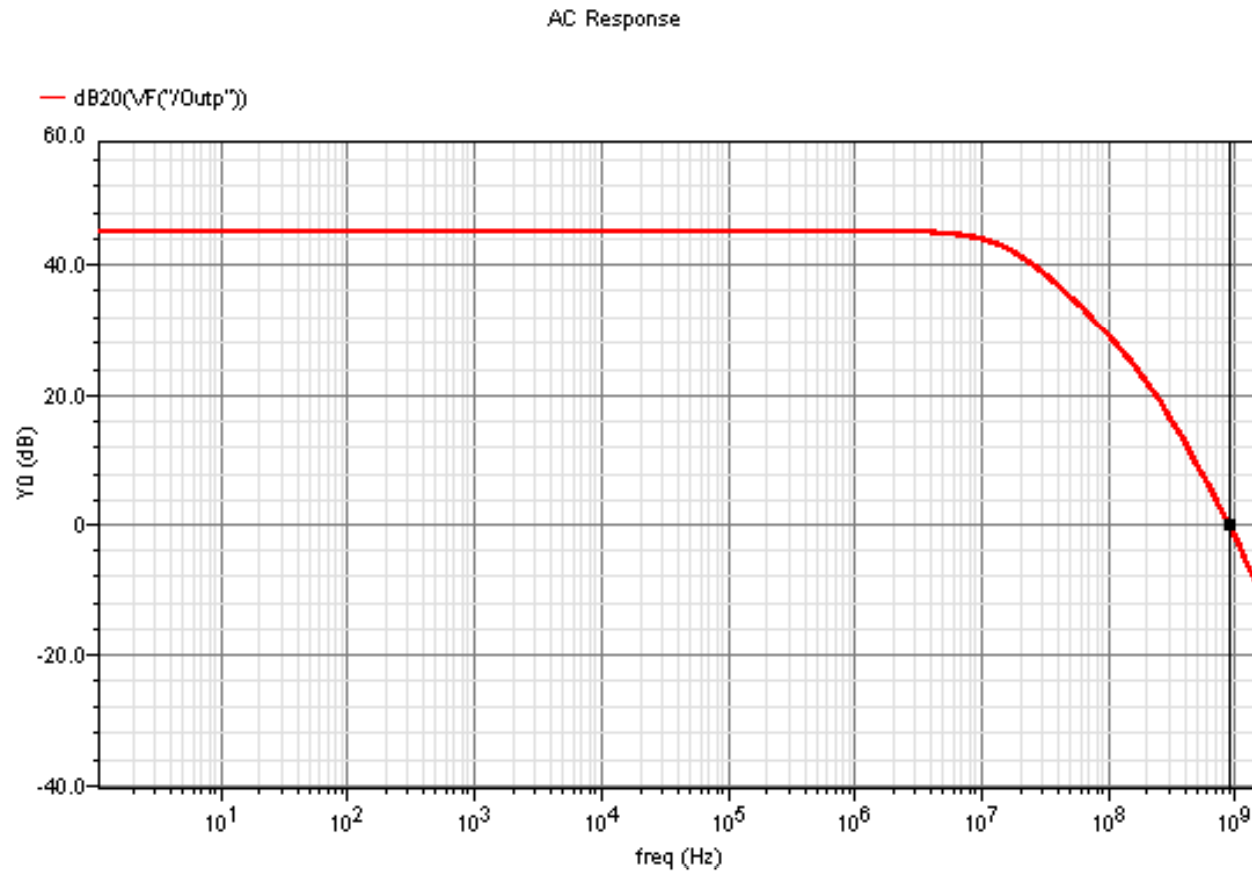
# Open loop gain simulation

Gain Bandwidth Product 900MHz (simulation for compensated cascode)




# Input impedance simulation

Input impedance 1 – 2k $\Omega$

 


# Phase margin simulation

Phase margin for Cinput 250fF ; 90°

 

 
# Phase margin simulation

Phase margin for Cinput 500fF ;  $87^\circ$



# Transient simulation

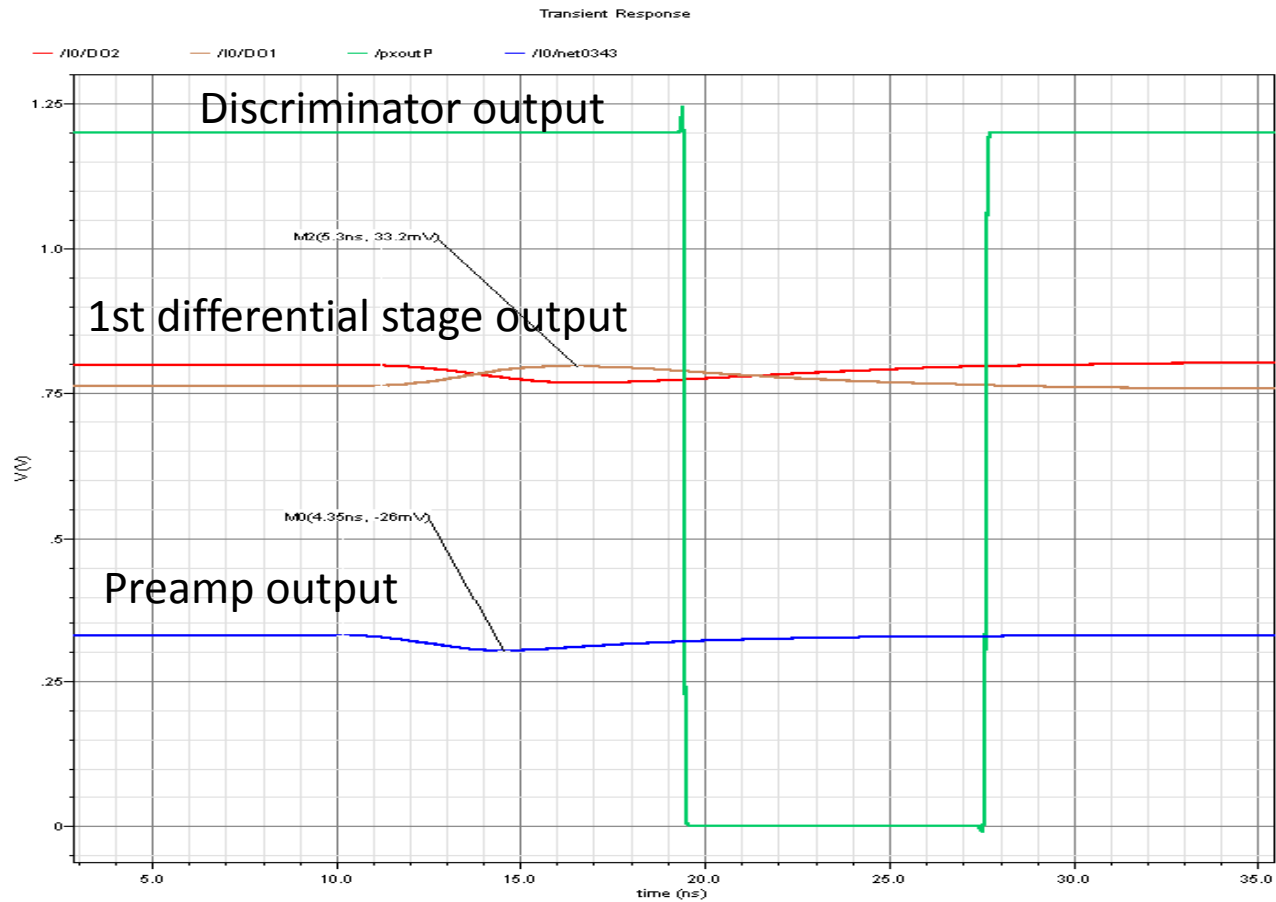


Peaking time; 4.5ns at preamp, 5.5ns at discriminator input



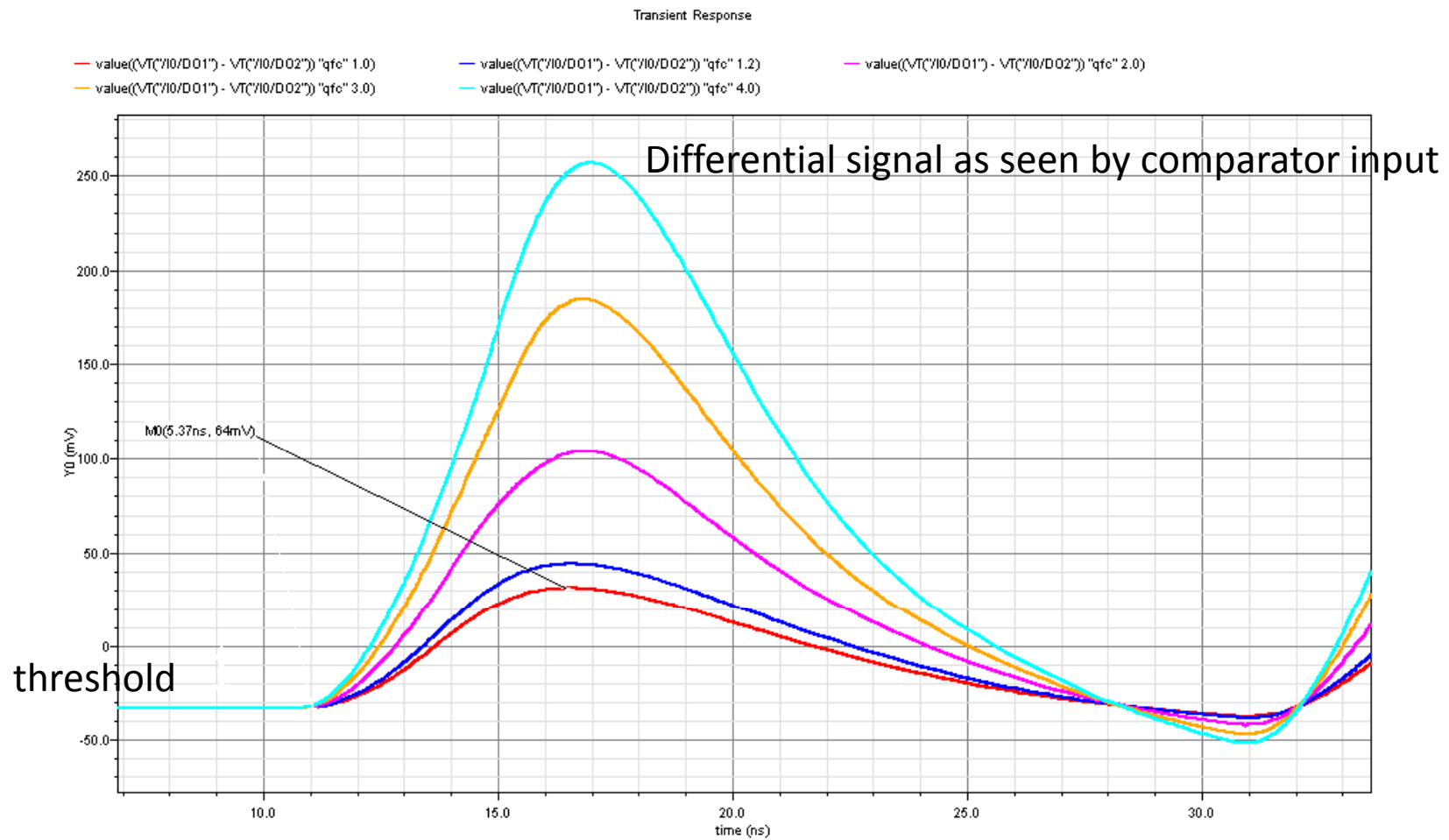
# Transient simulation

Good linearity and no degradation of peaking time up to 4fC (1,1.2, 3, & 4fC signals)




# Transient simulation

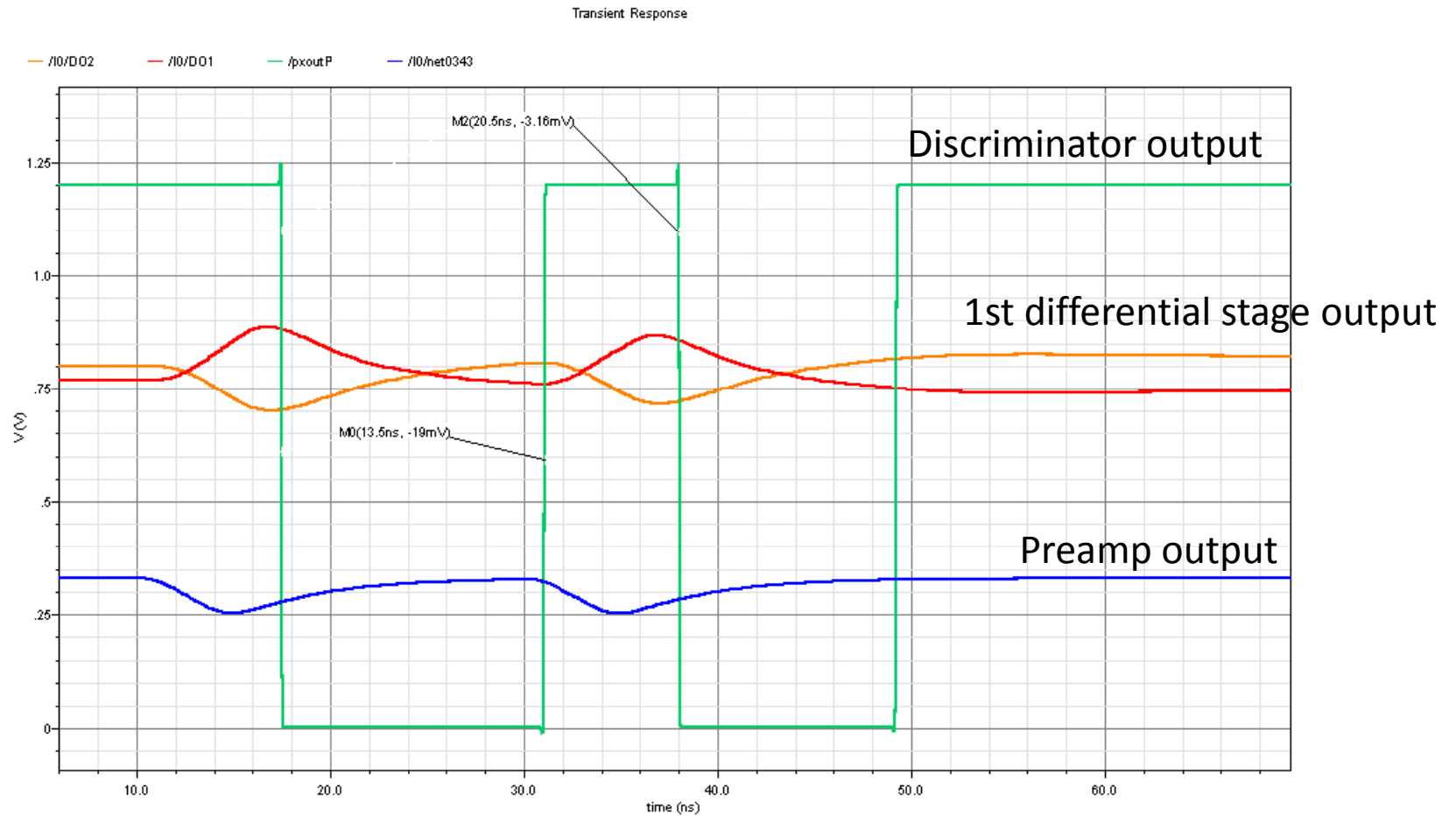

Double pulse resolution; 2 signals 3fC in 20ns distance at 0.7fC threshold

# Transient simulation

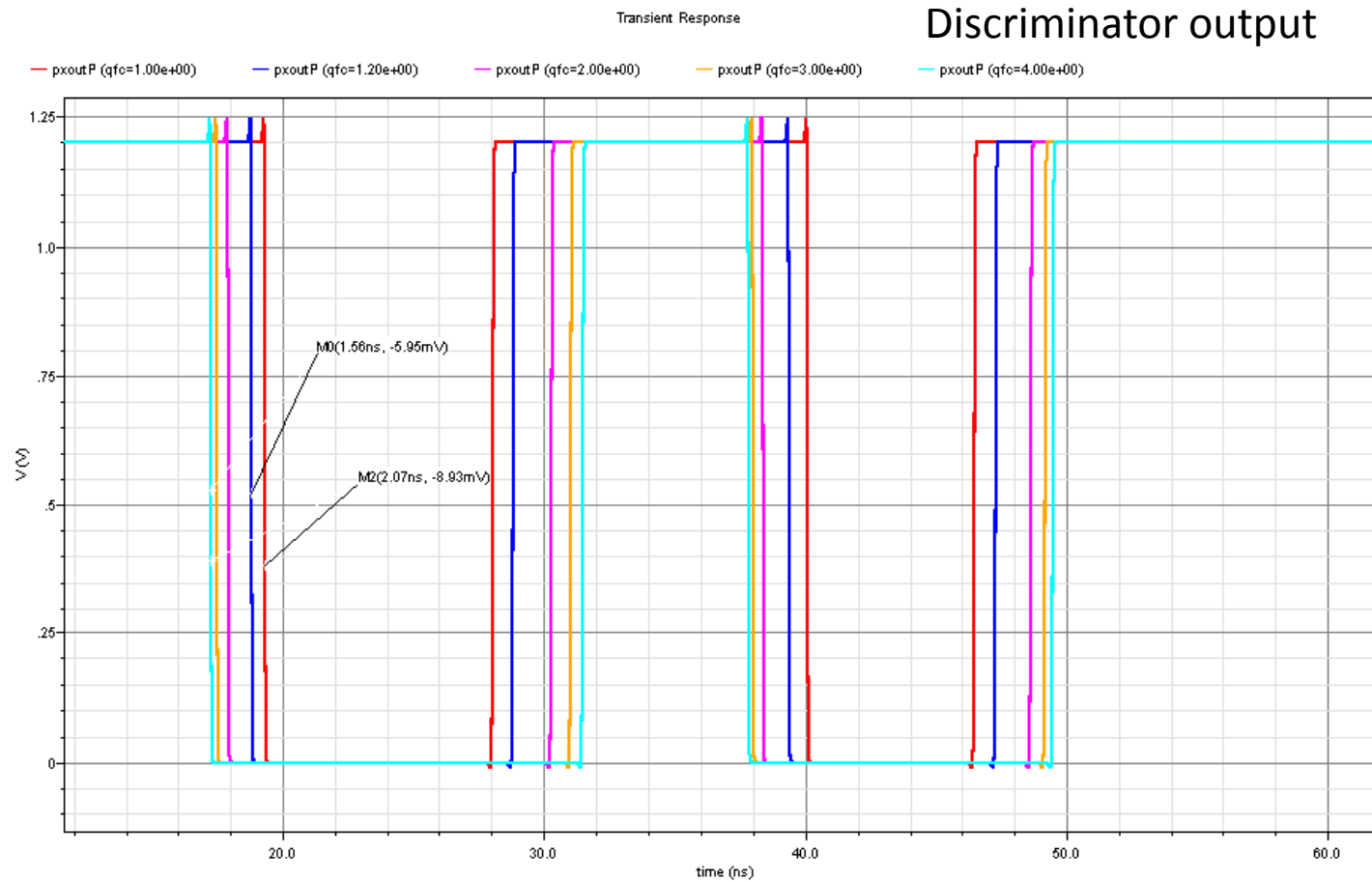


Walk; 1.5ns for 1.2 and 4fC (0.7fC threshold)

Walk; 2ns for 1 and 4fC (0.7fC threshold)

Pulse width; 8 to 14ns (1 to 4fC)



 
# PSRR (discriminator differential input)




Low and medium frequencies; 48dB, degrading after 1MHz

Worst case; 2dB at 100MHz (5dB for standard layout NMOS)

# PSRR

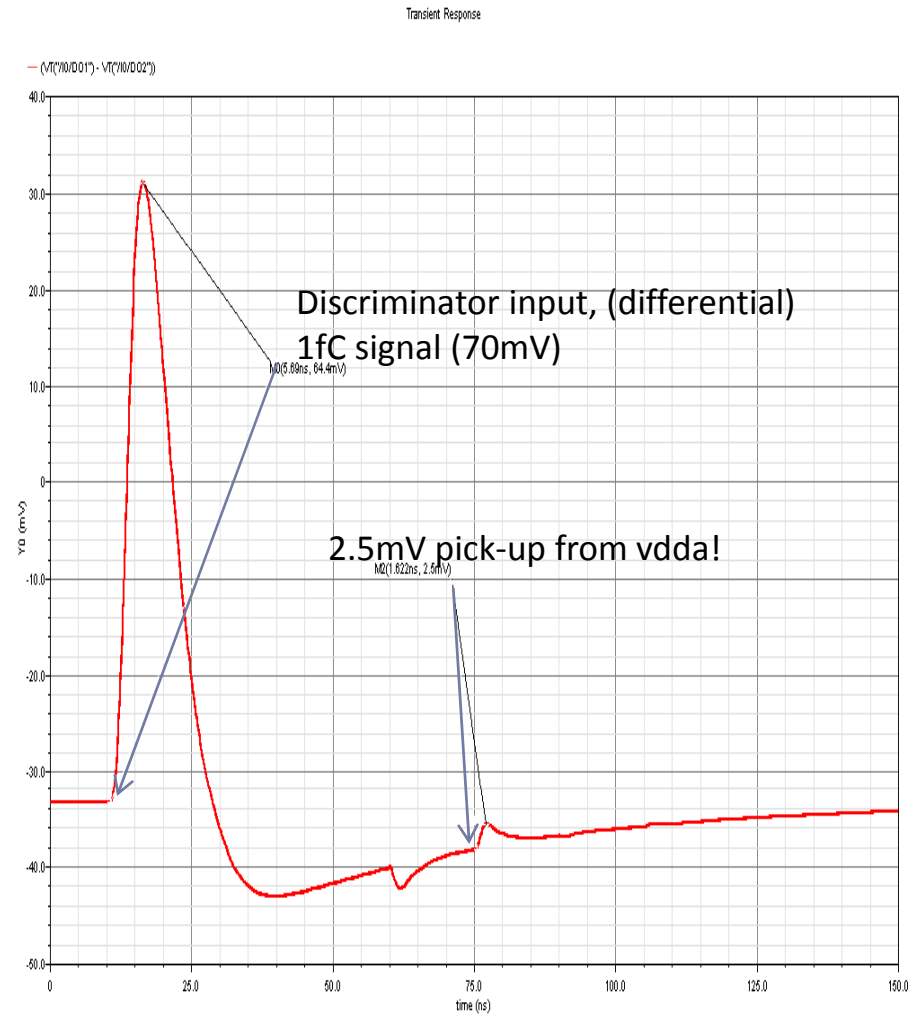 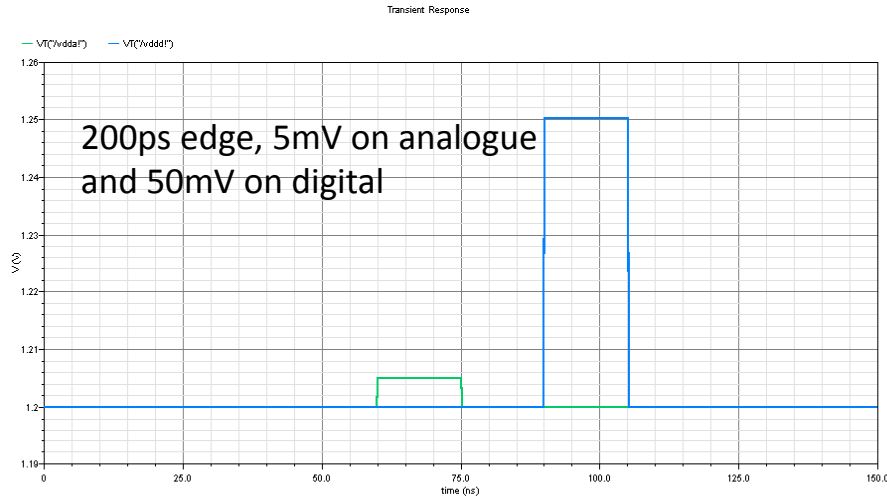
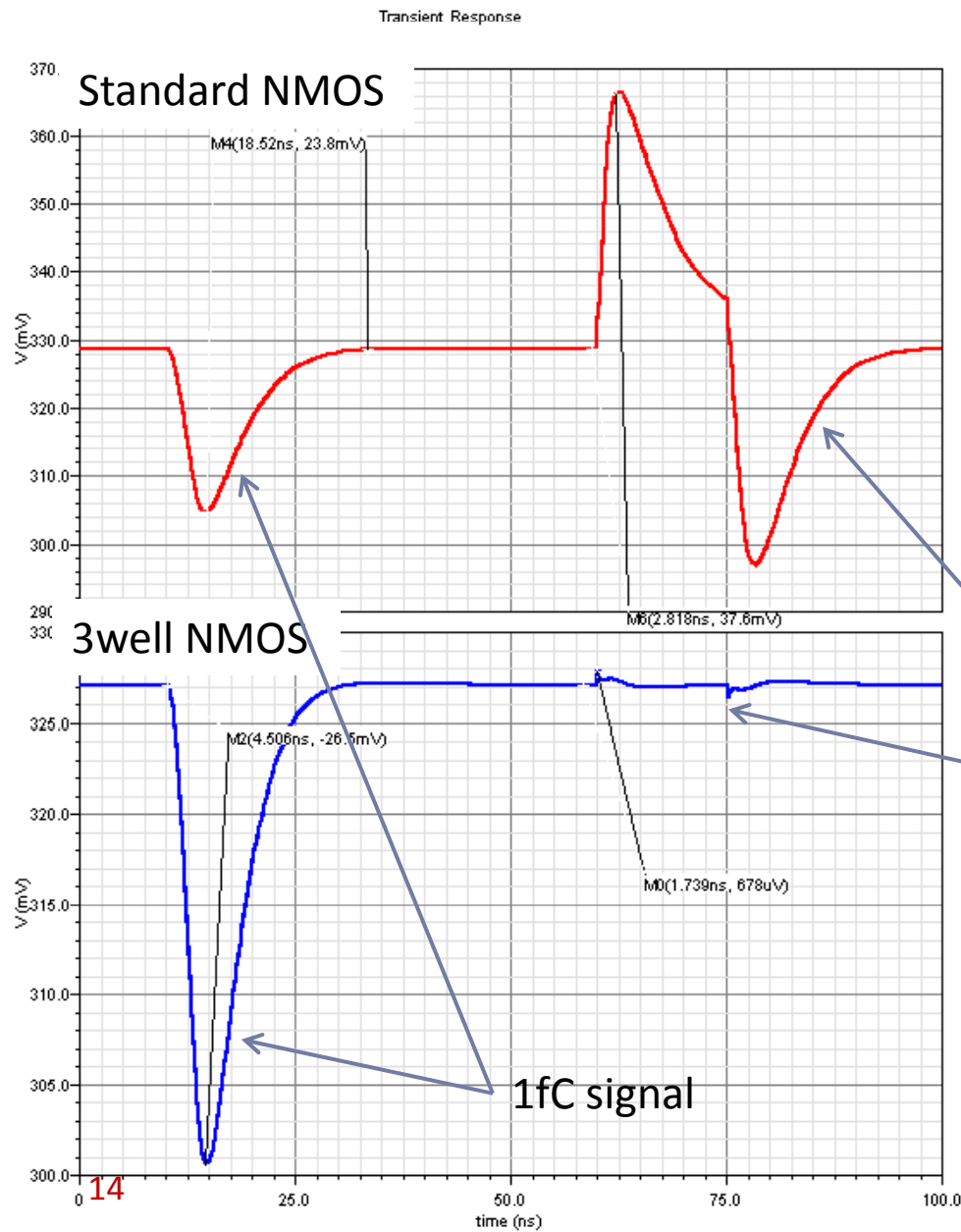
# Input stage, standard versus 3well NMOS




Comparison between standard and 3well NMOS susceptibility to substrate pick-up

5mV injection to substrate
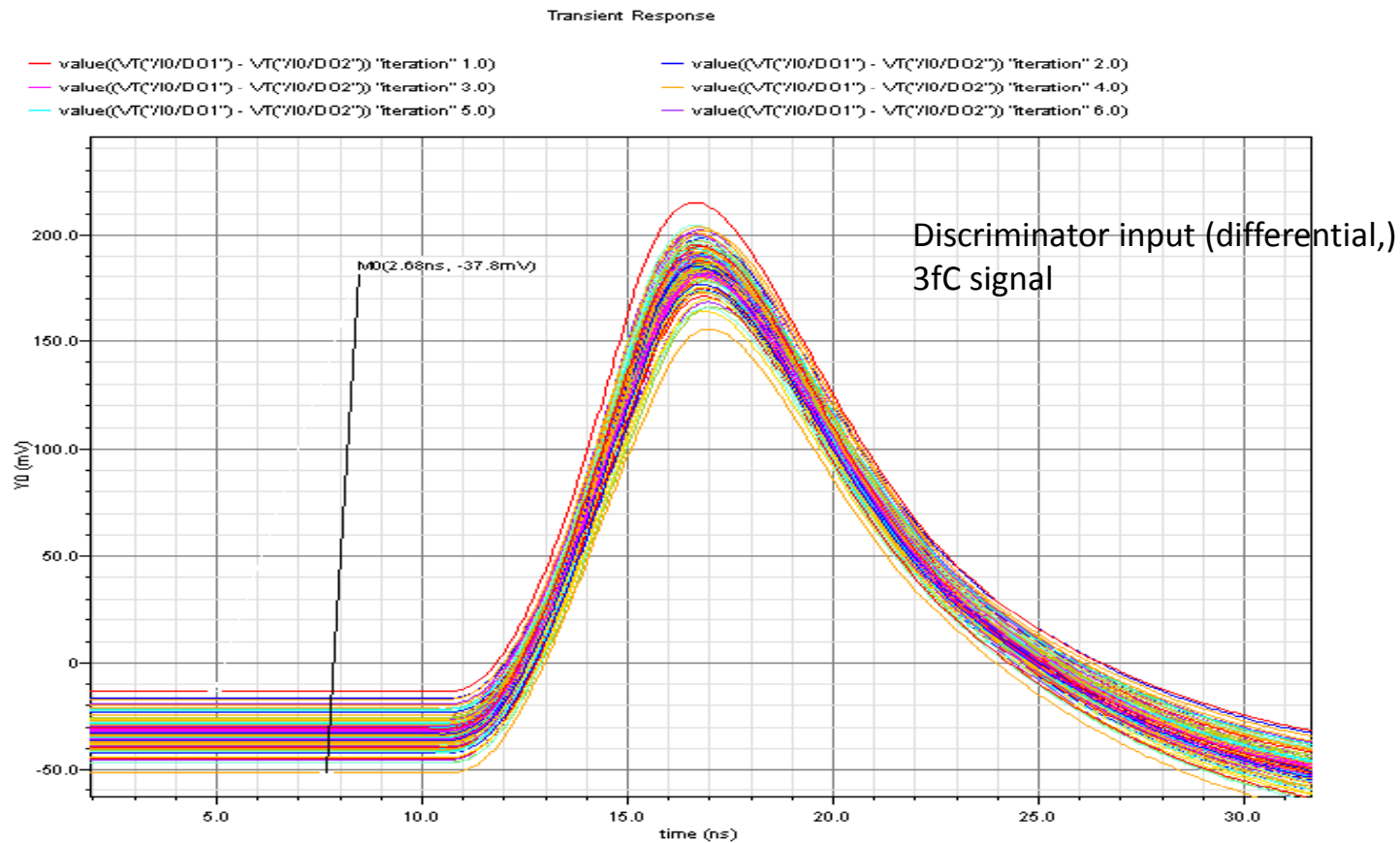
# Mismatch (no TRIM DACs)


3fC signal, mismatch 6mV RMS (0.1fC RMS) → minimum threshold without trimming 0.7fC

Assuming 5-bit TRIM DAC with 50mV range the mismatch can be minimized down to 1.5mV pk-pk (0.25mV RMS)


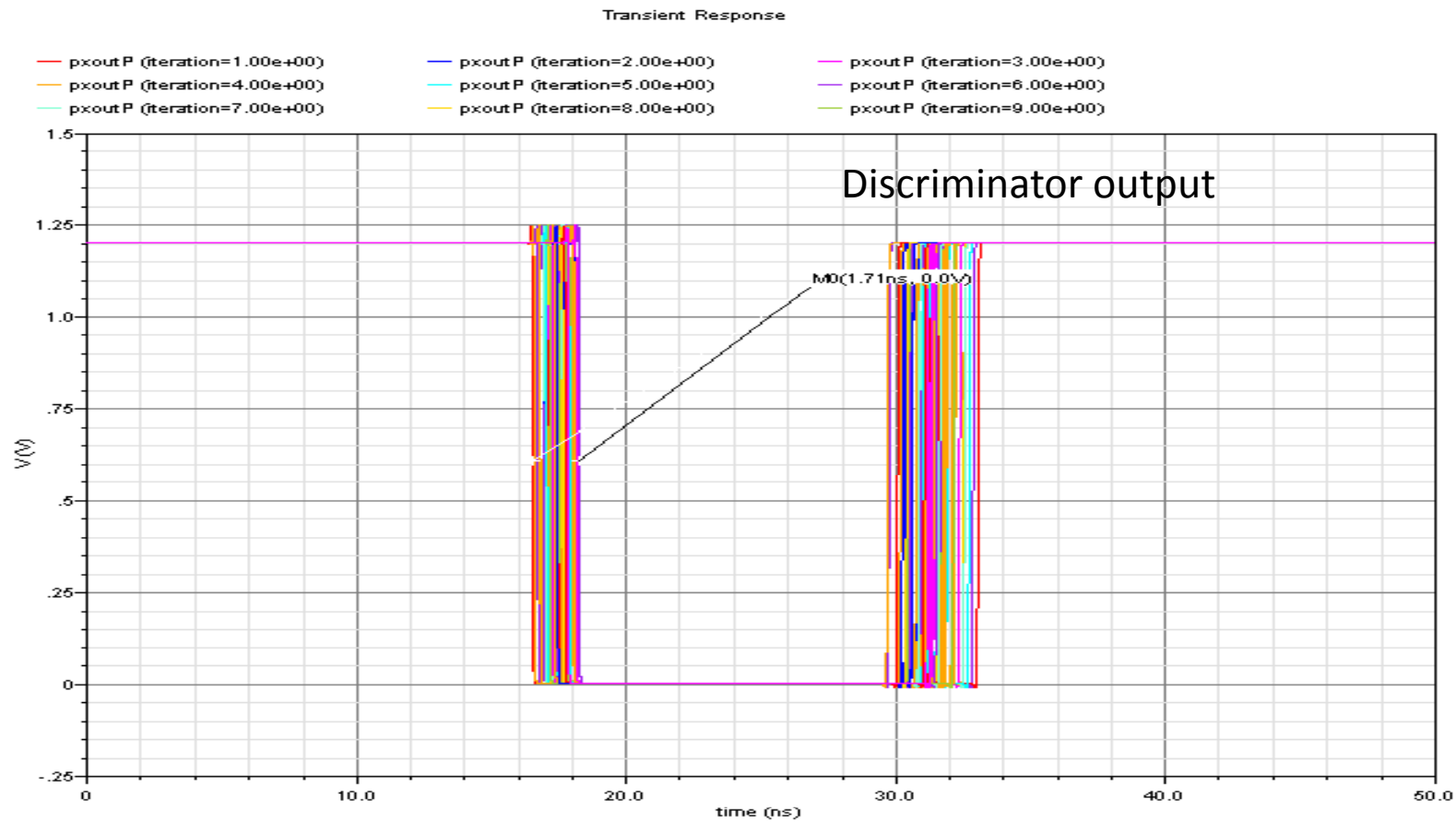
# Mismatch (no TRIM DACs)


3fC signal, mismatch 6mV RMS, 300ps RMS (1.7ns pk-pk)





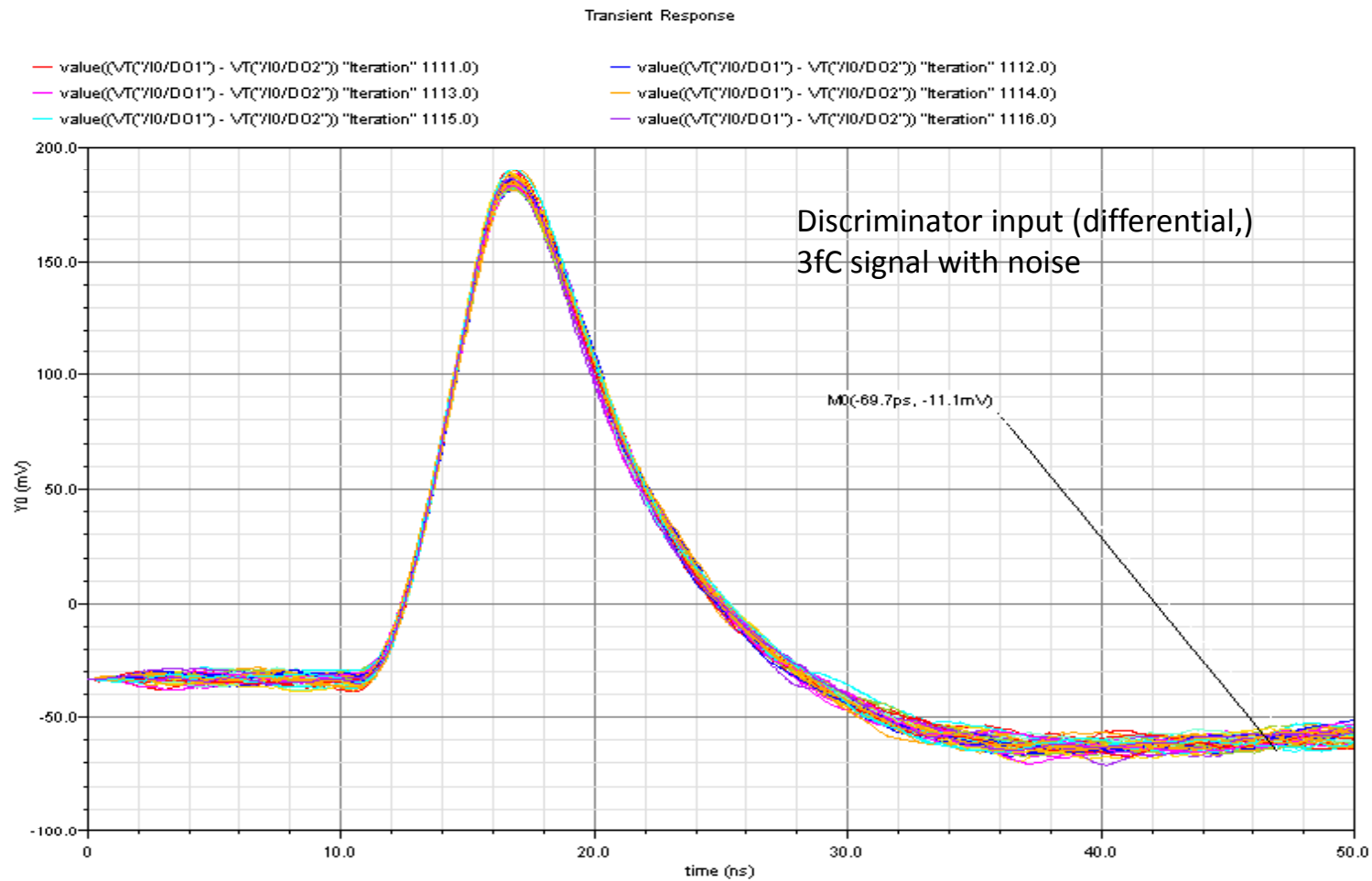
# Noise & Jitter (transient noise simulation)

3fC signal, noise  $\sim 2\text{mV RMS}$ ,  $\rightarrow \sim 180\text{e- RMS}$



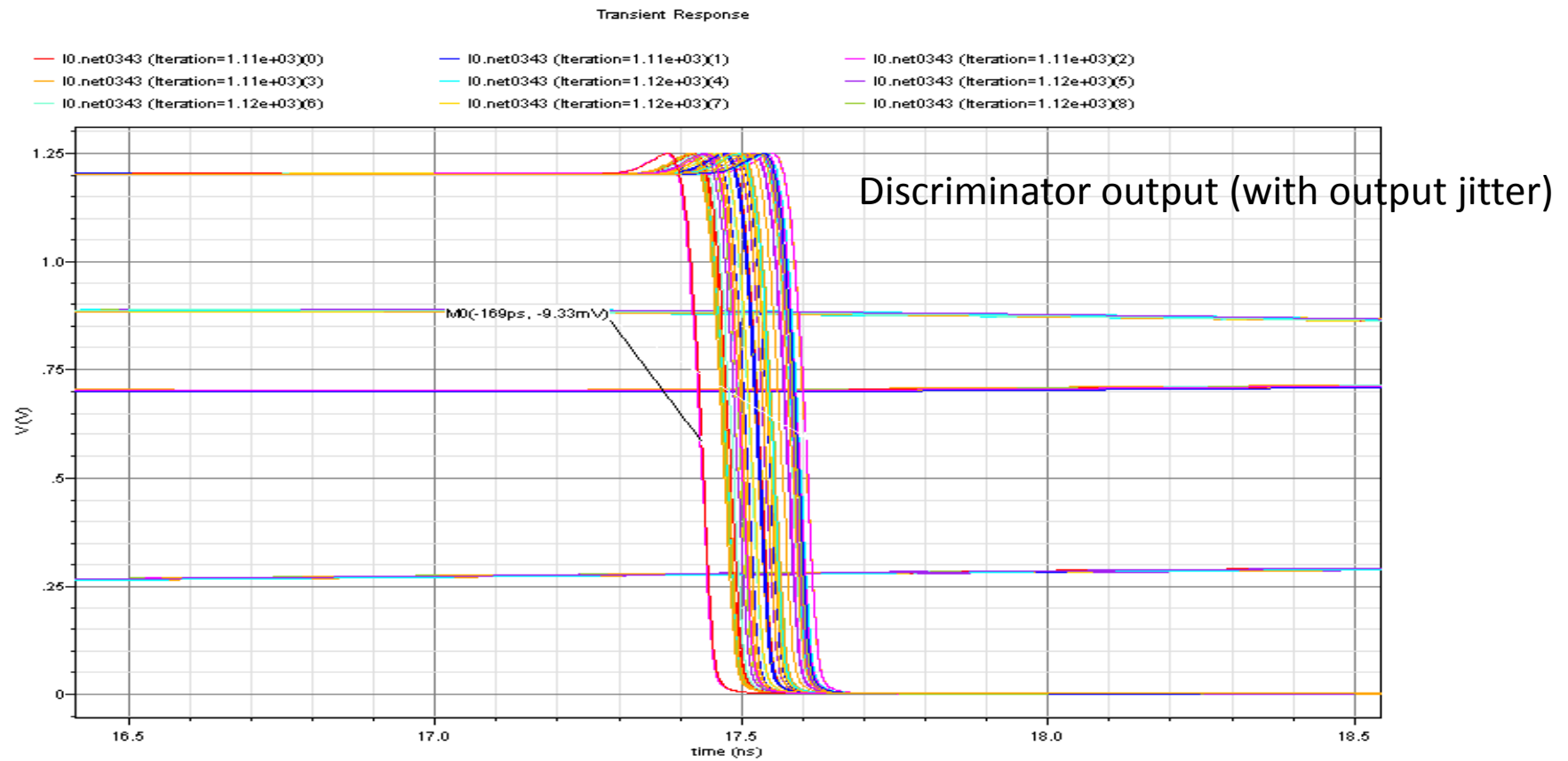
# Noise & Jitter (transient noise simulation)

3fC signal, noise  $\sim 180\text{e-}$  RMS  $\rightarrow$  jitter 30ps RMS (160ps pk-pk)




# Crossing the threshold

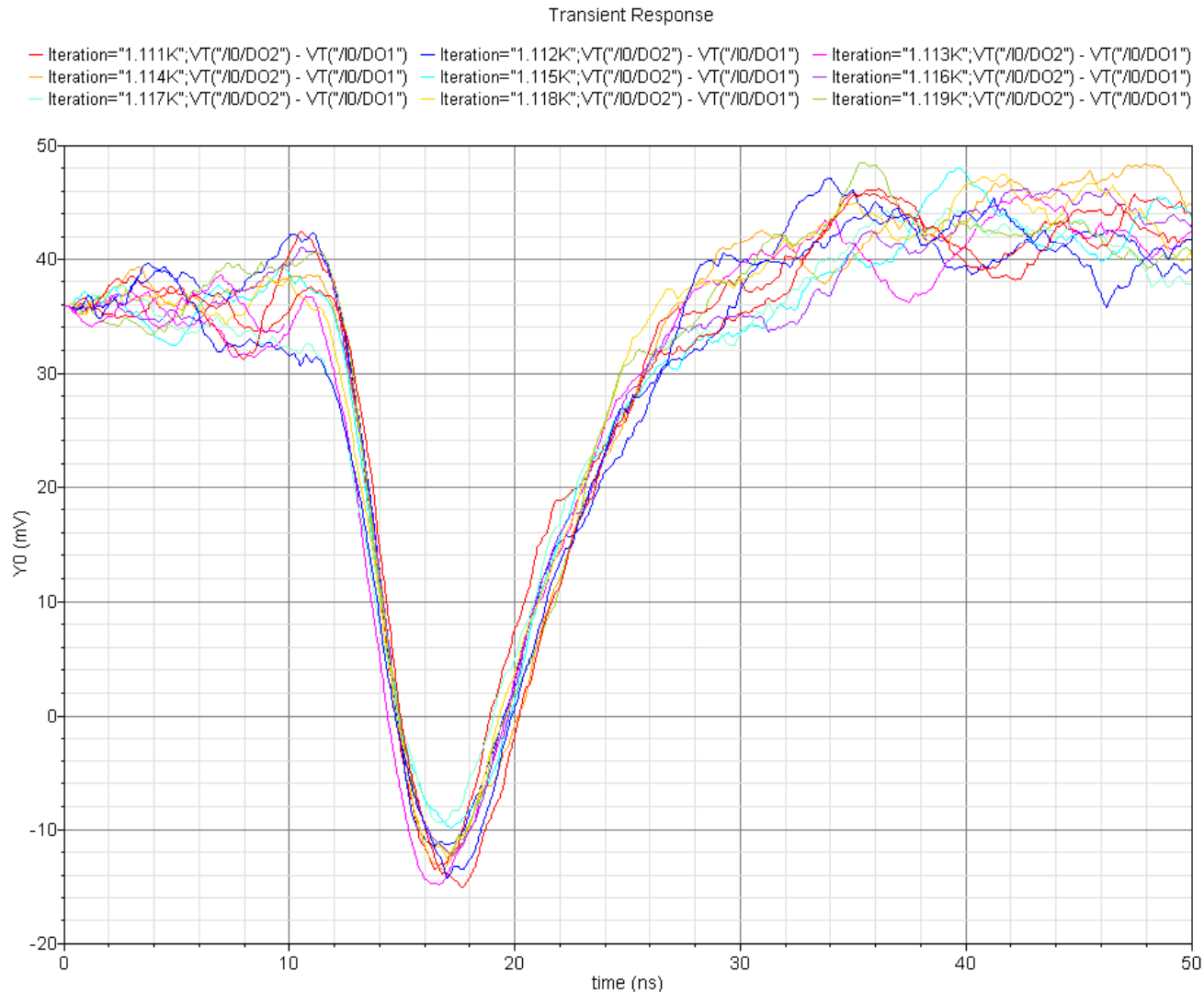0.7fC signal at 0.7fC threshold; noise triggering (~180e- ENC)



# Crossing the threshold


 
0.7fC signal at 0.7fC threshold; noise triggering (5 triggers out of 10, 1.2 to 4ns width)


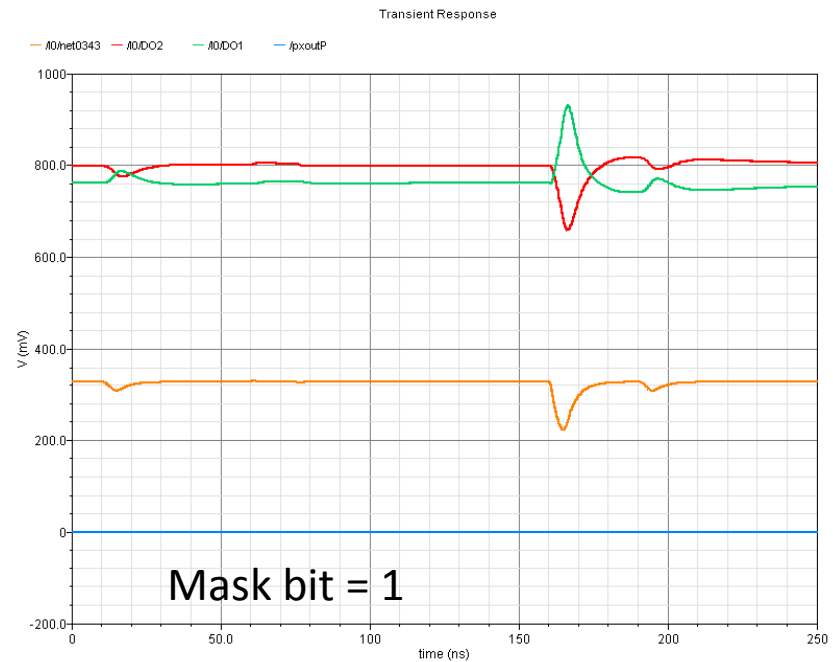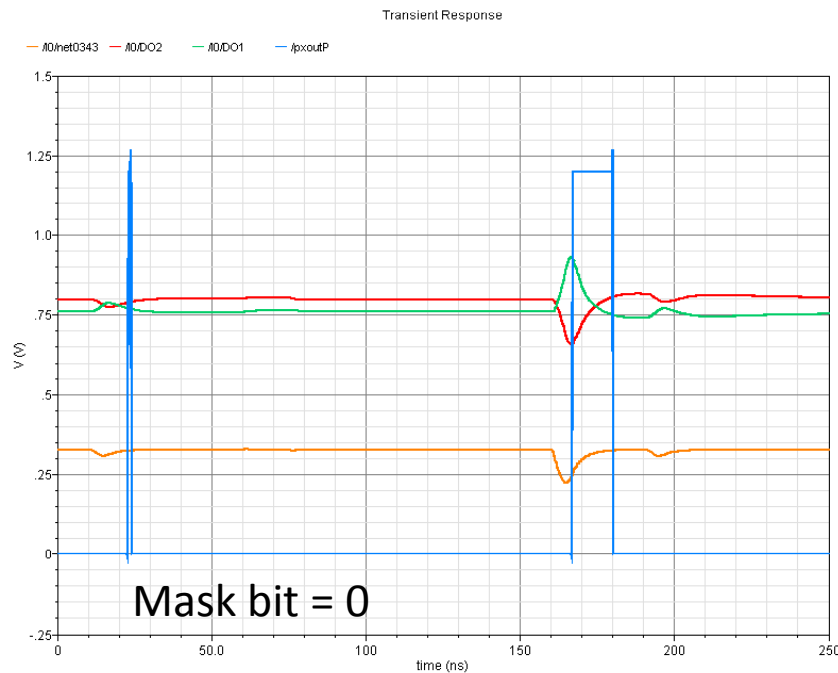
# Calibration and mask register


Two D flip-flops per pixel (on top level all D flip-flops connected in one serial register)

- 1<sup>st</sup> bit connect Calibration input (20fF capacitor) to common calibration line (1 = CAL LINE connected)
- 2<sup>nd</sup> bit for masking the output (OR logic – 1 block, / 0 – pass)


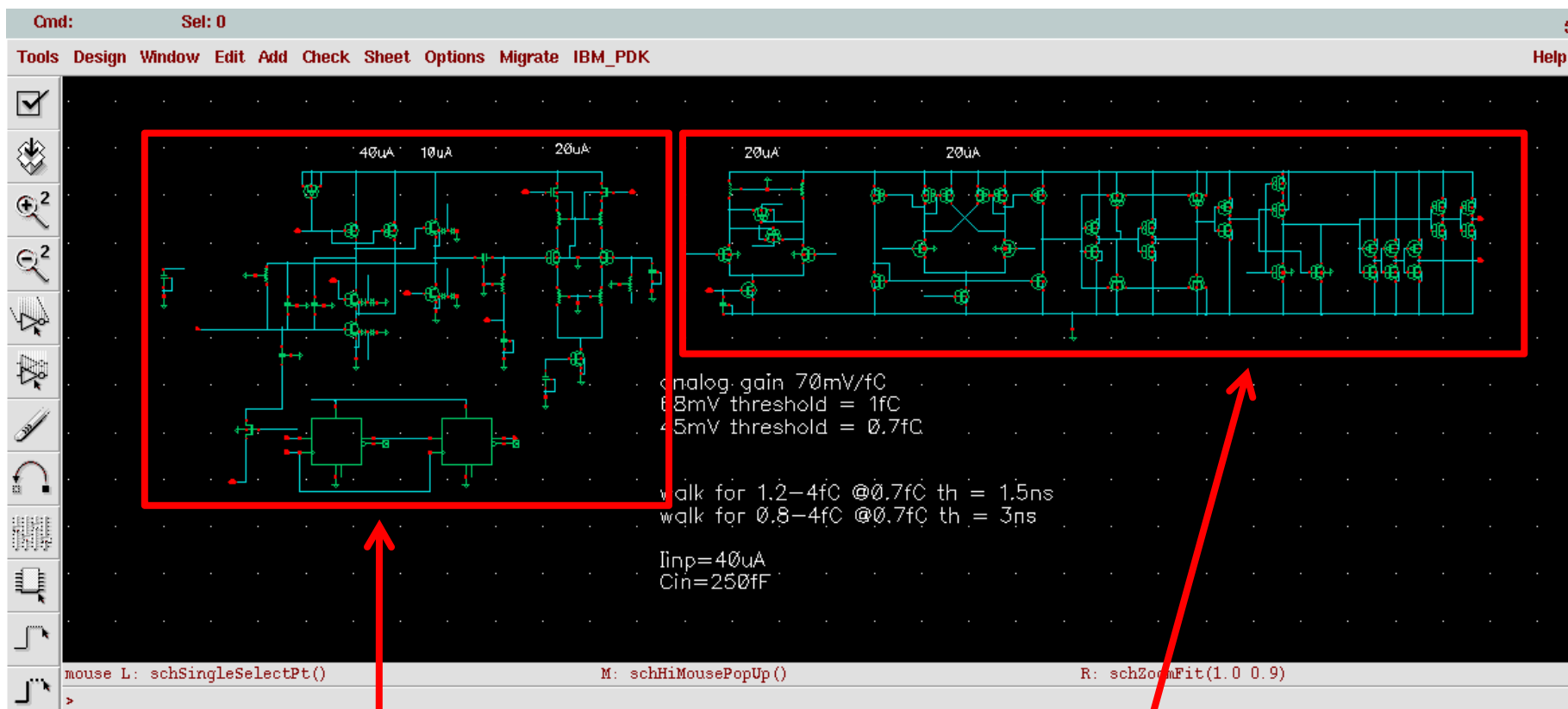
# Separation of analogue and digital part

2 domains of power supply and gnd on pixel




22

Analog vdda and gnda, all NMOS in preamplifier with 3well layout

Digital vdd and gnd

10/6/2008
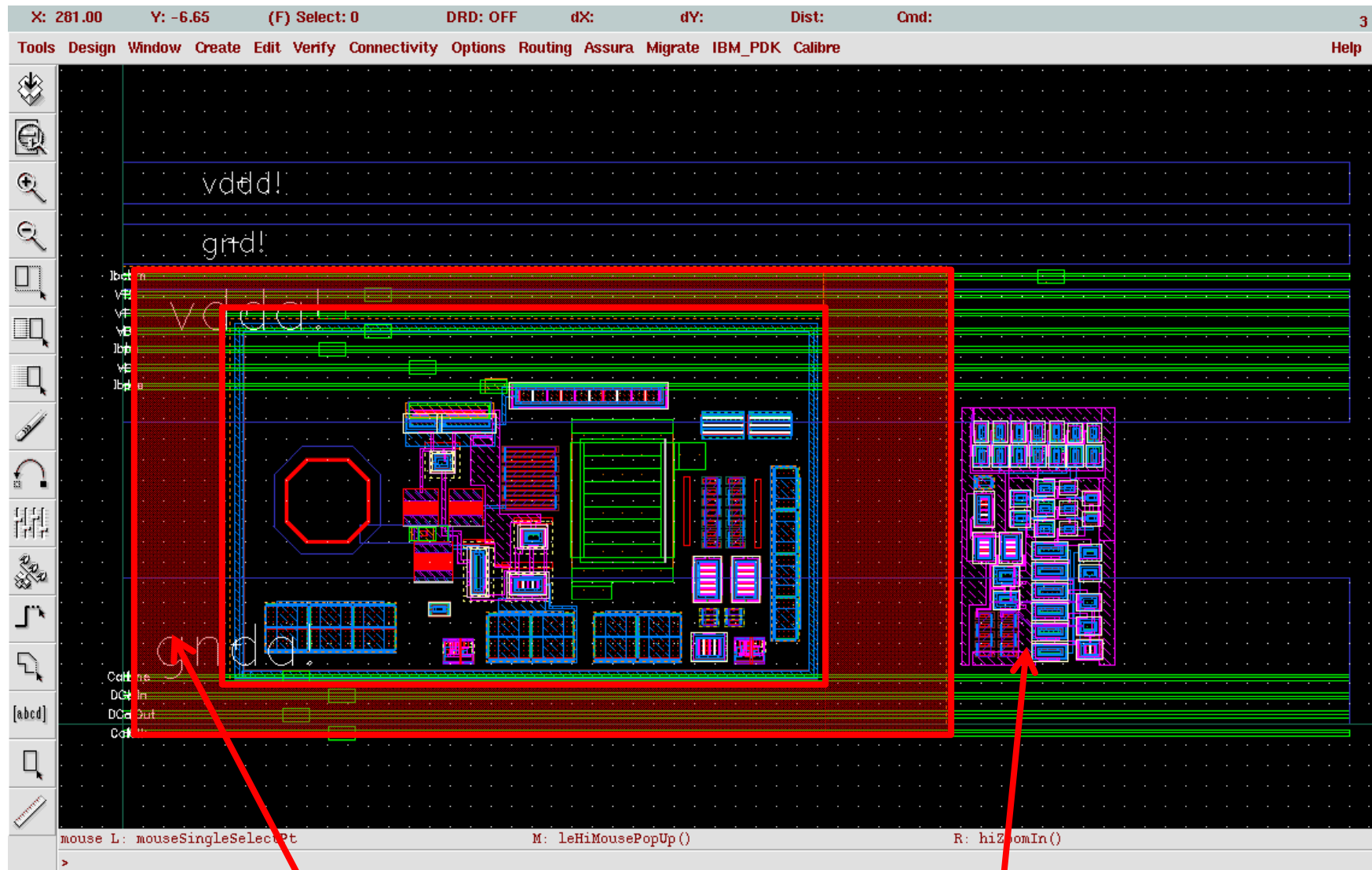
# Separation of analog and digital domain




23 MOAT separation of analogue and digital substrate ( $\sim 500 \Omega$ )

Digital part

10/6/2008
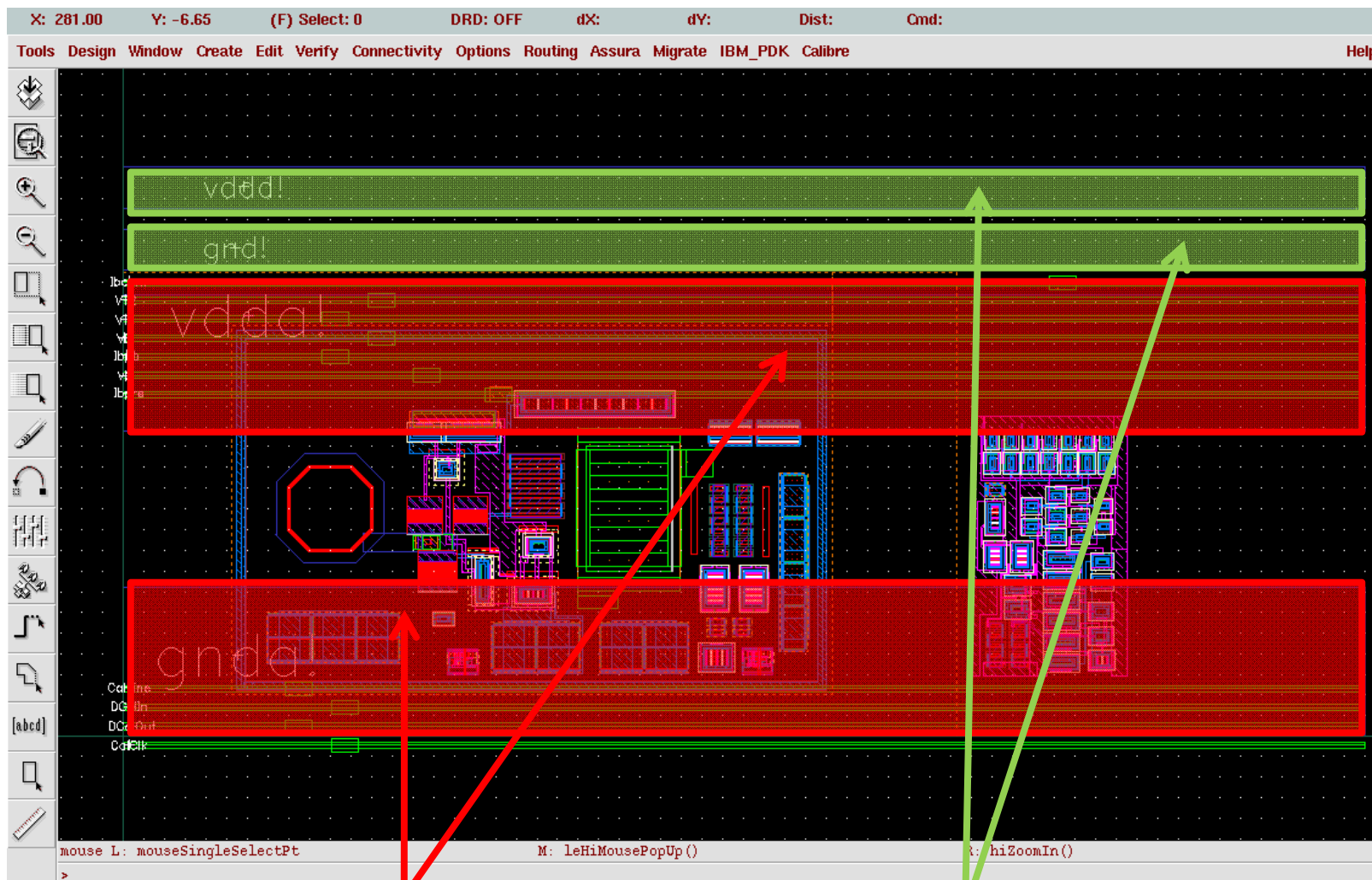
# Separation of analogue and digital power supply

Power distributed with last metal MA ( $7\text{m}\Omega/\text{sq}$ )



35um width for analog ( $70\mu\text{A}/\text{pixel}$ )

10 um width for digital ( $\sim 120\mu\text{A}$  for comparator + TL driver)