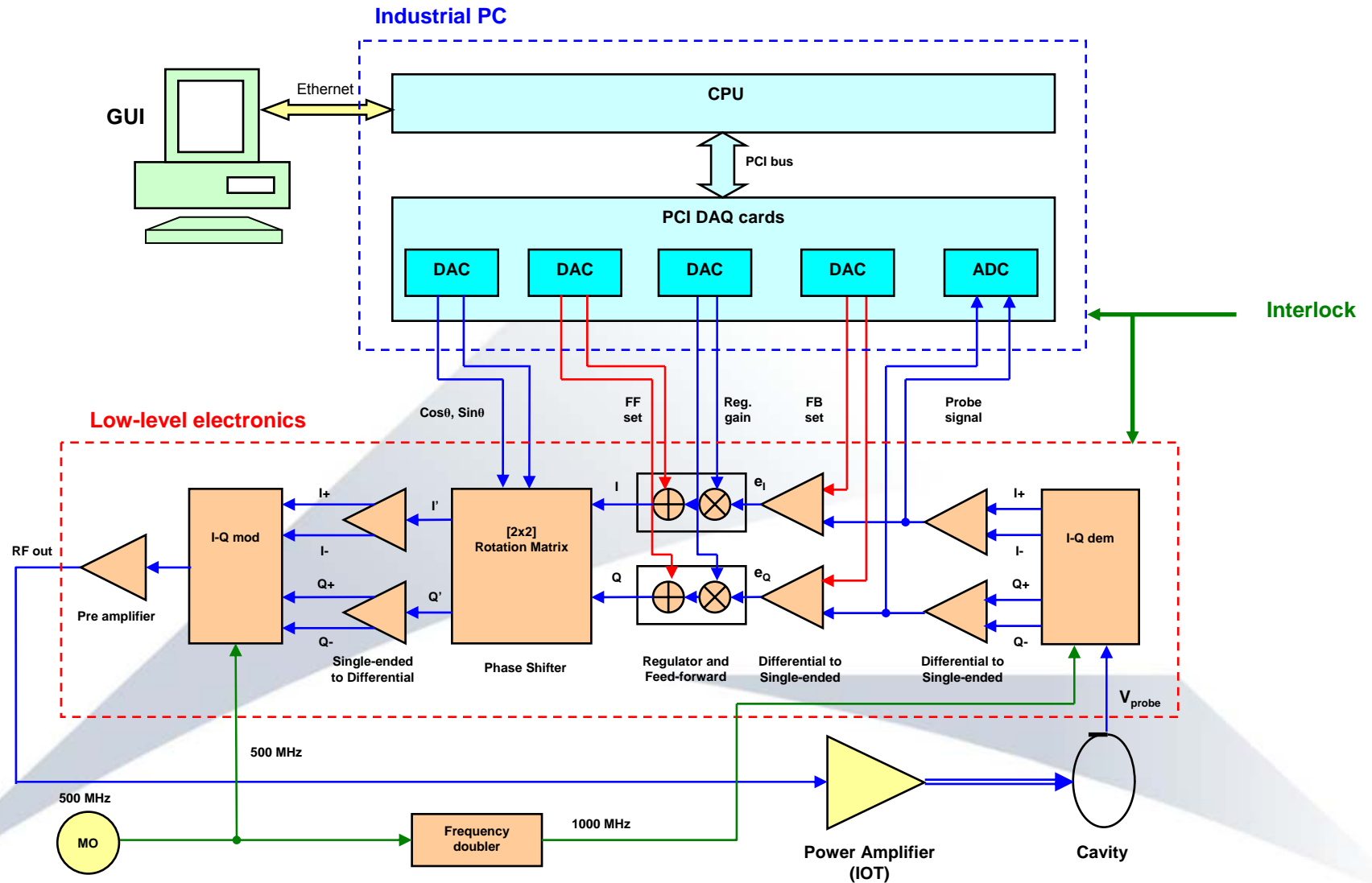


An IQ-based low-level RF prototype for ALBA

Hooman Hassanzadegan

Francis Perez

Design of the analog LLRF prototype



Specifications

Measured EU cavity parameters (E. Wehreter)

Nominal frequency	499.65	MHz
Tuning range	2	MHz
Shunt impedance	3.1	MΩ
Unloaded Q	26692	
Waveguide cut-off	615	MHz


ALBA storage-ring RF specifications

Master oscillator frequency	500	MHz
Cavity nominal frequency	499.654	MHz
Phase stability	±1	deg
Amplitude stability	±1	%
No. of cavities	6	
RF power (per cavity)	150	kW
RF voltage (per cavity)	600	kV
Overvoltage factor	2.8	
Synchronous phase	159	deg

ALBA LLRF specifications (analog prototype)

Phase loop			
	Design	Practice	
Type	Analog IQ with 'P' regulator	Analog IQ with 'P' regulator	
Bandwidth	1-2	~1 (measured)	MHz
No. of bits	16	16	Bits
DAC throughput	100	100	kHz
Phase stability	±1	?	deg
Amplitude loop			
	Design	Practice	
Type	Analog IQ with 'P' regulator	Analog IQ with 'P' regulator	
Bandwidth	1-2	~1 (measured)	MHz
No. of bits	16	16	Bits
DAC throughput	100	100	kHz
Amp. stability	±1	?	%
Tuning loop			
	Design		
Type	IQ dem and PCI tuner driver		
Bandwidth	~100		Hz
Tuning range	2		MHz
Tuning resolution	0.1 - 1		kHz

Current status

 

The low-level electronics




The industrial PC




The mockup cavity

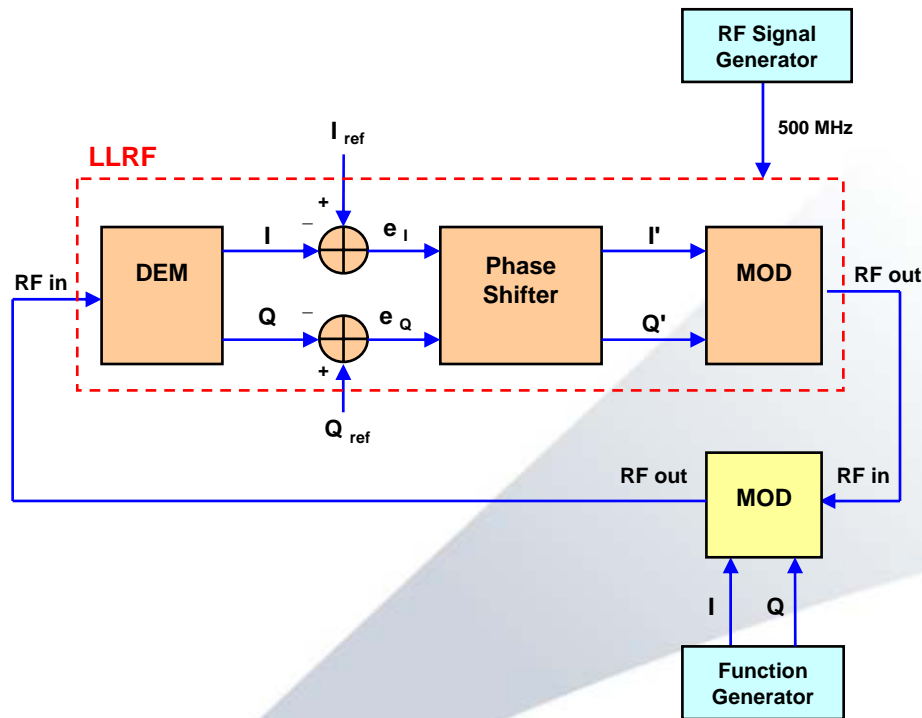Closed-loop test setup for amplitude and phase regulation




Setup for closed-loop test

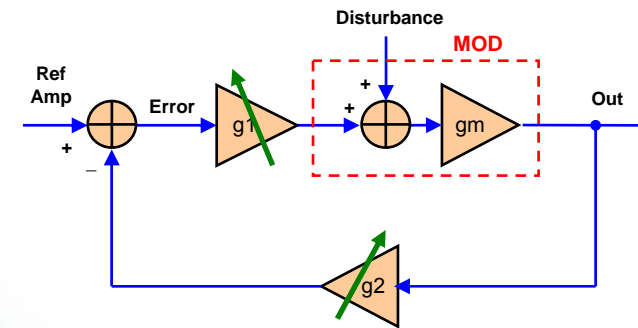

$$Out = ref \cdot \frac{g1 \cdot gm}{1 + g1 \cdot g2 \cdot gm} + dist \cdot \frac{gm}{1 + g1 \cdot g2 \cdot gm}$$


Simplified model of the loops

Closed loop test – amplitude regulation

 

Amplitude without regulation

Regulation

 

Amplitude with 'P' regulation

Steady state output

Measured: 7.6 mV
 Calculated: 7.5 mV

Ripple

Measured: ~2 mV
 Calculated: 3.5 mV


Loop delay

Measured: ~200 ns

Band width

Measured: ~1 MHz


Main problems we have faced

 


Problem

Solution


- | | | | |
|----|---------------------------|----|--|
| 1. | Noise and disturbance | => | Careful PCB design, filtering, grounding, good components, shielding, etc. |
| 2. | DC offsets | => | Variable resistors for DC adjust |
| 3. | Voltage ranges of the ICs | => | Careful circuit design |

 

Spikes

 


Oscillations

 

500 MHz

614 MHz

Filtering

 

Next steps

1. Use of a 'PI' regulator instead of 'P' to eliminate the steady-state error
2. Noise/disturbance reduction
3. Closed-loop tests with the mockup cavity for amplitude and phase regulation