



CLIC DR Kickers Inductive Adders – Status Update

J. Holma


CERN TE/ABT, Geneva, Switzerland

Acknowledgement M.J. Barnes
CERN





Overview

- **Background**
 - CLIC Layout with Damping Ring (DR) kickers
 - Specifications for CLIC DR Extraction Kicker System
 - Challenges and Issues
- **Inductive Adder Design**
 - Schematic
 - Improving the Pulse Stability
- **3.5 kV Prototype Inductive Adders**
 - Specifications for the First Prototype Inductive Adders
 - 3.5 kV Pulses without Modulation
 - Passive and Active Droop Compensation
 - Active Compensation of Droop and Ripple
 - Evaluation of Magnetic Core Material for 12.5 kV Prototypes
- **12.5 kV Prototype Inductive Adders**
 - Initial Measurements on Magnetic Cores
- **Summary and Future Work**

 


Ideal stripline current for 1 GHz option

  



CLIC General Layout

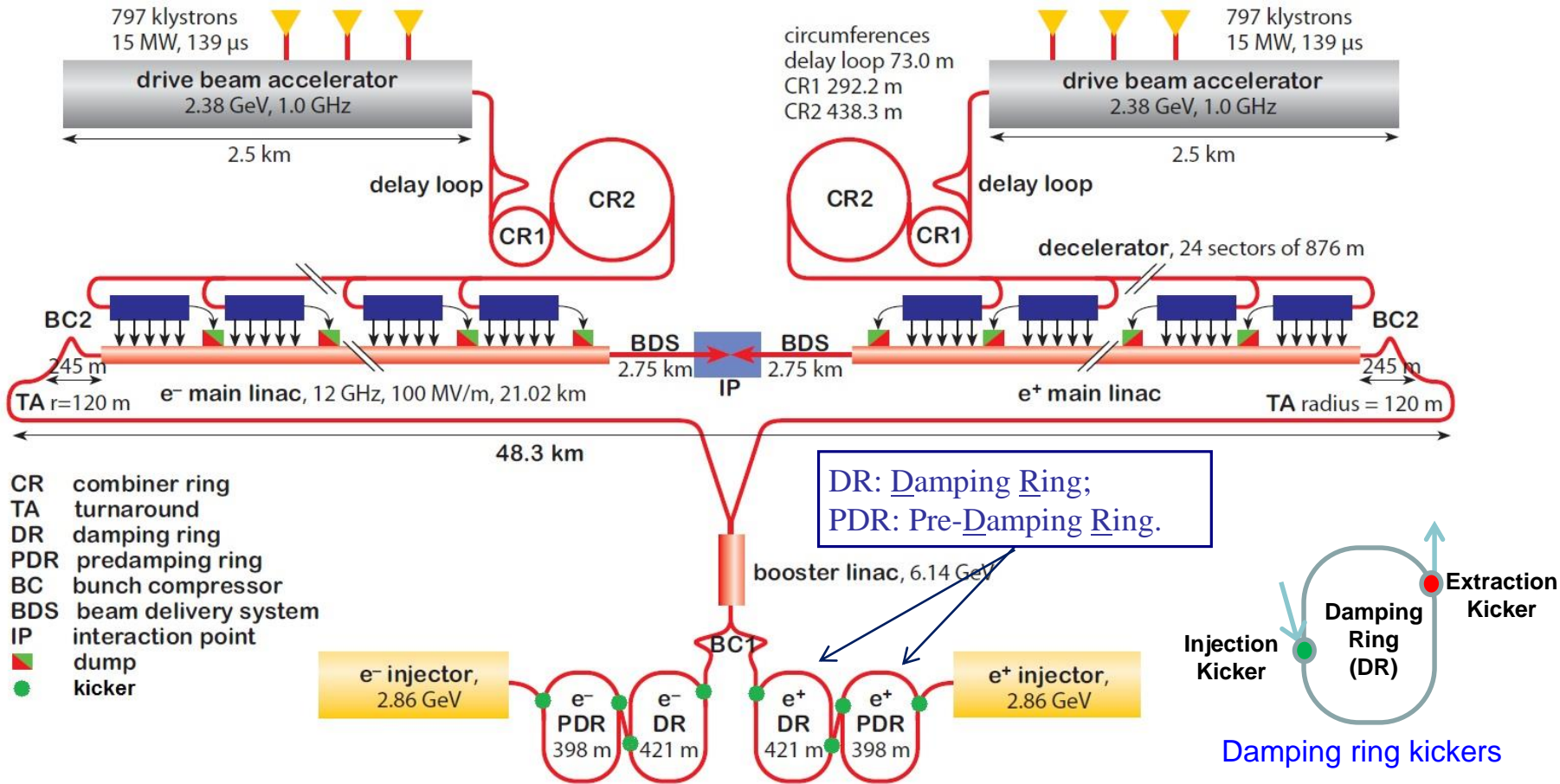



PDR & DR Kickers (●):

- One injection and extraction system per ring and per beam (8 systems);
- Damping rings reduce beam emittance; hence kickers must be high stability (low ripple);
- Low beam coupling impedance and good field homogeneity are required (talk by C. Belver-Aguilar).




Specifications for the CLIC DR Extraction Kicker Systems

| | CLIC DR (1 GHz 2 GHz) |
|---|---|
| Pulse voltage (kV) (per Stripline) | ± 12.5 |
| Stripline pulse current [50 Ω load] (A) | ± 250 |
| Repetition rate (Hz) | 50 |
| Pulse flat-top duration (ns) | ~ 160 ~ 900 |
| Flat-top repeatability | $\pm 1 \times 10^{-4}$ (± 0.01 %) |
| Flat-top stability [inc. droop], (Inj.) per Kicker SYSTEM (Ext.) | $\pm 2 \times 10^{-3}$ (± 0.2 %) $\pm 2 \times 10^{-4}$ (± 0.02 %) |
| Field rise time (ns) | 1000 |
| Field fall time (ns) | 1000 |
| Beam energy (GeV) | 2.86 |
| Total kick deflection angle (mrad) | 1.5 (0.09 deg) |
| Aperture (mm) | 20 |
| Effective length (m) | 1.7 |
| Field inhomogeneity (%) [3.5mm radius] [1mm radius] | ± 0.1 (Inj.) ± 0.01 (Ext.) |

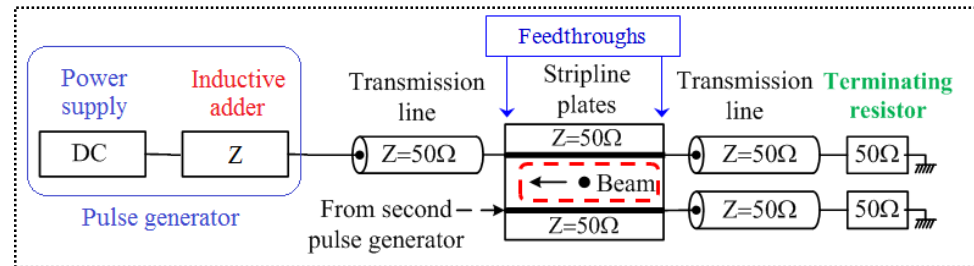 

Schematic of a kicker system

 


CLIC DR kicker pulse definition


NOTE:

- For rise/fall times, ≤ 100 ns desired!
- Close to 0 V intra-pulse (off-time) voltage required!

Challenges and Issues

 


CLIC DR kicker pulse definition

 

Schematic of a kicker system


- **$\pm 0.02\%$ ($\pm 2.5\text{ V}$)** requirement for the **flat-top stability** of $\pm 12.5\text{ kV}$, 160 to $\sim 900\text{ ns}$ pulse is an extremely demanding specification!
 - **An order of magnitude better than in any existing kicker systems!**
 - **Compensation of droop and ripple of the output voltage is required.**
- Adequate impedance matching to minimize duration of settling time:
 - Impedance (and field homogeneity) of the stripline kicker has been optimized: unfortunately the impedance cannot be $50\ \Omega$ for both power-off (even) and power-on (odd) operation modes!
 - Odd-mode impedance of the striplines is $\sim 41\ \Omega$ (see talk by C. Belver-Aguilar), which causes settling time to be $\sim 100\text{ ns}$. Therefore **the pulse flat-top duration is at least $\sim 260\text{ ns}$** (2 GHz option)
- Suitable high precision measurements of the pulse in the laboratory:
 - better relative precision than $\pm 2.5\text{ V}$ in 12.5 kV required!**

 




Inductive Adder

- Many primary “layers”, each with solid-state switches
- The output voltage is approximately the sum of the voltages of the primary constant voltage layers
- + Control electronics referenced to ground
- + No electronics referenced to high voltage despite the high voltage output of the adder
- + The output voltage can be modulated during the pulse with an analogue modulation layer
- + Modularity: the same design can potentially be used for kickers with different specifications (CLIC PDR & DR kicker modulators)
- + Redundancy and machine safety: if one switch or layer fails, the adder still gives full voltage or a significant portion of the required output pulse
- + Possibility to generate positive or negative output pulses with the same adder: the polarity of the pulse can be changed by grounding the other end of the output of the adder

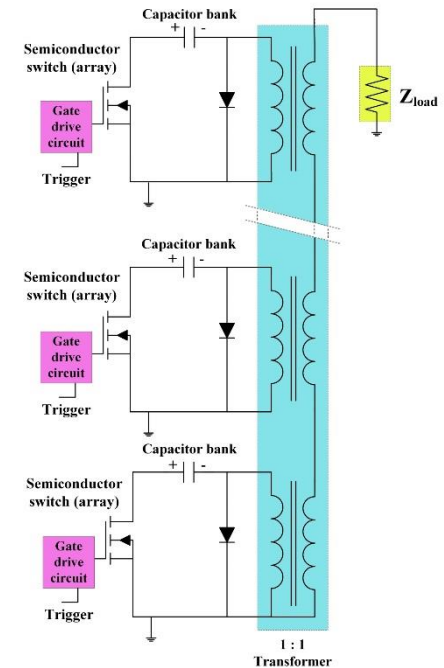


Schematic of an inductive adder

 

A prototype inductive adder

Improving the Pulse Stability


- Droop and ripple of the output pulse of an inductive adder can be compensated with an analogue modulation layer
- In the analogue modulation layer, resistor R_a is effectively in series with the load
- The load voltage is the difference of the voltage across the analogue modulation layer and the sum of the voltages across other layers
- Two modes:
 - **Passive mode:** During the pulse, current through L_m increases, which causes current through R_a to decrease. Therefore, voltage over R_a decreases, which can compensate for a reduction (droop) in the primary voltage of the other layers.

 

Passive analogue modulation

Improving the Pulse Stability

- Droop and ripple of the output pulse of an inductive adder can be compensated with an analogue modulation layer
- In the analogue modulation layer, resistor R_a is effectively in series with the load
- The load voltage is the difference of the voltage across the analogue modulation layer and the sum of the voltages across other layers
- Two modes:
 - **Passive mode:** During the pulse, current through L_m increases, which causes current through R_a to decrease. Therefore, voltage over R_a decreases, which can compensate for a reduction (droop) in the primary voltage of the other layers.
 - **Active mode:** A linear RF power transistor is connected in parallel with resistor R_a . The voltage across R_a can be controlled by controlling the current through the RF power transistor.

 




Two 5-Layer Prototype Inductive Adders

- The purpose of the prototype inductive adder has been:
 - To verify theoretical models, which have been used to predict the operation of an inductive adder with extremely high flat-top stability
 - To verify experimentally design steps for an inductive adder with high flat-top stability
 - To test both passive and active analogue modulation
 - To approach the required $\pm 0.02\%$ flat-top stability for the output pulse, as specified for the CLIC DR extraction kicker modulator


| Design Parameter | Prototype Inductive Adder | CLIC DR Extraction Kicker Modulator |
|---------------------------------------|---------------------------|-------------------------------------|
| Output Voltage (kV) | 3.5 | 12.5 |
| Output Current [50 Ω load] (A) | 70 (250) | 250 |
| Voltage per layer | 700 | 700 |
| Number of layers | 5 | 20 |
| Pulse flat-top duration (ns) | 160 – 350* (900) | 160 – 900 |
| Pulse rise time [0.1-99.9 %] (ns) | 100 | < 1000 |
| Pulse fall time [0.1-99.9 %] (ns) | 100 | < 1000 |
| Flat-top stability (for 160 ns) | $\pm 0.02\%$ | $\pm 0.02\%$ |
| Repetition rate (Hz) | 50 | 50 |

 * limited by transformer cores, design value 900 ns



The prototype inductive adder with two half-layers inserted


 
Measurements on the 5-Layer Prototype Inductive Adder



The prototype inductive adder with the measurement setup



  Measurements on the 5-Layer Prototype Inductive Adder



In initial measurements, only one branch per half-layer PCB was powered! 2 branches per layer.

The prototype inductive adder with a current transformer and a load




Measurements: 3.5 kV Output Pulse - No Modulation

➤ Setup for the measurement:

- The prototype adder with 5 layers
- 1 branch powered per half-layer PCB, 2 branches per layer
- Capacitors (24 μF /layer) charged initially to 750 V
- 50 Ω , 18 kV load by Diconex
- No modulation applied.




➤ Output pulse parameters

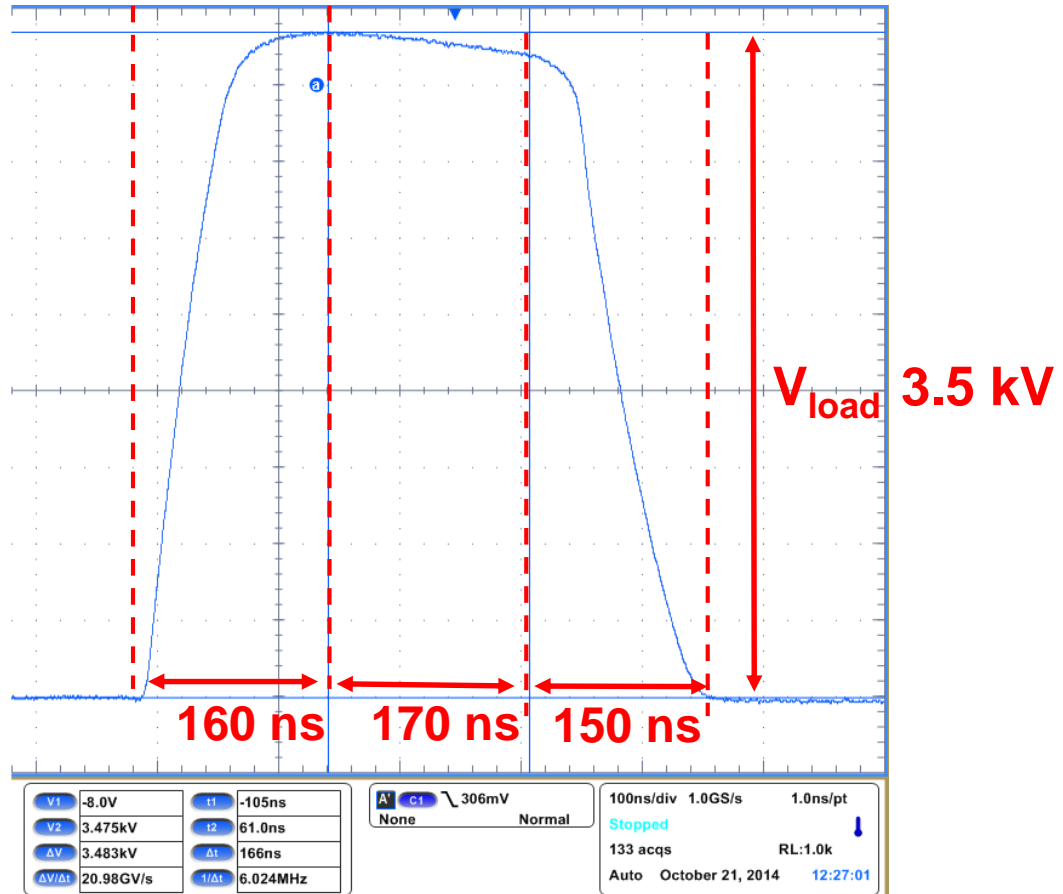- Output voltage: 3.5 kV
- Rise time (0.1...99.99 %) 160 ns
- Droop: $\sim 3.4\%$ (120 V) for 170 ns flat-top duration
- Small intra-pulse voltage (~ 10 V).



Measurements: Passive Compensation of Droop and Active Compensation of Droop and Ripple

 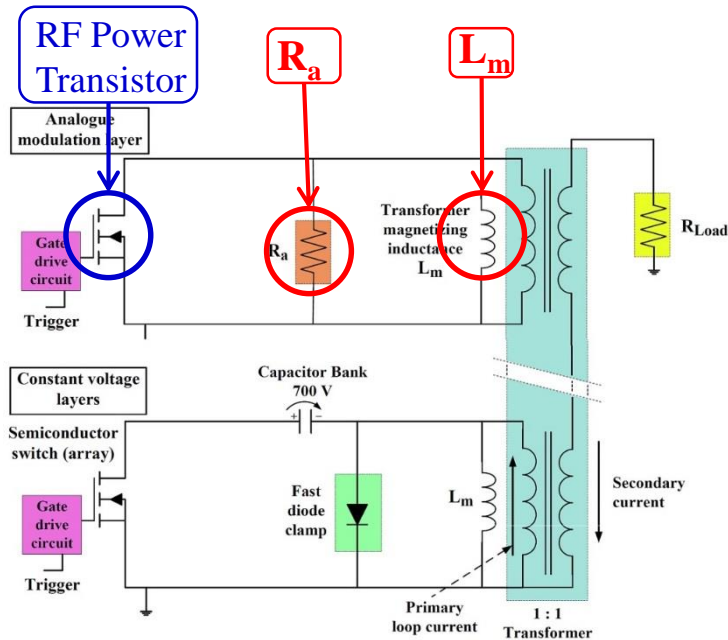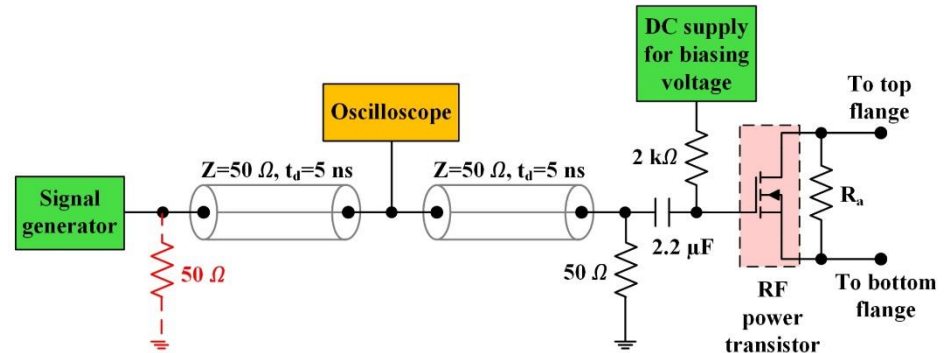
- Setup for the measurement:**
 - The prototype adder with 4 constant voltage layers and an analogue modulation layer
 - 1 branch powered per half-layer PCB, 2 branches per layer
 - Capacitors (24 $\mu\text{F}/\text{layer}$) charged initially to 350...553 V.
 - Passive or active analogue modulation applied



Schematic and layout of the active analogue modulation layer



Measurements: Passive Droop Compensation

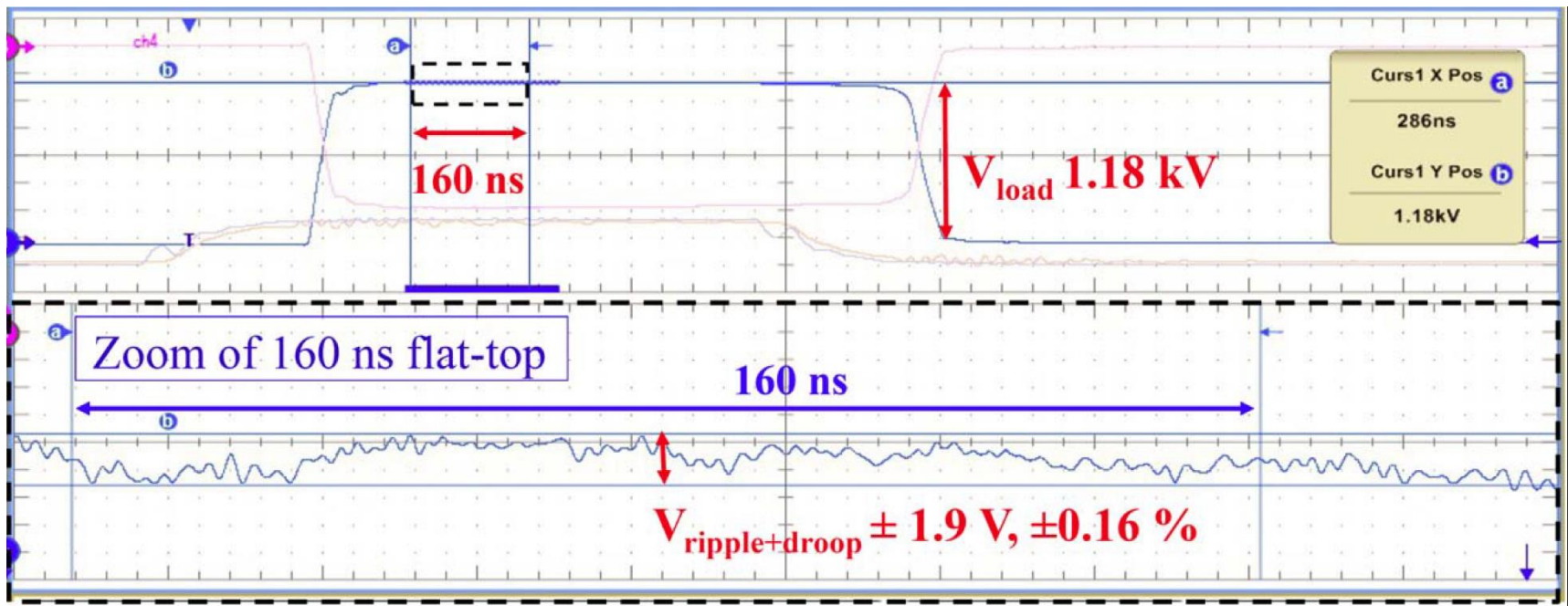

Setup for the measurement:


- 4 constant voltage layers and a passive analogue modulation layer
- 1 branch powered per half-layer PCB, 2 branches per layer
- Capacitors ($24 \mu\text{F}/\text{layer}$) initially charged to 350 V ($R_a = 7.9 \Omega$)

Notes:

- Tektronix scope used (DPO 5034) has a nominal vertical resolution of 8 bits ($< \pm 0.4\%$) – can be improved with oversampling and averaging
- The curve is an average of 1000 measured pulses
- **The optimal combination of R_a & L_m depends on the output voltage!**



Measurements: Active Droop Compensation

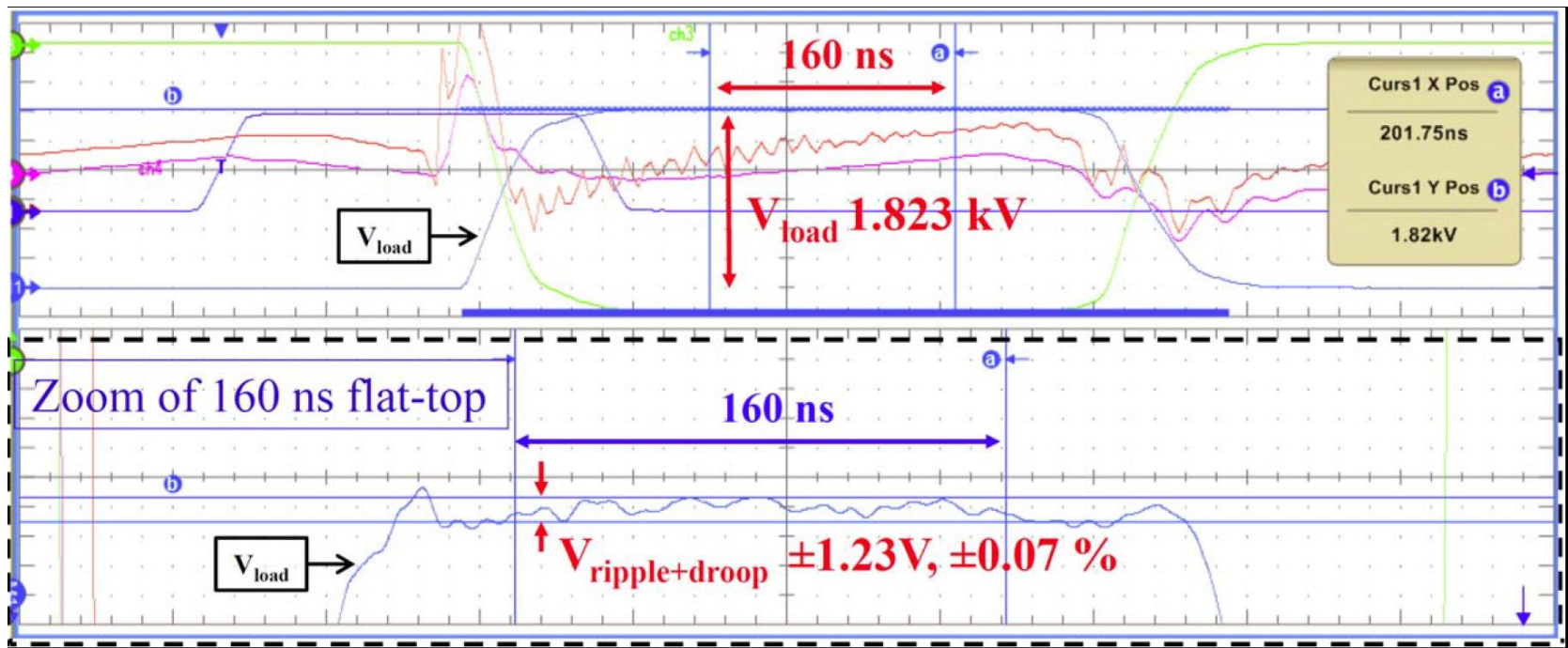

Setup for the measurement:


- 4 constant voltage layers and a passive analogue modulation layer
- 1 branch powered per half-layer PCB, 2 branches per layer
- Capacitors (24 μF /layer) initially charged to 551 V ($R_a = 7.9 \Omega$)
- Active droop compensation with piece-wise linear ramp function

Notes:

- The curve is average of 1000 measured pulses
- Repeat of the measurement with averaging of 4000 pulses resulted in $\pm 1.17\text{V}$ ($\pm 0.06\%$)!



Measurements: Active Ripple Compensation

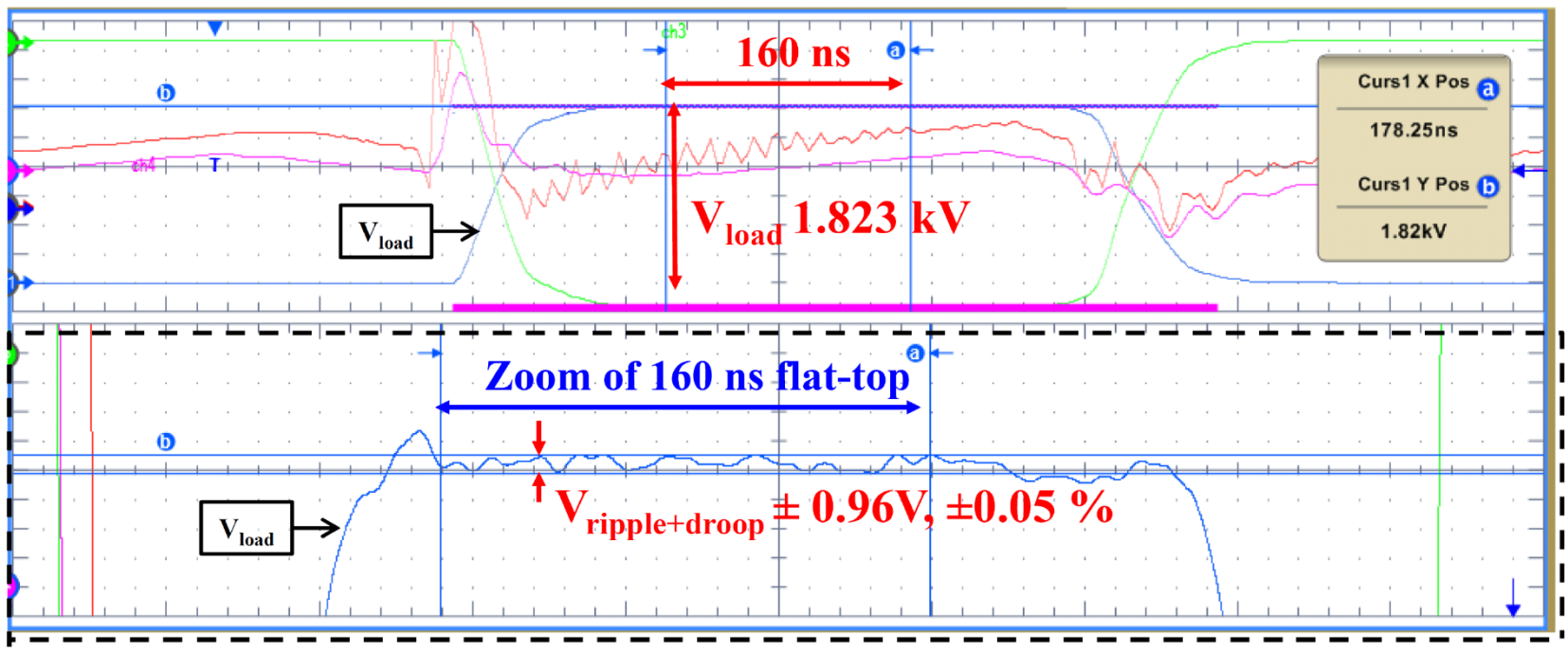

Setup for the measurement:

- 4 constant voltage layers and a passive analogue modulation layer
- 1 branch powered per half-layer PCB, 2 branches per layer
- Capacitors ($24 \mu\text{F}/\text{layer}$) initially charged to 551 V ($R_a = 7.9 \Omega$)
- Active droop and ripple compensation

Notes:

- The curve is an average of 1000 measured pulses
- Repeat of the measurement with averaging of 4000 pulses resulted in $\pm 1.02 \text{ V}$ ($\pm 0.06 \%$)!




Summary of the Measurements with 3.5 kV prototypes

- The required absolute stability (in absolute numbers) was achieved for all damping ring kicker systems ($\leq \pm 2.5$ V). Hence, the pulse power modulators for the kicker systems for the CLIC damping rings are very probably feasible.
- The required relative stability (relative to the pulse voltage or current) was not reached for the DR extraction kicker systems ($\leq \pm 0.02$ %).
- The required resolution for the direct electrical measurement of the pulse waveform is very close to the limit of the measurement set-up (Bergoz CT-E.01 current transformer & 8-bit Tektronix oscilloscope DPO 5034)
- Hardware limitations:
 - Maximum voltage up to 3.5 kV
 - Maximum pulse duration up to 350 ns flat-top at 700 V per layer (restricted by cross-sectional area of available magnetic cores)
 - 2 branches powered per layer (increased the amplitude of the droop to be compensated)
 - No amplifier between an RF power transistor and signal generator in the active analogue modulation layer (low gain)




Evaluation of Magnetic Core Material for 12.5 kV Prototypes

- Different core materials were evaluated for 12.5 kV prototypes with 3.5 kV prototype adders
- Based on measurements with 3.5 kV prototypes, the requirements for magnetic cores for inductive adders with extremely high flat-top stability are the following:
 - High magnetizing inductance L_m
 - Large linear flux swing of B-H loop (constant permeability)
 - Low remanent field (no biasing required)
 - Relatively low losses (high core loss resistance R_c)
 - Sufficient insulation between ribbon layers, to prevent break-downs with a high magnetization rate

 



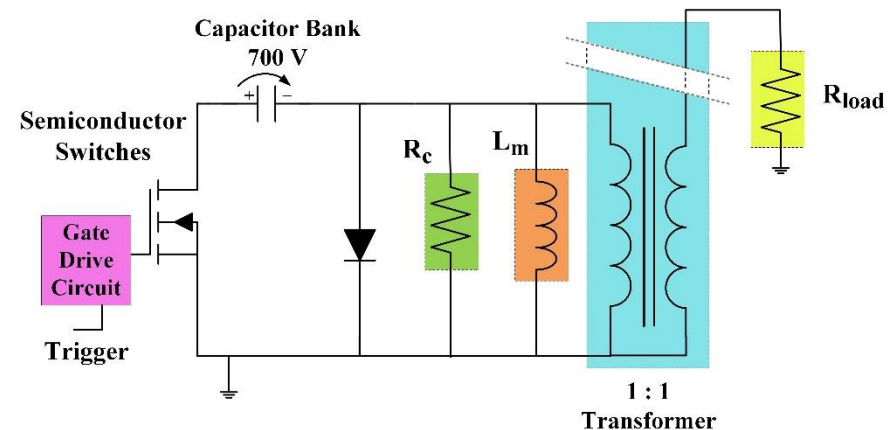
Examples of square-loop (black) and linear (blue) B-H curves





Evaluation of Magnetic Core Material for 12.5 kV Prototypes

 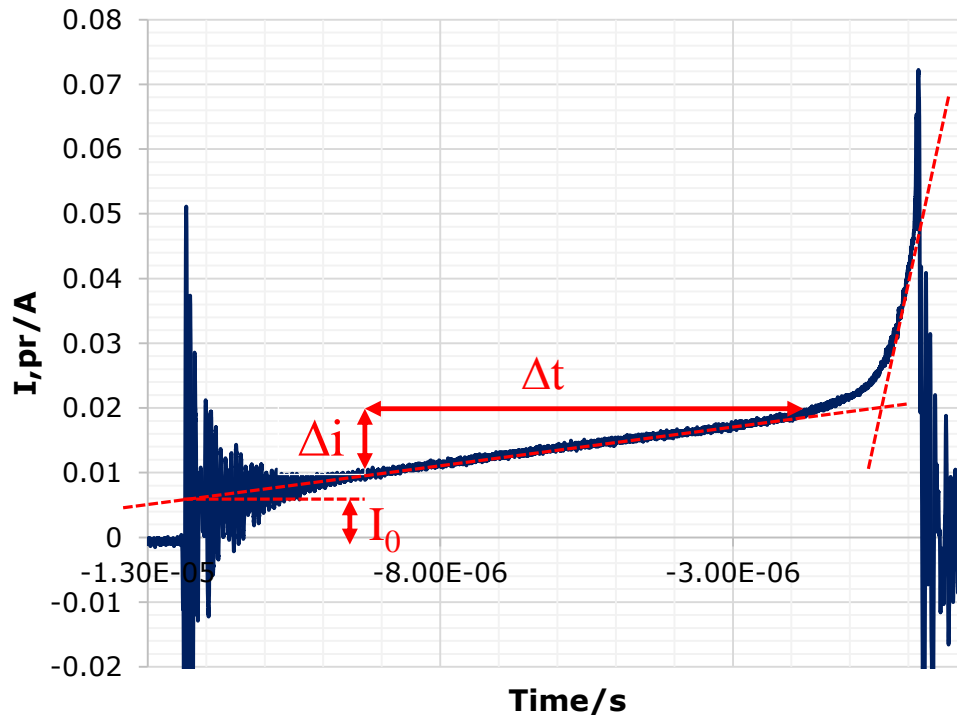 - Core materials were evaluated by measuring primary current (I_{pr}) of a single layer with a Rogowski coil current transducer.
- Numerical estimates for R_c and L_m :
 - $R_c \approx V_{Rc} / I_0$
 - $L_m \approx (V_{Lm} \times \Delta t) / \Delta i_{Lm}$






Measurement set-up for magnetizing current



Evaluation of Magnetic Core Material for 12.5 kV Prototypes – with Biasing

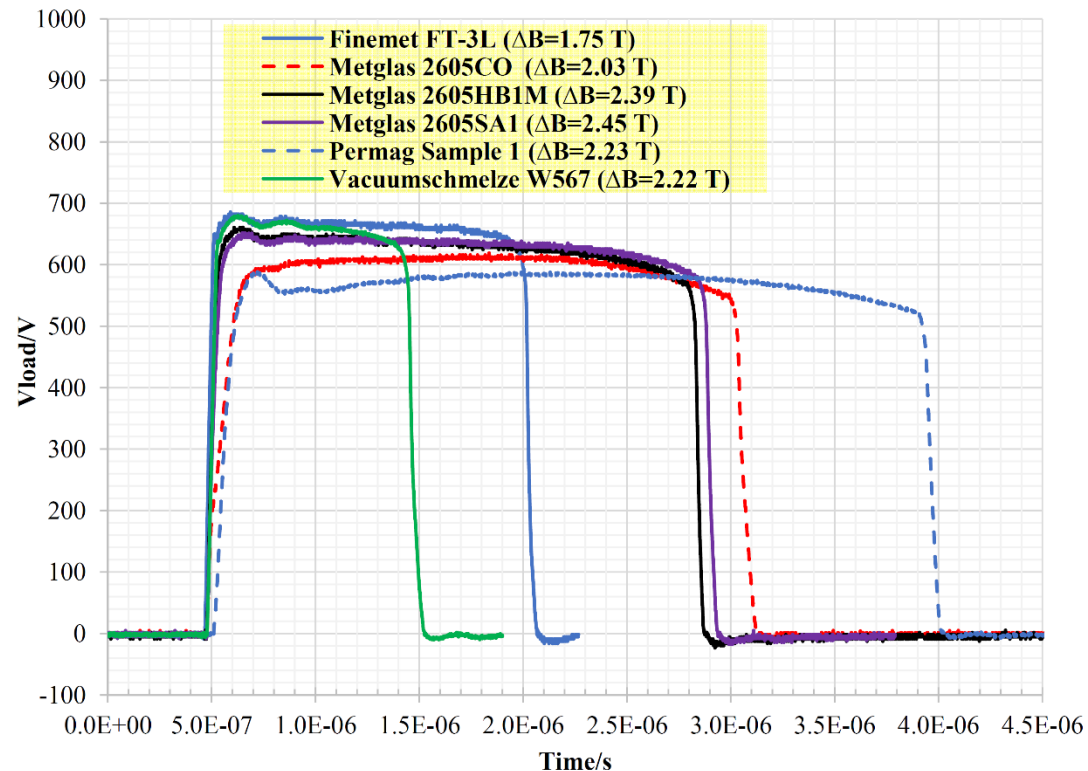 
 
- Set-up for measurement:
 - Output voltage of an inductive adder with single layer powered (700 V)
 - Biasing (8 A, DC) applied, to use most of the flux swing range
- Biasing circuit (large inductor) causes ripple for the pulse flat-top and off-time voltage, which is not acceptable for CLIC DR kicker system.





Evaluation of Magnetic Core Material for 12.5 kV Prototypes – No Biasing

- Setup for Measurement:
 - Output voltage of an inductive adder with a single layer powered (250 V)
 - No biasing applied
- Best candidates without biasing: Vacuumschmelze Vitroperm 500 F and Finemet FT-3L.
 - Lowest remanent field.
 - Lowest losses
- Limitations of Vacuumschmelze cores:
 - Not available in custom sizes and insulation
 - "Standard" insulation between ribbon layers is not adequate for this application.
- **Finemet FT-3L chosen for 12.5 kV prototypes.**

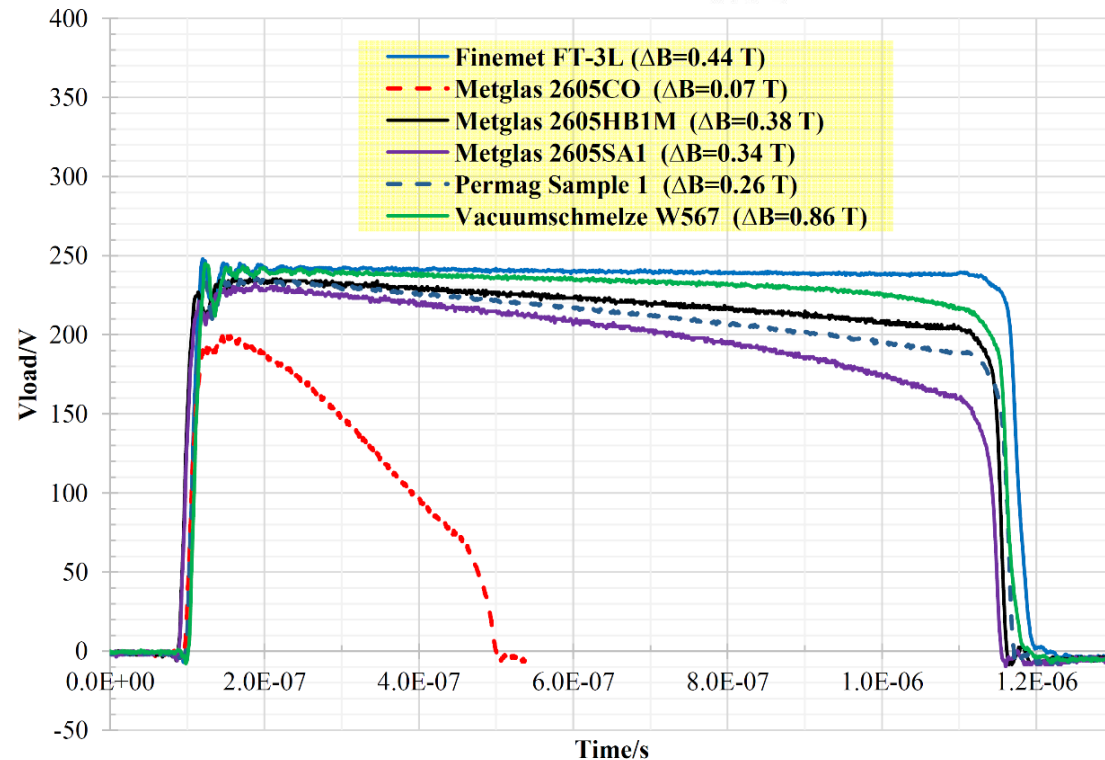 




Evaluation of Magnetic Core Material for 12.5 kV Prototypes

| Core | V_c (V) | I_b (A) | $I_{Lm,max}$ (A) | T_p (μs) | R_c (Ω) | L_m (μH) Max Min | $\mu_r \times 10^3$ Max Min |
|------------------------|--------------|--------------|---------------------|----------------------|-----------------------|-----------------------------------|----------------------------------|
| Finemet FT-3L | 700 | 0 | 100 | 0.9 | 25.0 | 110 0.9 | 58 0.5 |
| | 700 | 8 | 100 | 1.7 | 25.1 | 40 1.9 | 21 1.0 |
| Vacuumschmelze W567 | 700 | 0 | 100 | 0.6 | 25.3 | 4.9 0.8 | 4.8 0.8 |
| | 700 | 8 | 100 | 1.1 | 24.8 | 16 1.4 | 16 1.4 |
| Metglas 2605CO | 700 | 1 | 100 | 3.3 | 6.2 | n/a 40 | n/a 17 |
| | 700 | 8 | 100 | 3.5 | 6.3 | n/a 39 | n/a 17 |
| Metglas 2605HB1M | 700 | 1 | 100 | 1.1 | 8.4 | 13 7.4 | 6.3 3.7 |
| | 700 | 8 | 100 | 2.4 | 8.6 | 29 10 | 15 5.0 |
| Metglas 2605SA1 | 700 | 1 | 100 | 2.1 | 8.4 | n/a 5.2 | n/a 2.6 |
| | 700 | 8 | 100 | 2.6 | 8.3 | 36 3.3 | 18 1.6 |
| Permag Sample 1 | 700 | 1 | 100 | 0.5 | 10.5 | 7.4 3.8 | 2.6 1.4 |
| | 700 | 8 | 100 | 3.8 | 10.6 | n/a 11 | n/a 3.9 |



Next Prototypes: 12.5 kV Inductive Adders



- The design for the first of two full-power, 12.5 kV, 250 A, inductive adders has been completed:
 - Air insulated, nominal output impedance 50Ω
 - Mechanical parts for the first 5 cells (layers) received
 - 4 layers assembled for testing magnetic cores
 - Layout designs of PCBs finished (by Cern DEM) and the PCBs layouts have been sent to production (today!)
 - Magnetic cores (Hitachi Finemet FT-3L) ordered in 2015 and partly received (50 %)
- Hardware upgrades:
 - Maximum voltage up to 12.5 kV (20 layers)
 - Maximum pulse duration up to 1 μ s flat-top at 700 V per layer (excluding rise/fall times and settling time of 100 ns)
 - RF amplifier (Tabor A10160) for feeding the RF power transistor in the active analogue modulation layer (1 A, peak, up to 45 MHz)
 - 8 branches per layer (soldering pads for 24 branches)
 - Fault detection and protection in the PCBs (short-circuit, saturation of a magnetic core)

 





Initial Measurements on Magnetic Cores for 12.5 kV Prototypes

- First full-size Finemet FT-3L cores for the two 12.5 kV prototypes have been evaluated
- According to initial measurements, the cores fulfil the specifications:
 - 2 cores per layer, effective cross-sectional area in total at least 14.7 cm²
 - Magnetizing inductance $L_m \sim 50 \mu\text{H}$ for 1.6 μs at 700 V ($\mu_{r,\text{core}} \sim 35,000$)
 - Core loss resistance $R_c > 140 \Omega$
 - Maximum usable B-H flux swing ~ 0.9 T without biasing (from remnant field to the end of "linear" part of the B-H curve)
 - "Safe" pulse flat-top duration at least 1.1 μs (with ~ 100 % margin) at 700 V
- 12.5 kV prototypes can be used as a testbench for future projects at CERN (e.g. FCC):
 - Maximum pulse duration (at 700 V/layer) can be extended up to $\sim 3 \mu\text{s}$ by biasing the magnetic cores (compromises the pulse flat-top stability)
 - Maximum current capability of primary PCBs can be extended up to a few kA by powering 24 branches (depending on the semiconductor switches)
 - Soldering pads for 1.6 kV Leclanche prototype pulse capacitors. In the previous designs, only 1.2 kV NWL capacitors used (from USA).

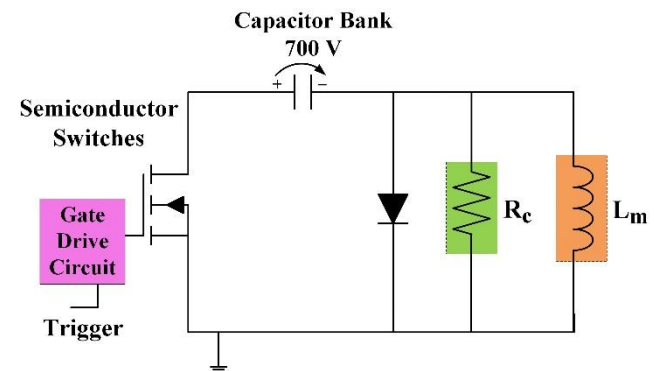 

- Two 5-layer, 3.5 kV prototype inductive adders have been built and tested at CERN
- Both passive and active analogue modulation methods tested to improve the flat-top stability of the output pulses
- The best measured flat-top stability for 160 ns pulse flat-top has been $\pm 0.05\%$ (± 0.96 V) at 1.8 kV, which was reached by applying active droop and ripple compensation.
- **The pulse power modulators for CLIC DR kicker systems are very probably feasible with inductive adder technology.**
- The design of the first full-size, 12.5 kV, 250 A, CLIC DR kicker prototype inductive adder is being finished. The main components and mechanical parts have been received and PCBs have been ordered.
- The initial measurements have commenced with full-size inductive adder cells to evaluate the magnetic cores.
- The evaluated Finemet FT-3L for 12.5 kV prototypes cores fulfil the specifications.

 









 


3D model of a 20-layer inductive adder at CERN (Courtesy of P. Faure)

- Assembly and testing of the first 20-layer, 12.5 kV, 250 A, prototype inductive adder
- Improve the precision of the active analogue modulation, to meet $\pm 0.02\%$ requirement for the combined droop and ripple:
 - Measurements with pulse flat-top duration up to 900 ns
 - Active analogue modulation layer with improved precision of ripple compensation (an RF amplifier between the RF MOSFET and a signal generator)
 - Measurements with a 16-bit oscilloscope
- Measurements of two 12.5 kV inductive adders with a stripline kicker installed in a beamline in an accelerator test facility
- Other possible applications for inductive adder technology at CERN:
 - FCC kicker systems (20 kV, 3.6 kA, 2.5 μ s)
 - PS KFA kicker system (40 kV, 1.5 kA, 2.6 μ s)



Questions & Comments?

         

January 21, 2016

CLIC WS 2016



References and Bibliography

1. Holma J., "A Pulse Power Modulator with Extremely Flat-top Output Pulses for the Compact Linear Collider at CERN", Ph.D. Thesis, Aalto University, School of Electrical Engineering, Helsinki, Finland, 2015.
2. Holma J., Barnes M.J.: "The Prototype Inductive Adder With Droop Compensation for the CLIC Kicker Systems.", IEEE Trans. Plasma Sci., Vol. 42, No. 10, Oct. 2014.
3. Holma J., Barnes M.J., Belver-Aguilar C.: "Measurements on a Prototype Inductive Adders with Ultra-flat-top Output Pulses for CLIC Kicker Systems", Proc. IPAC'14, Dresden, Germany, June 15-20, 2014.
4. Holma J., Barnes M.J.: "Initial Measurements on a Prototype Inductive Adder for the CLIC Kicker Systems", Proc. of PPC'13, San Francisco, CA, USA, June 16-21, 2013.
5. Holma J., Barnes M.J., Ovaska S.J.: "Modelling of Parasitic Inductances of a High Precision Inductive Adder for CLIC", Proc. of IPAC'13, Shanghai, China, May 12-17, 2013.
6. Holma J., Barnes M.J.: "Sensitivity Analysis for the CLIC Damping Ring Inductive Adder", Proc. of Int. Power Modulators and High Voltage Conference, San Diego, CA, USA, Jun. 3-7, 2012.
7. Holma J., Barnes M.J.: "Evaluation of Components for the High Precision Inductive Adder for the CLIC Damping Rings", Proc. of IPAC 2012, New Orleans, USA, May 20-26, 2012.
8. Holma J., Barnes M.J.: "Pulse Power Modulator Development for the CLIC Damping Ring Kickers", CLIC-Note-938, CERN, Geneva, Switzerland, April 27, 2012.




Spare Slides




Contributors to the Droop of the Output Waveform of an Inductive Adder


- The droop of the output pulse of an inductive adder is caused by:
 - The small voltage droop of the storage capacitor (C_s) as it supplies charge during the pulse
 - The resistive losses in the primary switch and in the primary circuit (R_{sw}), which depends on the current through the magnetizing inductance (L_m).
- **Only the voltage droop of the capacitors can be compensated by adding more capacitance per layer!**
- **The only methods to effectively decrease the droop, caused by a combination of resistive losses and magnetizing inductance of the transformer core, is to apply either passive or active analogue modulation (or both) for the output pulse.**
- **These methods are necessary to reach very low droop ($\ll 1\%$).**

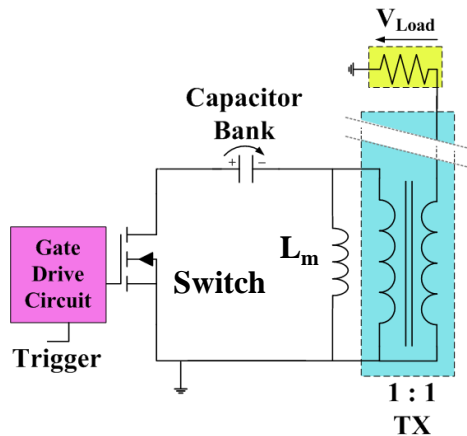

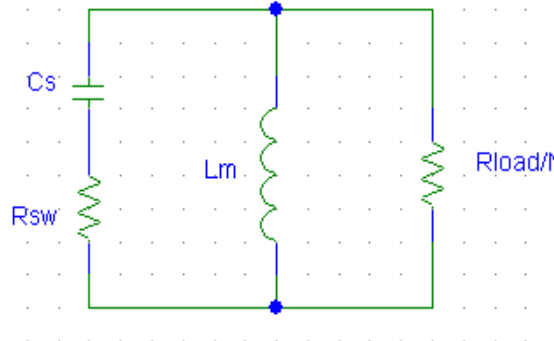Simplified schematic of a constant voltage layer of an inductive adder



 Simplified model of a layer of an inductive adder during the pulse



Capacitor voltage V_{cap} and voltage of a layer V_{layer} during a pulse. $C_s = 24 \mu\text{F}$, $R_{sw} = 0.34 \Omega$ and $R_{load}/N = 10 \Omega$.




Compensation of Droop and Ripple

- In analogue modulation layer, there is no storage capacitor but there is resistor R_a
- Resistor R_a is effectively in series with the load
- Load voltage during the flat-top:



$$V_{Load} \approx \frac{R_{Load}}{R_{Load} + R_a} V_{Max}$$

- V_{Max} is the sum of the voltages over the layers except the analogue modulation layer: $V_{Load} \leq V_{Max}$!
- Resistor R_a is in parallel with magnetizing inductance L_m
- Compensation modes:
 - **PASSIVE MODE:** During the pulse, current through L_m increases, which causes current through R_a to decrease. Therefore, voltage over R_a decreases, which causes V_{Load} to increase. This voltage change is reverse in comparison with voltage droop caused by storage capacitors in other layers.
 - **ACTIVE MODE:** A linear RF power transistor provides a shunt path for the current through resistor R_a . Therefore, the voltage over R_a can be controlled by controlling the current through the RF power transistor.

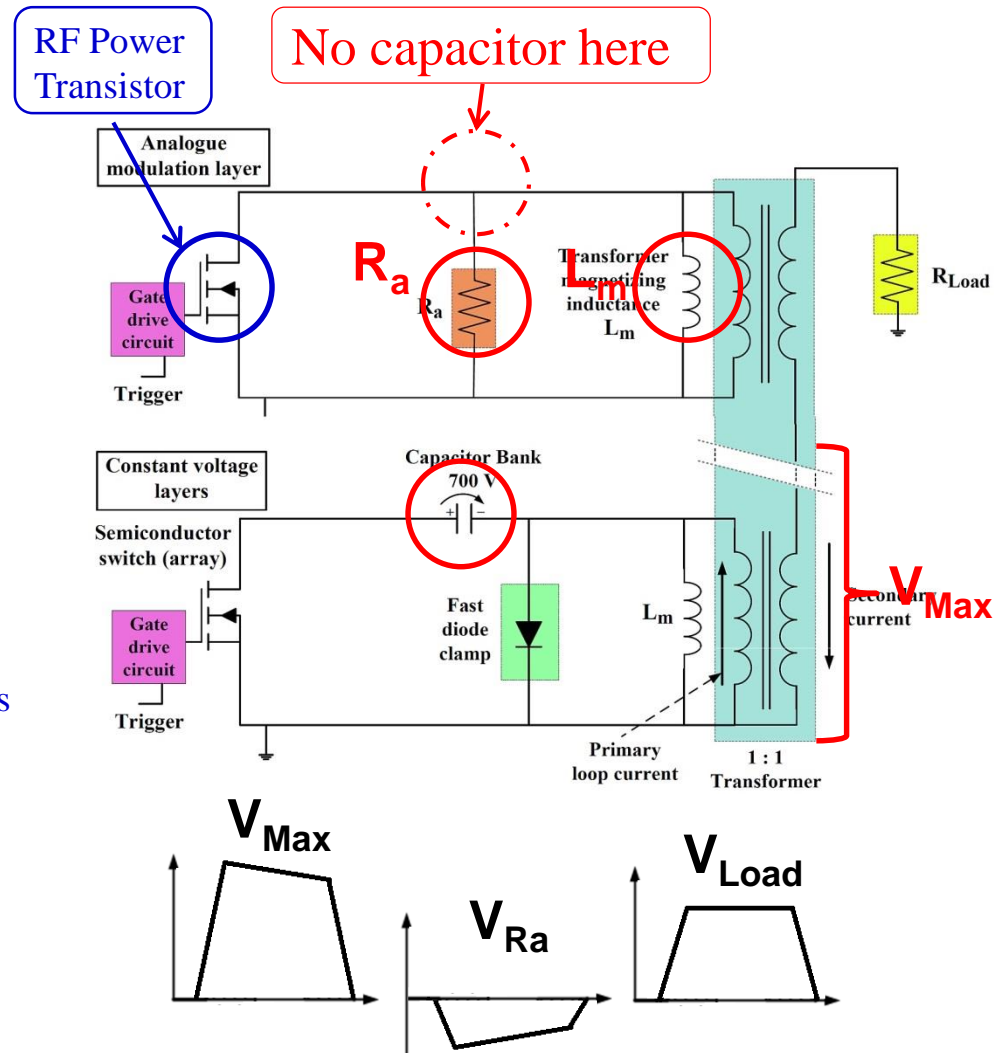




Compensation of Droop and Ripple

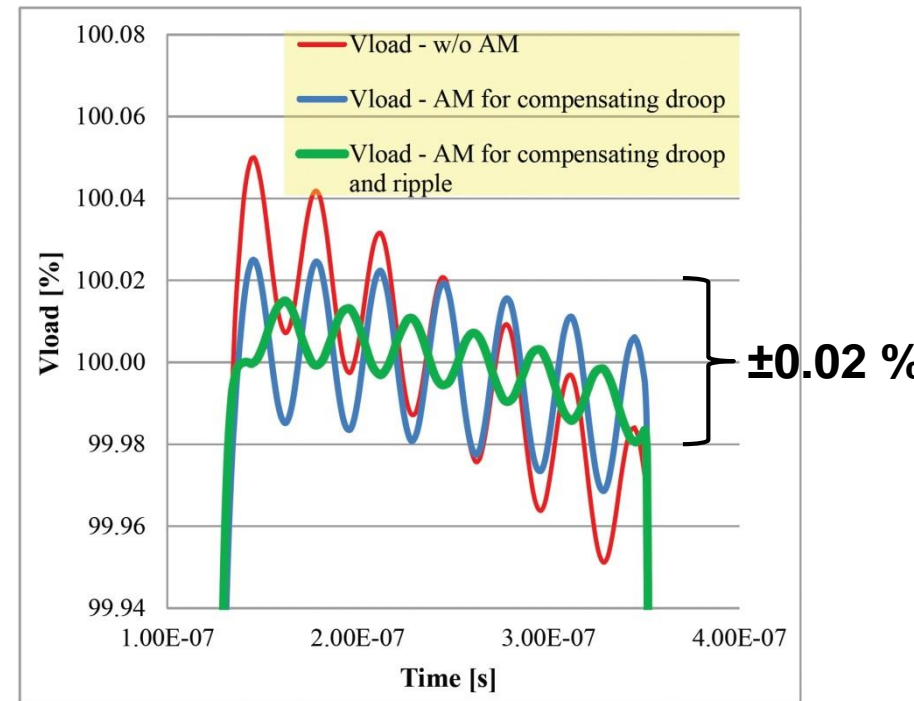 

- **Passive analogue modulation – partial droop compensation**
- **Active analogue modulation – partial droop and ripple compensation**
- **For the CLIC DR kicker modulator, both PASSIVE and ACTIVE modulation methods will be applied!**



Measurements: Active Ripple Generation

 

Setup for the measurement:

- 4 constant voltage layers and a passive analogue modulation layer
- 1 branch powered per half-layer PCB, 2 branches per layer
- Capacitors (24 μF /layer) initially charged to 200 V ($R_a = 7.9 \Omega$)
- Active ripple generation with a positive ramp (blue) and 2 MHz (red), 10 MHz (purple) and 30 MHz (green) sine waves.



Note:

- Modulation range: ~10 % of the maximum output voltage



Measurements: Active Ripple Compensation

- **Setup for the measurement:**
 - The prototype adder with 5 layers
 - 1 branch powered per half-layer PCB, 2 branches per layer
 - Capacitors (24 μ F/layer) charged initially to 551 V
 - Active analogue modulation layer
 - Modulation signal: a ramp + a sine wave with a frequency of 5...25 MHz.
- **Steps for active ripple compensation**
 - Gain and phase responses for the injected compensation signal from the signal generator to the load voltage were measured
 - Correction factor were defined for compensation signal
 - Load voltage was measured
 - Fast Fourier Transform (FFT) was applied to define the most significant ripple components
 - A compensation signal, consisting of ramp to compensate the droop and a sine wave to compensate the most significant ripple component was created.
 - The compensation signal was applied and the load voltage was measured.

 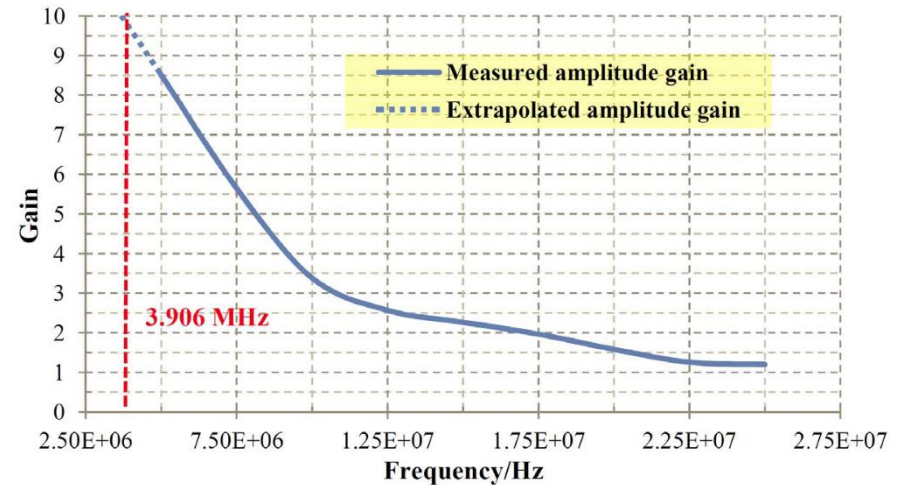





Demonstration of Active Ripple Compensation in Time and Frequency Domains

Time domain

- Original waveform: load voltage with ramp compensation applied (blue)
- Compensated waveform (green): the droop and the most significant ripple frequency has been compensated
- A ripple component deliberately amplified (red): the most significant ripple component has been amplified (phase shift of the ripple component -180 degrees in comparison with the green curve)

Frequency domain

- Magnitudes of FFTs of the original load voltage (blue), ripple compensation applied (green) and a ripple component amplified (red).
- FFT of original waveform: load voltage with ramp compensation applied (blue)
- FFT of compensated waveform (green): the droop and the most significant ripple frequency has been compensated
- FFT of a the waveform in which a ripple component has been amplified (red): phase shift of a ripple component -180 degrees in comparison with the green curve

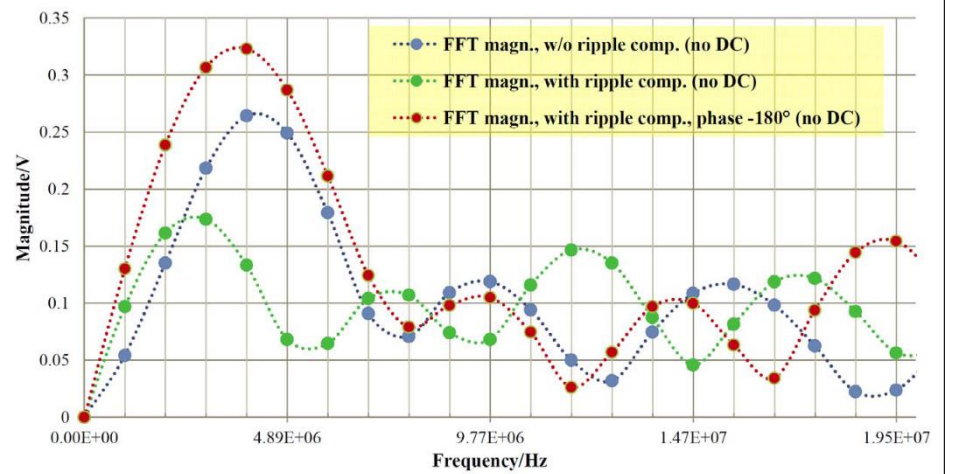 



Evaluation of Accuracy of the Measurements

- The effective bit length of a 8-bit ADC is 6-7 bits.
- The effective bith length of the oscilloscope can be increased with the following means
 - Oversampling (OS)
 - Ensemble averaging (EA)
 - **Both these methods were applied**
- Accuracy of the measurements
 - **Active droop compensation:**
 - The best measurements: **$\pm 0.06\%$ ($\pm 1.17\text{ V}$)**
 - The effective number of bits of the ADC: **6** (effective length of bits) + **1** (OS,4x) + **6** (EA,4k) = **13**
 - Absolute precision: **0.37 V** (in the range of 3 kV)
 - **Active droop and ripple compensation:**
 - The best measurements : **$\pm 0.05\%$ ($\pm 0.96\text{ V}$)**
 - The effective number of bits: **6** + **1** (OS,4x) + **5** (EA,1k) = **12**
 - Absolute precision: **0.73 V** (in range of 3 kV).
 - With EA of 4k, the numbers were $\pm 0.06\%$ ($\pm 1.02\text{ V}$), 13 bits and 0.37 V.

| Mod. method | PM (d) | AM (d) | AM (d&r) |
|------------------------------|------------|--|--|
| ΔU_{d+r} (%) | ± 0.16 | ± 0.07 (1k) ± 0.06 (4k) | ± 0.05 (1k) ± 0.06 (4k) |
| ΔU_{d+r} (V) | ± 1.9 | ± 1.23 (1k) ± 1.17 (4k) | ± 0.96 (1k) ± 1.02 (4k) |
| Res _{Enh,OS} (bits) | 0 | 1 1 | 1 1 |
| Averaging (n) | 100 | 1000 4000 | 1000 4000 |
| Res _{Enh,EA} (bits) | 3.3 | 5 (1k) 6 (4k) | 5 (1k) 6 (4k) |
| V _{r,ADC} (V) | 2000 | 3000 (1k) 3000 (4k) | 3000 (1k) 3000 (1k) |
| Res _{Rel} (%) | 0.16 | 0.024 (1k) 0.012 (4k) | 0.024 (1k) 0.012 (4k) |
| Res _{Abs} (V) | 3.2 | 0.73 0.37 | 0.73 0.37 |

ΔU_{d+r} = combined droop and ripple (flat-top instability), Res_{Enh,OS} = resolution enhancement by oversampling (averaging of samples), Res_{Enh,EA} = resolution enhancement by ensemble averaging (averaging of pulses), V_r = voltage range of a measurement channel, Res_{Rel} = relative accuracy, Res_{Abs} = absolute accuracy