

JUAS 2012 – RF Exam (solutions)

F. Caspers, M. Betz

1 Transmission lines

1. $C' = 1/(v Z) \quad C' = 1/(0.5 \cdot c \cdot 75 \Omega) = 88.9 \text{ pF/m}$
 $L' = Z/v \quad L' = 75 \Omega / (0.5 c) = 500 \text{ nH/m}$
2. $C' = 100 * \sqrt{\epsilon_r} / (3Z) \quad \rightarrow \quad \epsilon_r = (C' \cdot 3Z / 100)^2 \quad \rightarrow C' = 0.889 \text{ pF/cm}$
 $\epsilon_r = 4.0$
3. $Z = \sqrt{\mu_r/\epsilon_r} \cdot 60 \cdot \ln(R/r) \quad \rightarrow \quad R/r = \exp[Z / (\sqrt{\mu_r/\epsilon_r} \cdot 60)]$
 $r = R / \exp[Z / (\sqrt{\mu_r/\epsilon_r} \cdot 60)]$
 $r = 0.82 \text{ mm}$
4. Which of these are TEM transmission lines? Mark them:
 - ✓ Stripline
 - ✓ Coaxial cable
5. Advantages of microstriplines
 - ✓ Easier to incorporate lumped components (like transistors, capacitors, inductors, etc.)