

# JUAS 2016 – RF Tutorial

F. Caspers, M. Betz, M. Wendt

$$\mu = \mu_0 \mu_r$$

$$\mu_0 = 4\pi \cdot 10^{-7} \text{ Vs/(Am)}$$

$$\varepsilon = \varepsilon_0 \varepsilon_r$$

$$\varepsilon_0 = 8.854 \cdot 10^{-12} \text{ As/(Vm)}$$

$$c_0 = 2.998 \cdot 10^8 \text{ m/s}$$

## Cavity Equivalent Circuit

### Exercise 1:

A low-Q cavity resonator has an equivalent parallel RLC circuit with an inductance  $L = 15.915 \text{ nH}$ , a capacitance  $C = 1.5915 \text{ pF}$ , and a shunt (parallel) impedance of  $R = 1 \text{ k}\Omega$ .


### Questions:

Determine some of the relevant parameters of this parallel equivalent circuit of the cavity resonator:

1. the resonant frequency  $f_{res}$ .
2. the characteristic impedance  $R/Q$ .
3. the quality factor  $Q$ .
4. the 3-dB bandwidth.
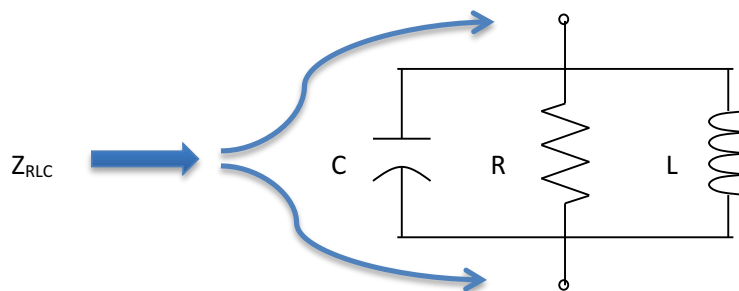
### Exercise 2:

Given is the low-Q cavity with the equivalent RLC parallel circuit and the values from Exercise 1.




### Questions:

1. Plot the impedance of the equivalent parallel circuit of the resonator as locus curve in the complex plane.  
(Use paper, triangle ruler and a pair of compasses. Scale: e.g.  $100 \text{ }\Omega \rightarrow 1 \text{ cm}$ ).
2. Indicate the 3-dB bandwidth points, and measure  $|Z_{3dB}|$  by using a ruler.
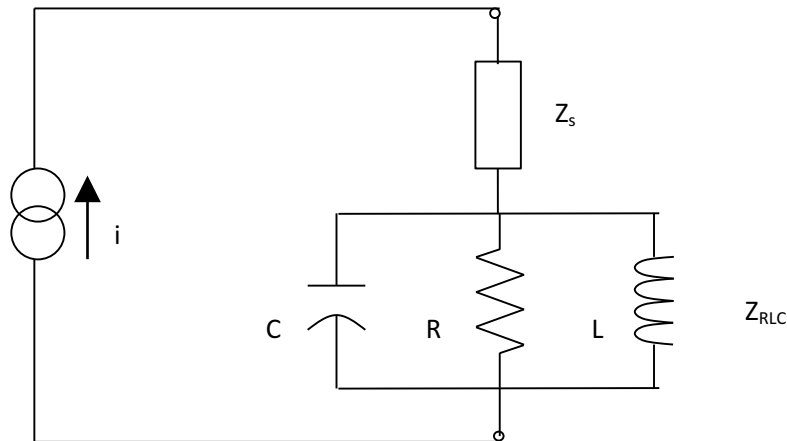
### Exercise 3:

Now the cavity resonator with the above RLC equivalent parallel circuit is driven by an ideal current source  $i$ , i.e. a generator with an infinite high impedance. In series an impedance is added to the RLC parallel resonator, the total impedance  $Z_{tot}$  is given by the series impedance  $Z_s$  in series to the impedance of the RLC parallel resonator  $Z_{RLC}$ . For the  $Z_s$  assume three cases:

- a pure resistive impedance  $R_s = 200 \text{ Ohm}$  (e.g. due to cable losses)
- a pure inductive impedance  $L_s = 31.831 \text{ nH}$  (e.g. inductive coupling)
- a pure capacitive impedance  $C_s = 0.7958 \text{ pF}$  (e.g. a defect of the cable or connector)



### Questions:

1. Plot the locus curve of the total impedance  $Z_{tot} = Z_{RLC} + Z_s$  in the complex plane (assume a constant frequency  $f \cong f_{res}$  for the series impedance).
2. How does the series impedance  $Z_s$  affect the locus curve of the overall impedance  $Z_{tot}$  for the 3 cases?
3. Now assume the resistive series impedance  $R_s$ , is the internal source resistor of a voltage source generator, which is the more typical case. What is the effect on the RLC resonator? Plot the  $Z_{tot}$  in the complex plane for  $R_s = 200 \text{ Ohm}$

### Exercise 4: <http://www.amanogawa.com/index.html> (for home)

Open the above website and locate

“Circuits -> Java™ Applets browser window -> Parallel Resonant Circuit”

- Verify the Java applet starts
- Make yourself familiar with the settings (it will be difficult to exactly set the parameters of the above example)
- Notice the settings for “Impedance” and “Generator”!
- Find an Impedance setting similar to Exercise 1, e.g.  $L = 15.915 \text{ nH}$ ,  $C = 1.592 \text{ pF}$ ,  $R = 1 \text{ kOhm}$ ,  $f = 1 \text{ GHz}$
- Find a Generator setting which approximates a high impedance source such that unloaded and loaded  $Q$  have similar value.
- Check the “Resonance Data”, and verify  $f_{res}$ ,  $Q$ , and  $BW$
- Modify the Generator settings and observe the changes on the Resonance Data. Notice the change of loaded  $Q$  and  $f_{res}$  while changing  $Z_G$  which is here a current source parallel to the cavity equivalent circuit.