

Solid State RF Amplifier Development at the Advanced Photon Source

D. Horan, D. Bromberek, A. Goel,
A. Nassiri, K. Suthar, G. Waldschmidt
June 23, 2016

Outline

- **9.77-MHz Driver Amplifier**

- *Application, design requirements and process*

- *Construction*

- *Performance*

- **352-MHz Amplifier Development**

- *Application, design requirements and process*

- *Construction*

- *Performance*



9.77MHz Design Requirements

- Replacement for original 20-year old obsolete driver amplifiers in accumulator ring rf system
 - *supplies rf drive to grounded-grid triode output stage*
- 9.77MHz operating frequency
- Output 50-500 watts cw
- Use Freescale MRFE6VP61K25 part
- RF gain 25dB minimum
- Forced-air cooling
- Fit into existing enclosures



ORIGINAL DRIVER AMPLIFIER



TRIODE POWER AMPLIFIERS




Design Process

- Circuit simulation tools not useful – *accurate model not available for transistor at 9.77MHz*
- Design was “cut-and-try” process, with measurements along the way
- Started with simple circuit, then made modifications necessary to achieve desired stability, gain, and efficiency
- Two prototype units were built: air-cooled and water cooled
- Separate output harmonic filter was designed and tested – *with interesting results*



Basic Circuit

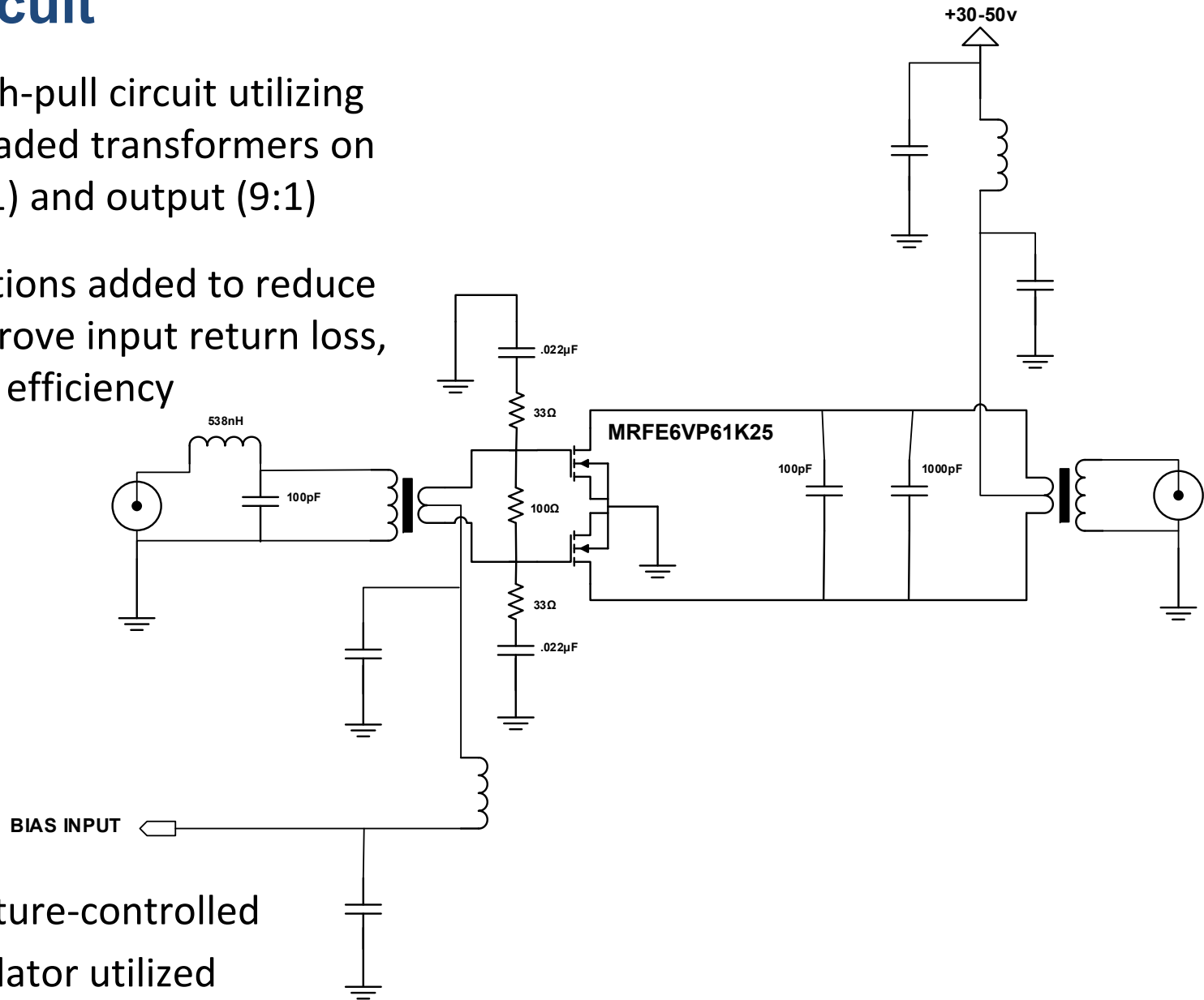- Basic push-pull circuit utilizing ferrite-loaded transformers on input (4:1) and output (9:1)
- Modifications added to reduce gain, improve input return loss, and peak efficiency





- Temperature-controlled bias regulator utilized




First Prototype Construction and Initial Testing

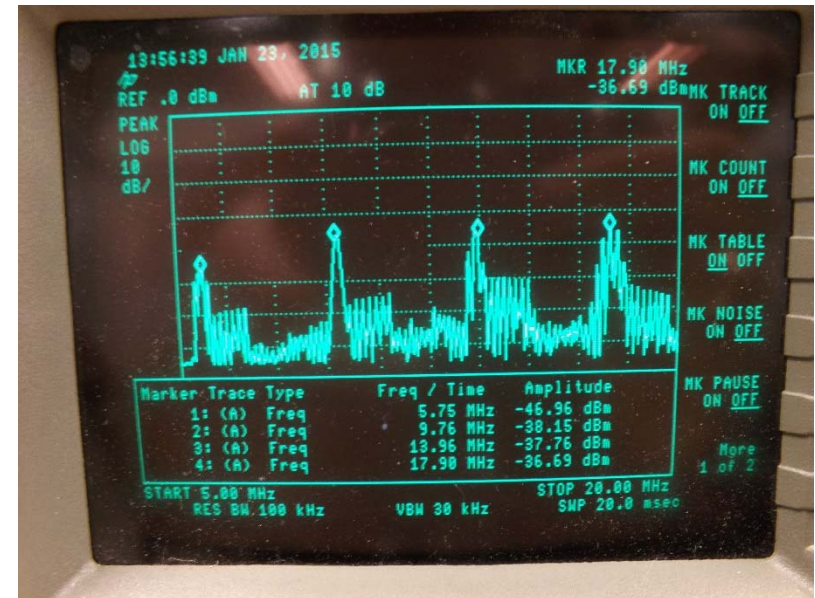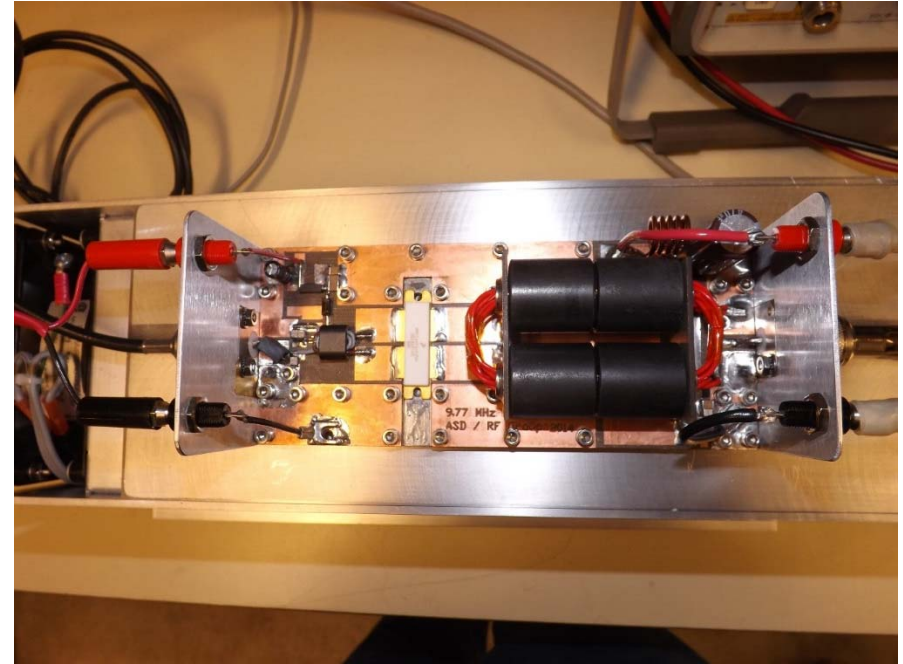- #61 ferrite cores used in both transformers
- $V_d = 45\text{v}$
- $V_g = 2.46\text{v}/I_{dq} = 200\text{mA}$
- RF in = 117mW – gain over 30dB!
- 136 watts rf output
- Input return loss only 5.65dB
- Numerous spurious rf signals seen in output →




First Prototype Construction and Initial Testing

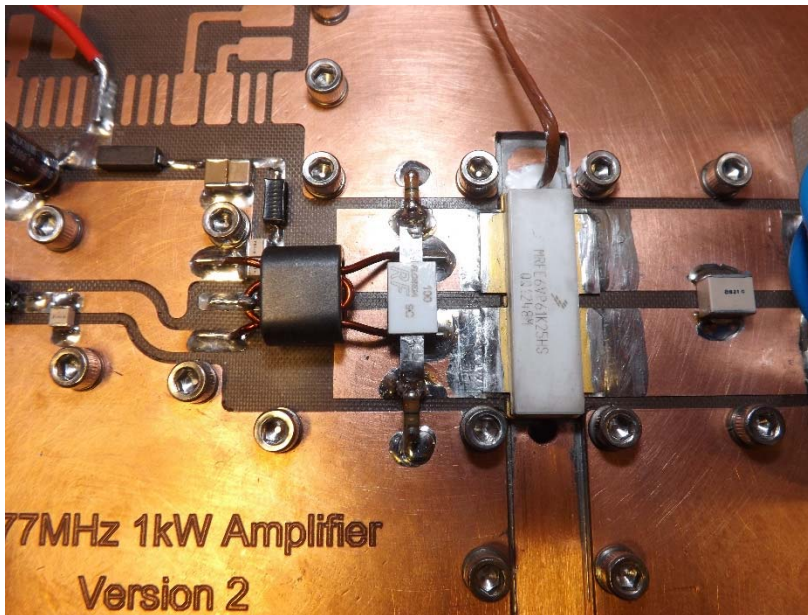- “Snubber” networks needed between gates and ground to reduce gain at lower frequencies
- Added 100Ω swamping resistor between gates



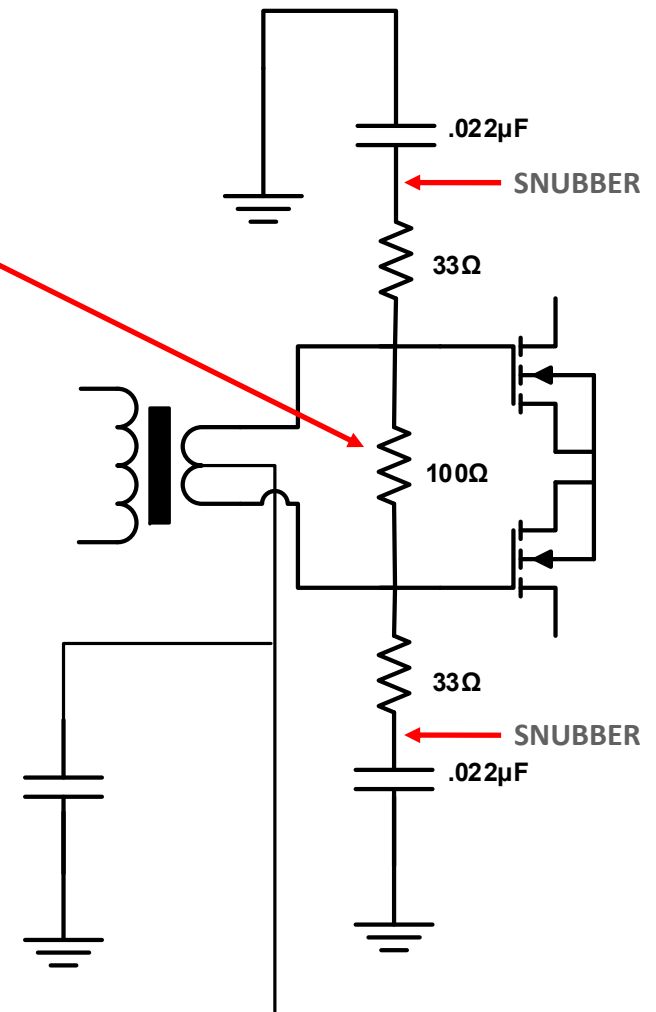- Oscillation and resulting spurs are gone
- Input return loss now 17-19dB depending on rf drive level




Output Transformer

-- Ferrites and Compensation

- Impedance measurements made using a spare board with a 12.5Ω resistance across primary winding
- Parallel capacitor across primary winding to optimize impedance seen by transistor:


PARALLEL CAPACITOR	SECONDARY IMPEDANCE
NONE	$112 + j27$
1,000pF	$74 - j29$
1,470pF	$62 - j30$
1,690pF	$53.2 - j31$

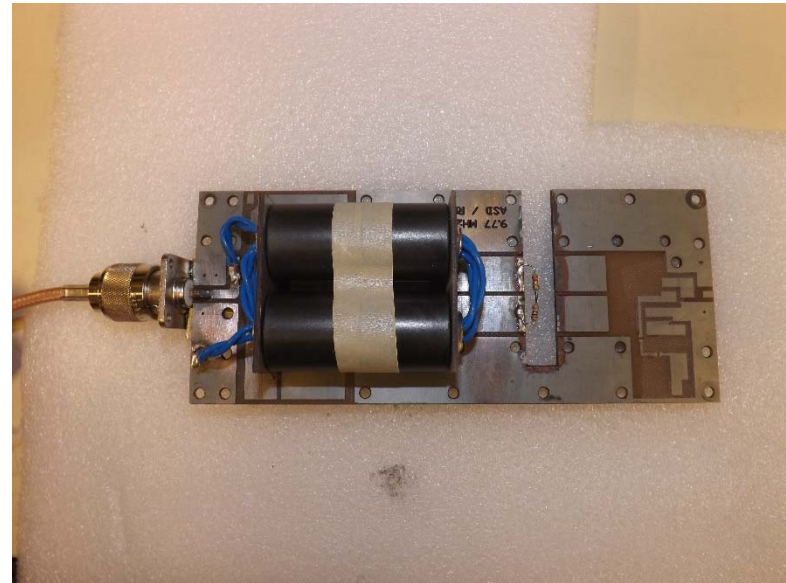- Little difference seen between #31 and #43 ferrites



Optimization of Output Transformer Compensation

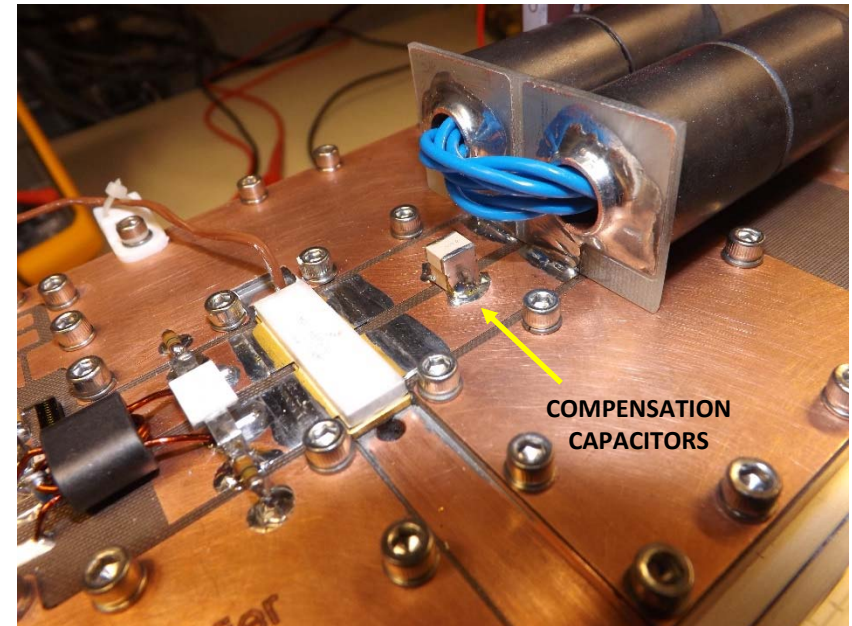
- Output transformer cores switched to #43 material
- Full-power efficiency measured for different compensation capacitor values
- Drain voltage = 50V



COMPENSATION CAPACITOR	RF INPUT POWER	RF OUTPUT POWER	GAIN	DRAIN CURRENT	EFFICIENCY
820 pF	1.84 watts	1,050 watts	27.56 dB	31.16 A	68.6%
1,000 pF	1.85 watts	1,130 watts	27.85 dB	31.09 A	73.9%
1,100 pF	1.98 watts	1,170 watts	27.71 dB	31.42 A	75.8%



Harmonics and Bandwidth

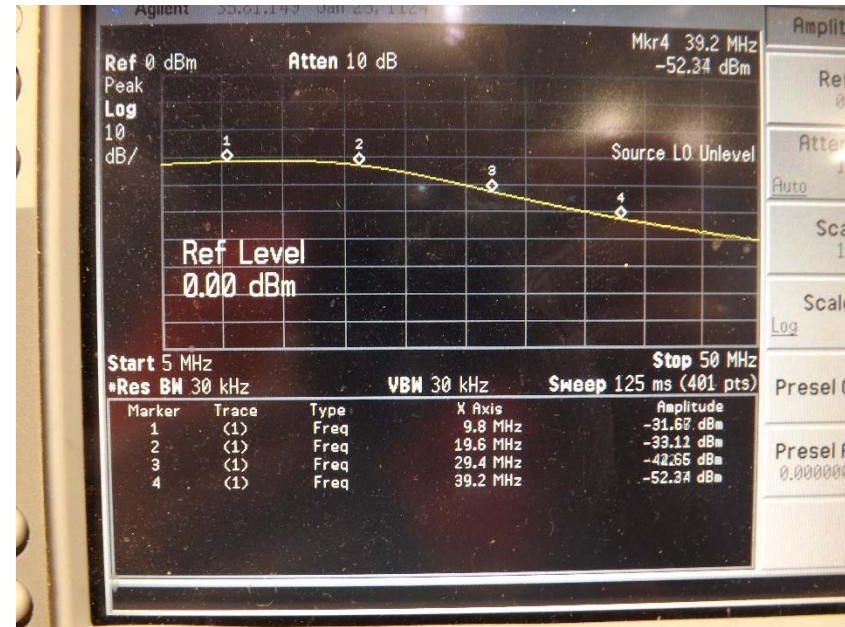


- Unfiltered harmonic amplitudes are quite high because of transformer coupling – *filtering required*
- Broad bandwidth – reasonable performance out to ≈ 15 MHz





30-Volt Operation

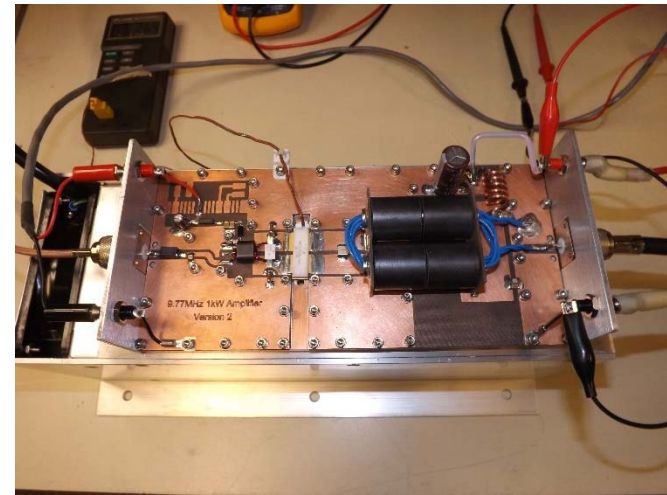- Thermal performance test:
 - 30 minutes continuous operation at saturation
- Forced-air cooling of heatsink



RF INPUT POWER	RF OUTPUT POWER	GAIN	DRAIN CURRENT	EFFICIENCY	TRANSISTOR FLANGE TEMP
0.538 watts	422 watts	28.9 dB	18.42 A	75.56%	34.1° C


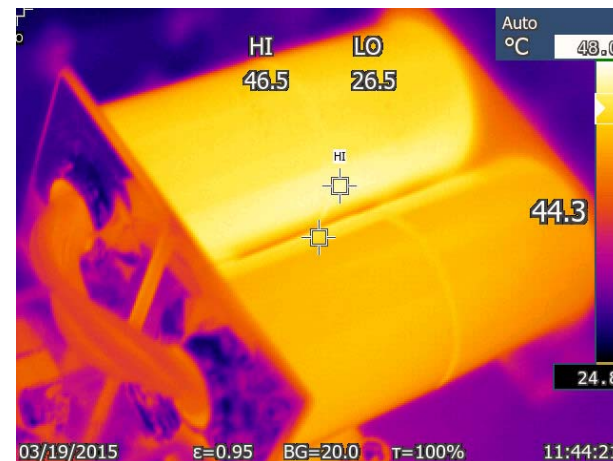
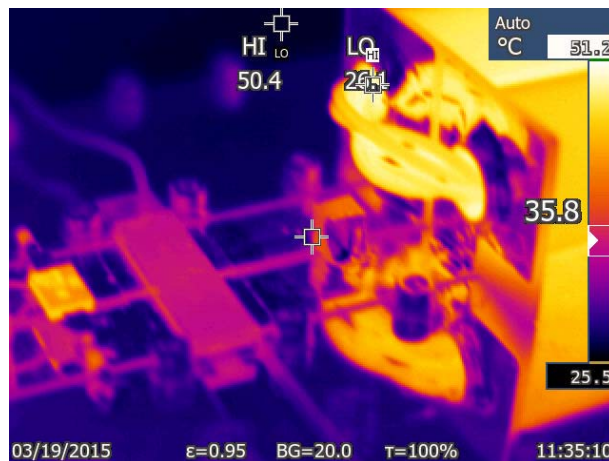


9.77MHz Output Harmonic Filter

-- Five-Element 50Ω Low Pass Chebyshev


- 30-volt operation with harmonic filter increases efficiency:

RF INPUT POWER	RF OUTPUT POWER	GAIN	DRAIN CURRENT	EFFICIENCY
1.28 watts	411 watts	25.06 dB	15.62 A	87.7%

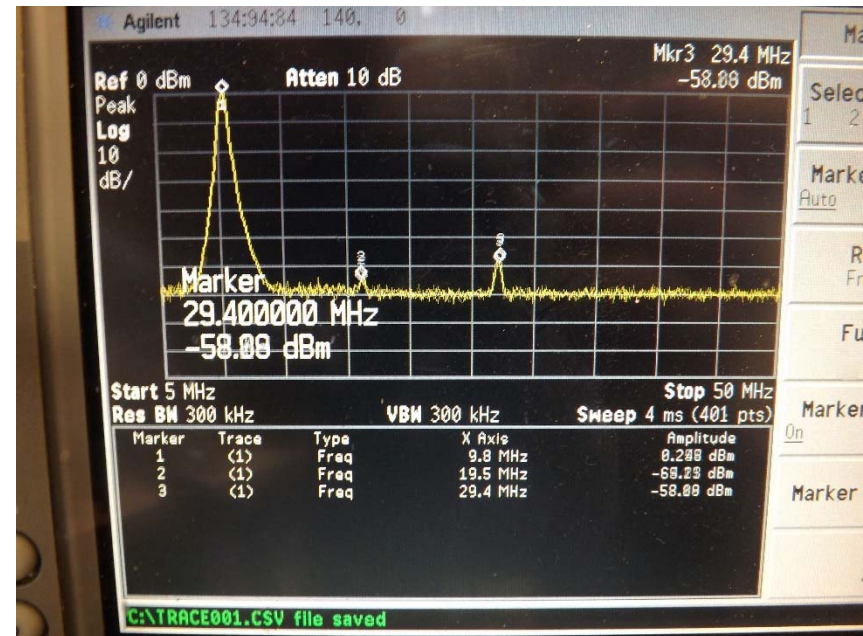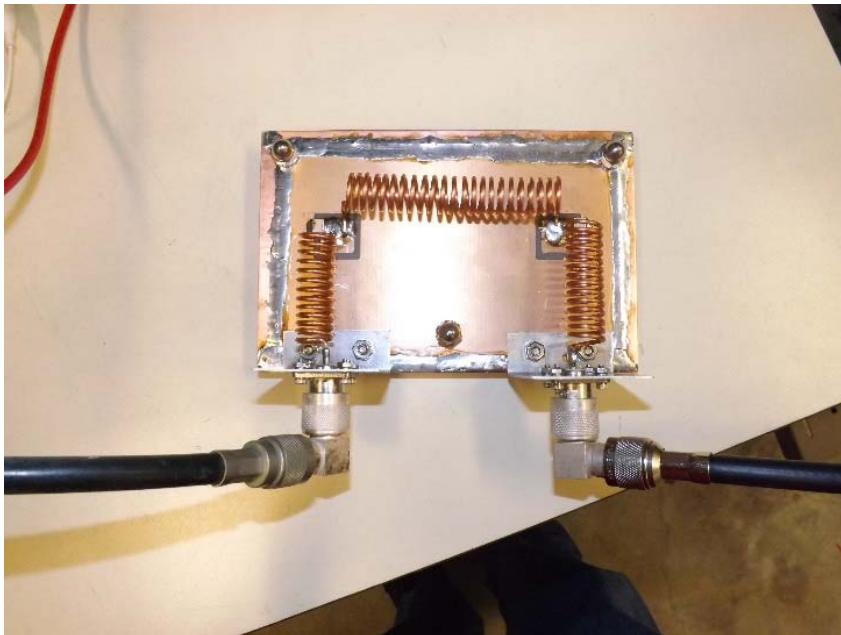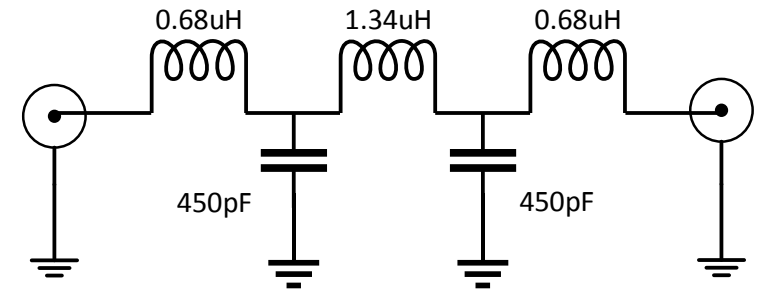

System Test

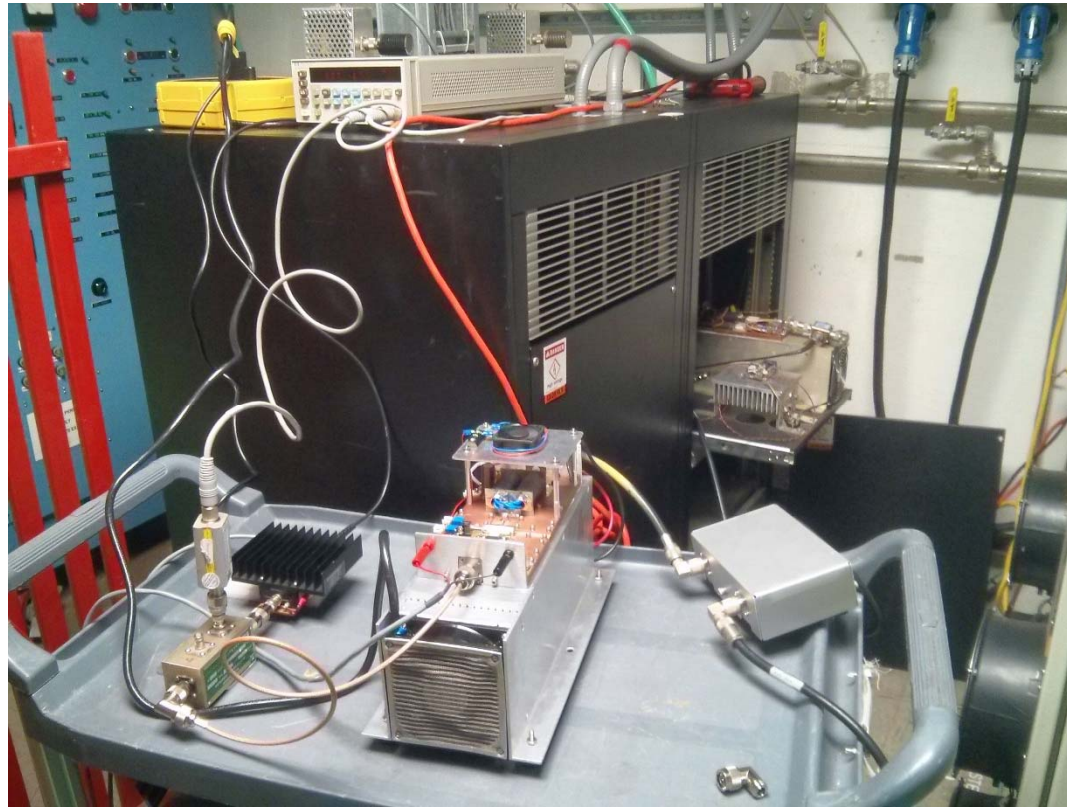- First prototype tested in accumulator ring rf system under beam conditions:





- No problems noted




Final Version – *Added Features*

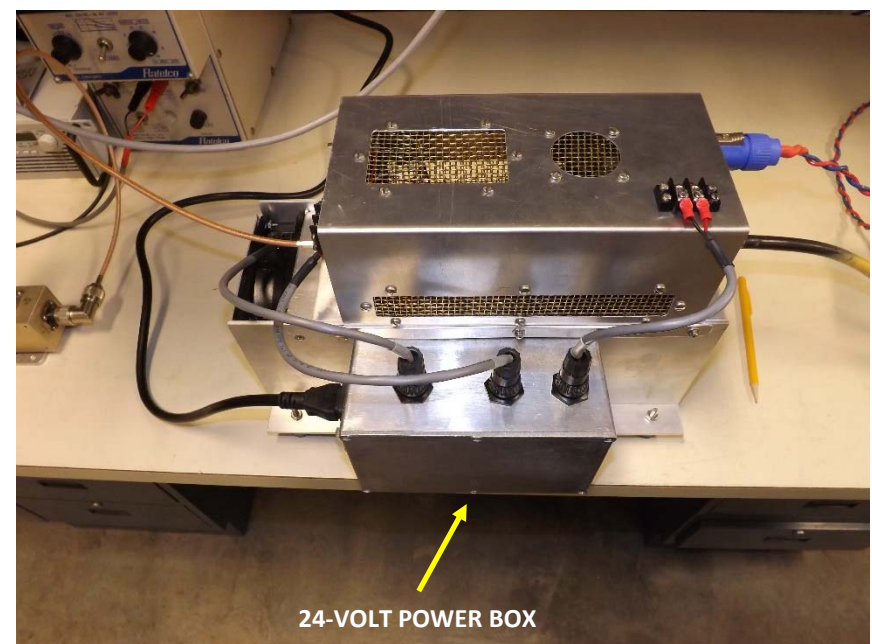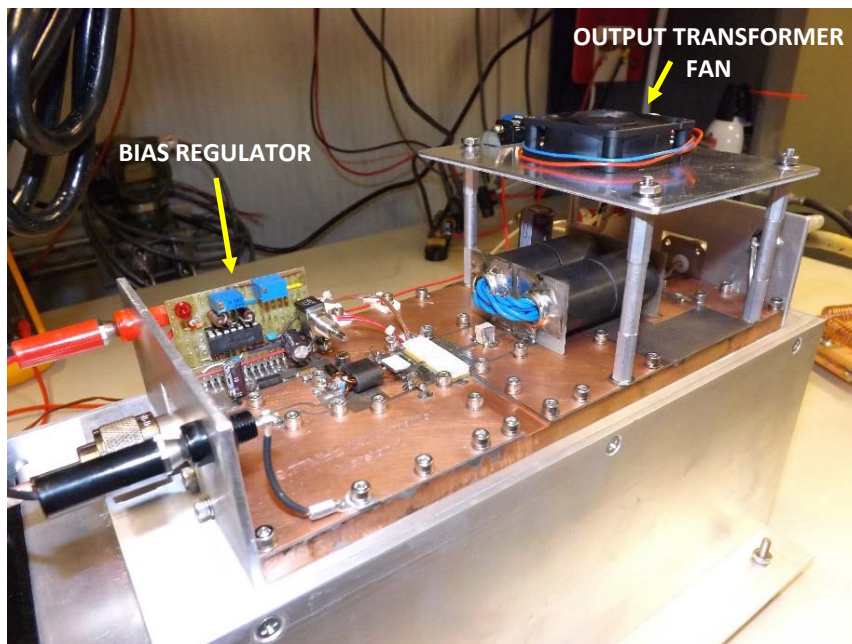- Thermal tracking bias regulator
- Fan for output transformer
- Central 24-volt power for bias regulator and fans
- Shielded enclosure



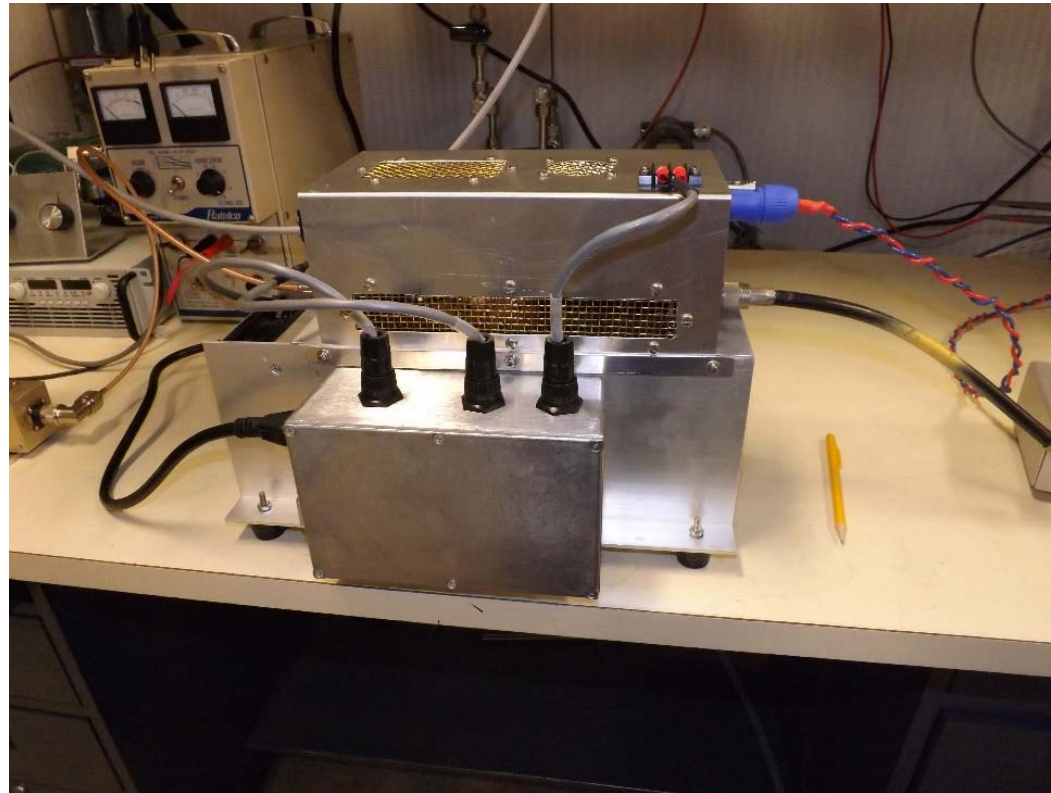9.77MHz Driver Amplifier -- Summary

- Four units will be built and tested
- Two units will be installed in rf systems in 2016-2017



352-MHz Solid State Amplifier Development

- **Ultimate goal**: Design and build a 352-MHz/200kW rf system that could be used for both the storage ring and booster
 - Achieve 2kW output per LDMOS device to minimize system complexity
 - Utilize a resonant cavity output combiner to reduce complexity and enhance efficiency

Initial R&D goal: Build a 12kW cw demonstration amplifier utilizing six 2kW amplifier modules driving a combining cavity:


- 2kW cw output per module
- Module efficiency > 65%
- Single push-pull package
- Operate device at 60V
- Use Freescale (now NXP) MRFE6VP61KH25 device



352-MHz/2kW Amplifier Design --

Cooling System

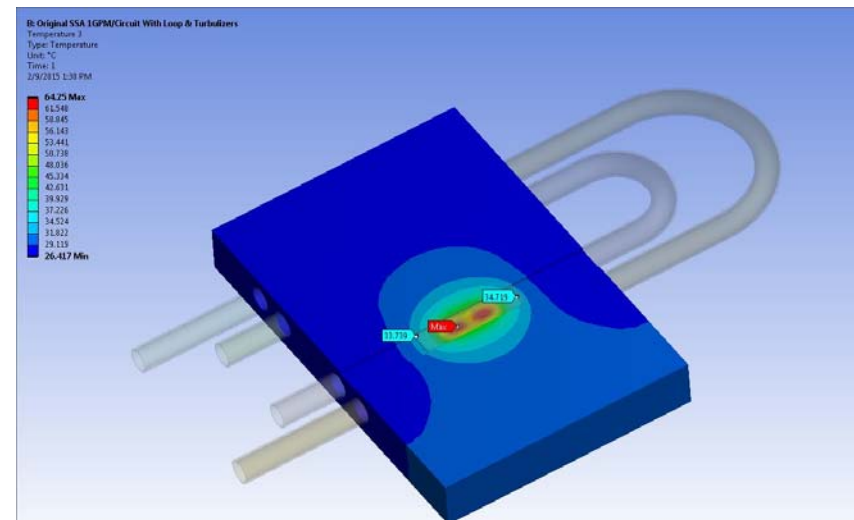- Conventional copper cold plate + carrier construction used for prototype amplifiers
- Thermal model developed and verified



352-MHz/2kW Amplifier Design – A. Goel

Source/Load Impedance from Simulation


- Source and load pull simulations provided the answer, but:
 - If starting impedance guesses are not correct, search space is the entire smith chart.
 - Large search space leads to model convergence errors
 - Iterative and time consuming
 - Prone to errors
- A better approach:
 - Use simultaneous Load and Source impedance optimization with specified goals of output power and efficiency.
 - Both ADS and MWO have simulation components that can do this




352-MHz/2kW Amplifier Design – A. Goel

Matching Network: Balun

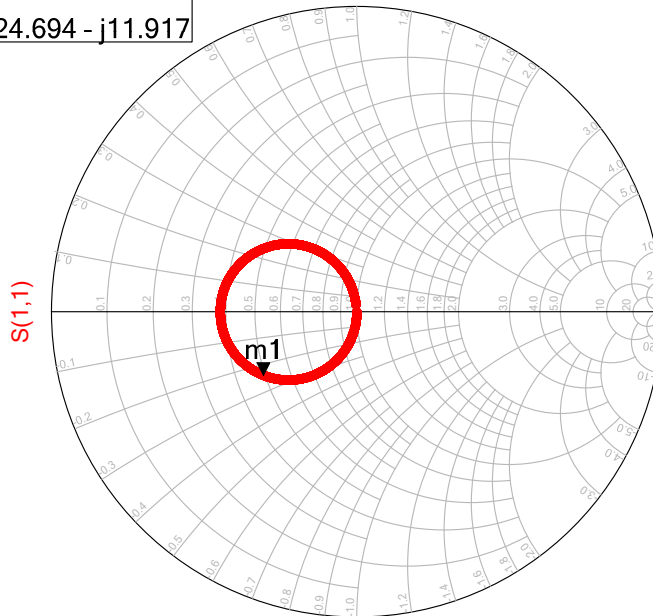m1
freq=352.0MHz
S(1,1)=-0.306 - j0.208
Len=3.448E3
impedance = 24.694 - j11.917



freq (352.0MHz to 352.0MHz)


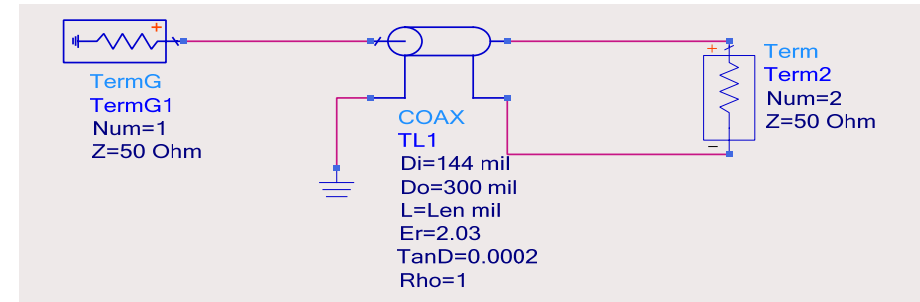


- Start with the balun and decide upon a practical length if using a coax balun
- 25 ohm coax used as balun on input and output:
 - Provides a complex 1:2 transformation ratio for real part in unbalanced mode
 - Practical length considerations prevented use of quarter wavelength



352-MHz/2kW Amplifier Design – A. Goel

Matching Network Design

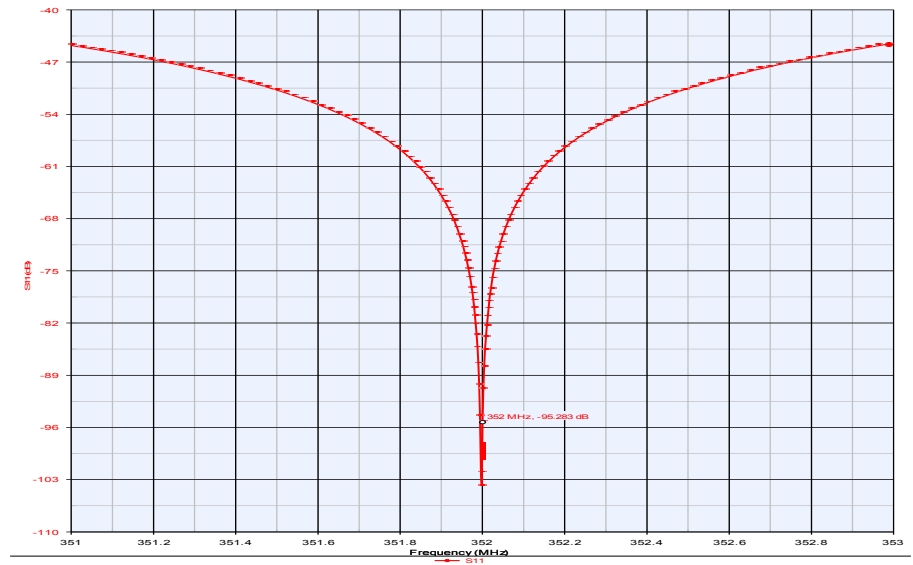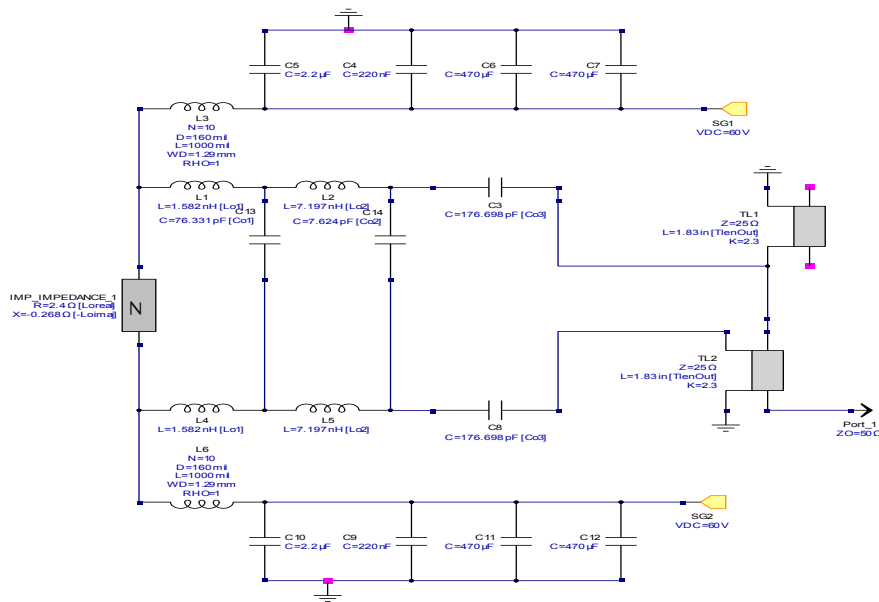


- Start with a lumped element LC matching network
- Take the conjugate of the complex impedance value obtained from the impedance optimization
- Convert results from an unbalanced simulation to balanced mode
- Bias filtering network included when designing the matching network
- Design the LC match such that inductors are confined to the series section and there is at least one series capacitor (for DC blocking)
- Replace the inductors with equivalent transmission lines
- Use the widest possible trace width for the input and output as this maximizes current carrying capability and makes soldering much easier



352-MHz/2kW Amplifier Design – A. Goel



Version 1

- Test at 60 volts
- Design based entirely on simulation results
- Input section match worked very well: *needed to move only 1 capacitor a few cm*
- Input return loss was -16dB.
- DC simulation results matched well
- ***Did not produce any power amplification -- output match problems!***
- Model errors are the most likely cause:
 - Model only validated at 50V operation
 - Model de-embedding at high power is difficult and error prone
 - Parameters used to develop high power models are taken under pulsed conditions
- Version 1 used to measure device DC dissipation and validate thermal models

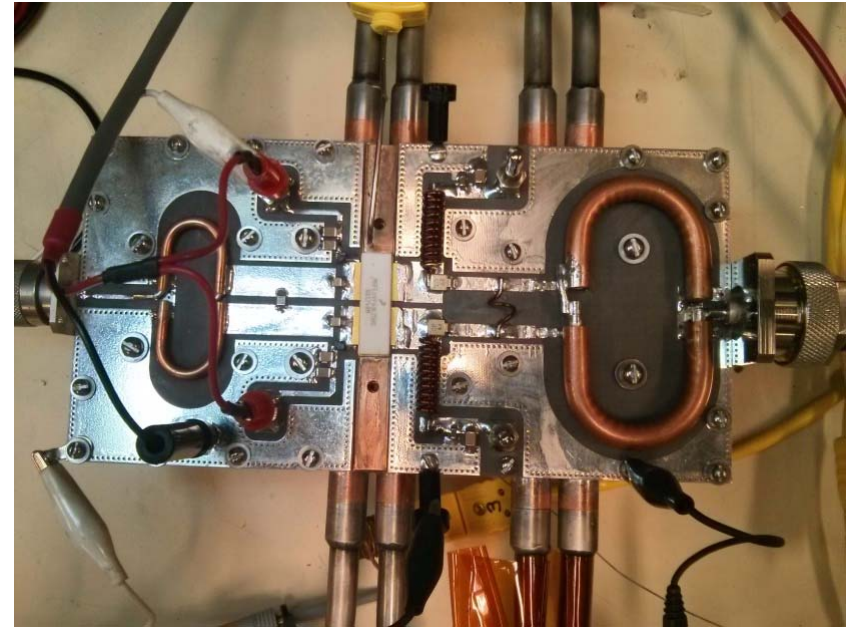

352-MHz/2kW Amplifier Performance – A. Goel

Modified Version 1

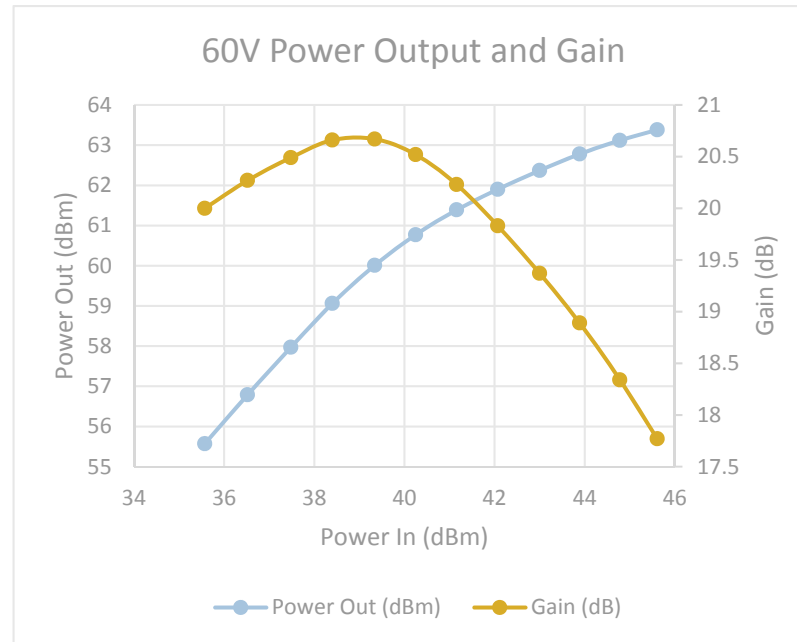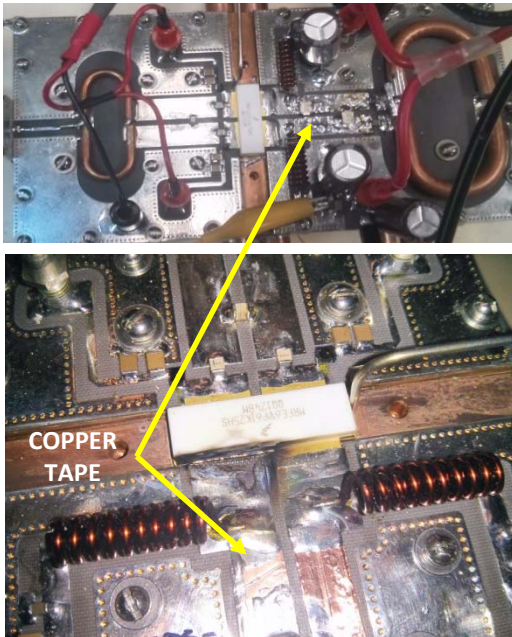

- Since input match was good no changes were made to input
- Modified drain circuit traces with copper tape to increase width
- Restricted components to all-metal mica caps to ensure thermal reliability
- After several days of tuning, stable pulsed operation achieved: 2.18kW, 10% duty cycle, 500Hz rep rate, $V_d = 60$ volts
- Used a mix of trend analysis and simulation to optimize component values
- *Destroyed one transistor in the process!*




352-MHz/2kW Amplifier Performance – A. Goel


Version 2



Power and Efficiency at $V_d = 60$ volts


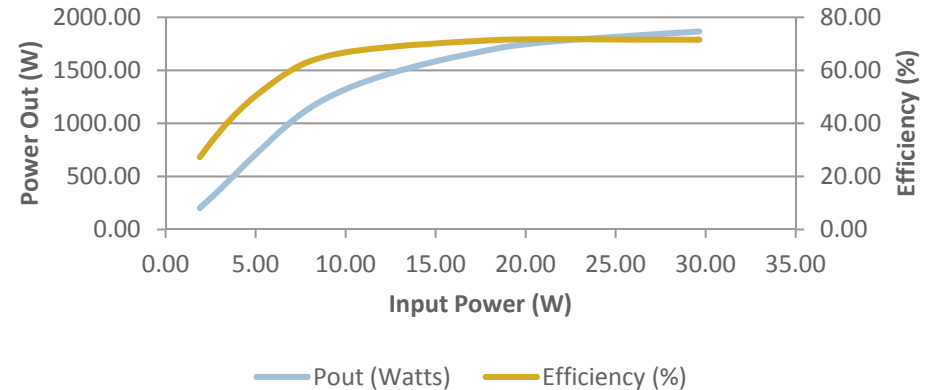


- Applied lessons learned from Version 1: Design new board with wider drain traces, and single break in trace for DC blocking
- No changes were made to input side
- After tuning: 1.86kW cw with 71.6% efficiency, 18dB gain
- Very stable and continuous operation for 2Hrs with no signs of thermal runaway or drift
- Harmonics are well controlled: at least -47dBC
- Further tune up has yielded 1-2% additional efficiency -- but no additional rf power

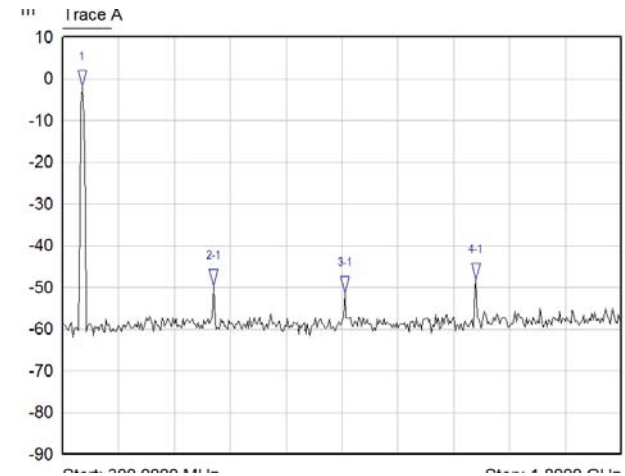

352-MHz/2kW Amplifier Performance – A. Goel

Version 2 - Drain Voltage Control

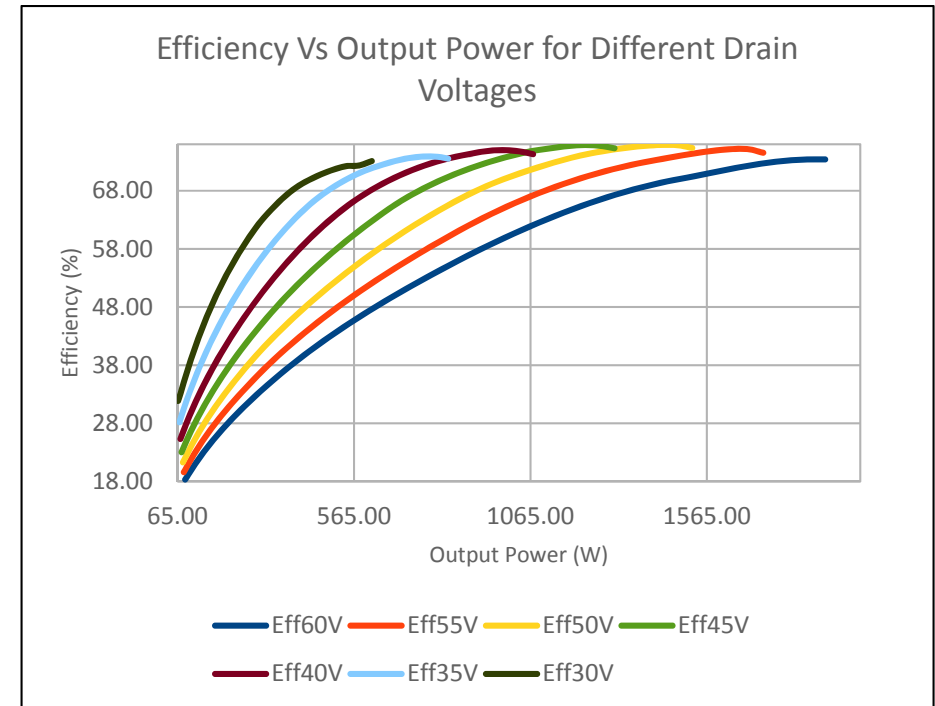
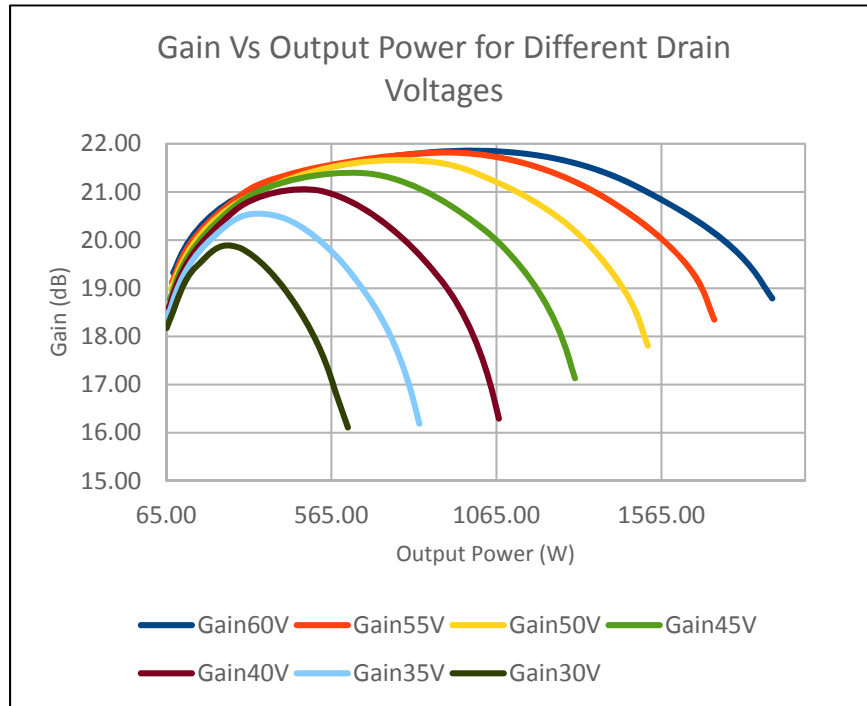


- The amplifier was operated at different drain voltages to characterize performance
- At least 70% efficiency is achievable over a wide output range by varying drain voltage



352-MHz/2kW Amplifier Performance – A. Goel

Version 2 - Drain Voltage Control

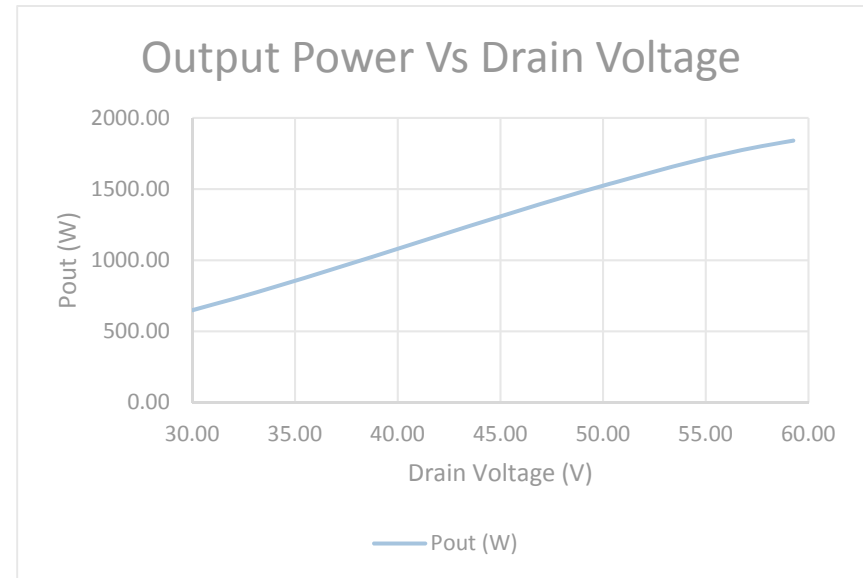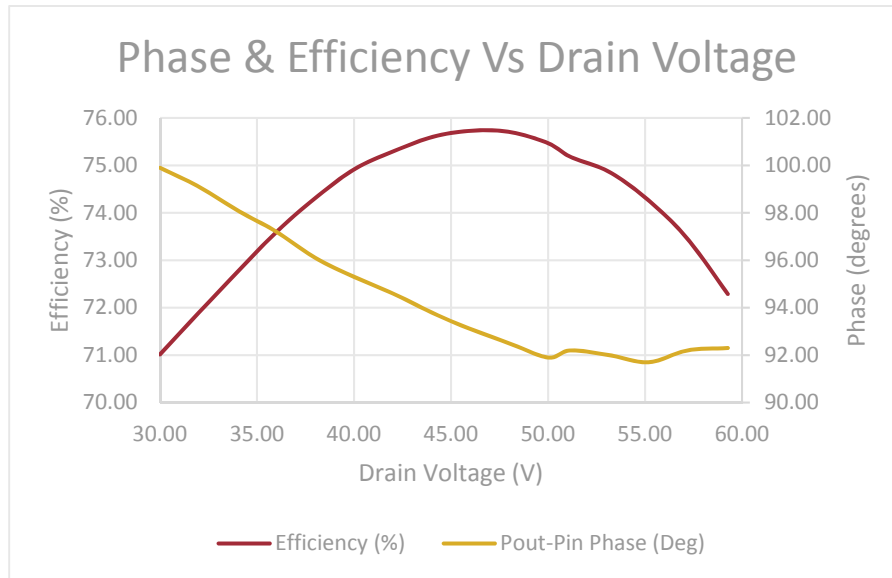


- Only 7.6 degrees of phase change from 30V to 60V change in drain voltage
- 1.27% Change in Efficiency for the same range
- Change in output power is very linear




352-MHz/2kW Amplifier Performance – A. Goel

Version 2 - Thermal

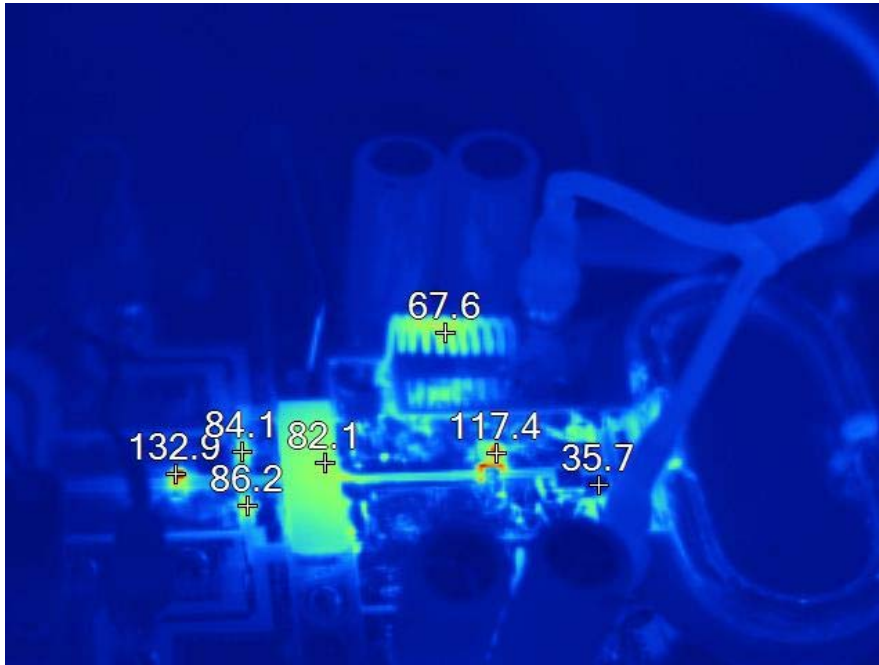

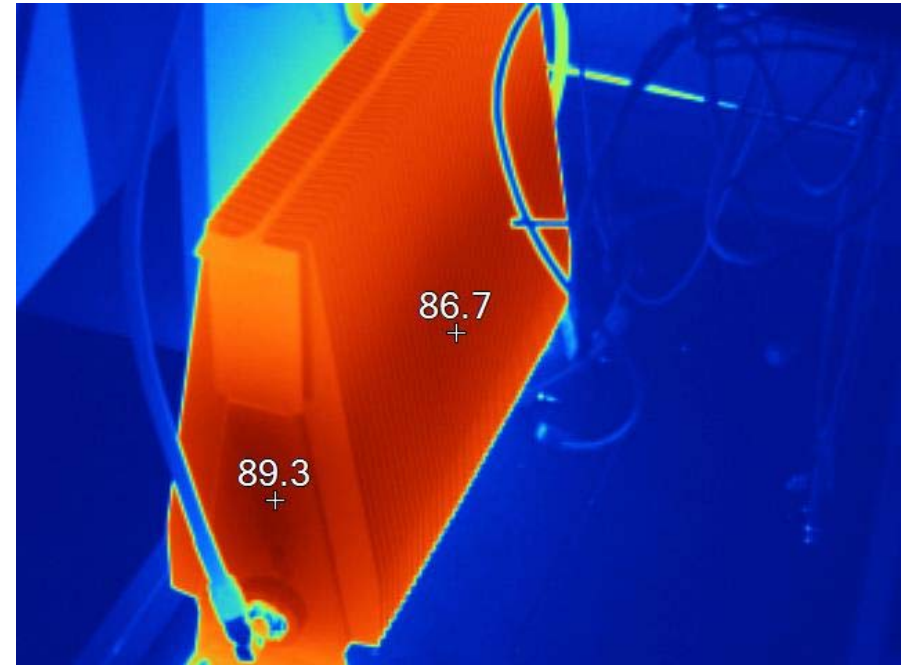INFRARED SCAN OF BOARD AFTER FIFTEEN
MINUTES OF OPERATION AT $\approx 1.7\text{Kw}$



INFRARED SCAN OF 2kW RF LOAD



- Electro-thermal equilibrium reached after ten minutes of operation
- Transistor flange temperature reached 98°C , below the manufacturer recommended maximum of 150°C
- Passive components need better cooling



352-MHz/2kW Amplifier Performance – A. Goel

Version 2 - Replication

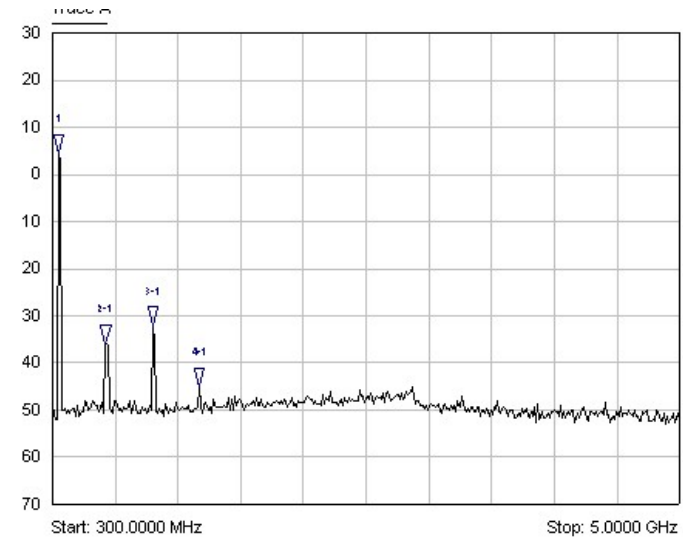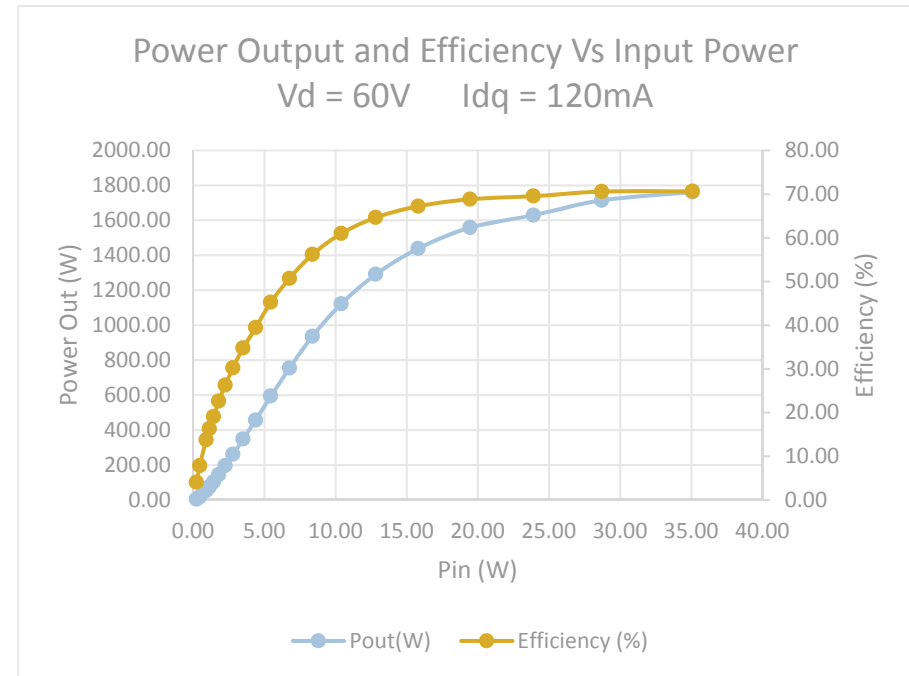
- Identical electrical design was replicated with slight modifications to the cold plate and carrier
- 1.76kW produced at first turn on -- *no tuning needed*
- All performance parameters closely matched the first prototype
- Hand made components (balun and bias filter inductors) may be the cause of performance variations




Thermal Challenges

- Operation at 60 volts and 2kW rf power will require enhanced cooling to prevent premature failure of transistor and passive components
- Several cooling strategies are being considered:

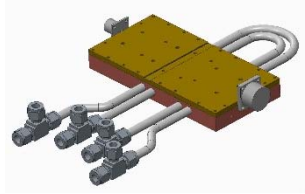
→ *Conventional copper cold plate + copper carrier:*



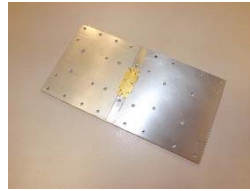→ *Conventional copper cold plate + heat spreader:*



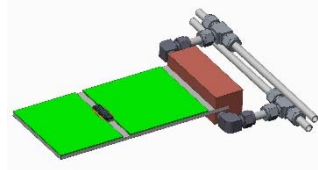→ *Conventional copper cold plate + vapor chamber:*




- Tests are underway to determine the most practical solution




Thermal Tests -- Copper Carrier and Euclid Heat Spreader on Water-Cooled Cold Plate – D. Bromberek

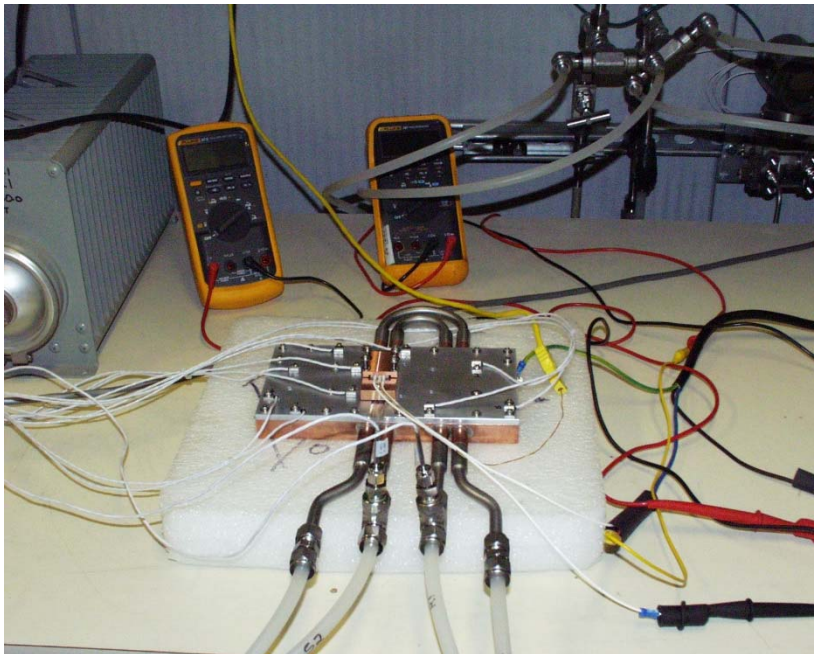500-WATT CERAMIC HEATER AND SPREADER BLOCK TO SIMULATE TRANSISTOR THERMAL FOOTPRINT



EUCLID ALUMINUM HEAT SPREADER

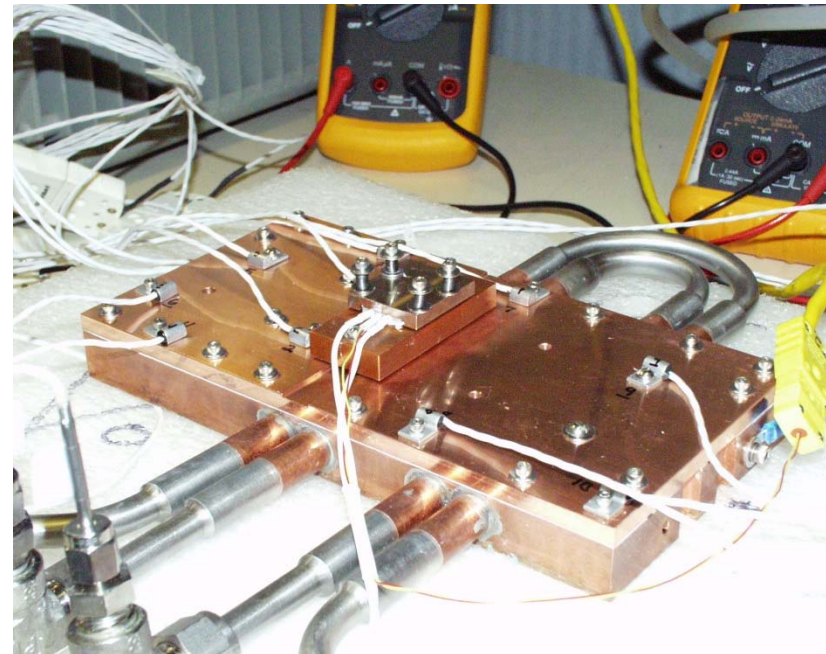Euclid TechLabs LLC -- Dr. Chunguang Jing,
Vice President for Engineering




COPPER CARRIER



Thermal Tests -- *Copper Carrier and Euclid Heat Spreader on Water-Cooled Cold Plate* – D. Bromberek


RTD MEASUREMENT LOCATIONS

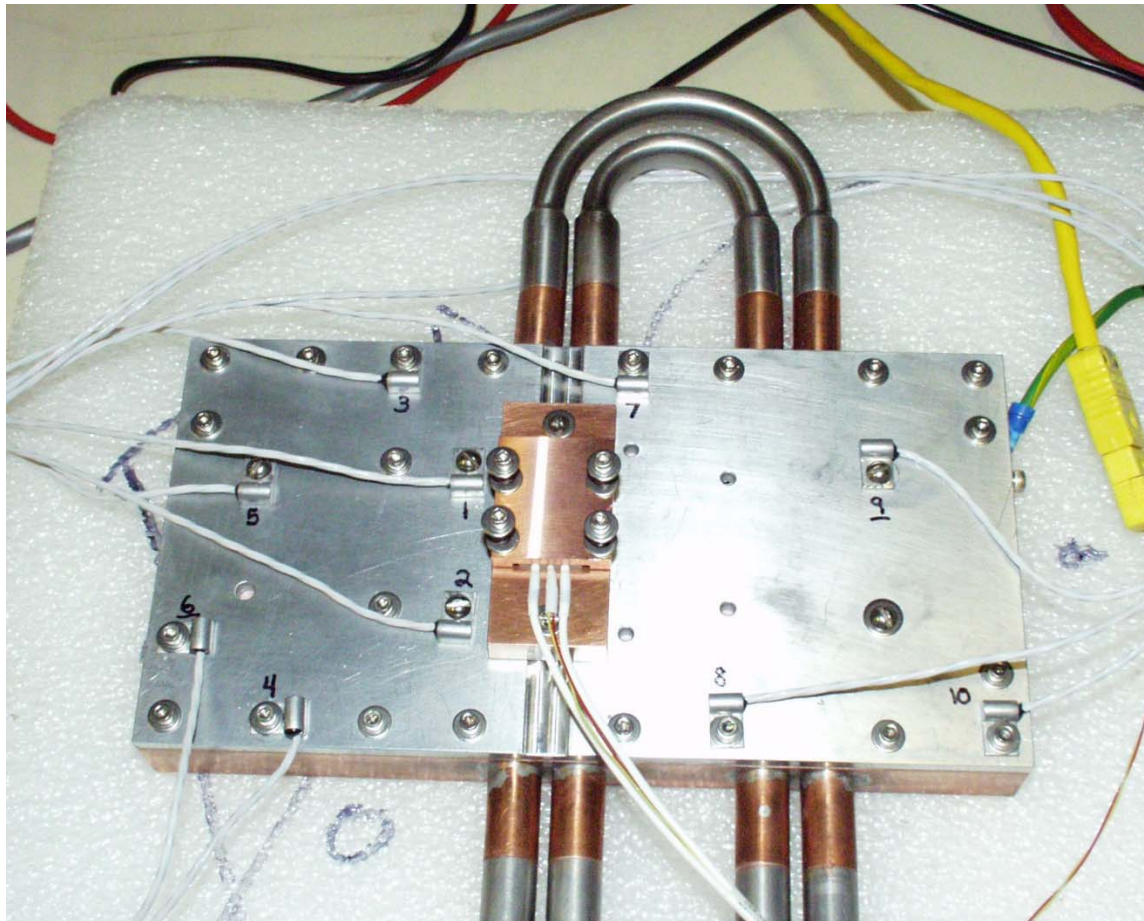

Thermal Tests -- Copper Carrier and Euclid Heat Spreader on Water-Cooled Cold Plate – D. Bromberek



500-WATT HEATER WITH INTERNAL THERMOCOUPLE AND MOUNTING BLOCK

THERMAL GREASE JOINTS

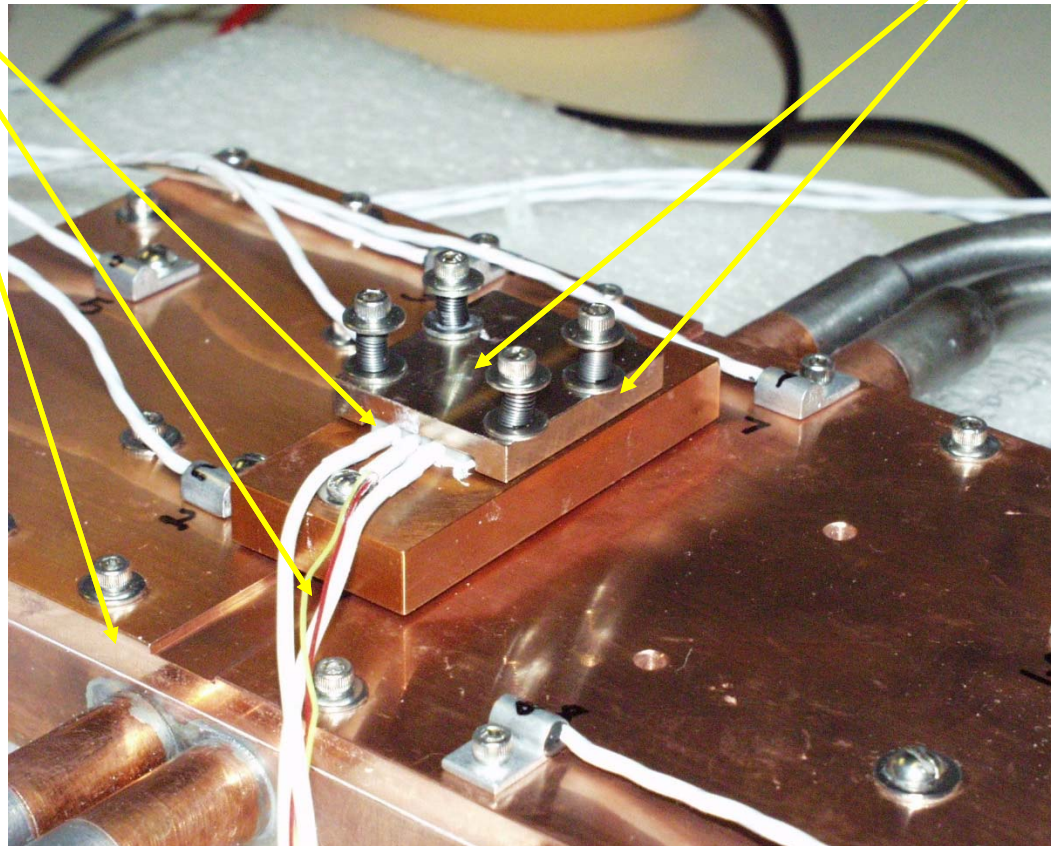


Thermal Tests -- Copper Carrier and Euclid Heat Spreader on Water-Cooled Cold Plate – D. Bromberek

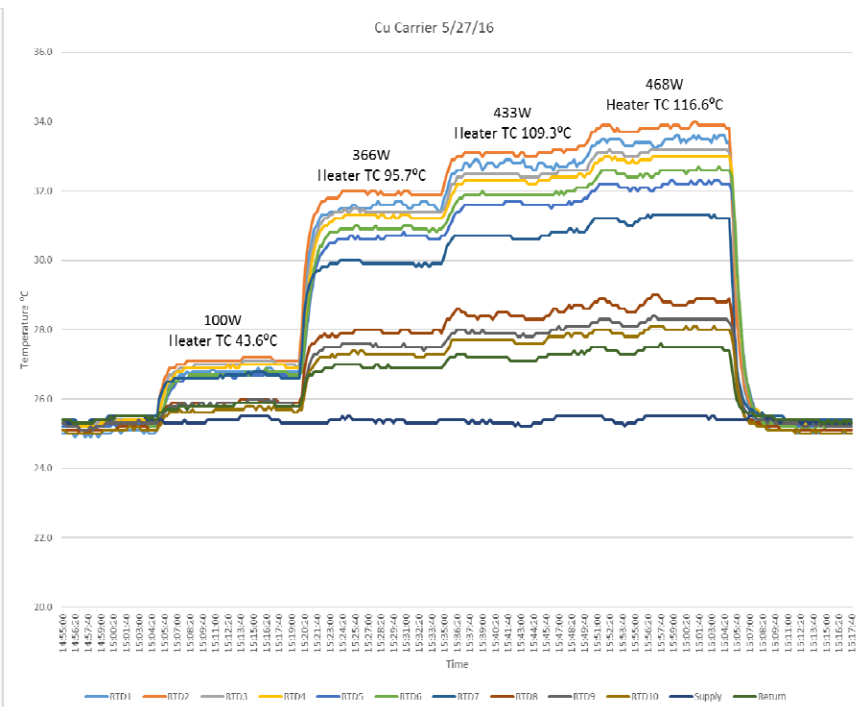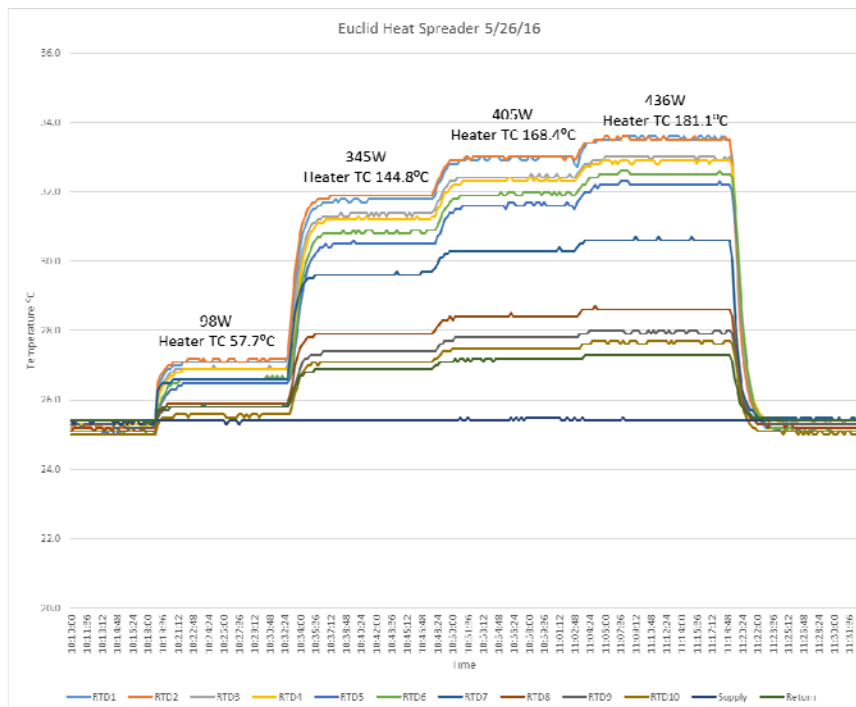- Multiple tests run on both units results very repeatable
- Heater voltage steps of 50, 100, 110, & 115VAC at 15-minute intervals
- Tests limited by thermal grease maximum temp (~200°C) and heater rated voltage
- Copper carrier outperformed Euclid heat spreader due to placement of water channels directly under heat source rather than around perimeter





Thermal Tests -- Copper Carrier and Euclid Heat Spreader on Water-Cooled Cold Plate – D. Bromberek

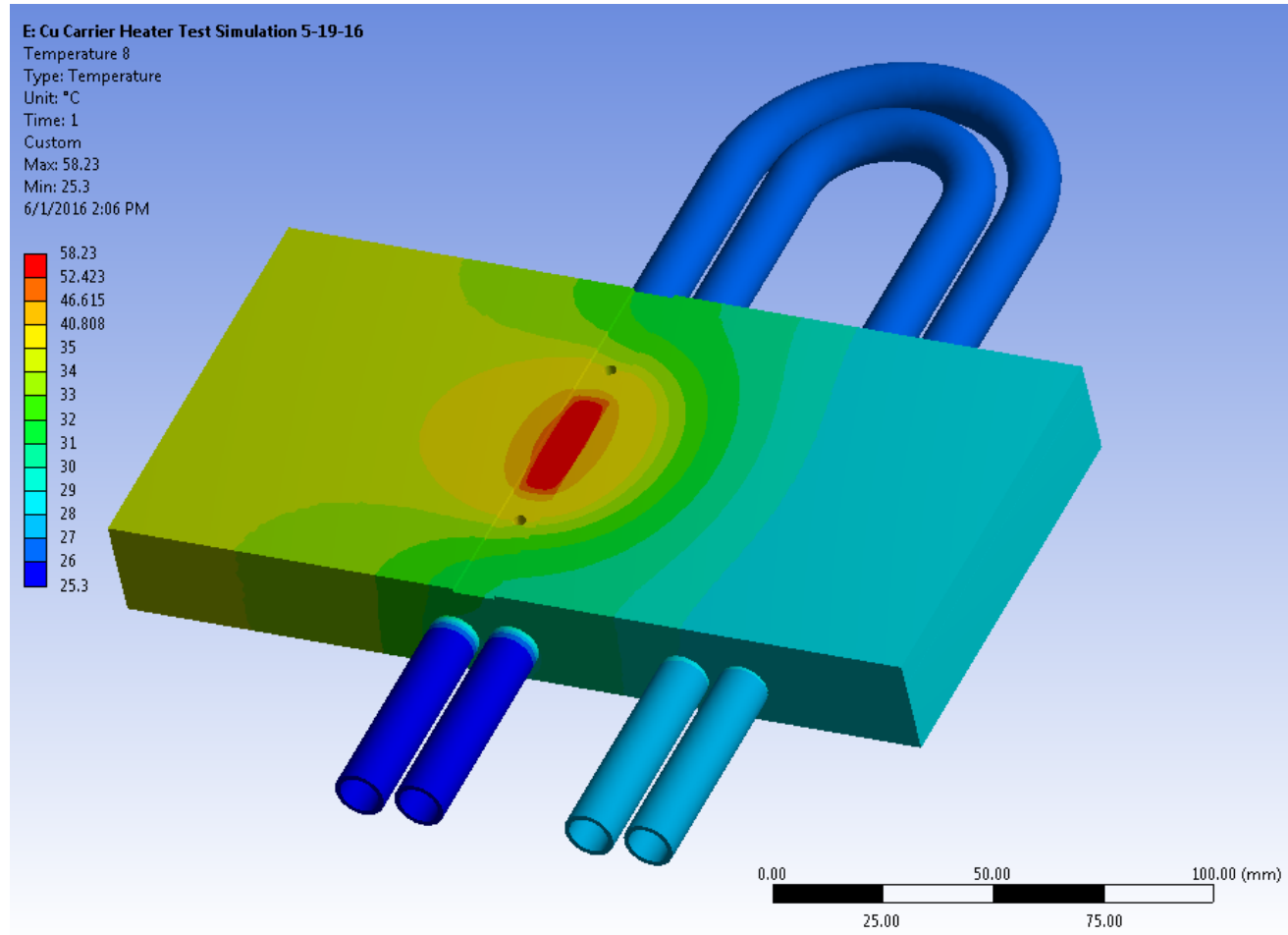ANSYS SIMULATION RESULTS OF HEATER BLOCK TEST CONFIGURATION



Output Cavity Combiner Design -- G. Waldschmidt

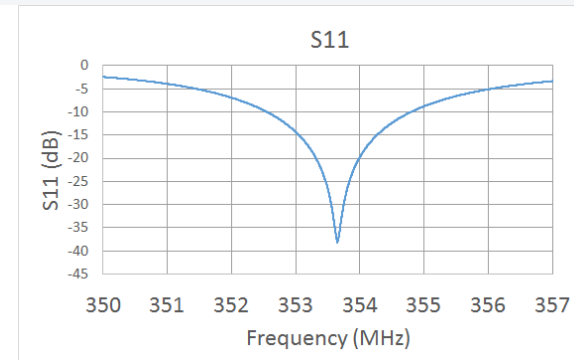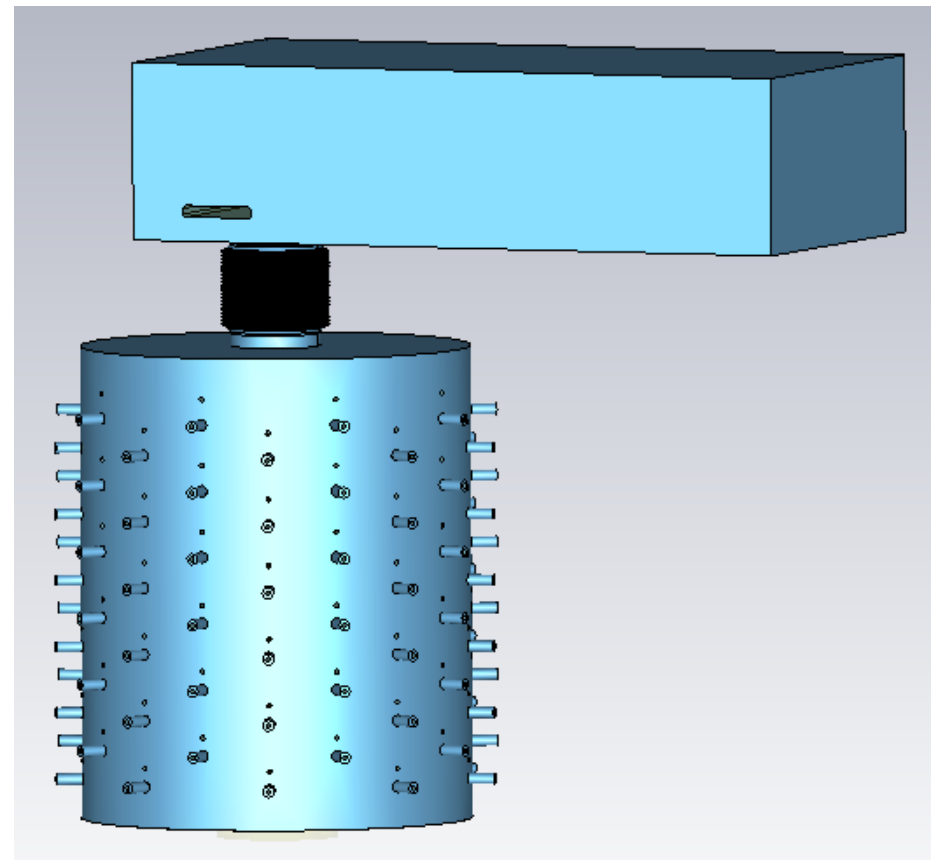- Design for 100 kW minimum
- 108 input ports for solid state amplifier modules – *1.5kW per amplifier nominal*
- Eighteen individual 6-port panels, utilizing rf spring contacts
- Heavily over-coupled output coupler to reduce cavity losses
- Peak fields minimized for high gradient operation
- Single WR2300 full height waveguide output feed




Output Cavity Combiner Design

-- *Thermal and Electrical Simulations at 100kW* -- G. Waldschmidt

- Peak fields (output coupler and tuner) are less than 0.5 MV/m
- T-bar geometry facilitates conductive and convective cooling
- Water cooling of output coupler with conductive cooling of waveguide is planned
- Top and bottom plate will be water cooled
- Tuner cooling is conductive through contact springs
- Remaining geometry is air cooled

THERMAL PROFILE WITH 100kW INPUT POWER

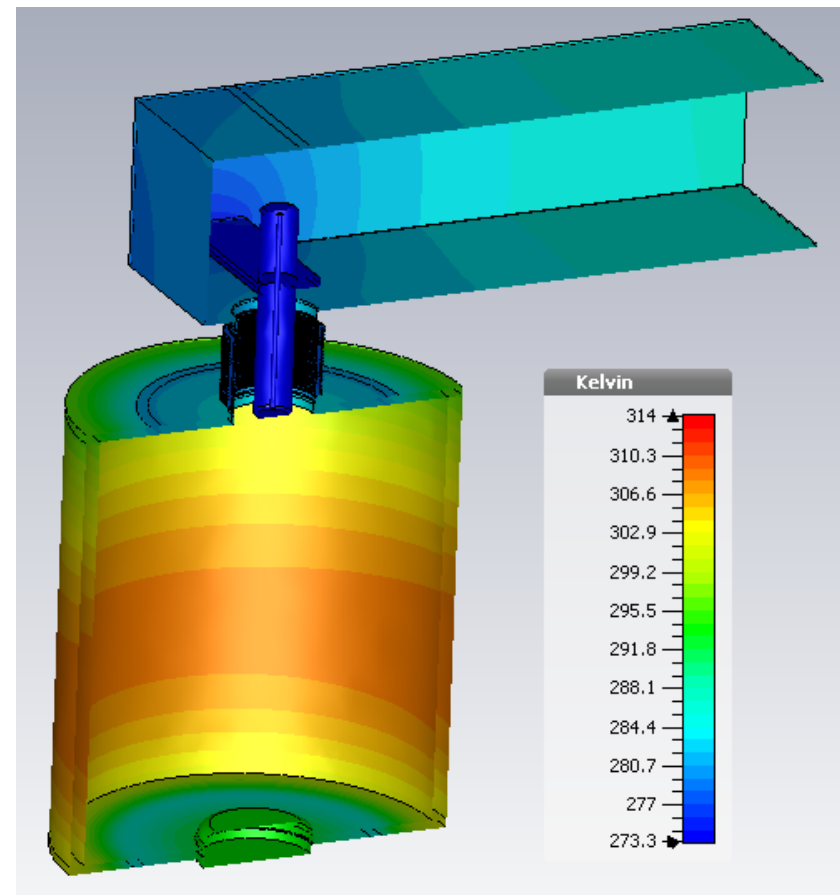

WATER COOLING: T-BAR OUTPUT COUPLER, TOP AND BOTTOM PLATE



FORCED AIR COOLING: CAVITY AND BELLOWS



Output Cavity Combiner Design

-- 6-Port / 12kW Prototype – G. Waldschmidt

- 12kW prototype is based on full cavity combiner design, with one 6-port panel populated with input connectors and coupling loops
- Six 2kW amplifiers will be used
- Cavity built from aluminum with silver plating
- Output coupler bellows is adjustable to accommodate additional amplifiers
- Tuner has $\pm 3\text{MHz}$ tuning range
- Input couplers are tunable with a sliding cross member fitted with fingerstock rf contacts

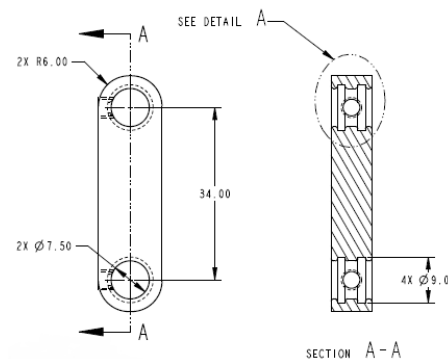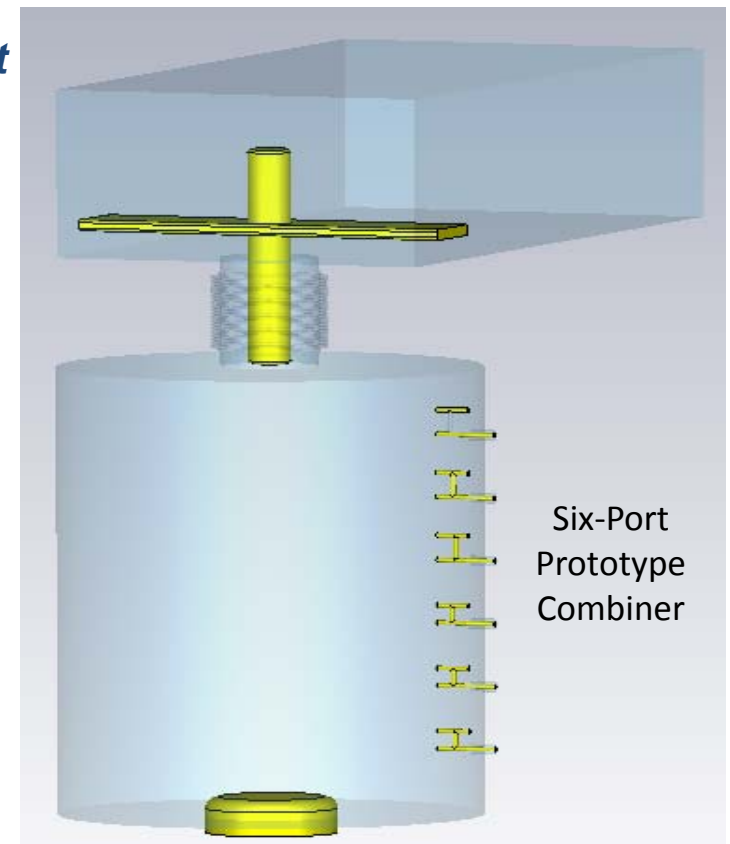


Adjustable input coupling



Output Cavity Combiner Design


-- Waveguide Transition Tuning – G. Waldschmidt

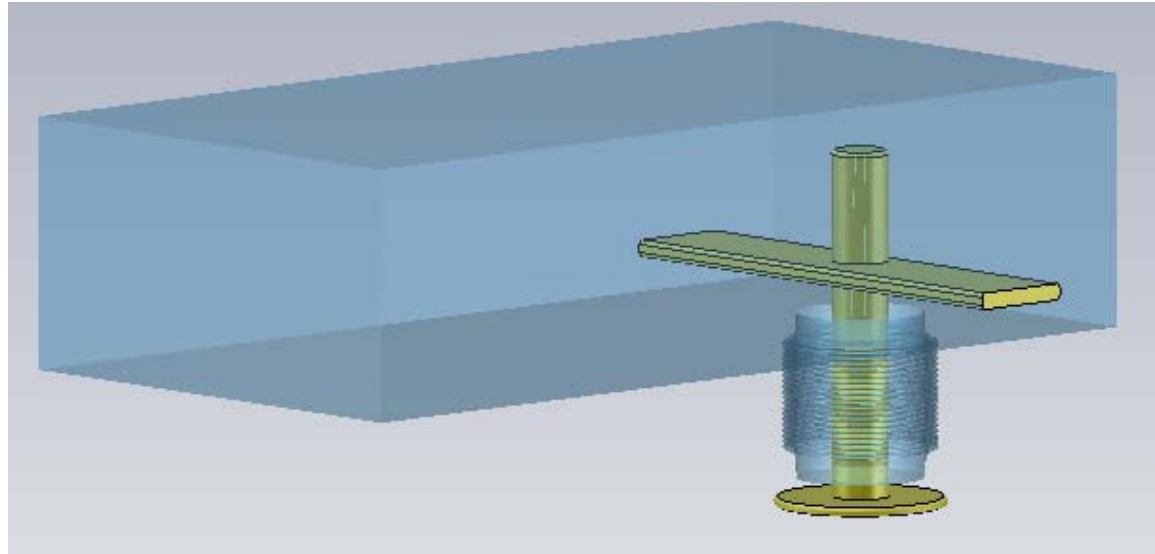- T-bar waveguide transition designed as matching element for waveguide
- Permits internal cooling of output coupler and facilitates higher power handling
- Allows flexibility for number of amplifier feeds



Algorithm for sequential input coupler tuning of prototype cavity algorithm:

$$\Gamma_m := \frac{-(m-2) - N}{m+N}$$

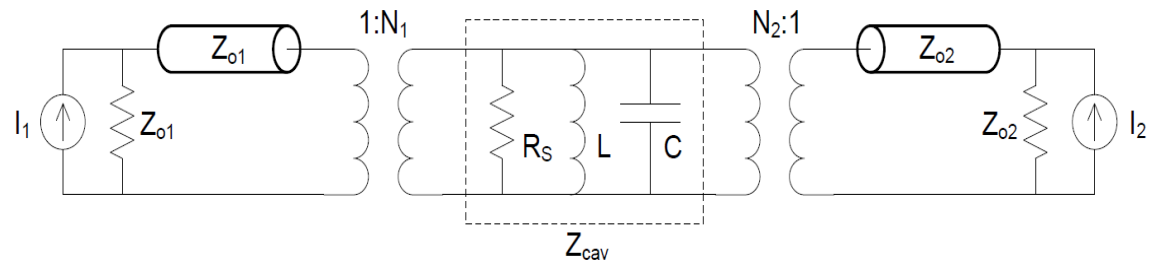

Critically matched response:

$$\Gamma := \frac{1-N}{N}$$

$$\beta := \frac{1}{2 \cdot N - 1}$$




Output Cavity Combiner Design


-- Other-Order Modes – G. Waldschmidt

- Input couplers couple to other cavity modes that are within amplifier bandwidth
- Multiple input couplers may tend to cancel fields due to opposite circulation of magnetic flux
- Field non-uniformity is compensated at 352 MHz, but not at other modes so cancellation is not complete
- Bandpass filter is being considered

FREQUENCY RESPONSE AT OUTPUT COUPLER



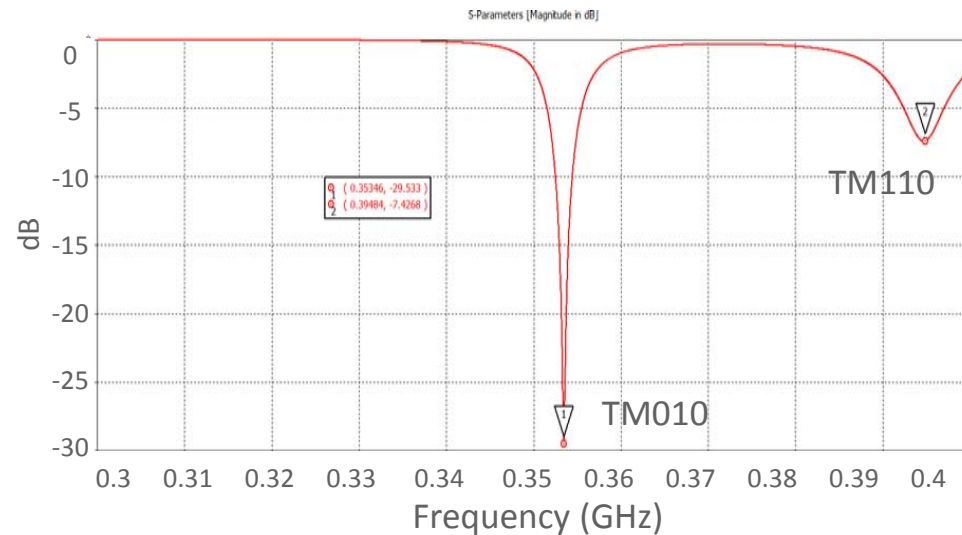


FREQUENCY RESPONSE AT INPUT COUPLERS

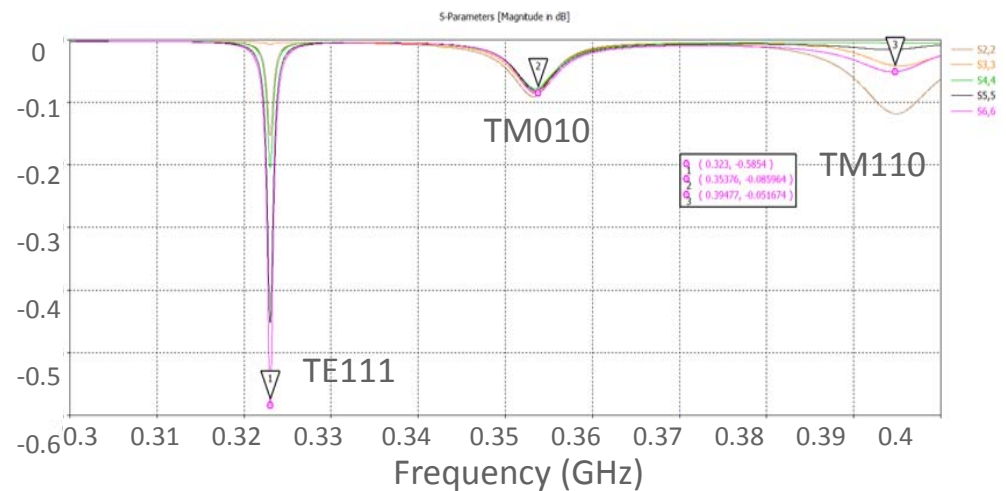

Output Cavity Combiner Design


-- CAD Figures

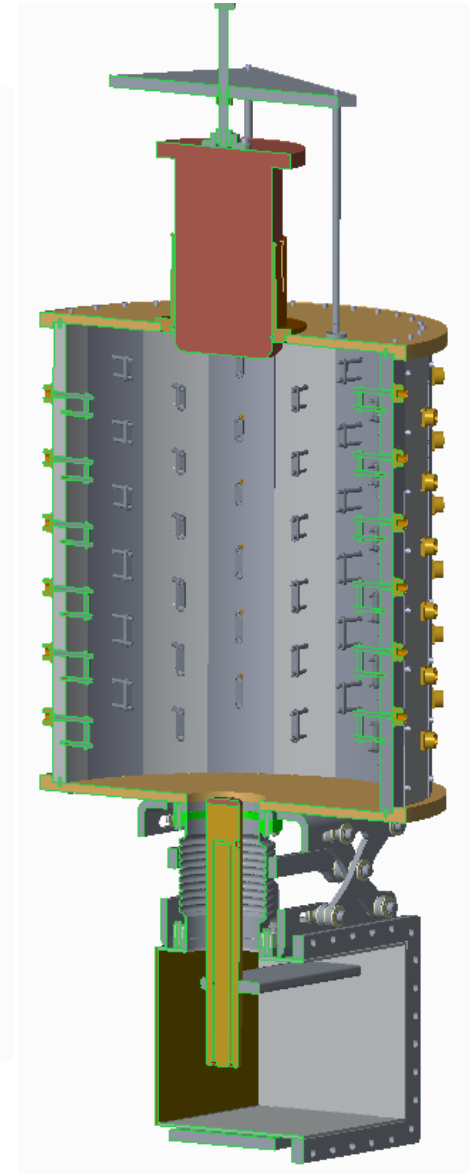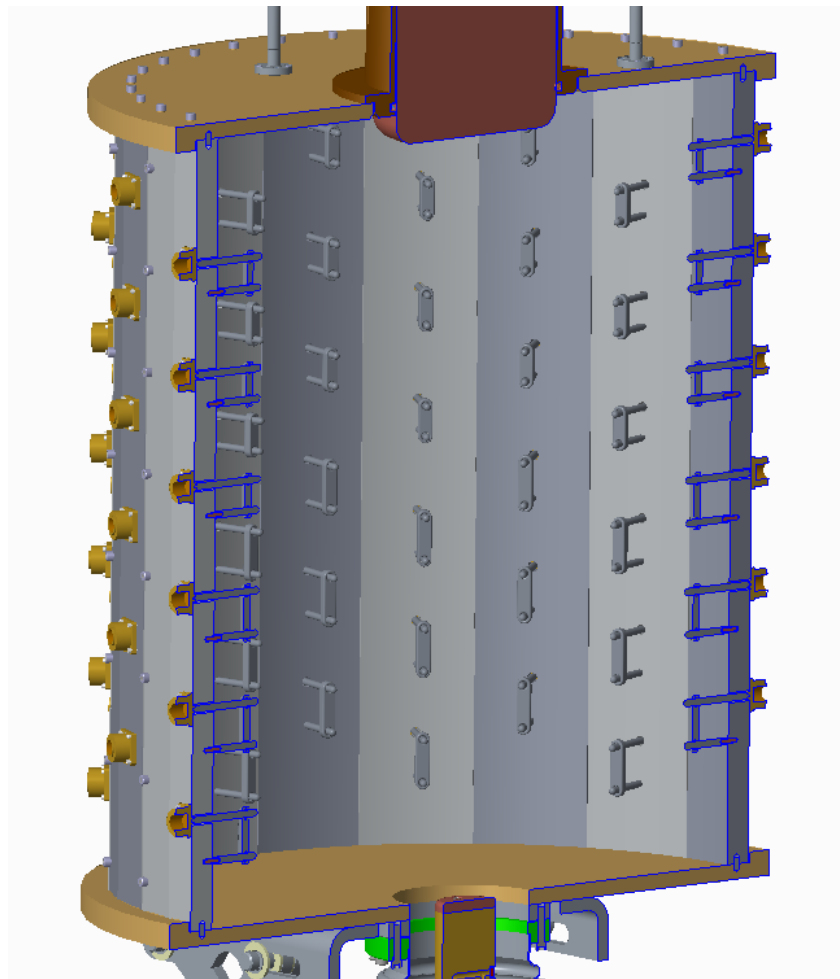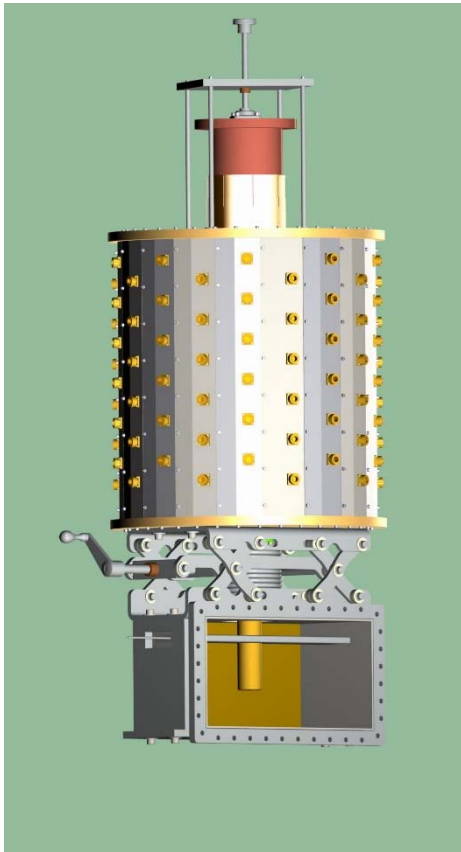

Nanobonding – K. Suthar

-- *An Alternative to Soldering?*

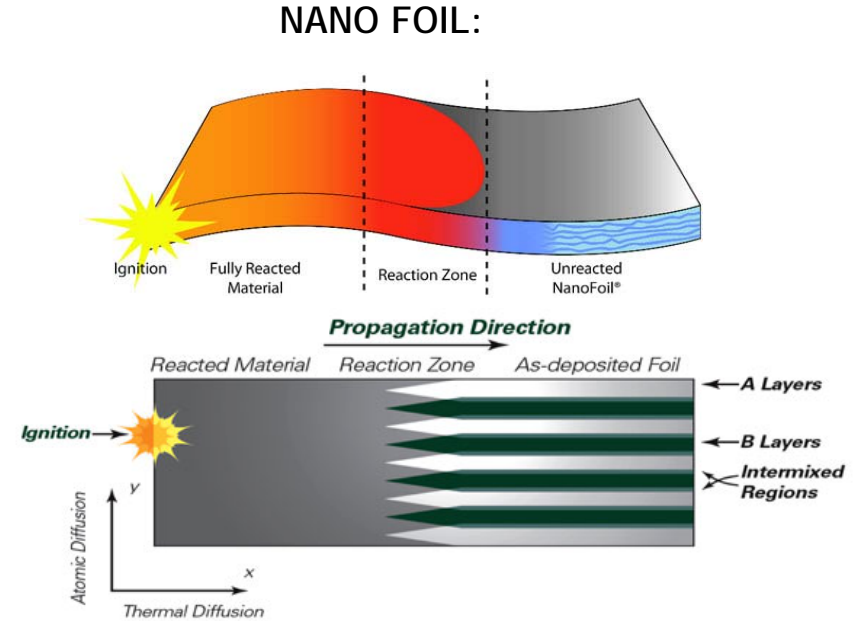- Nanobonding: High-temperature exothermic reaction between nickel and aluminum in foil, triggered by electron flow
- Tin coating on foil melts during the reaction and bonds mating surfaces
- Exploring as an alternative to soldering for transistor package and circuit board



**NANOBONDING OF TIN-COATED
COPPER SLABS**




**NANOBONDING OF SiC TO
COPPER SLAB**



Nanobonding -- K. Suthar

-- An Alternative to Soldering?

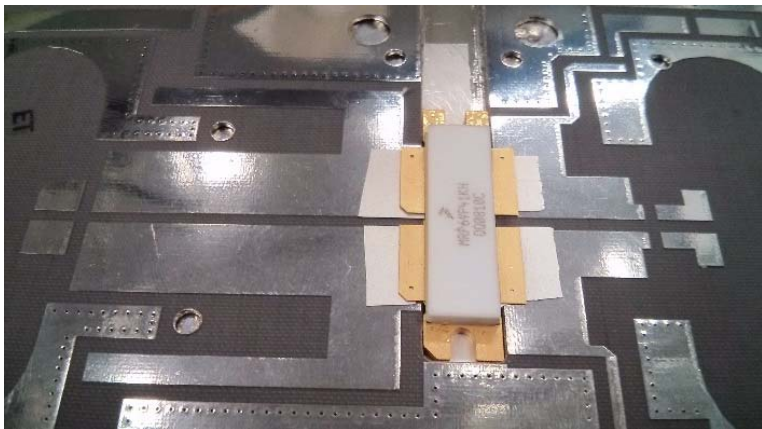- Exploring as an alternative to soldering for transistor package and circuit board:



- Thermal and electrical compatibility tests underway




352-MHz Solid State -- Summary

- 12kW demonstration system will be assembled and tested in 2017



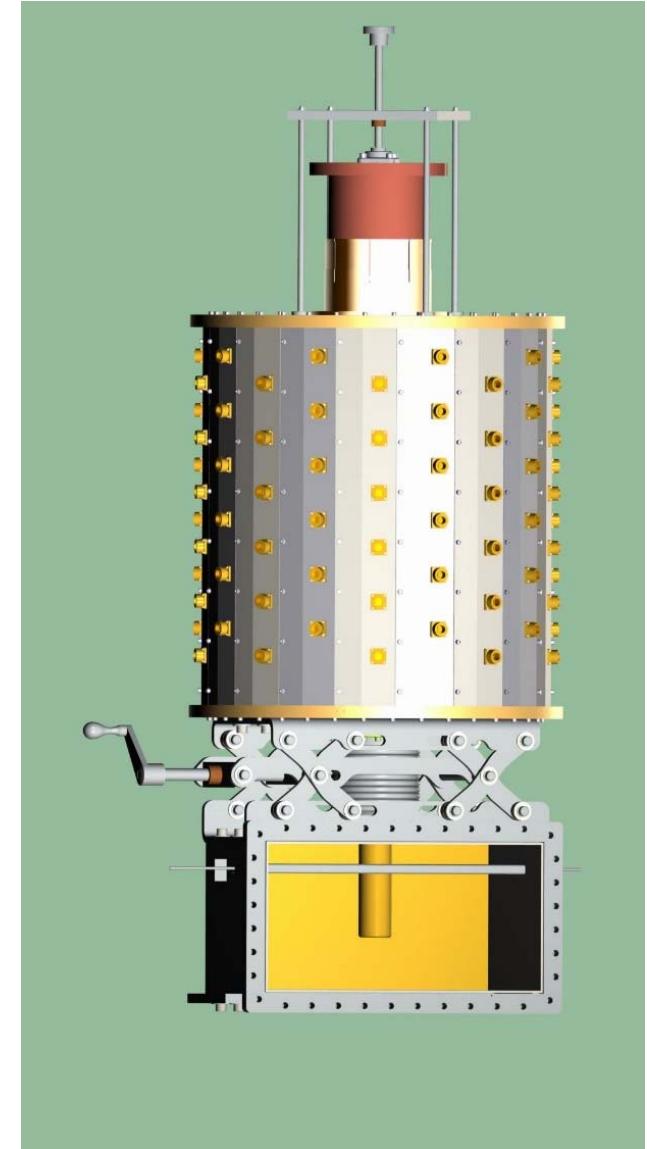- Performance data will be used to implement design changes necessary to increase reliable output power to 100+ kW



- 
- And now.....

Notable Failures!

RF1 Matching Transformer Fire

-- December 20, 2015

- 2.5MVA transformer steps down 13.2kV to 1,400 volts for thyristors in HVPS
- End-of-life insulation failure resulted in sustained arcing that progressed into a major fire
- Transformer and enclosure destroyed
- Replaced transformer with spare on hand, but had to emergency-order new enclosure
- Total repair time \approx five weeks



Output Window Arcing on Thales TH2089A Klystron



- Damage detected during visual inspection at maintenance shutdown:
Burned screw seen on output transition
- Further investigation revealed arcing damage to output center conductor
- Repair will be attempted

