

# Development of Superconducting TDC/ADC/ALU and Neutron Detectors

Ali Bozbey

TOBB University of Economics and Technology  
Department of Electrical and Electronics Engineering  
Superconductivity Electronics Laboratory (ETU SEL)

- Introduction to Superconducting Logic
- Time to Digital Converter
- Analog to Digital Converter
- Superconducting Stripline Detectors  
Towards Megapixel Neutron Imaging
- Arithmetic Logic Unit

- Based on switching of the Josephson Junctions
- They can switch **up to THz frequencies.**
- They have **very low power consumption (~mW).**
- Compatible with the standard design and fabrication tools.
- It is possible to integrate with semiconductor and/or optical devices.
- Circuit complexities of close to 100 000 Josephson junctions have been reported.
- Gates working about 750 GHz clock frequency has been reported.

# ITRS Report

## Emerging Technology Sequence

Emerging  
Technology  
Vectors

Architecture

Cellular  
array

Defect  
tolerant

Biologically  
inspired

Quantum  
computing

RSFQ

1-D  
structures

Resonant  
tunneling

SET

Molecular

QCA

Spin  
transistor

Logic

Phase change

Floating body  
DRAM

Nano  
FG

SET

Insulator  
resistance  
change

Molecular

Memory

Transport  
enhanced  
FETs

UTB single  
gate FET

Source/Drain  
engineered  
FET


UTB multiple  
gate FET

Quasi  
ballistic  
FET

Non-  
classical  
CMOS

Risk

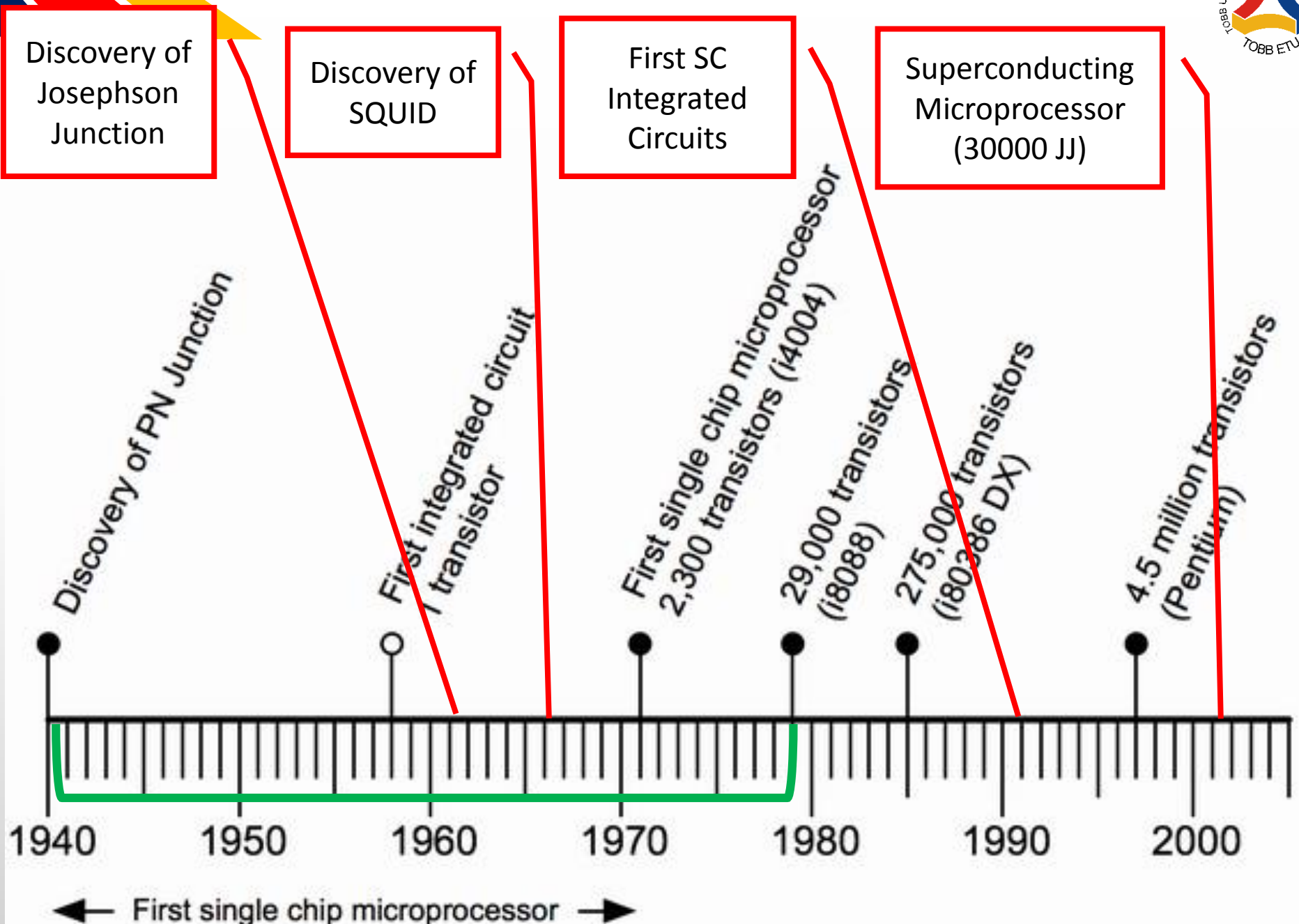ITRS: The International Technology Roadmap for Semiconductors



Discovery of Josephson Junction


Discovery of SQUID

First SC Integrated Circuits

Superconducting Microprocessor (30000 JJ)

← First single chip microprocessor →


# Generation of the SFQ Pulse

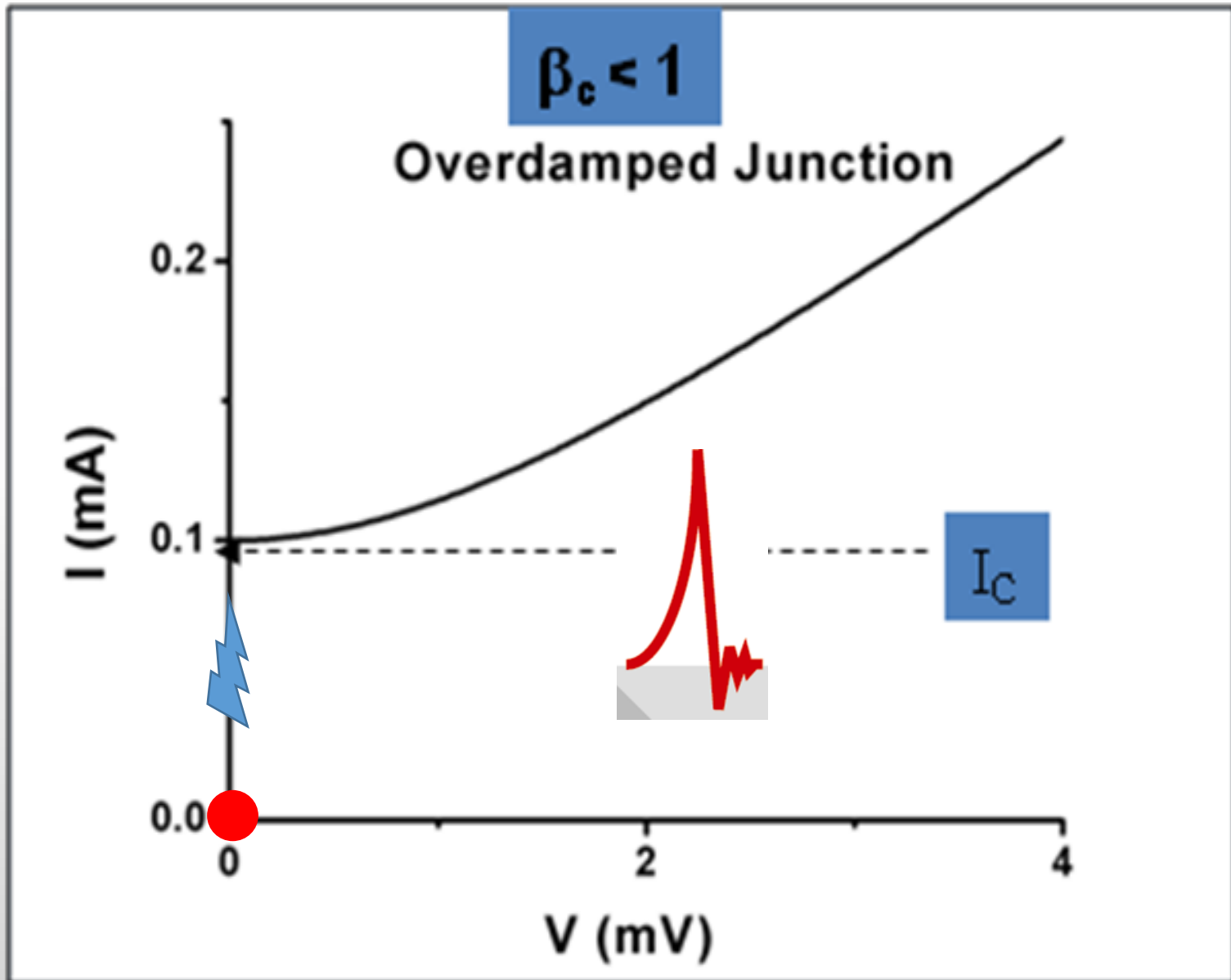

# RSFQ Circuit Samples

- Josephson Transmission Lines (JTL)
- SFQ Splitters
- SFQ Mergers
- Gates: AND, OR, NOT ...
- Flip-Flops
- DC/SFQ and SFQ/DC converters
- Passive Transmission Lines (PTL)

# Josephson Transmission Lines (JTL)

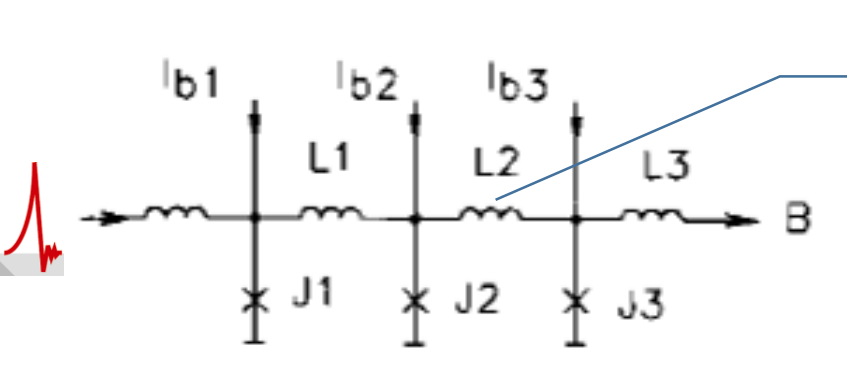

L1, L2, L3; should be small enough in order not to allow magnetic flux storage.  
( $I_c L \sim 0.5 \Phi_0$ )


0

10


- Interconnection of the logic gates and adjusting the timing of the circuits.
- $I_b = 0.75 I_c$
- SFQ pulse from input A propagates by switching the junctions J1, J2, J3 respectively and escapes from output B.
- Advantages: recovery of SFQ pulse during propagation
- Disadvantages: time delay, jitter, number of Josephson junctions







# SFQ Splitter

 



 
- Splitters are used to increase the fan-out of the logic circuits.
- Similar principle of operation with JTL. Critical currents of the junctions should be chosen properly. ( $I_{c1}=1.4I_{c2}=1.4I_{c3}$ )
- Hence, the SFQ pulse arriving from J1 can have enough power to move the J2 and J3 to voltage state.



# RS Flip-Flop

  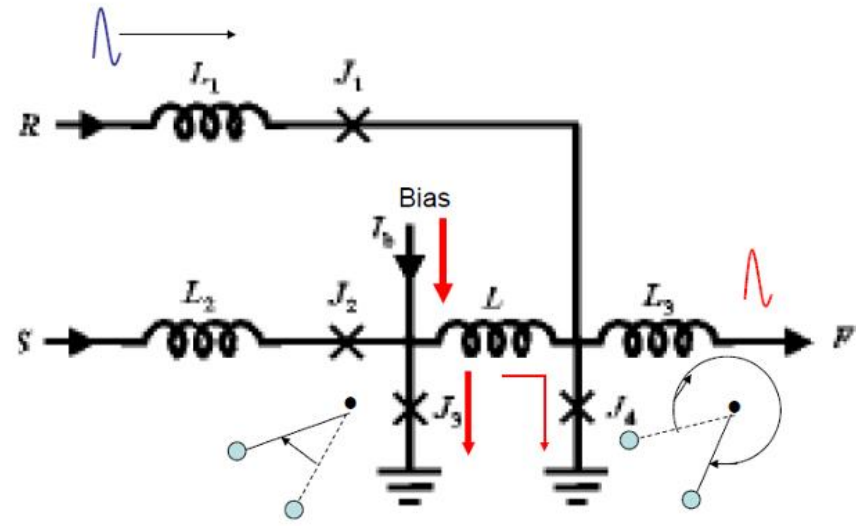 


# Circuit Fabrication (STP)

   


SiO<sub>2</sub> Nb Mo Si

# Design to Testing of Digital and Detector Circuits


## Design

 



Fabrication by  
commercial  
foundries

 

## Packaging

 


## Testing

  

# Measurement Setup




Frequency	Field	Attenuation
14 kHz	Magnetic	60 dB
100 kHz	Magnetic	80 dB
1 MHz	Magnetic	100 dB
1 MHz	Electric	100 dB
100 MHz	Electric	100 dB
100 MHz-10 GHz	Planewave	100 dB
18 GHz	Microwave	100 dB


 


- Time to Digital Converter
- Analog to Digital Converter
- Monolithic Neutron Detector
- Arithmetic Logic Unit


# 1-bit Comparator (QOS)

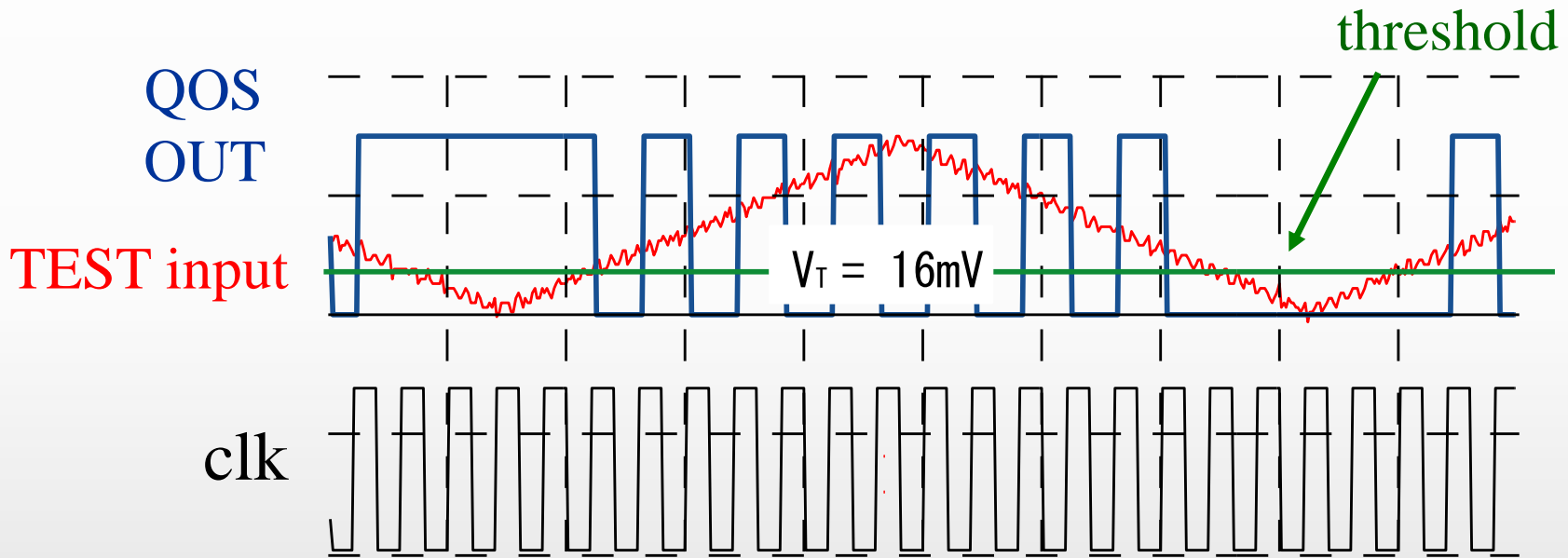


# Comparator Circuits

  

Tasarım 3


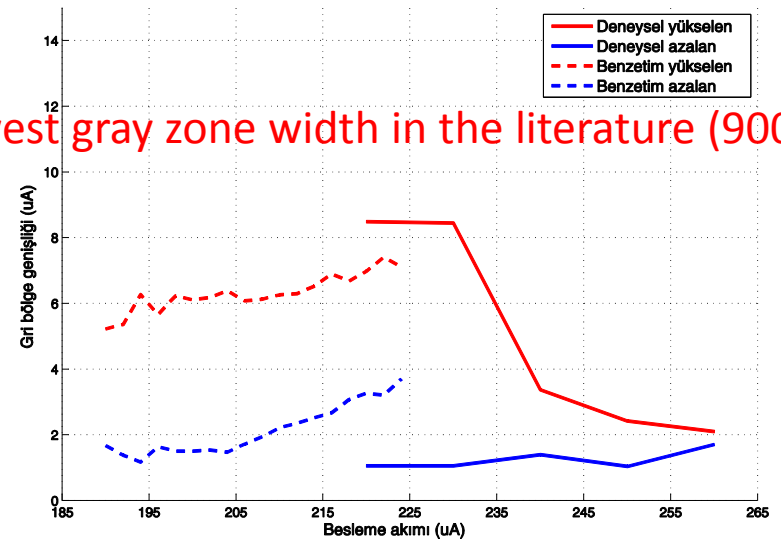


Tasarım 4

 





# Time-to-Digital Converter (Method 1)

 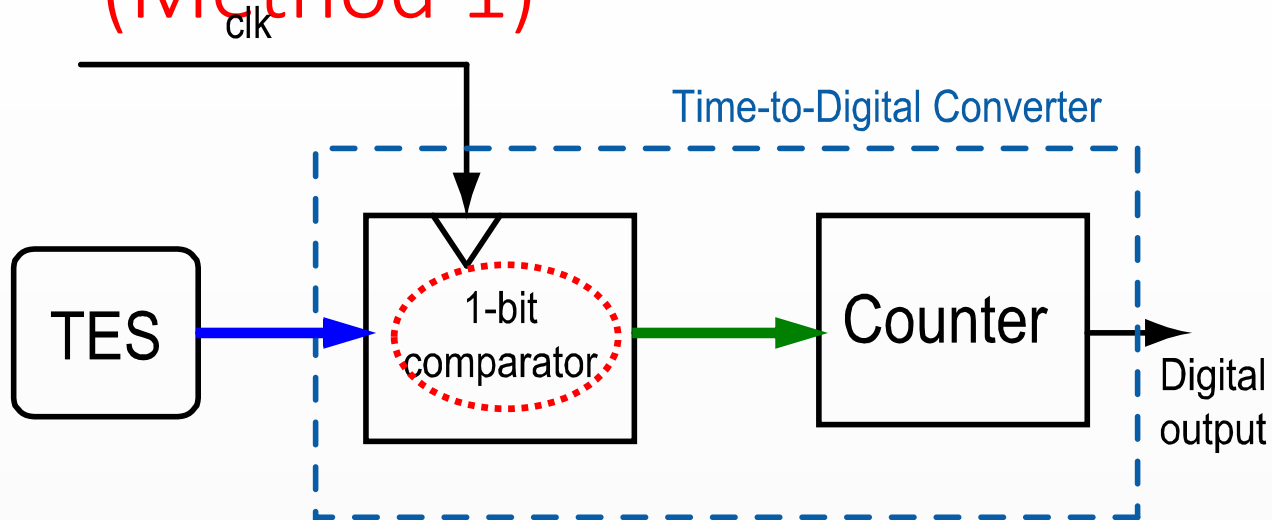

Comparator with high-speed response and high sensitivity

# Time to Digital Converter (Method 2)

  


## Vernier Caliper



# D-Flip Flop




# D Flip-Flop

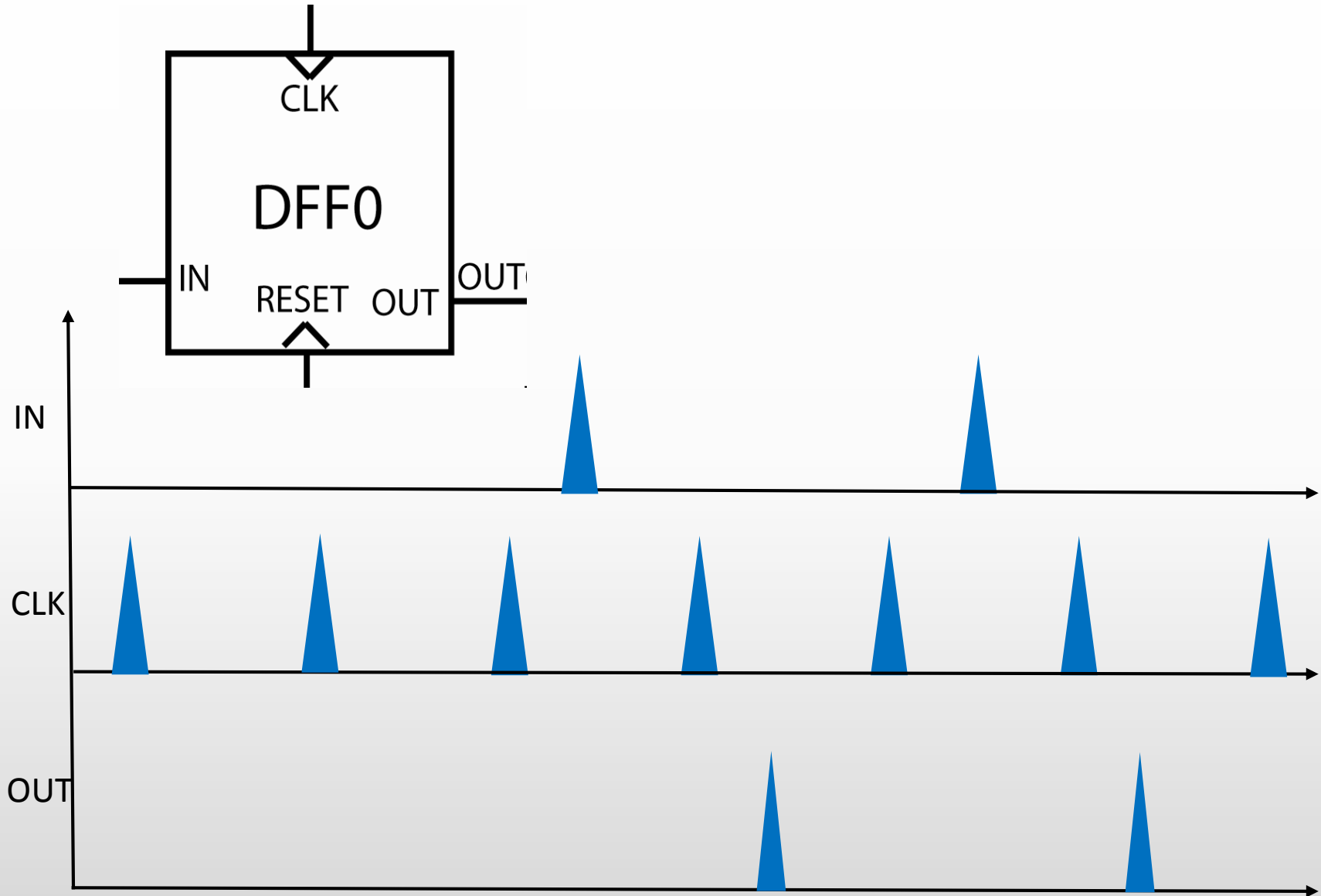


# TDC Block Diagram

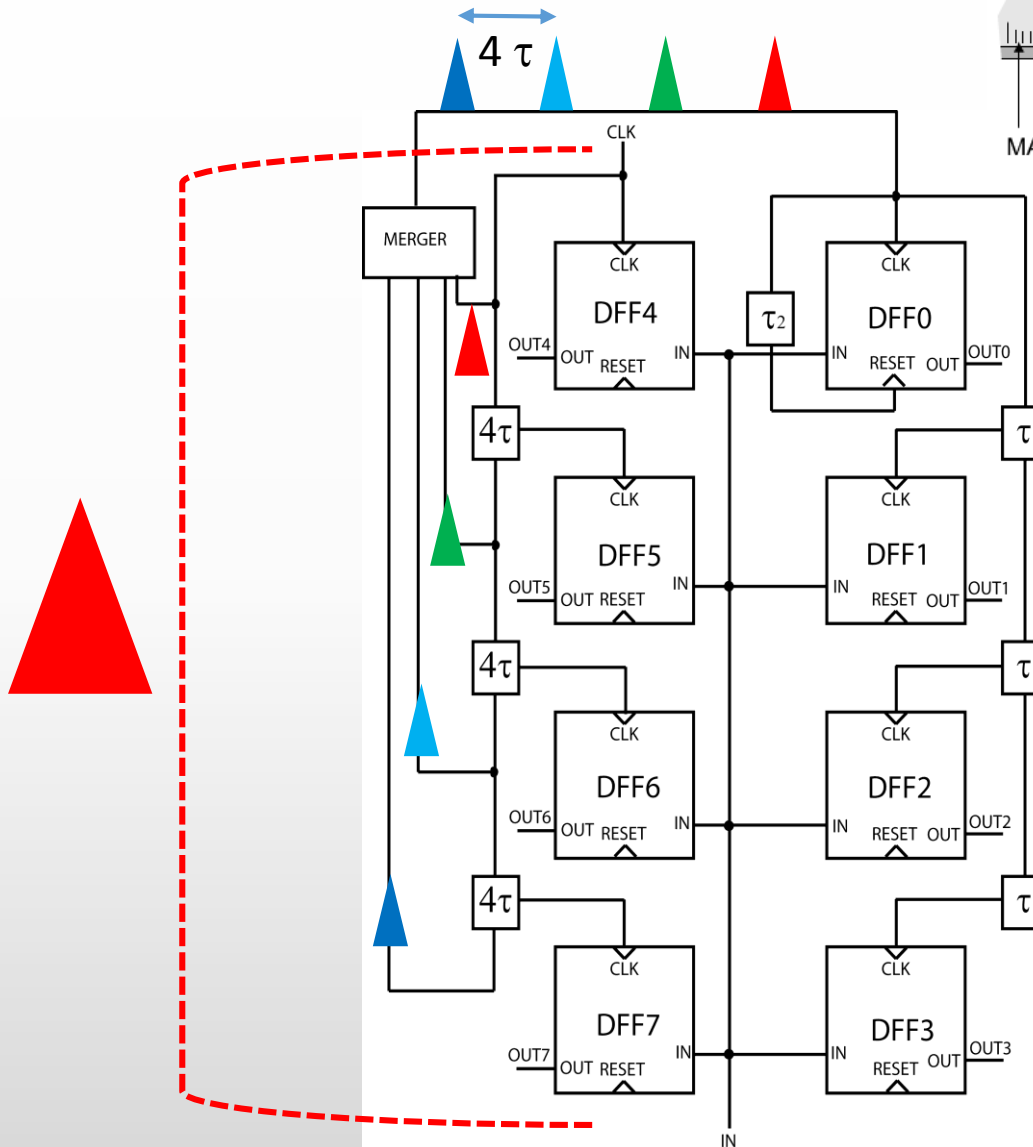 


# TDC Block Diagram

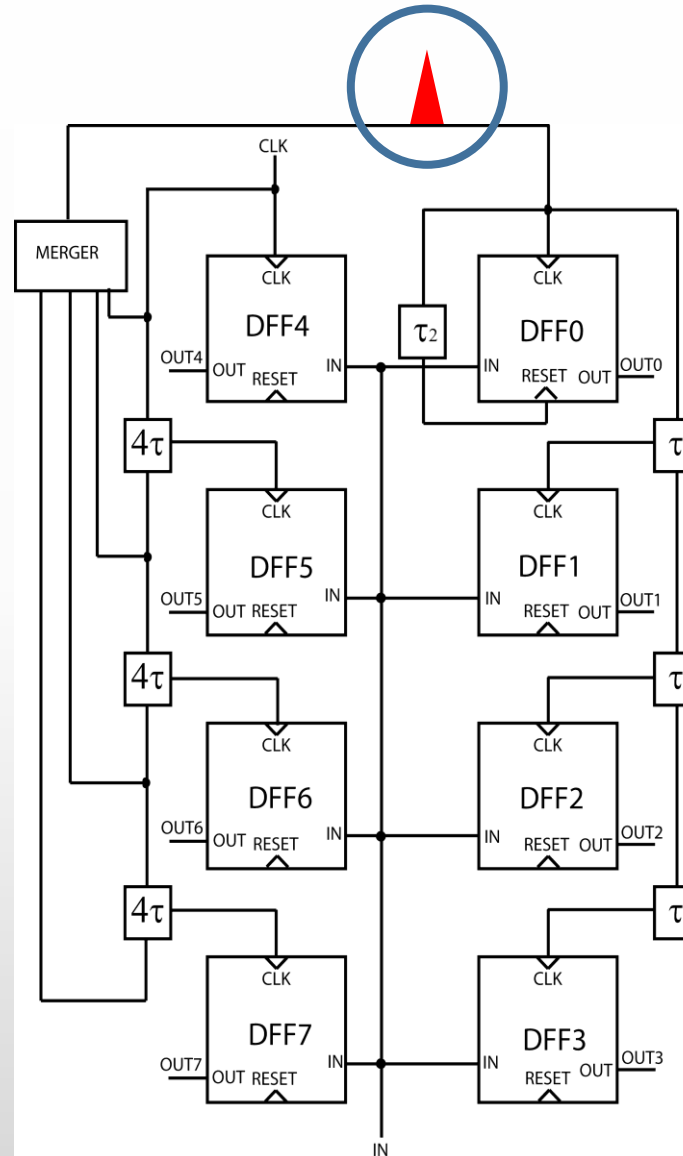

# TDC Block Diagram

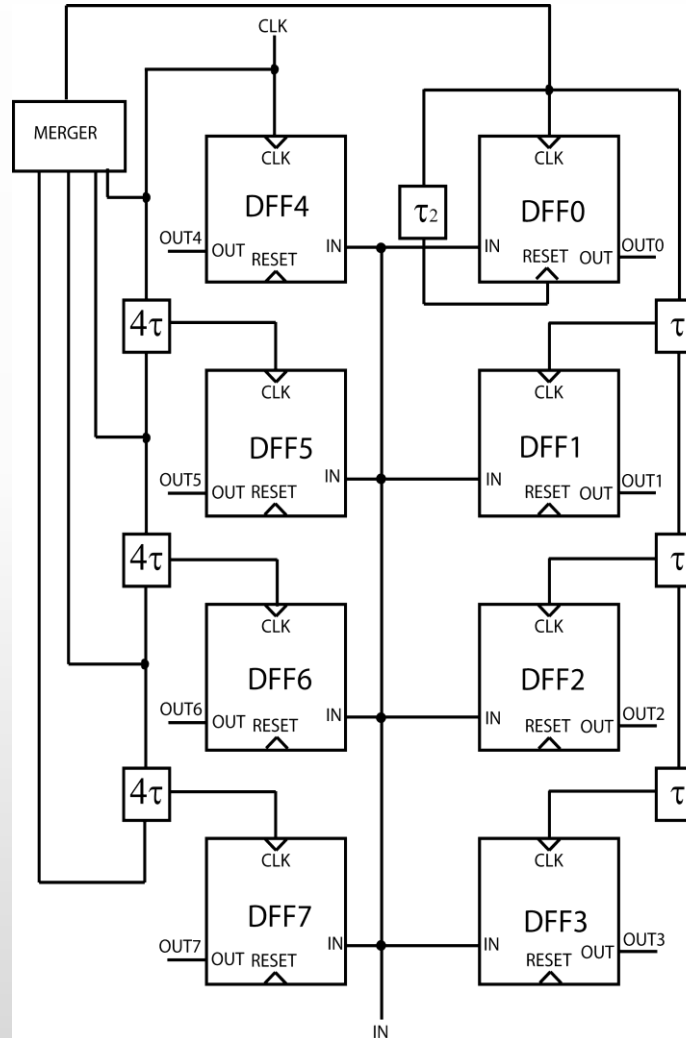


# TDC Block Diagram

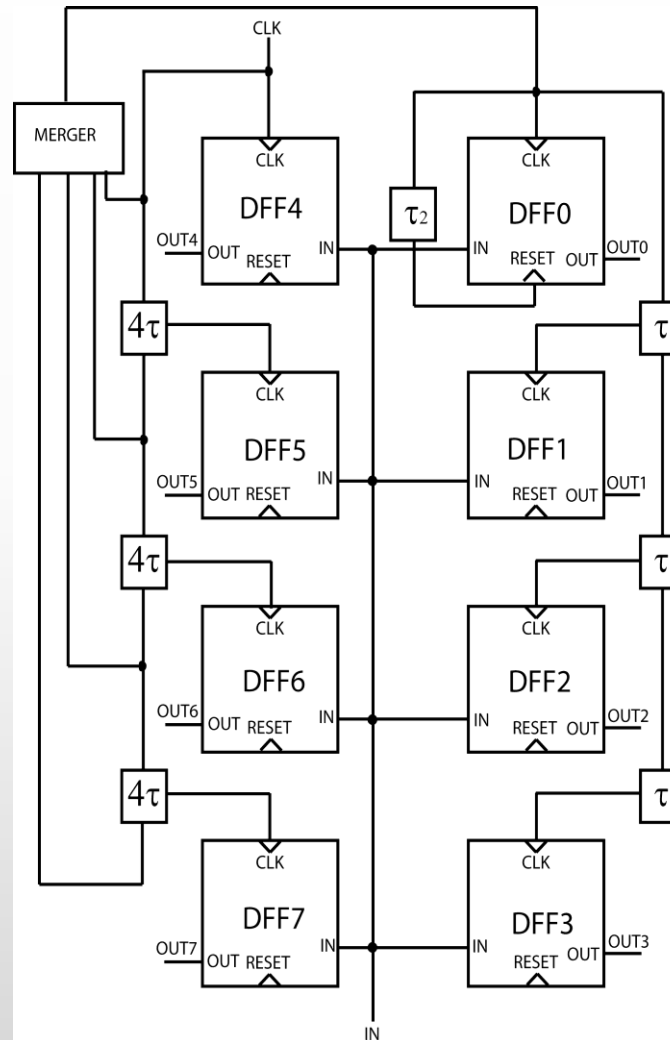






# TDC Block Diagram

 

# TDC Block Diagram

 

# TDC Timing for $\Delta t = 69$ ps

 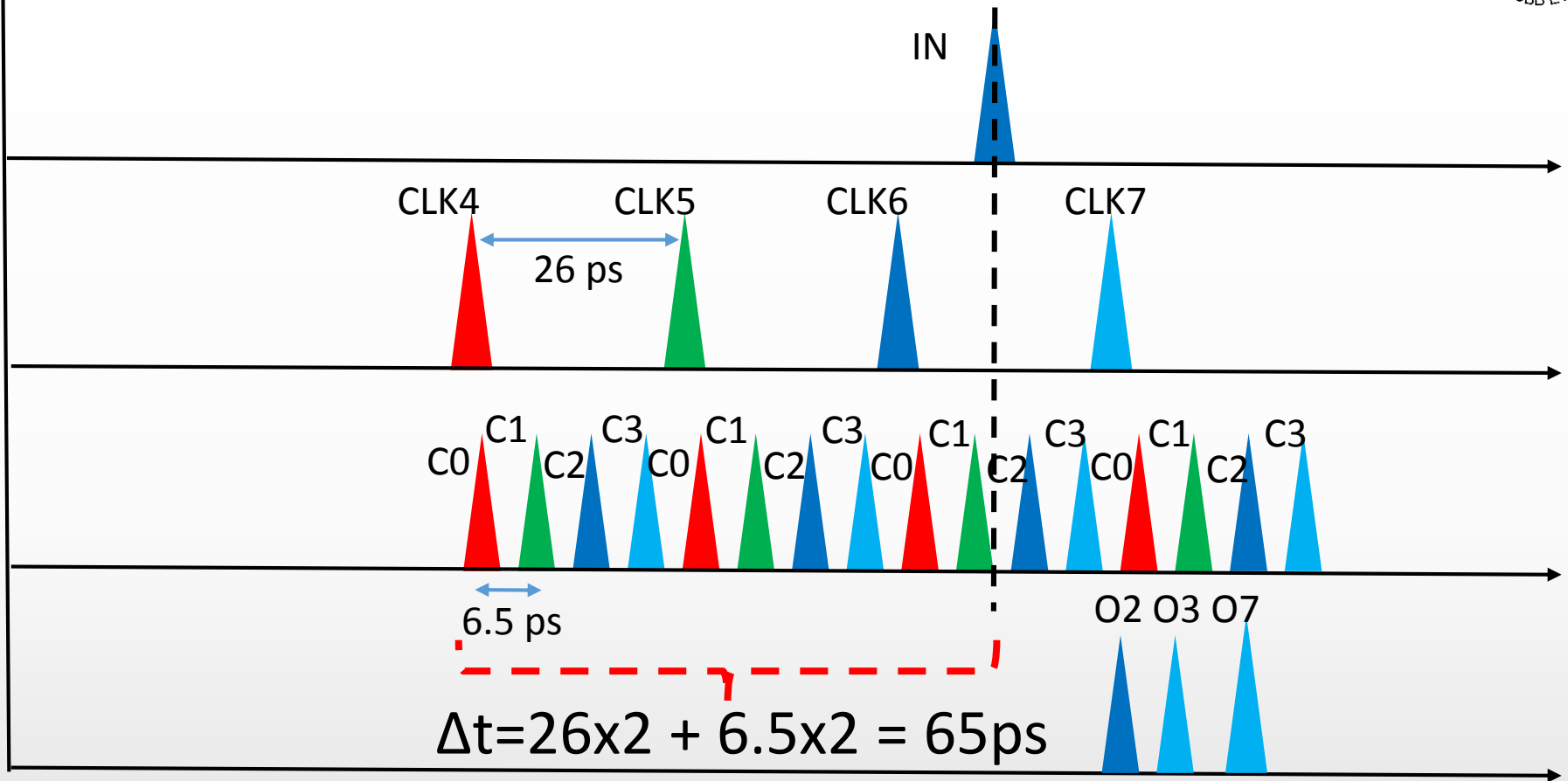


1000 1100  
 07-06-05-04 03-02-01-00

# TDC Decoder Look-up Table


07 – 04	03 – 00	TDC OUTPUT	$\Delta T$ (ps)
0001	0001	0000	0
0001	001X	0001	6.5
0001	01XX	0010	13
0001	1XXX	0011	19.5
001X	0001	0100	26
001X	001X	0101	32.5
001X	01XX	0110	39
001X	1XXX	0111	45.5
01XX	0001	1000	52
01XX	001X	1001	58.5
01XX	01XX	1010	65
01XX	1XXX	1011	71.5
1XXX	0001	1100	78
1XXX	001X	1101	84.5
1XXX	01XX	1110	91
1XXX	1XXX	1111	97.5

# Analog to Digital Converter


# Flash ADC

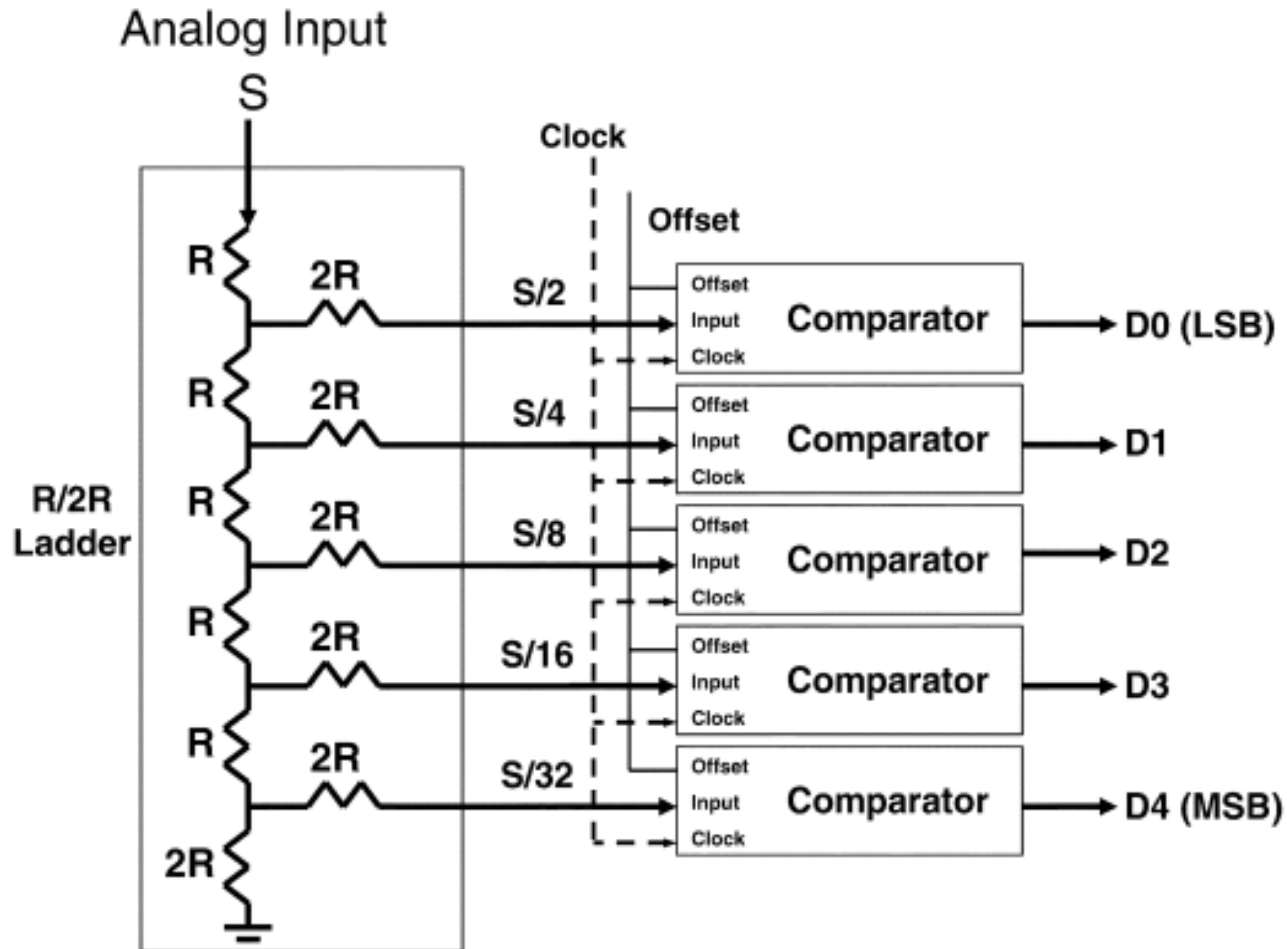


# 1-bit Comparator

 


(a)

 

(b)


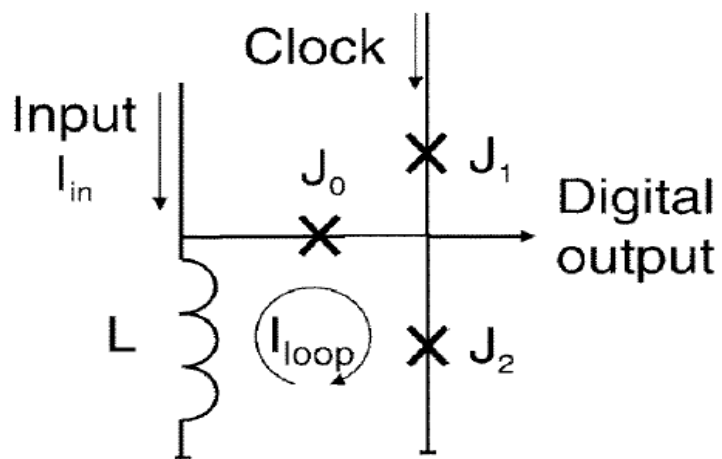


(c)

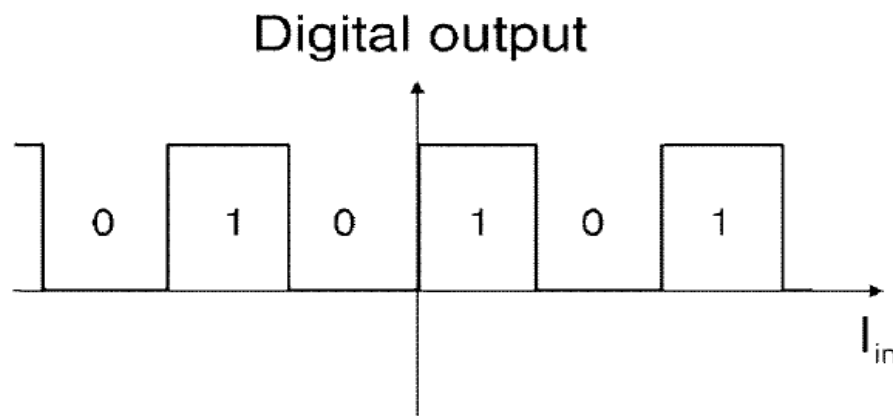


(d)

# Flash ADC

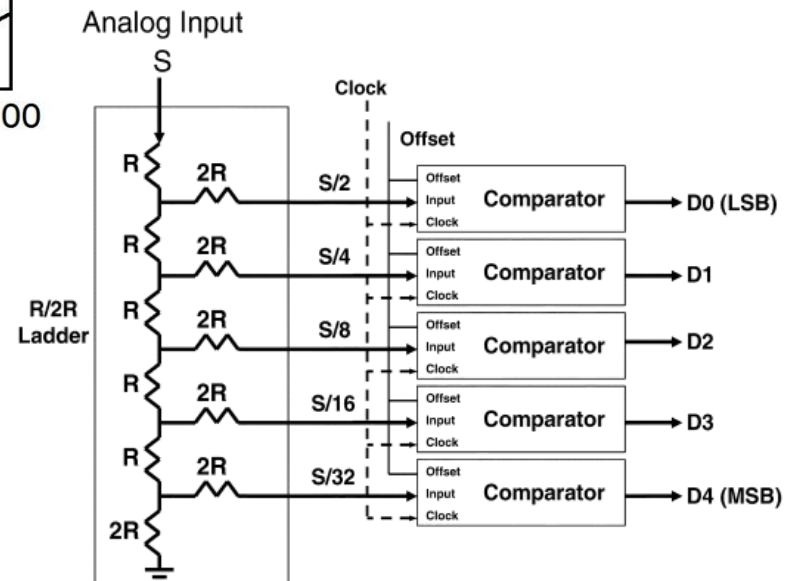
 




# Flash ADC

 


# Fabricated Flash ADC (10 GHz, 4 bit)

  


# Superconducting Stripline Detectors (SSLD) Towards Megapixel Neutron Imager

# SSLD (Kinetic Inductance mode)

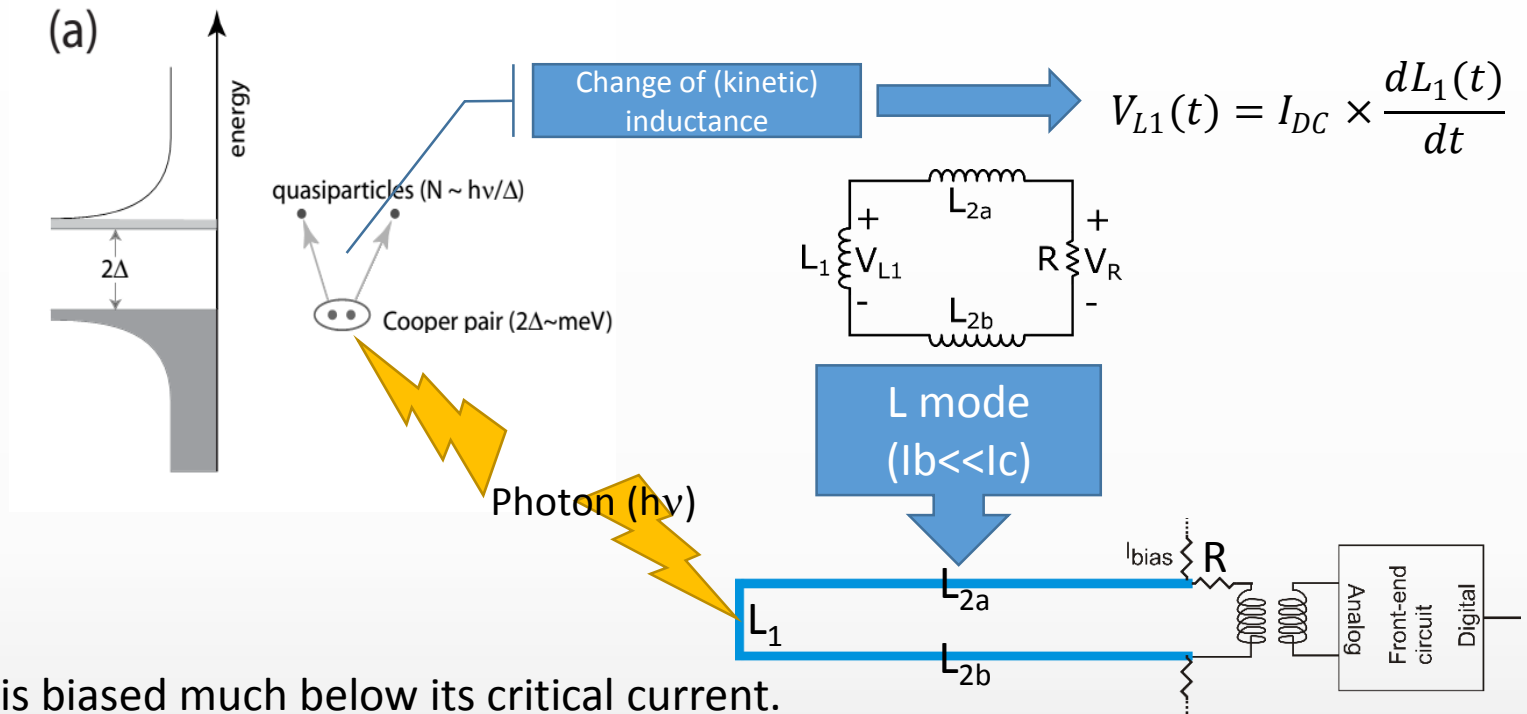


1. SSPD is biased much below its critical current.
2. Arrival of a photon over part of the SSLD ( $L_1$ ) breaks cooper pairs and generates quasiparticles.
3. Change of number of cooper pairs and quasiparticles cause change of the (kinetic) inductance ( $\Delta L_1$ ).
4. Change of inductance causes a voltage response to be generated ( $dL_1/dt$ ).
5. This voltage response is converted to current with an series resistance  $R$  in the loop ( $I = V_R/R$ )
6. The current is coupled to the read-out circuit and digitized to be processed by the encoder circuit.

# SSLD (Resistive Mode)

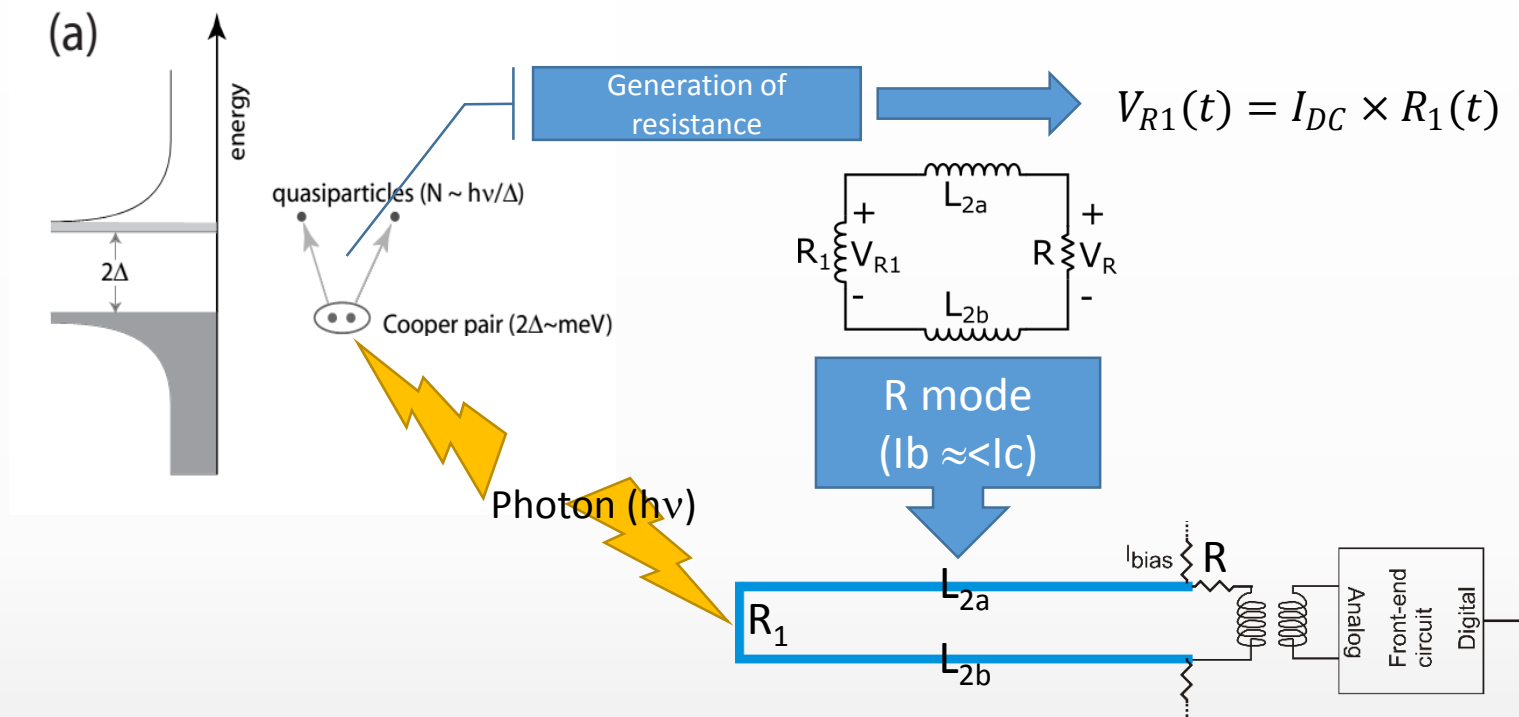

1. SSLD is biased just below its critical current.
2. Arrival of a photon over part of the SSLD destroys superconductivity locally.
3. Destruction of superconductivity causes a local resistance increase.
4. Generation of a resistance causes voltage signal under constant bias current.
5. This voltage response is converted to current with an series resistance  $R$  in the loop ( $I = V_R/R$ )
6. The current is coupled to the read-out circuit and digitized to be processed by the encoder circuit.


# Boron Layer

 

Ishida et al. DOI 10.1007/s10909-014-1159-8

# Fabrication Process

## AIST New Process for Monolithic Chip

 



- ✓  $J_c$  of  $10 \text{ kA/cm}^2$  is applied.
- ✓ Die size is  $22 \text{ mm} \times 22 \text{ mm}$ .
- ✓ Test of detector array was carried out with a monolithic chip without a  $^{10}\text{B}$  layer.

# Design Objectives of the SSLD Monolithic Chip



1. Fit inside an A1ST new process for a monolithic chip die (22mm\*22mm).
2. Achieve 1000\*1000 pixel sensor resolution
  - Detector width  $< 22\text{mm}/1000=22\mu\text{m}$
3. Have sufficient sensitivity for incoming neutron
4. Have small dead time ( $\sim 10\text{ns}$ )
5. Use a single bias point
6. Achieve crosstalk free operation and SFQ read-out
7. Operation in both CB-KID or CB-TED modes is acceptable.



# Single SSLD Circuit Model

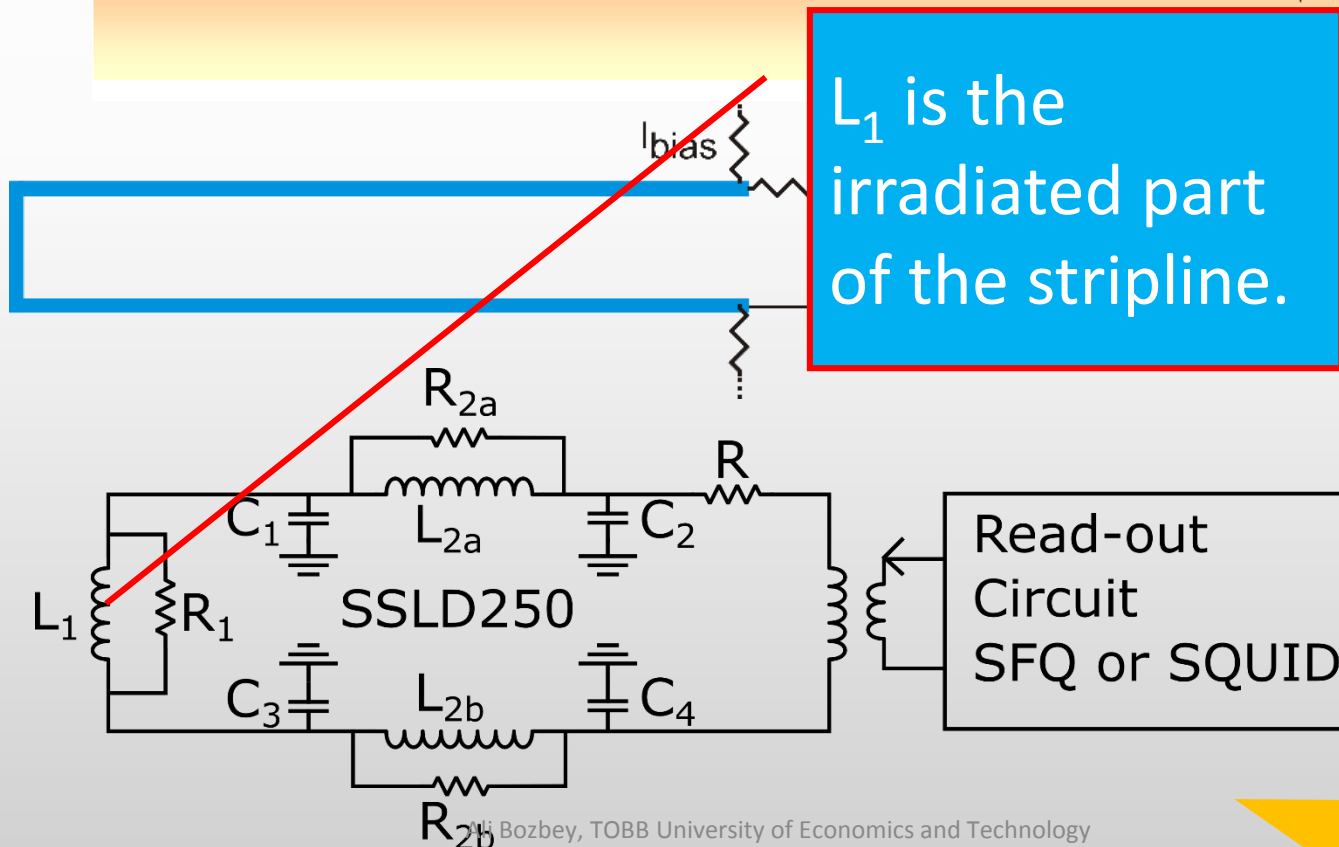 


# Single SSLD Circuit Model

 
 


- $L_2 \gg L_1$ ,  $L_{2a}/L_{2b}$  ratio is determined by the location of the irradiation on the stripline.
- Shunt resistors represent the resistive layer fabricated under the stripline layer.
- $C_1$ - $C_4$ : Parasitic capacitance of the stripline


$\pi$  model for the stripline.

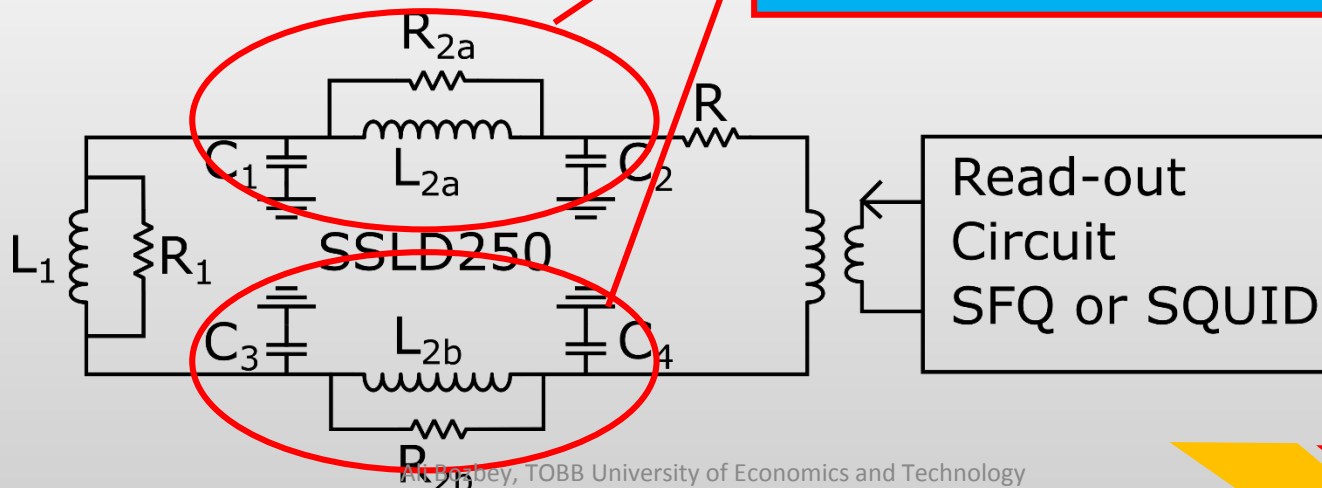



# Single SSLD Circuit Model

  


R is the LR loop resistance

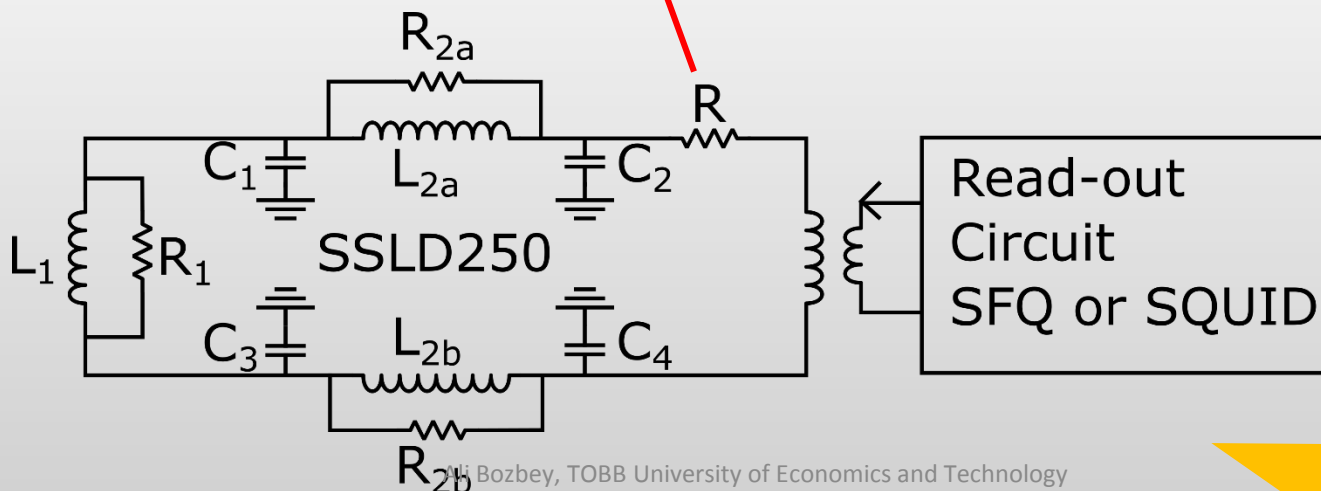



# Single SSLD Circuit Model

  



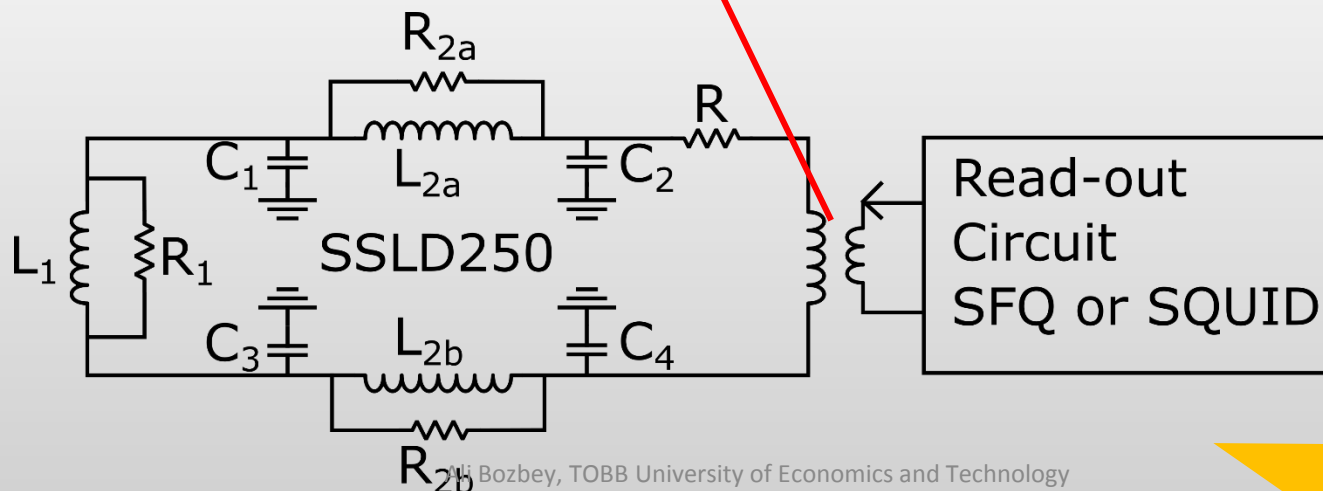
Coil transfers the current associated with the radiation to the read-out circuit.








# Detector Model and Front-end Circuit

 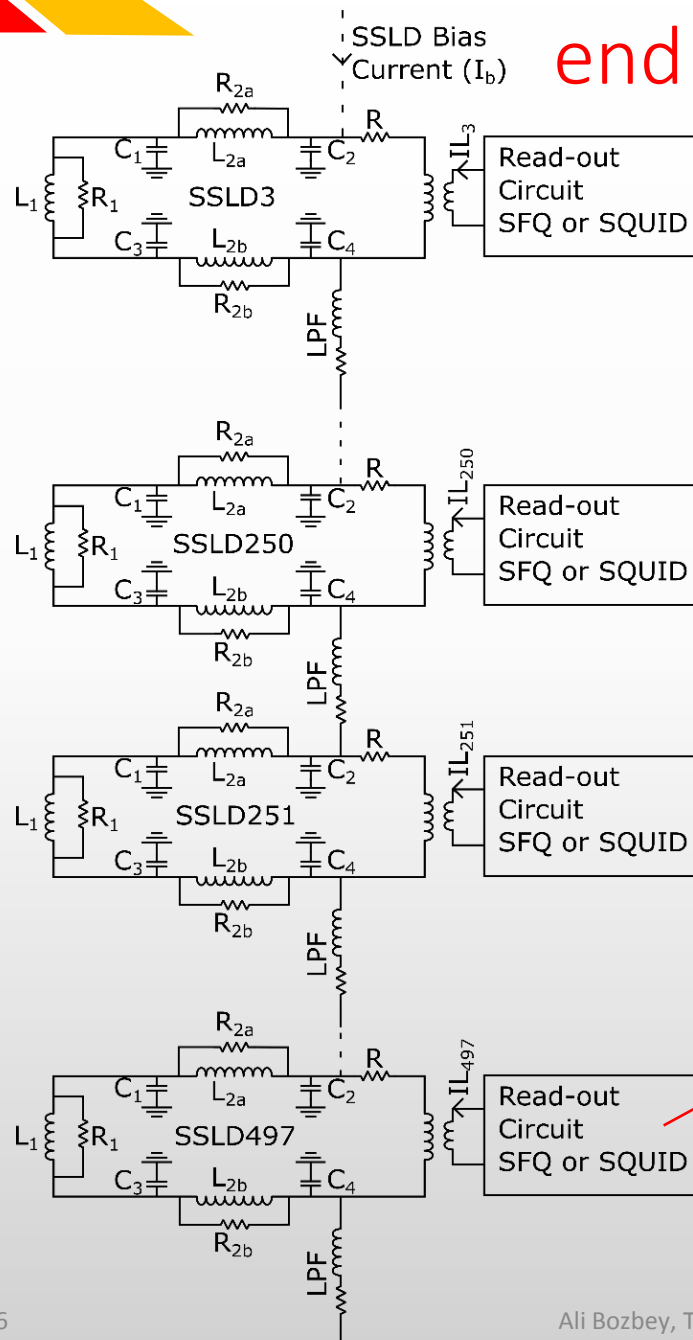




# Front-end Circuit: Sim and Exp

  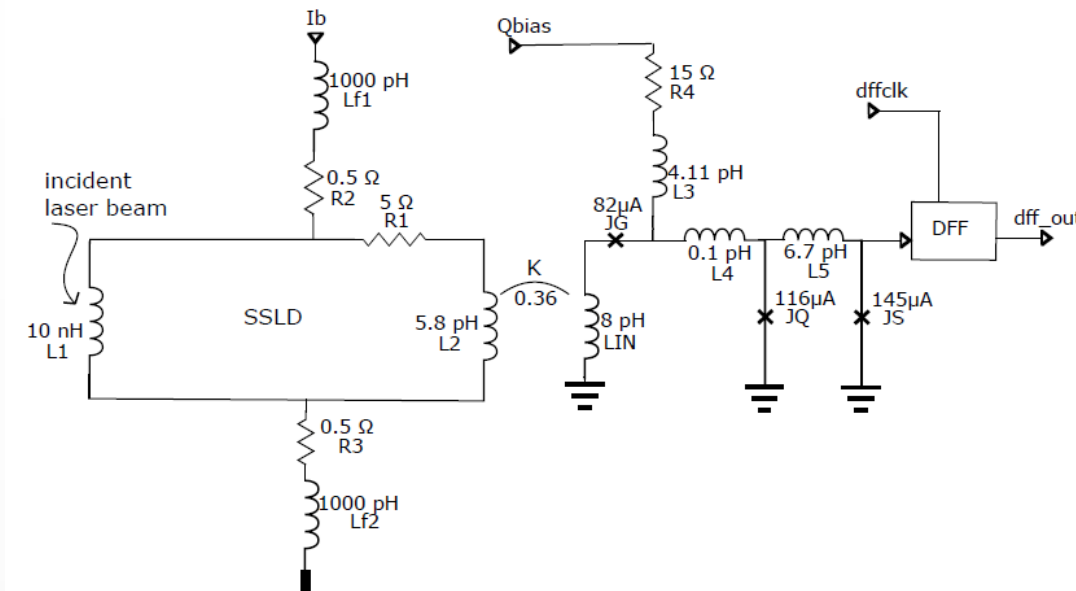

# Experimental Setup

  
 
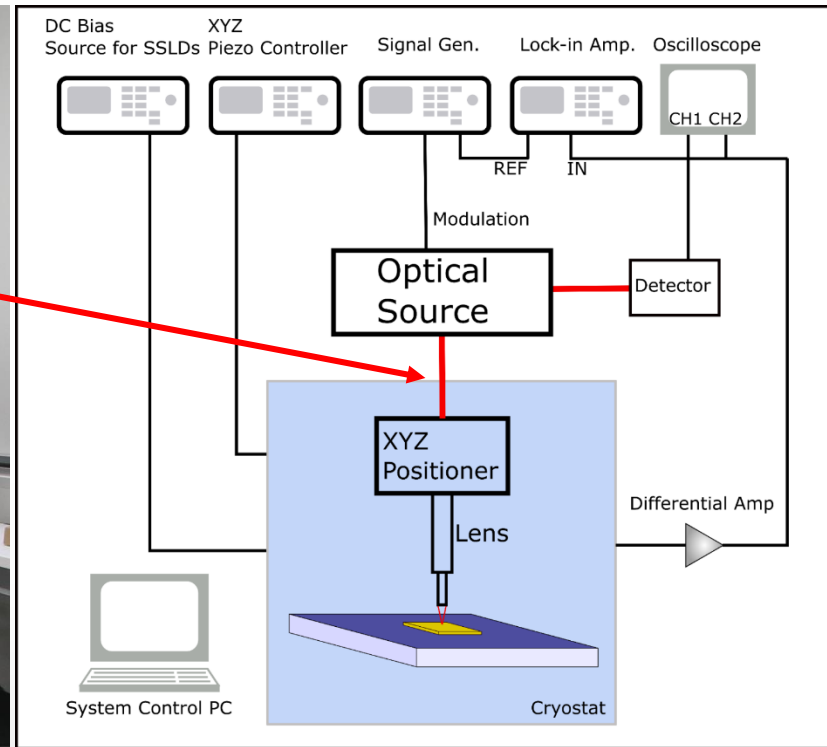
 


# Experimental Setup

  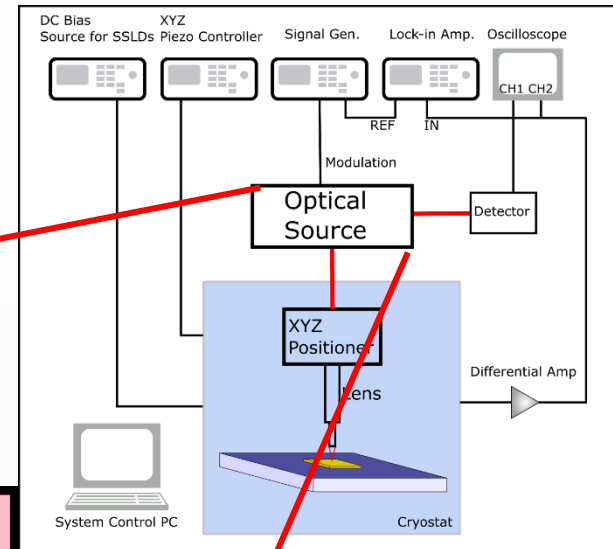




# Monolithic IR Detector

    




# Dual Tone Multi Frequency Coding

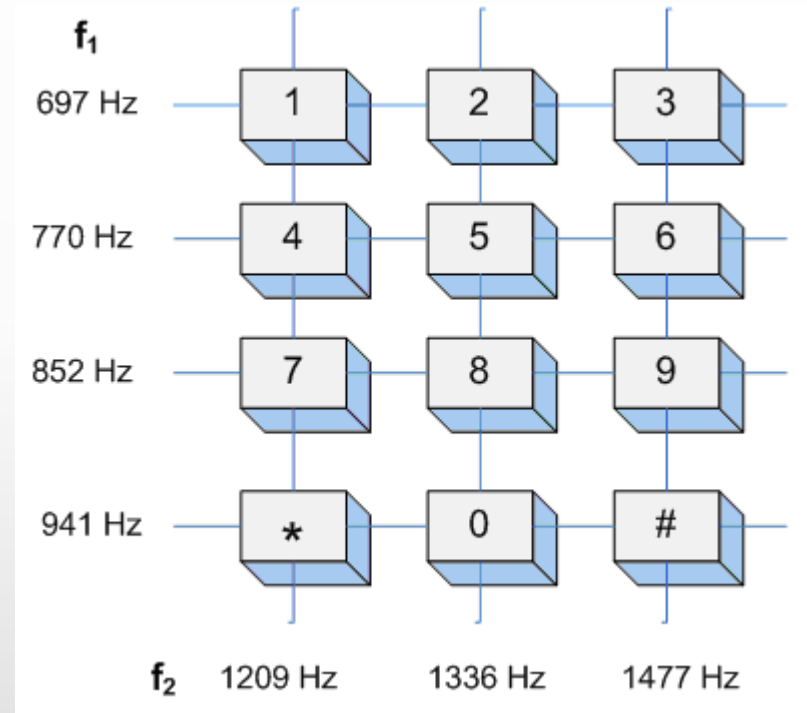


# Many Pixel Operation

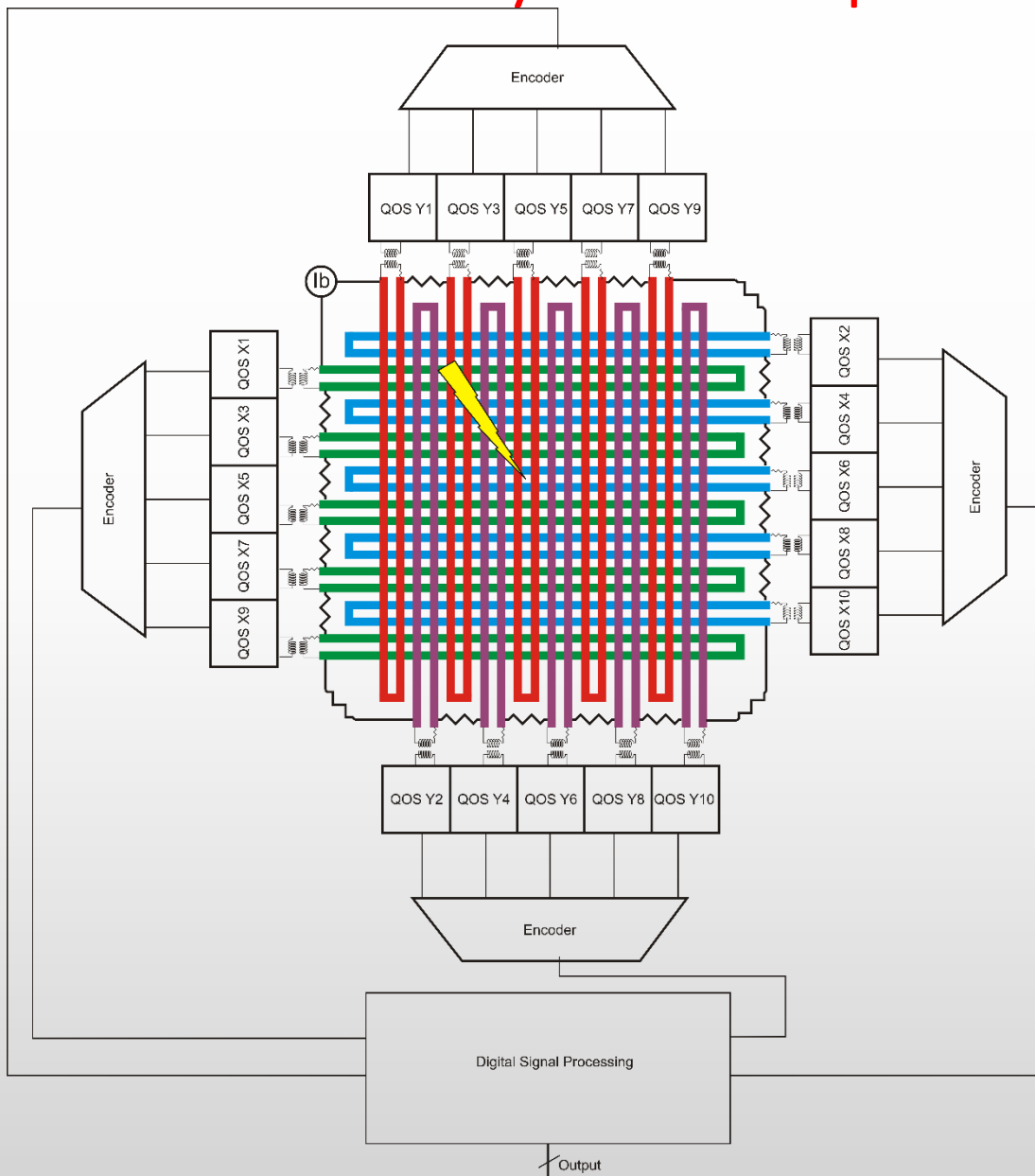


- Only one bias point is sufficient to bias all the SSLDs.
- Each SSLD is separated with low pass filters
- Individual SSLD's are coupled to 1-bit comparator circuits with coupling coils.
- Comparator outputs are fed to encoders to extract the address information for the radiated cell.
- Row and column addresses of SSLD's are determined by front-end circuit and encoder circuits.
  - In the figure, Y5 and X6 are triggered with the incoming photon.

# Bit Serial ALU

 

# Bit Parallel ALU

 

25 GHz,  
2.5 mW

# Acknowledgements

- TUBITAK (108E242, 111E191, 114E099)



- Akira Fujimaki and his associates



- Ministry of Development





- Center of Excellence for Superconductivity Research (CESUR)



The circuits mentioned in these slides were fabricated in the clean room for analog-digital superconductivity (CRAVITY) of National Institute of Advanced Industrial Science and Technology (AIST) with the standard process 2 (STP2). The AIST-STP2 is based on the Nb circuit fabrication process developed in International Superconductivity Technology Center (ISTEC).



# RSFQ Circuit Synchronization

  

If there is an SFQ pulse between two consecutive CLK pulses, logic “1”, otherwise logic “0”