



AGH UNIVERSITY OF SCIENCE
AND TECHNOLOGY



SALT Design I **(Silicon ASIC for LHCb Tracking)**

Marek Idzik on behalf of AGH-UST

Faculty of Physics and Applied Computer Science
AGH University of Science and Technology

INFN Milano LHCb UT workshop
Milano 17-19 May 2016




Outline

- Introduction
- SALT architecture and design
 - Analog and Mixed-Mode
 - Other...
- Simulations, Status and Plans

Introduction

The goal and short history

 The Goal – SALT readout ASIC for UT detector



AGH-UST Design team:

- staff: M. Firlej, T. Fiutowski, M. Idzik, J. Moroń, K. Świentek
- PhD students: Sz. Bugiel, R. Dasgupta, M. Kopec, M. Kuczyńska

SALT story in short:

- Two submissions (5 ASICs) of key functional blocks (Preamplifier&Shaper, Single-to-Diff converter, 6-bit ADC, SLVS, PLL, DLL) done in IBM CMOS 130 nm - designed&fabricated and mostly tested
- In 2014 collaboration decided to move to TSMC CMOS 130 nm
- In February 2015 a large submission – 8 chips, including SALT8 and various blocks, were submitted in TSMC 130 nm – partially tested, problems with ESD/pads (mainly FE and ADC chips)
- In November 2015 SALT8 version 2, 8-channel FE&ADC chips plus other blocks (e.g. bandgaps) submitted, just fabricated, SALT8 tested by JC
- June 2016 we will submit complete 128-channel SALT chip (**why not May ?**)



Introduction

SALT – Specification

- TSMC CMOS 130 nm technology
- 128 channels, Front-end&ADC in each channel
- Input Pitch 80 um (**plus ground pads on the sides!!!**), Output pitch =140um
- Sensor: capacitance 5–20 pF, AC coupled
- Both input signal polarities (p-in-n and n-in-p sensors)
- Input charge range $\sim 30ke^-$
- Noise: ENC $\sim 1000e^- @10pF + 50e^-/pF$
- Pulse shape: $T_{peak} \sim 25$ ns, very short tail: $\sim 5\%$ after $2 * T_{peak}$
- Crosstalk $< 5\%$
- ADC: 6-bit resolution (5-bit/polarity), 40MS/s
- DSP functions: pedestal and common mode subtraction, zero-suppression
- Serialization&Data transmission: 320 Mbps e-links to GBT, SLVS I/O
- Slow control: I2C
- Power < 6 mW/channel
- Radiation hardness ~ 30 MRad

SALT ver 3 chip documentation

Mirosław Firlej, Tomasz Fiutowski, Marek Idzik,
 Jakub Moron, Krzysztof Swientek
 Szymon Bugiel, Roma Dasgupta, Marika Kuczynska

Created: January 2016

Last change: May 13, 2016


Contents

1. ASIC overview	4	9. Chip description	20
2. Analogue front-end	5	10. I/O interfaces	23
3. Analog to Digital Converter	6	10.1. Slow I ² C interface	23
4. Generation of common mode voltages	7	10.2. Fast data interface with DDR serializer	27
4.1. Bandgap reference and temperature sensor	8	10.3. Fast TFC interface with DDR deserializer	28
5. Clock generation	8	11. Padding	30
5.1. Delay Locked-Loop (DLL)	8	12. Open issues, questions, proposals . . .	37
5.1.1. DLL configuration procedure	9	12.1. DSP and back-end data processing modification	37
5.2. Phase Locked-Loop (PLL)	10	12.2. DSP modification propositions	37
5.2.1. PLL configuration procedure	11	A. ASIC registers	39
6. Digital Signal Processing	11	A.1. Analogue and mixed-mode registers	39
6.1. Pedestal subtraction	12	A.2. DSP registers	47
6.2. Mean Common Mode Subtraction	13	A.3. Memory registers and counters	61
6.3. Zero Suppression	15	A.4. Serializer registers	63
6.4. NZS data	16	A.5. Other configuration registers	65
7. Back-end data processing	16	A.6. TFC counters	70
7.1. Packet building and recording	17	B. Changes in comparison to previous version	75
7.2. Data stream buffering and splitting	17		
8. TFC debug block	20		

SALT documentation is not yet completed, work in progress...

Introduction

SALT Architecture

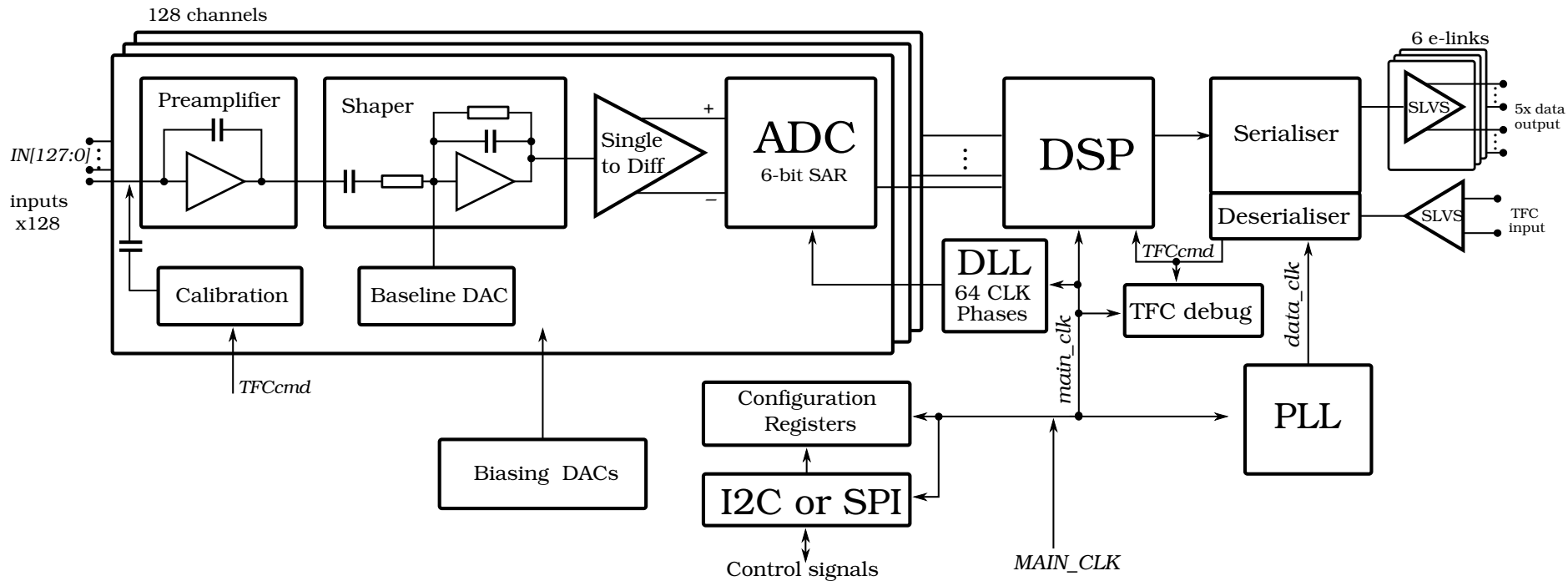


Most of key blocks of SALT were included in 8-channel prototypes called SALT8 version1&2. In SALT8 version2 important parts (e.g. ELT transistors for small currents, new Single to Diff) have been improved or corrected. But since SALT is a very complex chip several features will appear only in next submission...

SALT design Front-end considerations

Is it possible, with realistic shaper complexity and power consumption, to shorten the pulse tail to decrease to 5% of pulse amplitude after $2 \cdot T_{\text{peak}}$?

 
Matlab simulations of the front-end response for various configurations of poles and zeros in the shaper transfer function



Introducing complex poles and zeros in transfer function one can shorten the pulse tail to the required goal

SALT design

Preamplifier and Shaper

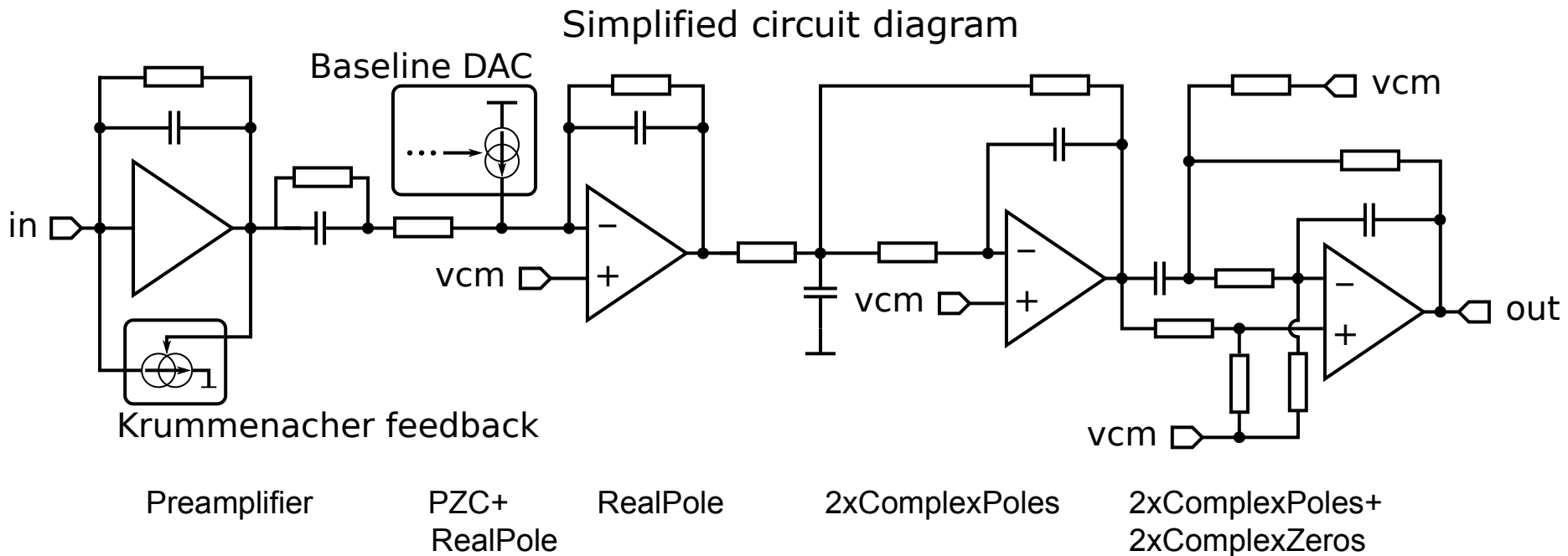


- 3-stage shaper gives the requested pulse with short tail
- Common mode (vcm) is kept at half power supply to work with both pulse polarities

Same as in SALT8 version 2

SALT design

 Single to Differential Converter (S2Diff)




- Pseudo-differential solution based on single-ended amplifiers chosen
- Additional gain by 2 may be obtained in S2Diff

Same as in SALT8 version 2

SALT design

6-bit ADC

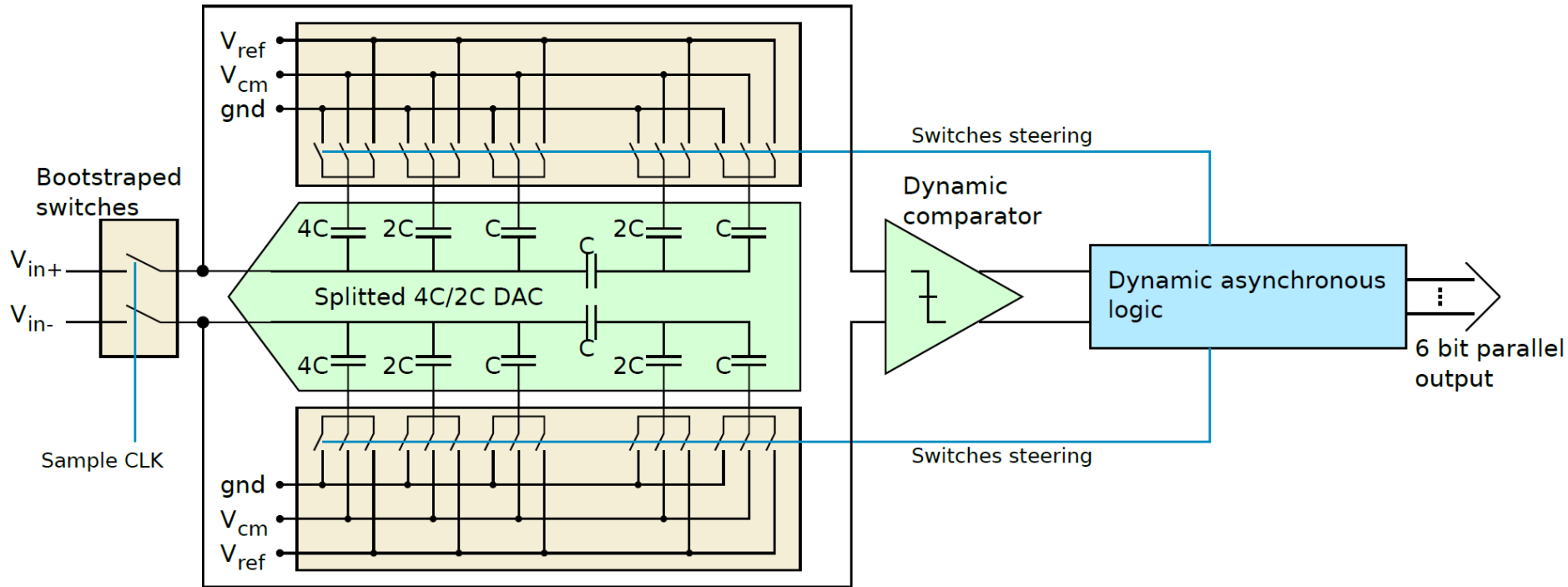


Main features:

- SAR architecture, 6-bit resolution
- 40 MSps nominal sampling rate
- Split DAC with MCS switching scheme
- Asynchronous logic

Same as in SALT8 version 2

SALT design

 Common mode voltages generation and bandgap reference



Reference signals:

- Bandgap reference of 0.6V. The circuit includes also temperature sensor
- VCMA 0.6V for first two shaper stages
- VCMB 0.6V for third shaper stage
- VCMC 0.6V for single-to-differential
- VCMD 0.6V common mode voltage for ADC

Newly designed for SALT



SALT design


Biasing, Calibration Monitoring,

Other Analog&Mixed-mode components:

- Two test channels (one on each side), various signals are buffered and go to pads
- Calibration circuit (set separately for each channel)
- 7 DACs setting various biases: preamp, Krummenacher, shaper, S-2-Diff, Calibration, SLVS-Ibias, SLVS-Vref. Could be readout via test-pads
- Six Monitoring 6-bit ADCs: Vctl-PLL, Vctl-DLL, 7 DACs multiplexed to 2 ADCs, PTAT-temperature, Vref-bandgap

Mostly newly designed for SALT or modified

SALT design DLL

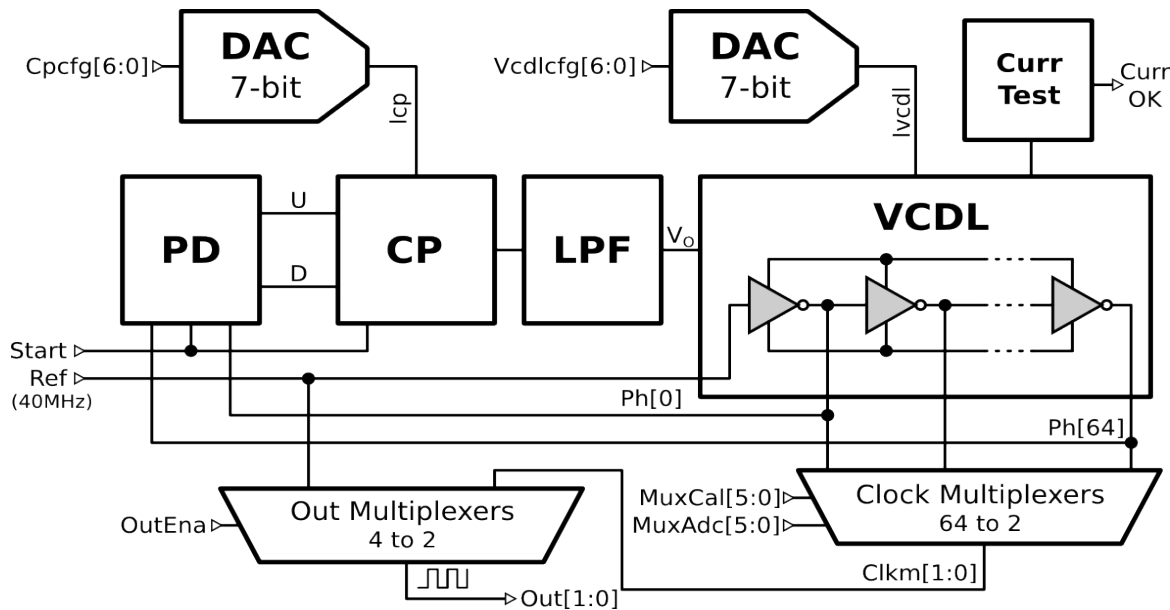


DLL features:

- Operating frequency: 40MHz
- 64 clock phases
- Two selectable output phases
- VCDL Current Test Logic
- Power < 2mW @ 40MHz
- Jitter < 15 ps @ 40MHz

PFD change to PD to improve radiation hardness

Monitoring and calibration improved

SALT design PLL

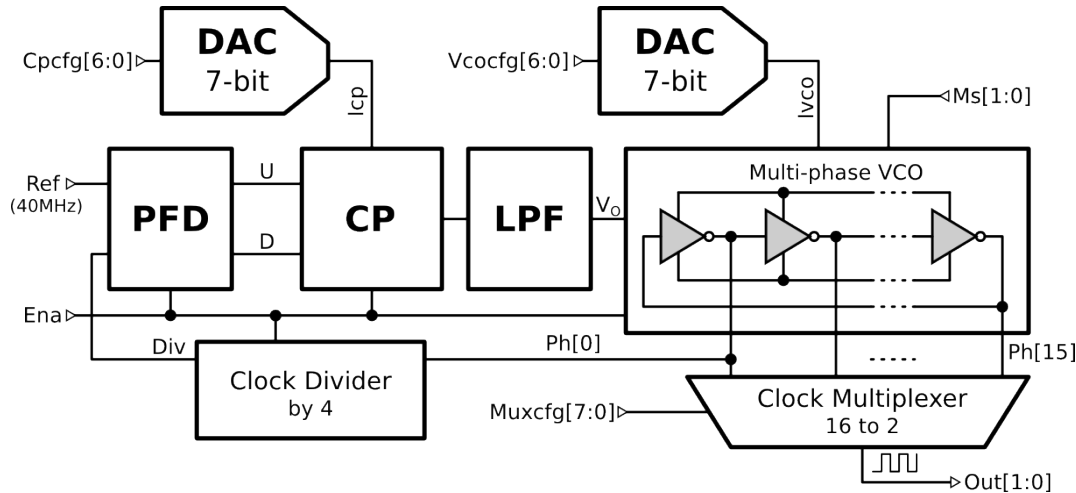


PLL features:

- Output frequency 160MHz
- Divider by: 4
- Reference frequency 40MHz
- 16 phases available
- Two selectable output phases
- Power < 2mW @ 160MHz
- Jitter < 10ps @ 160MHz

Practically, the same as in SALT8 version 2
(not used functionality removed)


SALT design

DSP and Data Processing Chain

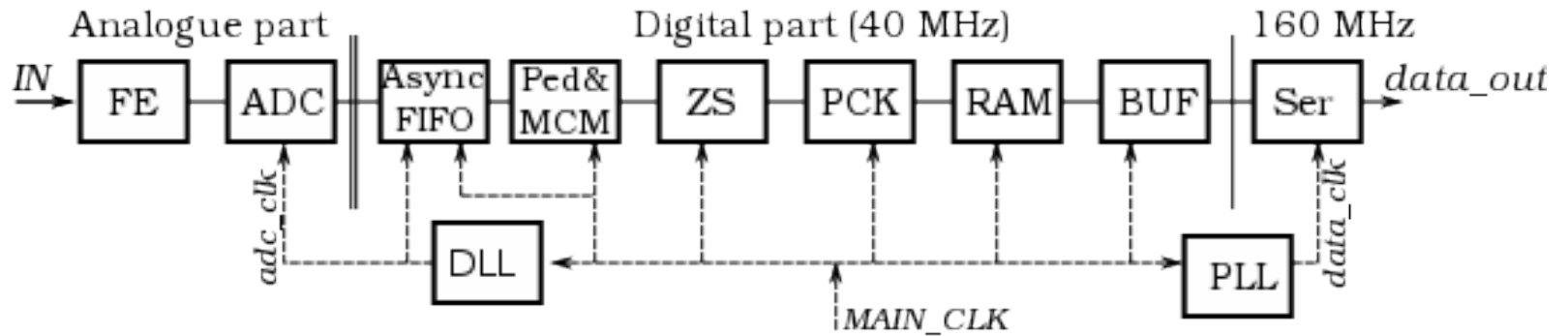

Many changes → Krzysztof


SALT integration Floorplan and layout

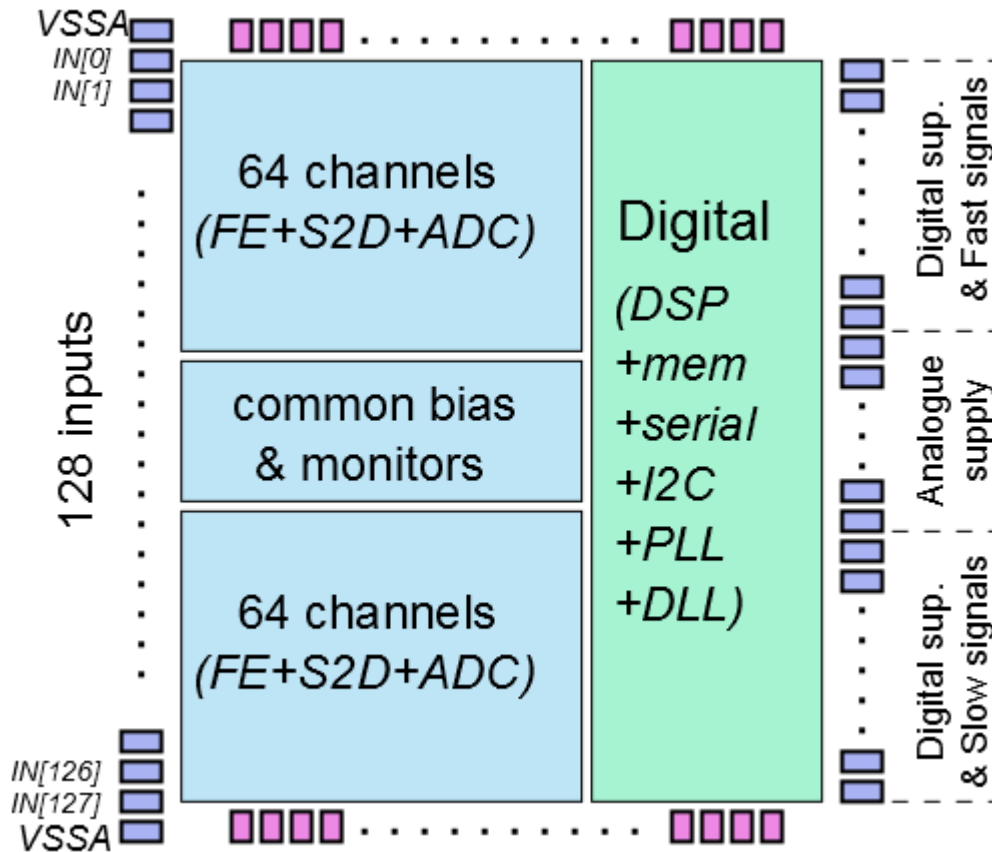

Completely new → Tomek

SALT – simulations, status and plans

- Layout of 128 channels
 - Analog&Mixed-mode just completed → Tomek
 - Digital in progress → Krzysztof
- Top level simulations – by now done either on schematic or only part of extracted view (lack of computing power/memory)
- When taking into account realistic supply network various parameters
 - crosstalk, disturbances, PSRR deteriorate, how much ?
 - we need 128-channel simulation on extracted view

 

Schematic 128 channels,
Cdet=3pF, Cint=2x5pF

SALT – simulations, status and plans

- Last week we managed to prepare a workstation with ~300GB of RAM
- We have managed to extract the netlist of 128 channels of Analog&Mixed-mode part
- First simulations just started (~week for simple run)
- **Few words about power...**
-
- Submission planned for mid-June