 





# **Front end electronics for silicon strip detectors in submicron technologies**

Jan Kaplon  
CERN, Geneva


 
# Outline

- Silicon strip detectors for the High Luminosity LHC upgrade
- Requirements and constraints
- Basic architectures of the input stages
- Examples of the channel architecture for ATLAS and CMS
- Summary




# Silicon strip trackers for LHC high luminosity upgrade

Silicon strip sensors are baseline solution for the inner tracking detectors at HL LHC<sup>(\*)</sup> for  $30\text{cm} < r < 1\text{m}$

- ATLAS: strips 2.5 and 5cm/70um pitch, (ABCStar chip in GF 130nm)
- CMS: strips 5cm/90um pitch (CBC in GF 130nm), 2.5cm/100um pitch (SSA chip in TSMC 65nm) combined with 1.44mm strips (MPA chip in TSMC 65)
- LHCb: strips 5 and 10cm/pitch 95 or 190um (SALT chip in TSMC 130nm)

 (\*) experiments operating with high luminosity and in highly radiation environment (not ALICE)




# Silicon strip trackers for LHC high luminosity upgrade (2)

- Radiation environment: doses in the range of 100MRad and  $10^{15}$ N/cm<sup>2</sup> → CMOS deep submicron (now 130 or 65 nm)
- High luminosity = high granularity →
  - lower sensor capacitances (usually a few pF)
  - power/area constant ( $\sim 10$ mW/cm<sup>2</sup>) → reduced power/channel
- Lower signals (thinner sensors, severe radiation damage) → maximum ENC below 800 to 1000 e-

→ impact on the optimization of the input stage
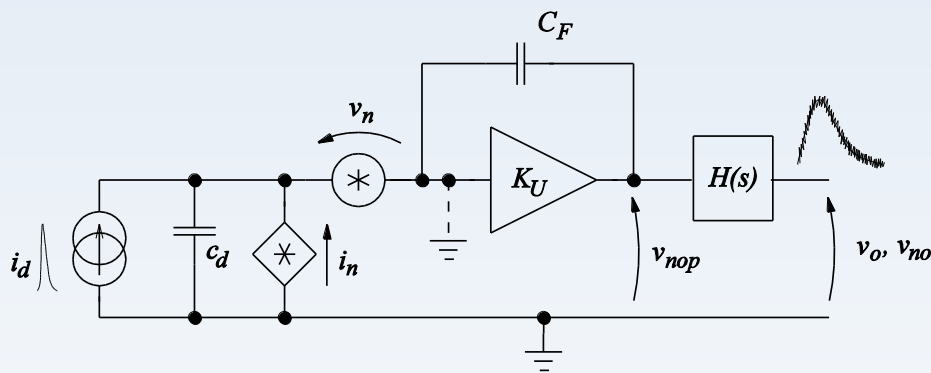
# Reception of signal from sensors

- Charge Sensitive Amplifiers & CR-RC shaper ( $T_p < 25\text{ns}$ )
- Main contributions from electronics to ENC (ideal case, SE stage): input transistor and feedback



$$ENC^2 = \left( F_V \overline{v_{ne}} c_d / \sqrt{\tau} \right)^2 + \left( F_i \overline{i_{ne}} \sqrt{\tau} \right)^2$$

where the first term is labeled **SERIES** and is enclosed in an orange box.

where


$$\overline{v_n} = \sqrt{\frac{4 k T \gamma n}{g_m}}$$

where  $g_m$  is enclosed in an orange box.

Higher granularity of the sensor helps for noise/power optimisation (series noise dominant)

$\tau$  – peaking time  $c_d$  – detector capacitance  
 $F_V, F_i$  – filter coefficients for CR-RC<sup>n</sup> filter

# Reception of signal from sensors (2)

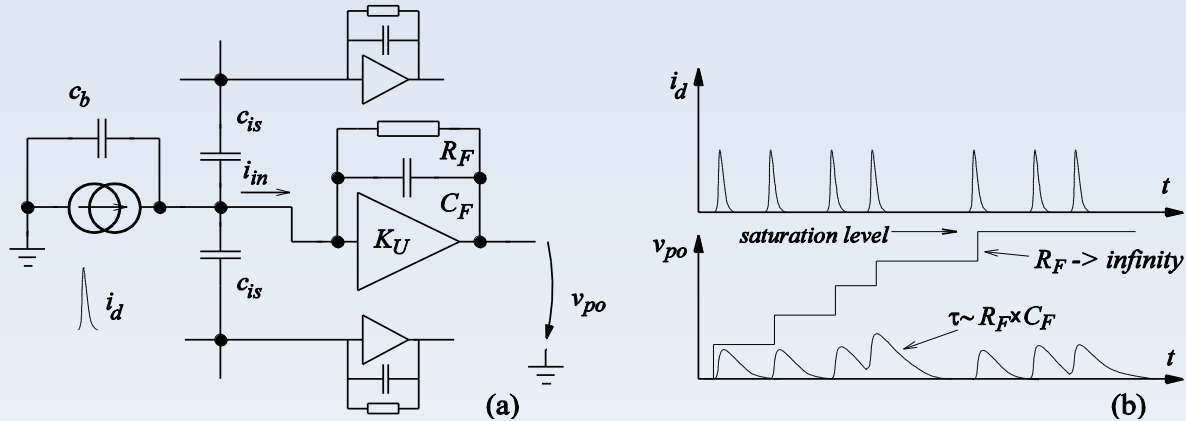

Strip detector: mesh of the parasitic capacitances  $\rightarrow$  basic task for the input stage: effective charge collection and crosstalk minimization (low input impedance of the preamplifier)

CSA input impedance: feedback impedance divided by open loop gain  $\rightarrow$


- trade off between input impedance and close loop gain
- transimpedance amplifier preferable

For electronics at ATLAS and CMS we require GBP above 1GHz and open loop gain 70-80dB (for detector capacitances of the order of 3-8pF the crosstalk signals below 5%)

Optimisation of the input stage  $\rightarrow$  driving the open loop gain and GBP preserving the power budget (single ended input stage preferable)



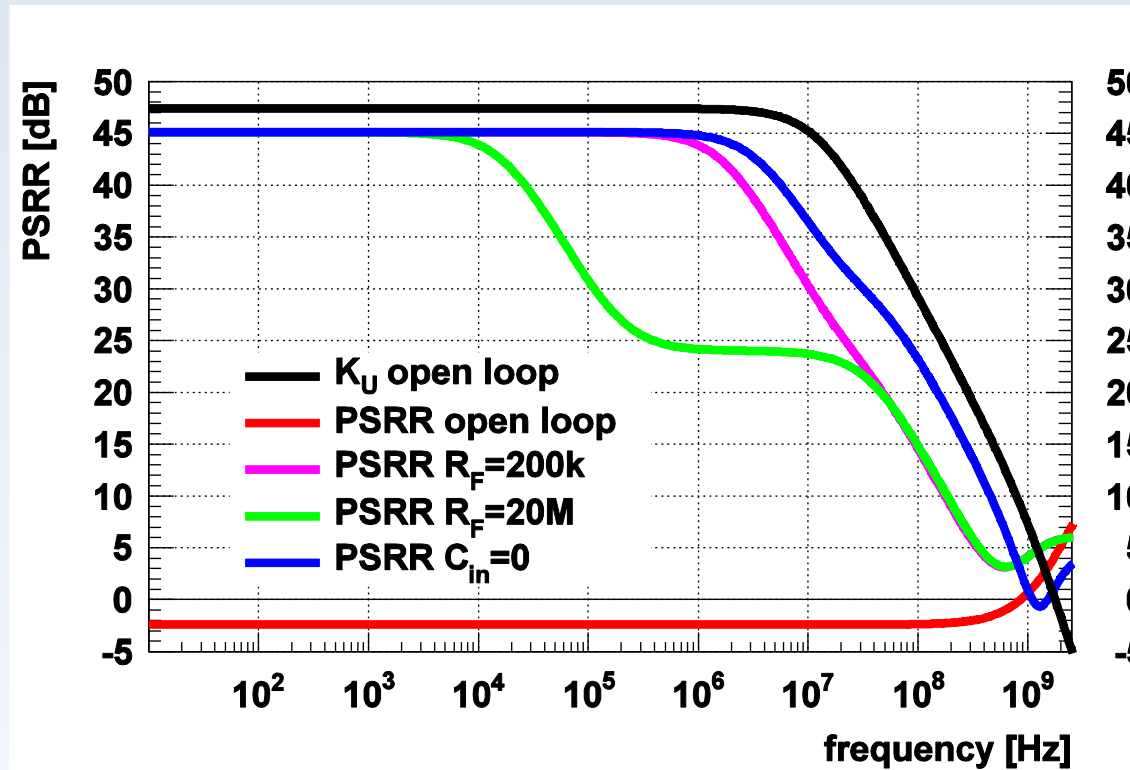
# PSRR: another motivation to increase GBP and open loop gain



Open loop gain and PSRR characteristics on the example of TDCPix preamp (fast ( $T_p=5ns$ ) pixel, GF 130nm) working in charge and transimpedance mode
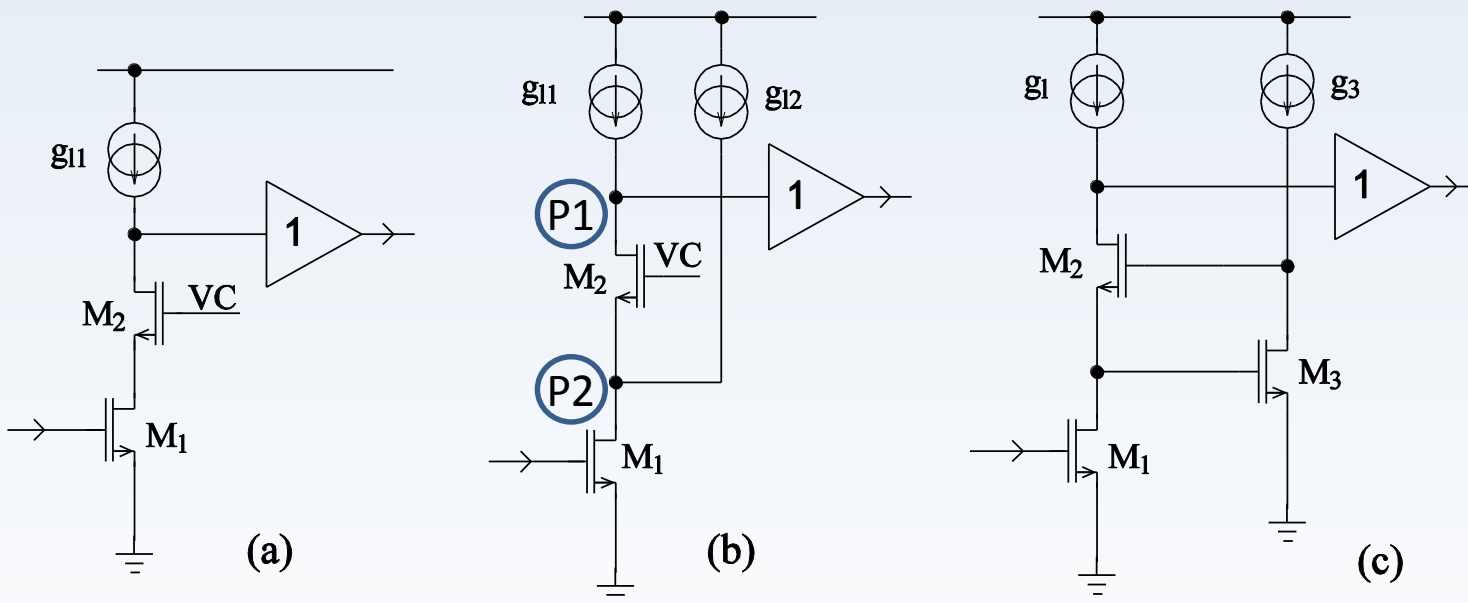
# High gain input stages for CSA

- **Requirements: High radiation** → CMOS devices only, 130 and 65nm processes.  
**Low power** → single stage, high bandwidth and high open loop gain (50-80dB) amplifier → telescopic cascode.
- Dominant noise source for fast shaping: series noise of the input transistor (thermal) → NMOS transistor preferable
- Unity gain buffer to avoid loading effect from the feedback circuit



(a) Telescopic cascode, (b) telescopic cascode with GBP improvement (shifting P1, limit by P2), (c) regulated telescopic cascode






# High gain and GBP: technology limitation

IBM CMOS	250nm RF (IBM)	130nm RF (GF)	65 nm LP (TSMC)
$t_{ox}$	5nm	2.2nm	2.6nm
$K_p@I_{spec}$ NMOS	330 $\mu A/V^2$	720 $\mu A/V^2$	320 $\mu A/V^2$
Vdd	2.5V	1.2V (1.5V)	1.2V
$g_m/g_{ds}$ moderate inv. (example for input transistor)	70 ( $l=500nm$ )	30 ( $l=300nm$ )	18 ( $l=140nm$ )*
Peak ft	35 GHz	94 GHz	240 GHz

(\*)  $g_m/g_{ds} \sim$  constant for the same transistor length



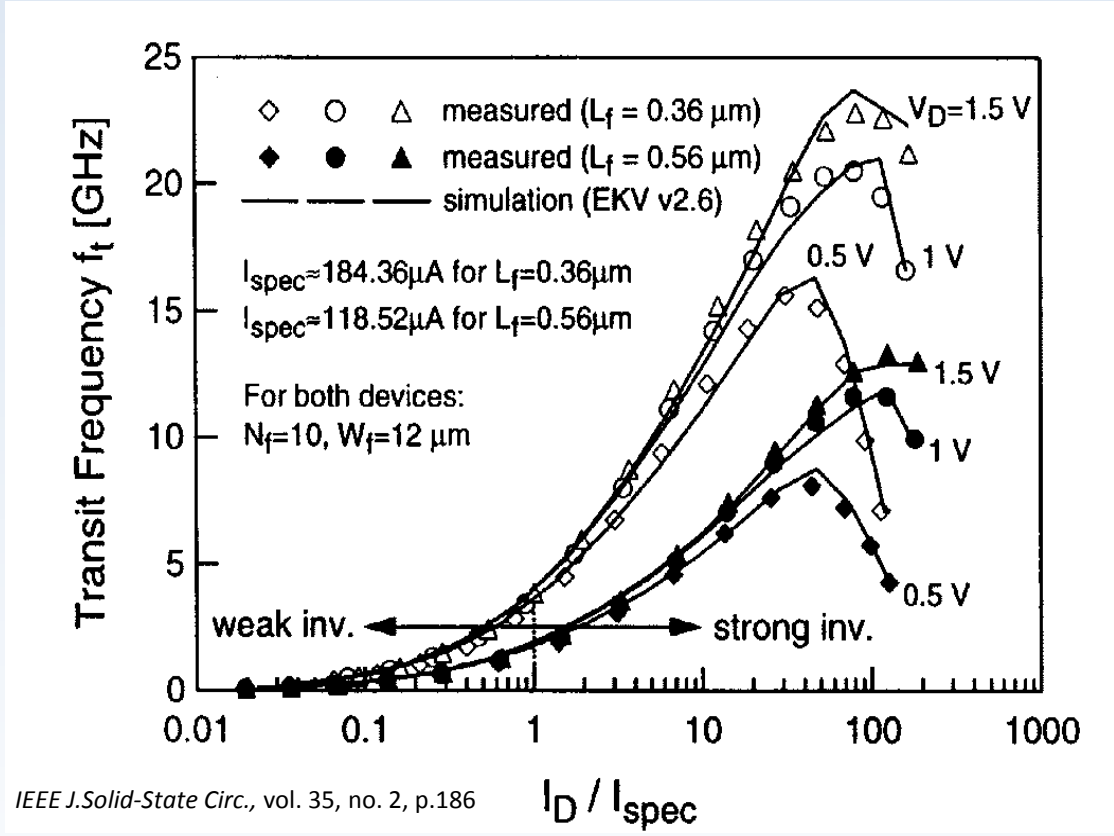
# Limitations for GBP: consequence of the operating point



Transit frequency  $f_t$  as a function of inversion order for 250nm CMOS technology

 
Transit frequency is degraded with device dimensions and depends strongly on the bias (inversion region); in front end electronics we are far away from the maximum  $f_t$



# Limitations for GBP: layout constraints

Multichannel (128-256) ASIC: front end electronics layouted in narrow pitches (22um for ABCStar) – not optimal for preserving GBP (differences between schematics and layout for GBP up to 30%)



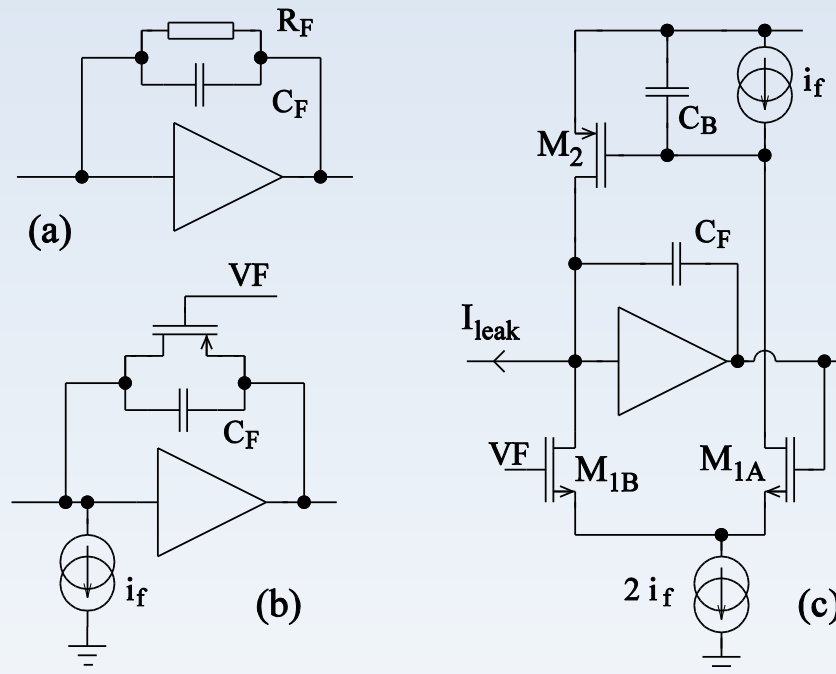
# Input stages: feedback circuits in ATLAS and CMS front end amplifiers



- Main tasks:
  - Integration of charge on the feedback capacitor  $C_F$  (defines signal gain)
  - Baseline restoration (resistor or active circuit):
    - discharge of the  $C_F$  (high data rates  $\rightarrow$  short time constant)
    - leakage current compensation (in case of DC coupled sensors)


   
# Input stages: feedback circuits in ATLAS and CMS front end amplifiers



## (a) Resistive feedback


Discharge with  $\tau \sim R_F C_F$ , ENC: parallel noise contribution  $\sim 1/R_F$

Disadvantage: no control of DC at preamp output

Advantage: simple and robust, tolerance to low level of leakage (DC change but no extra noise contribution), leakage compensation can be added


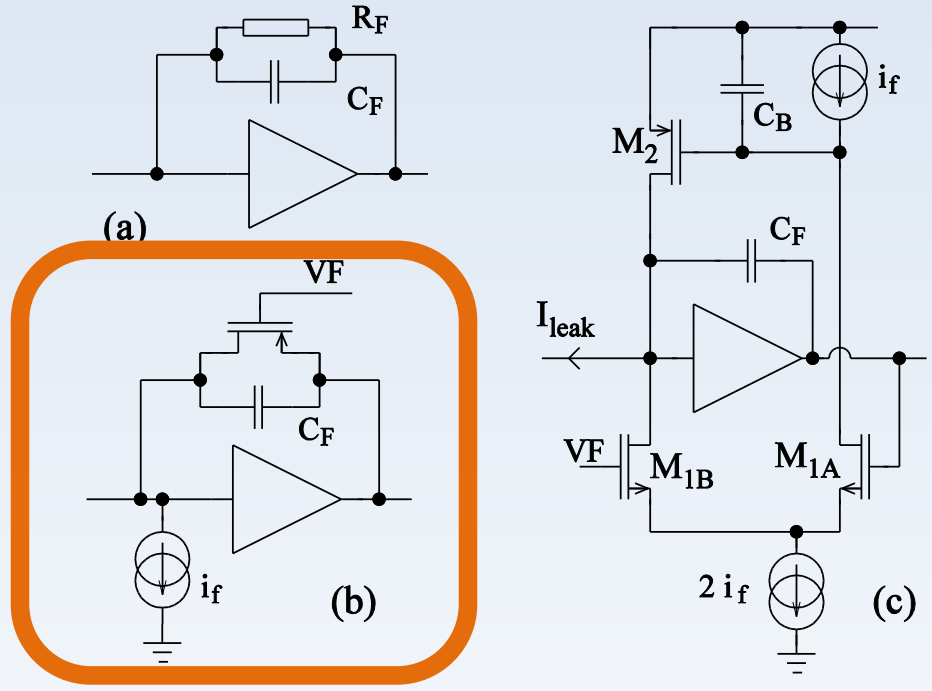
# Input stages: feedback circuits in ATLAS and CMS front end amplifiers



## (b) Active feedback with MOS in saturation

Discharge with  $\tau \sim C_F/g_m$ , ENC: parallel noise contribution  $\sim g_m$  of feedback transistor (and from  $i_f$ )



Disadvantage:

- no leakage compensation – AC coupled sensors
- Signal compression for negative charges (n-on-p sensors)

Advantage: easy control of DC at the preamp output (with  $V_F$ ), fast response for signal overdrive (quadratic compression)

Used in ABC250 and ABC130 prototypes.
 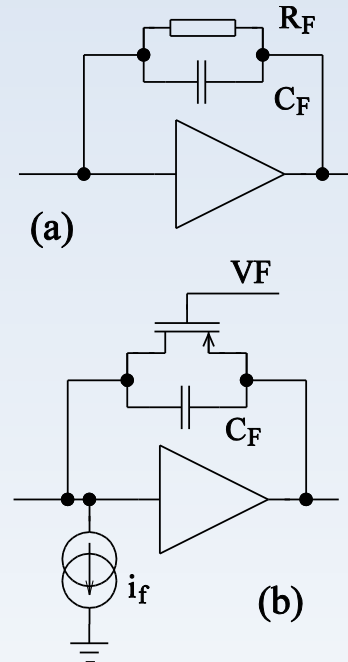
# Input stages: feedback circuits in ATLAS and CMS front end amplifiers



## (c) Krummenacher feedback

Discharge with  $\tau \sim 2C_F/g_{m1}$ , ENC: main parallel noise contribution  $\sim g_m$  of transistor  $M_2$  (still some contribution from  $M_{1B}$ )


Disadvantage: extra low freq. zero, 2x higher parallel noise when compare to simple AFP

Advantage: leakage compensation, small silicon area for high feedback impedance

implementation (important for pixel circuit), DC at the output controlled with  $V_F$ , no signal compression



 
# ATLAS strip tracker – ABCStar amplifier



- Application: ATLAS silicon strips (2.5cm and 5cm),  $C_{in}$ : 3-8pF
- GF130nm process
- Regulated cascode with NMOS input transistor biased with 140uA
- Open loop gain: 78dB (standard cascode load)
- GBP boosting (GBP~1.5GHz)
- Miller compensation with poles splitting
- Resistive feedback
- Strong (120mV) degeneration of active loads (noise minimization), minimum  $V_{dd}$  1.1V (max=1.6V)




# CMS short strips (PS) – SSA

 


- Application: CMS short strips (2.5cm),  $C_{in} \sim 5\text{pF}$
- TSMC 65nm process
- Regulated cascode with NMOS input transistor biased with 130uA
- Open loop gain: 80dB (fully regulated cascodes)
- GBP boosting ( $\text{GBP} \sim 2\text{GHz}$ )
- Miller compensation with poles splitting
- Resistive feedback
- Light (60mV) degeneration of active loads (noise minimization), minimum  $V_{dd}$  1.15V (max 1.26V  $\rightarrow$  tight for power distribution system)
- Mixture of regular, HVT, LVT and native transistors (to optimize the operating point)

# CMS ultra short strips (PS) – MPA

 

 
- Application: CMS ultra short strips (1.44mm),  $C_{in} < 0.5\text{pF}$
- TSMC 65nm process
- Telescopic cascode with NMOS input transistor biased with 12uA
- Open loop gain: 54dB
- GBP boosting (2GHz)
- Miller compensation with poles splitting
- Krummenacher feedback
- Light (60mV) degeneration of active loads (noise minimization), minimum  $V_{dd}$  1.1V



# Front End channel: examples

- ATLAS and CMS strip trackers: binary architecture (low power, simple and robust) → to limit so called “common mode” effects we need:
  - Reasonable PSRR
  - Good separation between analog and digital domains in terms of:
    - substrate isolation (triple well, BFMOAT, NT\_N)
    - architecture (single ended to differential conversion (at least between analog and digital part of discriminator))
  - Reasonable gain in the front of the discriminator (50-100mV/fC) → in most cases we need booster amplifier (for few pF input capacitance the preamp feedback capacitor is around 100fF → preamp gain <10mV/fC)
- Maximum one AC coupling (difficult to DC couple 3 gain stages) after preamp or after booster (it limit the mismatch propagation and improves PSRR at low and medium frequencies)
- Low pass filter in the last gain stage (shaper) to improve the PSRR. The final shape is similar to CR-RC<sup>2</sup> because of bandwidth limitations in all gain stages.


# ABCStar channel

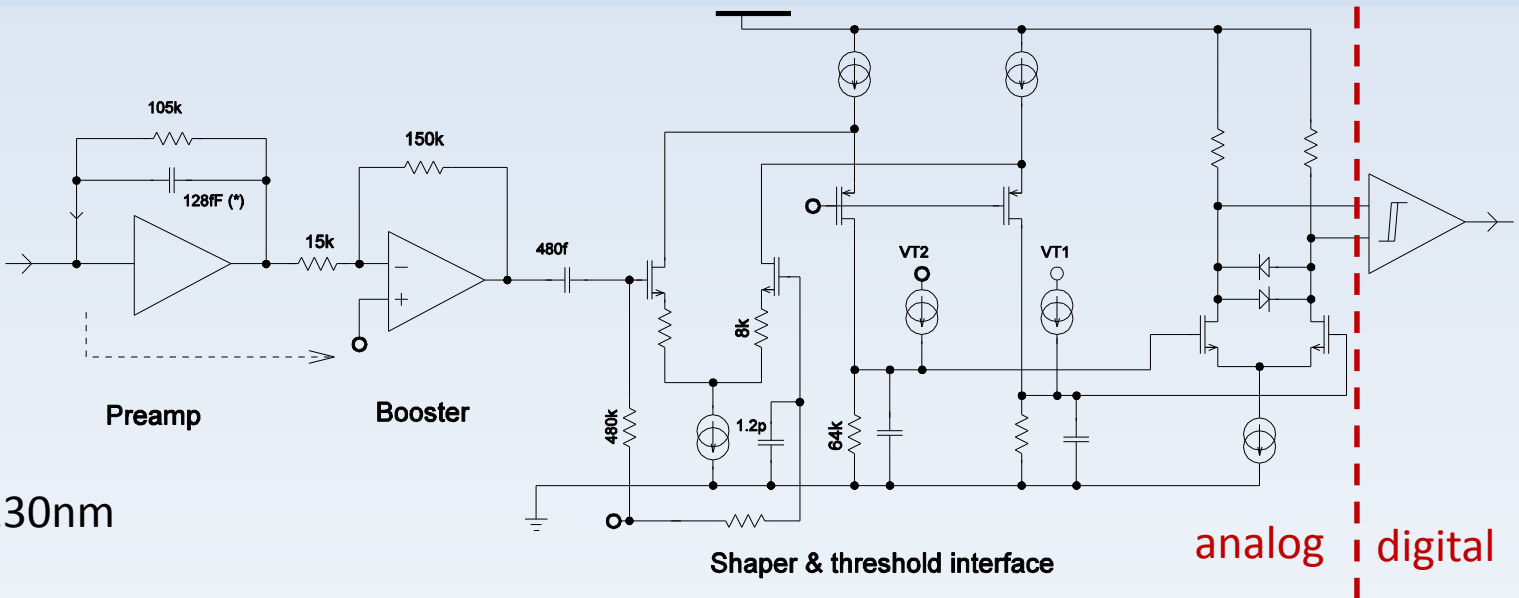

GF 130nm


- Preamp with resistive feedback (105k) and 115fF equivalent capacitor
- 10V/V booster amplifier
- AC coupled single ended to differential shaper/threshold interface (folded cascode with resistive load and degeneration)
- Differential thresholds current sources (VT1&VT2: global DAC and TRIM DAC) → architecture has impact on gain matching but allows for optimisation of the dynamic range for 1.2V supply
- Shaping 22ns, ENC@5pF 600e-, gain 95mV/fC
- Power **consumption** ~320uW

# CMS short strips (PS) – SSA

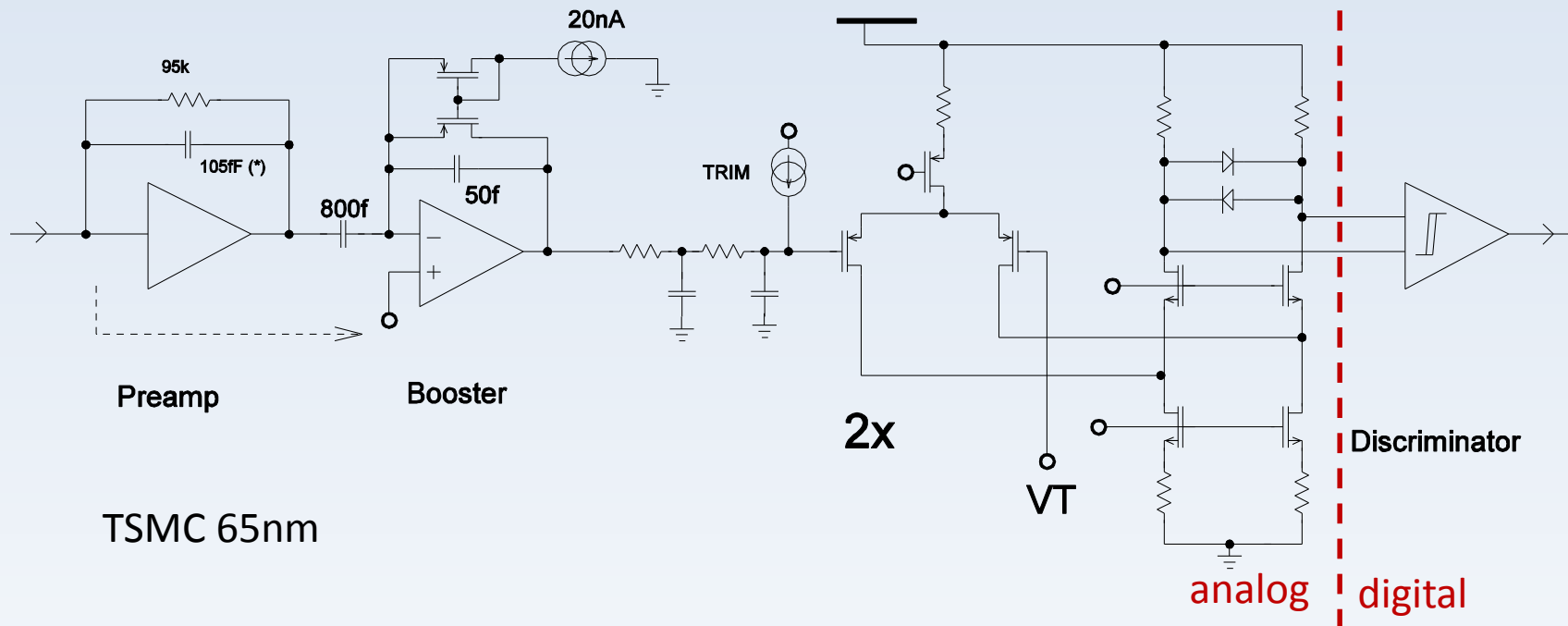

- Preamp with resistive feedback
- Booster: capacitive feedback ( $\sim 15V/V$ ) with active feedback for overshoot compression (PMOS in linear region with overshoot compression); architecture optimized for double pulse resolution ( $< 50ns$ ), (same principle as in CBC chip for CMS long strips)
- Passive RC filter
- Shaping  $17ns$ ,  $ENC \sim 700e^-$  at  $C_{in} = 5pF$ , gain  $50mV/fC$  (to allow for higher linearity; over MIP signal detection)
- 2x 3 stage discriminator, (1<sup>st</sup> stage; folded cascode with resistive load); differential coupling between analog and digital domains
- Overall power:  $300\mu W$

# CMS ultra short strips (PS) – MPA

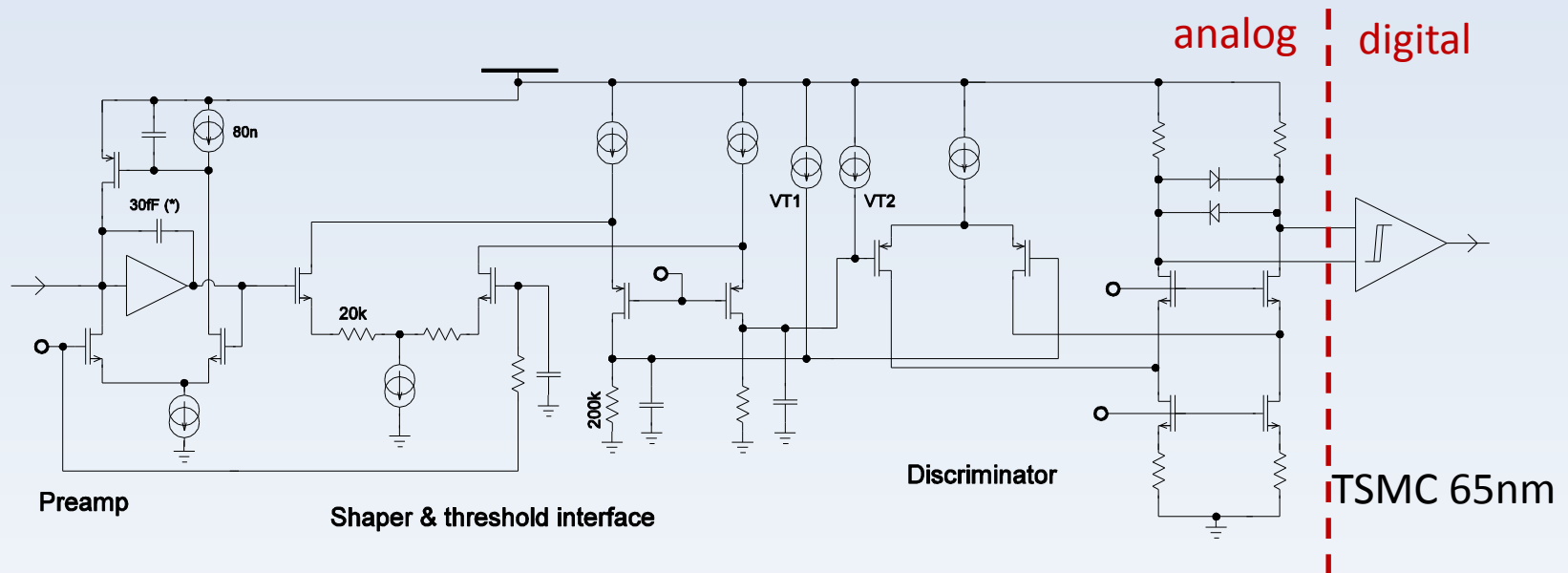

- Higher gain in the preamp ( $C_{in} < 0.5\text{pF}$ ) → no need for booster
- Second stage DC coupled: folded cascode with resistive load and degeneration (NMOS input possible because of DC output stabilization) → still one low freq. zero in transfer function from Krummenacher
- 3 stage discriminator
- Power per channel  $\sim 35\mu\text{W}$
- Peaking time 24ns, ENC with detectors  $< 200e^-$ , gain 85-90mV/fC




# Booster amplifiers: requirements

- For 20ns peaking time shaper and 10V/V gain:
  - open loop gain above 40dB
  - GBP above 250MHz



# Booster (ABCStar)

 


GF 130nm

- Folded cascode with PMOS input (to match DC from preamp) with zero VT NMOS
- open loop gain 48dB/280MHz GBP
- Consumption: 50uA




# Booster (SSA)

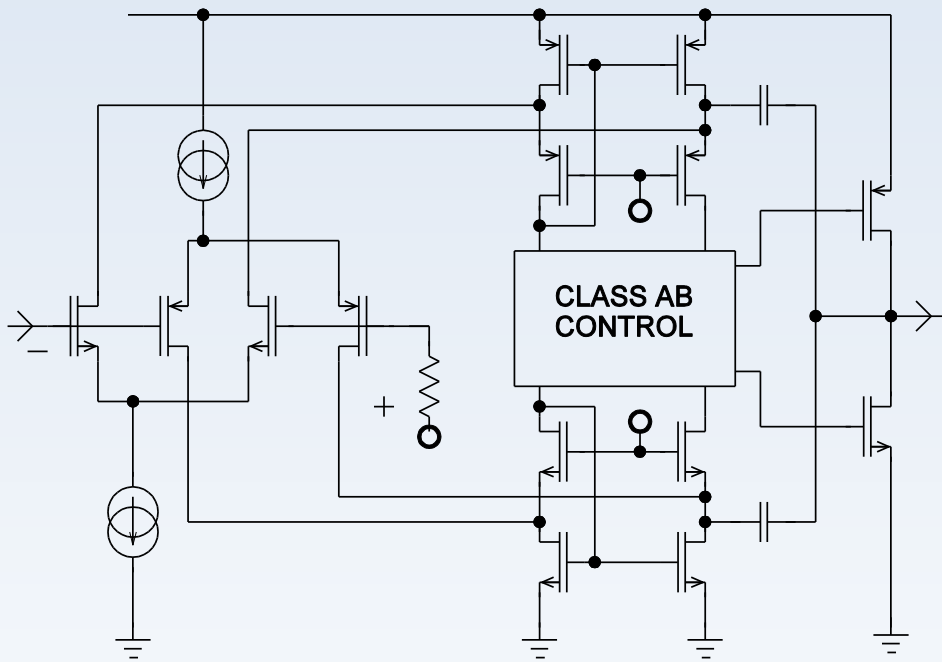

TSMC 65nm

 - Classical RtR amplifier with class AB output stage
- open loop gain 60dB/400MHz GBP
- Consumption: 35uA



# Summary

- Presented selection of circuit is limited to the new designs for upgraded ATLAS and CMS
- Clear tendency to use telescopic cascodes (standard or regulated) with NMOS input device
- Binary architecture in all designs