



Update On Powering Of Inner Triplet Circuit

Hugues Thiesen – Samer Yammine on behalf of HL-MCF

6th HL-LHC Collaboration Meeting

15 November 2016

Paris, Espace St Martin

Input from contributors of the Magnet Circuit Forum: Felix Rodriguez Mateos, Emmanuele Ravaioli, Susana Izquierdo, WP2, WP3, WP6a, WP6b, WP7, WP9, WP15, WP16, WP17

<https://espace.cern.ch/project-HL-LHC-Technical-coordination/MCF>




Contents

- 01** HL-LHC Inner Triplet Circuits
- 02** Powering of the Main Quadrupole Circuit
- 03** Quench Protection of the Main Quadrupole Circuit
- 04** Conclusion


01

HL-LHC Inner Triplet Circuits

HL-LHC Magnet and Circuit Layout

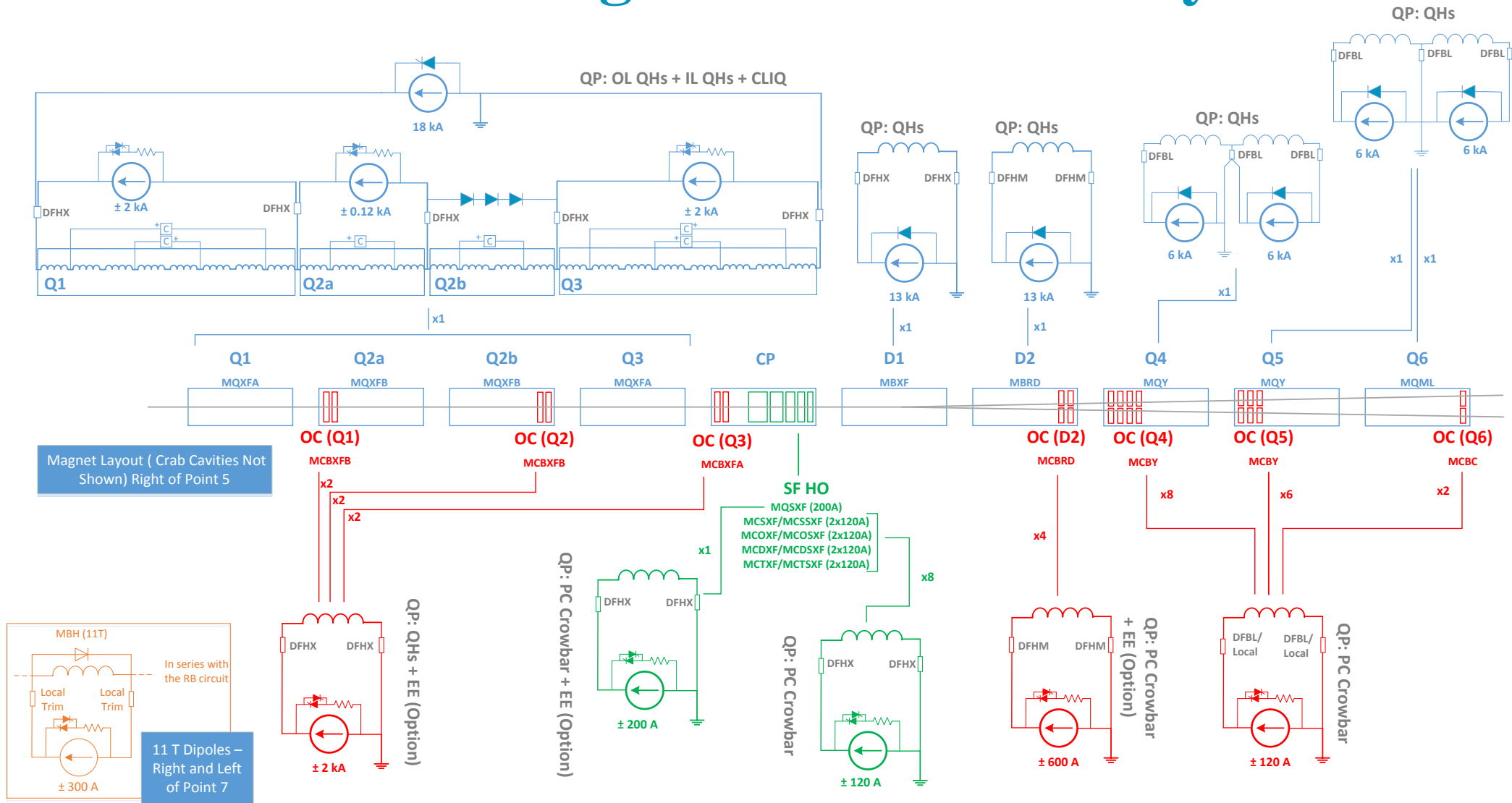

HL-LHC Inner Triplet Circuits

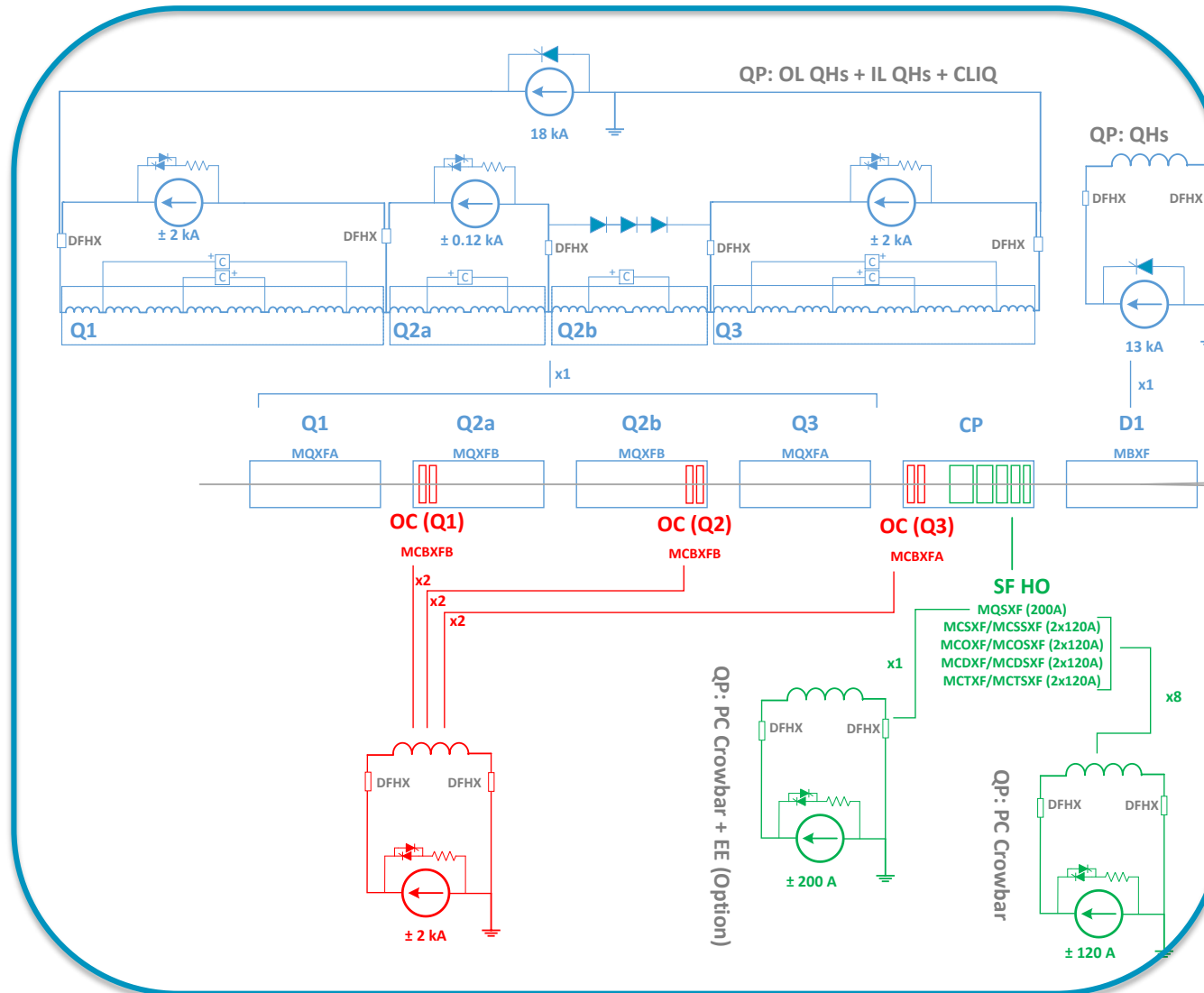

Definition:

- All circuits powered by the DFHX

Main Circuits:


- Main quadrupole circuit: Q1, Q2a, Q2b, Q3
- D1 circuit

Orbit Correctors of MQ:



- MCBX

Superferric High Order Correctors

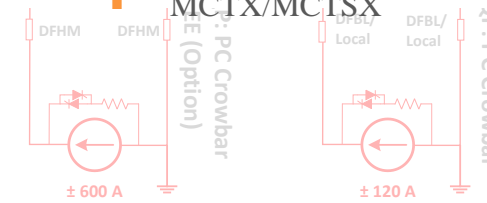- MQSX
- MCSX/MCSSX
- MCOX/MCOSX
- MCDX/MCDSX
- MCTX/MCTSX



HL-LHC Inner Triplet Circuits

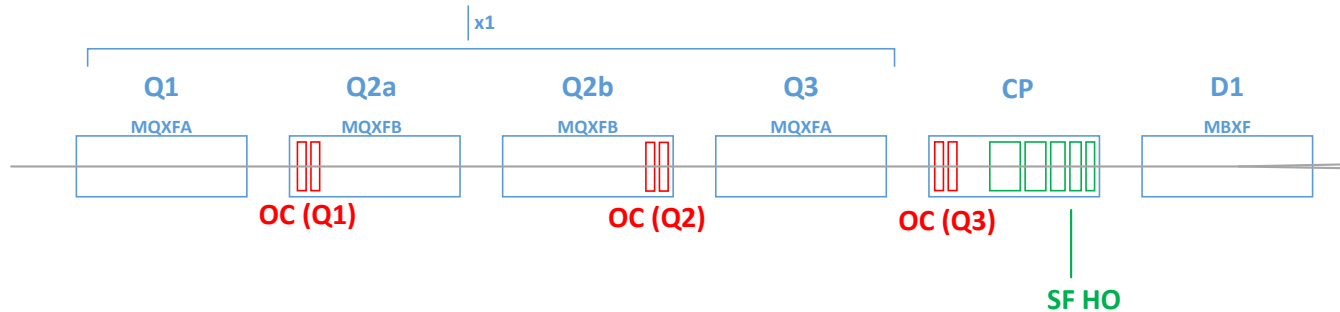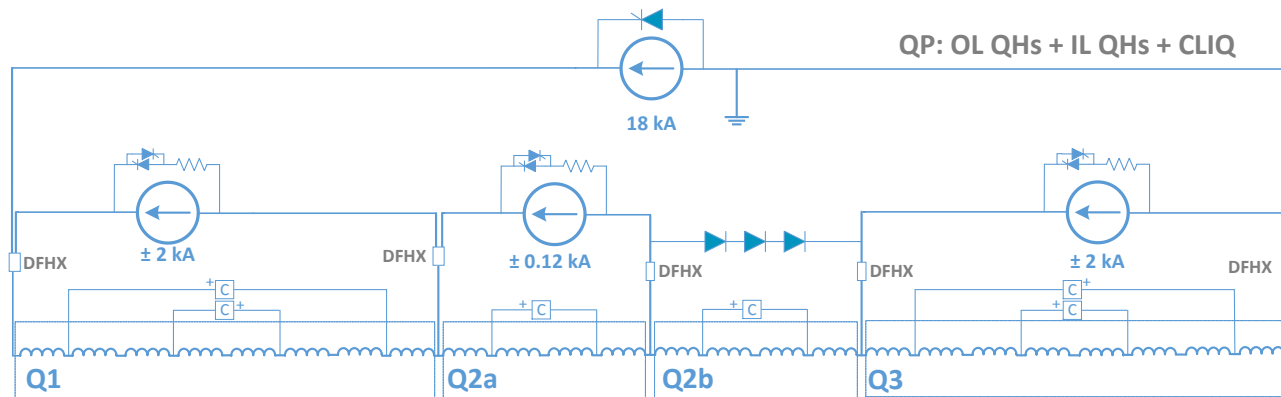


MQ Circuits:

- 1 main circuits per IP
 - 18 kA / Unipolar in Current – 2Q
- 3 trim circuits par IP
 - 2 x 2 kA / Bipolar in Current – 4Q (Q1 and Q3)
 - 1 x 0.12 kA / Bipolar in Current – 4Q (Q2a)

Magnet Protection (E = 41 MJ):

- Outer Layer Quench Heaters
- CLIQs
- Inner Layer Quench Heaters

HL-LHC Inner Triplet Circuits

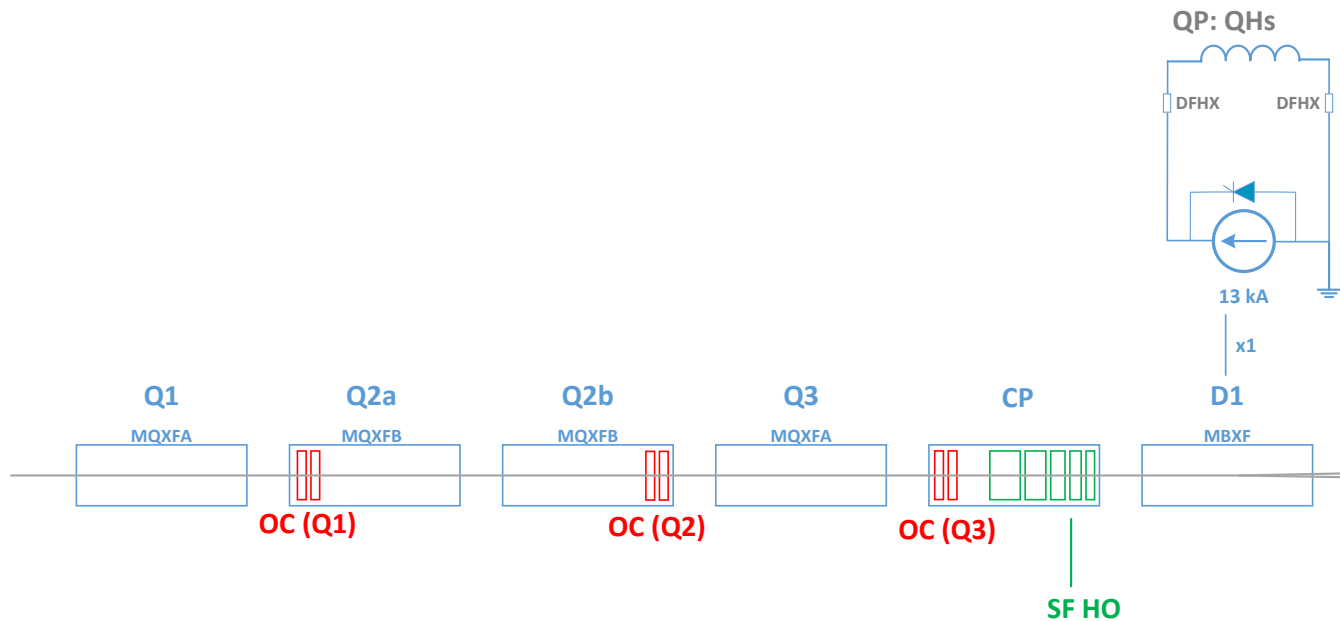


■ D1 Circuits:

- 1 circuits per IP
- 13 kA / Unipolar in Current – 1Q

■ Magnet Protection:

- Quench Heaters ($E = 2.3 \text{ MJ}$)

HL-LHC Inner Triplet Circuits

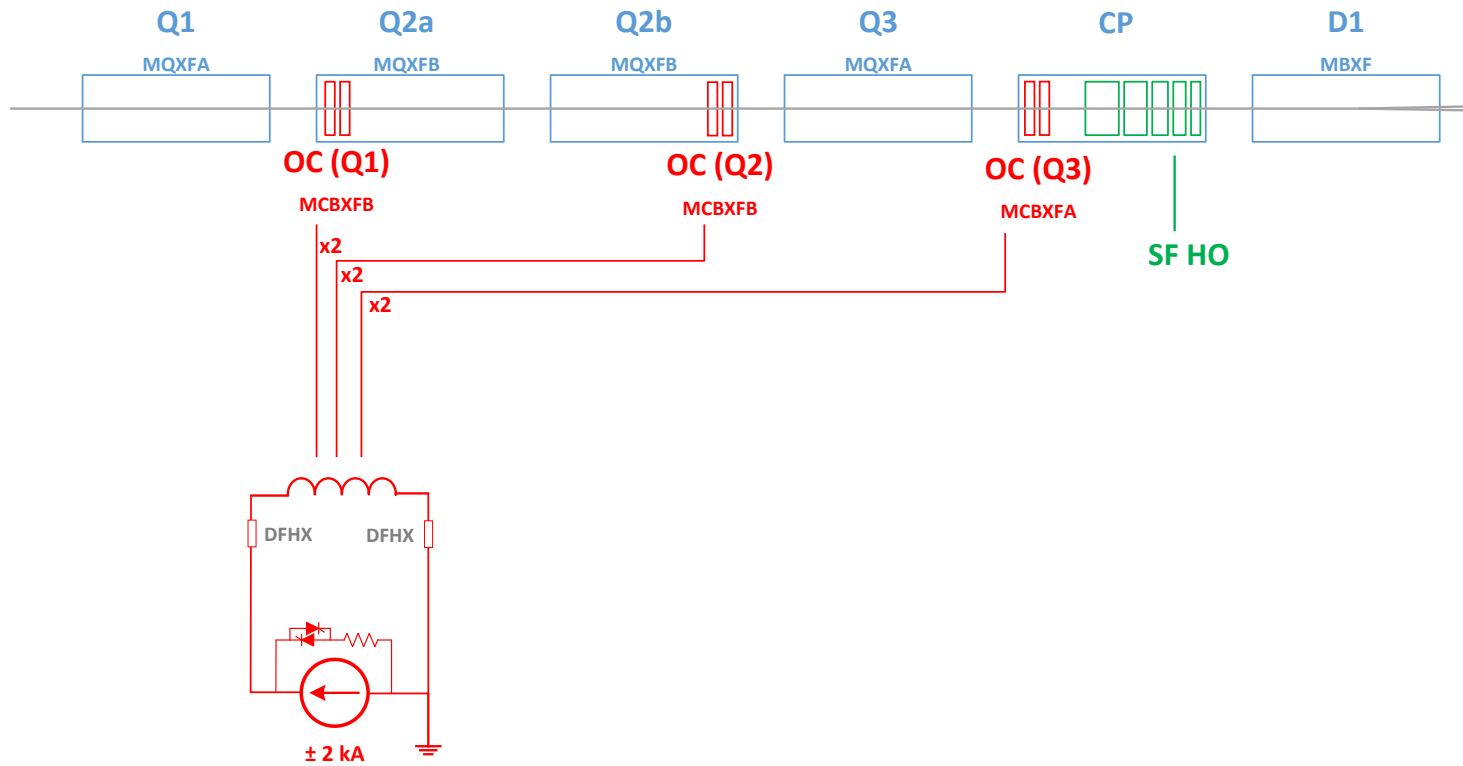


- Orbit Corrector Circuits:

- 6 circuits per IP
- 2 kA / Bipolar in Current – 4Q

- Magnet Protection:


- Quench Heater (baseline)
- Energy Extraction (Option – 90 to 320 kJ)

HL-LHC Inner Triplet Circuits

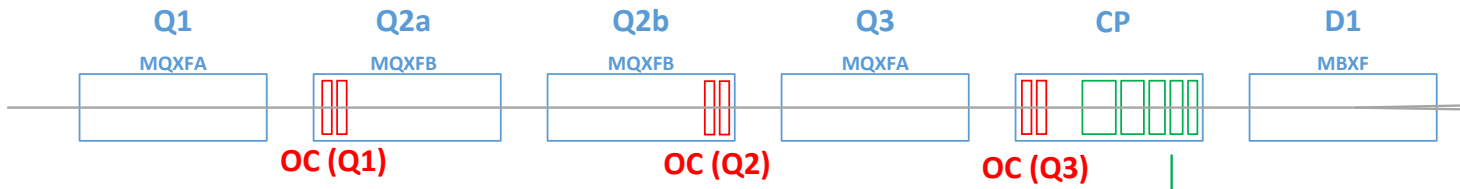

- SHOC Circuits:
 - 9 circuits per IP
 - 0.12 or 0.2 kA / Bipolar in Current – 4Q

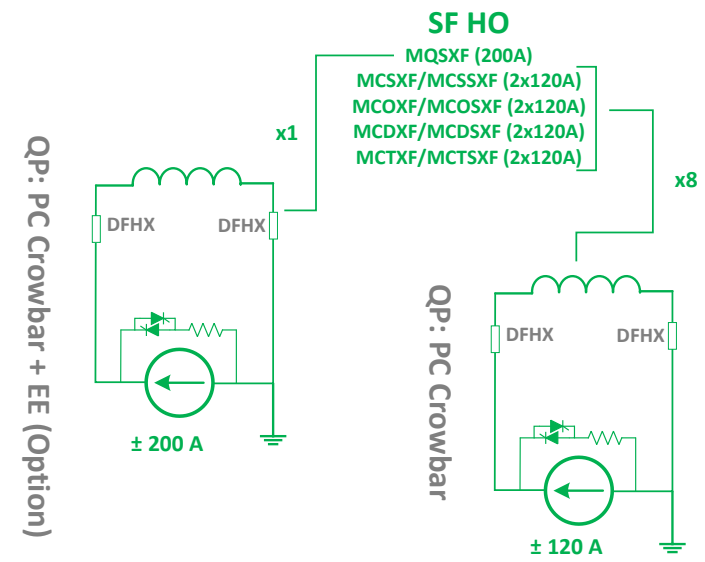- Magnet Protection:
 - PC crowbar ($E < 2$ kJ)
 - Energy Extraction (Option)



HL-LHC Inner Triplet Circuits


Circuits for HiLumi	Magnet Type	Number of circuits per IP side	I _{nominal} (7 TeV) [kA]	I _{ultimate} [kA]	L per circuit [mH]	R per circuit [mΩ]	Time constant [s]	E [kJ]	Protection
Triplet Q1, Q2a, Q2b, Q3	MQXFA / MQFXB	1	16.5	17.82	255	0.264	965.91	40487.9	OQH + CLIQ + IQH
Trim Q1	-	1	2	2	69	1.44	47.92		
Trim Q3	-	1	2	2	69	1.44	47.92		
Trim Q2a	-	1	0.12	0.12	58.5	13.372	4.37		
Orbit correctors Q2a/b - vertical	MCBXFB	2	1.6	1.73	59	1.512	39.02	88.3	QH (+ EE)
Orbit correctors Q2a/b - horizontal	MCBXFB	2	1.47	1.59	135	1.656	81.52	170.6	QH (+ EE)
Orbit correctors CP - vertical	MCBXFA	1	1.6	1.73	109	1.728	63.08	163.1	QH (+ EE)
Orbit correctors CP - horizontal	MCBXFA	1	1.47	1.59	247	1.728	142.94	312.2	QH (+ EE)
Superferric, order 2	MQSXF	1	0.182	0.2	1247	9.853	126.56	24.9	PCC
Superferric, order 3, normal and skew	MCSXF / MCSSXF	2	0.105	0.12	118	13.372	8.82	0.8	PCC
Superferric, order 4, normal and skew	MCOXF / MCOSXF	2	0.105	0.12	152	13.372	11.37	1.1	PCC
Superferric, order 5, normal and skew	MCDXF / MCDSXF	2	0.105	0.12	107	13.372	8.00	0.8	PCC
Superferric, order 6	MCTXF	1	0.105	0.12	229	13.372	17.13	1.6	PCC
Superferric, order 6, skew	MCTSXF	1	0.105	0.12	52	13.372	3.89	0.4	PCC
Separation dipole D1	MBXF	1	12	12.96	27	0.27	100.00	2267.5	QH

02

Powering of the Main Quadrupoles Circuit



Power Converters for the MQ Circuit

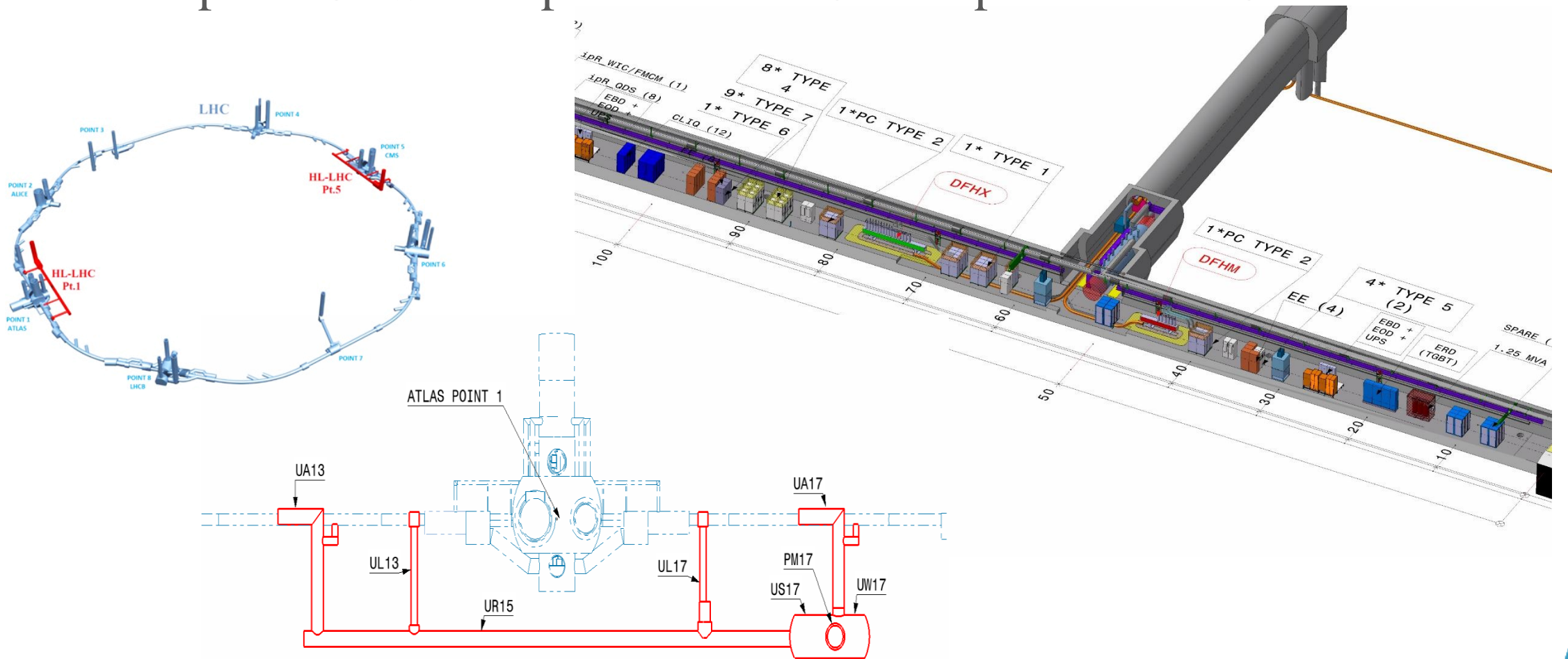- Inner triplet PCs will be placed in the URs at points 1 and 5




Cold Powering of the MQ Circuit

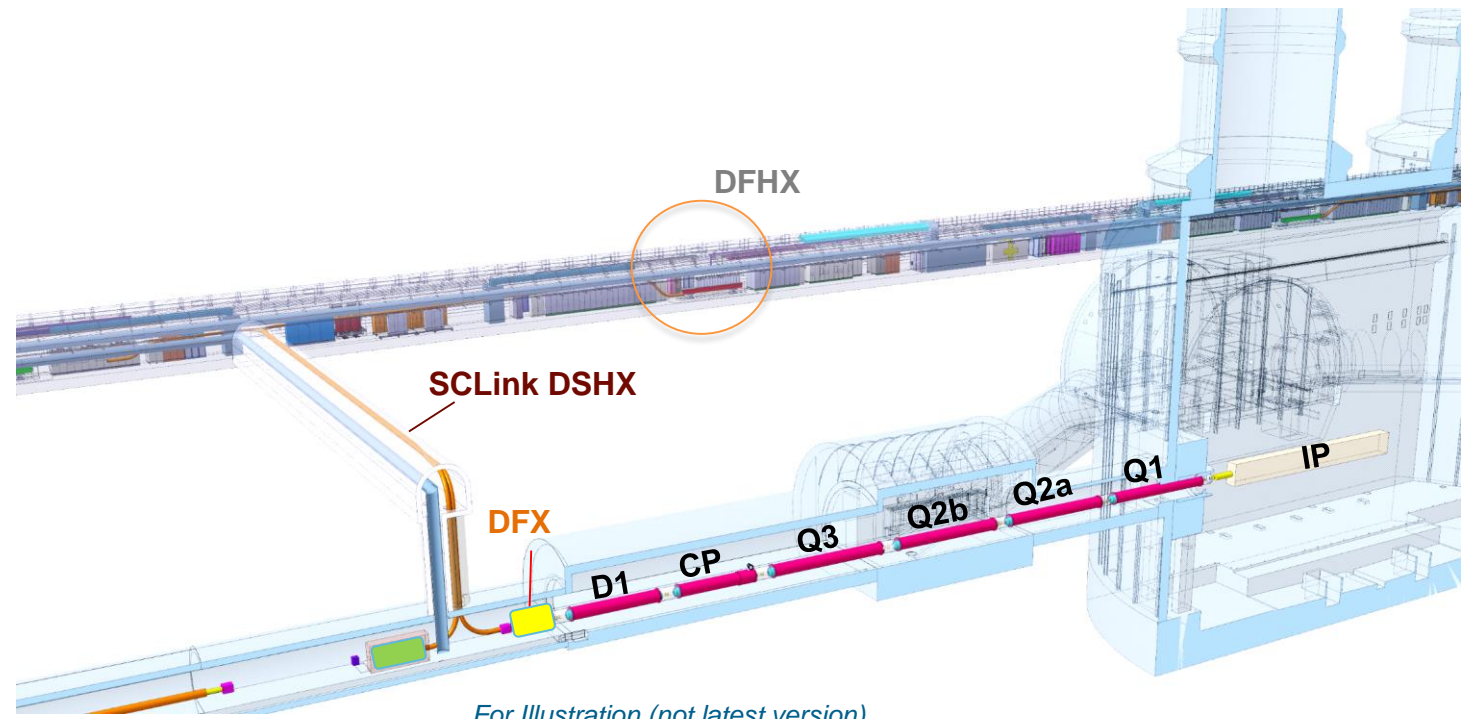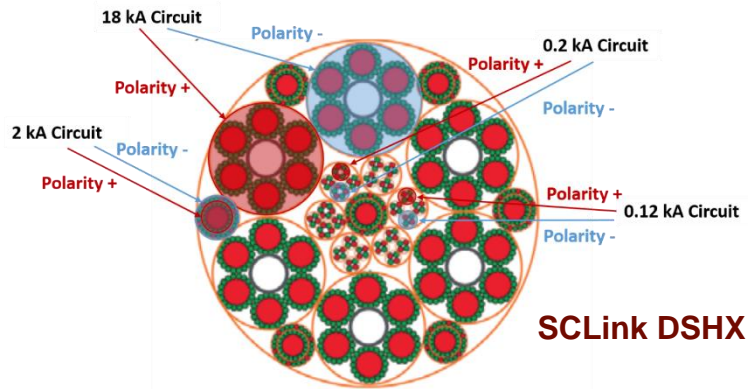- PCs → DFHX → DSH (SC Link) → DFX → Magnets (via busbars)




Cold Powering of the MQ Circuit

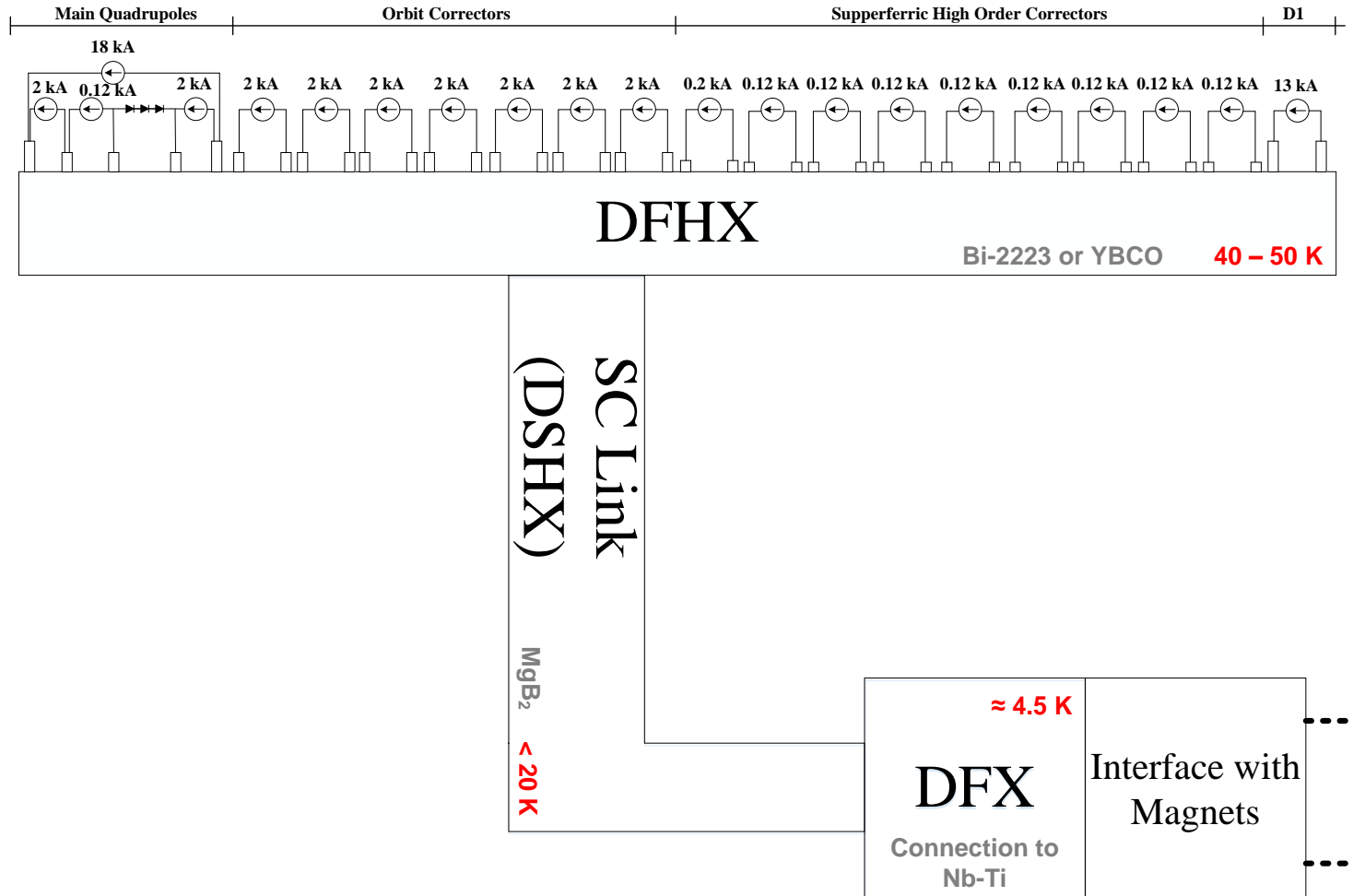

Gas Helium Cooling in DFHX
and DSHX
Liquid Helium Cooling in DFX

Powering of the MQ Circuit

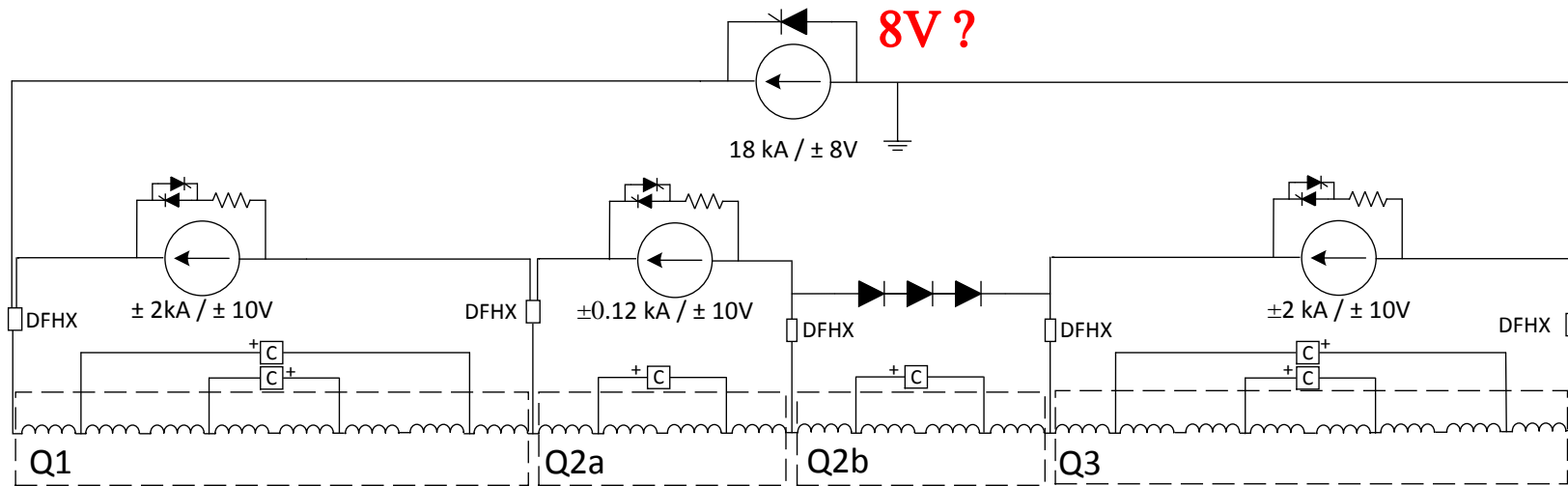


- 1 Main Power Converter:
 - Q1, Q2a, Q2b and Q3 powered in series
 - [18 kA / ± 8 V]
- 3 Trim Power Converters:
 - 2 x [± 2 kA / ± 10V] (Q1 and Q3)
 - 1 x [± 0.12 kA / ± 10V] (Q2a)
- $\tau = 1$ ks
- Total Energy of 41 MJ
- Warm Diodes over Q2b for Quench Protection (not necessary for warm powering)

Circuits for HiLumi	Magnet Type	I _{nom} (7 TeV) [kA]	I _{ultimate} [kA]	L per circuit [mH]	R per circuit [mΩ]	Time constant [s]	di/dt* [A/s]	V _{PC} [V]	E [kJ]	R Crowbar [mW]
MQ (Q1, Q2a, Q2b, Q3)	MQXFA / MQFXB	16.5	17.82	255	0.264	965.91	13.8	±8.2	40488	?
Trim Q1	MQXFA	2	±2	69	1.44	47.92	1.5	±3.9	10956	tbd
Trim Q3	MQXFA	2	±2	69	1.44	47.92	1.5	±3.9	10956	tbd
Trim Q2a	MQXFB	0.12	±0.12	58.5	13.372	4.37	0.1	±2.4	9288	tbd
Q2b	MQXFB			58.5			13.8	±0.8	9288	

* Estimated value to be verified by WP2

Powering of the MQ Circuit


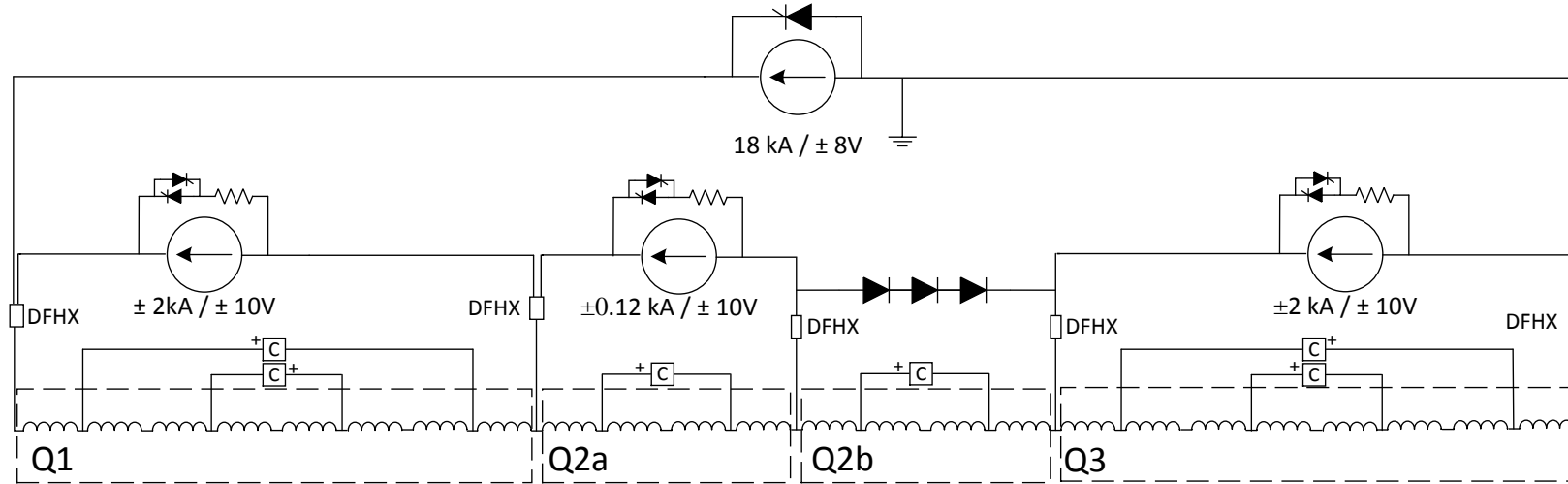
- Maximum Output Voltage of Power Converters



$$\begin{aligned}
 V_{qx} &= R_{qx} * I_{qx} & + L_{qx} * didt_{qx} & & + L_{q1} * didt_{q1} & + L_{q2a} * didt_{q2a} & + L_{q3} * didt_{q3} & \sim 8.2 \text{ V} \\
 V_{q1} &= R_{q1} * I_{q1} & + L_{q1} * didt_{q1} & & + L_{q1} * didt_{qx} & & & \sim 3.9 \text{ V} \\
 V_{q2a} &= R_{q2a} * I_{q2a} & + L_{q2a} * didt_{q2a} & & + L_{q2a} * didt_{qx} & & & \sim 2.4 \text{ V} \\
 V_{q3} &= R_{q3} * I_{q3} & + L_{q3} * didt_{q1} & & + L_{q3} * didt_{qx} & & & \sim 3.9 \text{ V} \\
 V_{q2b} &= & & & + L_{q2b} * didt_{qx} & & & \sim 0.8 \text{ V}
 \end{aligned}$$

Powering of the MQ Circuit

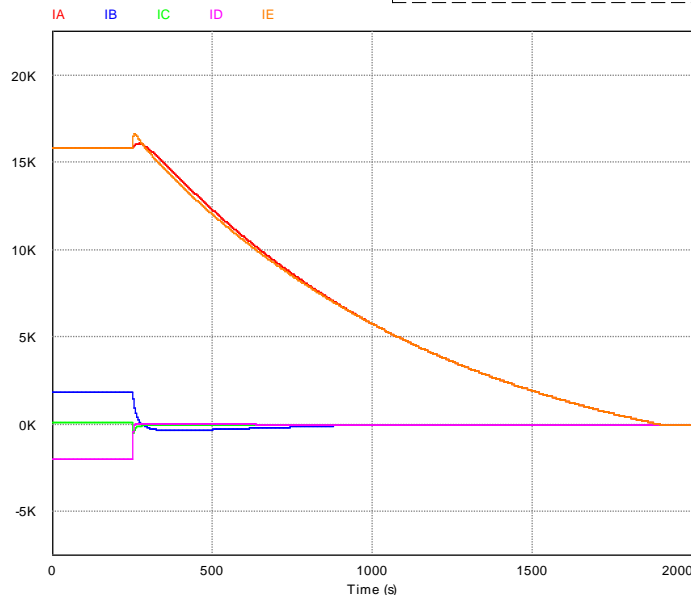
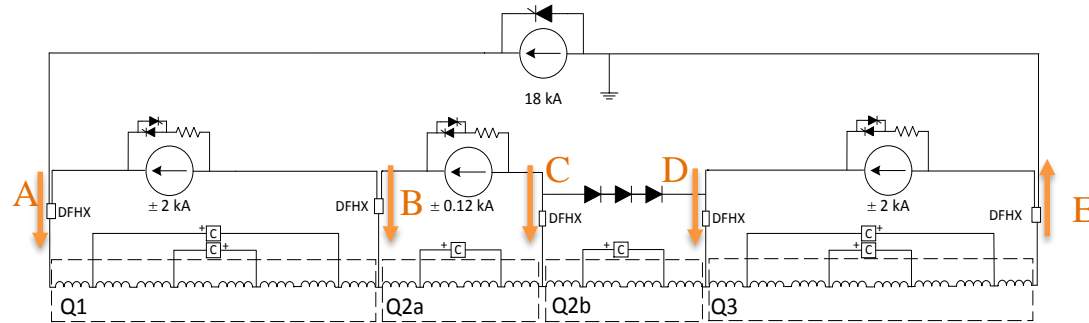
- Powering Failure Simulation (No Quench)




- No Looping Current in Trim Circuits Even if Crowbar Resistances = 0 due to Relatively High Trim Cable Resistance:
 - $R_{cableQX} = 0.264$ m Ω
 - $R_{cableQ1} = 1.44$ m Ω
 - $R_{cableQ2a} = 13.4$ m Ω
 - $R_{cableQ3} = 1.44$ m Ω

Powering of the MQ Circuit

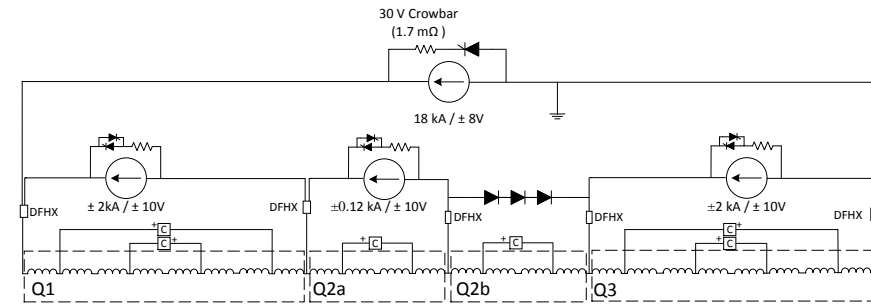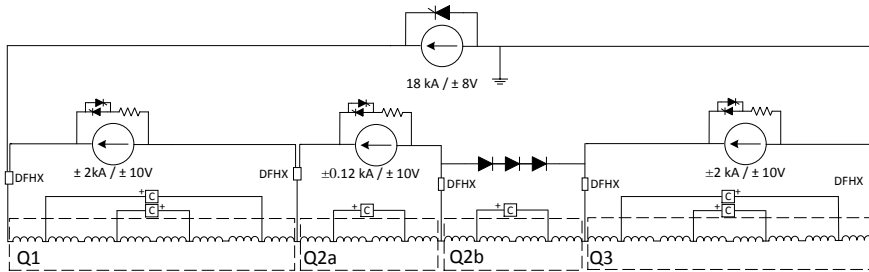Water Failure and Main Converter Crowbar Resistance




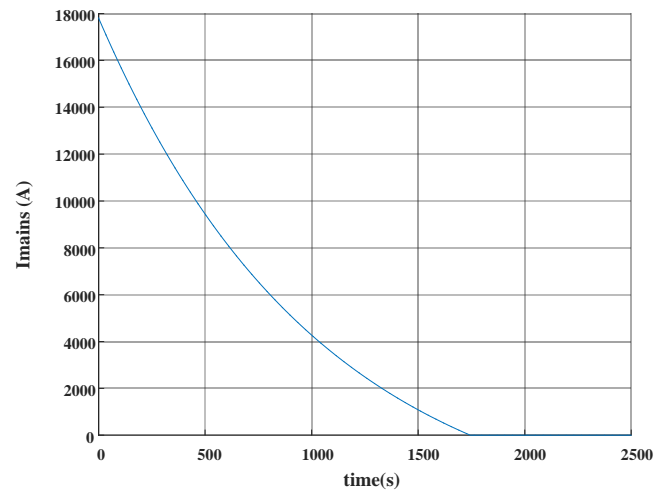Discharge of the MQ Circuit without Quench / $R_{crow} = 0 \text{ m}\Omega$



Introduction of 30 V Crowbar Resistance

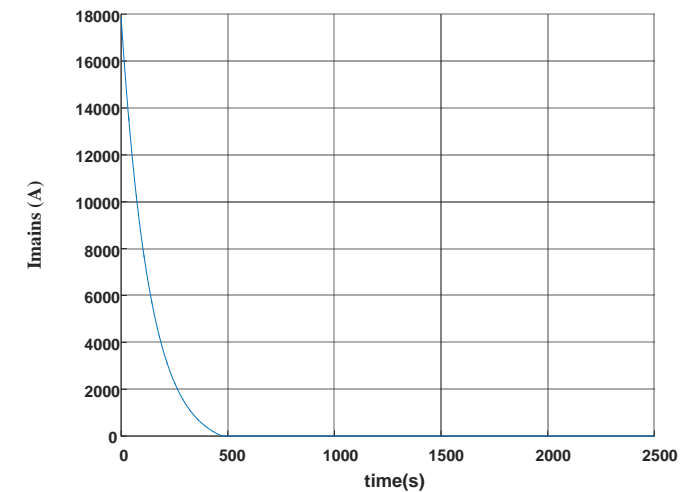Discharge of the MQ Circuit without Quench / $R_{crow} = 1.7 \text{ m}\Omega$



- Energy Dissipated in Free-Wheeling Thyristor = 11.5 MJ
- Energy Dissipated in DC Cables = 30 MJ → $\Delta T = 86 \text{ }^\circ\text{C}$ in case of water failure

- Energy Dissipated in Free-Wheeling Thyristor = 2.12 MJ
- Energy Dissipated in DC Cables = 5 MJ → $\Delta T = 15 \text{ }^\circ\text{C}$ in case of water failure
- Energy Dissipated in Crowbar Resistance = 34 MJ

03

Quench Protection of the Main Quadrupole Circuit


Quench Protection of the MQ circuit

- Outer layer (OL) quench heaters
 - In the baseline
 - Can protect the magnet at all current levels ($T_{\max}=320$ K) and provide some redundancy.
- Inner layer (IL) heaters
 - In the baseline
 - In combination with the OL quench heaters, the hot spot temperature can be reduced by 90 K ($T_{\max}=230$ K).
 - Work in progress to address issues of reliability (linked to coil manufacturing).
- CLIQ
 - In the baseline
 - In combination with the OL quench heaters, the hot spot temperature can be reduced by 90 K ($T_{\max}=230$ K)
 - Work in progress to address open questions:
 - Assess the long-time reliability and availability
 - Impact on other elements of the circuit, for instance the superconducting link.

Quench Protection of the MQ circuit


- Quench heaters (OL or IL)

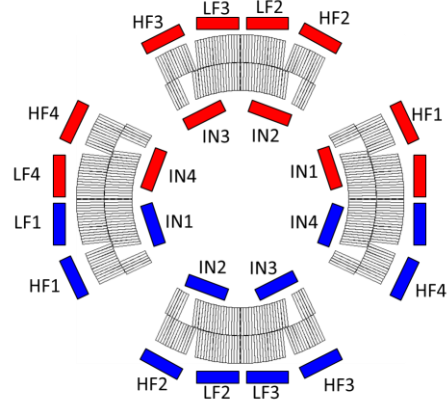- Quench provoked by thermal diffusion.
- Electrically separated from the coils.




- CLIQ

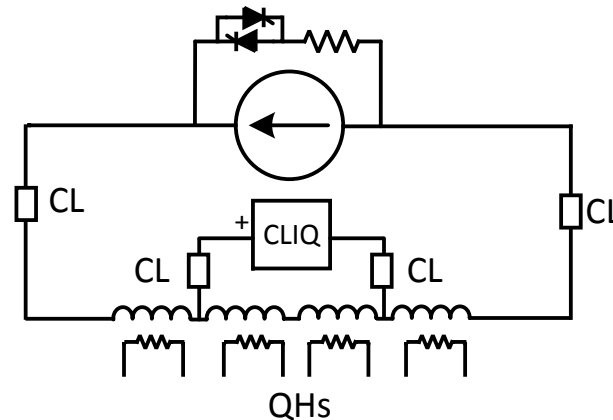- Quench propagation by current oscillations.
- Electrical interaction with the powering circuit (warm and cold)



Quench Protection of the MQ circuit

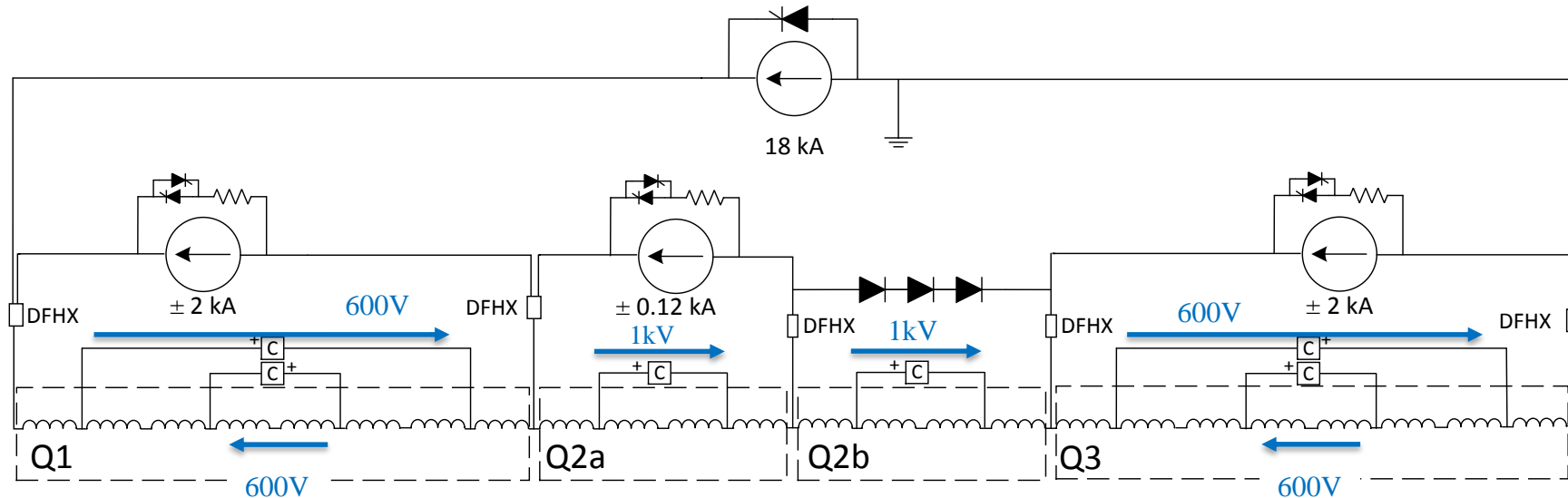- CLIQ
 - 2 x 600V CLIQ units per MQXFA magnet
 - 1 x 1 kV CLIQ units per MQXFB magnet




- 2 magnets in series
- 300 V per pole

- 1 magnet
- 500 V per pole

- 2 magnets in series
- 300 V per pole

Quench Protection of the MQ circuit

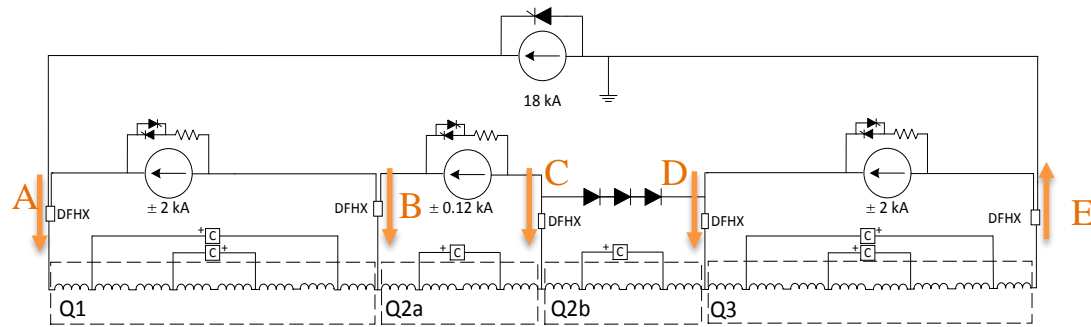- Quench Simulations: Synchronised Quench without Initial Trim Currents





$$I_{ms} = 16.5 \text{ kA}$$

$$I_{ts1} = 0 \text{ A}$$

$$I_{ts2a} = 0 \text{ A}$$


$$I_{ts3} = 0 \text{ A}$$

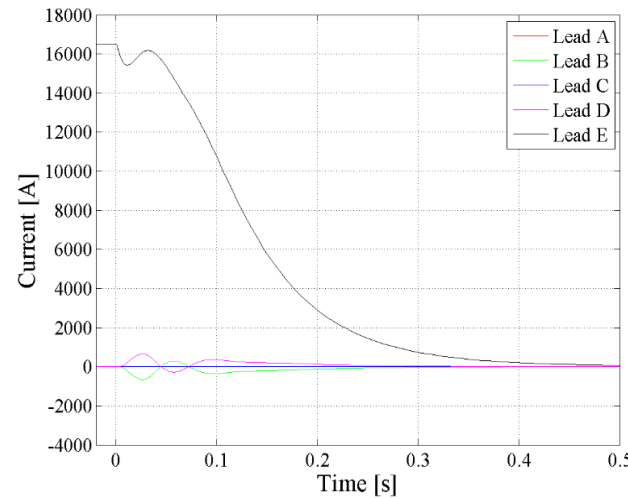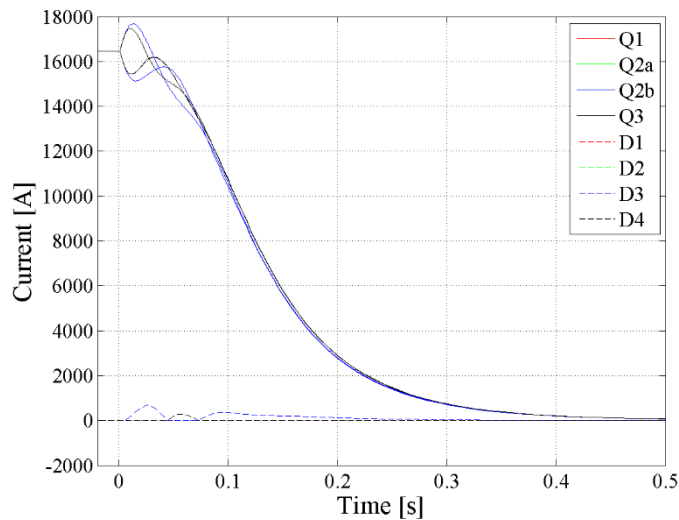



- The behaviour of the magnets are similar (Quench resistance development)
- No issue if the quenches of the 4 MQ are synchronised
- No over-current through leads

Quench Protection of the MQ circuit

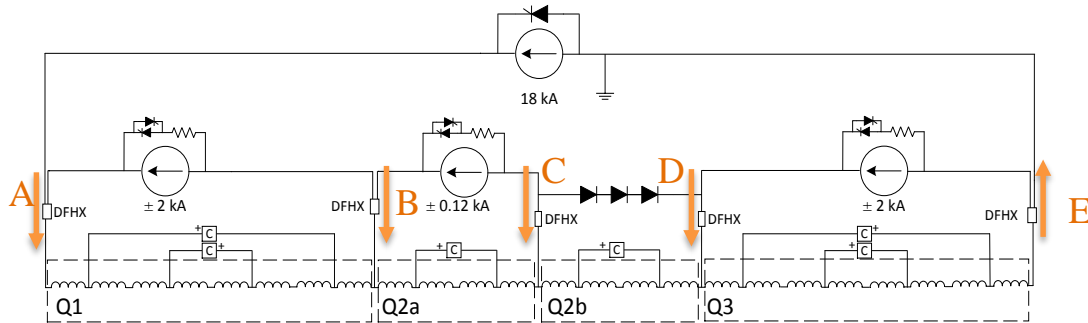- Quench Simulations: Synchronised Quench with Initial Trim Currents


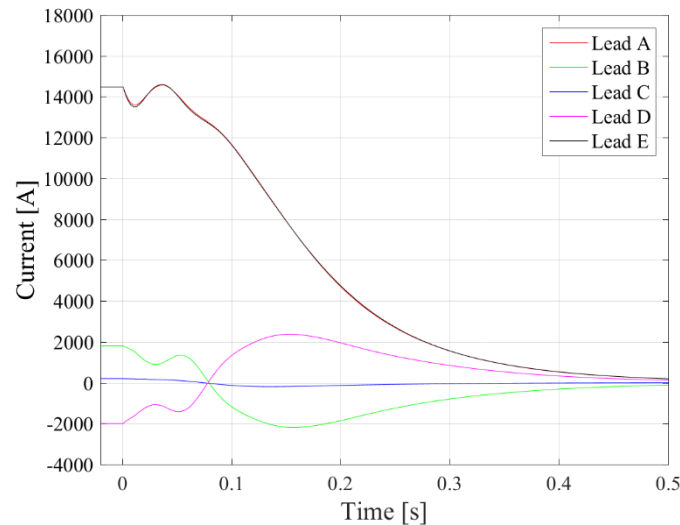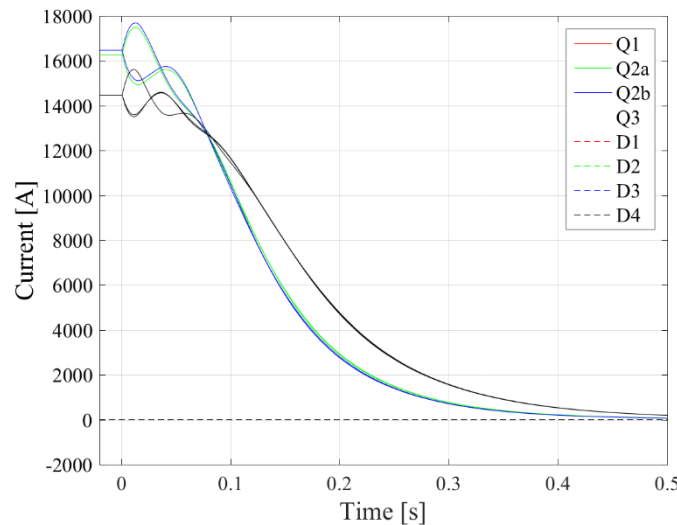
$$\begin{aligned}
 I_{ms} &= 16.5 \text{ kA} \\
 I_{ts1} &= -2 \text{ kA} \\
 I_{ts2a} &= -0.12 \text{ kA} \\
 I_{ts3} &= -2 \text{ kA}
 \end{aligned}$$




Currents estimated through the SC Link/Leads:

- Leads B and D see 2 kA
- Lead C sees 0.1 kA


Quench Protection of the MQ circuit

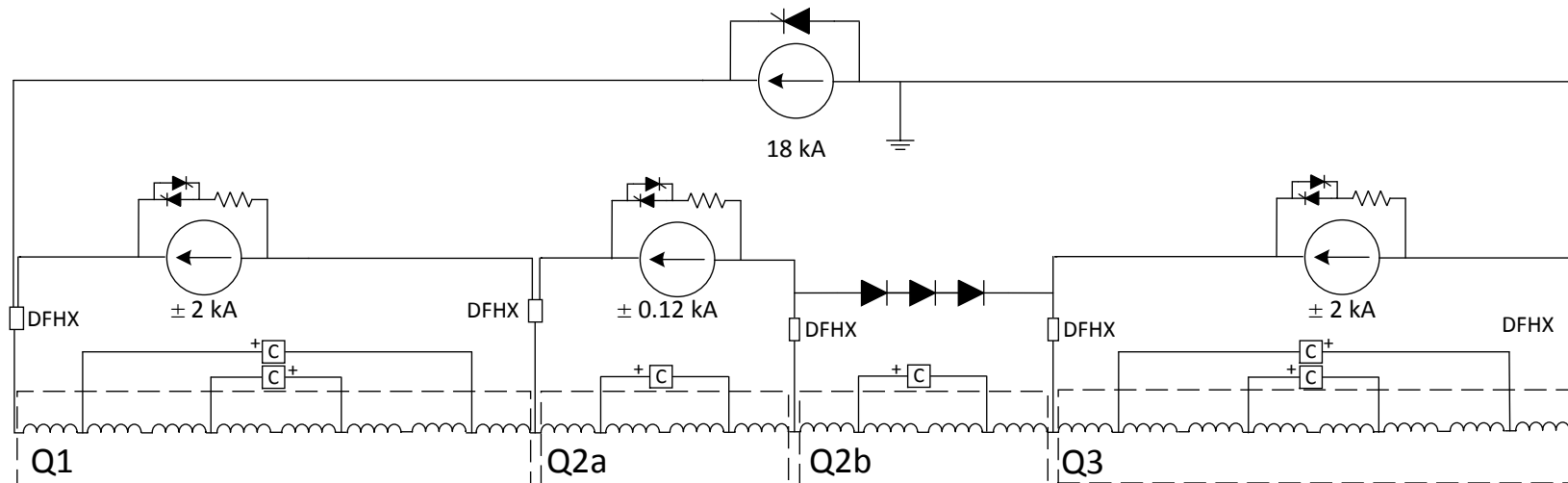- Quench Simulations: Worst Case Scenario Considered (Conservative Case)
 - Case of the non-detection of a quench is not considered
 - The case considered is one full magnet (i.e. 4 poles) quenches by effect of beam
 - Quench protection system needs:
 - 15 ms to detect the quenchion
 - +1 ms to fire the CLIQ modules (16 ms after the quench)
 - +5 ms to fire the QH (20 ms after the quench)



Quench Protection of the MQ circuit

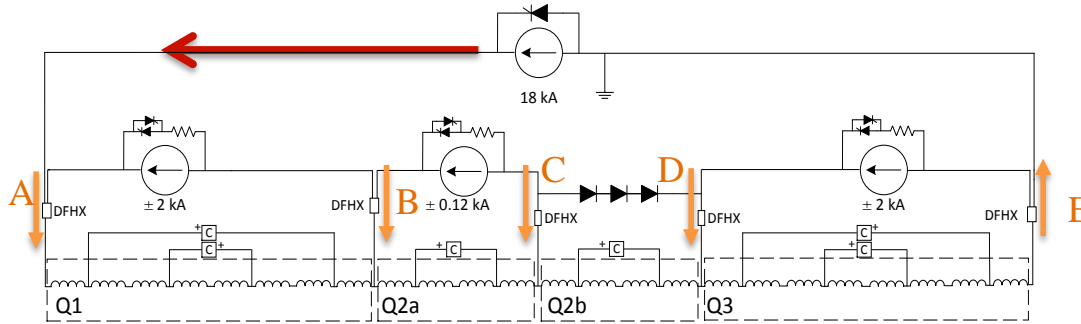- Quench Simulations: Worst Case Scenario Considered





$$I_{ms} = 16.5 \text{ kA}$$

$$I_{ts1} = -2 \text{ kA}$$

$$I_{ts2a} = -0.12 \text{ kA}$$


$$I_{ts3} = -2 \text{ kA}$$

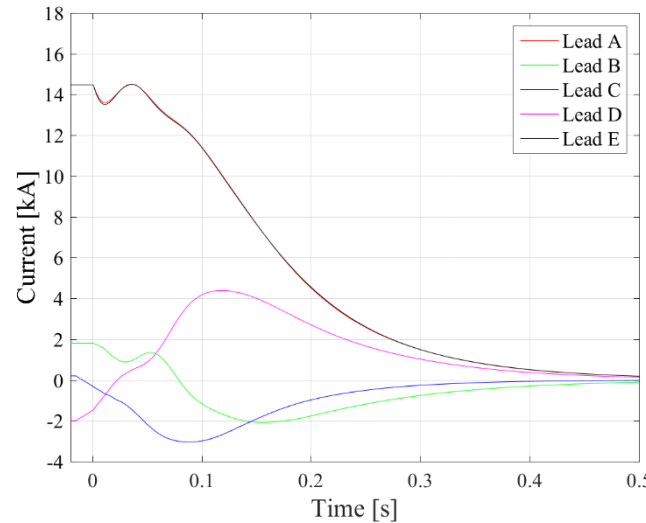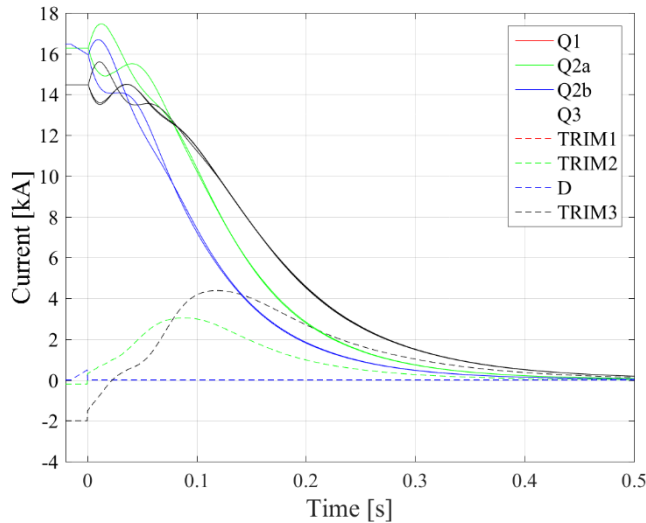

- High overcurrent through the SC Link/Leads:
- Leads B and D see 4.4 kA for an eq. time = 120 ms
 - Lead C sees 3.2 kA for an eq. time = 100 ms



Quench Protection of the MQ circuit

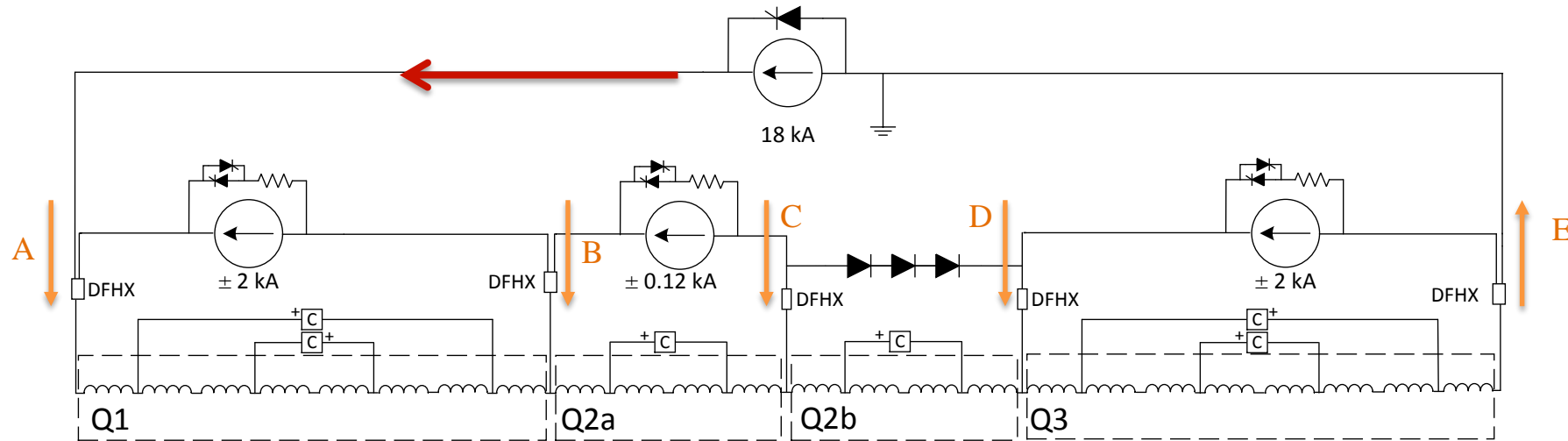- Quench Simulations: Worst Case Scenario Considered
 - Attempt 1 to reduce the currents through the leads: Increasing the crowbar resistances



$R_{\text{crow}Q1} = 15 \text{ m}\Omega$
 $R_{\text{crow}Q2a} = 80 \text{ m}\Omega$
 $R_{\text{crow}Q2b} = 80 \text{ m}\Omega$
 $R_{\text{crow}Q3} = 15 \text{ m}\Omega$

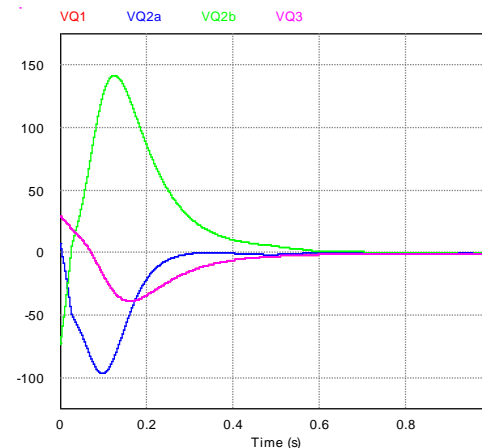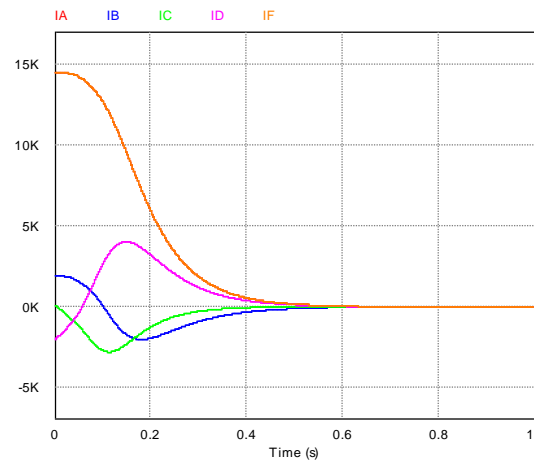
$I_{\text{ms}} = 16.5 \text{ kA}$
 $I_{\text{ts1}} = -2 \text{ kA}$
 $I_{\text{ts2a}} = -0.12 \text{ kA}$
 $I_{\text{ts3}} = -2 \text{ kA}$



Maximum current decrease of less than 200A in the trim circuits → Low impact (MIITS and current peaks)



Quench Protection of the MQ circuit

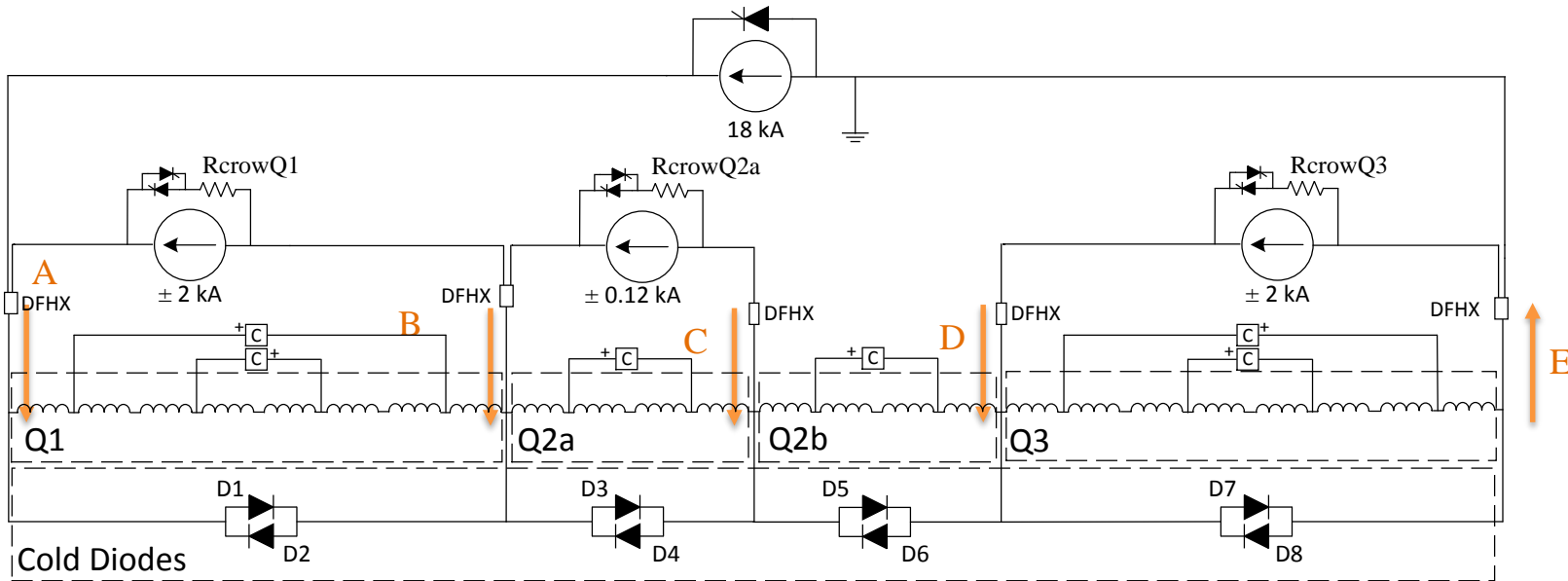- Quench Simulations: Worst Case Scenario Considered
 - Attempt 2 to reduce the currents through the leads: Introducing cold diodes



$R_{crowQ1} = 15 \text{ m}\Omega$
 $R_{crowQ2a} = 80 \text{ m}\Omega$
 $R_{crowQ3} = 15 \text{ m}\Omega$
 Diode $V_f = 6 \text{ V}$

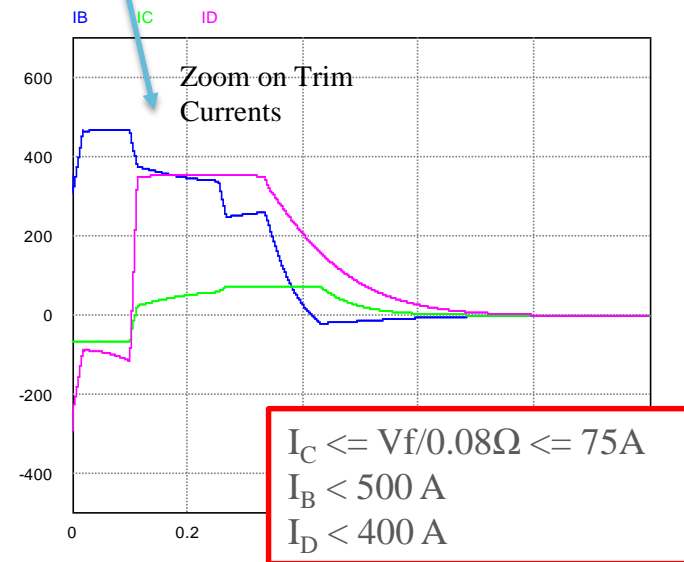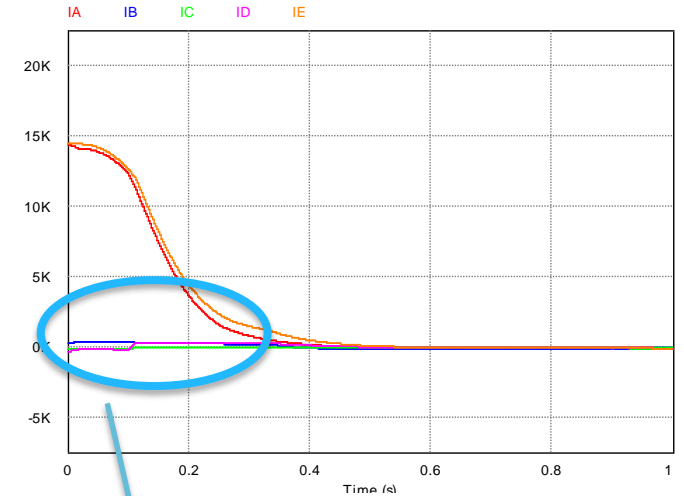$I_{ms} = 16.5 \text{ kA}$
 $I_{ts1} = -2 \text{ kA}$
 $I_{ts2a} = -0.12 \text{ kA}$
 $I_{ts3} = -2 \text{ kA}$



Cold diodes Status

- Long development programme was conducted for the LHC
- Design aspects:
 - Radiation tolerance
 - Electrical properties (turn-on, forward and reverse voltage characteristics)
 - Thermal property (endurance for long time constants and long term behavior)
 - Cryogenic temperature operation
- Main issue for inner triplet diode integration: Radiation tolerance
 - Radiation resistance limit for the LHC diode (diffusion type): **~2 kGy, 10^{13} n.cm⁻²**
 - Epitaxial diodes (tested more than 20 years ago) up to **~ 50 kGy, 10^{15} n.cm⁻²**
 - Studies interrupted when revised (much lower) radiation calculations were presented, together with the success with diffusion diodes
 - Needed to stack them to have sufficient margin for ramping, had reduced reverse voltage capabilities and were much more expensive

Proposed Solutions

- These results are being confirmed at present
- If results are confirmed, two solutions could be considered:
 - Cold diodes with present equipment design
 - More compact than dipole diodes since time constants are 1000 times lower
 - Studies undergoing for radiation exposure in the inner triplet zone (till the DFX)
 - Complex integration
 - Redesign of equipment to withstand the high transitory over-currents
 - Over-currents of 2-3 kA in leads for an equivalent time of 100-150 ms
- Adding a resistance in the crowbar of the main converter may have implications to be analyzed.
- Final layout due date: End of the 2016 in the MCF

04

Conclusion

Conclusion

- IT circuits powering scheme has been presented
- IT main quadrupole circuit is complex due to its interconnectivity
- Circuit layout definition is in final stage
- Protection scheme to be finalized when tests are done
- For quench detection and protection instrumentation, see R. Denz's talk



Thanks for your attention

