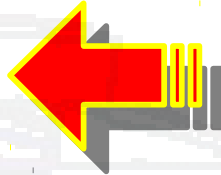


Introduction to the Design of Full-Custom Front-End & Data Transmission ASICs*

Table of Contents

■ The Big (but Brief) Picture

- Briefly **front-end** - FE
- Briefly **read-out** - RO
- Briefly **serializer** - SER
- Briefly **phase-lock loop** - PLL



■ Feed-Back Concept

- A **qualitative** introduction
- **Natural frequency** concept - ω_n
- Real-world examples:
 - **Binary** read-out
 - **Time-over threshold**
- Adjusting/optimizing loop behavior
 - **Damping ratio**

■ Reminder on Detectors

- Photodetectors **vs** photon counters
- **Position-sensitive** detectors
 - Resistive charge division
 - Discrete array of elements
- **Time-resolved** detection

■ Detector Front-End ASICs

- **Pre-Amp**: basic idea - V_{OUT} / V_{IN}
- **Transconductance** of a transistor - g_m
- Evolving a **single-stage amplifier** into a real-world application

■ Processing Technology

- **Transistor** switch – A masterpiece
 - **Lithography**
 - Formation of an **nMOS** transistor
- VLSI design flow
 - Parasitic **extraction**
- Real-world ASIC examples

■ Radiation Tolerance Issues

- Definitions:
 - **Single event upset, analog**
 - **single event transient, latch-up**
- **Simulating** radiation effects on analog circuits


Motivation for the TOC

Composition within the ISOTDAQ curriculum

- One of the **official goals** of the school is to “**expose the participants to a maximum variety of topics**”
- What comes just after the “detector” is the **first link** of the **DAQ chain**
- Therefore, this lecture will try to deliver:
 - ➔ an **intuitive approach** to what is listed in the **TOC**
 - ➔ **without** providing “**dry and ugly**” math **phrases**
- This lecture will have **no specific hands-on laboratory session** in the current program of the school
 - ➔ However it will **always** be there at the lowest level of all the laboratory sessions you will attend
- The pages will contain **enough amount of text** necessary for you **NOT** to need a lecturer in order to understand the slides at home (naively assuming that you will refer to this lecture in near future)
 - ➔ Therefore, please be aware of the above fact, in case you start feeling that the pages are a little bit **overloaded**




An Ordinary Heavy Ion Collision

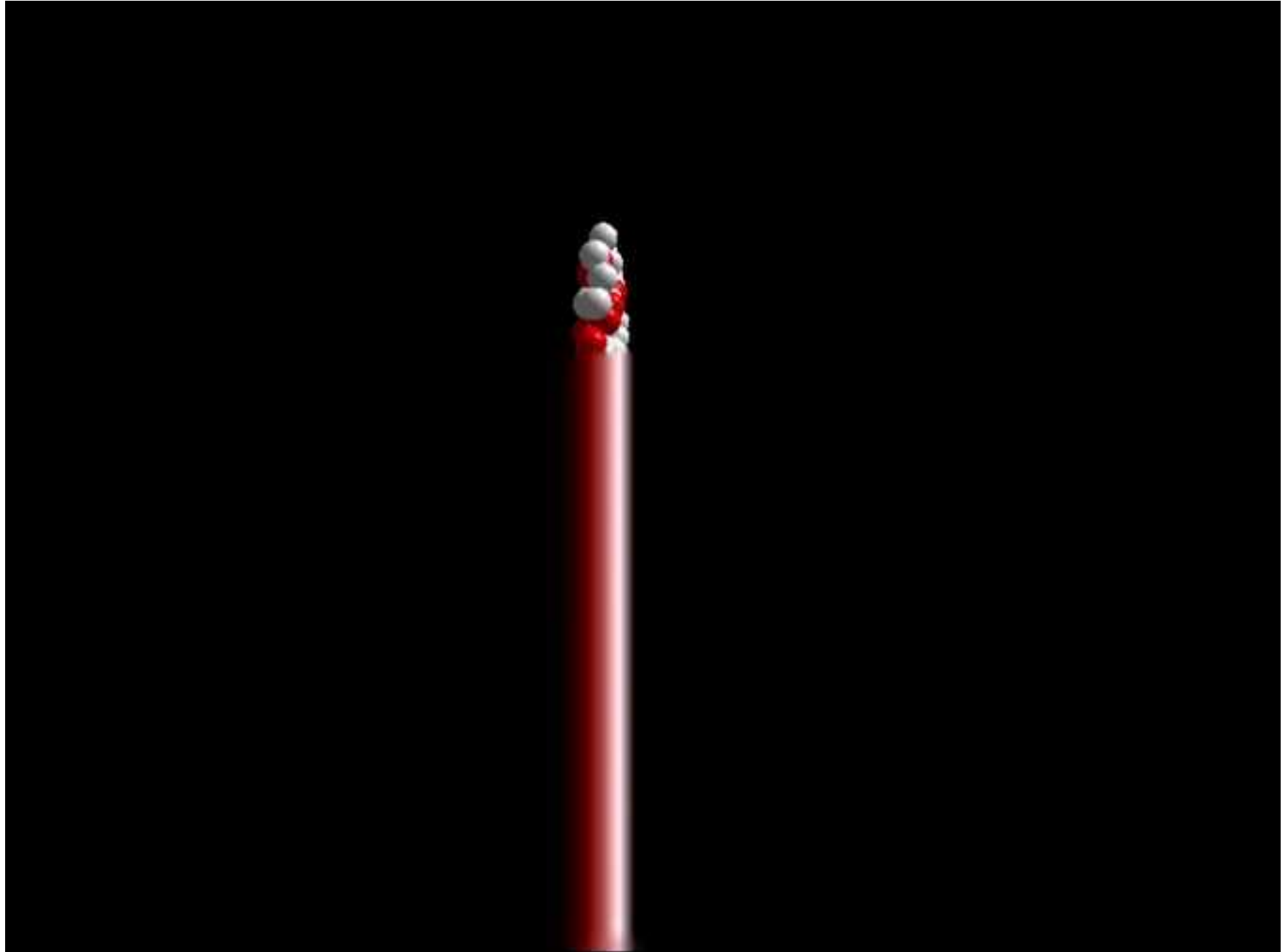Heavy ions at the center of ALICE detector; a short movie of 5 ns






The Big (but Brief) Picture

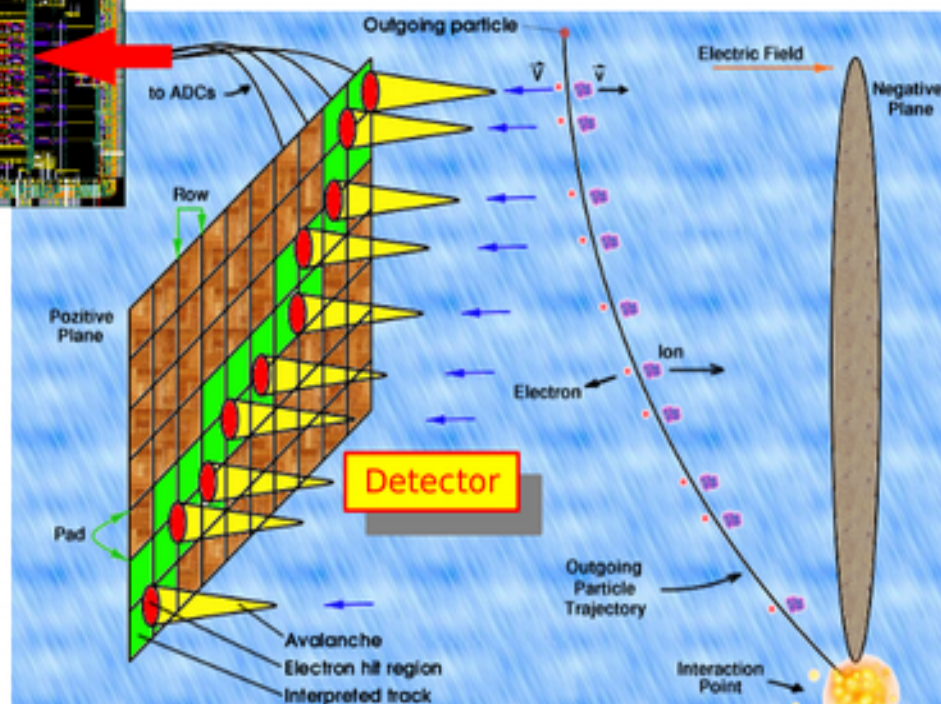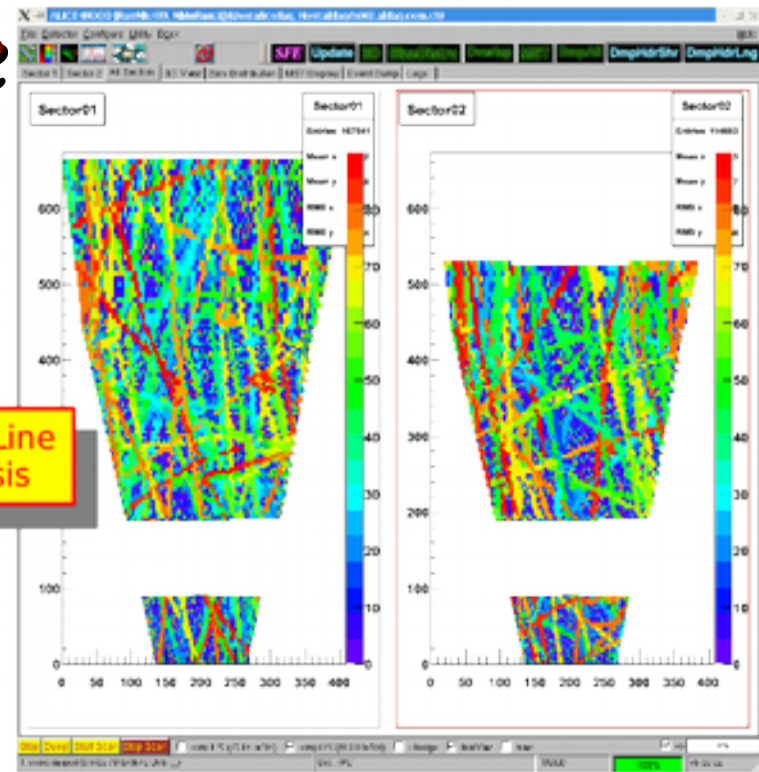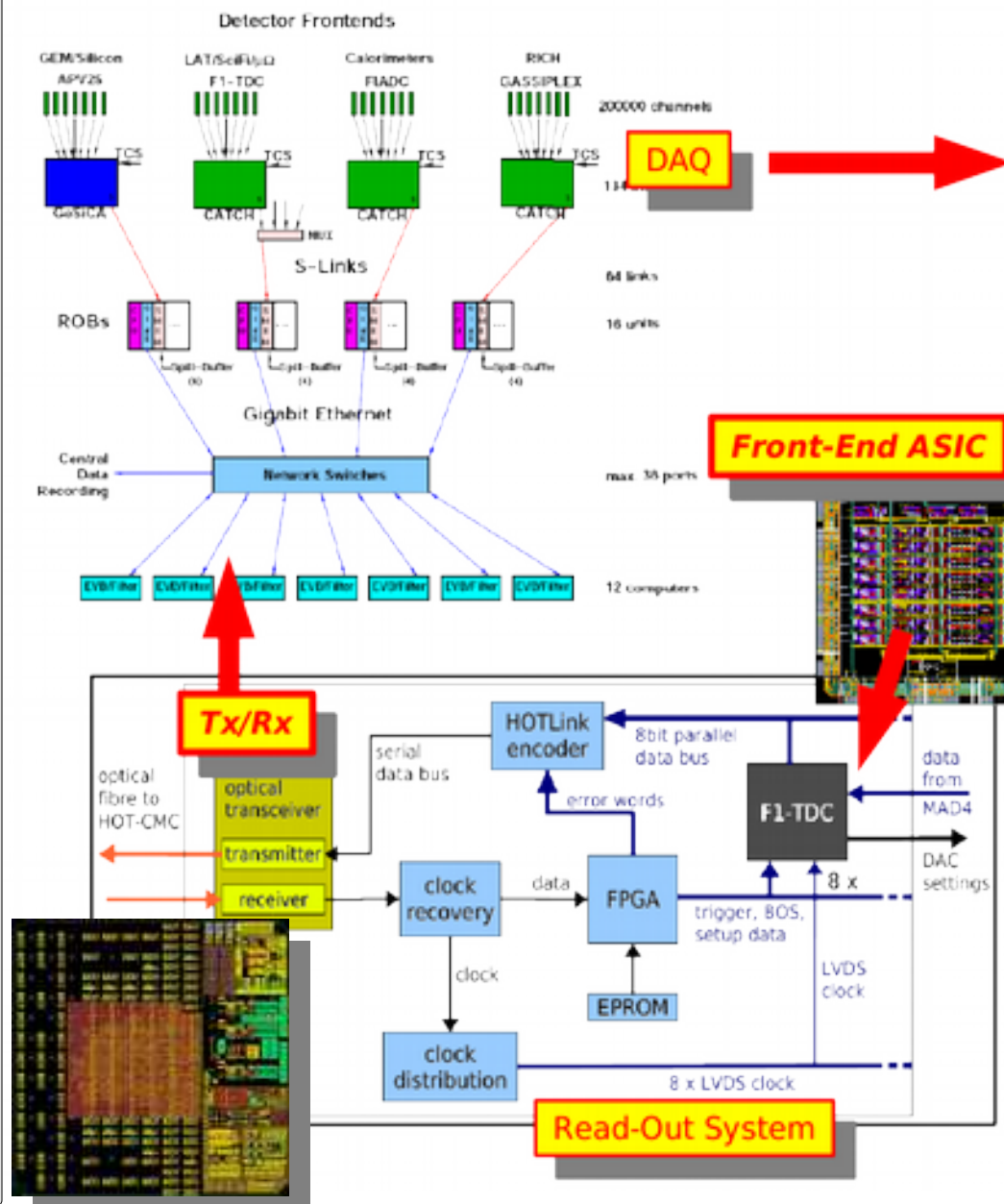From colliding particles at the interaction point
to the generation of meaningful data for analysis



First interpretation of detector data

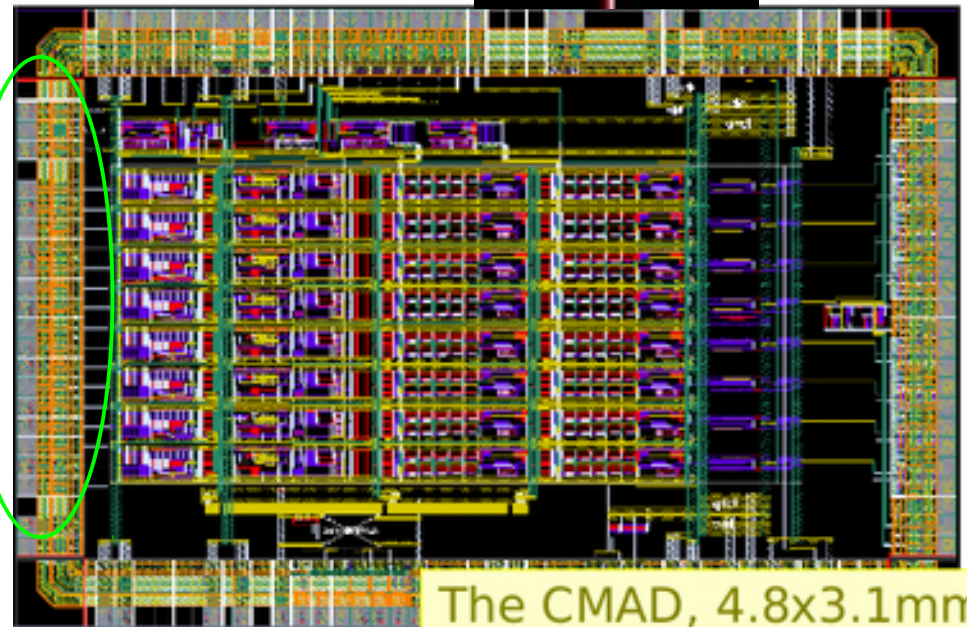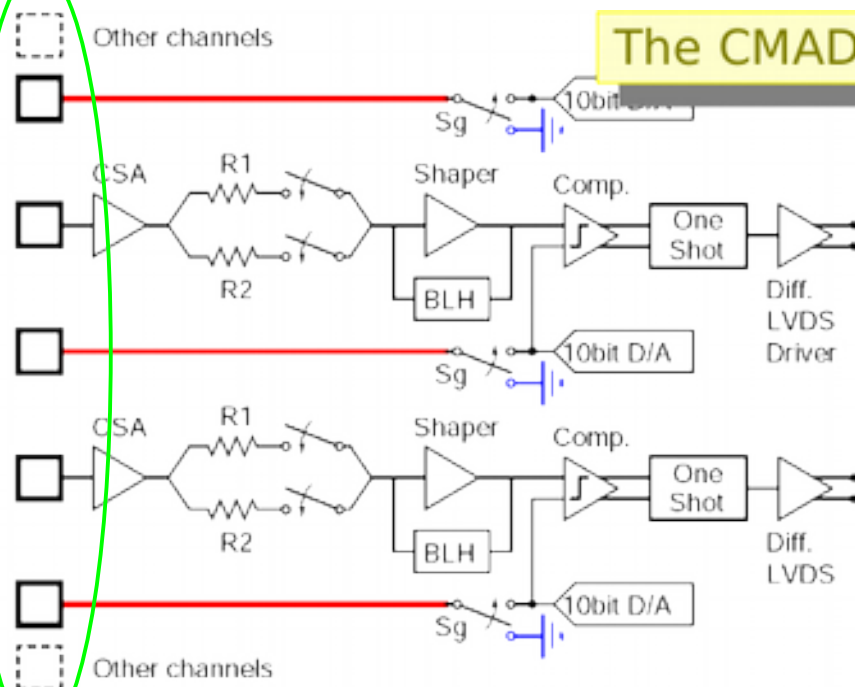
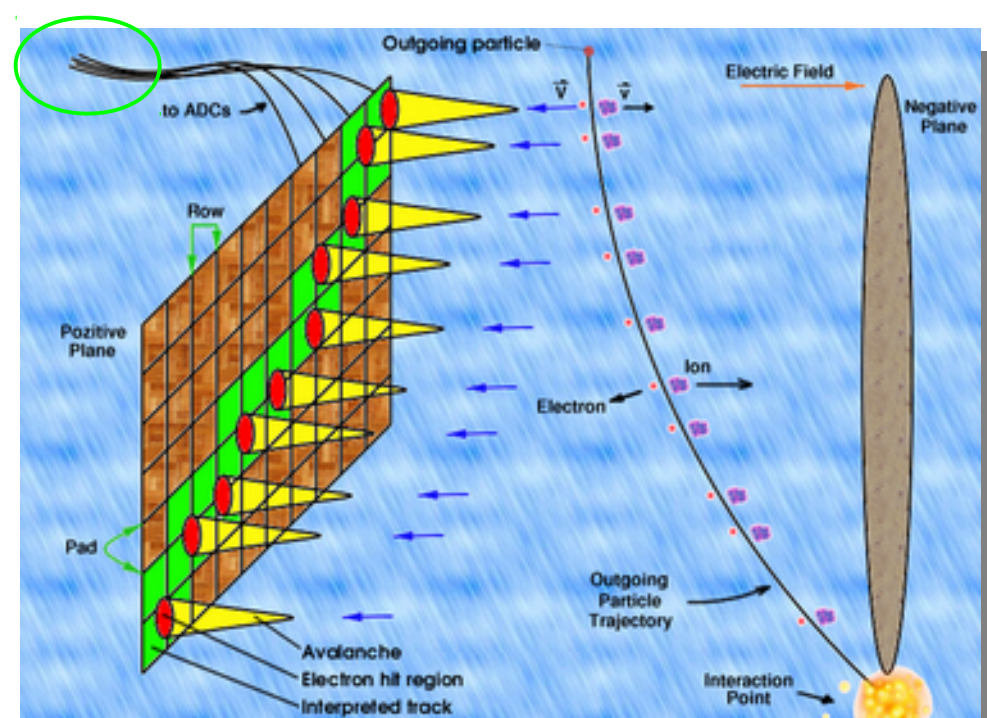
- **Integrate** the **charge** as a **pulse**
- **Shape** this **pulse**
 - 1) **Compare** pulse height to a threshold
 - Higher ? Yes : No
 - 2) **Digitize** the pulse for further processing
 - Digital filters, corrections, etc.
- **Send** the result to **read-out**



Briefly Read-Out

How to get data from FE and deliver to DAQ

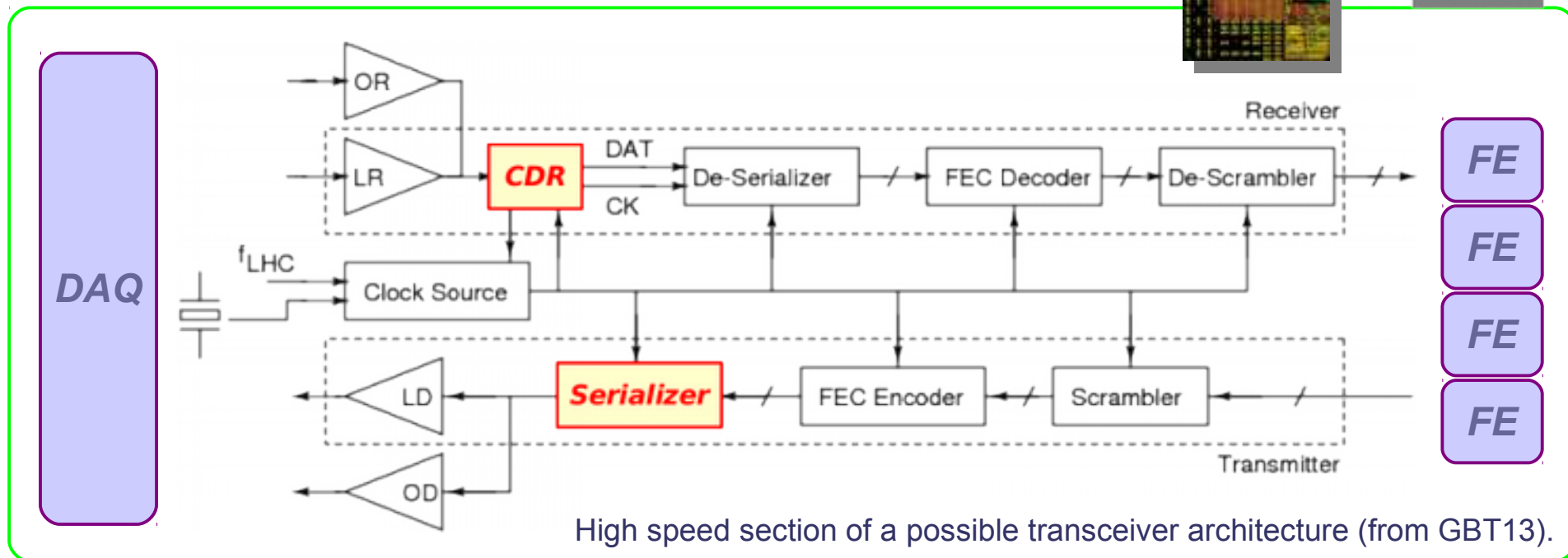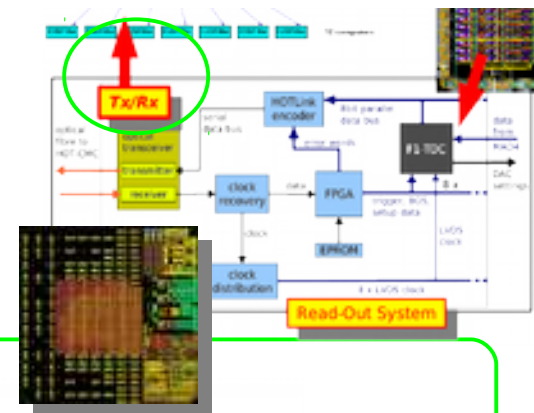- Add **header/trailer** to the data created by the detector FEs
- Combine payload fragments into **frames** to be transmitted to DAQ



■ Receiver


- ➔ **Receive** laser light representing **serial data** from fiber
- ➔ Check **FEC** code and **correct** errors (if possible)
- ➔ **Parallelize** data
- ➔ **Deliver** data to the next stage e.g. FE

■ Transmitter:

- ➔ Get data **from FE**
- ➔ **Calculate** FEC and **add** to frame, increasing resistance against transmission errors
- ➔ **Serialize** parallel data
- ➔ Drive a **laser diode** over fiber to DAQ

Briefly SER


Parallel → Serial

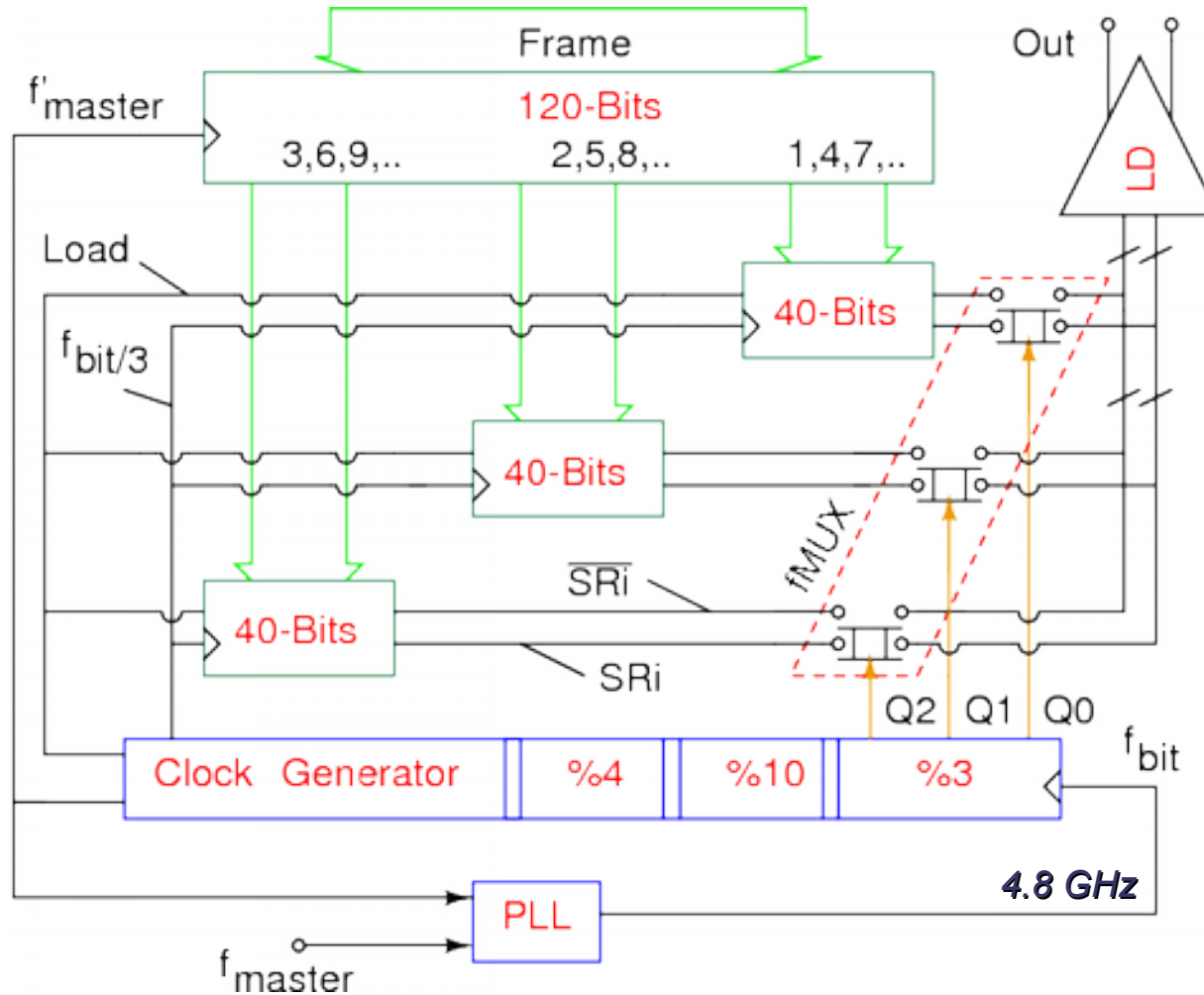


Operation:

- @ rising edge of f_{MASTER} , **load** 120-bit-wide **frame** into input register (**40 MHz**)
- @ rising edge of Load, **divide** the frame into 3 **40-bit-wide** words (**40 MHz**)
- @ rising edge of $f_{BIT/3}$, **right shift** 30-bit-wide words **sequentially** (**1.6 GHz**)
- After every shifting, **multiplex** the right bit **to output** (**4.8 GHz**)


DAQ

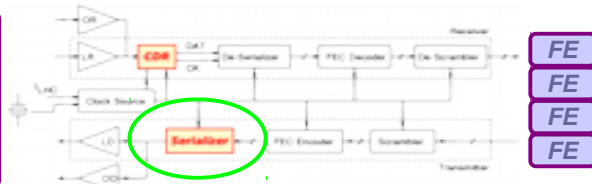


Timing Diagram

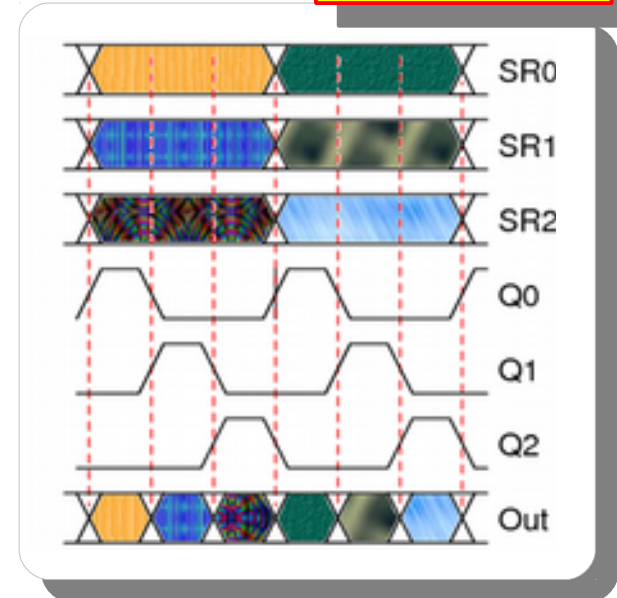

Eye Diagram

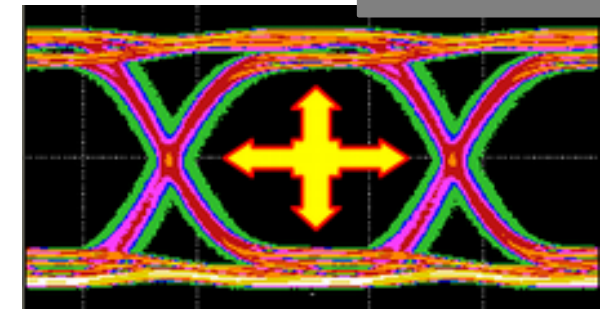

-
- The diagram illustrates a 120-bit parallel multiplier architecture. A 120-bit frame is divided into three 40-bit segments. These segments are processed by three parallel 40-bit multipliers. The inputs to the multipliers are f_{master} , Load, and $f_{bit}/3$. The outputs of the multipliers are combined to produce the final output Out and f_{bit} . A PLL block is connected to f_{master} and f_{bit} .

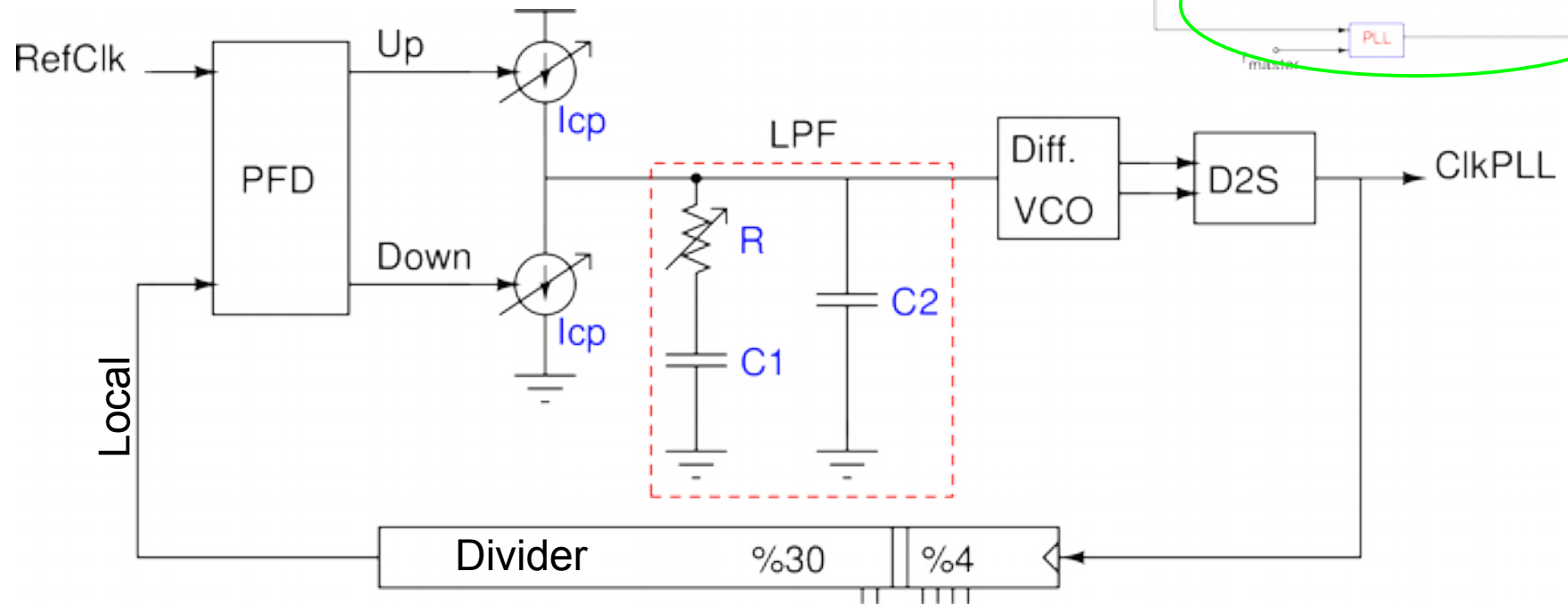

- **Measure** the rising instant **timing difference** between **RefClk** and **ClkPLL** by the phase-frequency detector (PFD)
 - ➔ **Generate** correction commands depending on this measurement (**Up**, **Down**)
- Correction commands control the charge pump (Icp) **pumping/sinking current** into/from the filter capacitor, varying the **control voltage** for the Voltage Controlled Oscillator (VCO)
 - ➔ Gradually, the **timing error** of the two signals at the inputs of the PFD would **vanish** (ideal locked condition)

Introduction to the Design of Full-Custom Front-End & Data Transmission ASICs*


Table of Contents

■ The Big (but Brief) Picture

- Briefly **front-end** - FE
- Briefly **read-out** - RO
- Briefly **serializer** - SER
- Briefly **phase-lock loop** - PLL

■ Feed-Back Concept

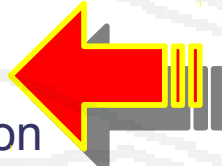- A **qualitative** introduction
- **Natural frequency** concept - ω_n
- Real-world examples:
 - **Binary** read-out
 - **Time-over threshold**
- Adjusting/optimizing loop behavior
 - **Damping ratio**



■ Reminder on Detectors

- Photodetectors **vs** photon counters
- **Position-sensitive** detectors
 - Resistive charge division
 - Discrete array of elements
- **Time-resolved** detection

■ Detector Front-End ASICs

- **Pre-Amp**: basic idea – V_{OUT} / V_{IN}
- **Transconductance** of a transistor - g_m
- Evolving a **single-stage amplifier** into a real-world application

■ Processing Technology


- **Transistor** switch – A masterpiece
 - **Lithography**
 - Formation of an **nMOS** transistor
- VLSI design flow
 - Parasitic **extraction**
- Real-world ASIC examples

■ Radiation Tolerance Issues

- Definitions:
 - **Single event upset, analog single event transient, latch-up**
- **Simulating** radiation effects on analog circuits

Feed-Back

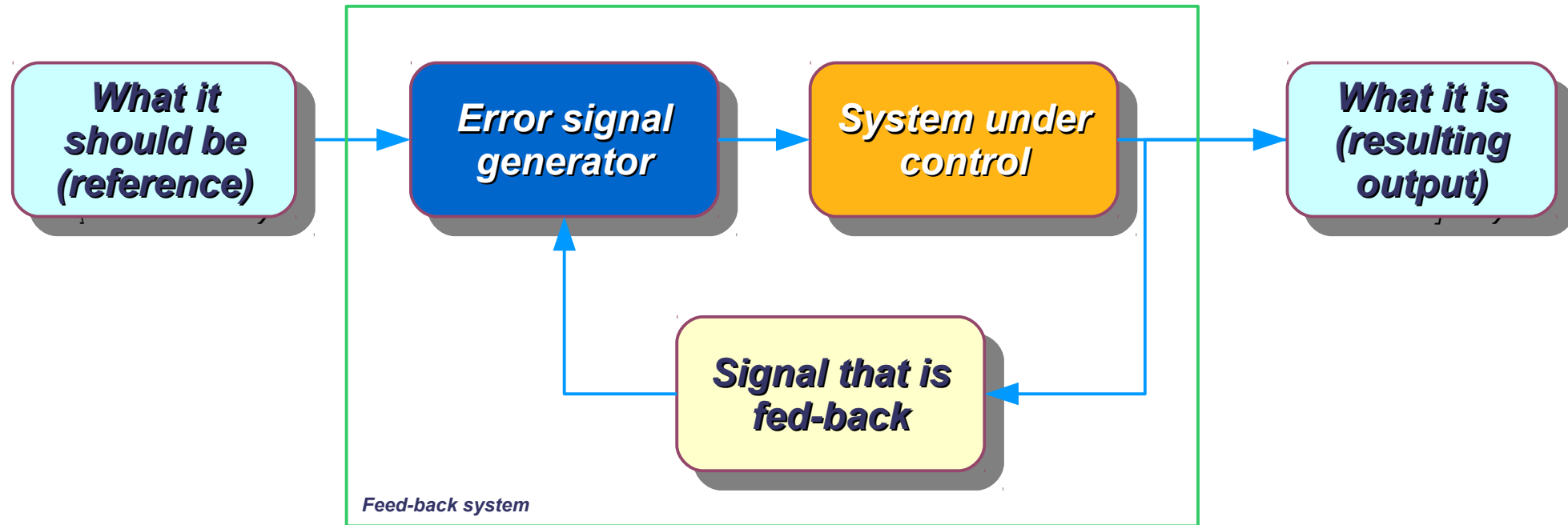
Actually a *very familiar* concept from *daily life*



- **Aim**, is decreasing the **difference** (the error signal) between the **reference** and the **output**
- **How ?** For each cycle:
 - A **portion of the output** is fed-back. Make the system be **sensitive** to a portion of what it outputs
 - **Measure** the difference between the reference and what is fed-back (only a portion of the output)
 - Depending on the difference, an **error signal** is generated which in turn causes a **correction step** to be taken **controlling the system** under control
 - **Repeat** the cycle

Feed-Back


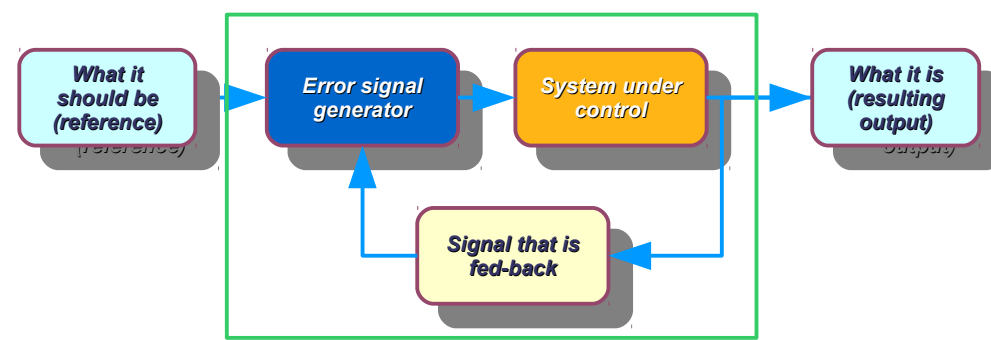
Actually a **very familiar**
concept from **daily life**



- Whistling or playing an instrument ?
 - How do I **know** what I play is “**Do**” but not “**Re**” ?
 - Does it make sense to say “I whistle **better** than you” ?
 - What happens when I try **to find the right** guitar solo for an existing song ?
- Drinking a glass of water ?
 - **Adjust** the angle & position of the glass accordingly **to keep** the water flow as it is **necessary** ?
 - Remember the childhood: sometimes the water gets dropped to the ground accidentally (What is the **failure mechanism** ?)
- Walking and biking ?
 - How do I **decide the frequency** of my steps **not to** fall down or **to be able to** reach somewhere ?
 - What about walking or biking **when drunk** ? (What is the **failure mechanism** ?)
- Ruling a country ?
 - Can “**referendum**” be a term borrowed from the **control theory** ?
 - How come politicians of the same ideology can **decide** in substantially different manners ? < Questionably ignoring corruption :D >

Feed-Back

Natural frequency concept

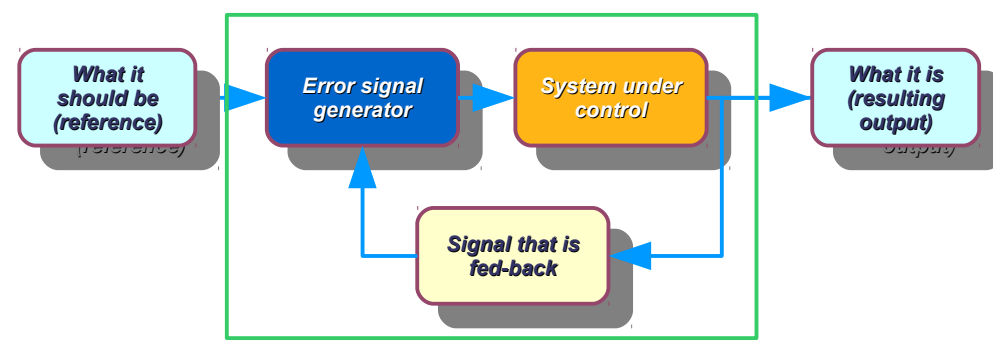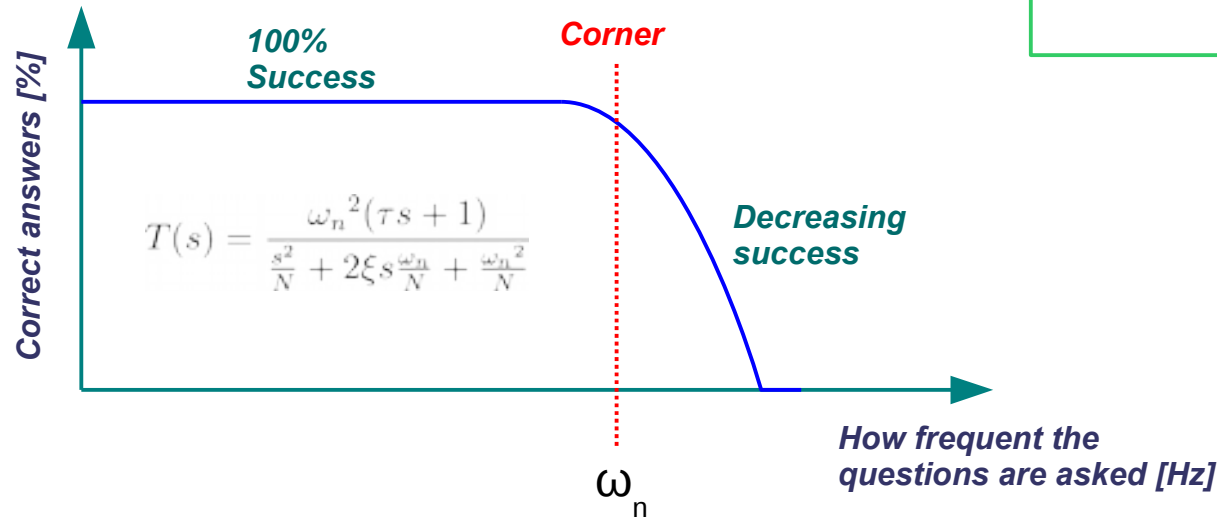


- An imaginary **system answering questions** asked continuously
- **Plot** (both logarithmic scale) the **success** level within a certain time window as a function of **frequency** of questions asked (transfer function)
- If the questions are asked **slow enough**, the system answers **all**, thus 100% success level
- Once the questions start to be asked **faster**, the system **starts failing** answering all, thus transfer function begins going down
- **Corner** is **at the natural frequency** of the control loop where the system **starts impairing significantly**


Feed-Back

Choosing for what to be *sensitive*

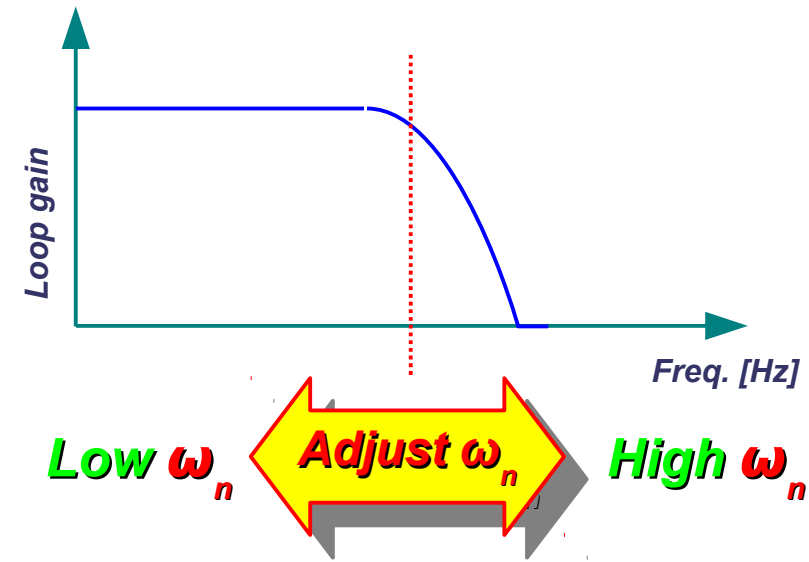- **Low ω_n** → Sense **slow variations**
 - Loop **acts** on **slowly varying** signals
 - Narrow bandwidth – slow loop
- **High ω_n** → Sense **fast variations**
 - Loop **acts** on **rapidly varying** signals
 - Wide bandwidth – fast loop





Example

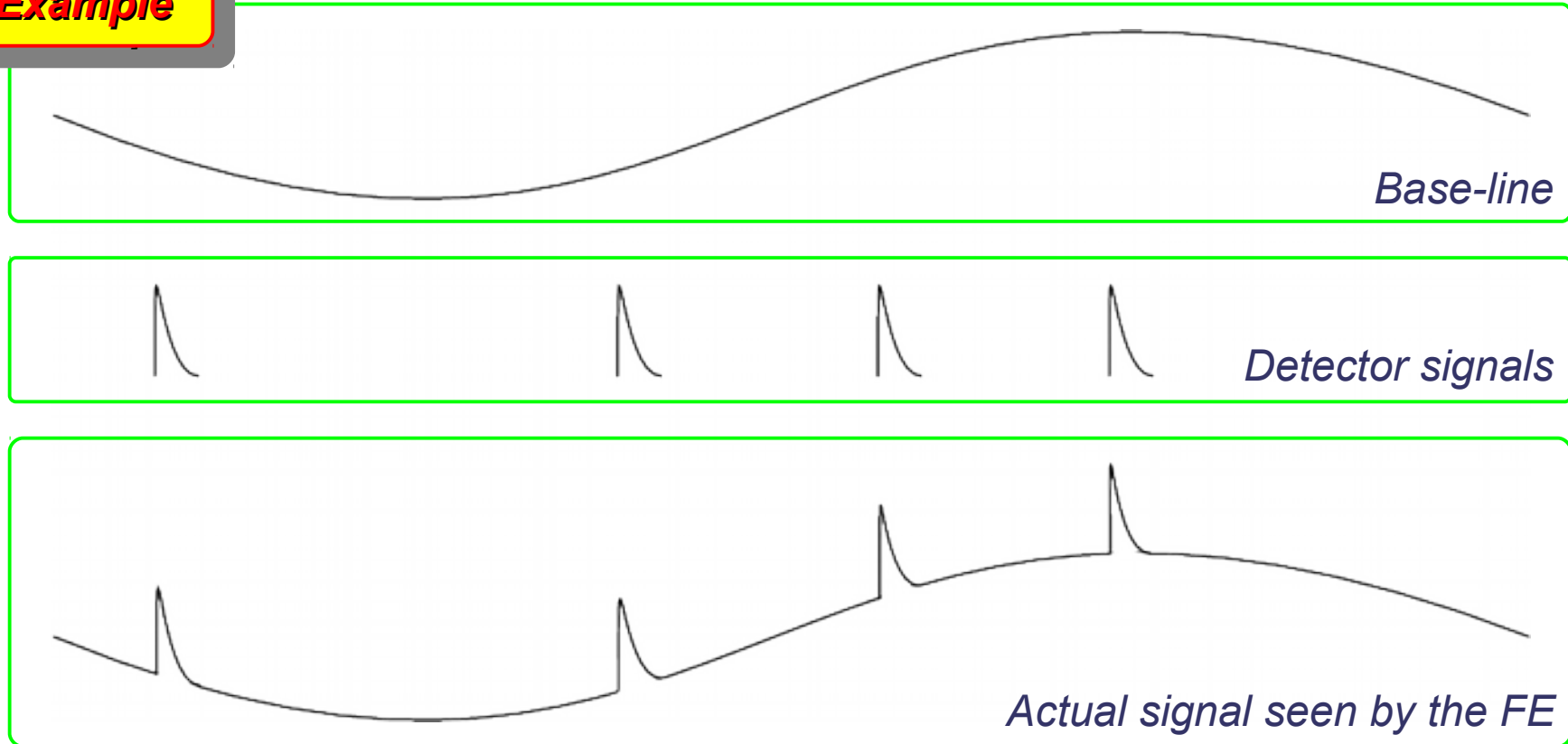

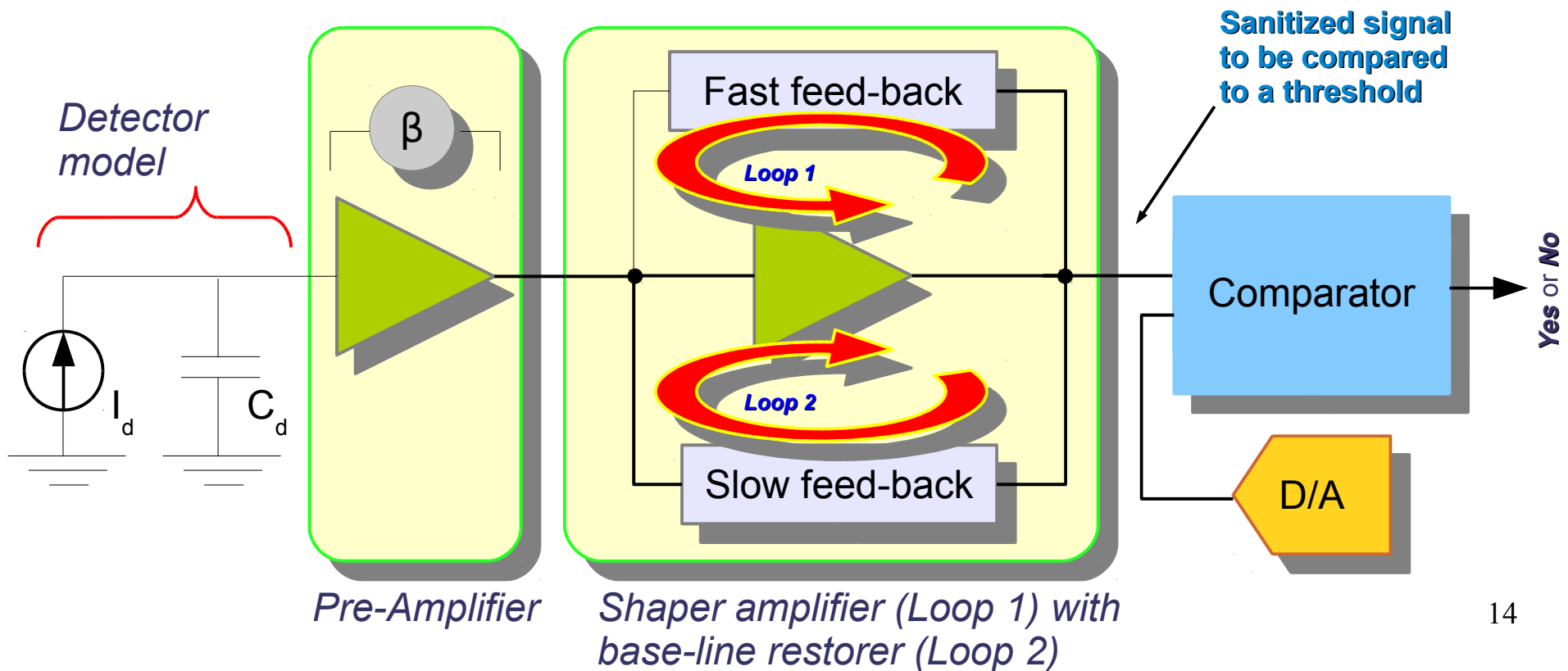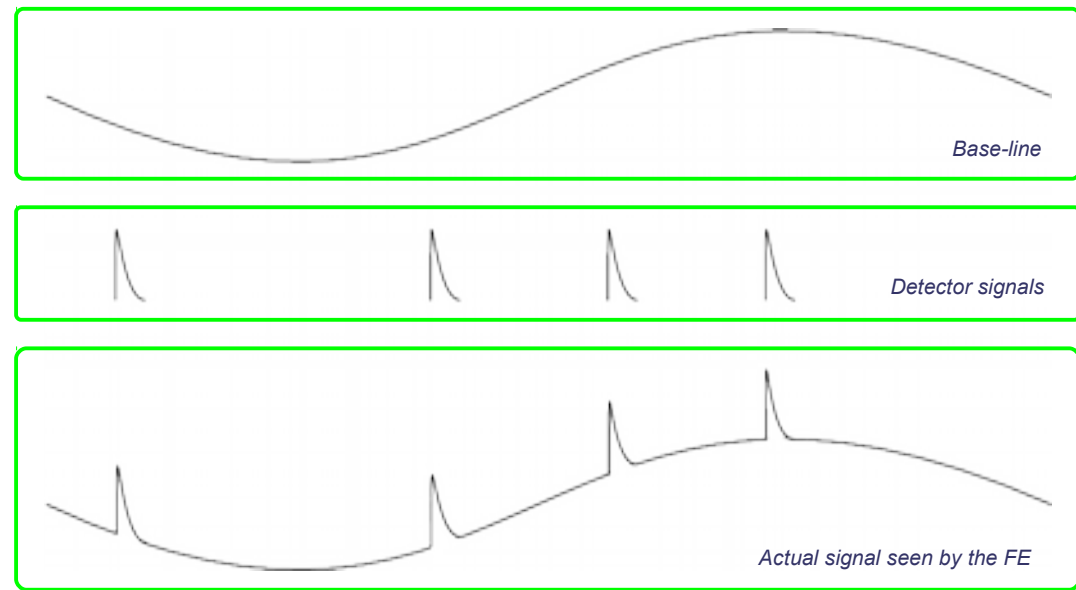Example

Binary read-out


- Requires stable **base-line**
 - Which varies slowly
 - A **narrow** loop bandwidth is needed (**Loop 2**)
- Requires a fast signal **shaper**
 - Which varies rapidly
 - A **wide** bandwidth is needed (**Loop 1**)



Real-World Example


Binary read-out for *time-over threshold* measurement

- **Random** detector **pulses** with **a few MHz** frequency; then...
 - **How fast** is the **fast loop** ?
 - **How slow** is the **slow loop** ?
- Depending on the read-out **speed** and the operating **environment**, parameters are **optimized**
 - Natural frequencies and gains of the loops, rise/fall-times, **etc.**
 - Settling behavior, radiation tolerance, damping ratio, power, **etc.**
 - Circuit footprint, robustness, redundancy, channel efficiency, **etc.**

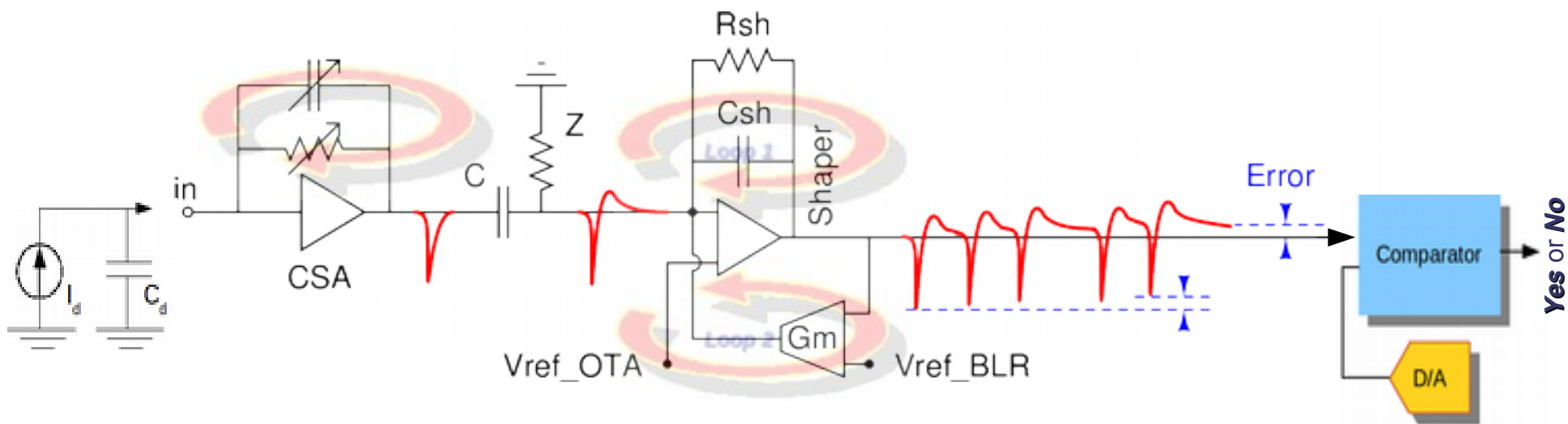


Feed-Back

Optimizing the loop behavior

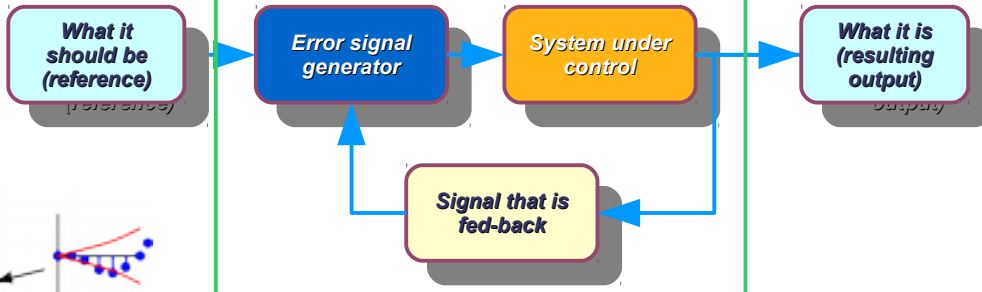


Transfer function

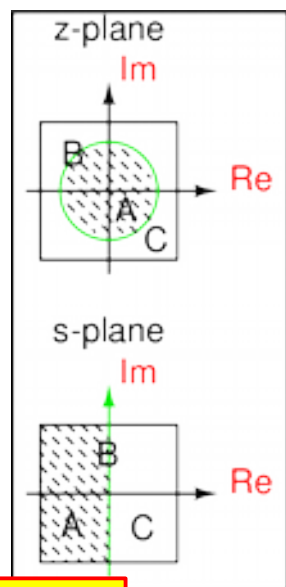
$$T(s) = \frac{\omega_n^2(\tau s + 1)}{\frac{s^2}{N} + 2\xi s \frac{\omega_n}{N} + \frac{\omega_n^2}{N}}$$




Stability regions

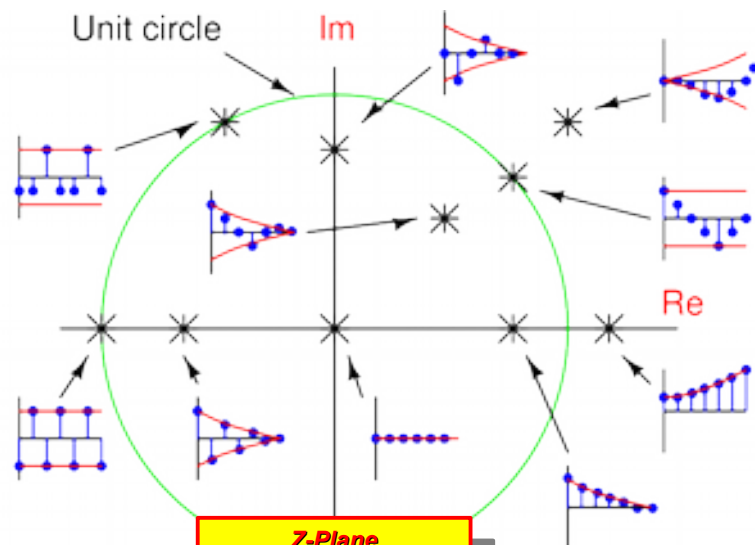

Z-Plane
(Discrete systems)

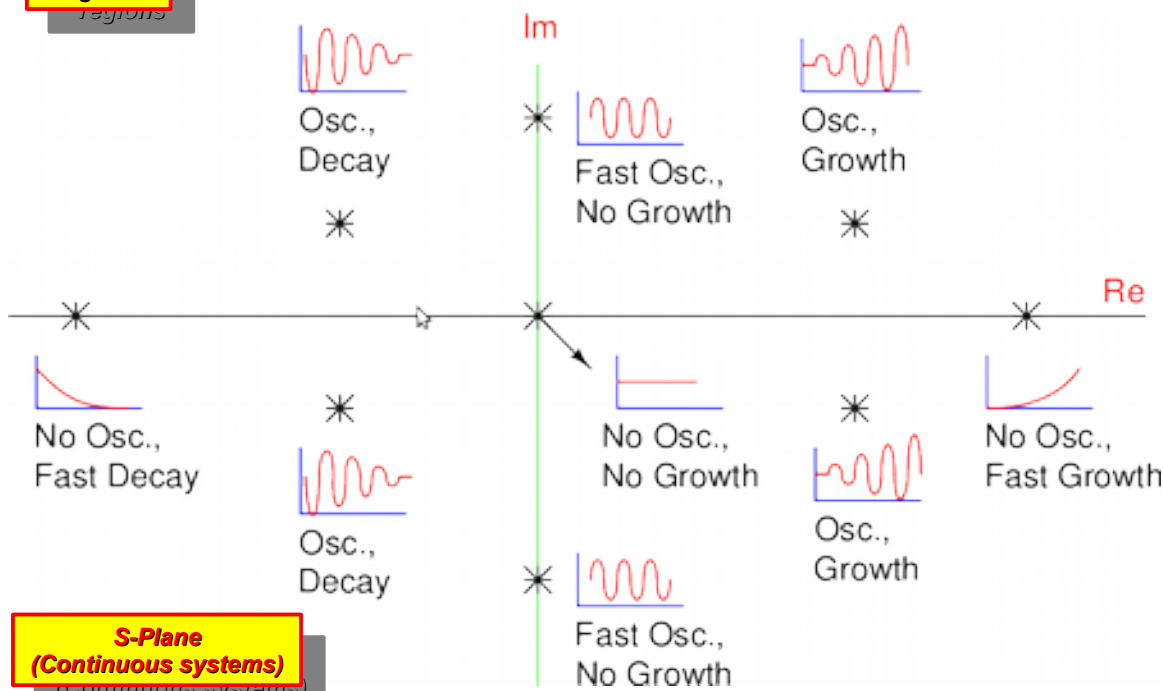



S-Plane
(Continuous systems)

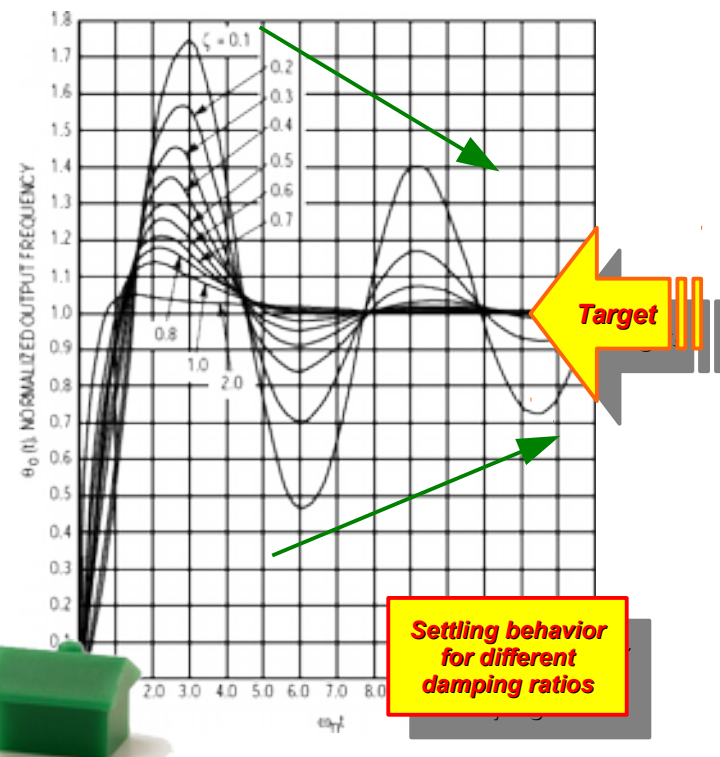

Settling behavior
for different
damping ratios

Simulation Movie Quiz


Remember the PLL

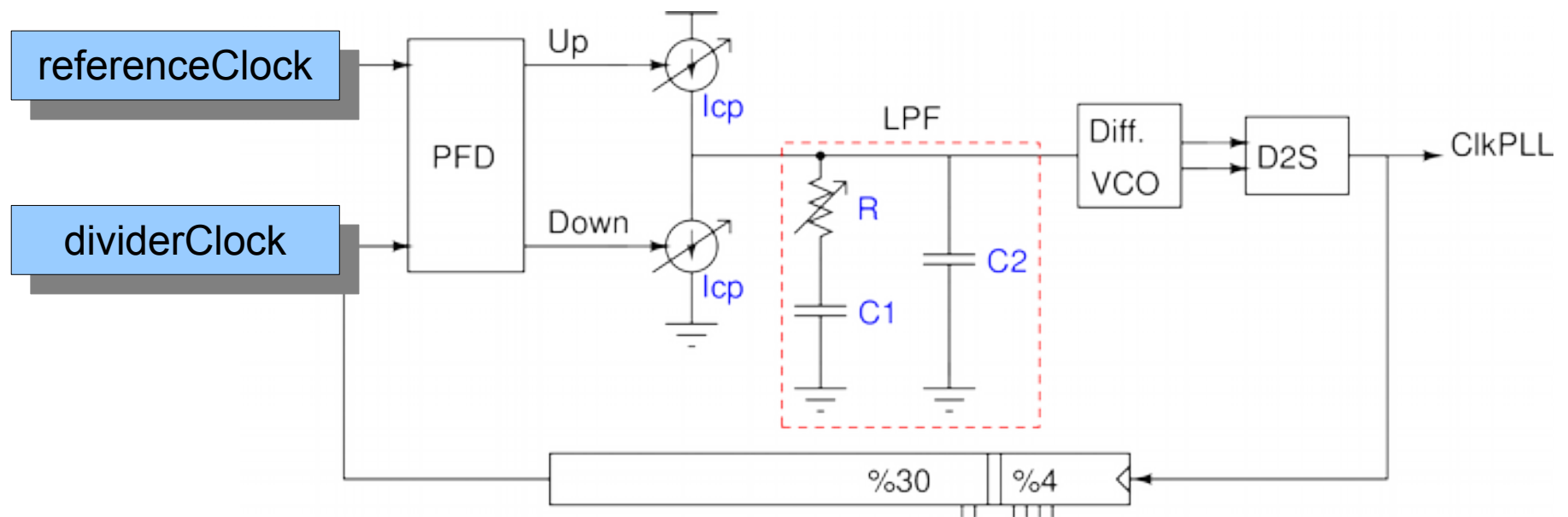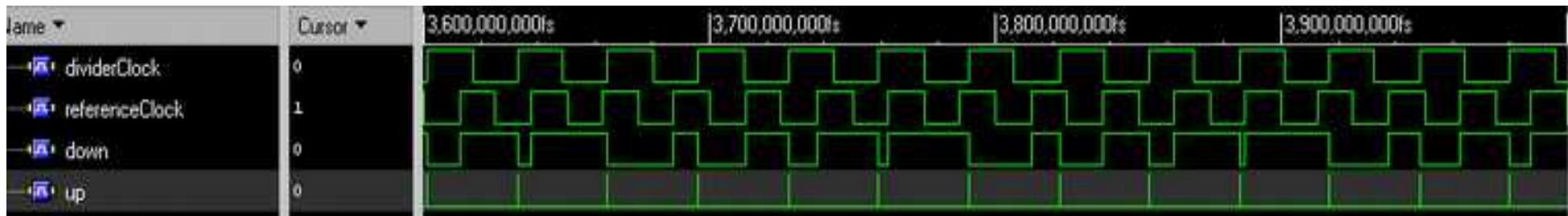


- **Slow down** the VCO, **if** it is **too fast** with respect to the reference
- **Speed up** the VCO, **if** it is **too slow** with respect to the reference


Simulation Movie Quiz

Different loop behaviors

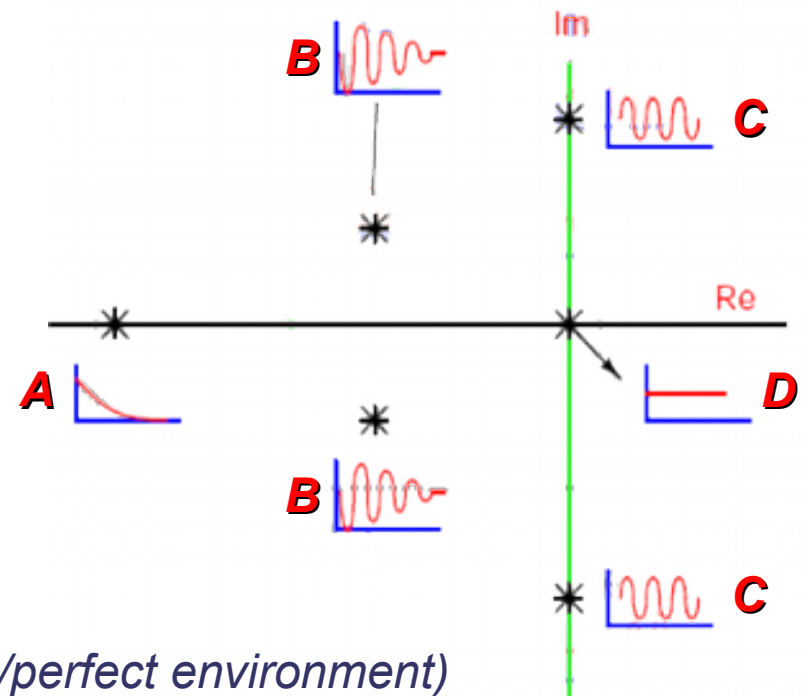- See the movies and **associate** the **behavior** to the **poles** on the **s-plane** (complex plane) 
- Use your **intuition**



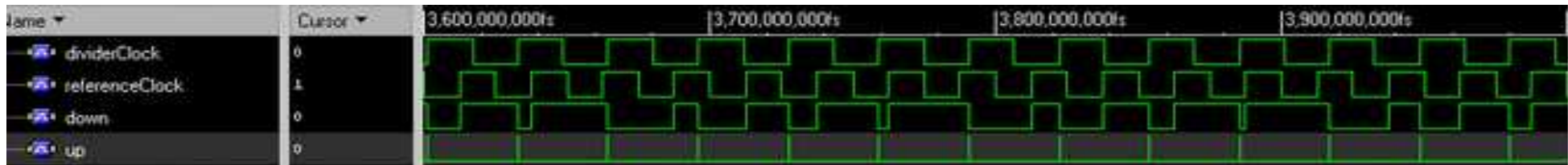? - **Slow-loop** with **low damping** ratio (**noiseless**/perfect environment)




? - **Fast-loop** with **high damping** ratio (**noiseless** environment)

? - **Slow-loop** with **low damping** ratio (**noisy** environment)


Simulation Movie Quiz

Different loop behaviors

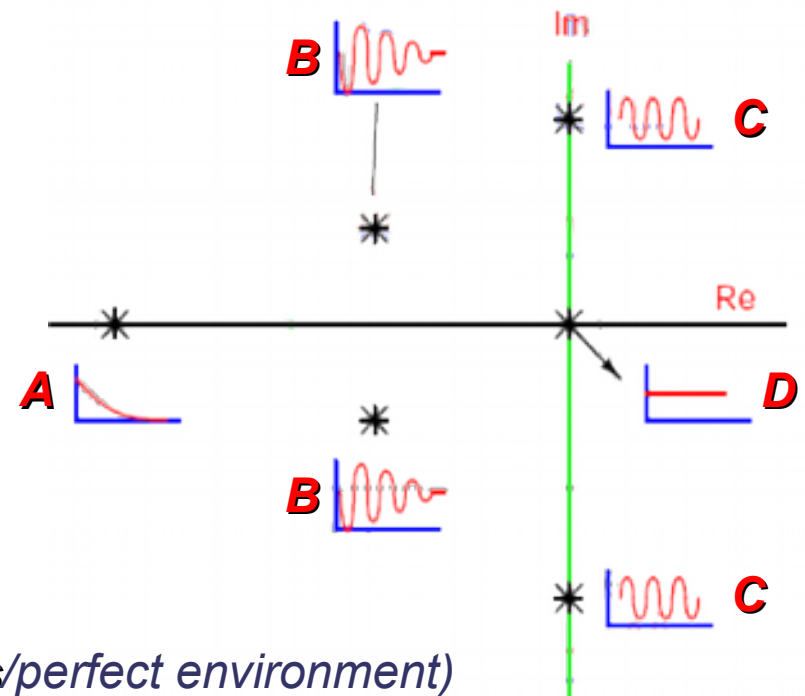
- See the movies and **associate** the **behavior** to the **poles** on the **s-plane** (complex plane) 
- Use your **intuition**



 B - **Slow-loop** with **low damping** ratio (**noiseless**/perfect environment)



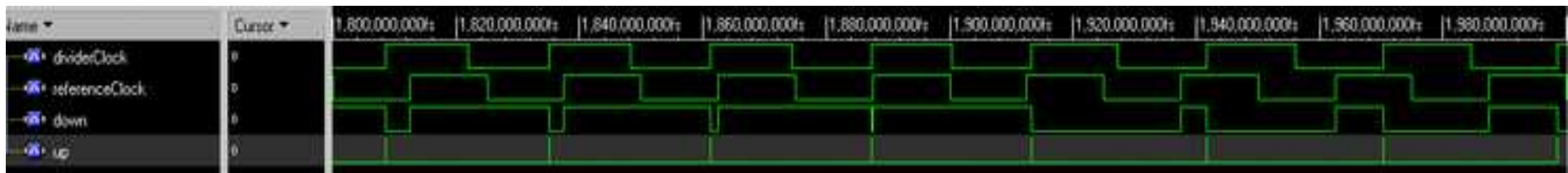? - **Fast-loop** with **high damping** ratio (**noiseless** environment)




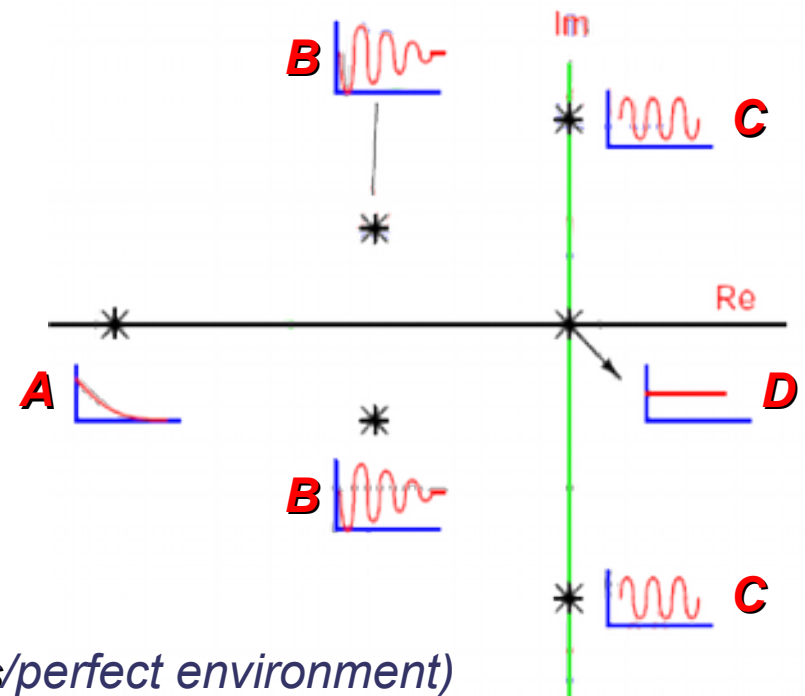
? - **Slow-loop** with **low damping** ratio (**noisy** environment)



Simulation Movie Quiz

Different loop behaviors

- See the movies and **associate** the **behavior** to the **poles** on the **s-plane** (complex plane) 
- Use your **intuition**




B - Slow-loop with **low damping** ratio (**noiseless**/perfect environment)



A - Fast-loop with **high damping** ratio (**noiseless** environment)



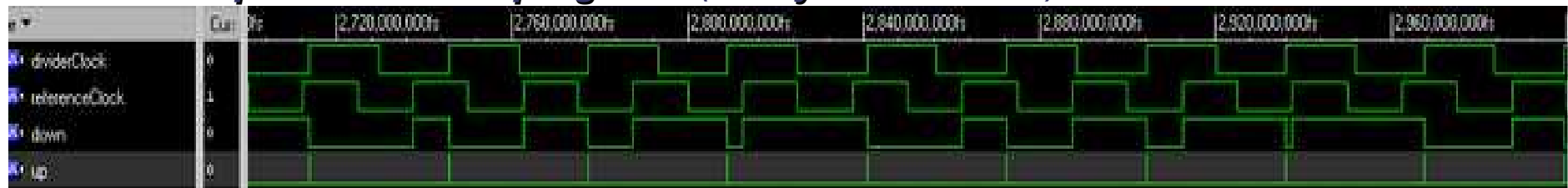
? - Slow-loop with **low damping** ratio (**noisy** environment)



Back to the big picture

If the PLL fails, then nothing works !..

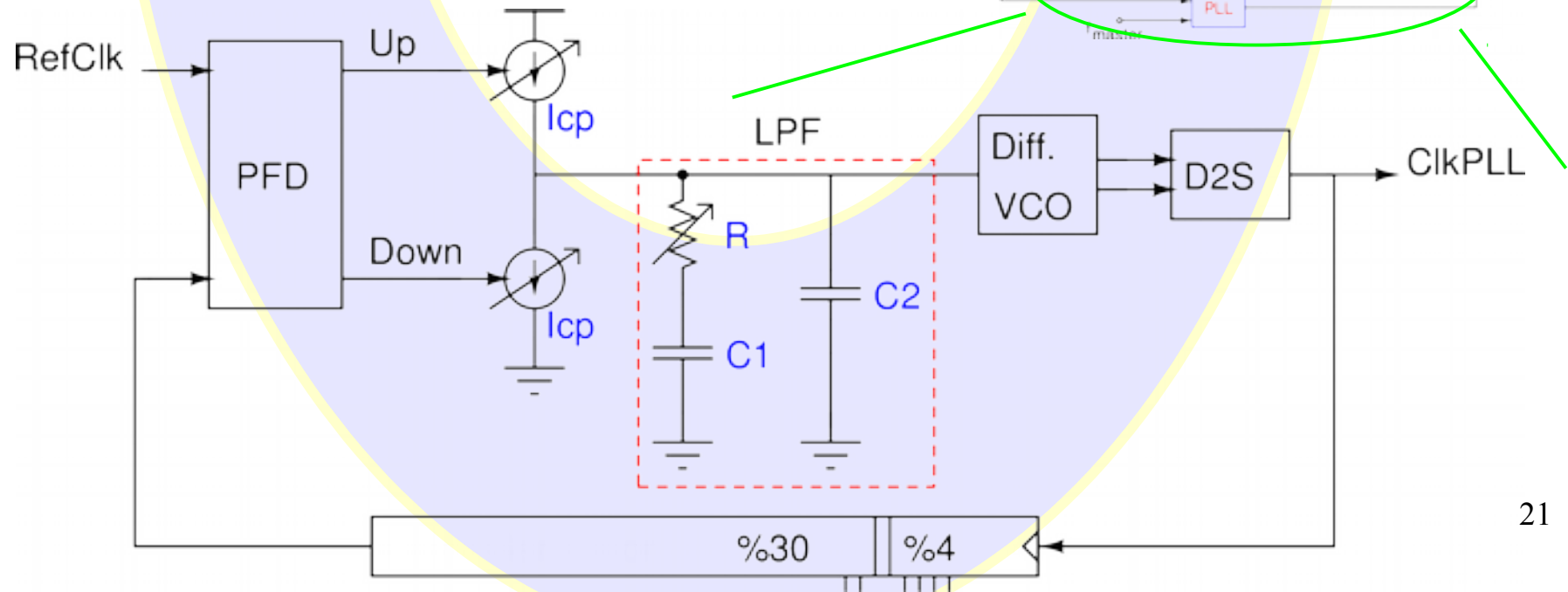- In case the loop **parametrization** is wrong:
 - ➔ PLL can not deliver a proper **clock**
 - ➔ No phase/frequency locked ClkPLL signal
 - ➔ Ignored LHC clock, no synchronization
 - ➔ SER fails
 - ➔ Some of the bits get **lost** or **duplicated**
 - ➔ High **jitter** leading to closed **eye diagram**
 - ➔ RO fails delivering the data from FE to DAQ
 - ➔ No DAQ → **Fatal error** !..



Introduction to the Design of Full-Custom Front-End & Data Transmission ASICs*

Table of Contents

■ The Big (but Brief) Picture

- Briefly **front-end** - FE
- Briefly **read-out** - RO
- Briefly **serializer** - SER
- Briefly **phase-lock loop** - PLL

■ Feed-Back Concept

- A **qualitative** introduction
- **Natural frequency** concept - ω_n
- Real-world examples:
 - **Binary** read-out
 - **Time-over threshold**
- Adjusting/optimizing loop behavior
 - **Damping ratio**

■ Reminder on Detectors

- Photodetectors **vs** photon counters
- **Position-sensitive** detectors
 - Resistive charge division
 - Discrete array of elements
- **Time-resolved** detection

■ Detector Front-End ASICs

- **Pre-Amp**: basic idea – V_{OUT} / V_{IN}
- **Transconductance** of a transistor - g_m
- Evolving a **single-stage amplifier** into a real-world application

■ Processing Technology

- **Transistor** switch – A masterpiece
 - **Lithography**
 - Formation of an **nMOS** transistor
- VLSI design flow
 - **Parasitic extraction**
- Real-world ASIC examples



■ Radiation Tolerance Issues

- Definitions:
 - **Single event upset, analog**
 - **single event transient, latch-up**
- **Simulating** radiation effects on analog circuits

An Example

Pilatus System: A hybrid of "sensor + electronics"

- "The development at PSI is **driven** by the design of the pixel detector for the **CMS** (Compact Muon Solenoid) experiment at the planned Large Hadron Collider (**LHC**) at **CERN**." (Ref: <http://pilatus.web.psi.ch/publications.htm>)
- **Hybrid**: fully depleted **detector** sitting on top of the **front end** electronics, reading out the detector, integrated within each of the pixels
- Composed of the **detector**, **charge-sensitive preamplifier**, **shaper**, **comparator** and **counter**

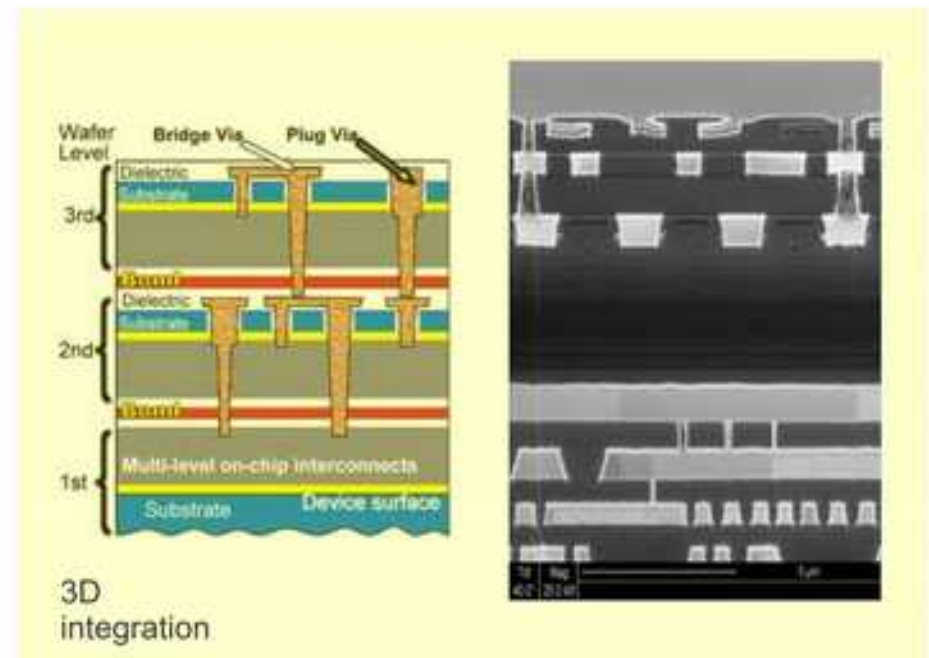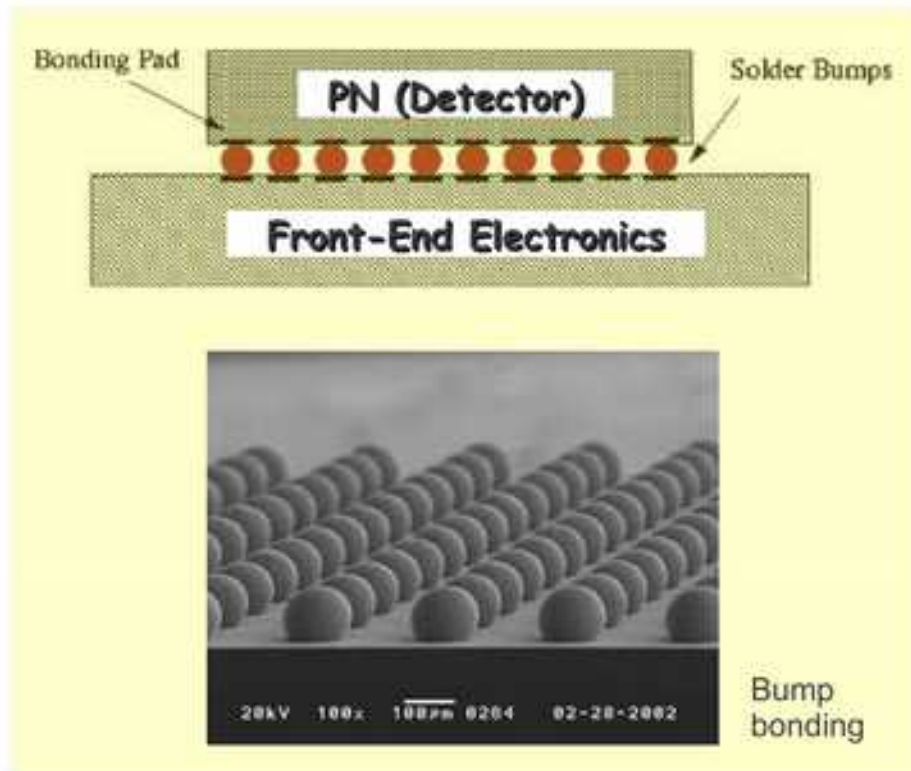




Case Study #3

Pilatus System: A hybrid of "sensor + electronics"

- "The development of FSI is driven by the design of the pixel detector for the CMS (Compact Muon Solenoid) experiment at the planned Large Hadron Collider (LHC) at CERN" (Ref: <http://pilatus.web.psi.ch/publications.htm>)

- Hybrid: fully integrated detector, integrating function of the front end electronics, reading out the detector, integrated within each of the pixels

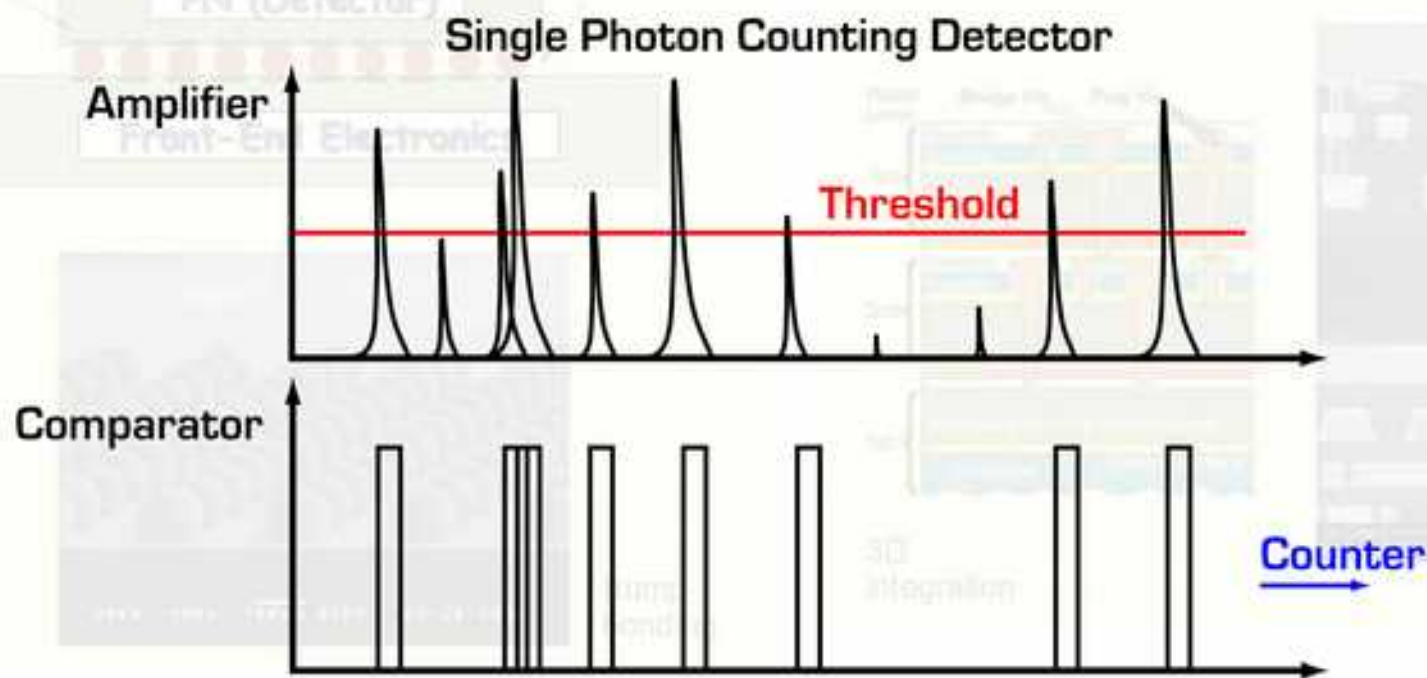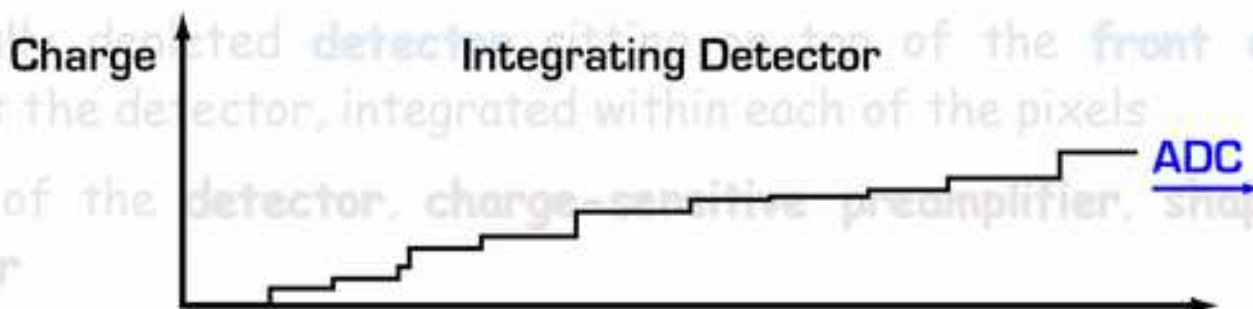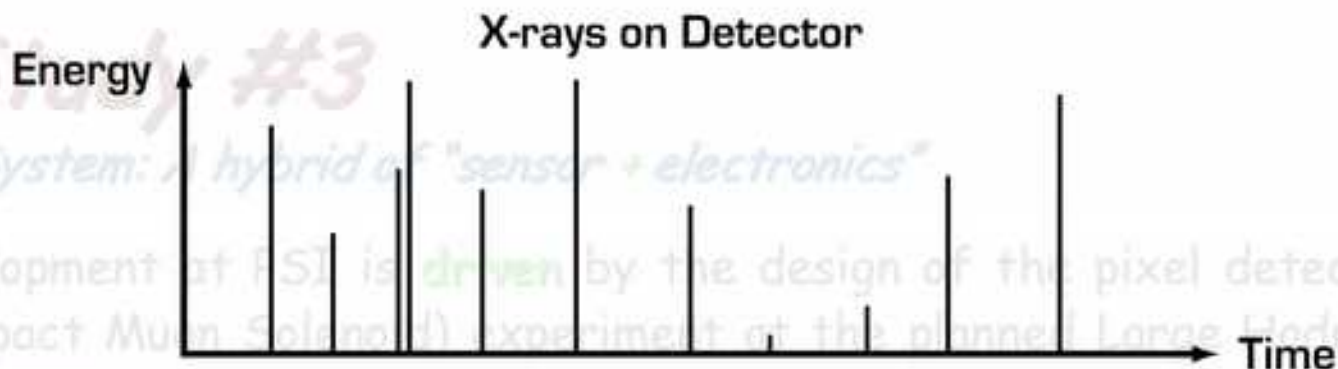- Composed of the detector, charge-sensitive preamplifier, shaper, comparator and counter



Case Study #3


Energy

X-rays on Detector

Pilatus System: A hybrid of "sensor + electronics"

- "The dev
- CMS (Co
- (LHC) at
- Hybrid:
- reading a
- Composed
- and coun

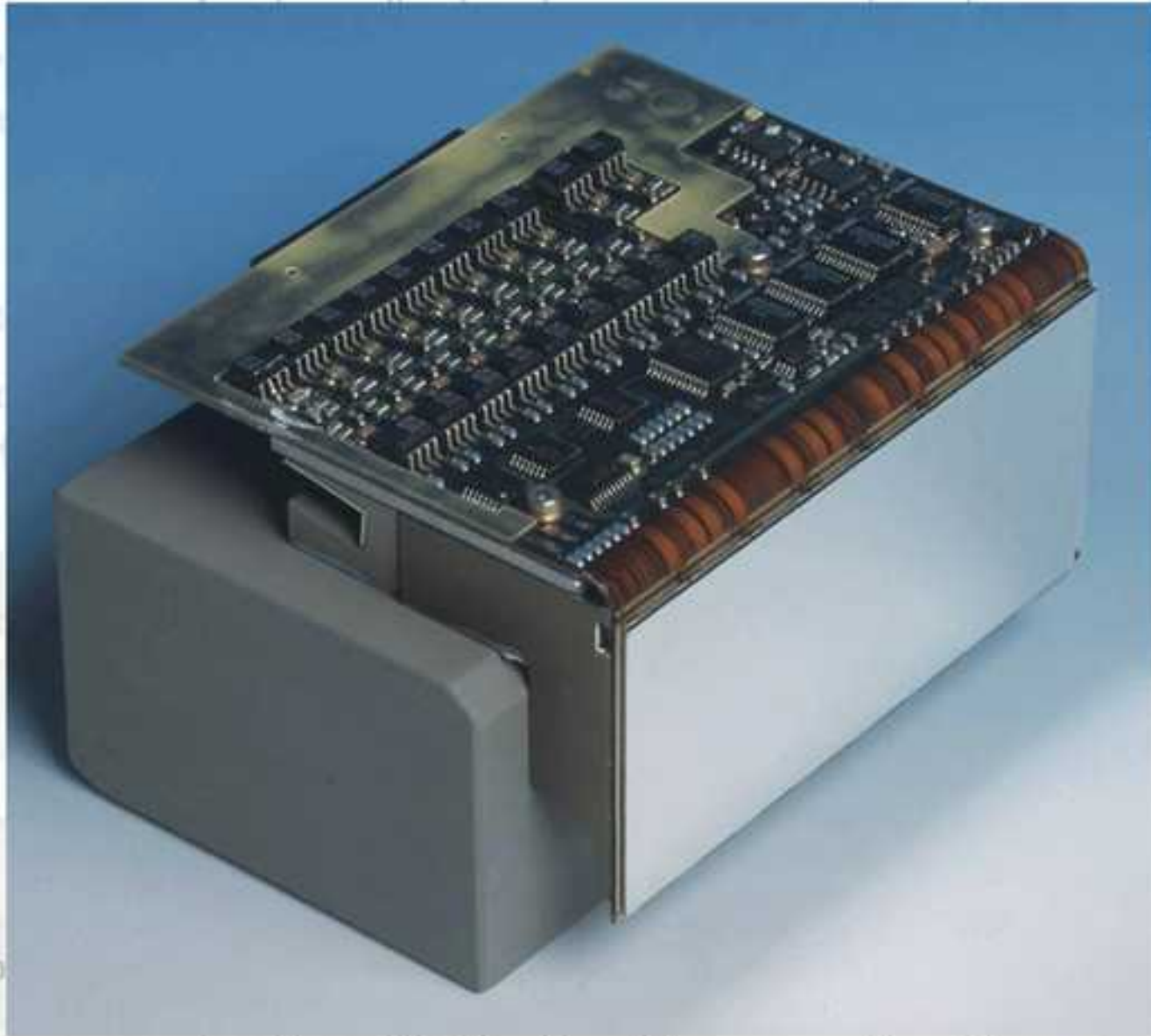detector for the
adron Collider
me
nd electronics,
er, comparator






Reading Pool

Co


Counter

Sum
Wording

3D
Integration

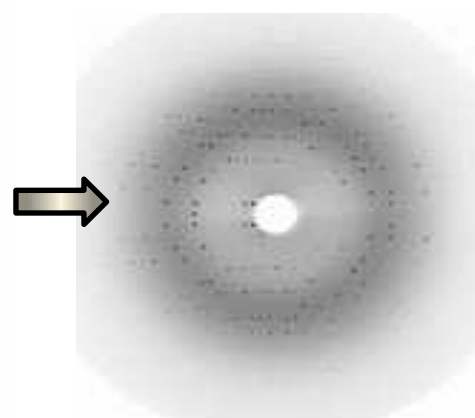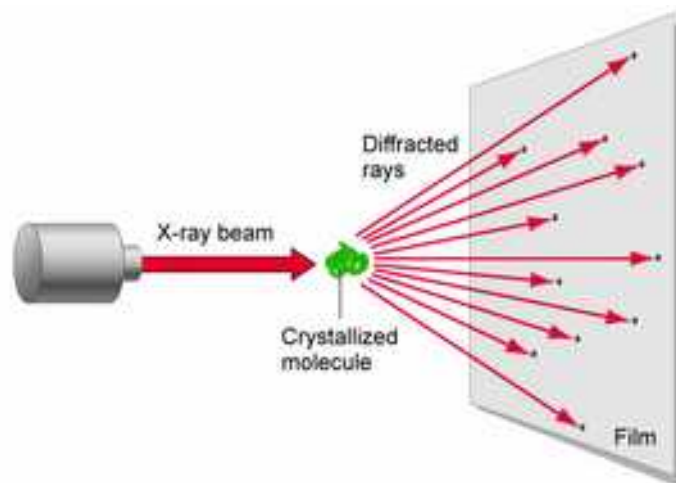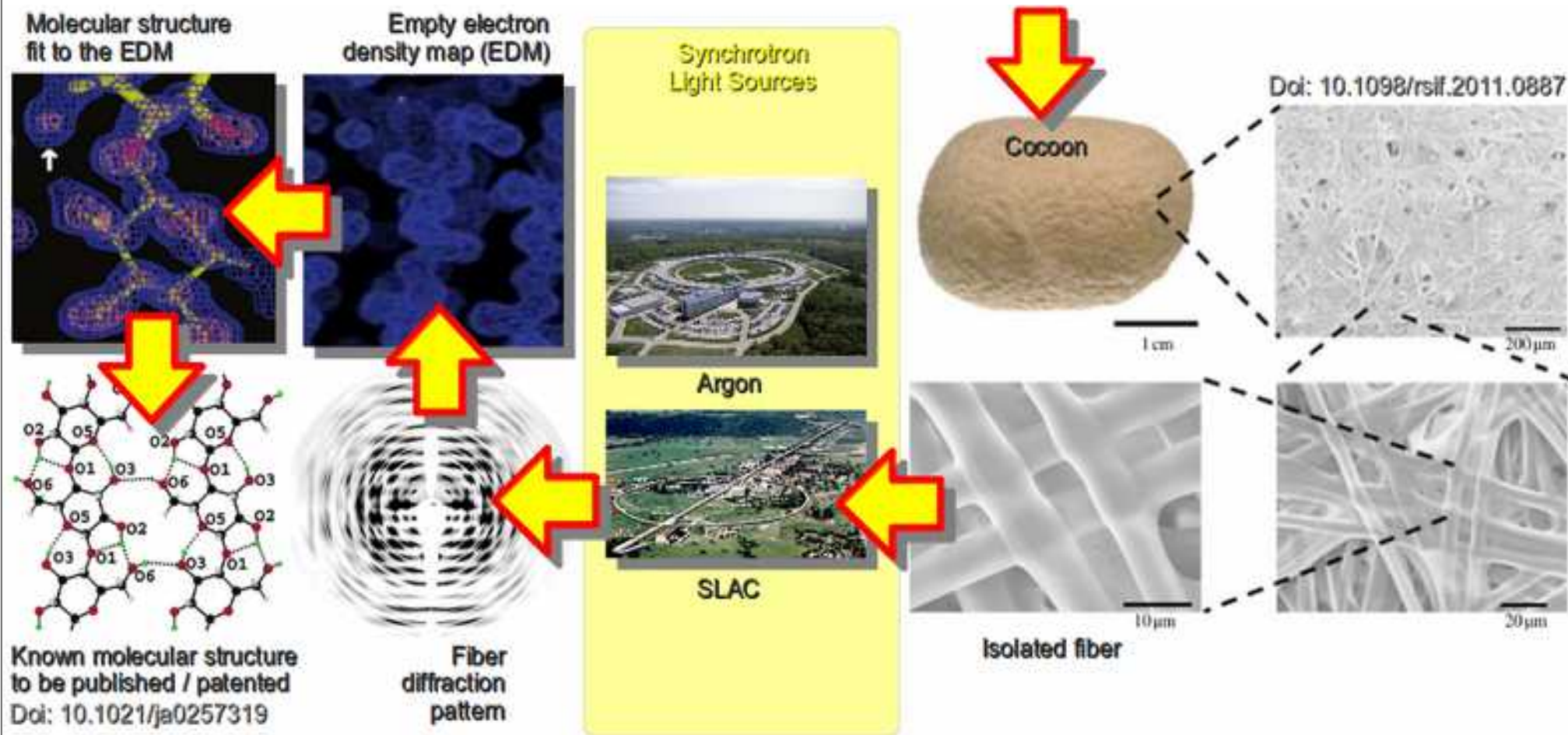

Diffraction pattern


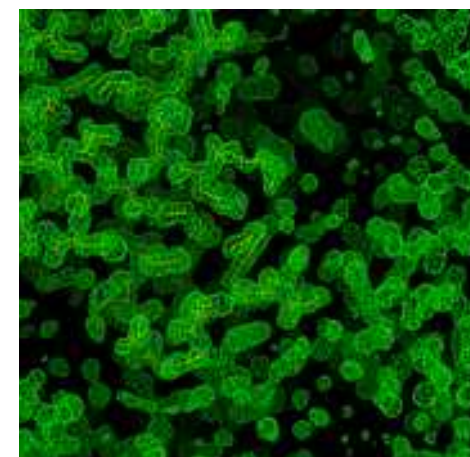


Electron density map

Crowd vs Counted Individuals

First interaction with the photons (and/or particles)

- Impossible to cover all
 - There are **many types** and even **many more examples** of particle detectors
- Therefore limited
 - Just a few types and examples **should be enough**, given the limited **time**
- “Seeing” the photons → **photodetector** != **photon counter**
 - **Photo-detectors**: generate an **analog level** (i.e. **I** or **V**) as a **function** of “light” **intensity** (e.g. **PN** and **PIN** structures)
 - **Photon counters**: **count** individual bursts of **photon bundles** or **single photons** (e.g. **PMTs** and **avalanche diodes**)

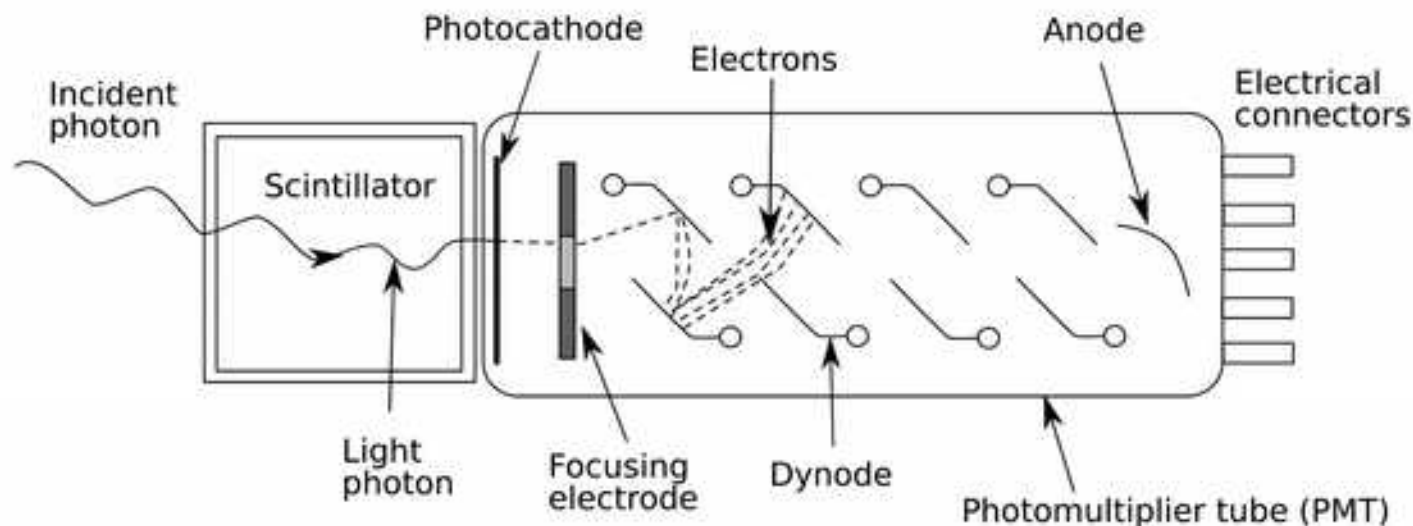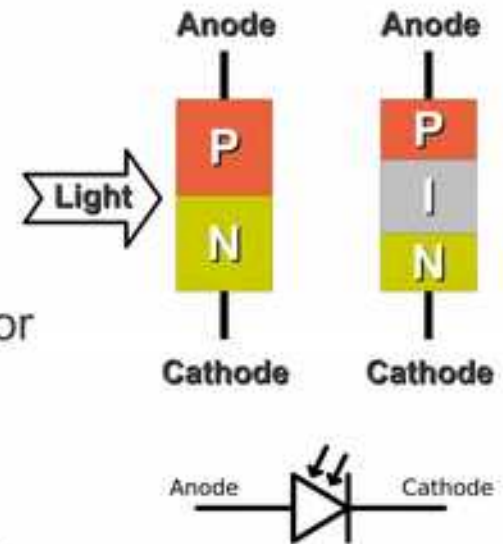

Crowd vs Counted Individuals

First interaction with the photons (and/or particles)

→ **Photo-detectors**: generate an **analog level** (i.e. I or V) as a **function** of "light" **intensity** (e.g. **PN** and **PIN** structures)

→ **Two modes** of operation:

◆ **Photo-voltaic** mode

→ Depleted region is **exposed to light** and **voltage** is measured, with **no bias**

◆ **Photo-conductive** mode

→ **Exposed light** generates a **current** flow, under **reverse-bias**

→ Some important features:

→ Responsivity (I/P_{optic})

→ Active **area**

→ Max **photo current** (limited by saturation)

→ **Dark current** (in photoconductive mode)

→ **Bandwidth** (rise, fall times)

→ ...

→ ...

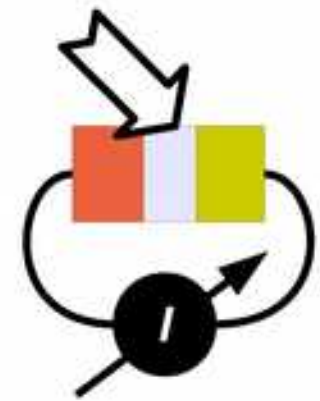


Photo-voltaic mode


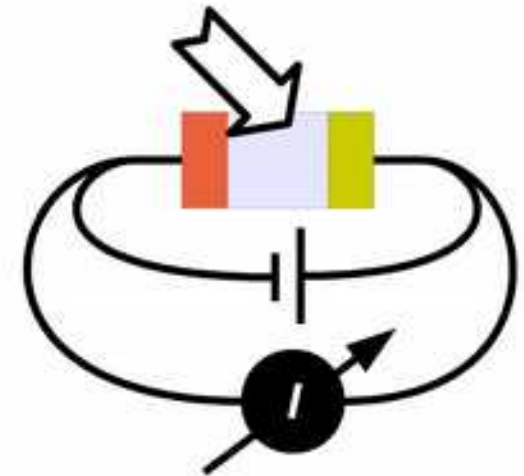



Photo-conductive mode

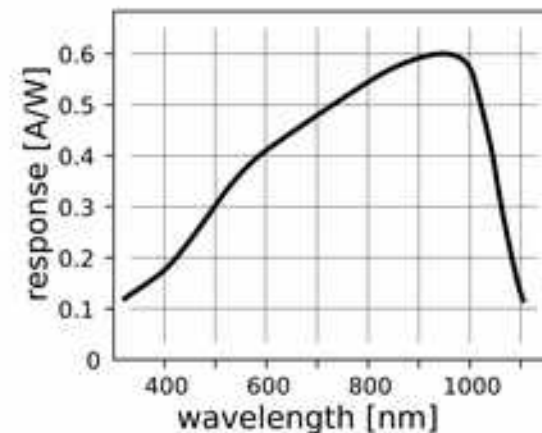


Grow vs Counted Individuals

First interaction with the photons (and/or particles)

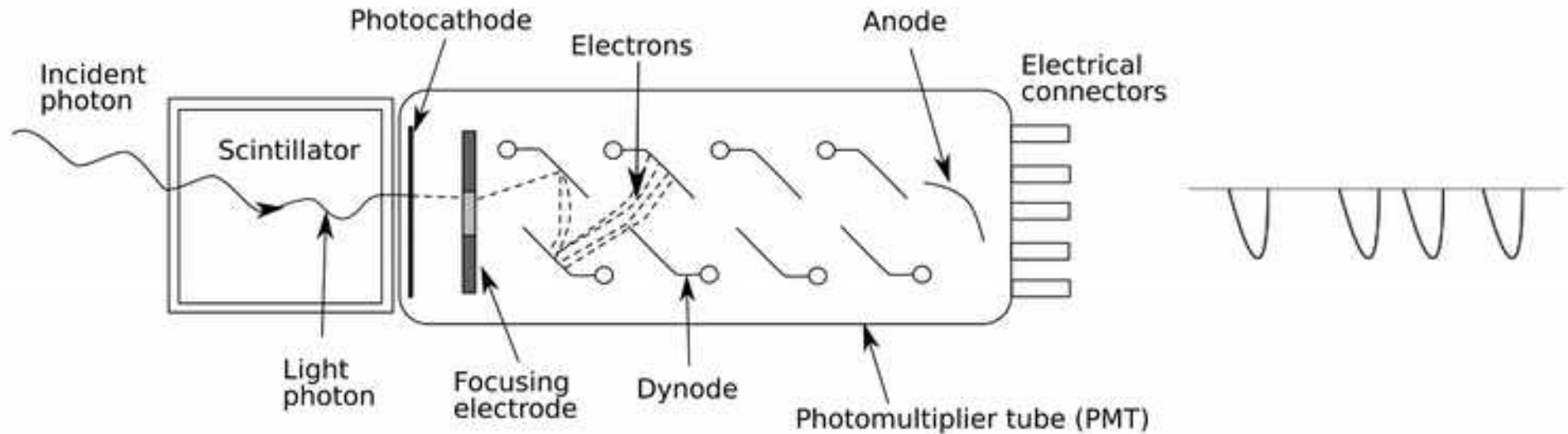- **Photon counters**: count individual bursts of **photon bundles** or **single photons** (e.g. **PMTs** and **avalanche diodes or SPADs**)
- **Photomultipliers**: if photons arrive at the detector with **low-enough frequency**



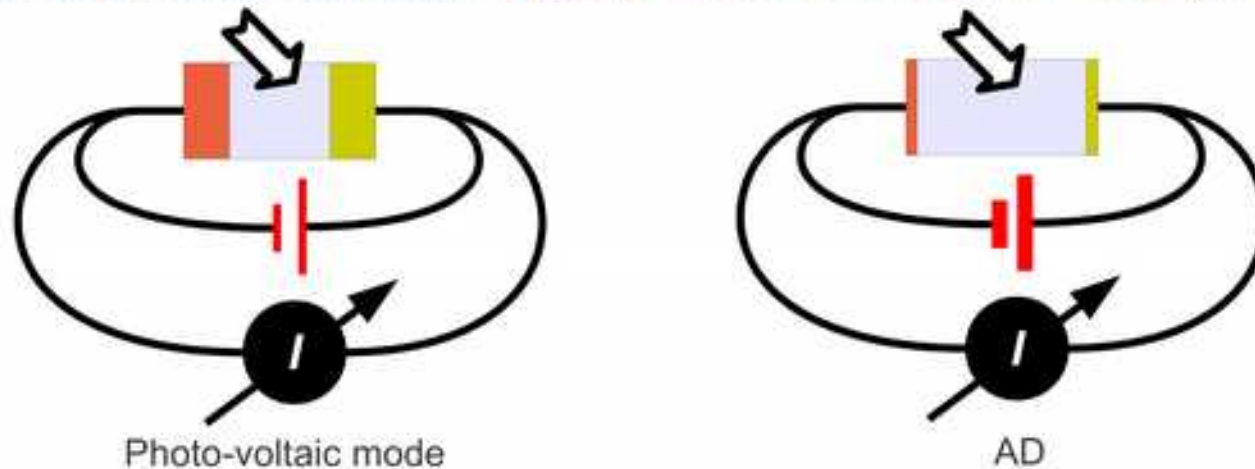- **Single Photon Avalanche Diodes (AD)**: PN junctions under strong reverse-bias



Grow vs Counted Individuals

First interaction with the photons (and/or particles)

- **Photon counters**: count individual bursts of **photon bundles** or **single photons** (e.g. **PMTs** and **avalanche diodes or SPADs**)
- **Avalanche Diodes (AD)** are PN junctions **reverse-biased** just **below** the break-down voltage such that single-photon induced electrons are accelerated within a few μms


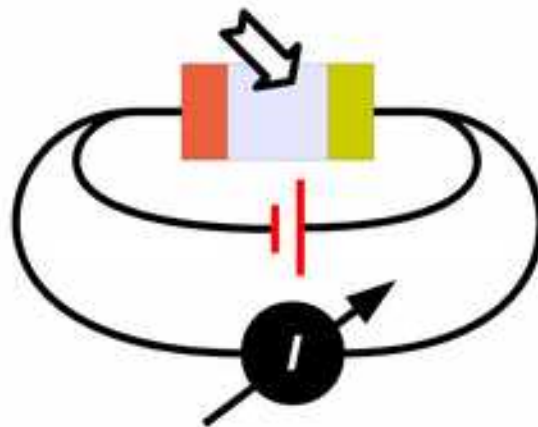


Photo-voltaic mode

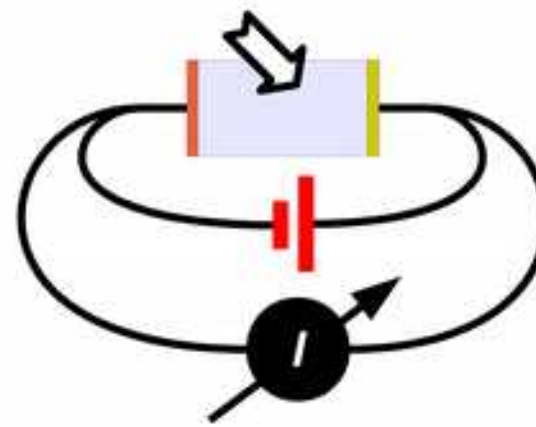

AD

- **Single-Photon Avalanche Diodes (SPAD)** are PN junctions **reverse-biased** just **above** the break-down voltage. When a photon strikes, bias voltage is dropped down **below the threshold** (but not to break-down) for a short time (e.g. 100 ns) by carefully designed electronics to recover, such that the detector is ready for the next detection
- **SPADs** can also be used for **time-resolved** techniques as they can provide information on photons **time of arrival** in addition

Position Sensitive Architecture

First interaction with the photons (and/or particles)

- Detect particles with the sensitivity of **where** they land; two main **paradigms**:

→ **Resistive charge division** on a single detection element:


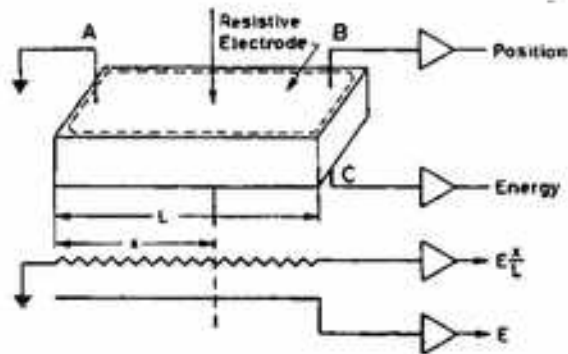


Fig. 10.14. Layout of a one-dimensional continuous position-sensitive detector using resistive charge division. A simplified equivalent circuit is shown below

* From Leo, p. 227

$$Position = \frac{B}{C}$$

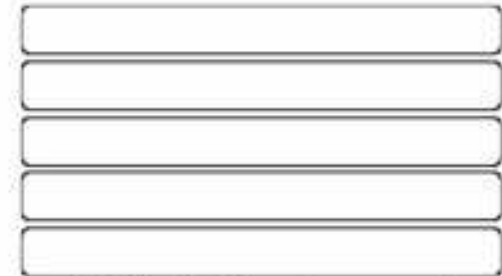

A hybrid: Discrete array of resistive charge division

→ **Discrete array** of individual detection elements:


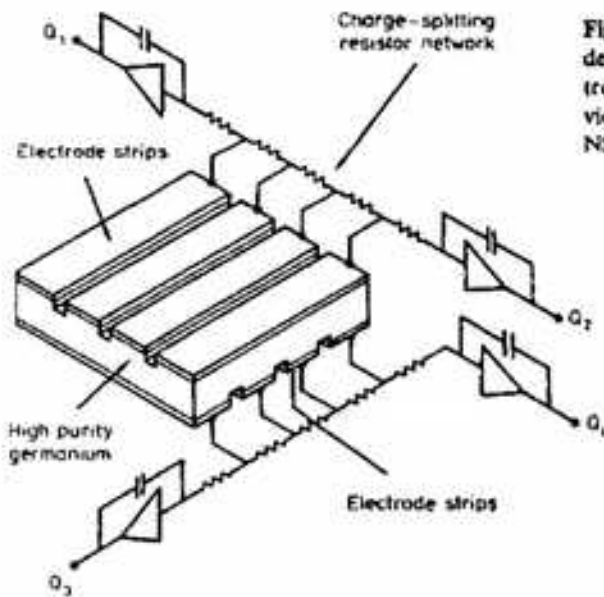


Fig. 10.15. Layout of a two-dimensional matrix detector. To reduce the readout electronics, the electrodes may be connected to an external resistive divider [from Gerber et al.: IEEE Trans. Nucl. Sci. NS-24, No. 1, 182 (1977)]

* From Leo, p. 229

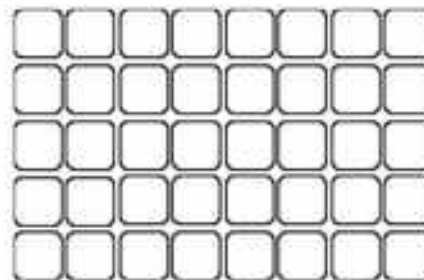


Pixel detector




MEDIPIX

Time Resolved Architecture

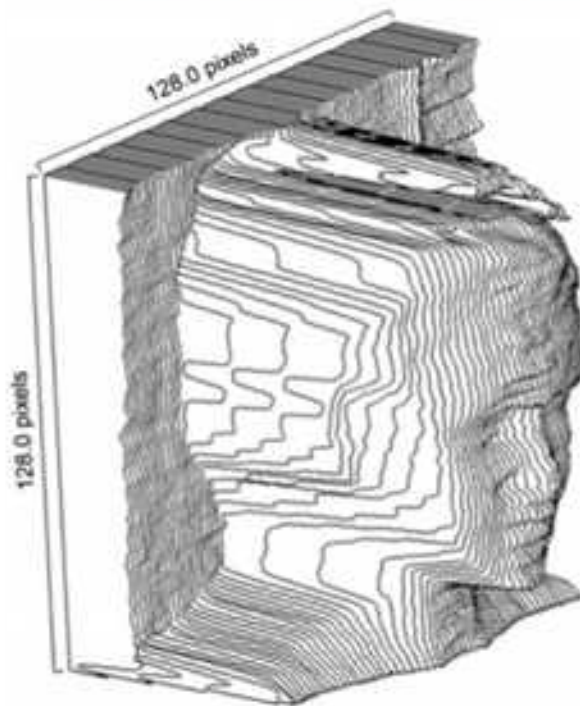
Flash the sample, start a timer, acquire single photons **and** their arrival times



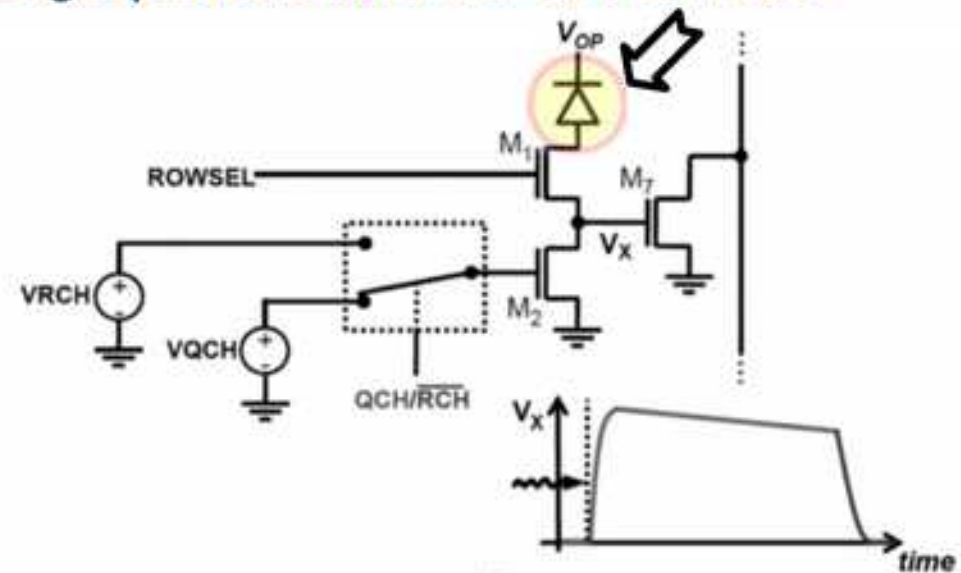
A 128 128 Single-Photon Image Sensor, With Column-Level 10-Bit Time-to-Digital Converter Array, IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. 43, NO. 12, DECEMBER 2008



(a)

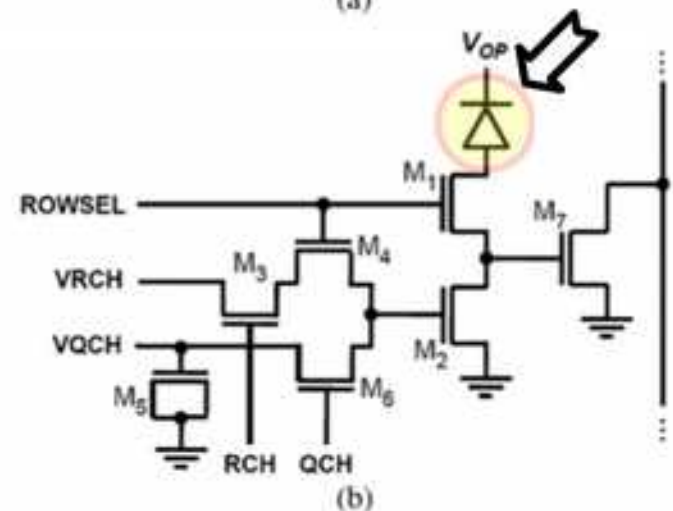

(b)


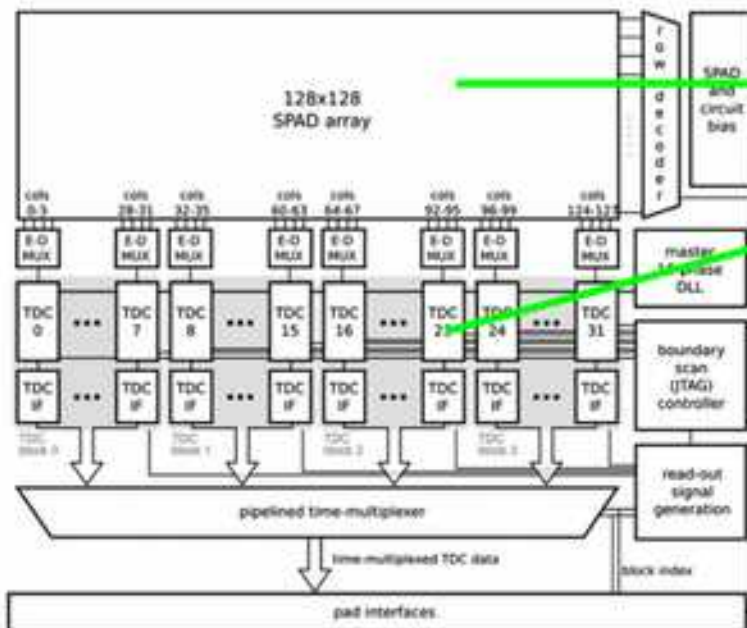


- Like an ordinary pixel detector (e.g. **CCD**)
- However measures "**time**" instead of "**color**" (e.g. **TPC**)
- Generates **3D** and **color-less** images

Time Correlated Architecture

First interaction with the photons (and/or particles)

- Measuring the profile of a **fast** (e.g. fluorescence, from ps to ns) and/or **weak** decay is tricky
- Recovering not only the **lifetimes** but also the **decay shape** requires the decay to be represented by at least 10s of samples
- The idea:
 - Meet the single photon counting **condition**(?)
 - Make your detector **fast**
 - Decrease the number of **photon creation** at the source
 - **Excite** the system to be probed (e.g. via a laser)
 - **Count** photons **per** reference excitation
 - Fill a **histogram** to visualize **decay profile**

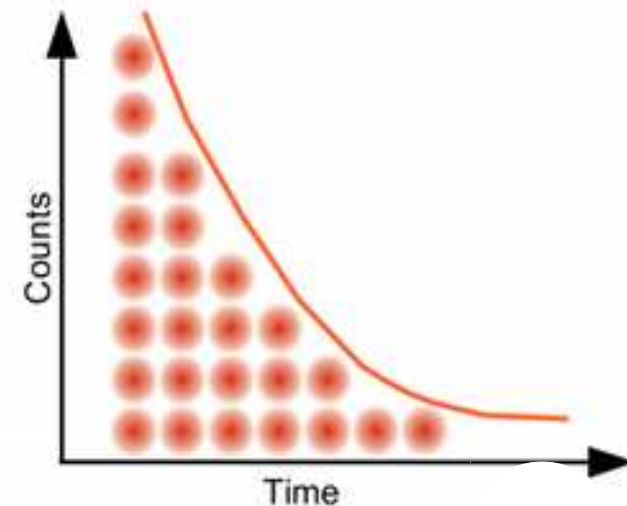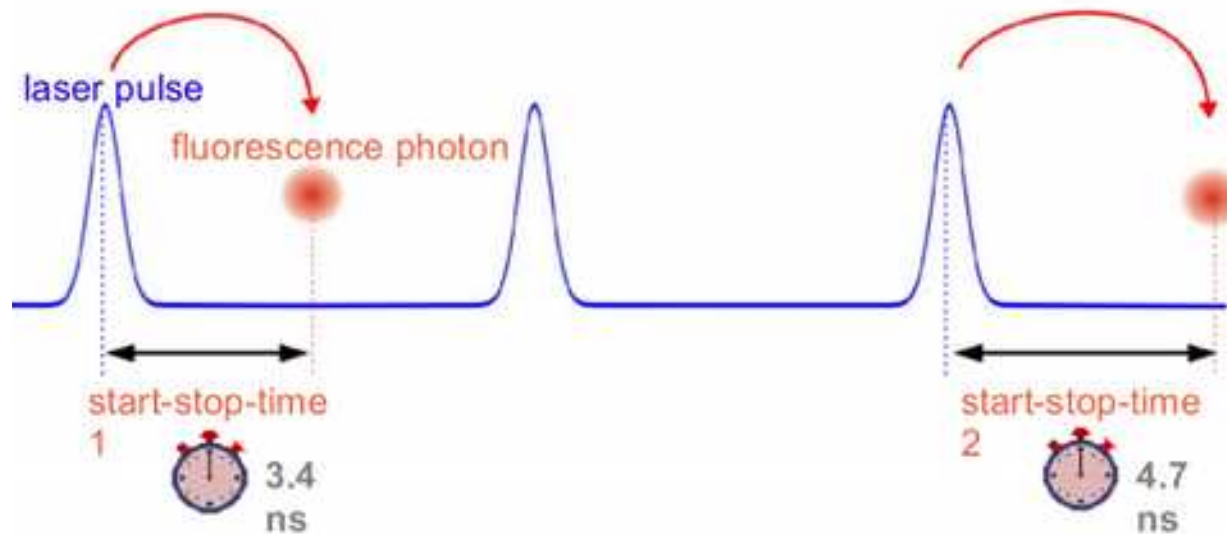

Introduction to the Design of Full-Custom Front-End & Data Transmission ASICs*

Table of Contents

■ The Big (but Brief) Picture

- Briefly **front-end** - FE
- Briefly **read-out** - RO
- Briefly **serializer** - SER
- Briefly **phase-lock loop** - PLL



■ Detector Front-End ASICs

- **Pre-Amp**: basic idea – V_{OUT} / V_{IN}
- **Transconductance** of a transistor - g_m
- Evolving a **single-stage amplifier** into a real-world application

■ Feed-Back Concept

- A **qualitative** introduction
- **Natural frequency** concept - ω_n
- Real-world examples:
 - **Binary** read-out
 - **Time-over threshold**
- Adjusting/optimizing loop behavior
 - **Damping ratio**

■ Reminder on Detectors

- Photodetectors **vs** photon counters
- **Position-sensitive** detectors
 - Resistive charge division
 - Discrete array of elements
- **Time-resolved** detection

■ Processing Technology

- **Transistor** switch – A masterpiece
 - **Lithography**
 - Formation of an **nMOS** transistor
- VLSI design flow
 - Parasitic **extraction**
- Real-world ASIC examples


■ Radiation Tolerance Issues

- Definitions:
 - **Single event upset, analog single event transient, latch-up**
- **Simulating** radiation effects on analog circuits

Pre-Amplifier

The first stage of the *interpretation*

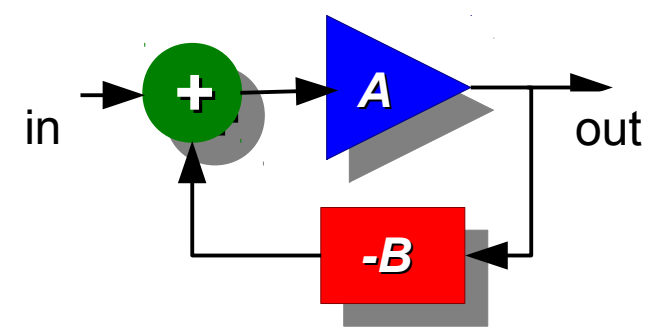
- **Standardized** experimental techniques **over time**
- Our discussion on **intuitive** & **descriptive** level
- Three types of pre-amplifiers:



$$T = \frac{V_{OUT}}{V_{IN}} = \frac{A}{1 + AB}$$

sage: $T(A, B) = A / (1 + A * B)$
 sage: $T.limit(A=infinity)$
 (A, B) |--> 1/B



- ➔ **Voltage sensitive:** usually **not preferred** due to the fact that, for a given amount of charge generated by the detector (Q_{DET}), the **output voltage** of the detector (V) is a **function** of the **effective capacitance** (C_{EFF}) of the detector which is **variable**
- ➔ **Current sensitive:** **not preferred** because they are **suitable** to be used with **low impedance** devices, **however** radiation **detectors** have usually **high impedance**
- ➔ **Charge sensitive:** **preferred** type because its output is **only** a function of the charge (Q_{DET}) and a fixed C_F , provided that amplifier **gain** is sufficiently **high**

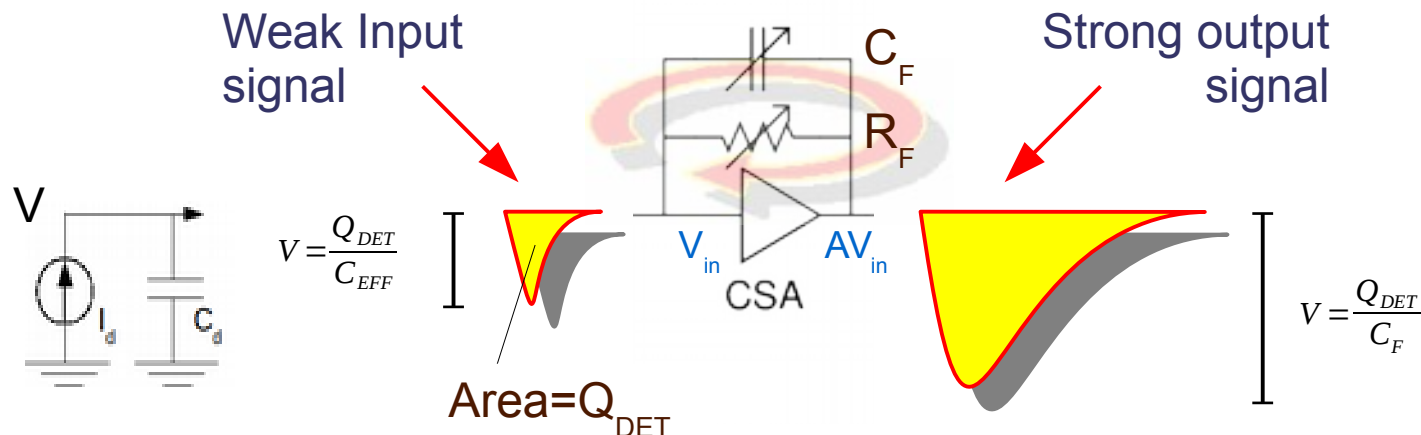

Amplifier Basic

How to amplify something

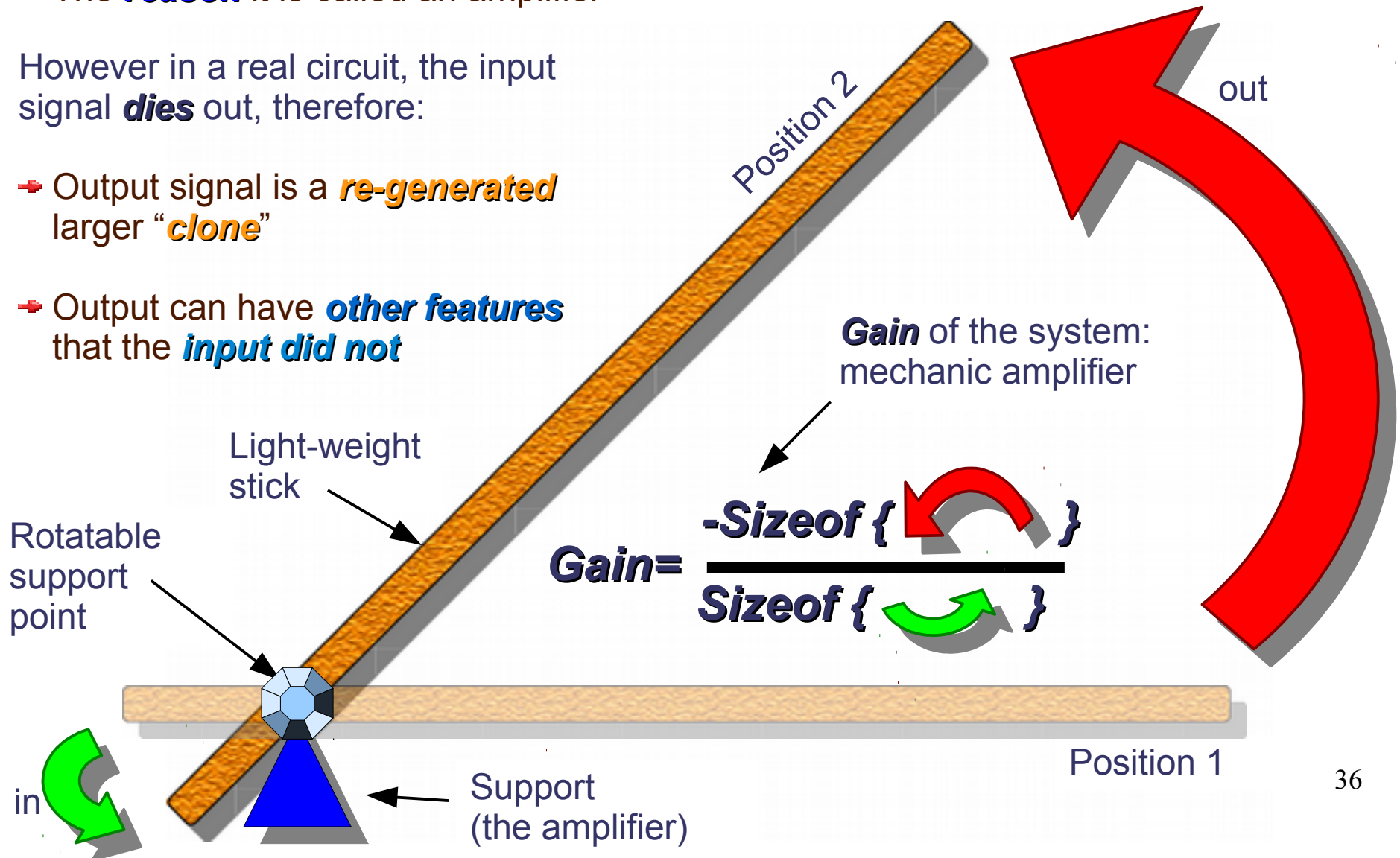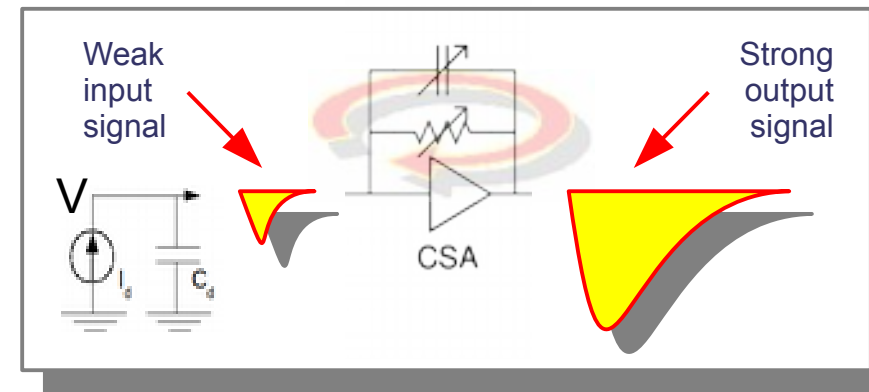
- We want a **small change** in the input to **cause** a **big change** at the output
 - The **reason** it is called an amplifier
- However in a real circuit, the input signal **dies** out, therefore:
 - Output signal is a **re-generated** larger "**clone**"
 - Output can have **other features** that the **input did not**




Transconductance - g_m

Figure-of-merit for a transistor

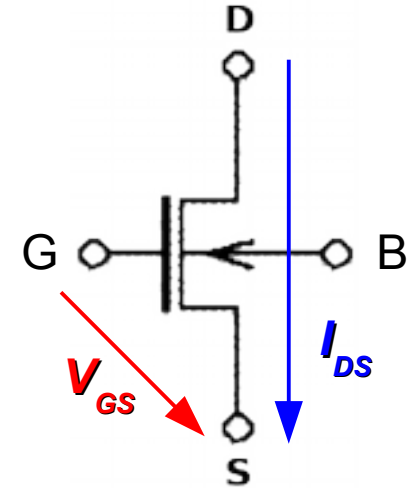- Define a figure-of-merit (**FOM**) for a single nMOS
 - **How well** a transistor **converts** voltage into current
 - From input V_{GS} to output I_{DS}




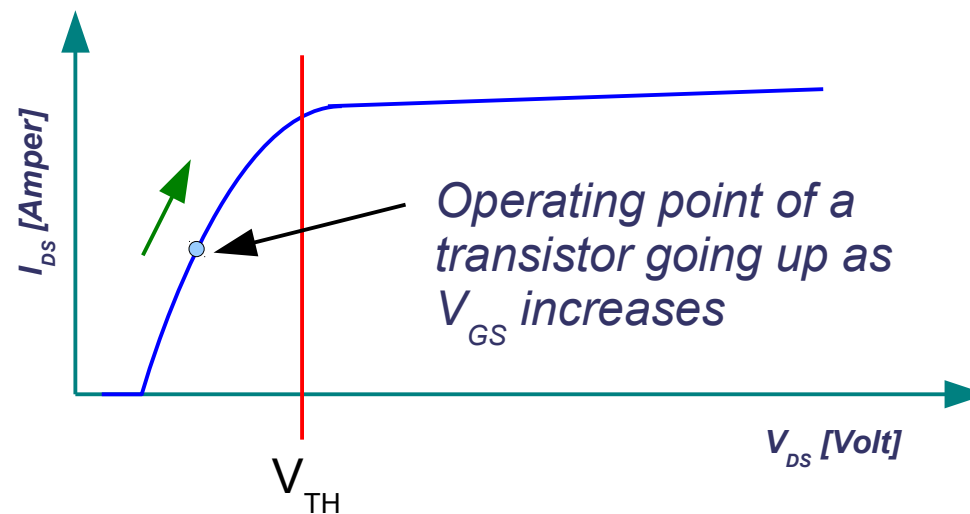
$$g_m = \frac{dI_{DS}}{dV_{GS}} = \frac{2I_D}{V_{GS} - V_{TH}}$$



Basic CMOS Amplifier


Single-stage **common-source** amplifier and its evolution into a complete circuit

- Sink current through R_D
 - As **in** increases, **out** decreases (faster)
- $-g_m R_D$ suggests that we should increase the **load impedance** to have **higher voltage gain**
 - An **ideal** current source has **infinite impedance**
- A **current mirror** is a practical **current source**
 - Simply a transistor biased as a current source
- Transconductance (g_m) **increases** with current
 - Supply **additional current** to the gain device to have higher gain

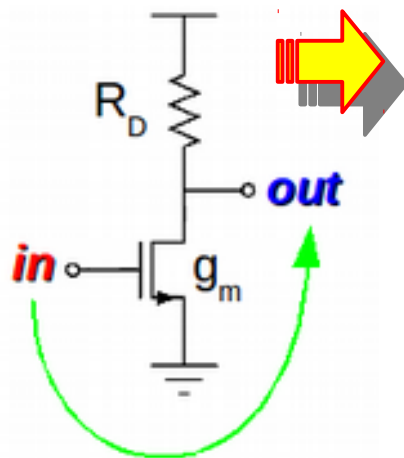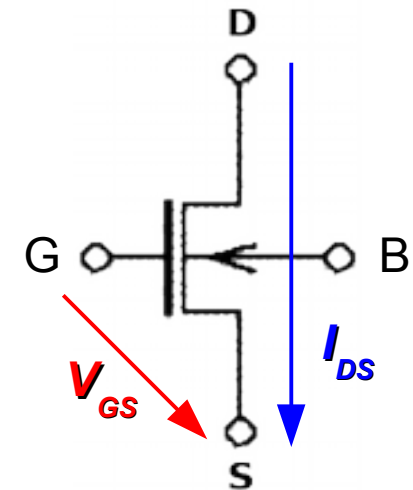


$$A_V = -g_m R_D$$

Common-source amplifier

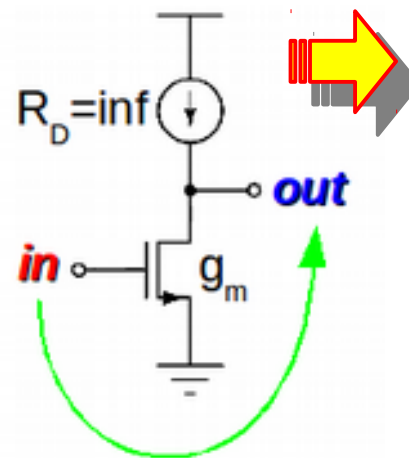


$$A_V = -g_m r_o$$

Common-source amplifier

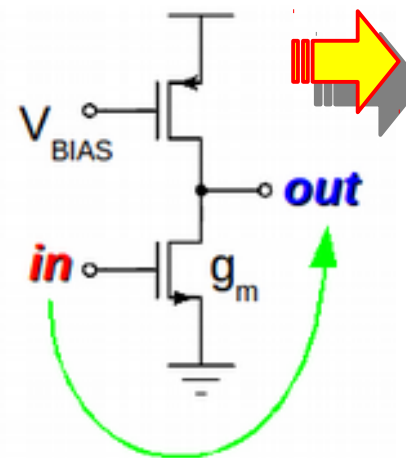

$$A_V = -g_m (r_{o1} || r_{o2})$$

Common-source amplifier

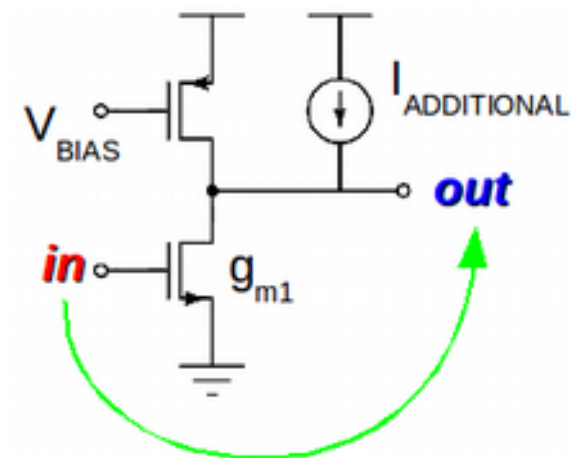


$$A_V > -g_m (r_{o1} || r_{o2})$$

Common-source amplifier with current source load featuring higher gain due to increased current

Basic CMOS Amplifier



Single-stage common-source amplifier and its evolution into a complete circuit

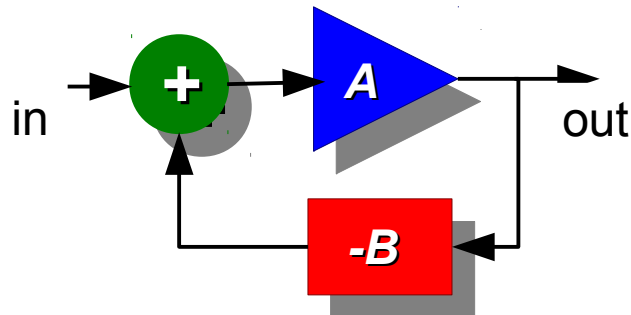- Add the feedback network C_F & R_F forming the B such that
 - For high enough A_V , closed loop gain is $1/B$




$$T = \frac{V_{OUT}}{V_{IN}} = \frac{A}{1 + AB}$$

sage: $T(A, B) = A/(1+A*B)$
 sage: $T.limit(A=infinity)$
 (A, B) |--> 1/B

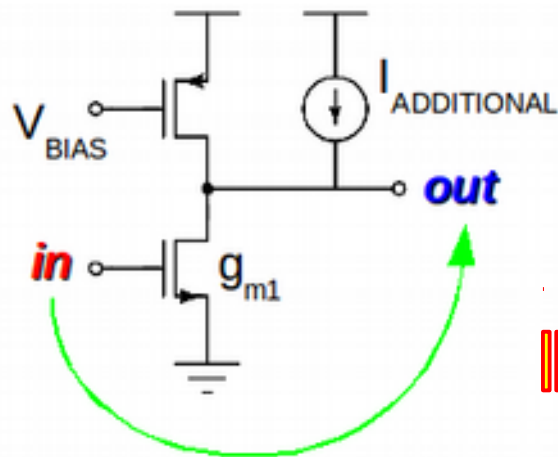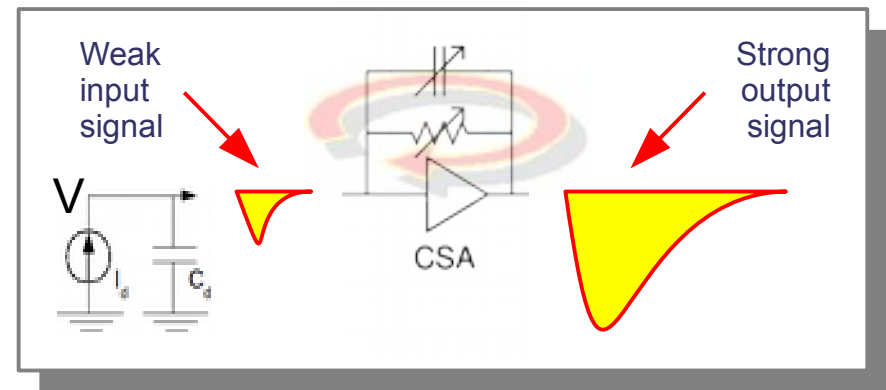

$$A_V > -g_m(r_{o1} || r_{o2})$$

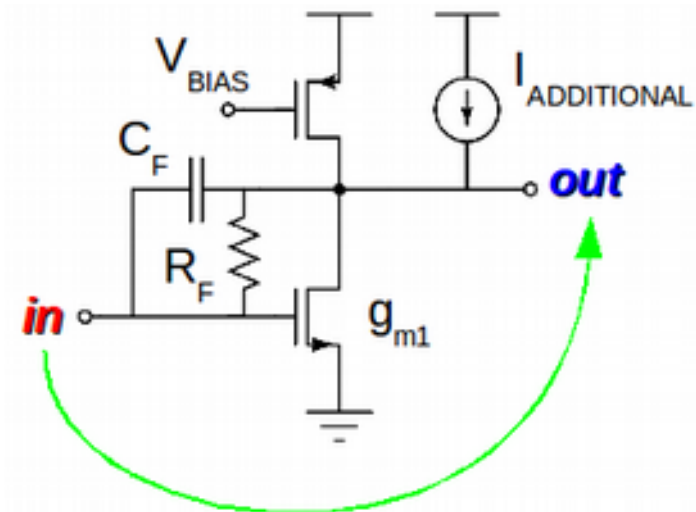Common-source amplifier with current source load featuring higher gain due to increased current





Full circuit with feedback network


Basic CMOS Amplifier

Avoid loading effect of the resetting resistor

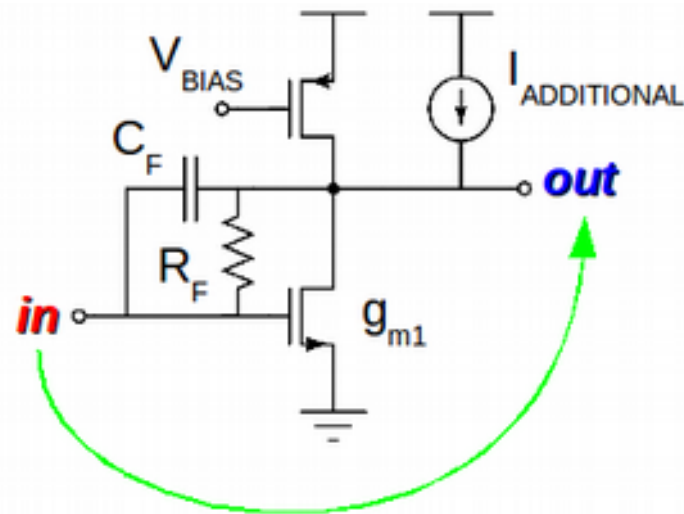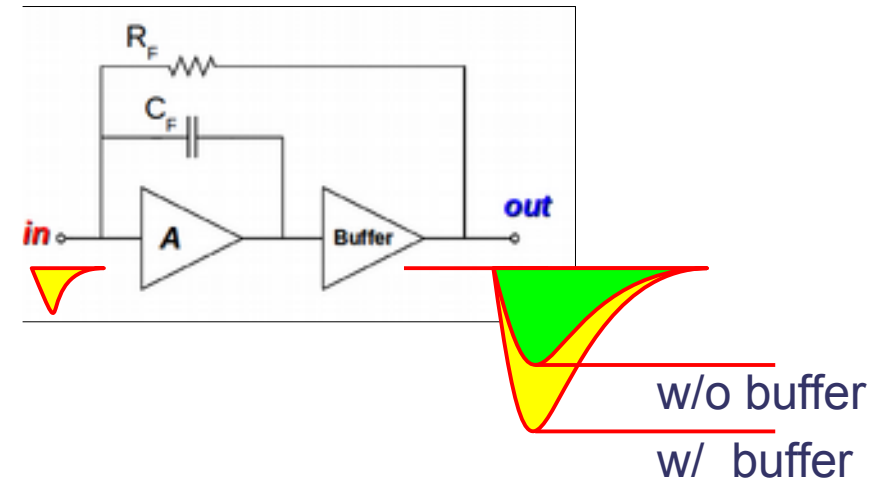- Problem: while C_F is charged, R_F resets **at the same time**
 - ➔ **Lowering** the voltage gain, therefore:
 - ➔ **Loading effect** of the feedback **resistor** should be **avoided**
 - ➔ **Integration** and **resetting** should be **de-coupled**
 - ➔ Employing a **buffer** is one of the possible solutions



Full circuit with feedback network


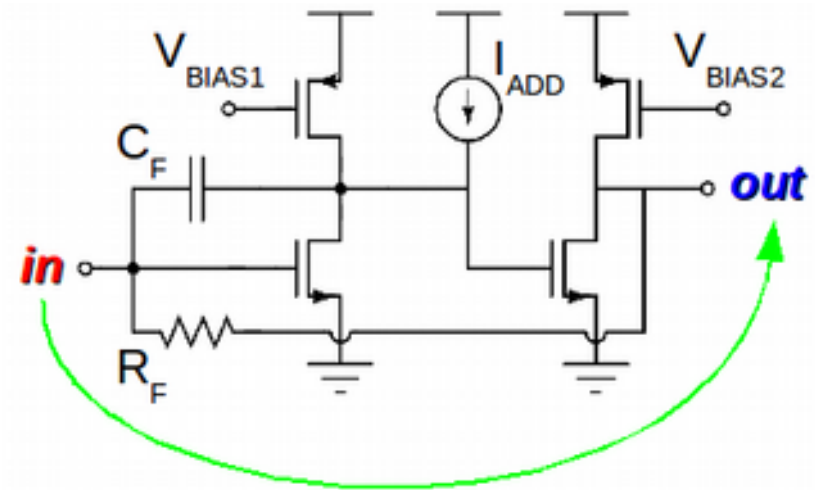


Full circuit avoiding resistor loading effect

Pre-Amplifier

Full circuit (currently in use at a RICH detector)

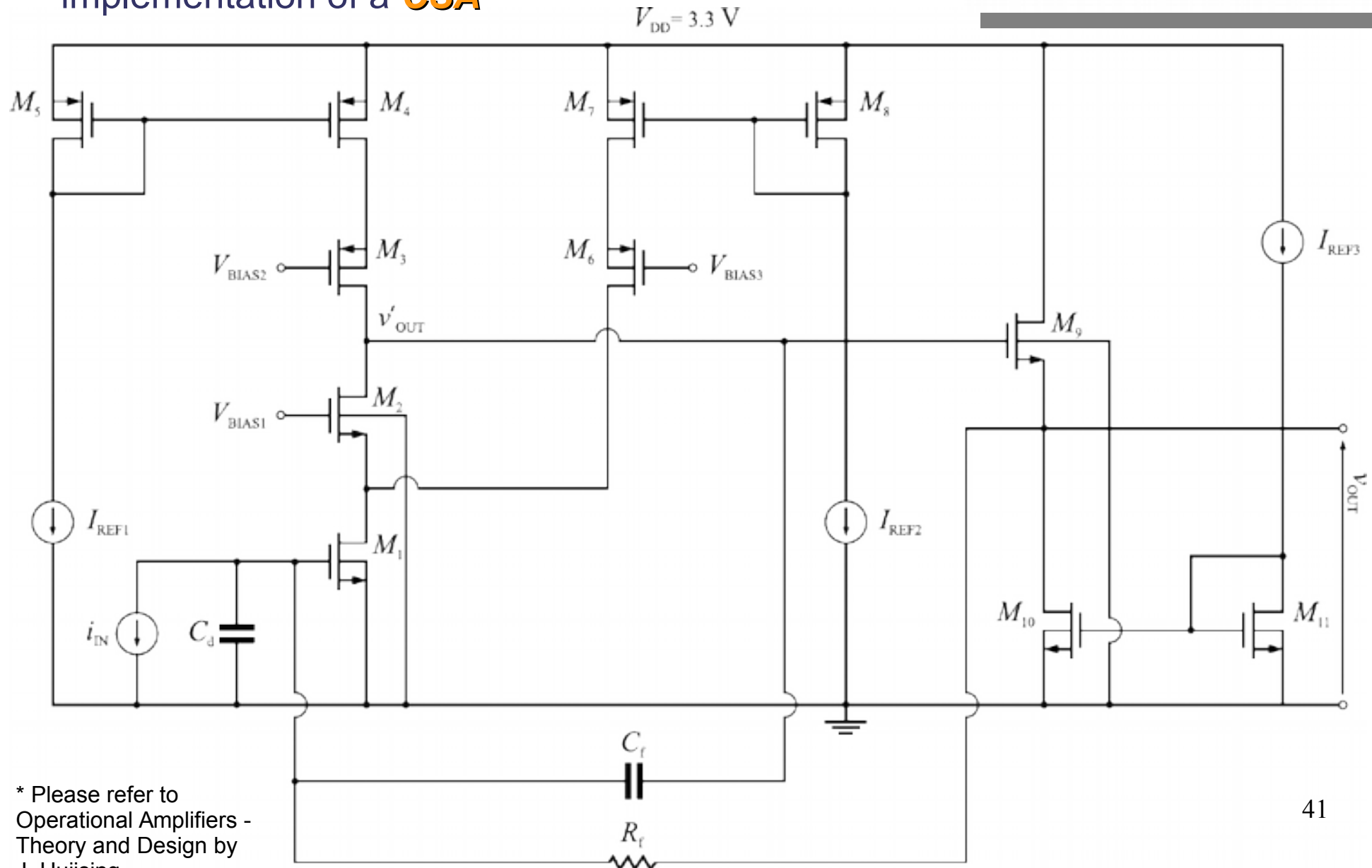
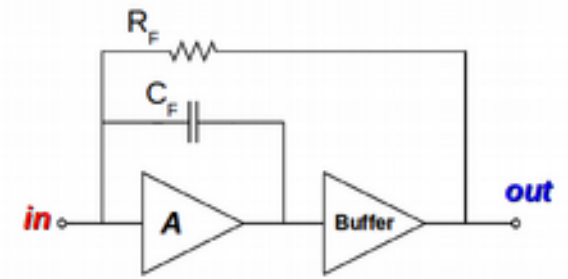
- Actual CMOS device-level implementation of a **CSA**



* Please refer to
Operational Amplifiers -
Theory and Design by
J. Huijsing


Differential Amplifier

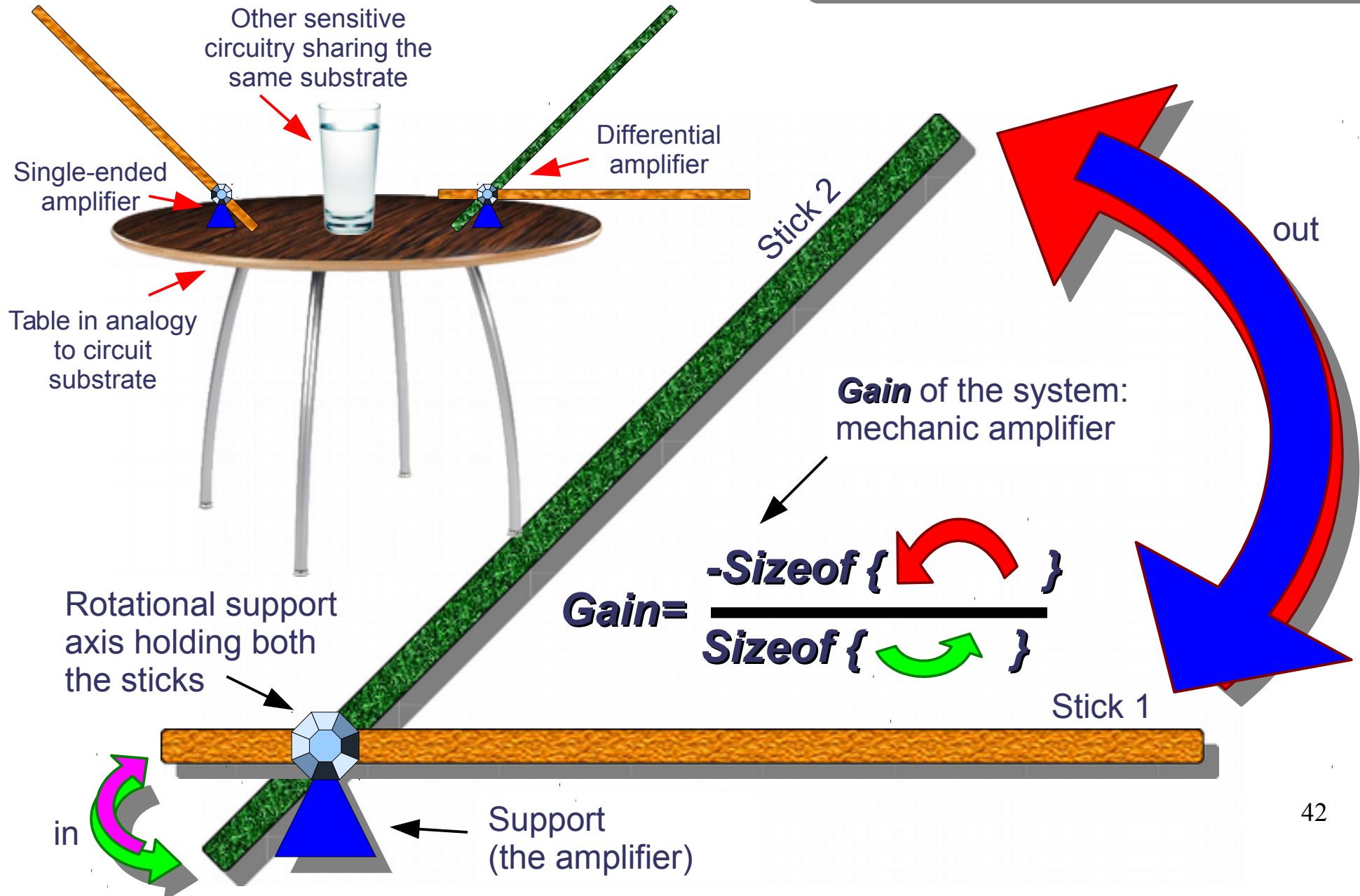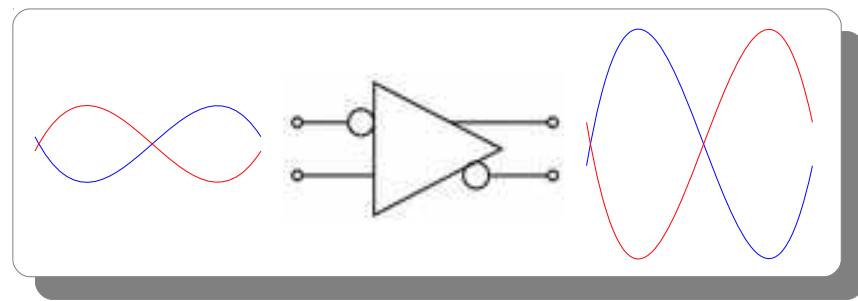Generating *less noise* (also for others)
in the cost of more *complex design*




Differential Signaling



Rejecting noise

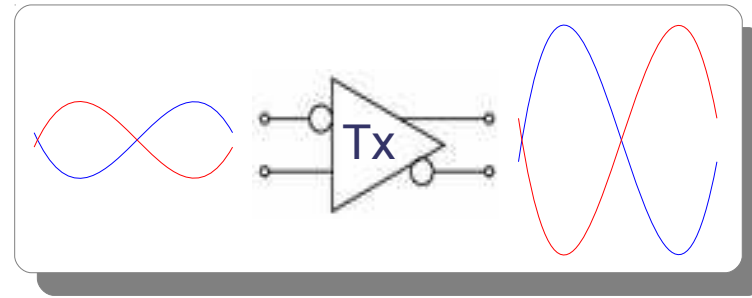

- The **information** Tx generates is in the **difference**
 - ➔ Signal creates **complementary current images** on the substrate
 - ➔ Generating **less noise** for neighboring circuitry
- Rx **compares** the voltage levels of the pair
- Any noise source should affect both of the lines similarly
 - ➔ Generating almost **identical transients** on both of the wires
 - ➔ Pair wires are **close** to each other
- Practically high **noise rejection** is feasible

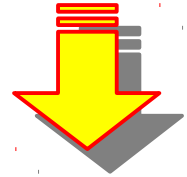


Metal wires

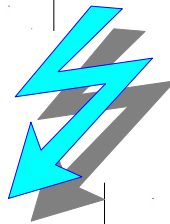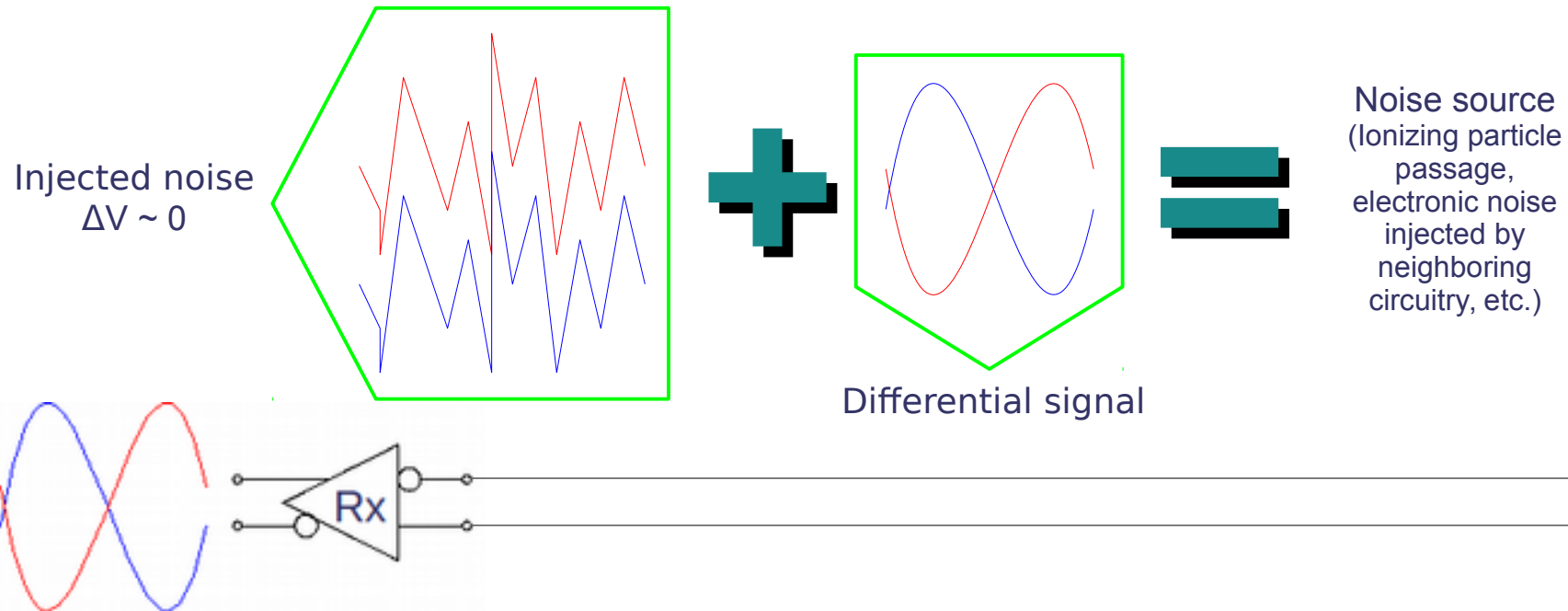


Differential Signaling

Differential gain stage

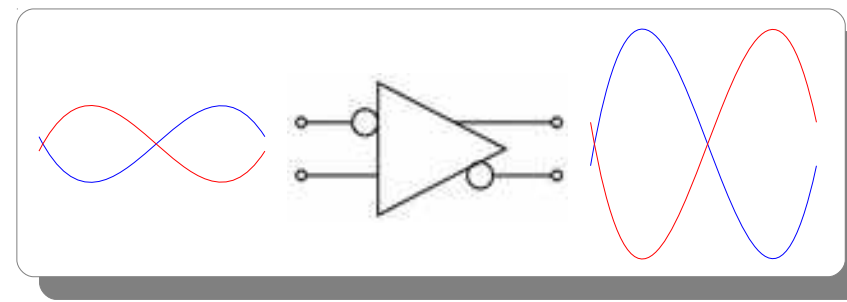

- Sink current through R_D
 - ➔ As **in** increases, **out** decreases (faster)
- Double the structure to act on both the signals
 - ➔ Drawback: signals can be identical (no differential information)
- Steer the current either through one inverter or the other
 - ➔ Transition at the input changes the path through which the current is steered
 - ➔ Unless metastable, the amplifier has always differential information at the output

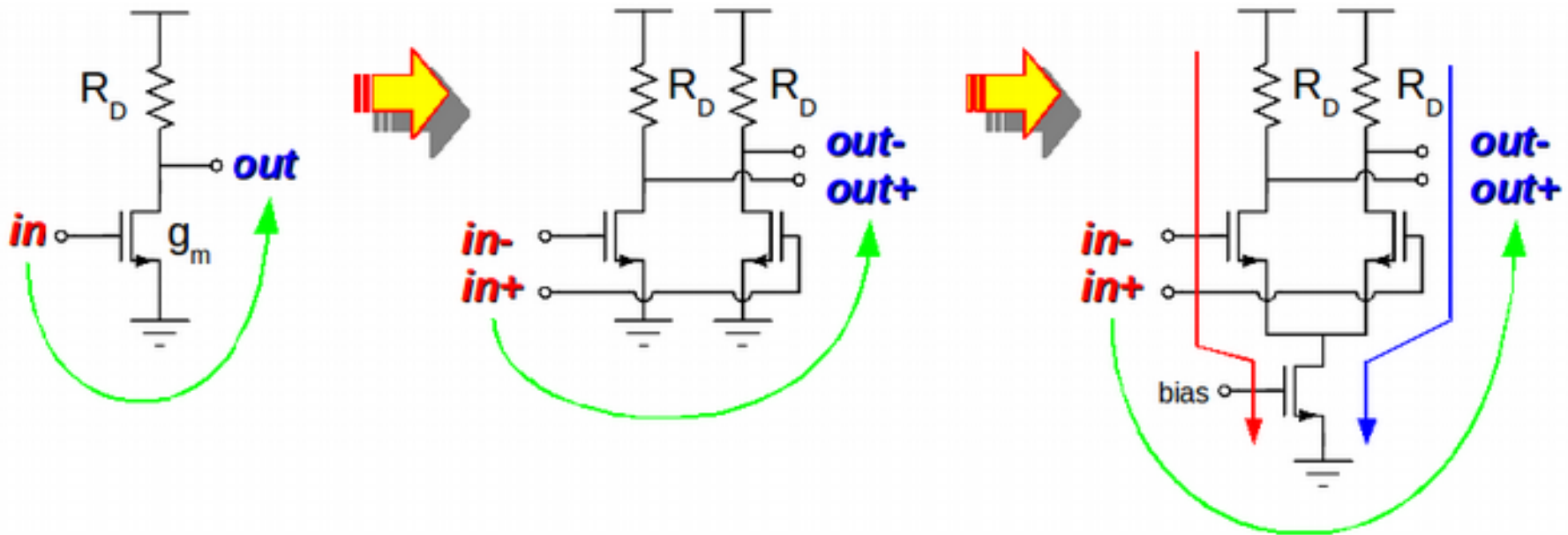

Introduction to the Design of Full-Custom Front-End & Data Transmission ASICs*

Table of Contents

■ The Big (but Brief) Picture

- Briefly **front-end** - FE
- Briefly **read-out** - RO
- Briefly **serializer** - SER
- Briefly **phase-lock loop** - PLL

■ Feed-Back Concept

- A **qualitative** introduction
- **Natural frequency** concept - ω_n
- Real-world examples:
 - **Binary** read-out
 - **Time-over threshold**
- Adjusting/optimizing loop behavior
 - **Damping ratio**

■ Reminder on Detectors

- Photodetectors **vs** photon counters
- **Position-sensitive** detectors
 - Resistive charge division
 - Discrete array of elements
- **Time-resolved** detection

■ Detector Front-End ASICs

- **Pre-Amp**: basic idea – V_{OUT} / V_{IN}
- **Transconductance** of a transistor - g_m
- Evolving a **single-stage amplifier** into a real-world application

■ Processing Technology

- **Transistor** switch – A masterpiece
 - **Lithography**
 - Formation of an **nMOS** transistor
- VLSI design flow
 - **Parasitic extraction**
- Real-world ASIC examples

■ Radiation Tolerance Issues

- Definitions:
 - **Single event upset, analog single event transient, latch-up**
- **Simulating** radiation effects on analog circuits




Semiconductor Switch - Transistor



A masterpiece

- Current conduction between **Drain-Source** as a function of **Gate-Source** voltage


3D view of a single MOS transistor

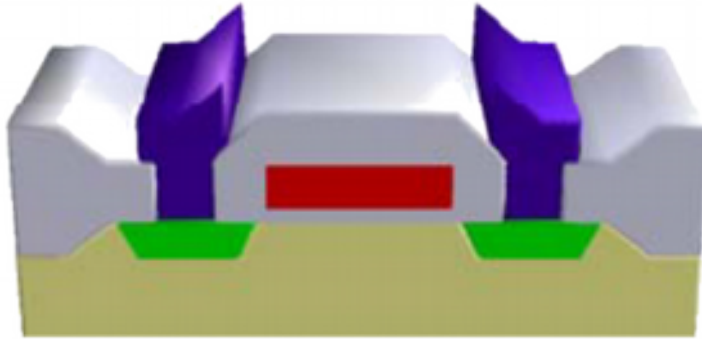

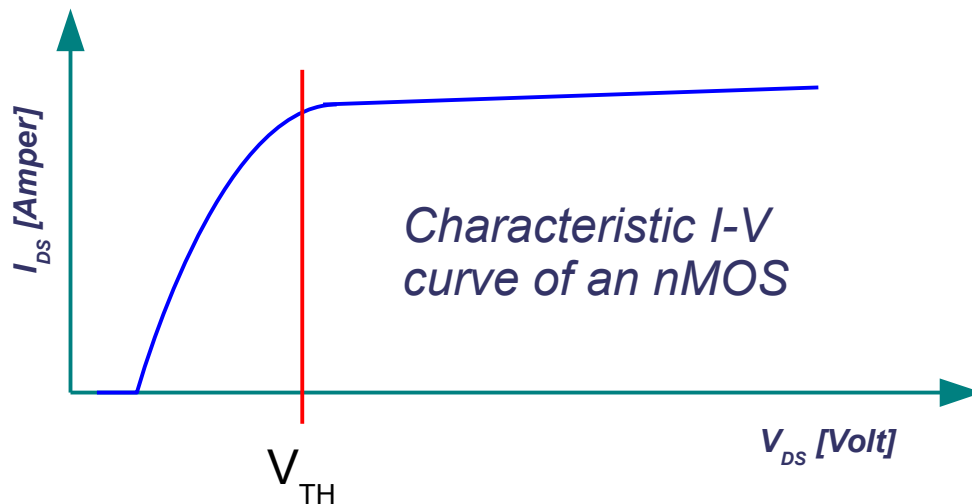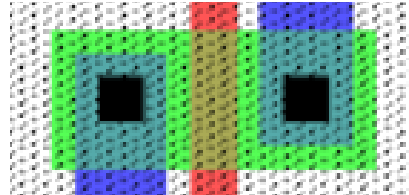
A single MOS transistor **as drawn by a designer**



Layout

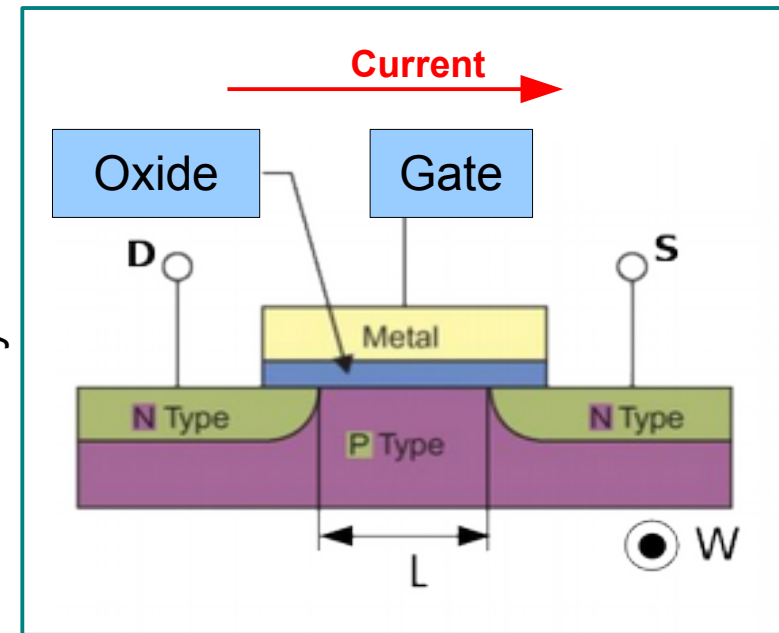


Symbol

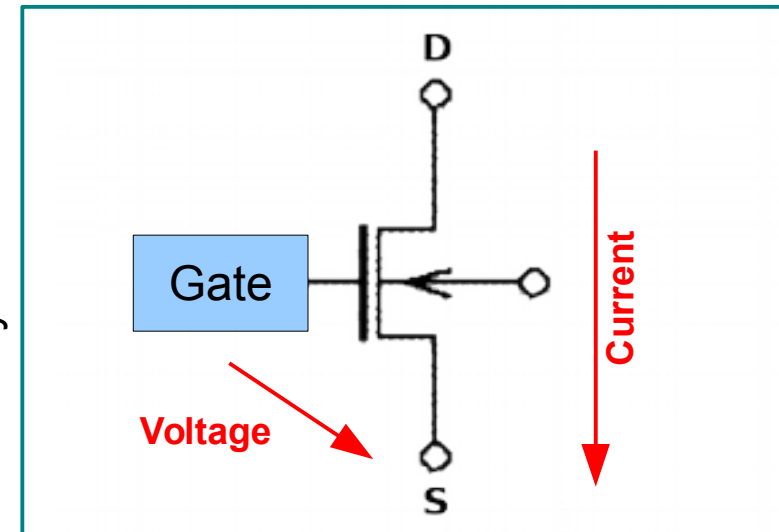



Lithography

The art of *light drawing*

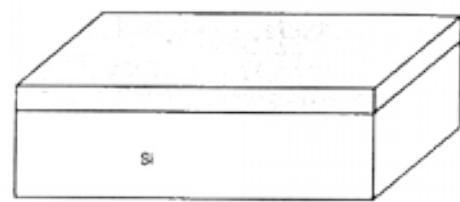- A real microelectronic circuit is like a **city** composed of **many layers**
- A specific **lithographic mask** is needed **for each layer** to be created
- As an **example** we will create a **"line"** on an **oxide layer**




Initial state

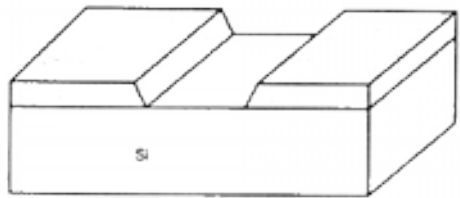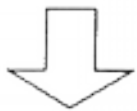




Target

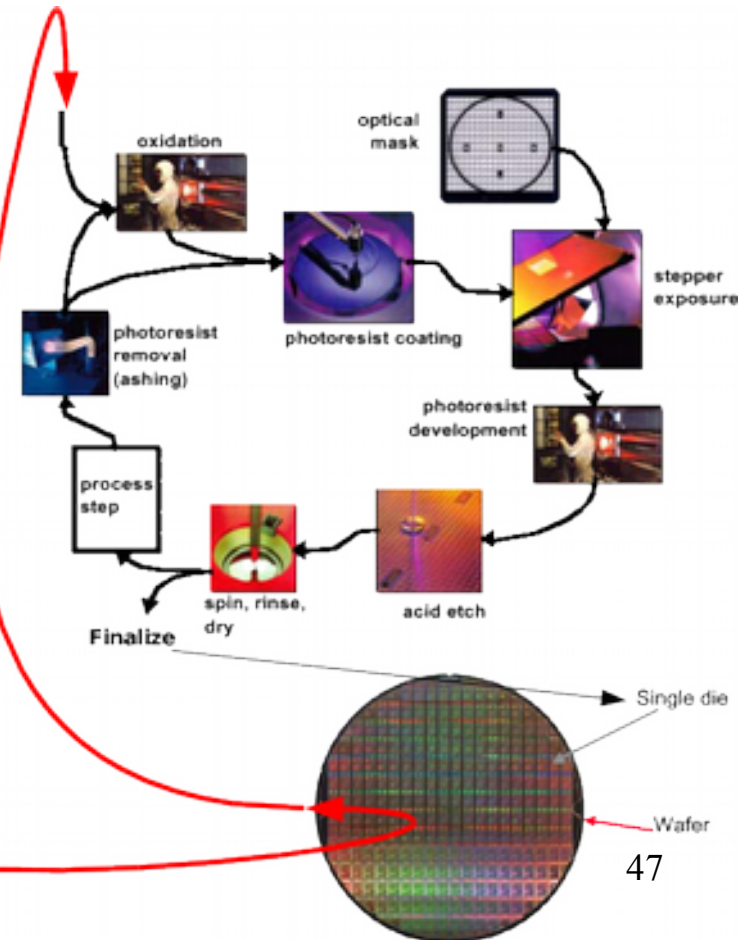The **ingot** to be sliced into **wafers**




Just to draw a single line

Seven simplified steps

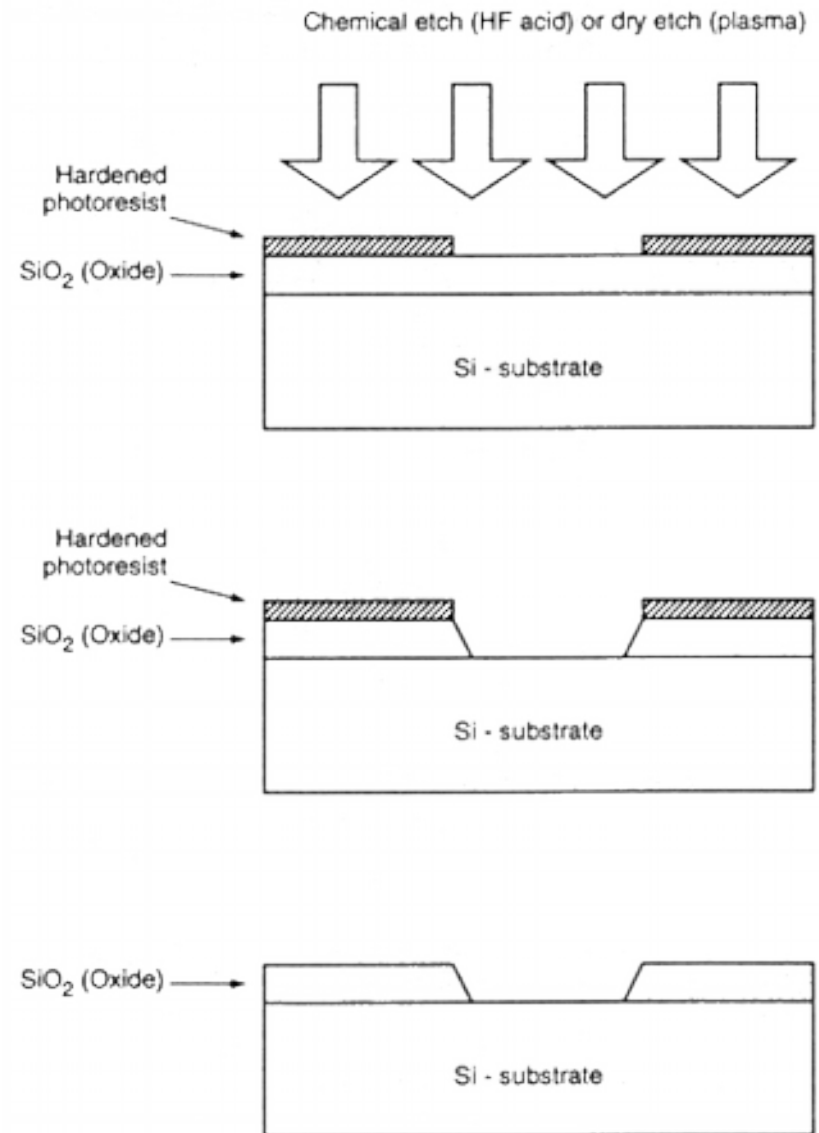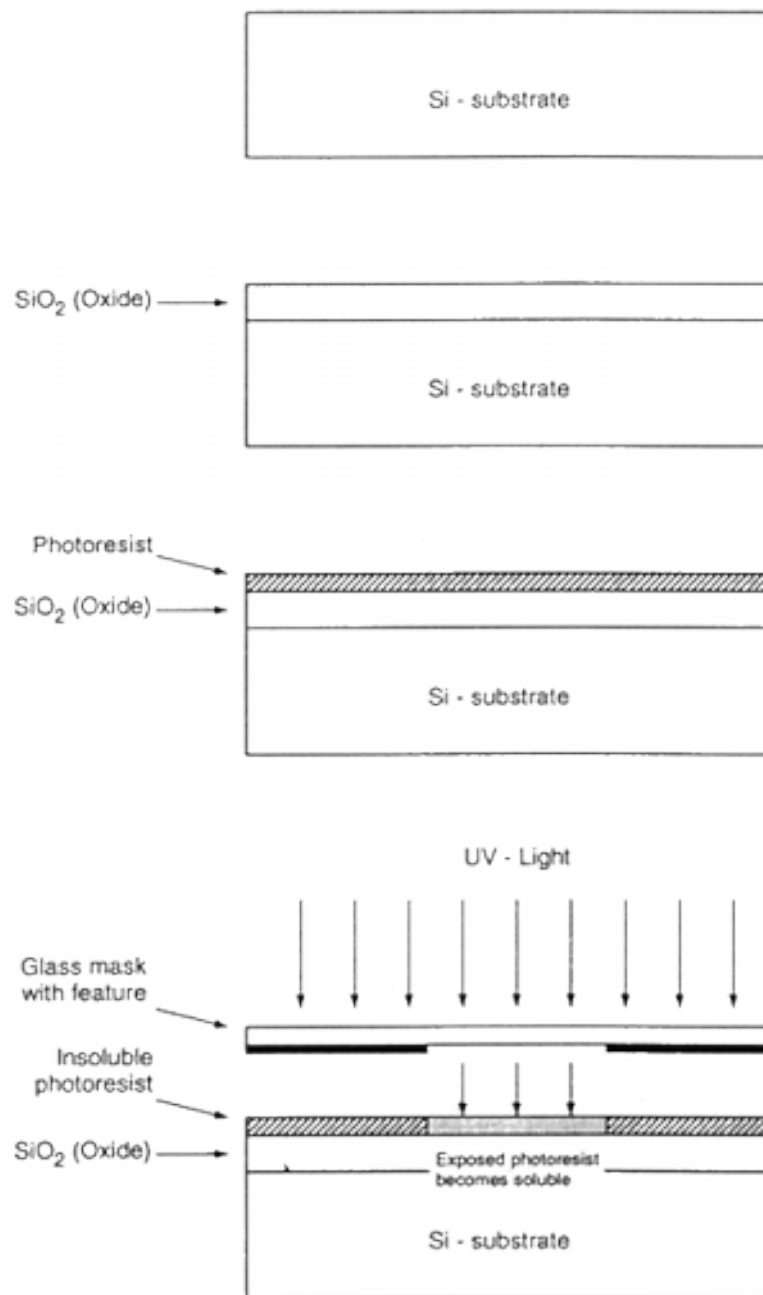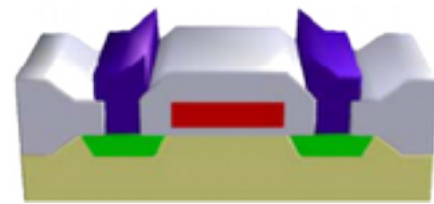

Fabrication of an nMOS


Simplified steps - Part I

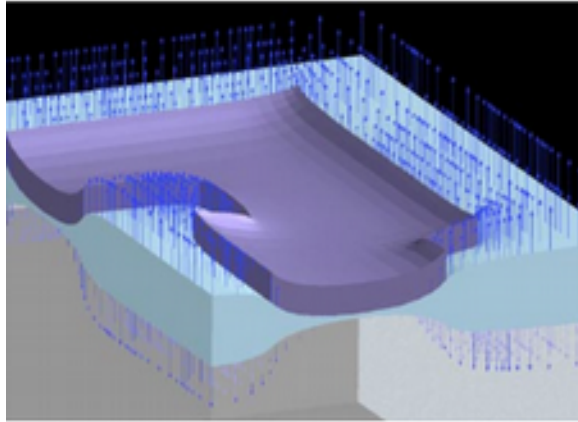

A. Definition of active area




B. Anneal and field oxide growth

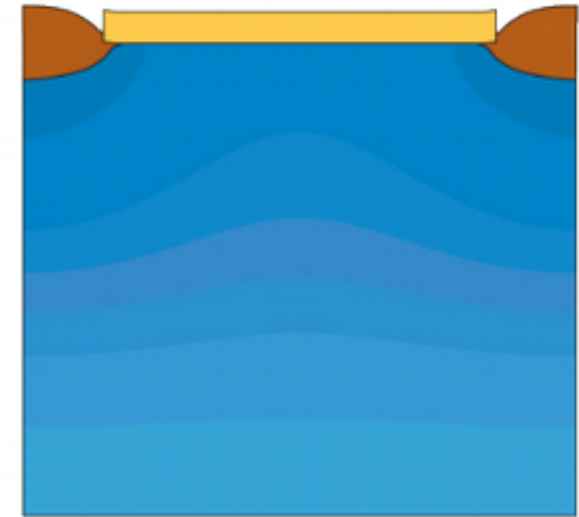


- **Nitride** defines the active areas
- **FOX** is developed
- Nitride is removed by a solvent
- Polysilicon is deposited

C. Channel implant

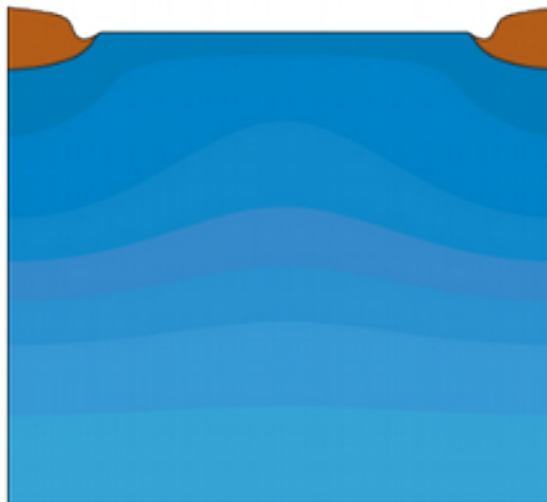

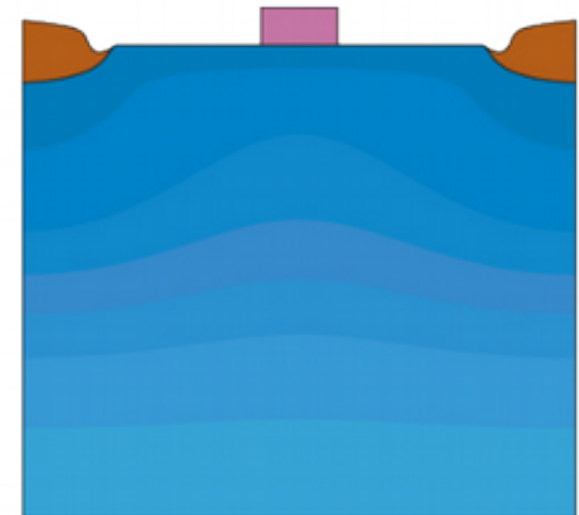D. Gate formation (polysilicon deposition)




	10^{20}
	10^{19}
	10^{18}
	10^{17}
	10^{16}
	10^{15}
	-10^{15}
	-10^{16}
	-10^{17}
Net[cm ³]	
PO	
OX	
SI	

Fabrication of an nMOS


Simplified steps - Part II

- **Spacer & active field formation**
- Dep. of **SiO₂**
- **Etching** contact holes
- **Metal** dep.


E. Spacer formation and S/D implant

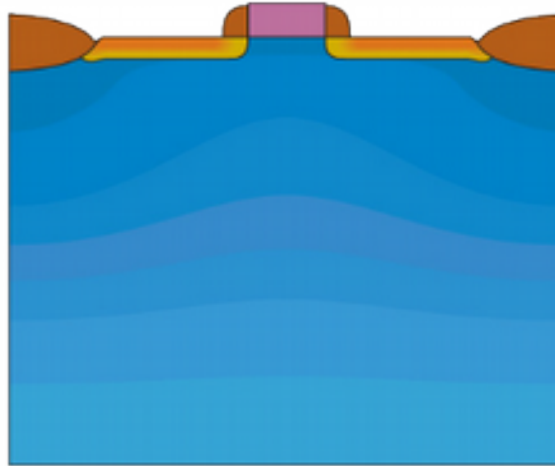


F. Oxide deposition

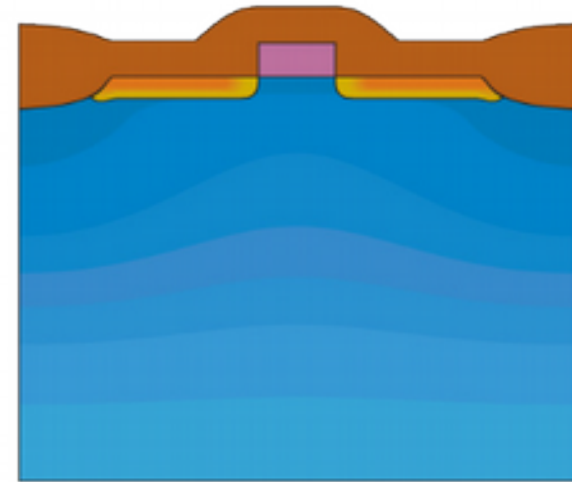

G. Contact hole etch

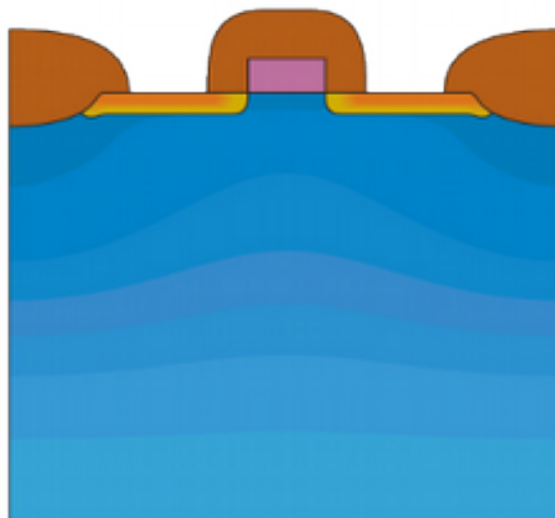


H. Metal deposition

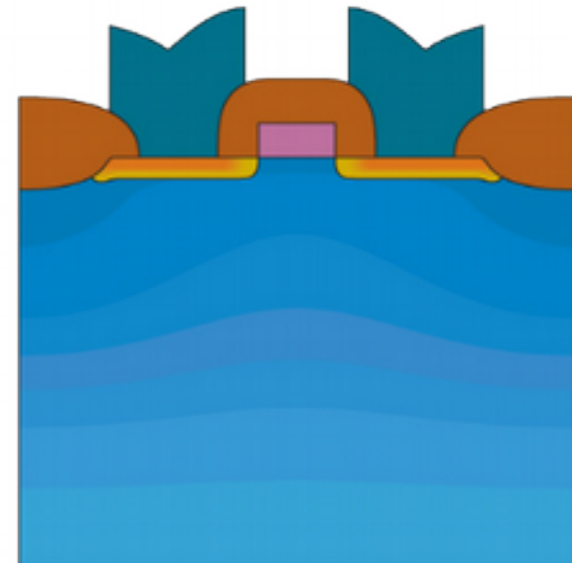

pn
10 ¹⁹
10 ¹⁸
10 ¹⁷
10 ¹⁶
10 ¹⁵
0
-10 ¹⁵
-10 ¹⁶
-10 ¹⁷
Net[/cm3]
AL
PO
OX
SI

How many layers do you see ?


A process repeated a few hundred times

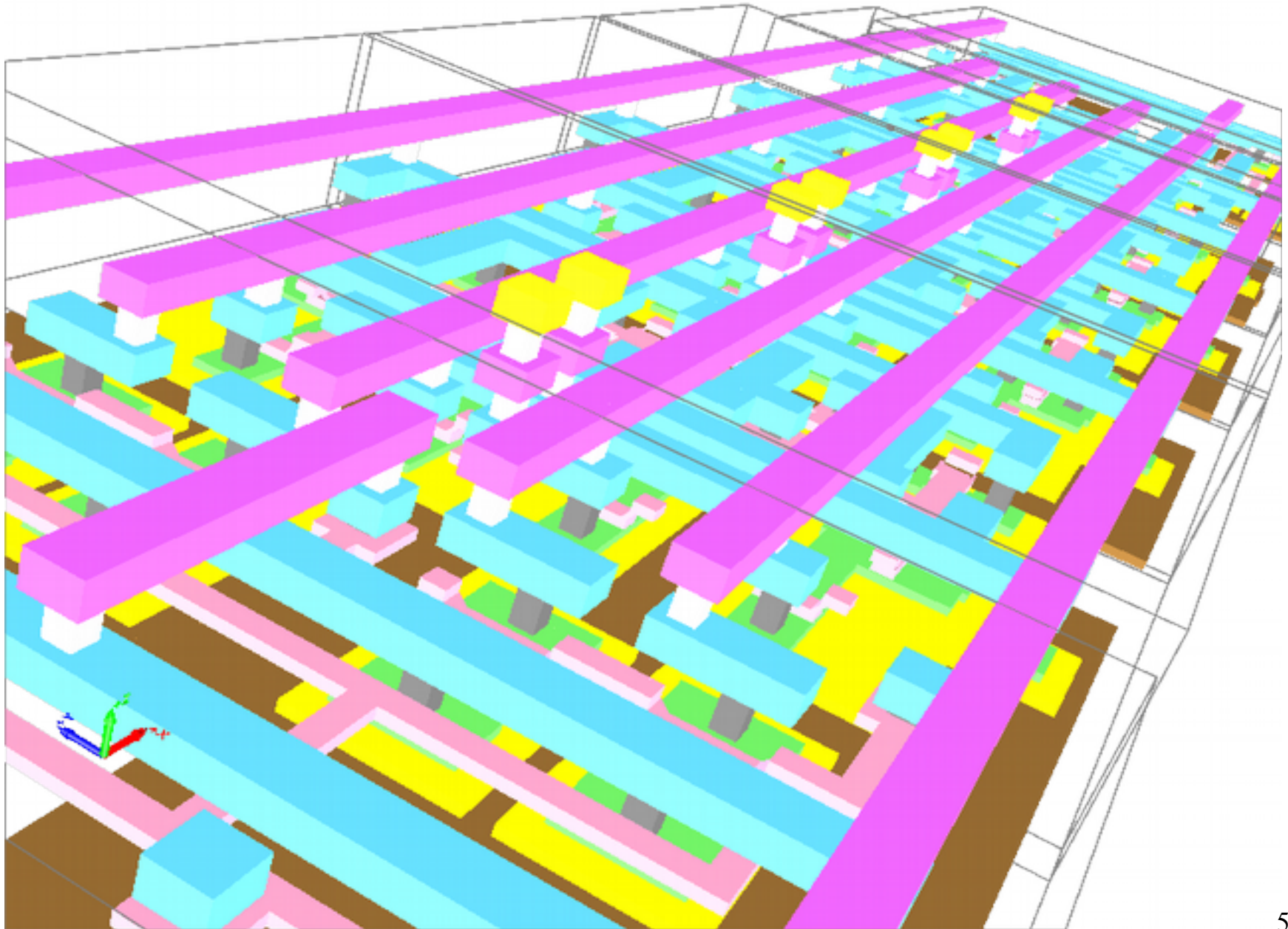

A ring-type oscillator

How many layers do you see ?




A process repeated a few hundred times

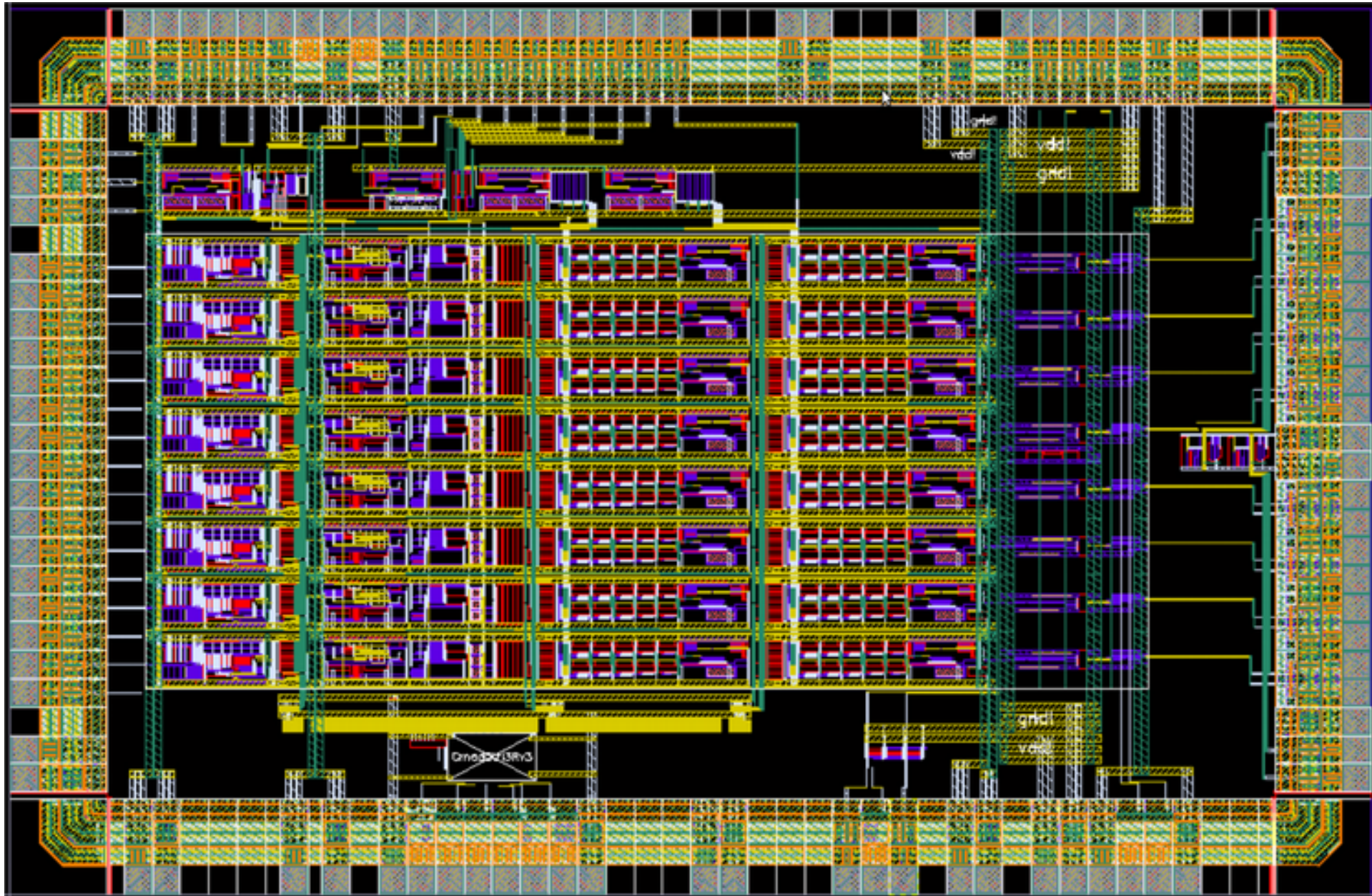

The CAMD front-end ASIC designed for RICH-I detector of COMPASS experiment at CERN.
(350 nm CMOS).

How many layers do you see ?

A process repeated a few hundred times

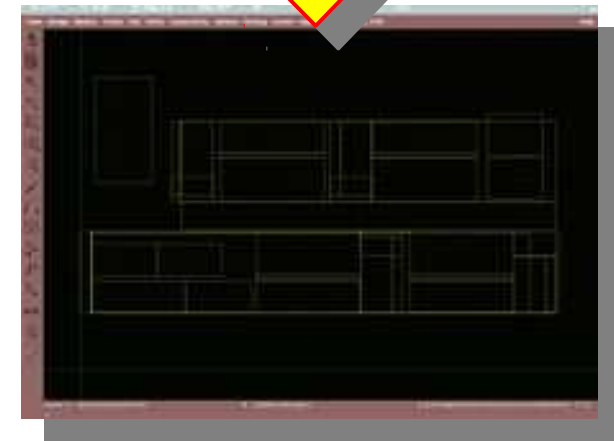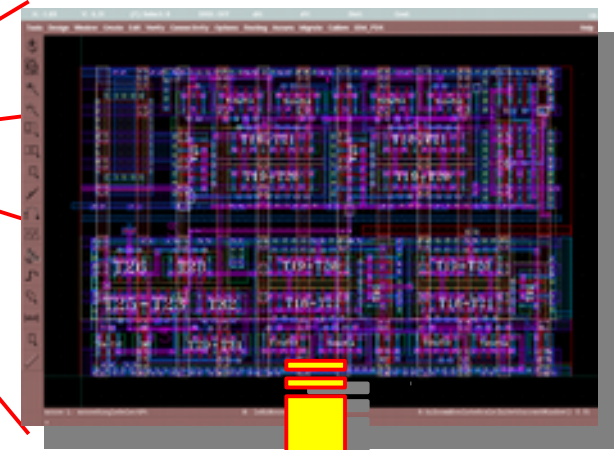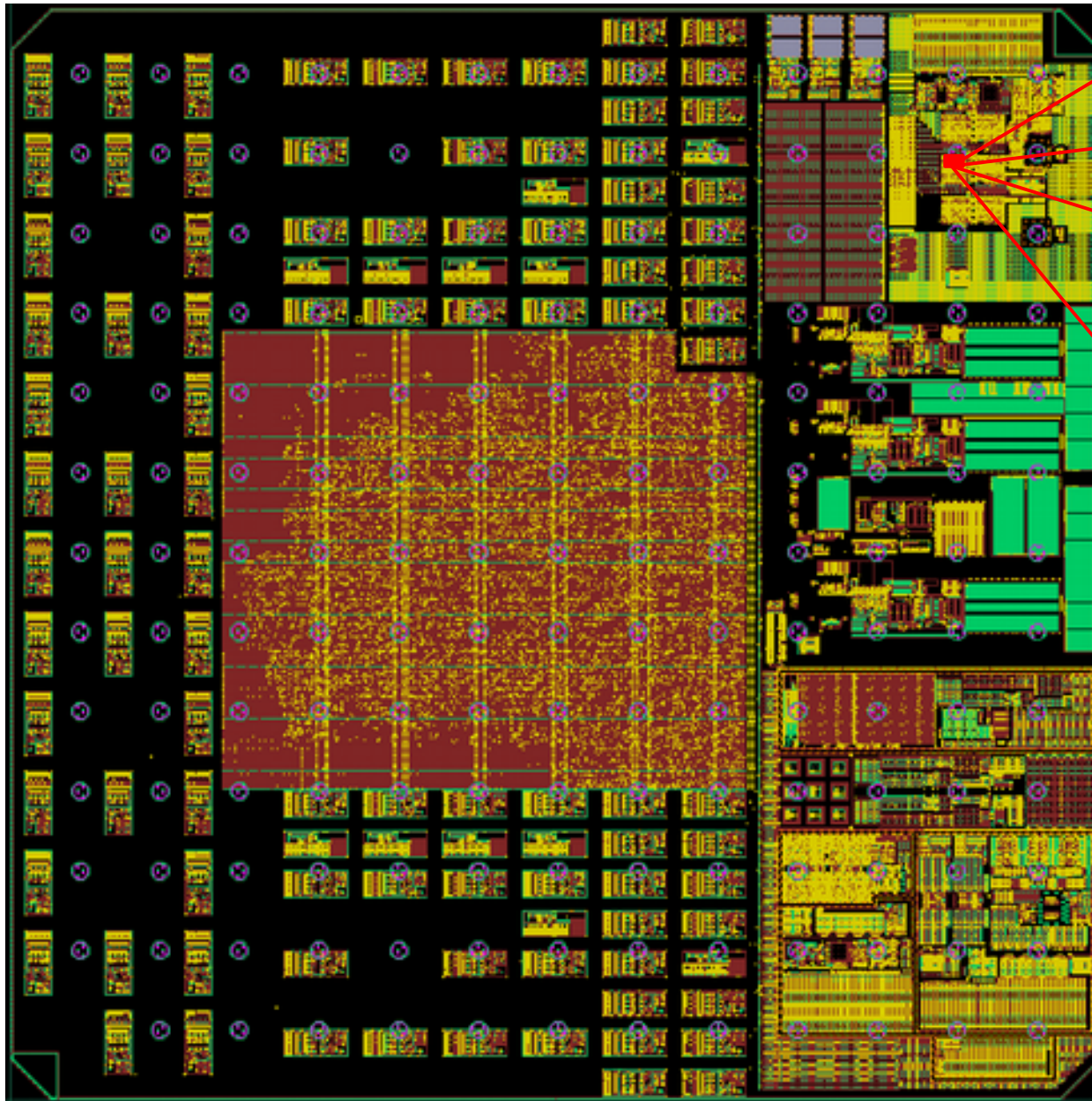

*A sub-set of masks
forming the above block
(Animated GIF image)*

The first prototype of the SER-DES ASIC for the GBT13 chip-set under development for the Super-LHC at CERN. (130 nm CMOS)

VLSI Design in Practice

Daily life of an ASIC designer

- Interface between **process scientist** and **designer**
- Focus on **reliability** and increased **manufacturability**

$$T(s) = \frac{\omega_n^2(\tau s + 1)}{\frac{s^2}{N} + 2\xi s \frac{\omega_n}{N} + \frac{\omega_n^2}{N}}$$

Contact

5.1	Exact contact size	2λ
5.2	Min. poly overlap	1.5λ
5.3	Min. spacing	2λ
5.4	Min. spacing to gate	2λ

6.1	Exact contact size	2λ
6.2	Min. active overlap	1.5λ
6.3	Min. spacing	2λ
6.4	Min. spacing to gate	2λ

Metal1

7.1	Min. width	3λ
7.2.a	Min. spacing	3λ
7.3	Min. overlap of any contact	1λ





Vial

8.1	Exact size	2λ
8.2	Min. spacing	3λ
8.3	Min. overlap by metal1	1λ
8.4	Min. spacing to contact	2λ
8.5	Min. spac. to poly or act. edge	2λ

Metal2

9.1	Min. width	3λ
9.2.a	Min. spacing	4λ
9.3	Min. overlap to vial	1λ

(*) Not Drawn

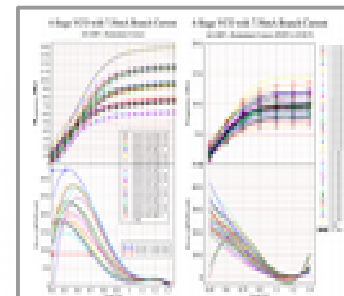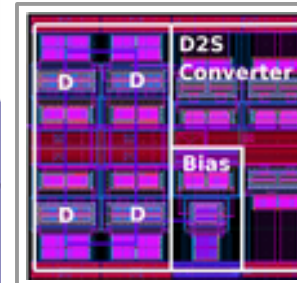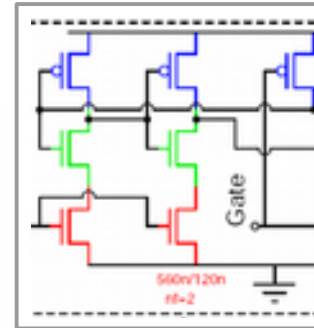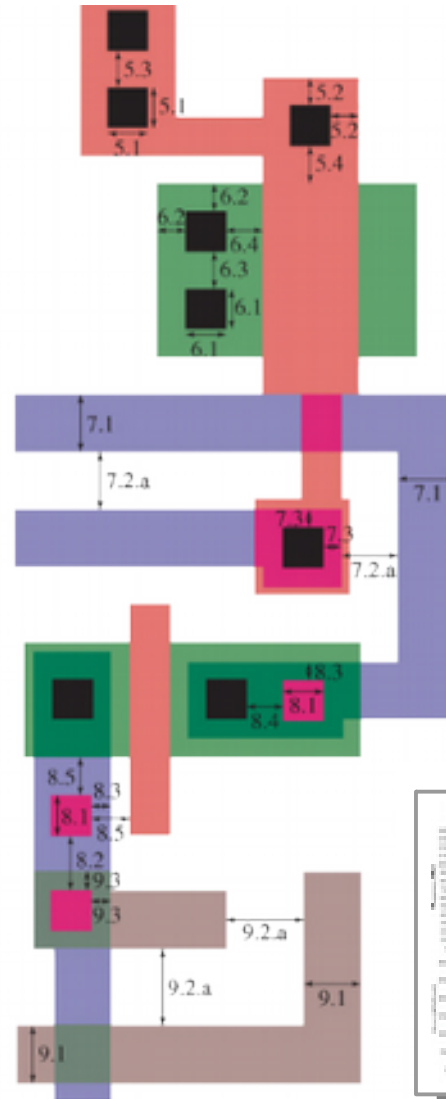

Specifications

Schematic entry

Simulation

Layout

Design Rule Check

Parasitic Extraction




Layout Versus Schematic check

Post-Layout Simulation


Architectural Choice

Quantitative comparison between different approaches

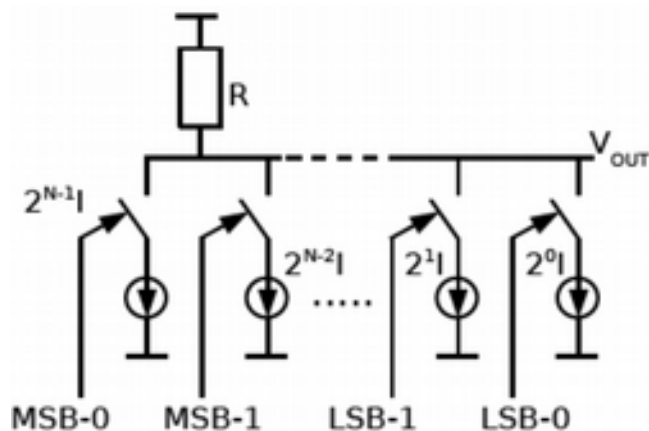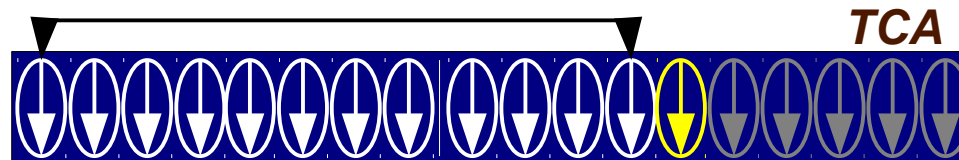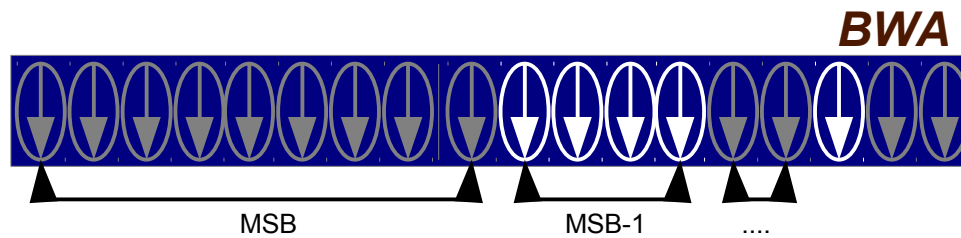
- A **10-Bit** current-mode D/A converter
- Two possible **architectures**; have to **choose one**
- Need for **qualitative comparison**: MC is a **must**



Binary weighted (BWA)

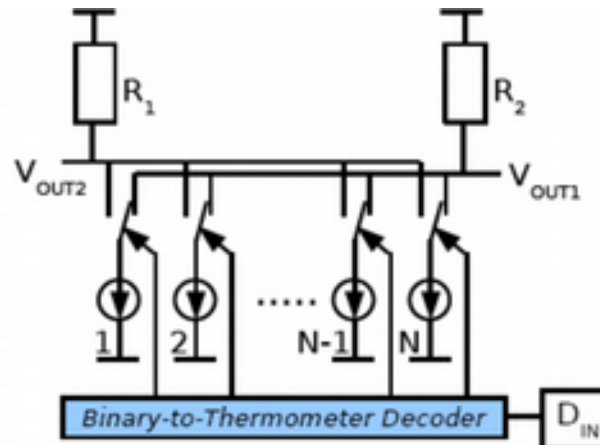






Thermometer coded (TCA)

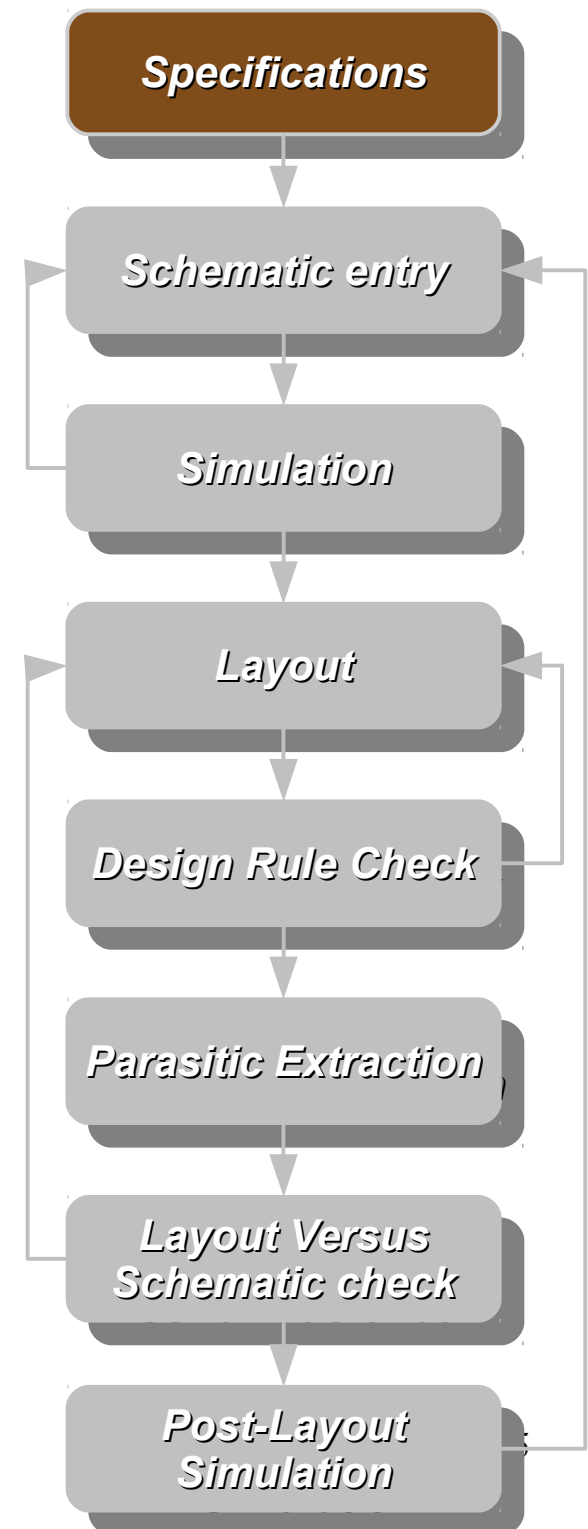

Parametrization

Optimizing the choice according to the application

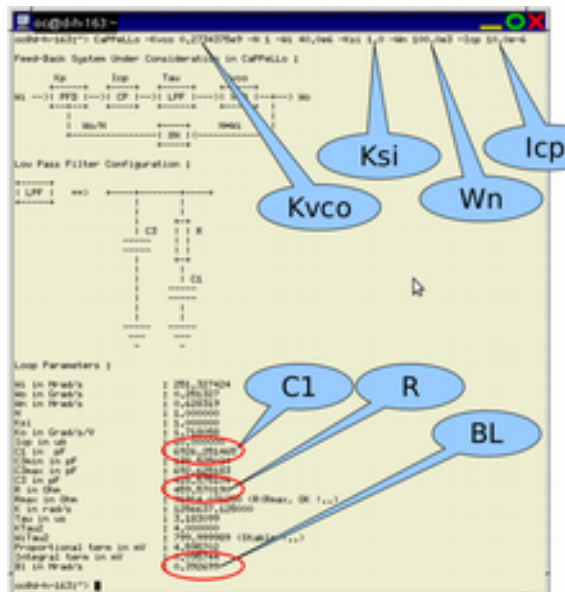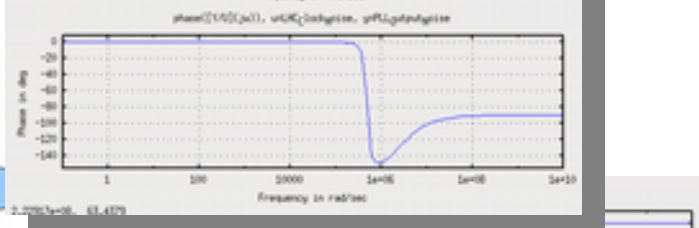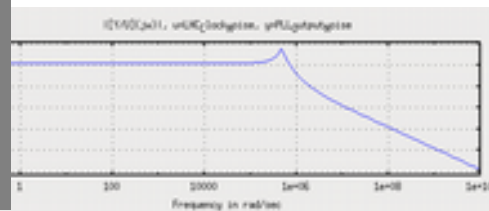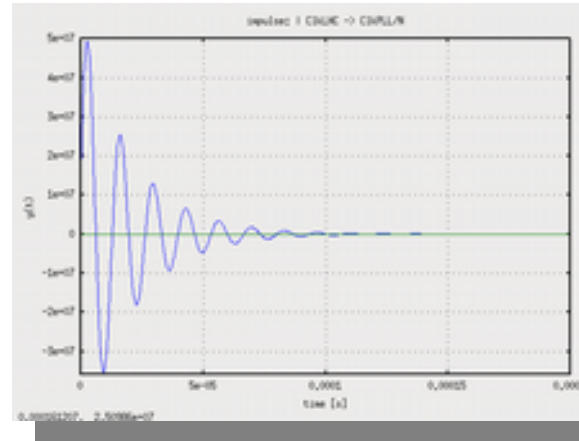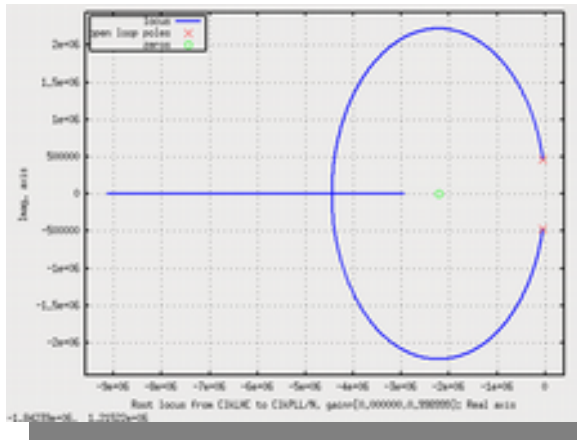- Hand **calculations**
- Corresponding time & frequency domain **behavior**
- Judgment**



Specifications

Schematic entry

Simulation

Layout

Design Rule Check

Parasitic Extraction

Layout Versus Schematic check

Post-Layout Simulation



The screenshot shows the QaPPeLLO software interface, version 13.1. The interface is divided into several sections:

- User inputs:** A section on the left with input fields for Kvco [GHz/V], N (divider), Wi [MHz], Wn [MHz], Ico [μA], and Ksi (damp). It includes a 'Grab Selected OP' button.
- External tools:** A section on the left with dropdown menus for M-interpret (octave), Report Comp. (pdflatex), TlSeAn (Available), Verilog (iverilog), Comp. Switches (-T typ), Editor (nedit), Editor Switches, Plotter (xmgrace), Plotter Switches (-nxy), VCD Viewer (gtkview), Viewer Switches (-L), and HTML Browser (firefox).
- Resulting loop parametrization:** A central section with a table of results including Wz [MHz], C3max [pF], C3min [pF], C3 [pF], C1 [pF], R [Ohm], Rm [KOhm], Bl [MHz], Wo [GHz], K [Hz], Tau [μs], KTau, WiTau, Vpro [mV], Vint [mV], Loop stable, # of OPs, and buttons for Add, Rmv, Simplify, and Save.
- Architecture under treatment:** A block diagram on the right showing a feedback loop with blocks CP, LPF, VCO, PFD, and %N, with inputs Wi and outputs Wo.
- Memory of selected loop operating points:** A list of operating points in the center-right, each represented by a line of parameters like -Kvco 21.000 -N 60 -Wi 40.000 -Wn 0.172 -Icp 1.000 -Ksi 0.
- Log view:** A section on the right showing the log of operations, including the parsing of input parameters and the extraction of parameters.

- ➔ **CaPPeLLO** gets just a few numbers and **all automatically**:
 - ➔ Calculates loop parameters and generates the stability map for comparison
 - ➔ Calculates frequency domain loop response as
 - ➔ Bode and root locus plots, step & impulse responses, noise transfer functions, etc.
 - ➔ Generates the verilog model of the architecture with the selected parameters
 - ➔ Compiles and runs the verilog model, displays the wave forms
 - ➔ Analyzes the jitter data generated during the this simulation
 - ➔ Searches for chaos by means of time series analysis and creates attractors, etc.
 - ➔ Generates a report summarizing all above actions

Schematic-Level Design

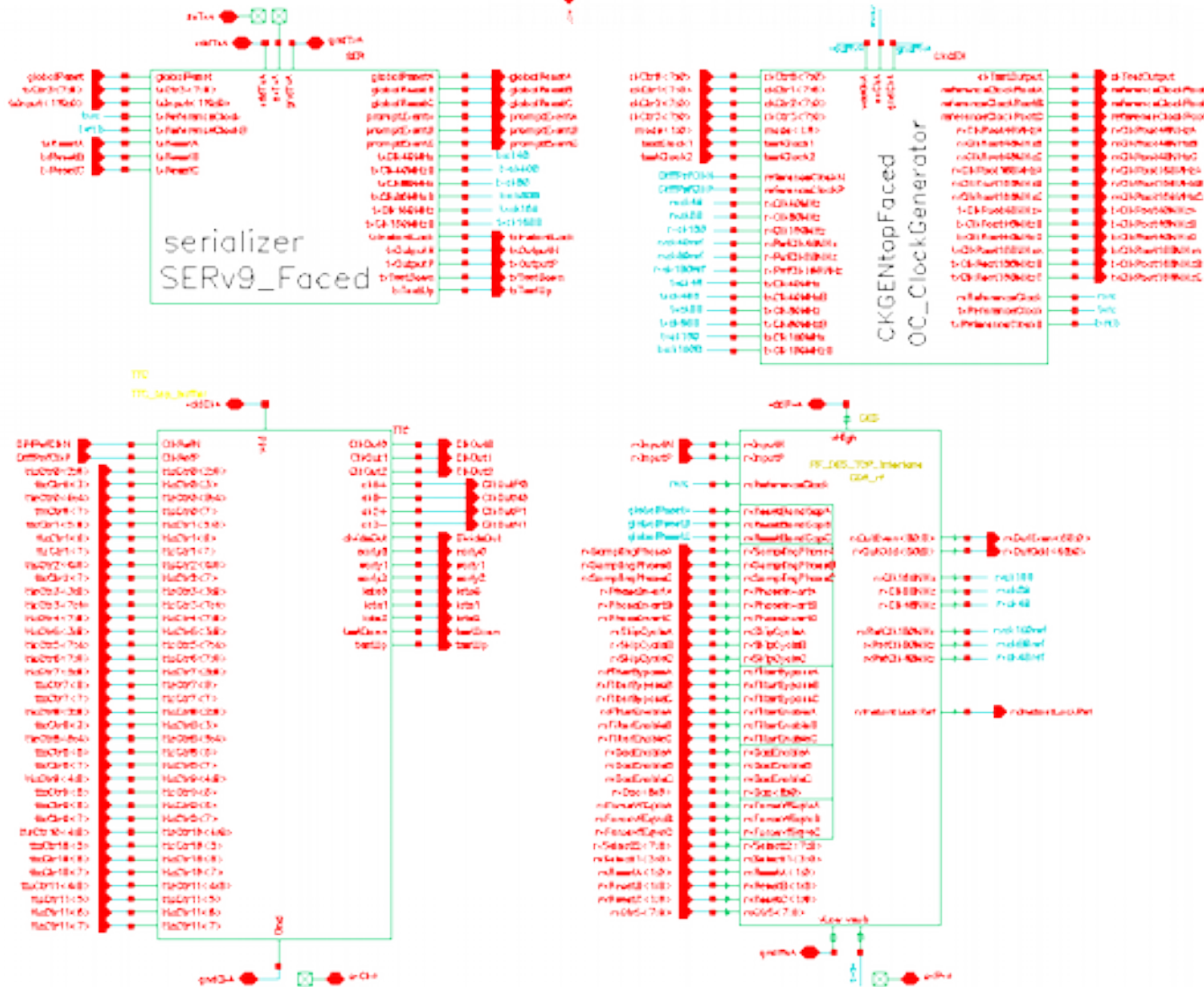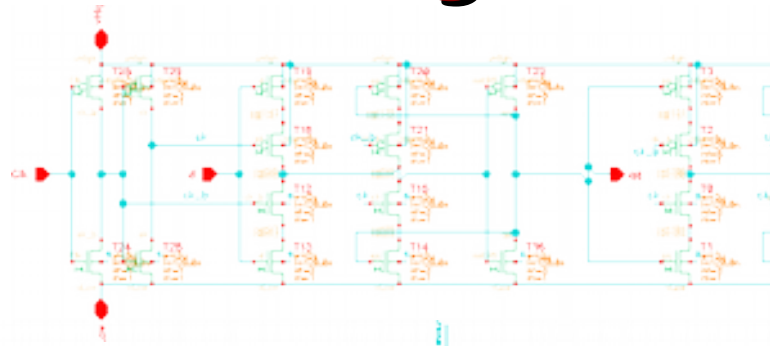- Place **devices**
- Connect **ports**
- Build a **hierarchy**



Specifications

Schematic entry

Simulation

Layout

Design Rule Check

Parasitic Extraction


Layout Versus
Schematic check

Post-Layout
Simulation


Simulation

- ♦ **Model-based** time-step simulations (HDLs, MatLab, Octave, Cadence, etc.)
- ♦ **Transistor-level** SPICE simulations (Spectre, UltraSim, etc.)
- ♦ **Radiation** simulations (Process simulators, Spectre, etc.)

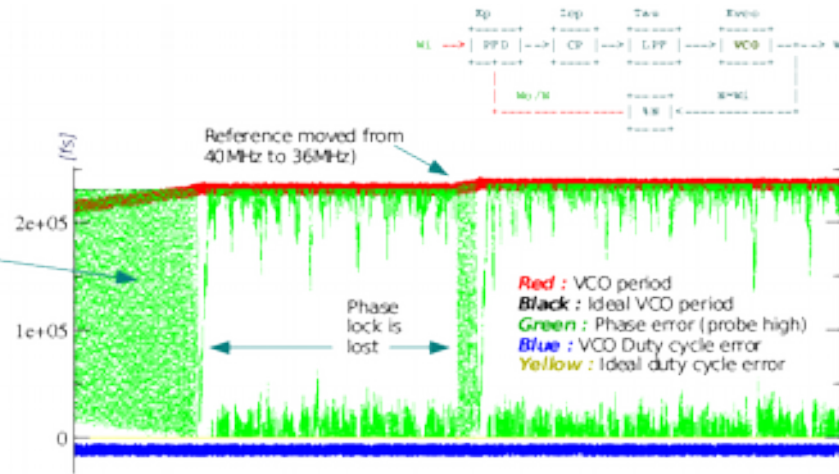- Very noisy VCO + very noisy reference
- Initially not locked
- Reference frequency step of 10% some time after locking
- Low bandwidth CP-PLL filters out the noise at the reference input (i.e. slow loop)
- Effect of damping factor for 0.3 and 1.0



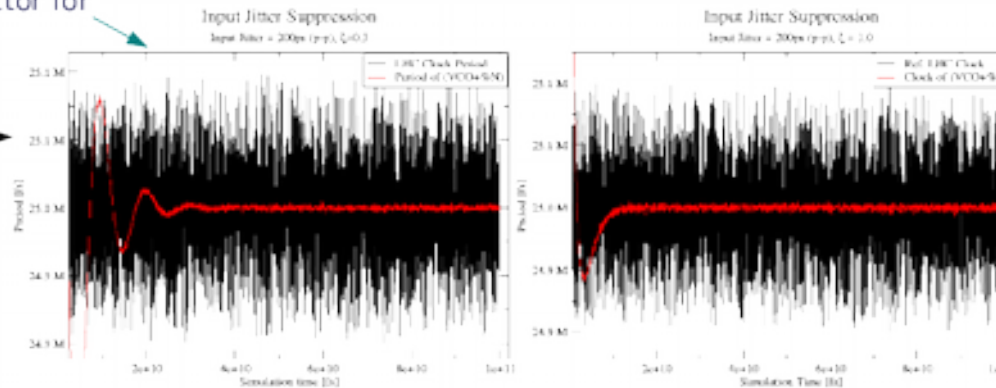- Red : Period of VCO+5%N
- Black : Reference period with 200ps (p-p) jitter



Specifications

Schematic entry

Simulation

Layout



Design Rule Check

Parasitic Extraction

Layout Versus
Schematic checkPost-Layout
Simulation



Layout

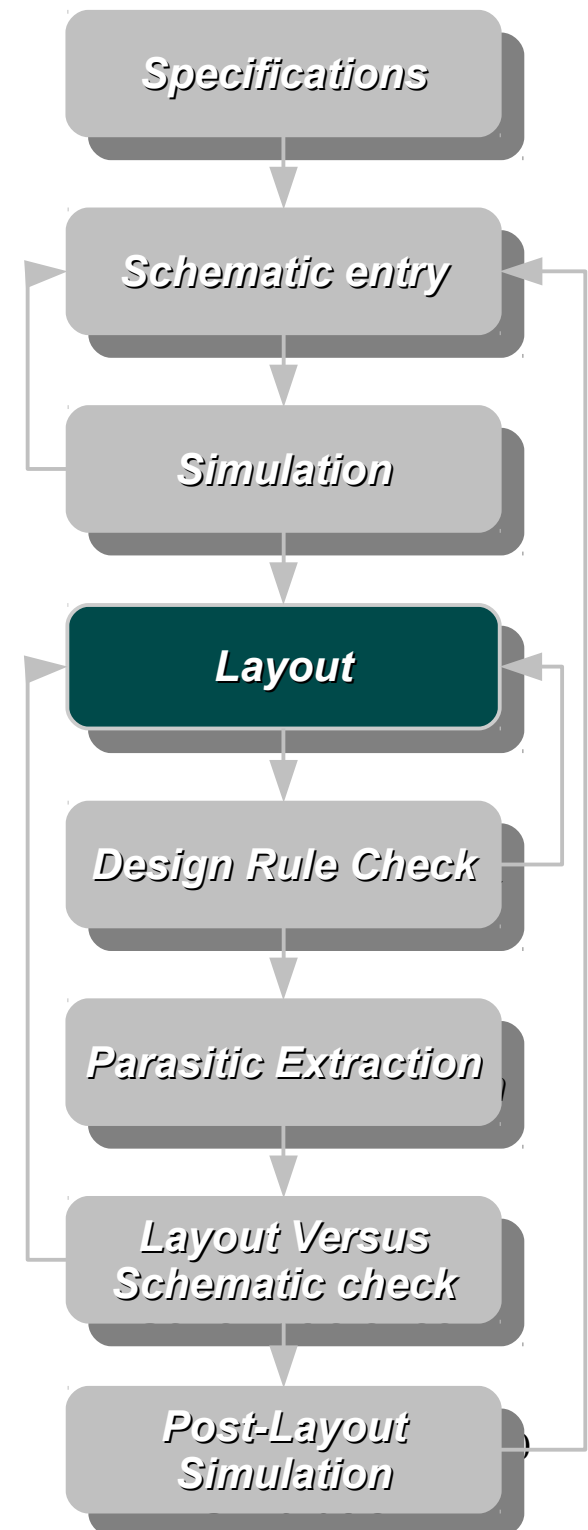
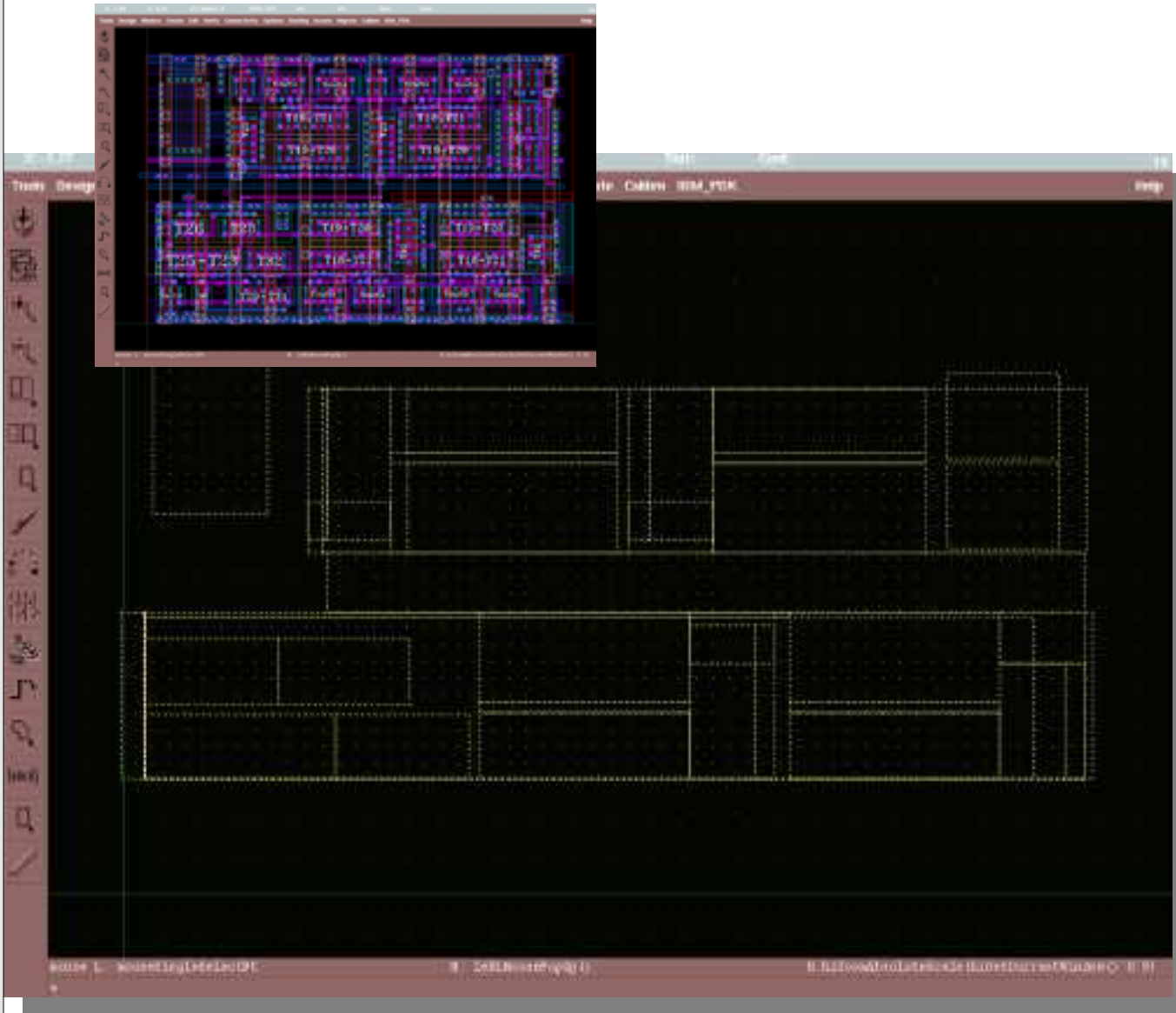
- ♦ Lithographic **masks** are designed
- ♦ Actual representation of a circuit on the **die**



DRC

- **Infinite** different paths of matching what the schematic represent (art)



	Contact		
	5.1	Exact contact size	2 λ
	5.2	Min. poly overlap	1.5 λ
	5.3	Min. spacing	2 λ
	Metal1		
	7.1	Min. width	3 λ
	7.2.a	Min. spacing	3 λ
	7.3	Min. overlap of any contact	1 λ
	Via1		
	8.1	Exact size	2 λ
	8.2	Min. spacing	3 λ
	8.3	Min. overlap by metal1	1 λ
	8.4	Min. spacing to contact	2 λ
	8.5	Min. spac. to poly or act. edge	2 λ
	Metal2		
	9.1	Min. width	3 λ
	9.2.a	Min. spacing	4 λ
	Metal3		
	6.1	Exact contact size	2 λ
	6.2	Min. active overlap	1.5 λ
	6.3	Min. spacing	2 λ
	6.4	Min. spacing to gate	2 λ
(*) Not Drawn			

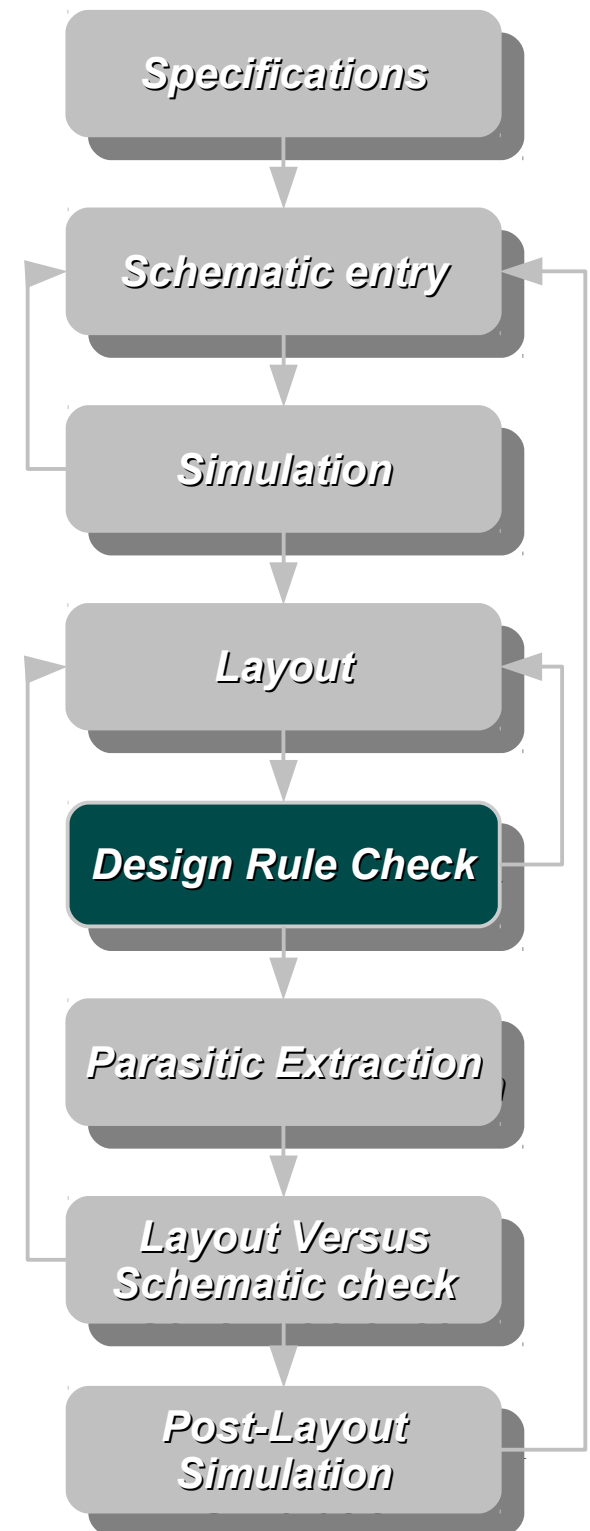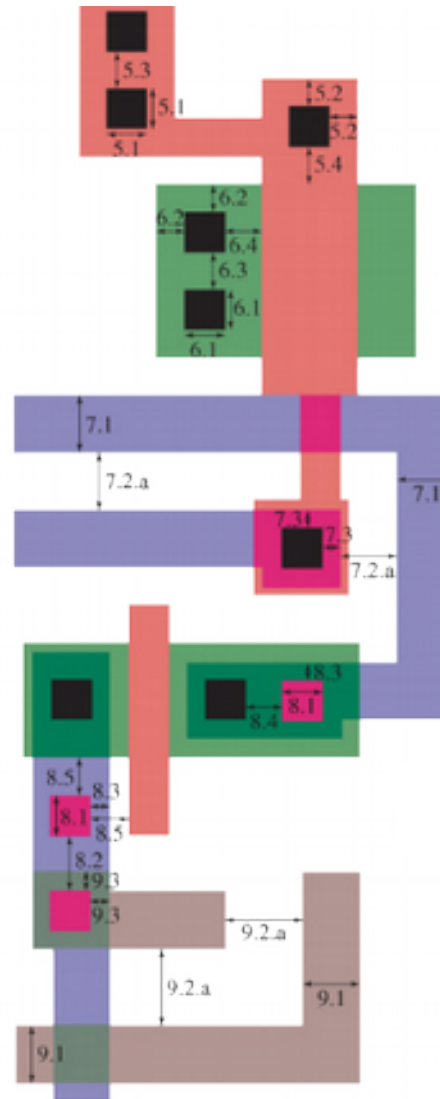

Parasitic Extraction

For a better physical representation of what is in the circuit


- Perform two **simple connections**:
 - Connect the pin **A** to pin **B** with **metal-1**
 - Connect the pin **C** to pin **D** with **metal-2**
- Designer **did not draw** any device but the **effective circuit** has at least the followings:
 - 4 capacitors
 - 2 resistors
 - 1 inductor
- Things which are not taken into account in schematic are the parasitic devices that **can not be avoided** but minimized/maximized
 - e.g. minimize input capacitance of a FE or wire capacitances between building blocks
 - e.g. maximize narrow-band PLL filter capacitance or de-coupling capacitors of any ASIC

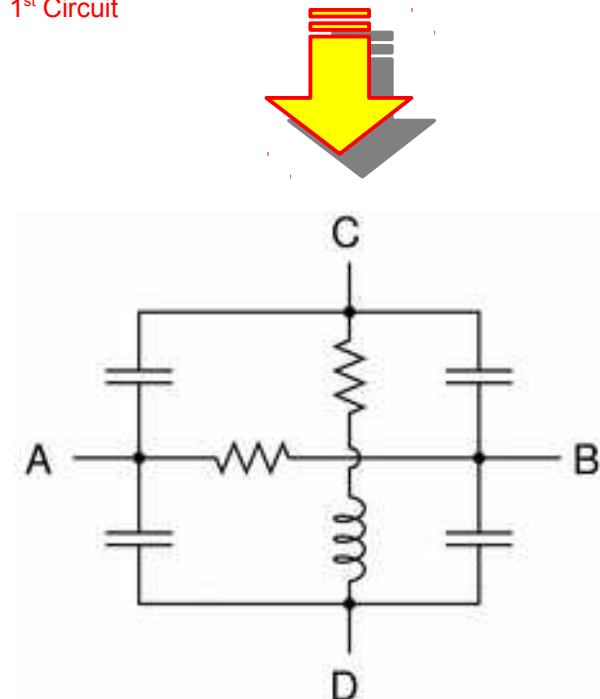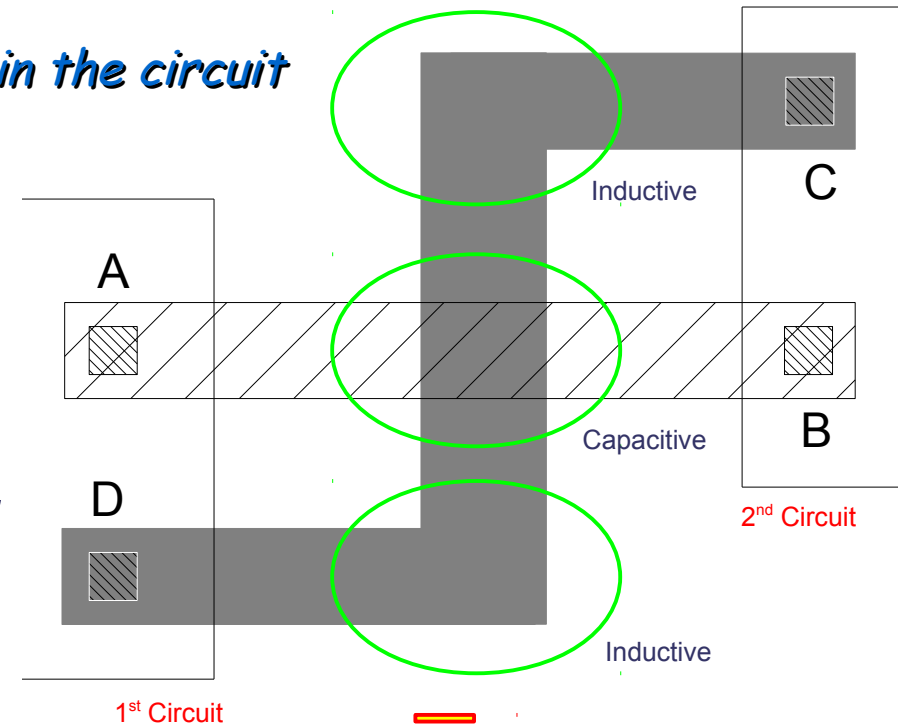

Test Boards

and tester/configurator application

Control bits

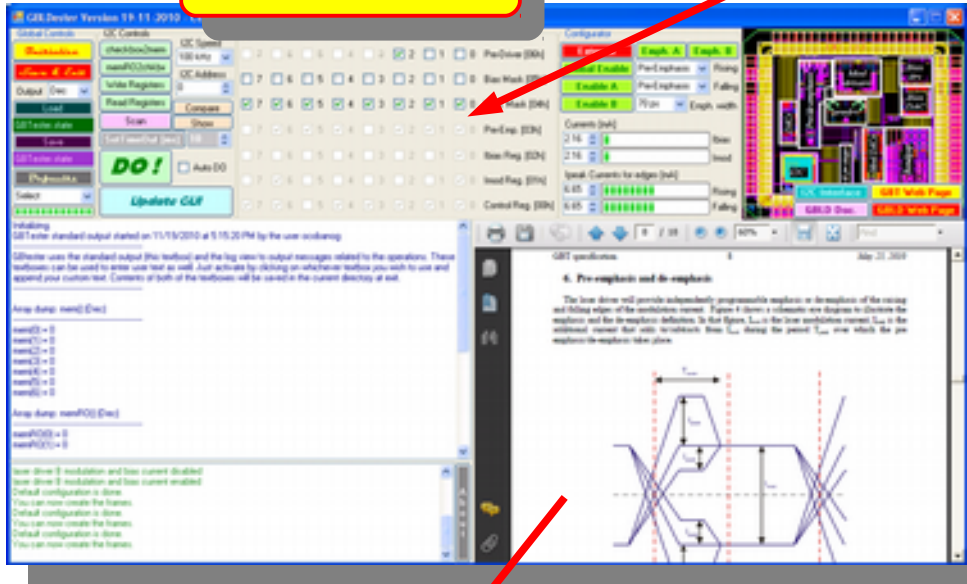


On-line documentation

USB → I2C adapter


I2C & JTAG ports

FPGA (Cyclon-III)

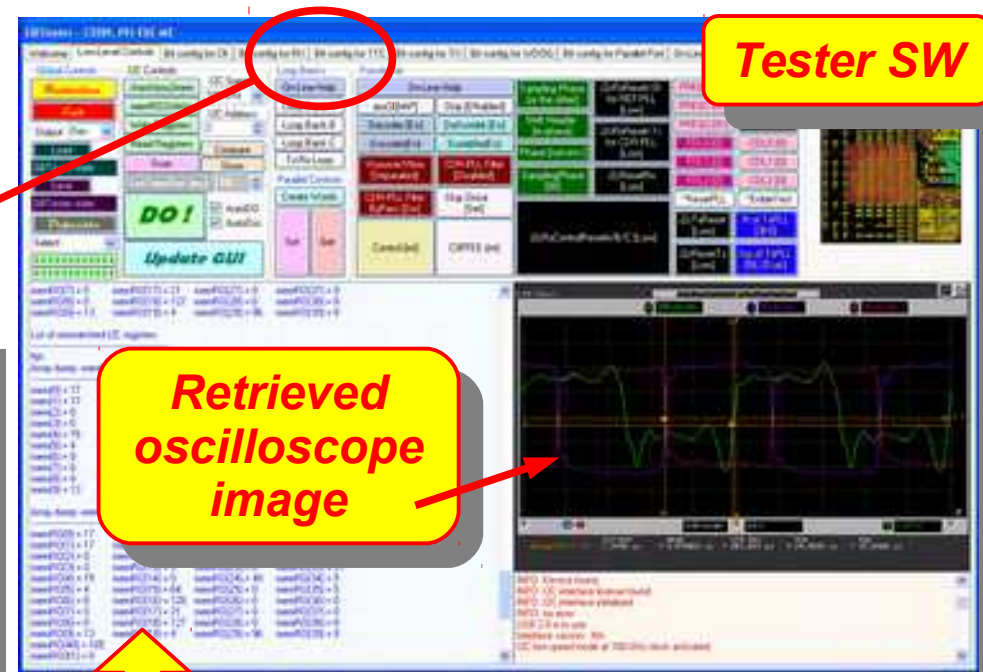Where the DUT resides
(DUT: Device Under Test)



Retrieved
oscilloscope
image

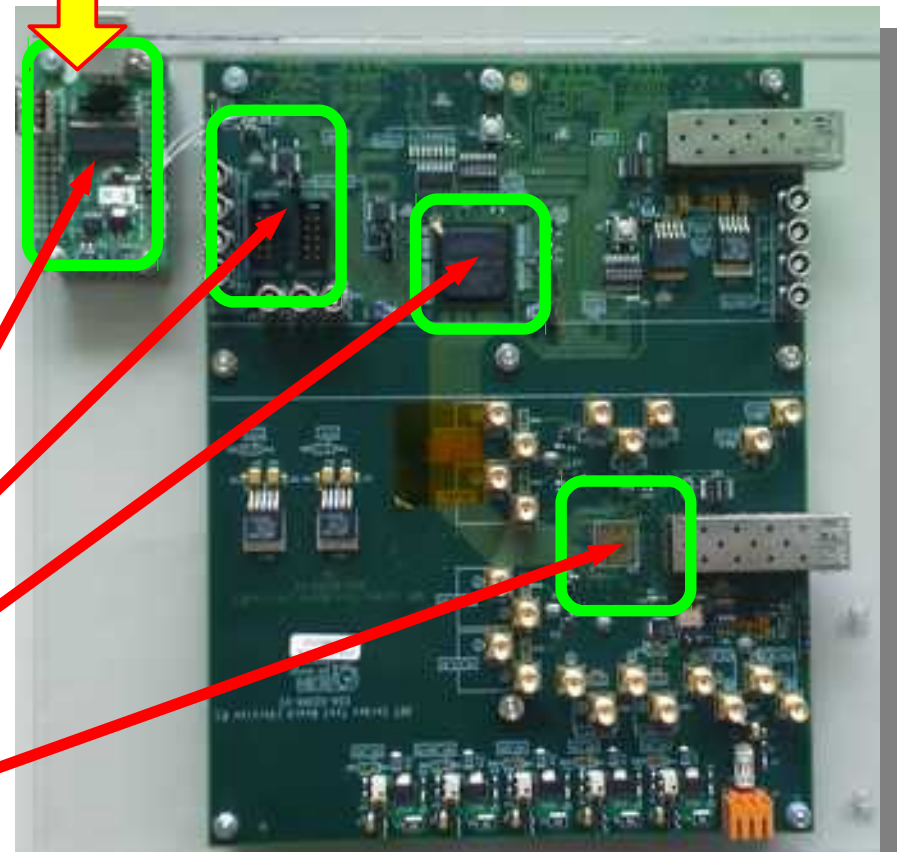

Tester SW

Introduction to the Design of Full-Custom Front-End & Data Transmission ASICs*

Table of Contents

■ The Big (but Brief) Picture

- Briefly **front-end** - FE
- Briefly **read-out** - RO
- Briefly **serializer** - SER
- Briefly **phase-lock loop** - PLL

■ Feed-Back Concept

- A **qualitative** introduction
- **Natural frequency** concept - ω_n
- Real-world examples:
 - **Binary** read-out
 - **Time-over threshold**
- Adjusting/optimizing loop behavior
 - **Damping ratio**

■ Reminder on Detectors

- Photodetectors **vs** photon counters
- **Position-sensitive** detectors
 - Resistive charge division
 - Discrete array of elements
- **Time-resolved** detection

■ Detector Front-End ASICs


- **Pre-Amp**: basic idea – V_{OUT} / V_{IN}
- **Transconductance** of a transistor - g_m
- Evolving a **single-stage amplifier** into a real-world application

■ Processing Technology

- **Transistor** switch – A masterpiece
 - **Lithography**
 - Formation of an **nMOS** transistor
- VLSI design flow
 - Parasitic **extraction**
- Real-world ASIC examples

■ Radiation Tolerance Issues

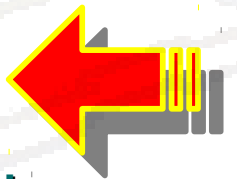
- Definitions:
 - **Single event upset, analog**
 - **single event transient, latch-up**
- **Simulating** radiation effects on analog circuits



Radiation Issues

Definitions and failure mechanism

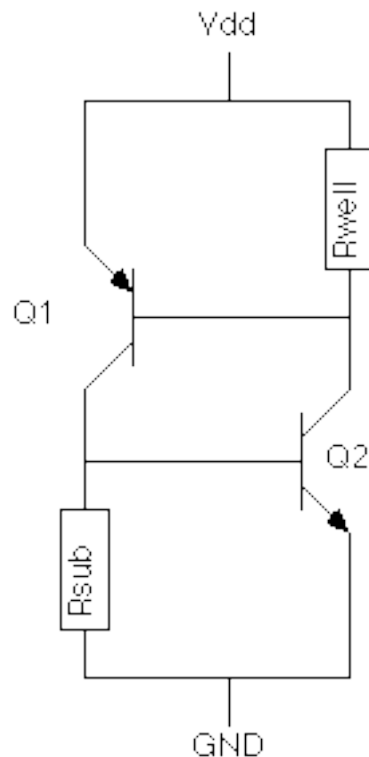
- **Single Event Transient (SET)**
 - A transient perturbation on an analog signal due to charge released by an ionizing radiation.
- **Single Event Upset (SEU)**
 - State change of a digital circuit due to charge released by an ionizing radiation.




*Equivalent parasitic
BiPolar circuit*

■ Latch-Up

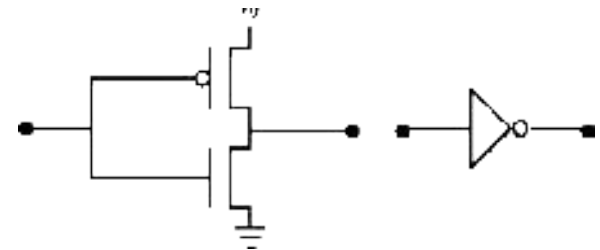- Creation of a low-resistance path between Vdd and Gnd due to a positive feedback loop formed by parasitic devices.



CMOS inverter and its symbol

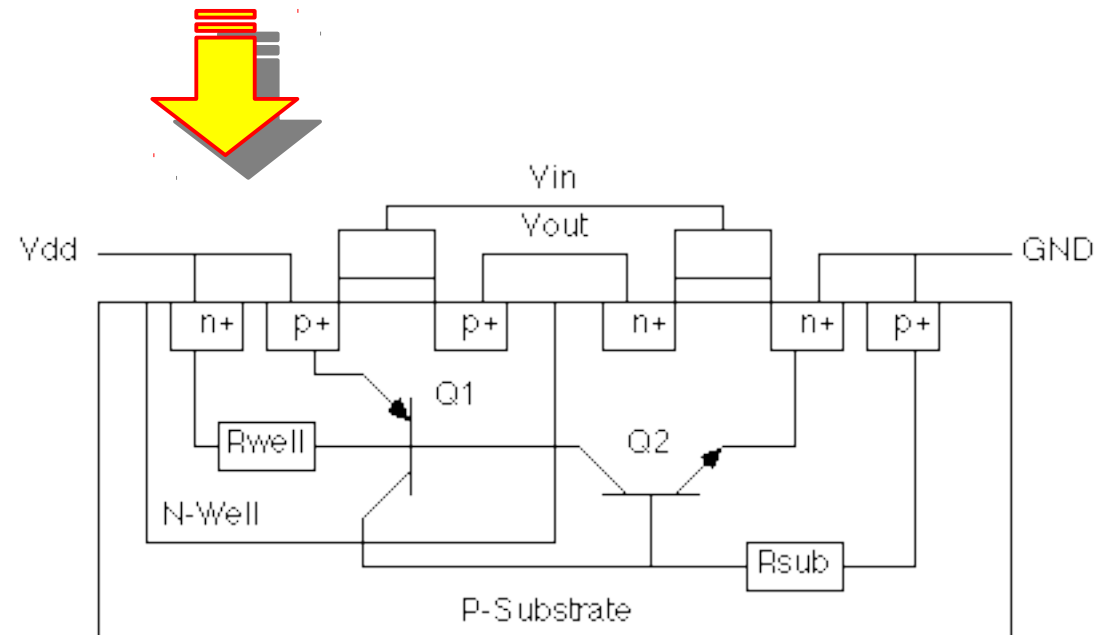

vertical PNP

lateral NPN


Wafer cross-section of the inverter

Modeling Radiation Effects

Taking radiation into account in simulations

- Radiation = current pulse
 - E.g.: 0.3 **pC** in 130 nm CMOS
- Plot: Effect vs Q
 - Define/check specifications
 - Repeat the cycle

Circuit

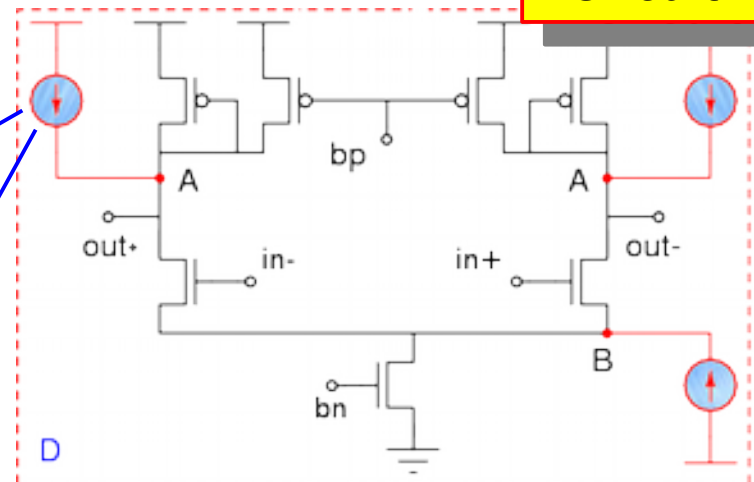


Q

Injected Current [mA]




SETs

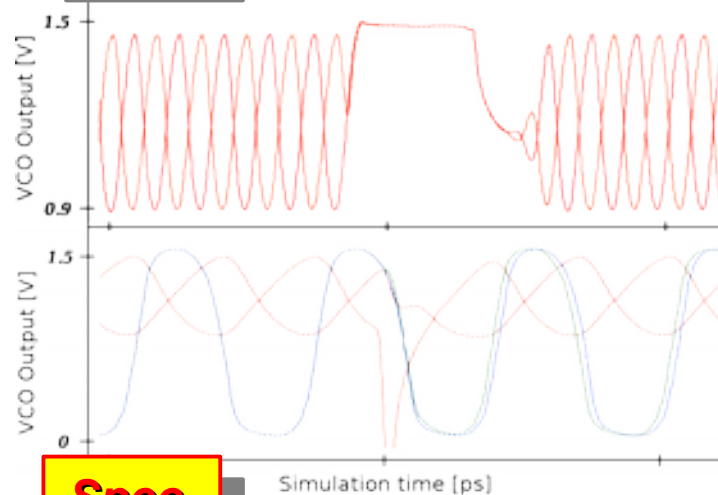


You start here !!

System

VCO

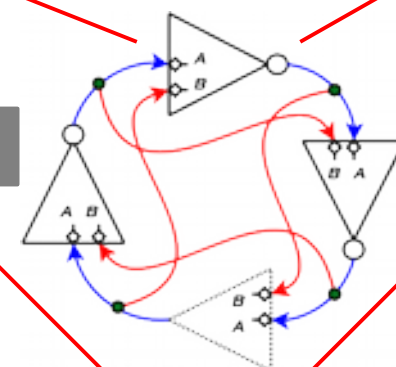



Spec.

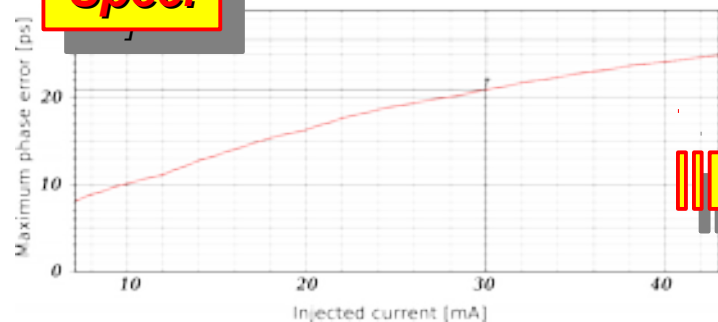

Rad-Hard Design Tricks

Adding robustness to circuits

- Use **higher current levels** and/or larger devices
 - ➔ The current/voltage excursions ionizing particles generate stay insignificant
 - ➔ Prise to pay: increased circuit footprint and power dissipation, slower operation, etc.
- Use **triple-well** and/or **guard-ring** structures frequently
 - ➔ To ground any noise before it reaches to sensitive circuitry
- Use **Modular Redundancy** (nMR)
 - ➔ Replicate circuitry and vote at the output, Triple Modular Redundancy (TMR) is commonly used
 - ➔ The probability for an ionizing particle to affect all the three blocks at the same time is very low, therefore this technique is commonly used to harden designs against SEU
- Use **dummy states** to protect Finite State Machines (**FSM**) against SEUs
 - ➔ If a state change occurs due to an ionizing particle passage, the FSM can return to a valid state without impairing
 - ➔ Prise to pay: more complex FSM design, increased power dissipation and circuit footprint
- Place the ASICs within magnet **shadows** (where applicable)
 - ➔ To decrease radiation tolerance requirements

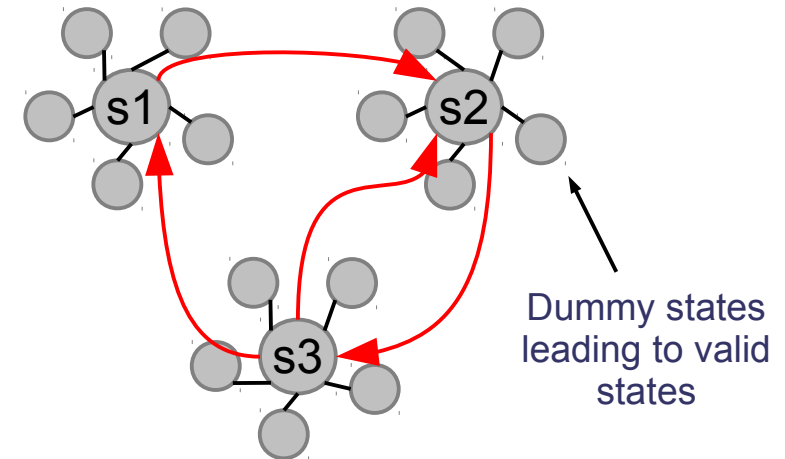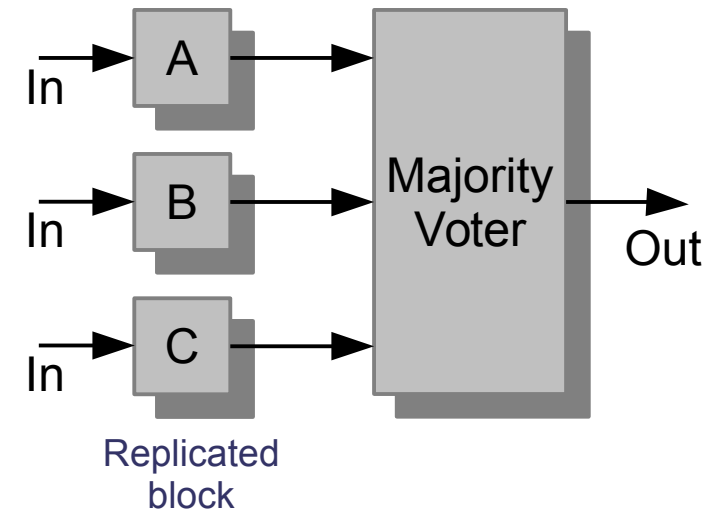

Introduction to the Design of Full-Custom Front-End & Data Transmission ASICs*

Table of Contents

- **The Big (but Brief) Picture**
 - Briefly **front-end** - FE
 - Briefly **read-out** - RO
 - Briefly **serializer** - SER
 - Briefly **phase-lock loop** - PLL
- **Feed-Back Concept**
 - A **qualitative** introduction
 - **Natural frequency** concept - ω_n
 - Real-world examples:
 - **Binary** read-out
 - **Time-over threshold**
 - Adjusting/optimizing loop behavior
 - **Damping ratio**
- **Reminder on Detectors**
 - Photodetectors **vs** photon counters
 - **Position-sensitive** detectors
 - **Resistive charge division**
 - **Discrete array of elements**
 - **Time-resolved** detection
- **Detector Front-End ASICs**
 - **Pre-Amp**: basic idea – V_{OUT} / V_{IN}
 - **Transconductance** of a transistor - g_m
 - Evolving a **single-stage amplifier** into a real-world application
- **Processing Technology**
 - **Transistor** switch – A masterpiece
 - **Lithography**
 - Formation of an **nMOS** transistor
 - VLSI design flow
 - **Parasitic extraction**
 - Real-world ASIC examples
- **Radiation Tolerance Issues**
 - Definitions:
 - **Single event upset, analog single event transient, latch-up**
 - **Simulating** radiation effects on analog circuits