

Status on the Development of FE & Readout Electronics for Large Silicon Trackers

**Jean- François Genat
LPNHE, Universités Paris 6 et 7/ CNRS- IN2P3**

**Jacques David, Marc Dhellot, Jean François Genat, Frédéric Kapusta, Hervé
Lebbolo, Thanh Hung Pham, François Rossel, Aurore Savoy- Navarro
(LPNHE- Paris)**

Erwin Deumens, Paul Malisse (EUROPRATI CE, I MEC Leuven)

Denis Fougeron, Richard Hermel (LAPP/CNRS- IN2P3, Annecy)

Forthcoming collaboration with CERN (Alessandro Marchioro et al, EUDET)

LCWS06, March 9-13th, Bangalore, India

Jean- Francois Genat, LCWS06, March 9- 13th, Bangalore, India

Outline

- Silicon strips detector context
- On-detector Electronics
- 180nm CMOS readout chip
- Test results
- Design in 130 nm
- Next ...

Silicon strips detector context

Silicon strips detector numbers

- 4-10 10^6 Silicon strips 10 - 60 cm long
- Readout Pitch 50-100 μm DC or AC coupled
- Occupancy defined as % channels hit per BC:
 - Outer barrel and end caps layers: < 1 %
 - Inner barrel and end caps layers: < 5 %
- ILC timing: 1 ms: bunch: 150-300ns / BC
200ms in between

Detector data

- **Pulse height:** Cluster centroid to improve position resolution to $O(\mu\text{m})$

Detector pulse sampling 5-10 samples 8-10 bit A/D (Wilkinson)
stored in an analog buffer

- **Time:** Two scales:
 - Coarse 150-300ns BCO tagging
 - Fine nanosecond timing for coordinate along the strip and fine BCO tagging for some regions

Not to replace another detector layer or double sided detector,
but give an estimation to a few cm


On-detector Electronics

Jean- Francois Genat, LCWS06, March 9- 13th, Bangalore, India

On-detector FE chip

- **Pulse sampling:** 5-10 samples over 2 shaping times
- **Buffering:** 8-deep 2D analog buffer
(8*5-10 samples cells) per channel
- **Analog-Digital conversion** Wilkinson optimum (SVX architecture)
- **Sparsification/calibration :** Integrated on detector FE chip
- **Digital processing:** Amplitude and time estimation + charge cluster algorithm
- **Power: 1/200 ILC duty cycle:** FE Power cycling

Front-end architecture

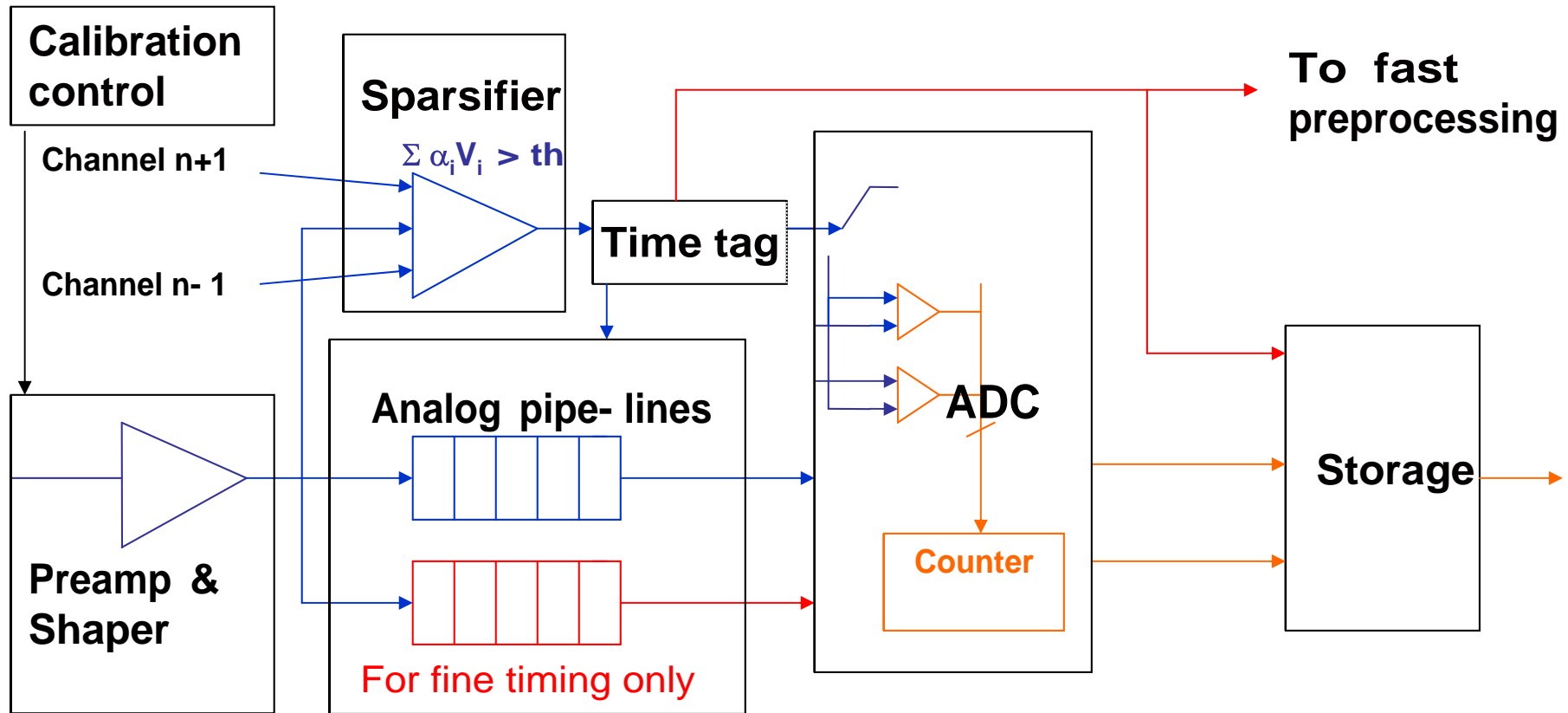

Charge 1- 40 MIP, S/N~ 15- 20, Time resolutions: BC tagging, fine: ~ 2ns

Present technologies - Deep Sub-Micron CMOS
 UMC 0.18 μm , 0.13 μm

Time-stamping on all layers
 fine time resolution
 on some layers

Jean- Francois Genat, LCWS06, March 9- 13th, Bangalore, India

Charge measurements Expected

- **Preamp + Shaper**
Gain: 20mV/ MIP over 1-30 MIP
Noise: CMOS 180 nm: $280e^- + 10.5e^-/pF @ 3 \mu s$
- **Analog buffer**
8-deep (cells of 5-10 100 fF caps)
- **Sparsifier**
Threshold an analog sum of 3 adjacent channels after pulse shaping
- **ADC**
10-12 bits
Clocked at 96 MHz
- **Signal-Noise ratio**
The larger, the best ! 15-20 ?

Time measurements Expected

- **Time stamping**

Order of 30 to 50 ns

Time-stamp the sparsifier output at $4 * \text{BCO clock}$ (12 MHz)

- **Fine time measurement**

Order of 1 to 3 ns


$32 * \text{BCO}$ on chip interpolated clock sampling (PLL @96 MHz)

Use digital processing over 5-10 digitized samples

Expected fine time resolution

Simulated (JFG) time resolution using a model of the whole electronics readout chain from preamplifier to the analog sampler (ideal A/D) using least square fit algorithm (William Cleland)

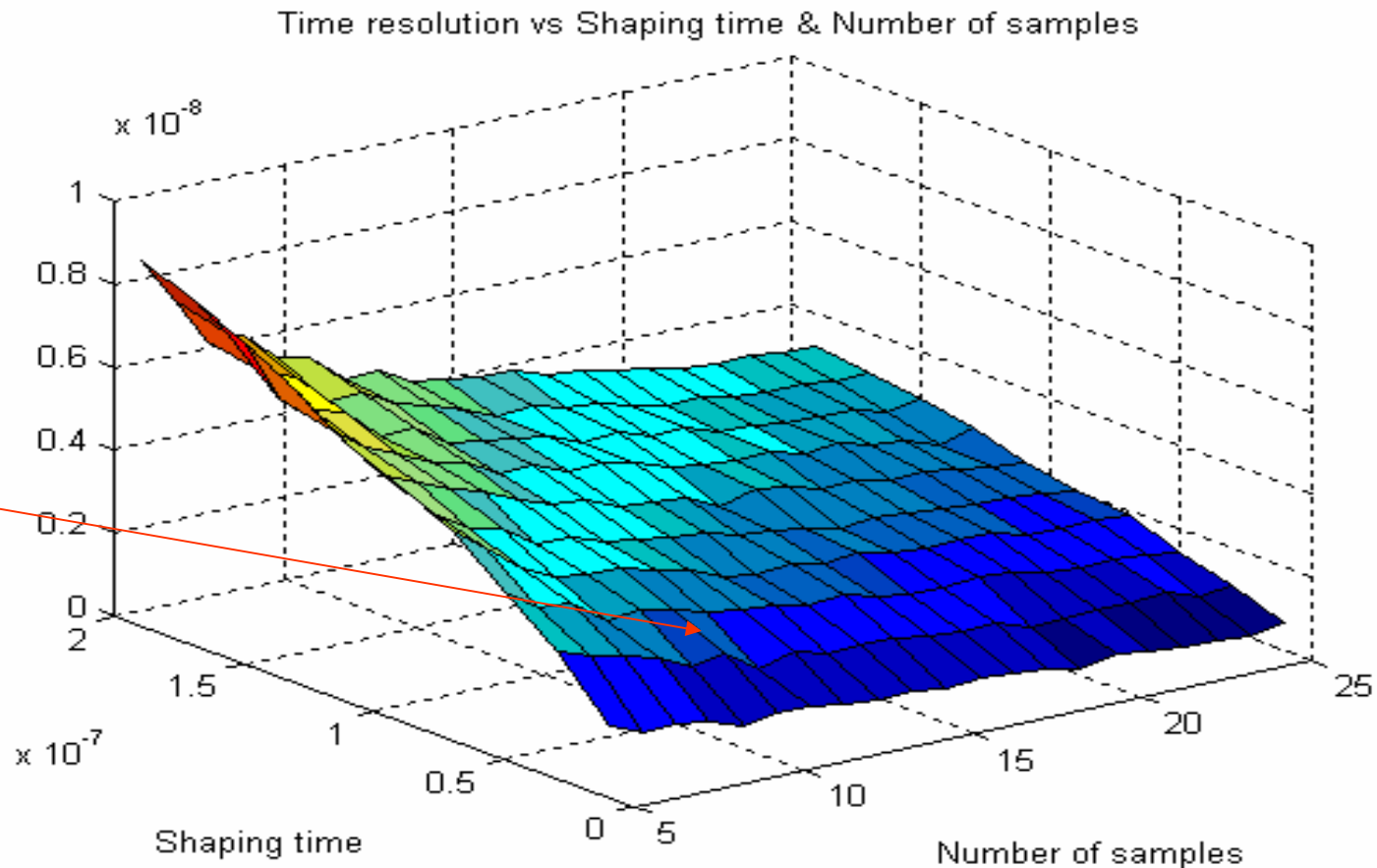- **S/N =25**
 - **8 samples**
 - **50 ns shaping**
- **1.8 ns time resolution**
(will still improve with actual time distribution in the detector)



SiGe technology

Jean- Francois Genat, LCWS06, March 9- 13th, Bangalore, India

Overall Noise Contributions


Source	Value	Noise 180nm CMOS
Input stage (measured)	$g_m=0.7\text{mA/V}$	615 e- (measured)
Detector leak	10 nA	588 e- (from literature)
Biasing resistor	10 M Ω	423 e- (thermal noise)
Total		950 e-

For seen over all ENC contributions at 30 pF detector capacitance and 3 μs shaping time:

- CMOS 180 nm: S/N ~ 20
- CMOS 130 under investigations



CMOS 180nm Chip

Front-end test chip in CMOS 180nm

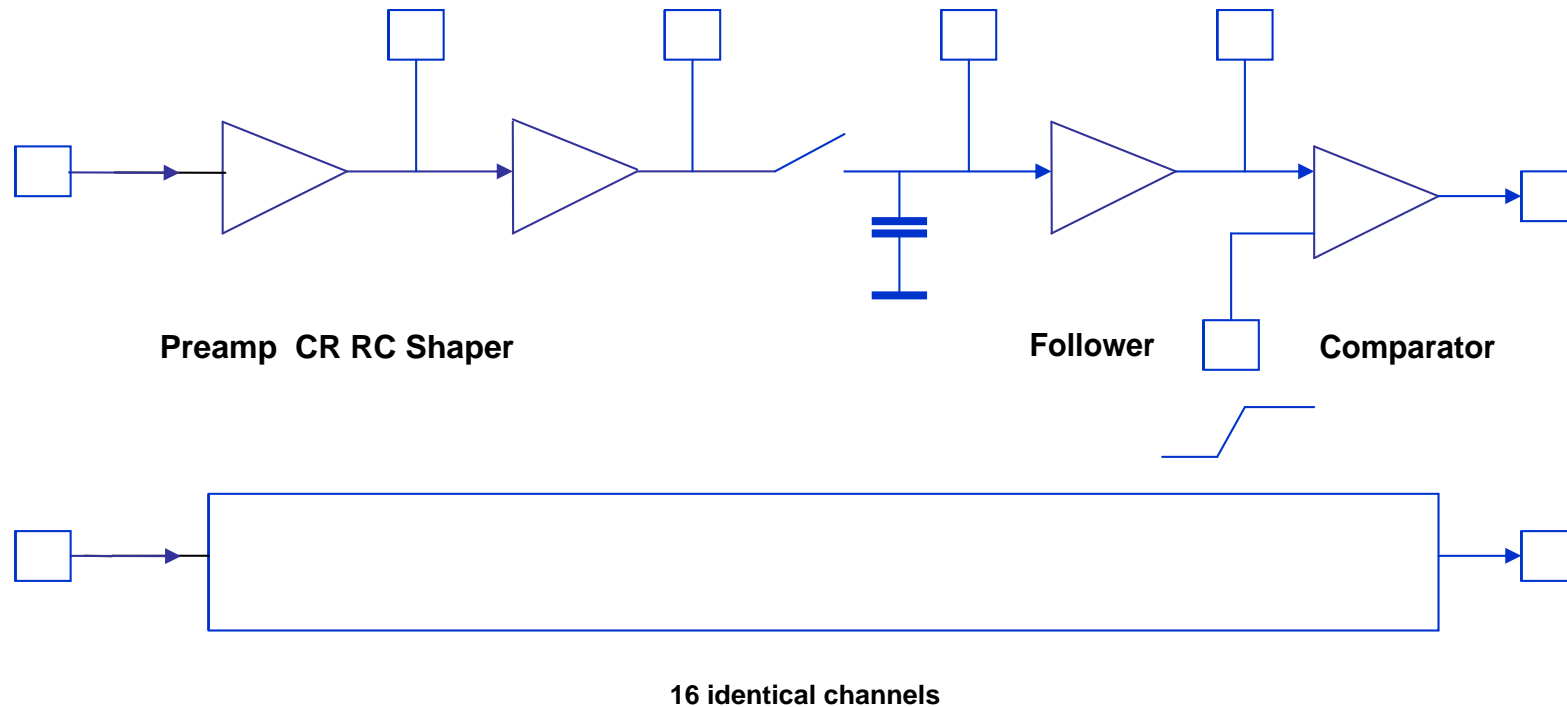

- Low noise amplification + pulse shaping
- Sample & hold
- Comparator

Silicon

  


← 3mm →

16 + 1 channel UMC 0.18 um chip (layout and picture)

Jean- Francois Genat, LCWS06, March 9- 13th, Bangalore, India

Tests Results

Protection can

 

Chip wired-bonded on board

Jean- Francois Genat, LCWS06, March 9- 13th, Bangalore, India

Preamp tests results


12 chips tested.

One failure: On chip # 8, comparator does not work.

Preamp:

- Gain: 8 mV/MIP OK
 - Linearity: +/-1.5% +/-0.5% expected
- Transistor used as a resistor
non linear with voltage
- Dynamic range: 50 MIP 90 expected, but within specs
 - Noise @ 70 μ W power, 3 μ s-20 μ s rise-fall times:
498 + 16.5 e-/pF 490 + 16.5 e-/pF expected
OK

Shaper Noise (wired-bonded on board)

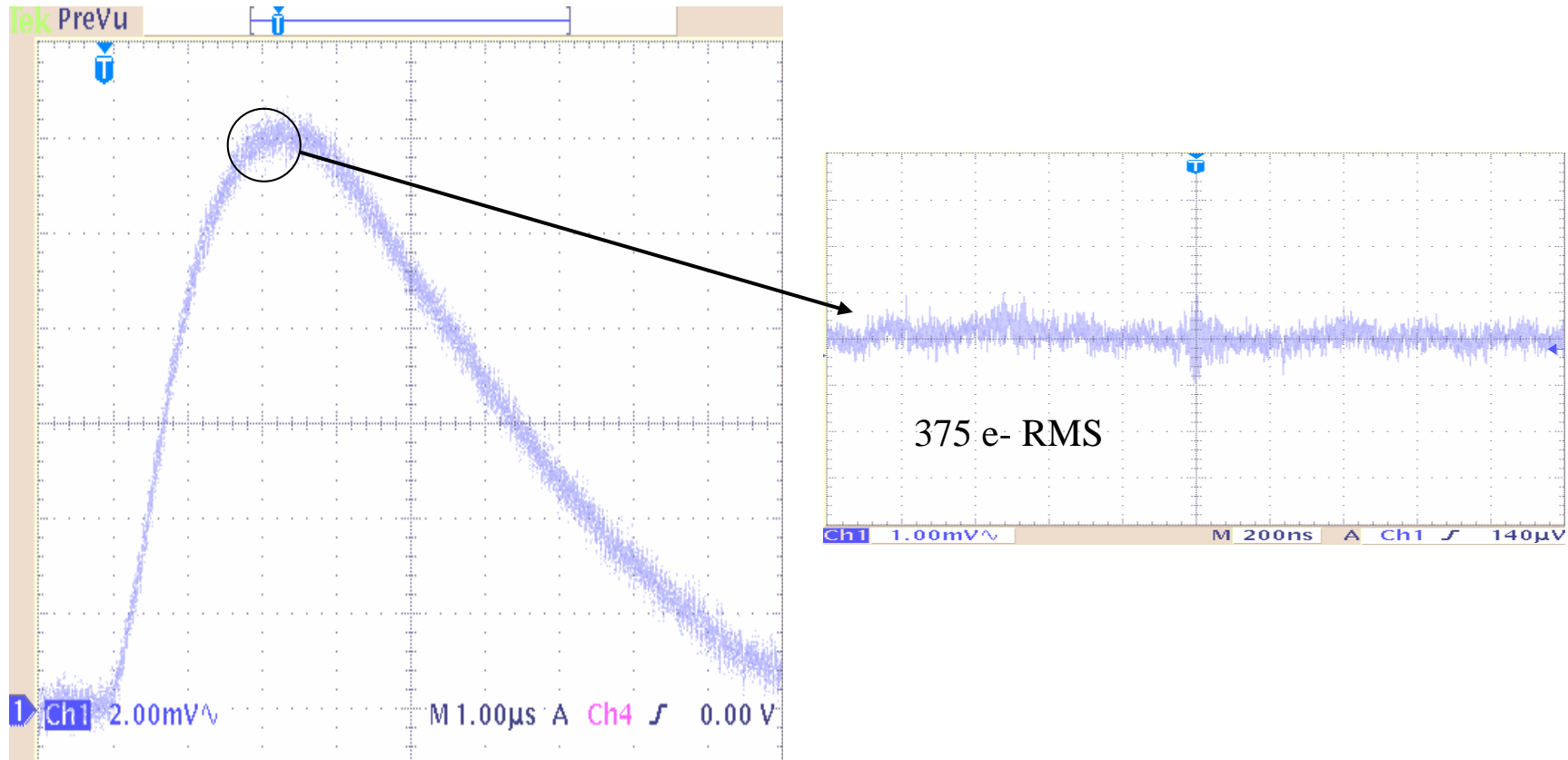

375 e- input noise with chip-on-board wire-bonding (against 280 simulated)

Shaper tests summary

Shaper: - Peaking time:

2 - 6 μs tunable peaking time 1-10 targeted

- 6 MHz bump (~ 650 e- added noise)

Not in simulations

Shows up in simulations at 10 pF load (actual is 1 pF)


- Noise @ 3 μs shaping time and 70 μW power:

375 + 10.4 e-/pF

274 + 8.9 e-/pF expected

Noise summary

good agreement with expected values

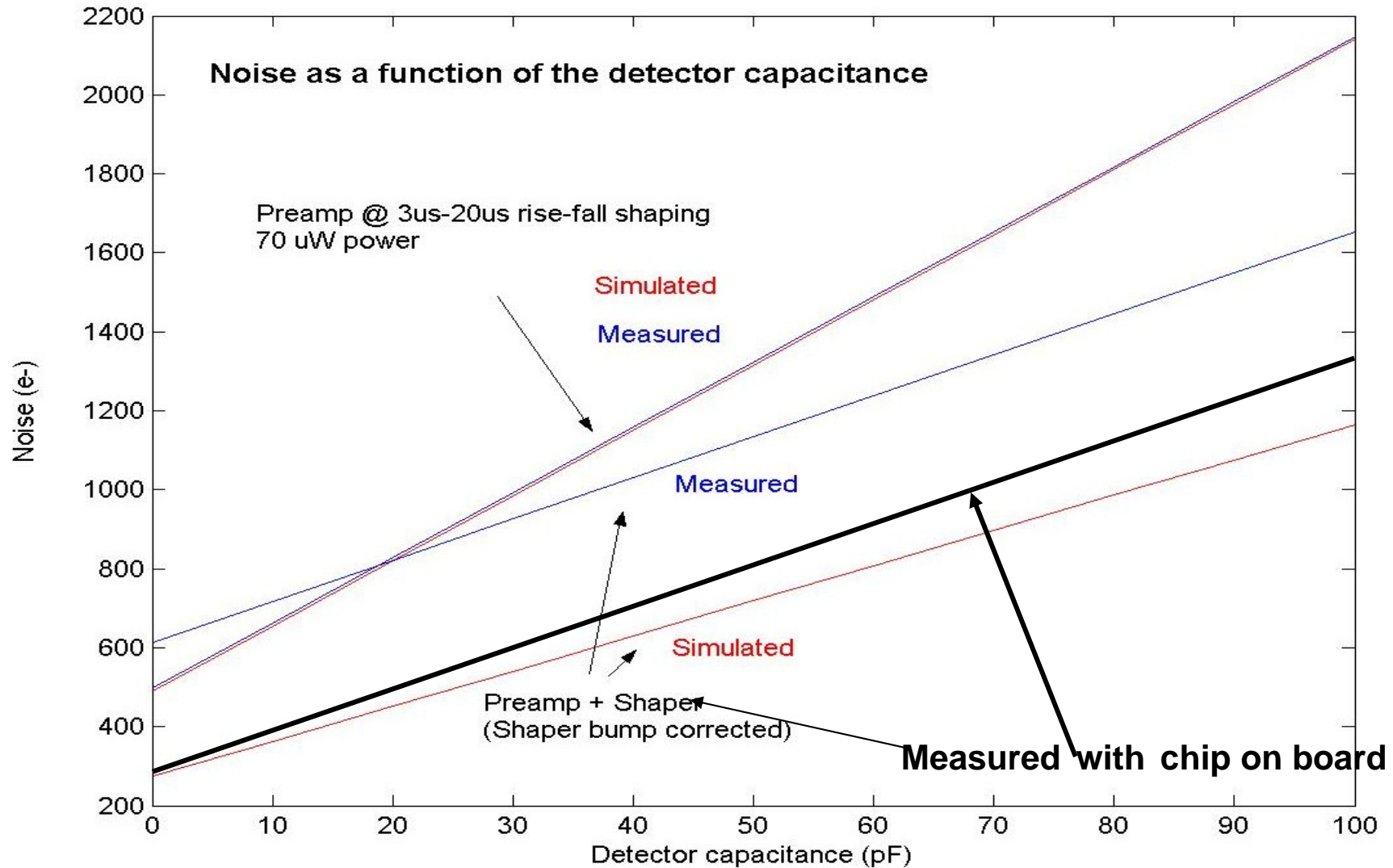

Jean- Francois Genat, LCWS06, March 9- 13th, Bangalore, India

Sample & Hold Comparator

- Sample and hold: OK
- Comparator:

Vt spreads of the order of 5 mV due to transistors sized too small

- Increase input transistors size from 10/0.5 to 200/10
- Increase Preamp + Shaper voltage gain from 8 to 25 mV/MIP

Tests Conclusions

12 chips tested

The UMC CMOS 180nm process looks quite mature and reliable:

- Models OK
- Only one transistor failure
- Process spreads of a few %

Preamplifier: almost according to specs

Shaper: a bit more noise than expected but OK with simulations

Comparator: V_t spreads understood

First proto delivered functional chips in a relatively new (in our field) DSM technology.

Encouraging results regarding CMOS DSM

Jean- Francois Genat, LCWS06, March 9- 13th, Bangalore, India

Next designs

Front-end in CMOS 130nm


Cooperation between LPNHE and LAPP Annecy and soon with CERN (A. Marchioro et al., EUDET)

Why 130nm ?

- VLSI
- Will be dominant in industry in the next few years
- Faster
- Lower power


Drawbacks for low noise analog design

Preamp in 130nm

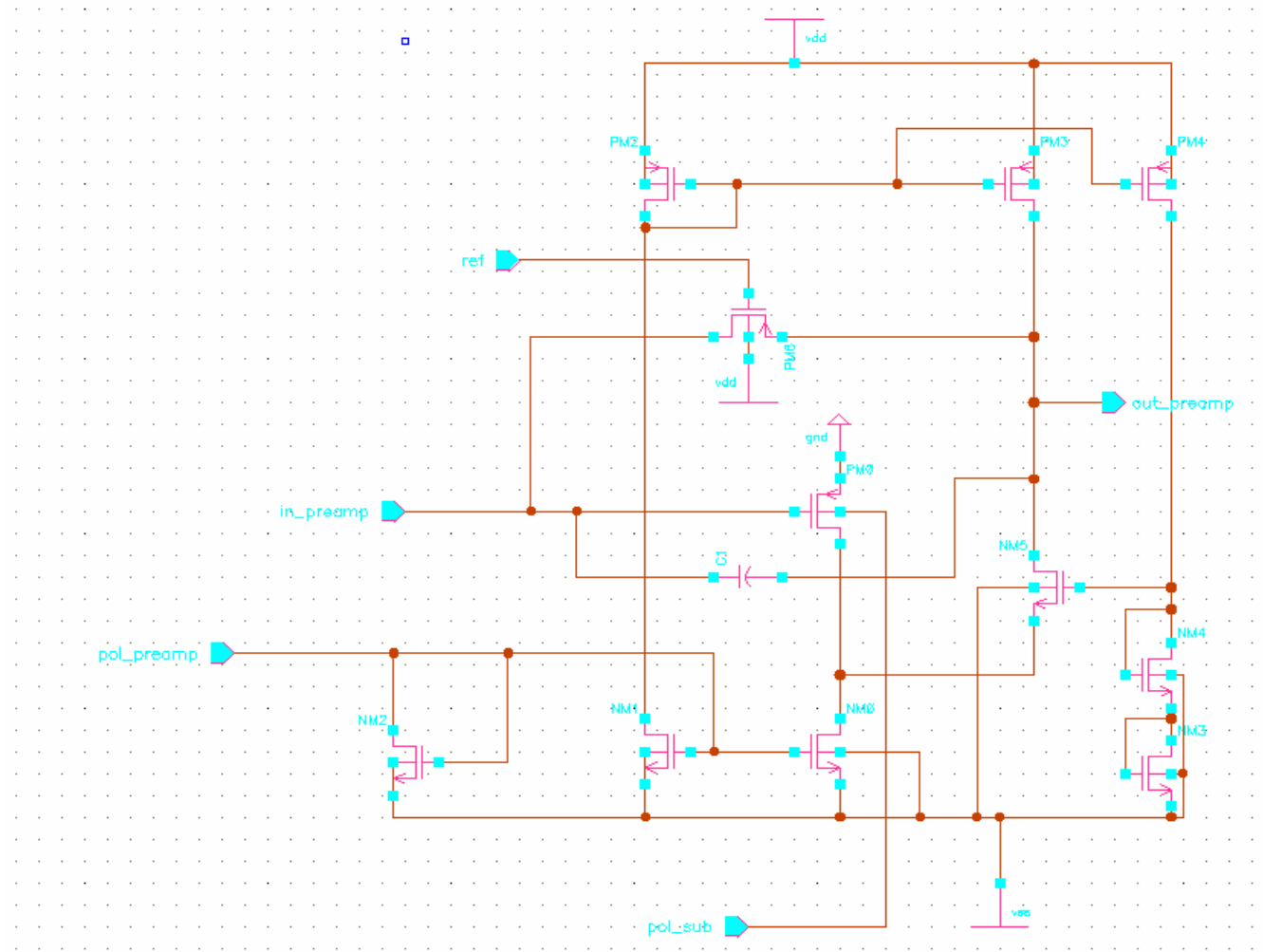


Jean- Francois Genat, LCWS06, March 9- 13th, Bangalore, India

Shaper in 130nm

 

130nm Sparsifier

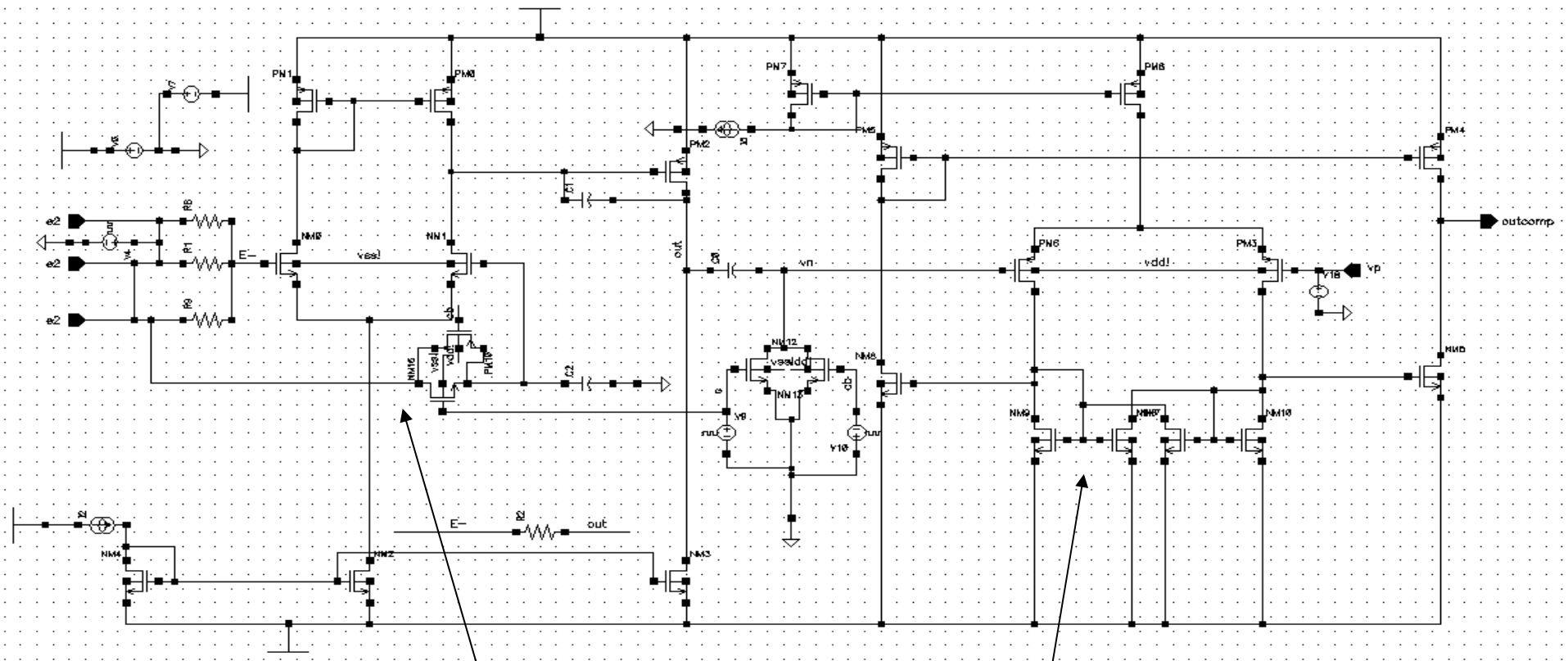

- Sum of adjacent channels
- Offset cancelled Threshold detection

Jean- Francois Genat, LCWS06, March 9- 13th, Bangalore, India

130nm plans

130 nm technology available end 2005 from Europractice

- Submit a 4 channel version end April 2006 including:
 - Preamp + Shaper
 - Sampling and analog pipe-line
 - ADC
 - Power cycling

Then, depending on tests

- Submit a 128 channel version end 2006 including digital

Front-End Digital in 130nm

- Chip control
- Buffer memory
- Processing for
 - Calibrations
 - Amplitude and time least squares estimation, centroids
- Tools
 - Digital libraries in 130nm CMOS available
 - Synthesis from VHDL/ Verilog
 - SRAM memory
 - PLLs

Conclusions

- CMOS 180nm chip tested, very encouraging results
- CMOS 130nm under way, include:

Preamps + Shapers
Analog pipe-lines
Sparsifiers
ADC
Power cycling

Submission end April 2006

- 180 and 130nm chips beam tests scheduled (DESY, CERN)
- Plans for 128 channels

This document was created with Win2PDF available at <http://www.win2pdf.com>.
The unregistered version of Win2PDF is for evaluation or non-commercial use only.