


RF Tutorial 2017

A) Design of a “pillbox” cavity

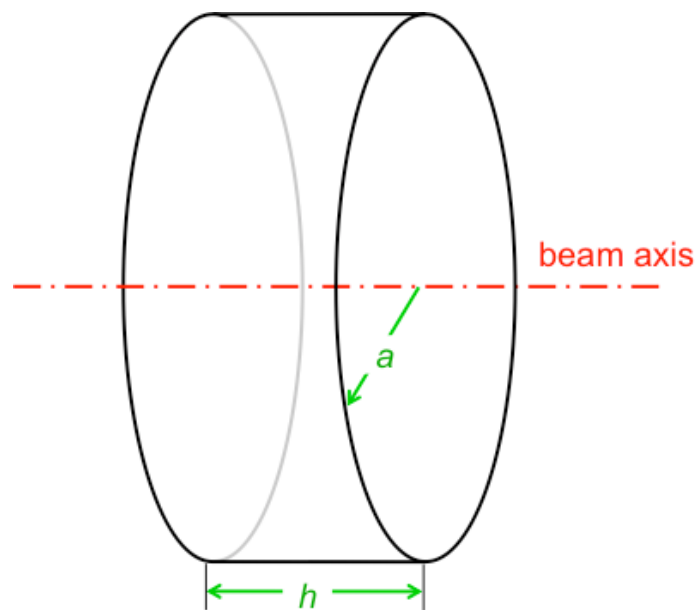Problem: Design a simple “Pillbox” cavity with the following parameters

Frequency: $f = 299.98 \text{ MHz}$ ($\lambda = 1.00 \text{ m}$)
Wall material: Copper (equivalent skin depth $\delta = 3.8 \text{ }\mu\text{m}$)
Axial length: $h = 0.2 \text{ m}$

For this example, we ignore beam ports, i.e. vacuum chamber stubs required for the beam passage, so that all analytical formulas describing the pillbox cavity apply.



Questions:

1. Find from the analytical formulas:
 - Cavity radius a
 - Cavity quality factor Q
 - “geometry factor”, also known as “characteristic impedance” R/QIs the cavity completely determined?
2. Find the equivalent circuit of the intrinsic cavity.
3. Calculate the 3-dB bandwidth of the intrinsic cavity.
4. Calculate the necessary RF power for a gap voltage of $V = 100 \text{ kV}$
5. The cavity is fed by an amplifier, designed for a load impedance of $50 \text{ }\Omega$. Determine:
 - The peak voltage at the cavity input.
 - The necessary transformer ratio k of the input coupler.

B) Impedances in the complex plane (1)

Questions:

1. Plot the following impedances in the Z-plane, use the plot axes on the next page:

$Z = (3 + 4j) \Omega$	$ Z = 2, \arg(Z) = \pi/4$	$Z = \text{short circuit}$
$Z = 2 \Omega$	$ Z = 1, \arg(Z) = -\pi/2$	$Y = Z^{-1} = (0.16 + 0.12j) \Omega^{-1}$
$Z = (1 - 4j) \Omega$	$ Z = 5, \arg(Z) = 53^\circ$	


2. Qualitatively, how would an inductor look like, plotted from DC to some arbitrary frequency, in the Z-plane?

Hint: $Z_L = j\omega L$

3. How would a capacitor look like? Hint: $Z_C = 1/(j\omega C)$
4. The input impedance of a RLC circuit has been plotted in the Z-plane (blue circle).


Mark the points in the diagram describing:

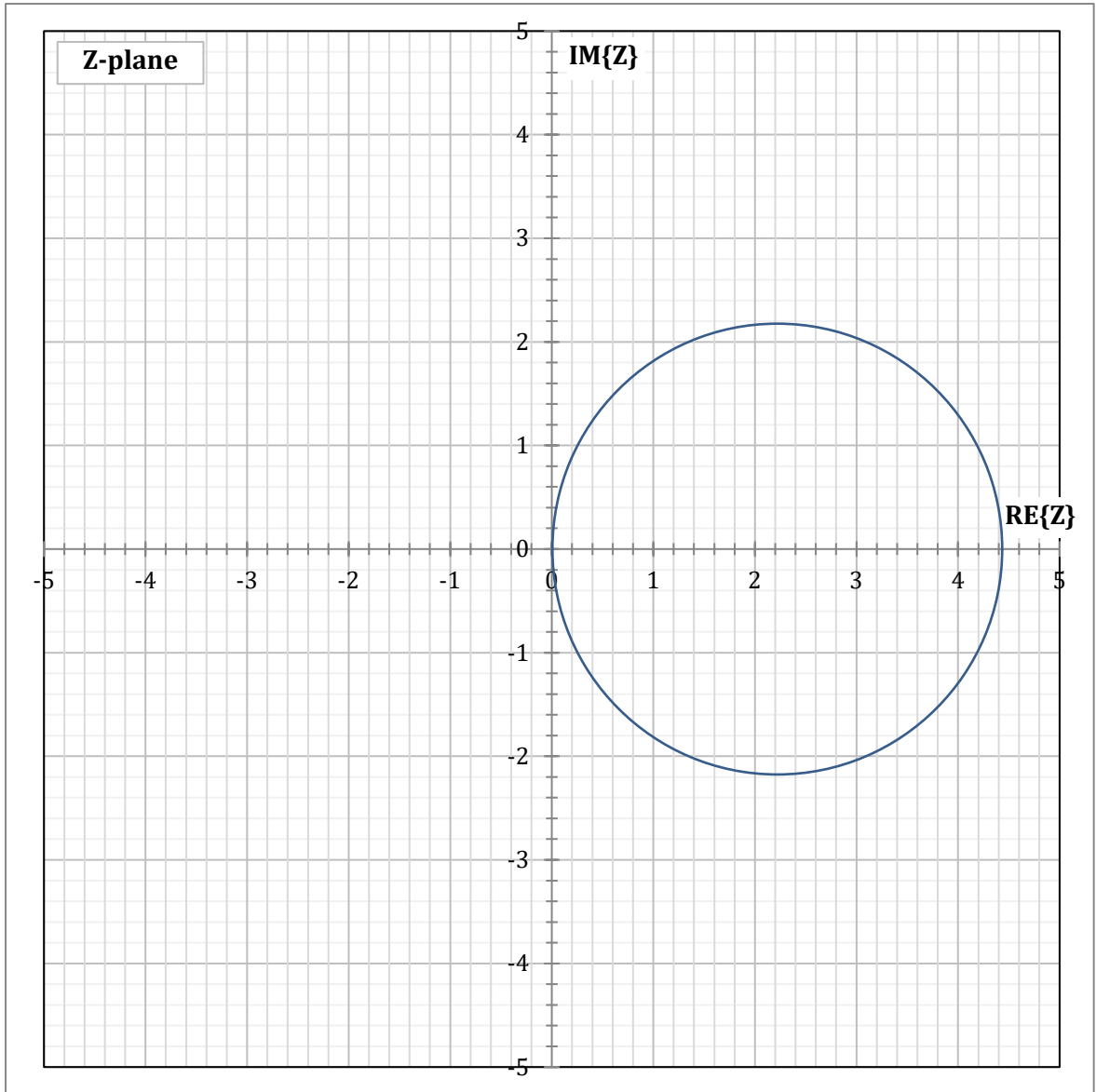- a. Impedance at the resonant frequency
- b. DC impedance
- c. 3-dB bandwidth
- d. Impedance at $f \rightarrow \infty$



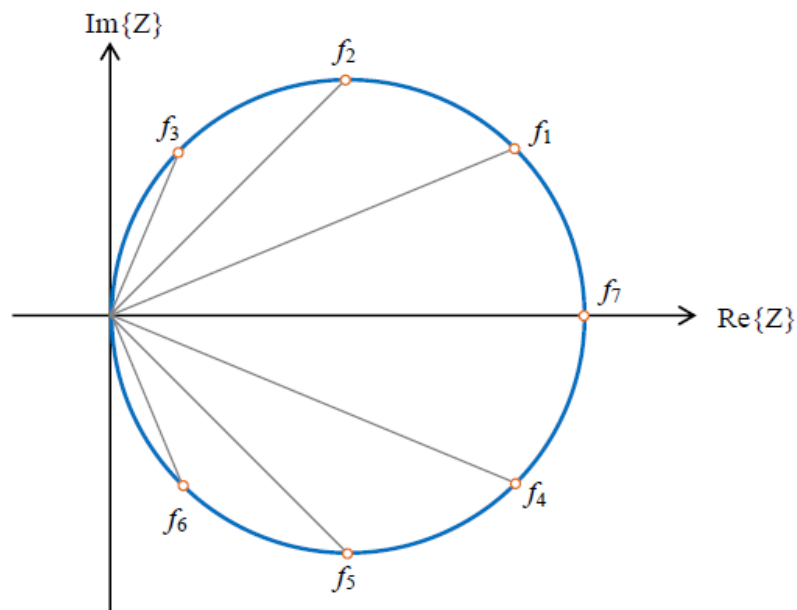D) Impedances in the complex plane (2)

The impedance of a resonant circuit is a function of frequency. For a given resonator the impedance was measured at 7 different frequencies, $f_1 \dots f_7$. The result is shown in the complex Z -plane:



	f_1	f_2	f_3	f_4	f_5	f_6	f_7
f / MHz	105.11	105.05	104.94	105.29	105.35	105.46	105.20
$Z / \text{k}\Omega$	$200 e^{j30^\circ}$	$162.6 e^{j45^\circ}$	$115 e^{j60^\circ}$	$200 e^{-j30^\circ}$	$162.6 e^{-j45^\circ}$	$115 e^{-j60^\circ}$	$230 e^{j0^\circ}$

Questions:

1. Determine the resonant frequency.
2. Determine the 3-dB bandwidth (BW) of this resonator.
(Hint: The bandwidth of a resonator is defined as the frequency difference between the upper and lower 3-dB frequency points.)

In order to evaluate the properties of a resonator, it is common to model it as equivalent circuit with lumped RLC elements.

3. Sketch the equivalent circuit for the measured resonator.
4. Determine R .
5. Draw the locus of admittance of this circuit in the Y -plane, and indicate lower and upper 3-dB points.
6. Determine the Q -value, as well as L and C for this circuit.

C) "Pillbox" cavity characteristics

The following data was measured on a "pillbox" cavity:

Inductance: $L = 15.915 \text{ nH}$
Capacitance: $C = 1.5915 \text{ pF}$
3-dB bandwidth: $BW = 50 \text{ kHz}$

Questions:

Determine

- the frequency at resonance
- the characteristic impedance R/Q
- the quality factor Q
- the time constant τ
- the peak induced voltage immediately after the passage of a short particle bunch with charge $q = 15.916 \text{e-}9 \text{ As}$
- the remnant cavity voltage $10 \mu\text{s}$ after the passage of the bunch

D) An accelerator cavity heats up under high RF power load

A cavity is constructed from a material with"

C_2/C_1

thermal expansion coefficient: $\Delta l/l = 20 \text{e-}6/^\circ\text{C}$ (per degree Centigrade)

thermal resistivity coefficient: $\Delta\rho/\rho = 4 \text{e-}3/^\circ\text{C}$ (per degree Centigrade)

At room temperature the cavities resonance frequency is $f_1 = 100 \text{ MHz}$, and has a 3-dB bandwidth of $BW_1 = 100 \text{ kHz}$.

Under RF power the cavity temperature increases by $100 \text{ }^\circ\text{C}$ (subscripts 2 apply).