

# Design and submission of the RD53A chip

Luigi Gaioni<sup>a,b</sup>

On behalf of the RD53 Collaboration

<sup>a</sup>University of Bergamo

<sup>b</sup>INFN Pavia



**AIDA-2020 2nd Annual Meeting**

**4-7 April 2017 - LPNHE, Paris**

# Outline


- RD53 - Challenges & Goals
- The RD53A demonstrator: overview and floorplan
- Analog front-end design
- Status and Conclusions

# RD53 - An overview

- Focused R&D program aiming at the **development of pixel chips** for ATLAS/CMS **phase 2 upgrades**
- 19 institutions from Europe and US
  - Bari, Bergamo-Pavia, Bonn, CERN, CPPM, Fermilab, LBNL, LPNHE Paris, Milano, NIKHEF, New Mexico, Padova, Perugia, Pisa, Prague IP/FNSPE-CTU, RAL, Seville, Torino, UC Santa Cruz.
- **65 nm CMOS** is the common technology platform
- RD53 Goals:
  - Detailed understanding of **radiation effects** in 65nm → guidelines for radiation hardness
  - Development of **tools and methodology** to efficiently design large complex mixed signal chips
  - Design of a **shared rad-hard IPs library**
  - Design and characterization of common engineering run with **full sized pixel array chip**
 
# RD53A - Large Scale prototype

- The efforts of the RD53 collaboration are leading to the submission of the RD53A chip
- 400 x 192 pixel, 50um x 50um pixel, 20mm x 11.8mm chip
- **Goal: demonstrate in a large format IC**
  - suitability of **65nm technology** (including radiation tolerance)
  - **high hit rate**: 3 GHz/cm<sup>2</sup>
  - **trigger rate**: 1 MHz
  - **Low threshold operation** with chosen **isolation** strategy and **power distribution**
- **Not intended to be a production chip**
  - will contain design variations for testing purposes (with **3 different versions of the analog very front-end**)
  - wafer scale production will enable prototyping of bump bonding assembly with realistic sensors in new technology
- **Final design almost ready**
- **Submission: May 31, 2017**



# RD53A main specifications

<http://cds.cern.ch/record/2113263>

From the Spec. document

- **Hit rate:** up to 3 GHz/cm<sup>2</sup> (75 kHz pixel hit rate)
- **Detector capacitance:** < 100 fF (200 fF for the edge pixels)
- **Detector leakage:** 10 nA (20 nA for the edge pixels)
- **Trigger rate:** max 1 MHz
- **Trigger latency:** 12.5 us
- **Low threshold:** 600 e<sup>-</sup> → severe requirements on noise and dispersion
- **Min. in-time overdrive:** < 600e<sup>-</sup>
- **Noise occupancy:** < 10<sup>-6</sup> (in a 25ns interval)
- **Hit loss @ max hit rate:** 1%
- **Radiation tolerance:** 500 Mrad @ -15° C

# Radiation tolerance

- RD53A should be able to withstand with radiation dose levels at least **up to 500 Mrad**
- Extensive irradiation campaign in past 3 years to qualify the technology
- Significant radiation damage above 100 Mrad:
  - Analog: transconductance,  $V_t$  shift
  - Digital: speed degradation


**See M. Menouni talk**

- **CHIPIX65** and **FE65-P2** demonstrator being characterized after irradiation

**See N. Demaria talk for the CHIPIX demonstrator**


- 200 Mrad and 500 Mrad **simulation models** were developed to “predict” the circuit behavior and have been extensively exploited during design phase

# RD53A floorplan

 
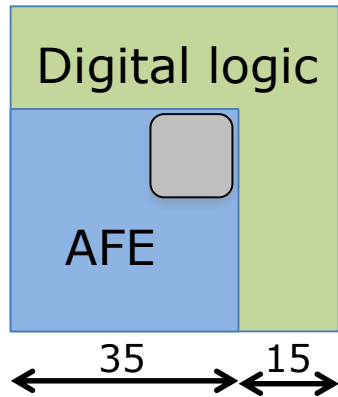
# RD53A Pixel floorplan


- 50% Analog Front End (AFE) - 50% Digital cells



The "analog island" concept



A "quad"

 


- The pixel matrix is built up of **8x8 pixel cores** → 16 analog islands (quads) embedded in a flat digital synthesized sea
- A pixel core can be simulated at transistor level with analog simulator
- All cores (for each FE flavour) are identical → Hierarchical verifications


 
# Pixel array logic organization

- **Basic layout unit:** 8x8 digital Pixel Core → synthesized as one digital circuit



- One Pixel Core contains multiple Pixel Regions and some additional arbitration and clock logic
- Pixel Regions share most of logic and trigger latency buffering

## Distributed Buffering Architecture (FE65\_P2 based):

- distributed TOT storage


## Centralized Buffering Architecture (CHIPIX65 based (4x4)):

- centralized TOT storage
- Integrated with Synch FE

See S. Marconi talk

# Digital Chip Bottom (DCB)

Single serial input stream

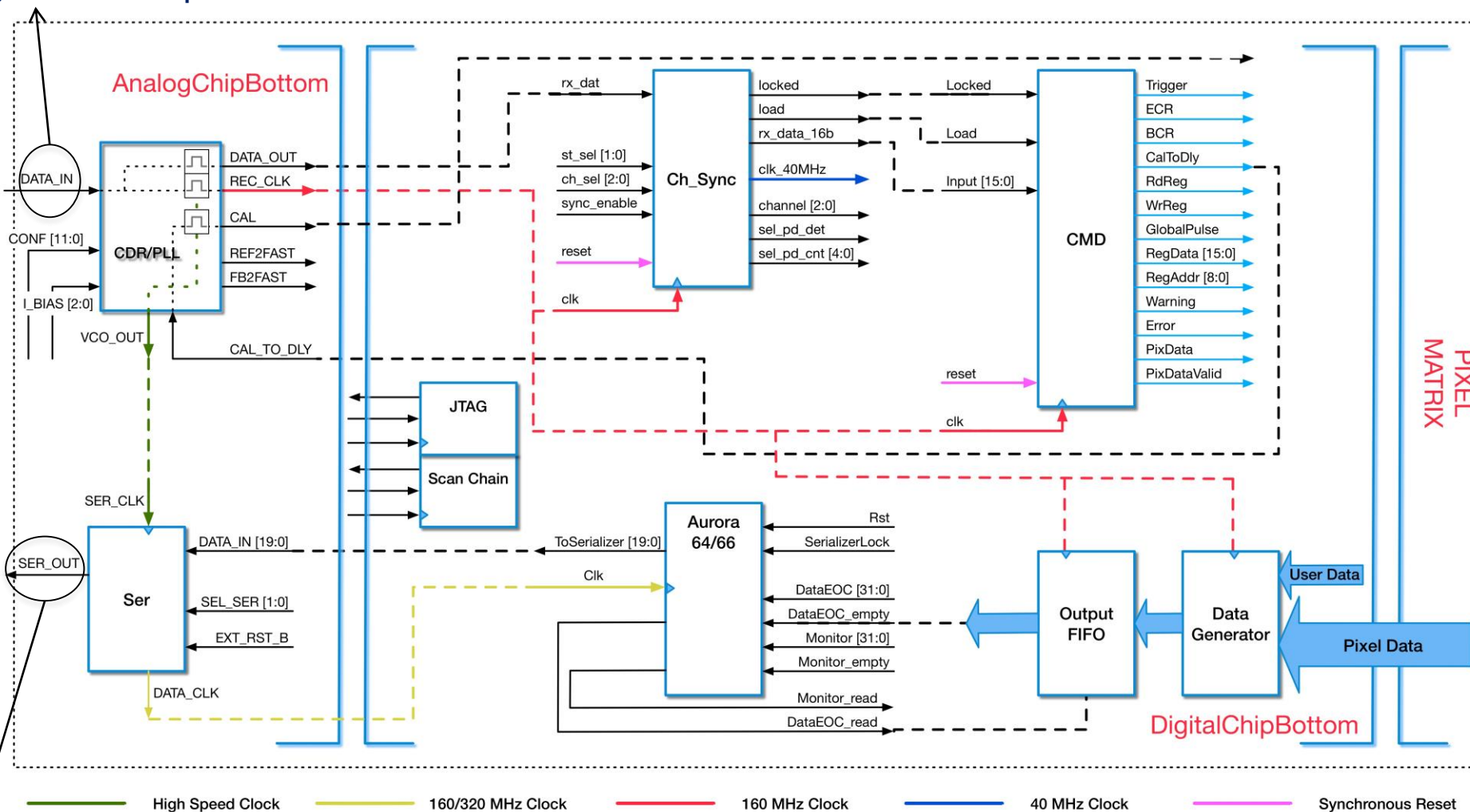


Port A: 1-2-4 CML outputs @ 1.28 Gbps

OR

Port B: 1 output @ 5.12 Gbps

 
# Serial Powering

- RD53A is designed to operate with **Serial Powering**  
→ constant current to power chips/modules in series
- Based on ShuntLDO
- Dimensioned for production chip
- **Three operation modes:**
  - ShuntLDO: constant input current  $I_{in}$  → local regulated VDD
  - LDO (Shunt is OFF) : external un-regulated voltage → local regulated VDD
  - External regulated VDD (Shunt-LDO bypassed)




# Analog front-ends


## Synchronous AFE

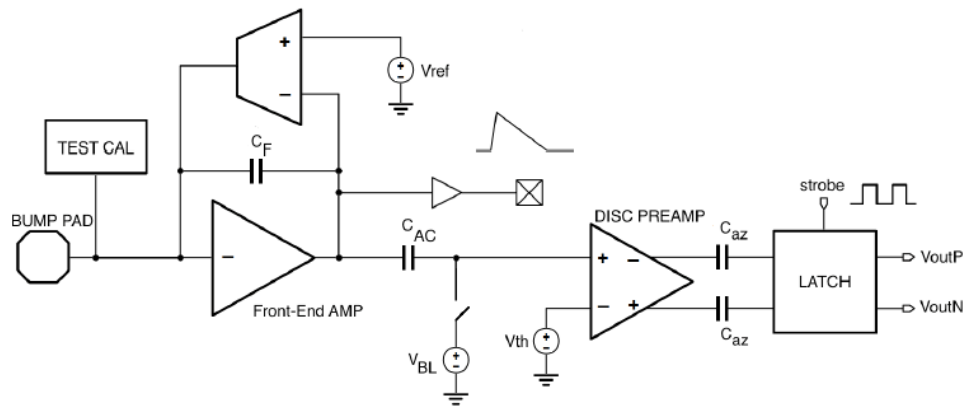

## Linear AFE

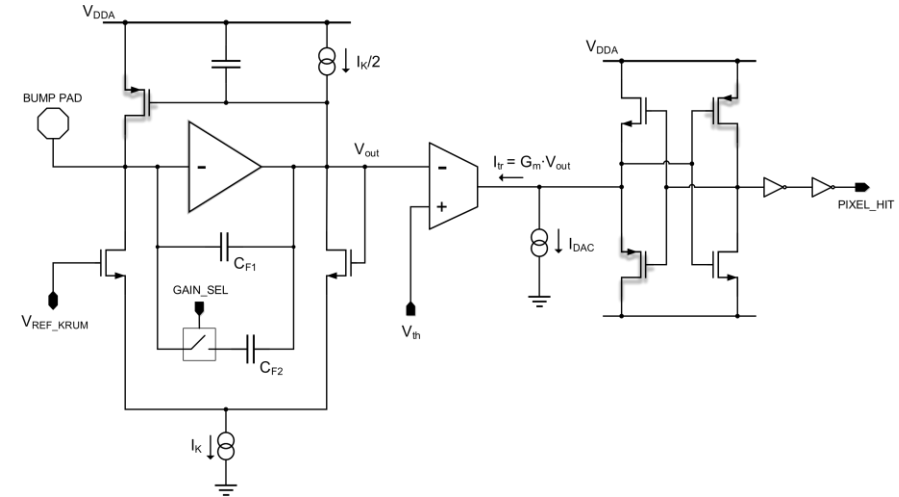


## Differential AFE

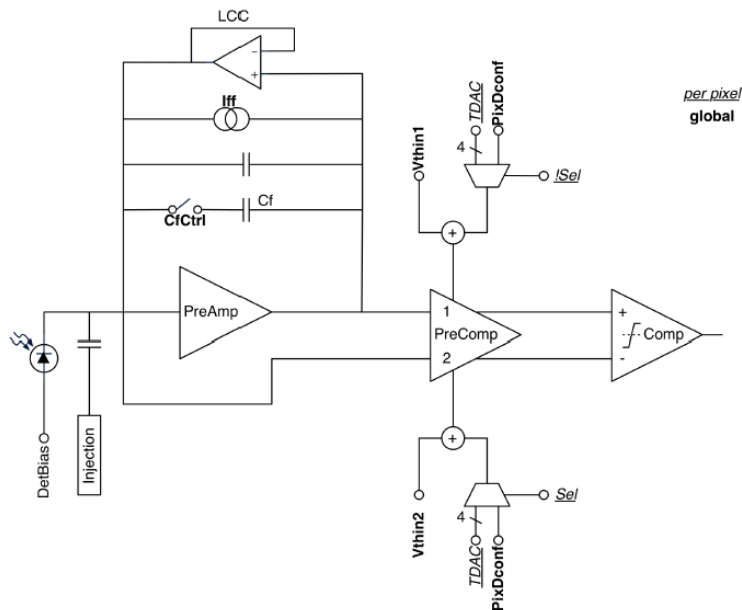


- 3 different version of the analog FE (AFE) will be integrated in RD53A
- Three design reviews (the last one in March 28, 2017) have been carried out for the AFEs.
- Final verifications of the AFEs ongoing

# Isolation strategy

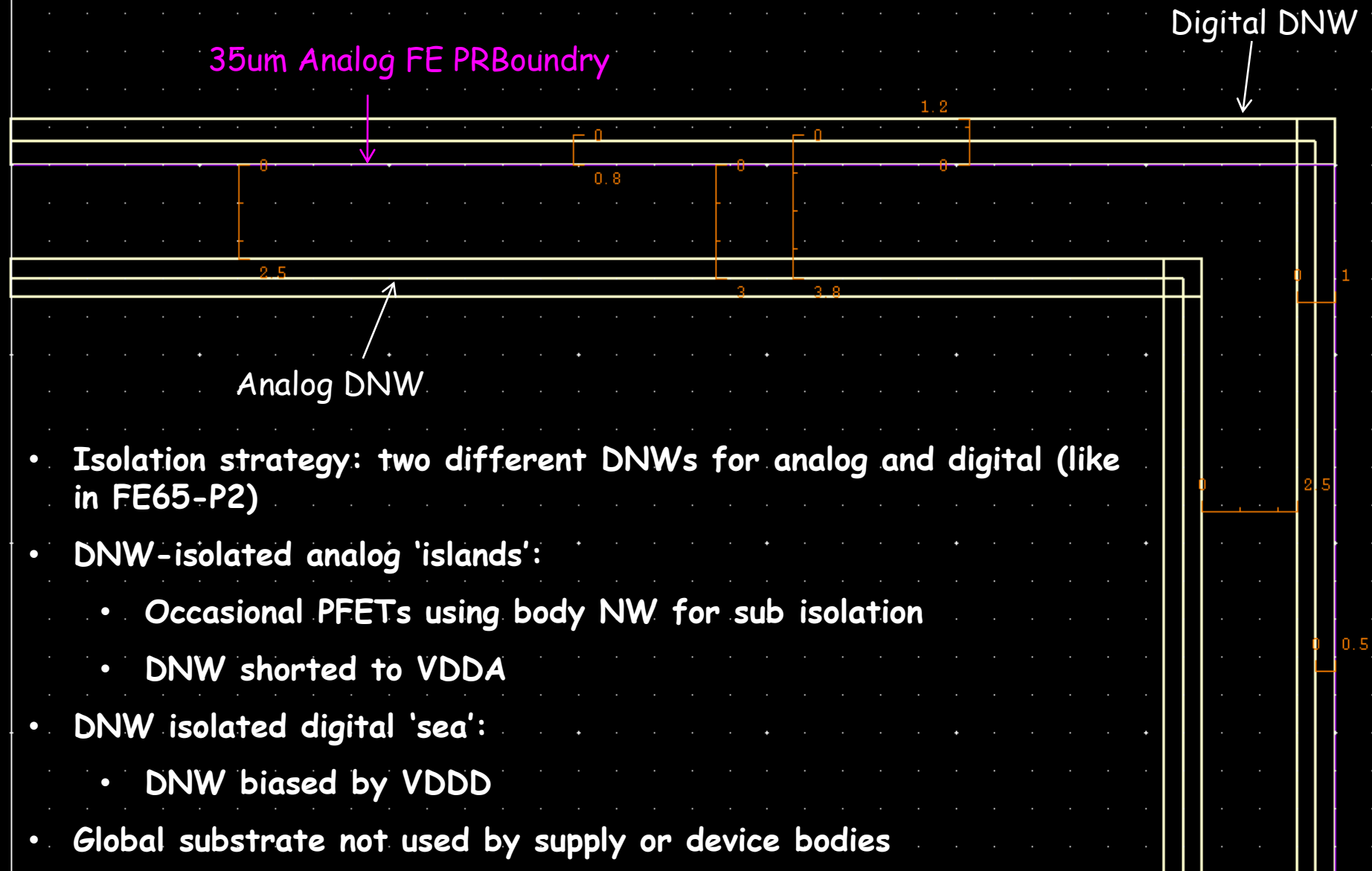


# Linear Analog Front-end

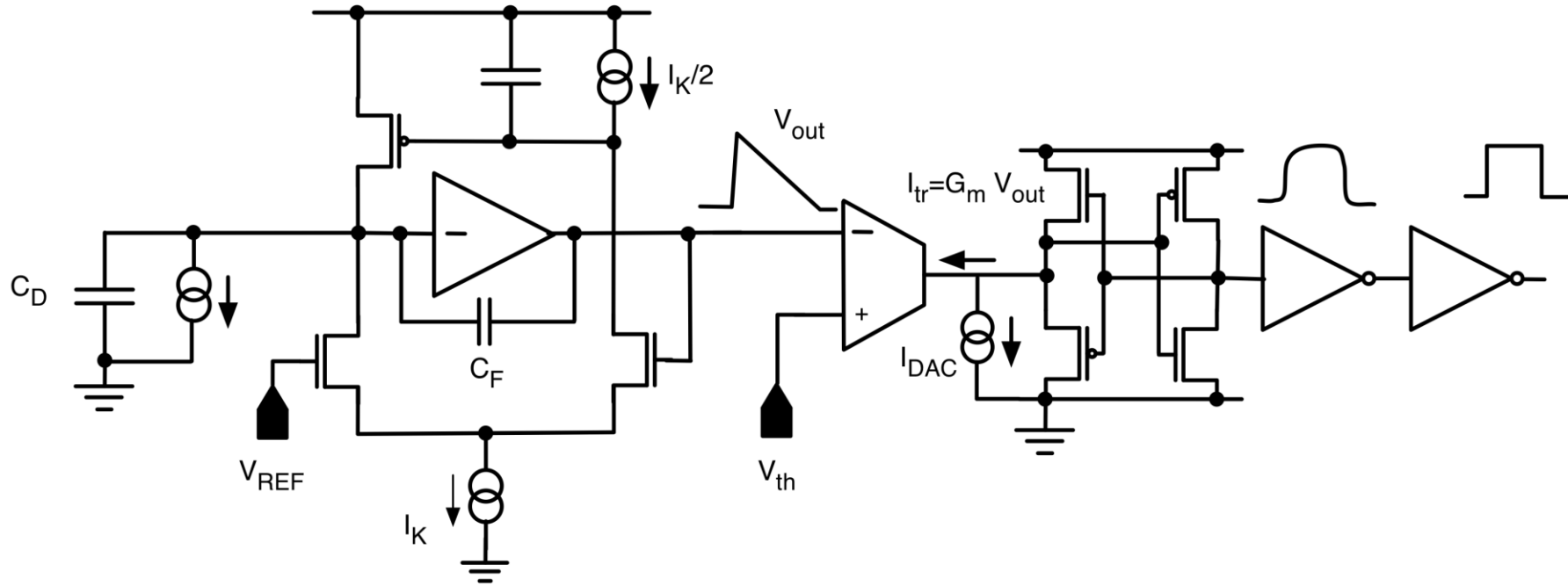


- **Single amplification stage** for minimum power dissipation
- **Krummenacher feedback** to comply with the expected large increase in the detector leakage current
- High speed, low power **current comparator**
- **4 bit local DAC for threshold tuning**
- **In-pixel calibration circuit**
- Selectable gain (1 bit) and recovery current (per. Bias DAC)
- Overall **current consumption**:  $\sim 4 \mu A$
- **Integrated/tested in CHIPIX65 (with slight modifications)**

# Synchronous Analog Front-end

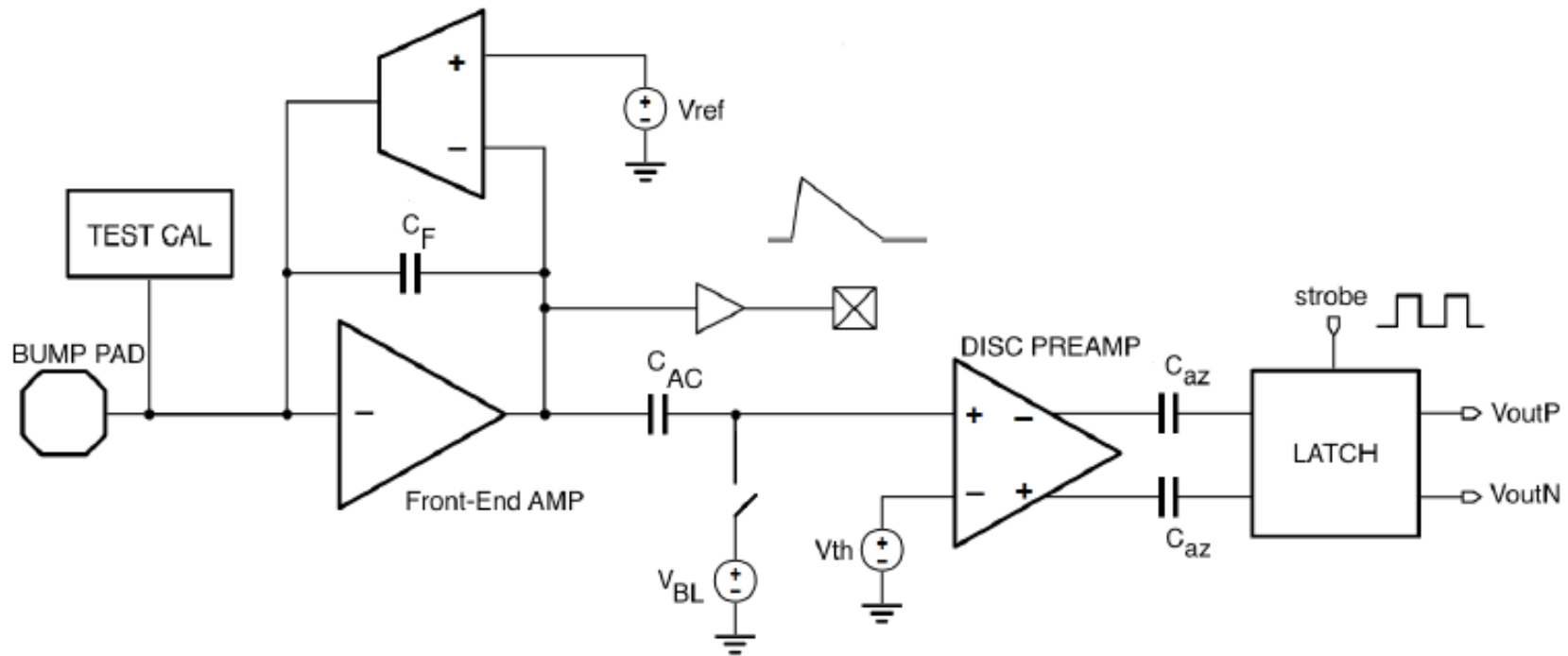

- **One stage CSA** with **Krummenacher** feedback for linear ToT charge encoding
- **Synchronous discriminator**, AC coupled to CSA, including offset compensated differential amplifier and latch
- Threshold trimming by means of autozeroing using capacitors
- **Fast ToT counting** with latch turned into a local oscillator (100-900 MHz)
- **Integrated/tested in CHIPIX65 demonstrator chip**

# Differential Analog Front-end

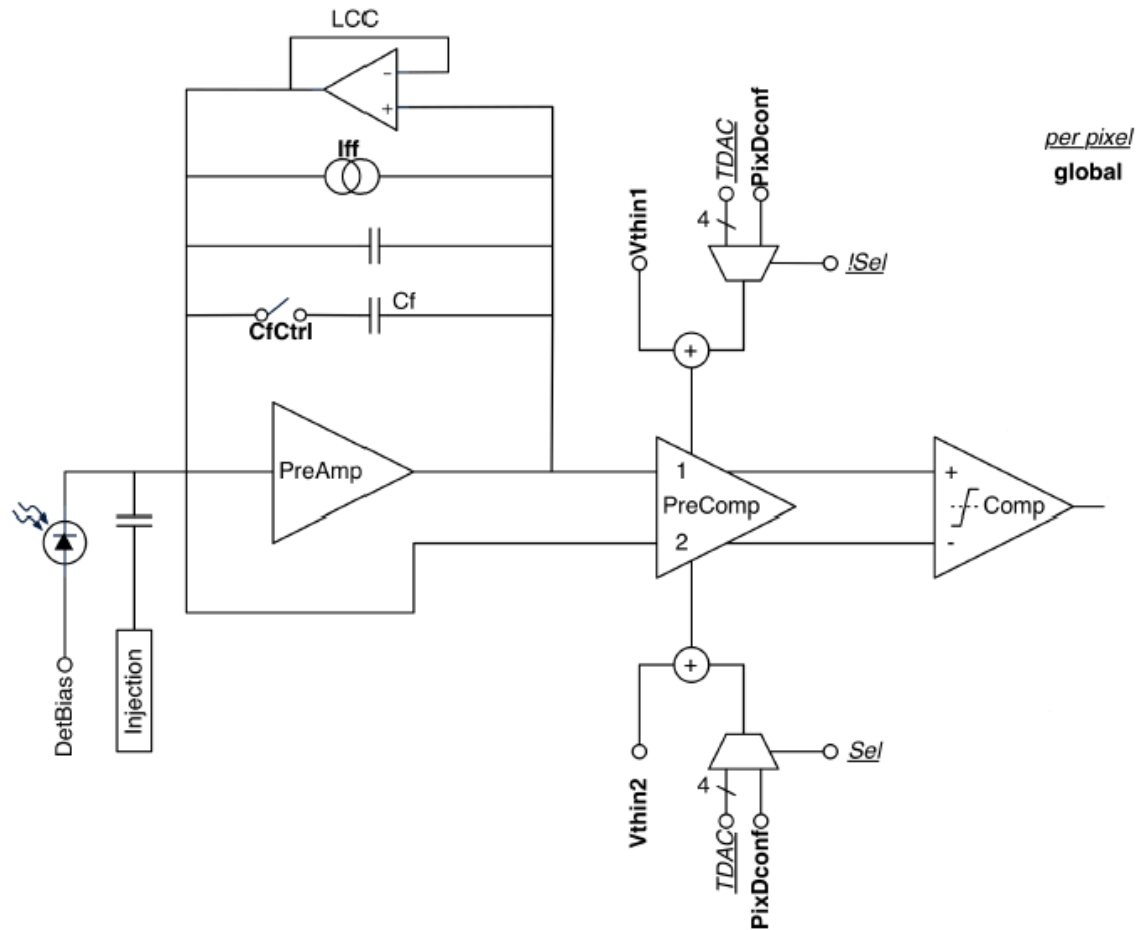


- **Continuous reset integrator** first stage with **DC-coupled pre-comparator stage**
- Two-stage open loop, **fully differential input comparator**
- **Leakage current compensation** (not shown) a la FEI4
- **Threshold adjusting** with global 8bit DAC and two per pixel 4bit DACs



# Calibration circuit

Common scheme for all the AFEs

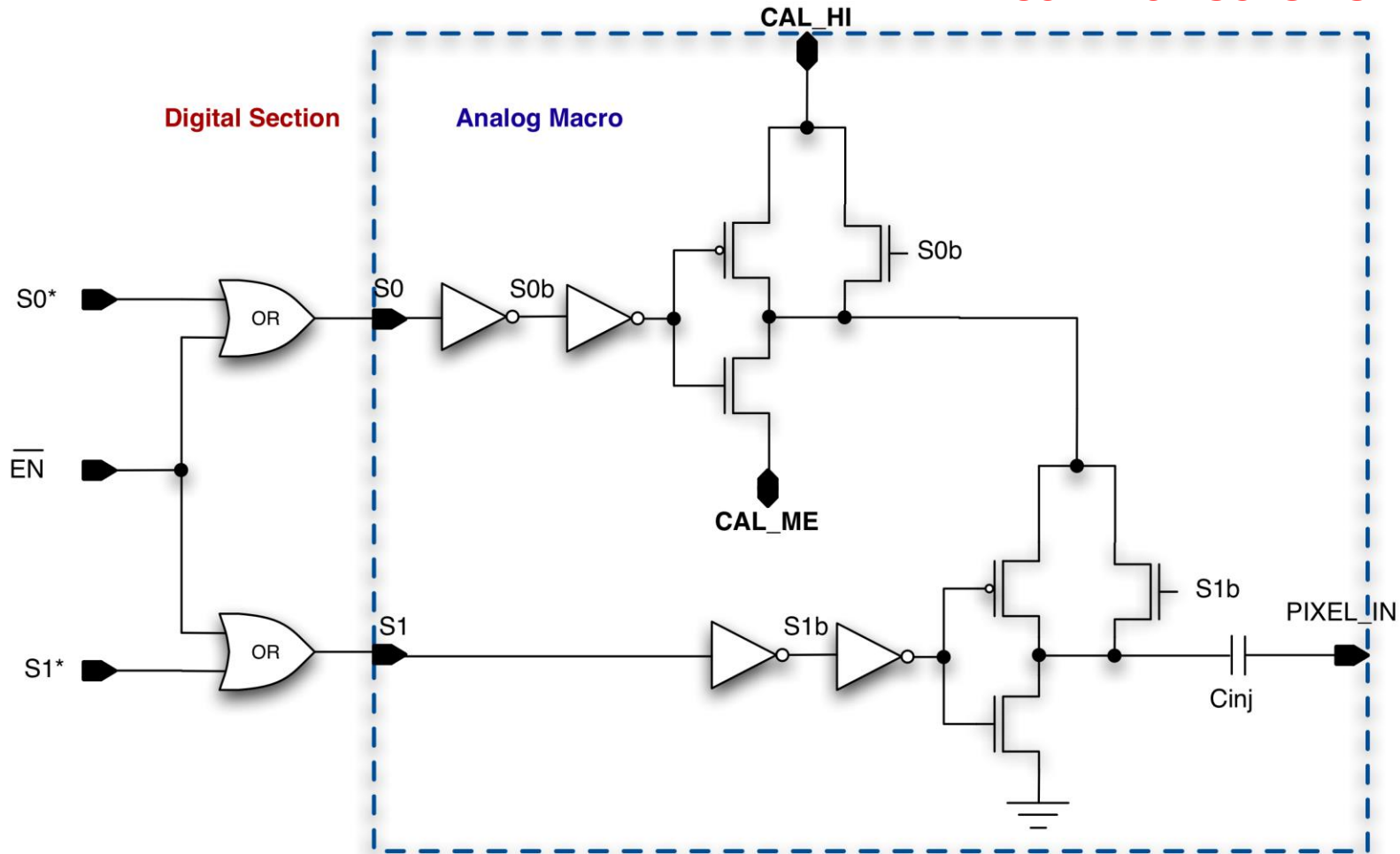

- **Local generation** of the analog test pulse starting from 2 defined DC voltages  $CAL\_HI$  and  $CAL\_ME$  distributed to all pixels and a 3<sup>rd</sup> level (local gnd)
- **Two operation modes** which allow to generate two consecutive signals of the same polarity or to inject different charges in neighboring pixels at the same time

# AFEs main features (reported in March design review)

	Synch AFE	Lin AFE	Diff AFE*	spec
Charge sensitivity [mV/ke]	43	25	103	-
ENC rms [e]	67	83	53	$\ll 126$
Threshold dispersion $\sigma(Q_{th})$ rms [e]	93	32	20	$\ll 126$
$\sqrt{ENC^2 + \sigma(Q_{th})^2}$ [e]	115	89	54	$\leq 126$
In-time overdrive [e-]	$\leq 50$	$\leq 100$	0	$\leq 600$
Current consumption [ $\mu A$ /pixel]	3.3 <sup>1</sup>	4.3	3.5	$\leq 4$
Time over threshold [ns]	121	99	118	$< 133$

- Post-layout simulations (\*except for the Diff AFE  $\rightarrow$  schematic level sim),  $CD=50fF$ ,  $T=27^\circ C$ ,  $Q_{th}=600e^-$ .
- In-time overdrive  $\rightarrow$  relative to a  $Q_{in}=30ke^-$
- Time walk  $\rightarrow$   $Q_{in}=1200 e^-$  (relative to a  $Q_{in}=30ke^-$ )
- ToT  $\rightarrow$   $Q_{in}=6ke^-$
- <sup>1</sup> 5.1uA including the latch

# Submission status

- **Analog Front-ends:**
  - Synchronous & Linear AFEs: final version ready → integrated with CORE
  - Differential AFE: final version ready → integration with CORE on going
- **Analog Chip Bottom (ACB):** assembly ready (RD53 IP blocks). Simulation with analog and mixed-signal simulator ongoing
- **Digital:** RTL ready, verifications on-going
- **Shunt-LDO:** 2A version of Shunt-LDO submitted on 19th Oct. 2016
  - Test of prototypes just started and looks promising
  - Irradiation campaign carried out
  - Simulation of full power system ShLDO-Bandgap-POR ongoing
  - Integration in IO Frame: almost done
- **IO Frame:** bottom PADS frame almost ready → 199 PADS with 100um pitch; passivation opening: 58um x 86 um; TSV Compatible. Top PAD frame (test and monitoring) assembly on-going.

**See H. Krüger talk**


# Conclusions

- The **RD53A demonstrator design** is being finalized in the framework of the RD53 Collaboration in a **65 nm CMOS technology**
- Goal of the RD53A chip is to demonstrate the feasibility of the 65 nm technology in facing the challenging requirements set by the **future experiment upgrades at the HL\_LHC**
- The large-scale chip will be submitted at the end of **May 2017**
- The **final design** is almost ready, extensive verifications are on-going




# Lin AFE schematic diagrams

## Preamplifier

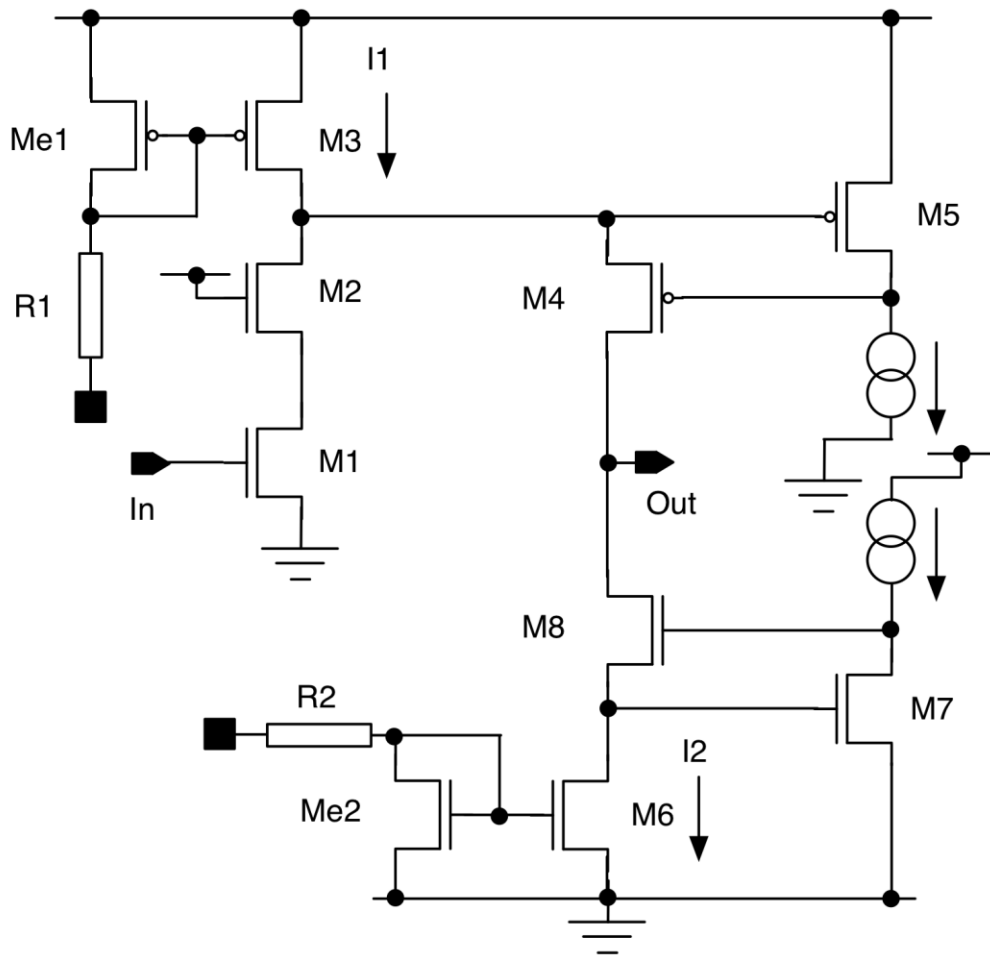

- Gain stage based on a **folded cascode** configuration ( $\sim 3$   $\mu A$  absorbed current) with a regulated cascode load


## Comparator

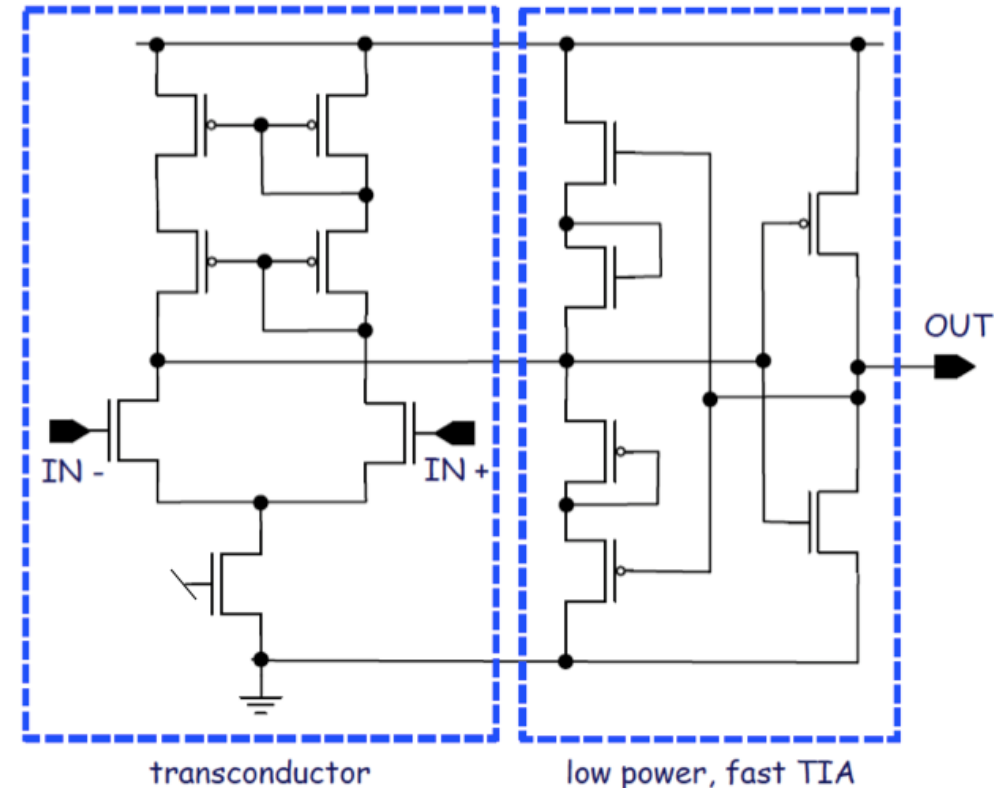

- Low power, **fast discriminator** ( $\sim 1$   $\mu A$  absorbed current) including  $G_m$  stage and a transimpedance amplifier providing a low impedance path for fast switching


# Sync AFE schematic diagrams

## Preamplifier

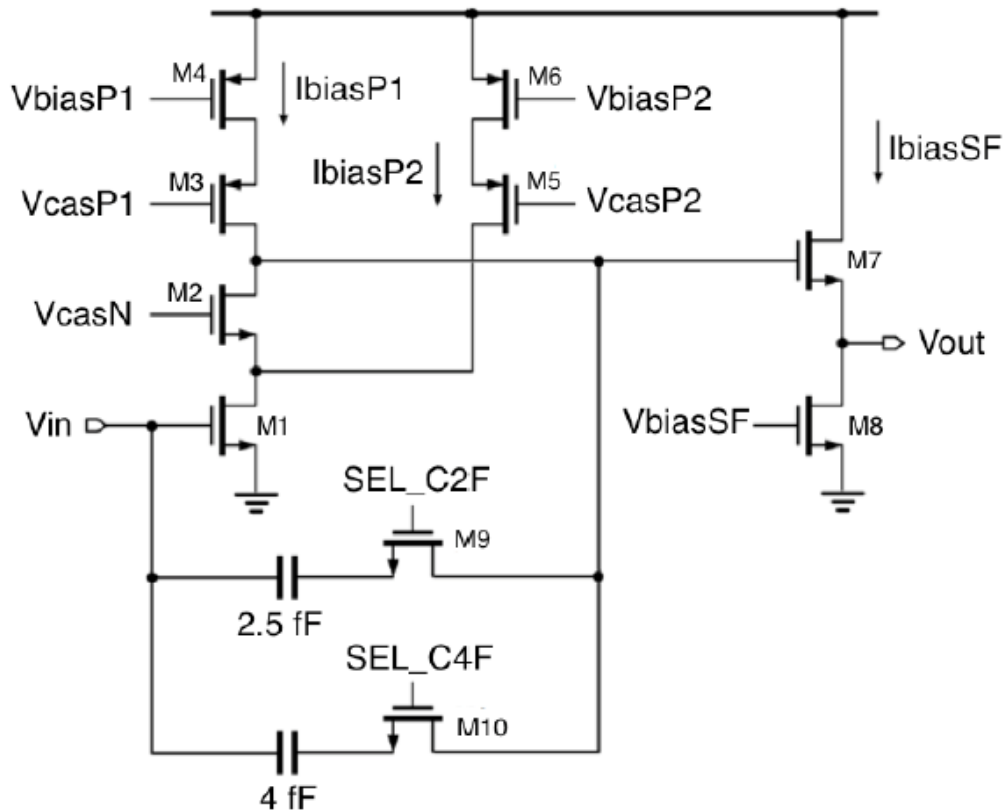


- Telescopic cascode with current splitting and source follower
- Two switches controlling the feedback capacitance value

## Comparator

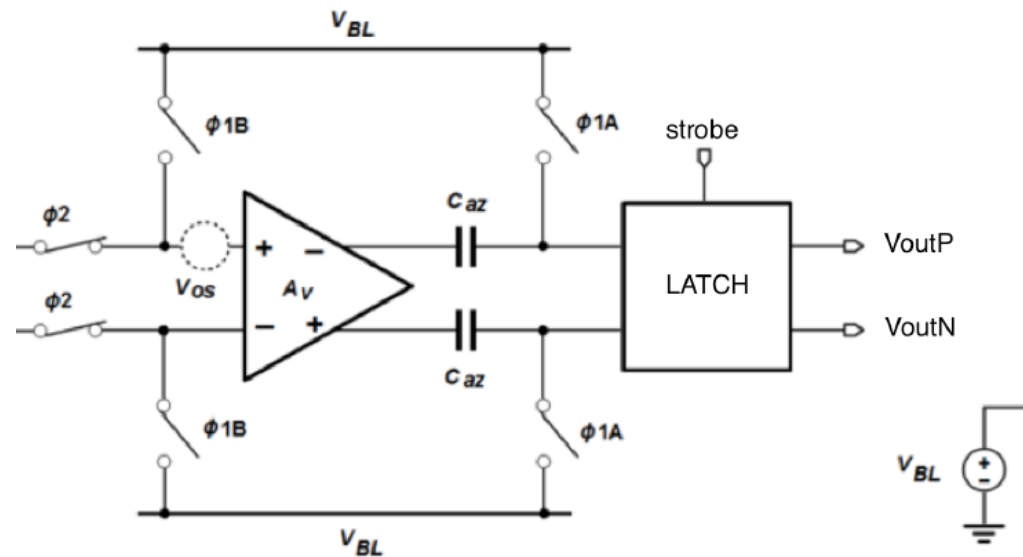


- Offset (and mismatch) cancellation based on **comparator autozero** (store offset on a capacitor, and then subtract it from signal + offset)

# Diff AFE schematic diagrams

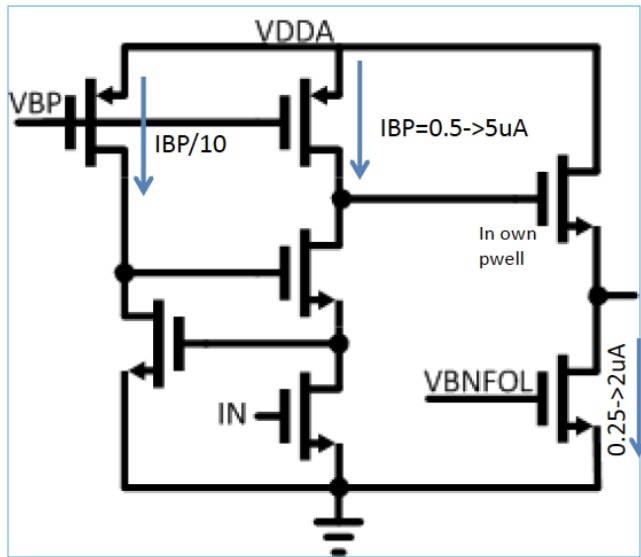
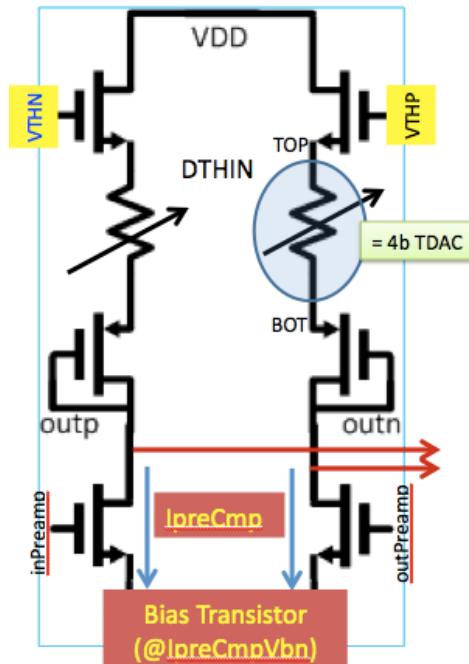
## Preamplifier

- Gain stage with active cascode
- Simple follower as buffer




## Pre-comp

- Fully differential amp w/ resistive load
- Acts as single-to-differential converter
- Global Vth DACs generates effective differential supplies
- Local DTHn trims binary-weighted resistive load
- Sets output CM and differential OP for comp




# Analog FE bias scheme

 

- Robust design
- Not sensitive to leakage
- "Double stage mirroring", biasing DACs and Bandgap references **already integrated/tested in CHIPIX65**

Pixel array


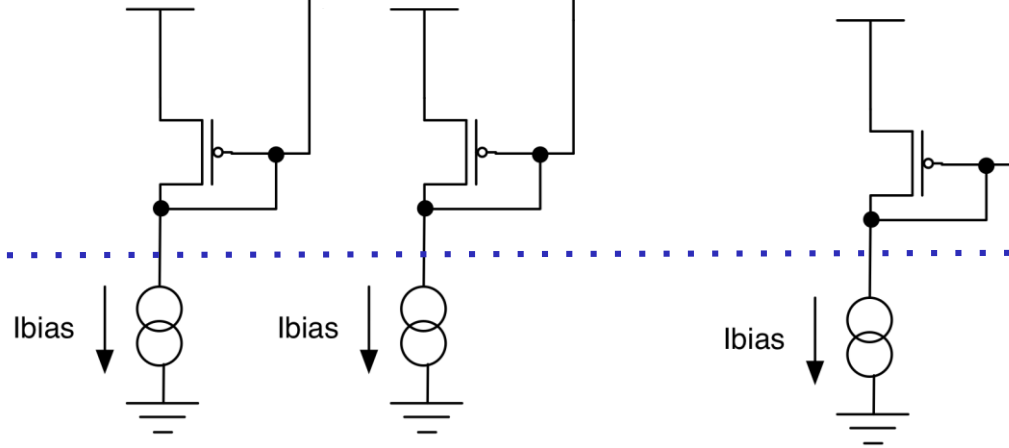


Second stage mirroring  
(Macrocol bias)

Biasing DACs + first stage mirroring  
(ACB)
 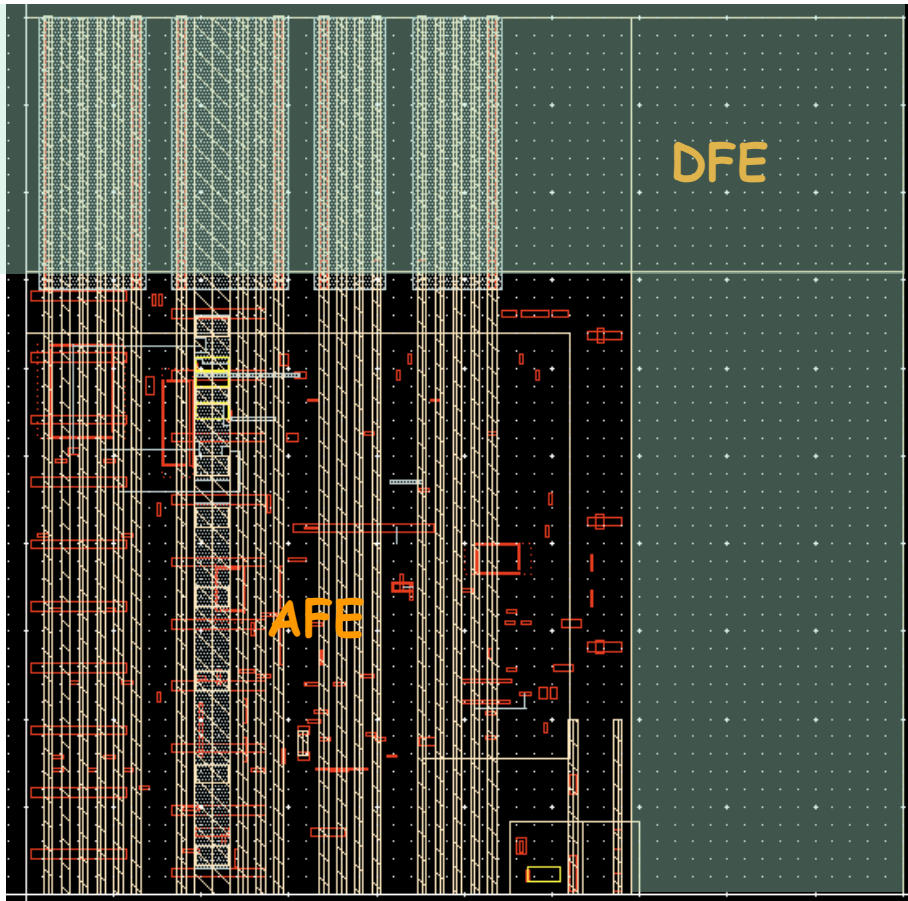
# Analog bias

- AFE area & arrangement → 35um x 35 um aspect ratio with "analog island" arrangement
- Same bump PAD structure
- Common strategy for power, bias distribution & shielding



- M6 V lines for the analog bias
- M5/M7 shield for bias lines in the digital section of the pixel
- AP/M9/M8 V supplies

# Pixel array logic organization

- Each Pixel Core receives all input signal from the previous core (closer to the Digital Chip Bottom)
- Regenerates the signals for the next core.
- The timing critical **clock** and **calibration injection** signals are internally delayed to have a uniform timing (within 1-2 ns)

