 




*Results on CHIPIX65 demonstrator:
a prototype of New Generation Pixel ROC
in 65nm CMOS technology*


L. Demaria, INFN / Torino



AIDA-2020 II Annual Meeting - Parigi 6/4/2017



CHIPIX65 demonstrator

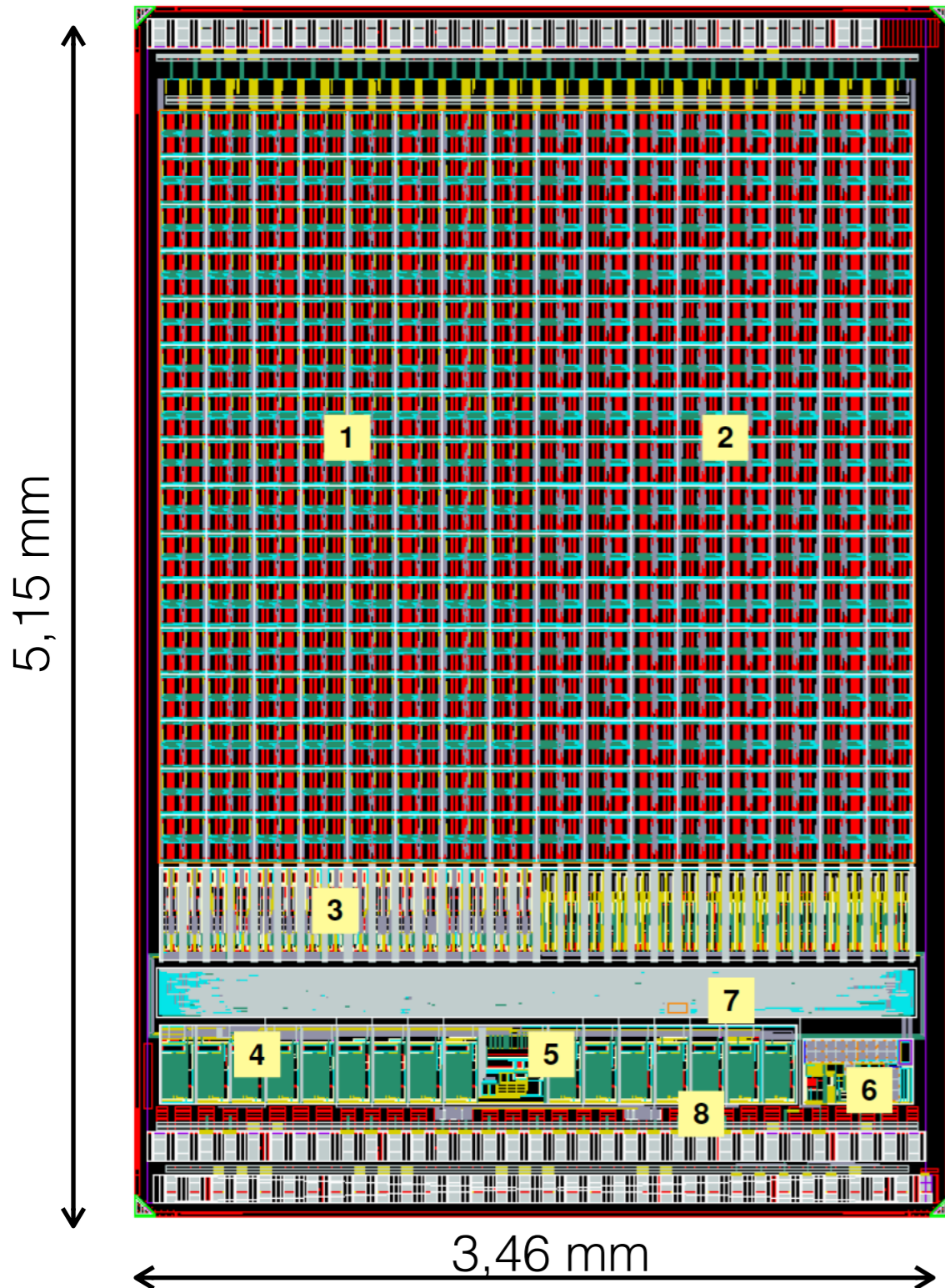

- 1) (32x64) pixels with Synchronous FE architecture
- 2) (32x64) pixels with Asynchronous FE architecture
- 3) replicated Bias Cells with current mirrors
- 4) 10-bit biasing DACs
- 5) Bandgap voltage reference
- 6) 12-bit monitoring ADC
- 7) readout/configuration digital block and High-speed Serializer at the chip periphery
- 8) SLVS transmitters/receivers and I/O cells

submitted: 5/7/2016
Arrived: 26/9/2016






Building Blocks made by CHIPIX65: summary table



| BLOCK | DIMENSIONS | POWER | Performance / Main-Characteristics |
|------------|--------------------------|-------------|---|
| Band-Gap | $100 \times 270 \mu m^2$ | $65 \mu W$ | based on MOS only |
| 10-bit DAC | $140 \times 240 \mu m^2$ | $150 \mu W$ | DNL < 0.4 LSB, INL < 1LSB |
| 12-bit ADC | $308 \times 535 \mu m^2$ | | 1V, 16-ch, 5kSample/s |
| SER | $100 \times 56 \mu m^2$ | 2.3 mW | 2 Gbps |
| DES | $180 \times 56 \mu m^2$ | 17.8 mW | 2 Gbps |
| sLVDS-TX | $160 \times 160 \mu m^2$ | 2 mW | 1.2 Gbps |
| sLVDS-RX | $70 \times 80 \mu m^2$ | 0.2 mW | 1.2 Gbps |
| Dice S-RAM | $1.8 \times 3.3 \mu m^2$ | | SEE recover in 2.5ns |
| VFE-syn | $25 \times 40 \mu m^2$ | $5 \mu W$ | ENC < 100 fF; Thr-trimm: offset-comp ToT($30ke^-$) = 270ns, ≤ 7 -bit with local oscill |
| VFE-asyn | $25 \times 50 \mu m^2$ | $5 \mu W$ | ENC < 100 fF; Thr-trimm: 4-bit DAC comp ToT($30 ke^-$) = 400ns ≤ 5 -bit ext-clock 80MHz |



CHIPIX65 periphery

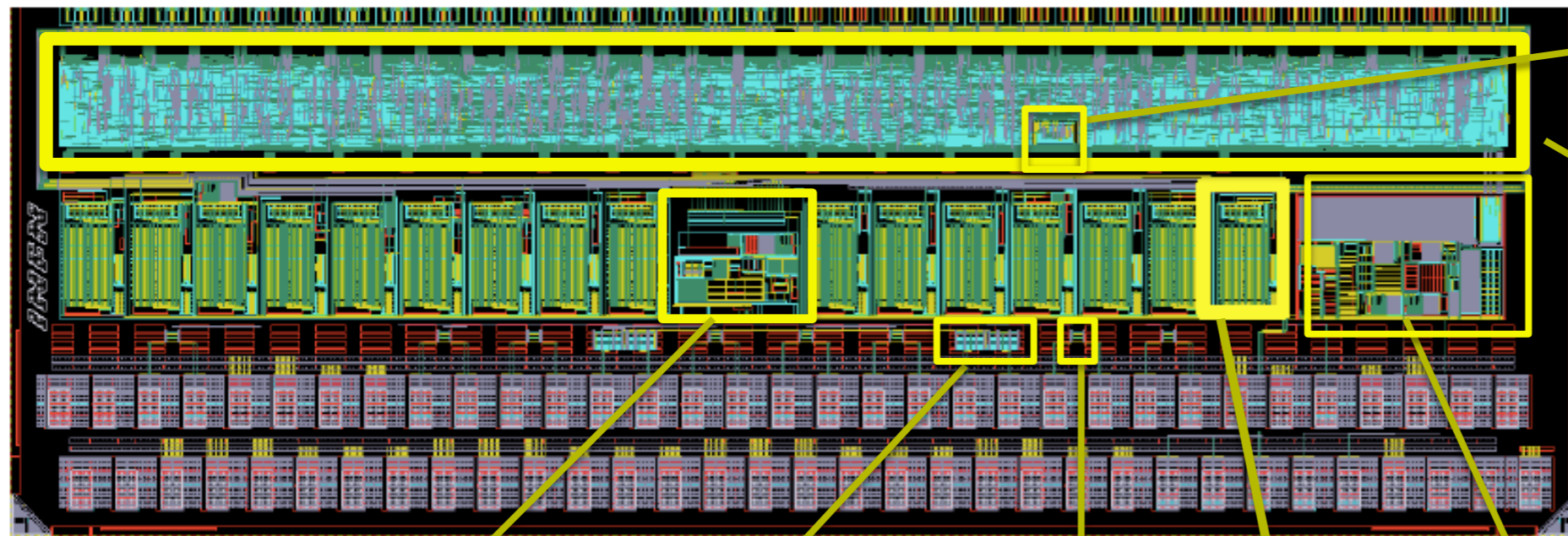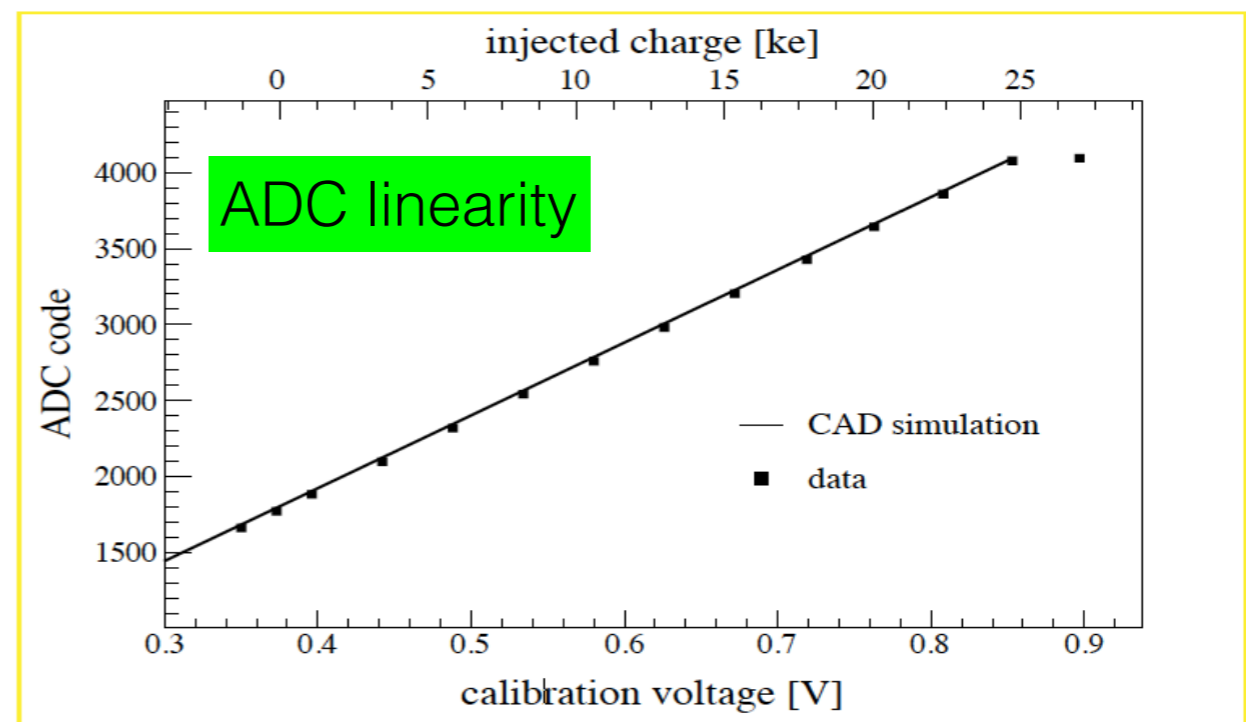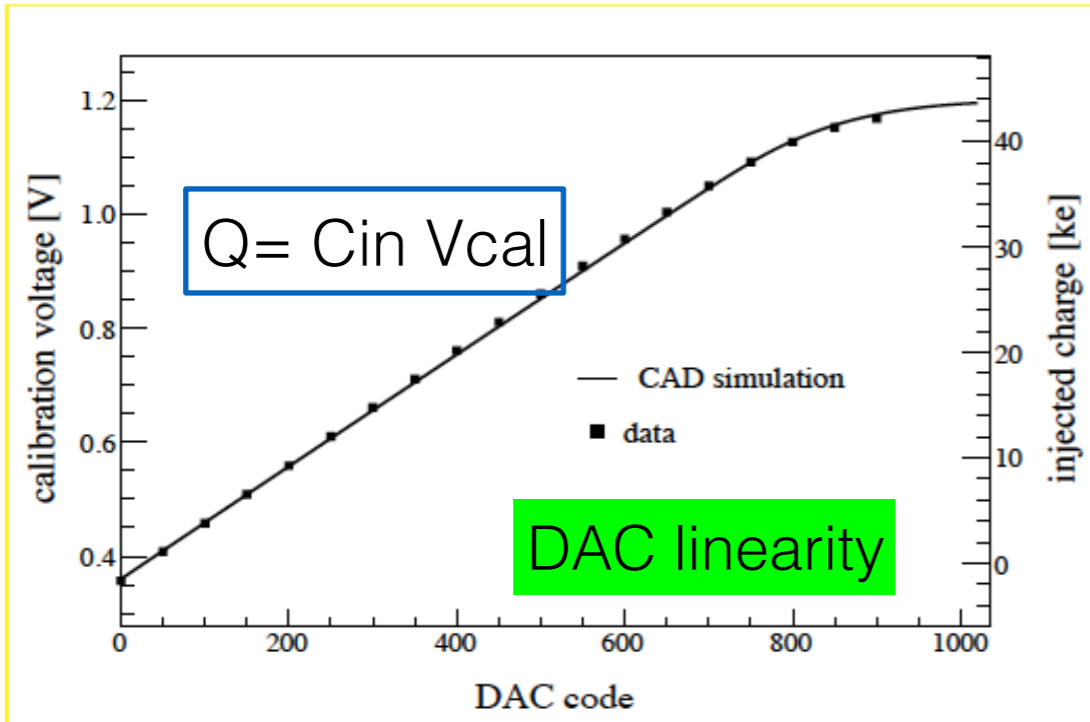

Serialiser

Digital-Chip-bottom

EndOfColumn FIFOs, CentralFIFO, 8b10b Encoder, Auto-zero, SPI-protocol

BandGap

sLVS-Tx

sLVS-Rx


DAC

(16 in total)

ADC



 CHIPIX65 Regional architecture extended to (4x4) pixels



Pixel region provides :

- pixel configuration register
- ToT counting
- Local storage waiting trigger
- Trigger matching (zero-suppr)
- Readout to end-of-column

Analog VFE in four (2x2) islands

Digital architecture logic distributed in the (4x4) Region

AREA for digital is tight: idea is to make real use of sharing digital resources among more pixel


- FEI4 architecture NOT convenient for regions larger than (2x2)
- NEW architecture developed by CHIPIX65 based on (4x4)



Some comparison...




PSI46 (150um x 100um)

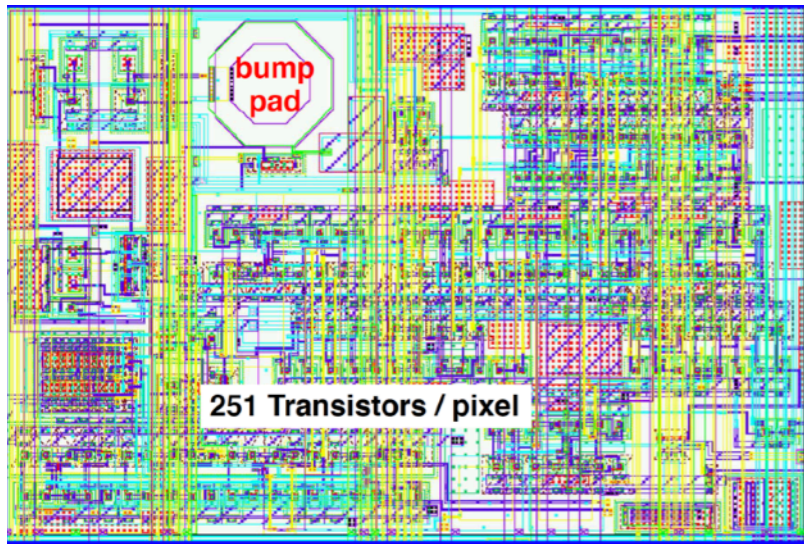


- 250nm CMOS tech
- **251** transistors/pix

YES !

 65nm technology allows to design a smaller pixel capable to sustain extreme particle fluxes and long latencies




FEI4 (50um x 250um)

 

- 130nm CMOS techn
- ~**2500** transistors/pix
- ~0,5 trans/um²

CHIPIX65 (50um x 50um)


 


- 65nm CMOS tech
- ~**2500** transistors/pix
- ~2 trans/um²


50% of area to digital



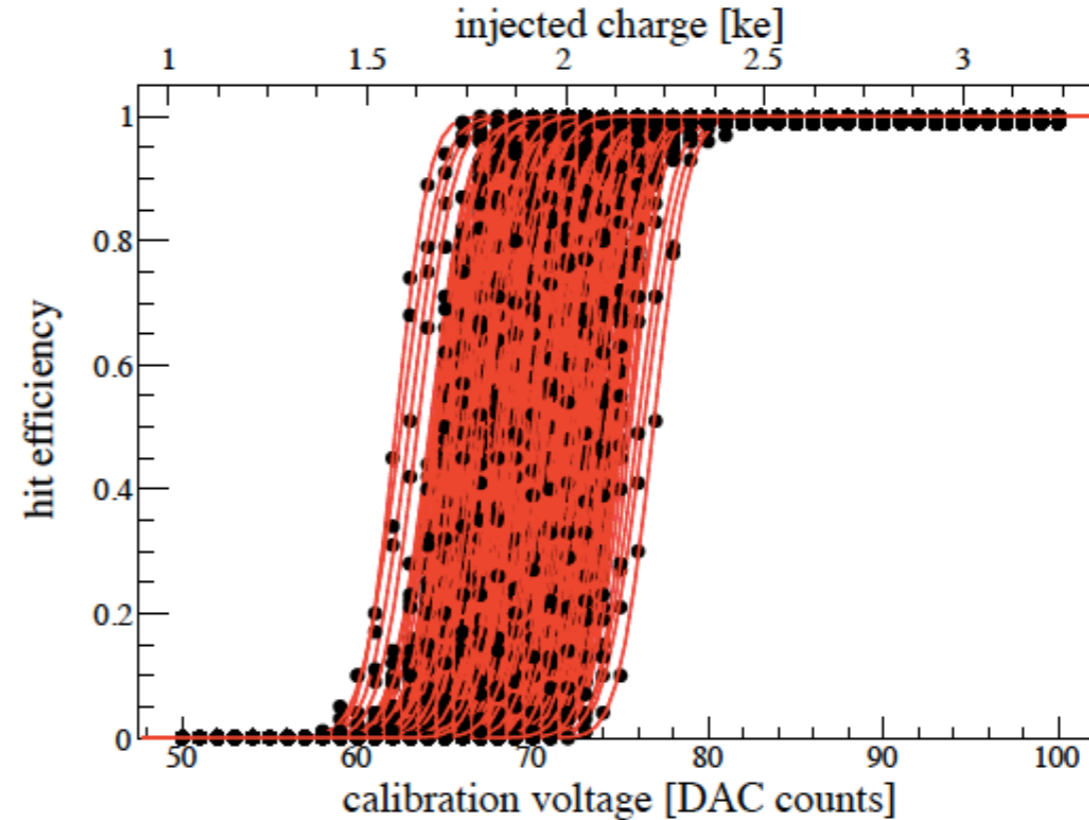 Measurement of Threshold and noise S-Curve: Charge scan




- all pixels tested and fully working
- autozeroing performed each $200 \mu s$
- effective **NOISE** and **THRESHOLD** values determined by means of S-curves
- measurements performed with **CHARGE SCANS** and **FIXED THRESHOLD**
- **HIT EFFICIENCY** recorded for 100 charge-injection pulses
- measured points fitted using an error function (sigmoid)
- noise and threshold values extracted from means and variances distributions

 

Synchronous VFE (Torino)





Low Threshold

 

- Low threshold possible, **250-300e⁻** for bare chip
- The **auto-zeroing** is working well



- The measurements have been repeated after a TID = 600 Mrad has been reached with X-ray irradiation at -20°C with the chip in working conditions. **The irradiated chip is still fully operational**

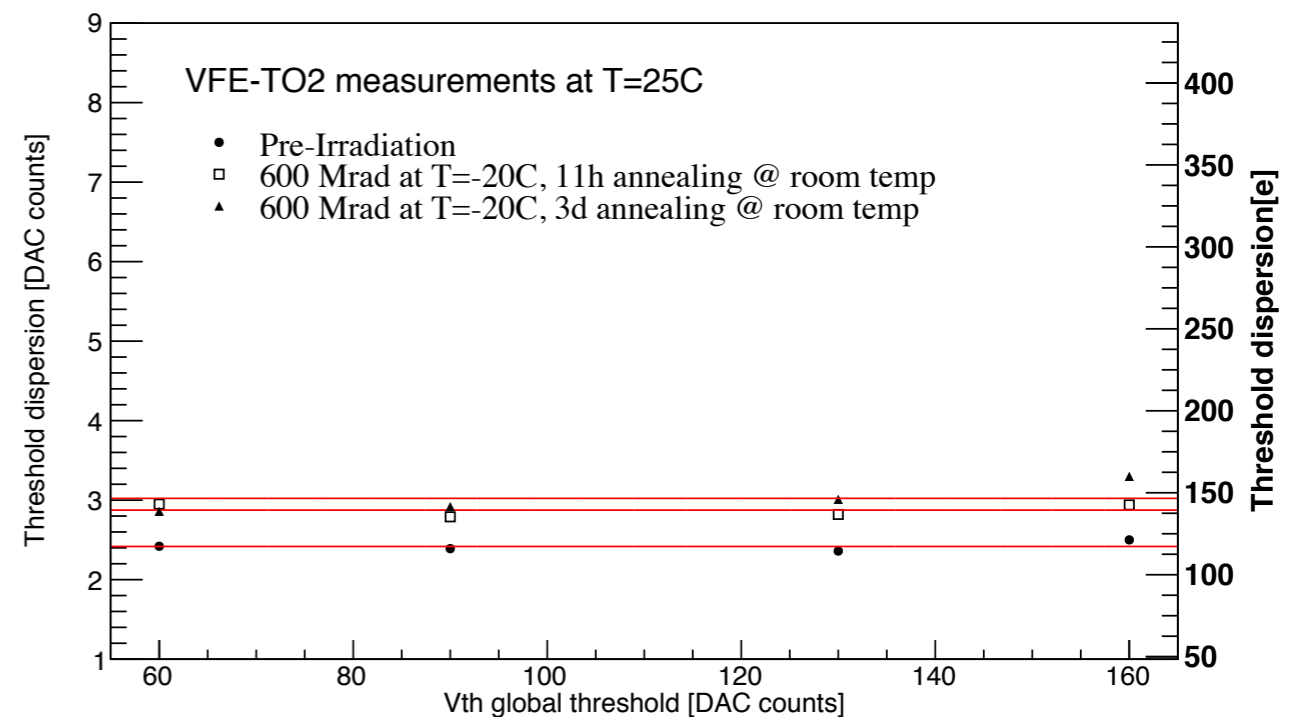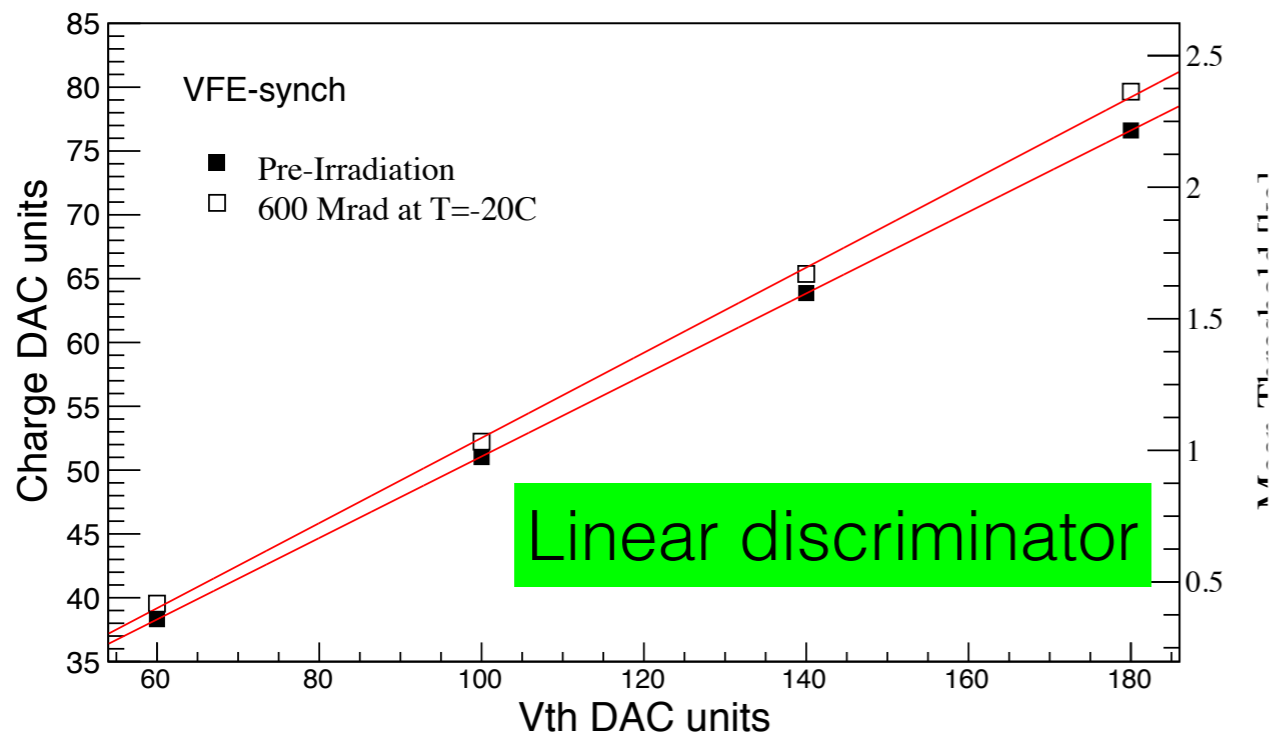- For thresholds below 1 ke⁻, which is the region of interest, the increase of the dispersion with radiation is below 10%






ENC

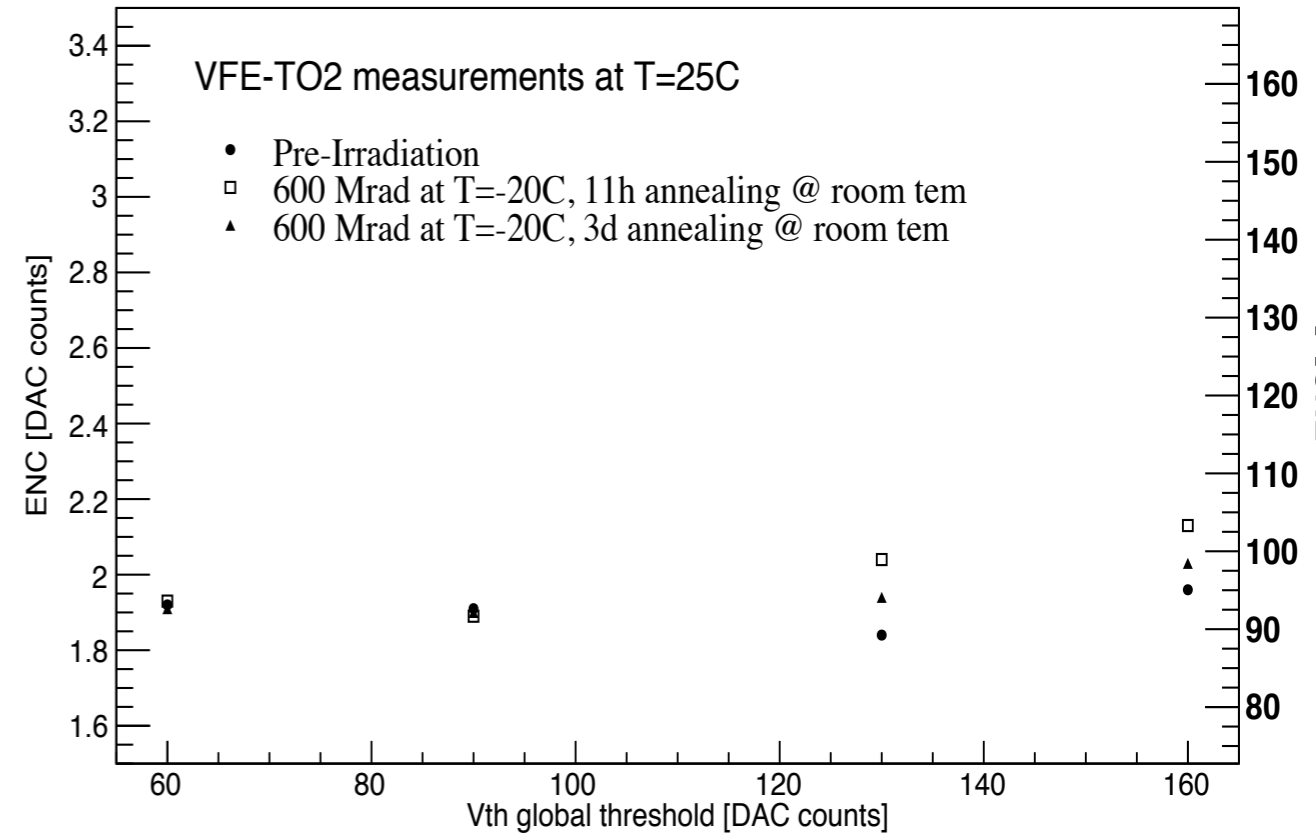 


- ENC $\sim 90e^-$: very low noise performance despite digital activities
- Almost no increase of noise after irradiation. Value for Vth=60-90 are relevant



Fast ToT measurements

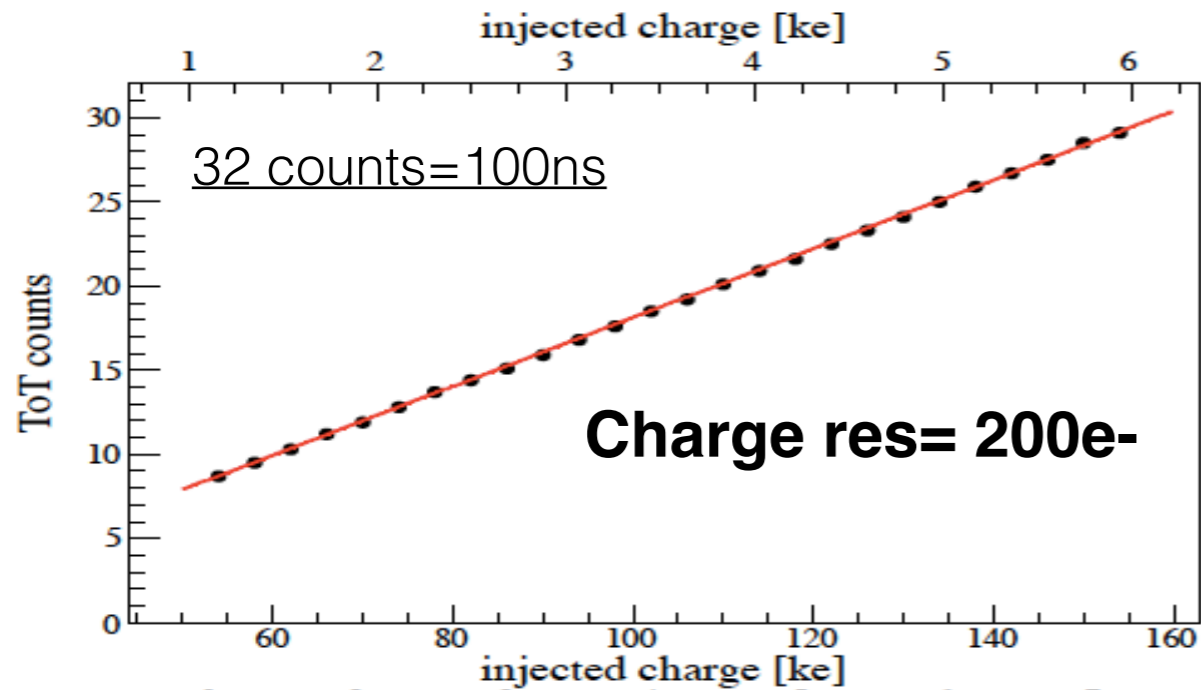

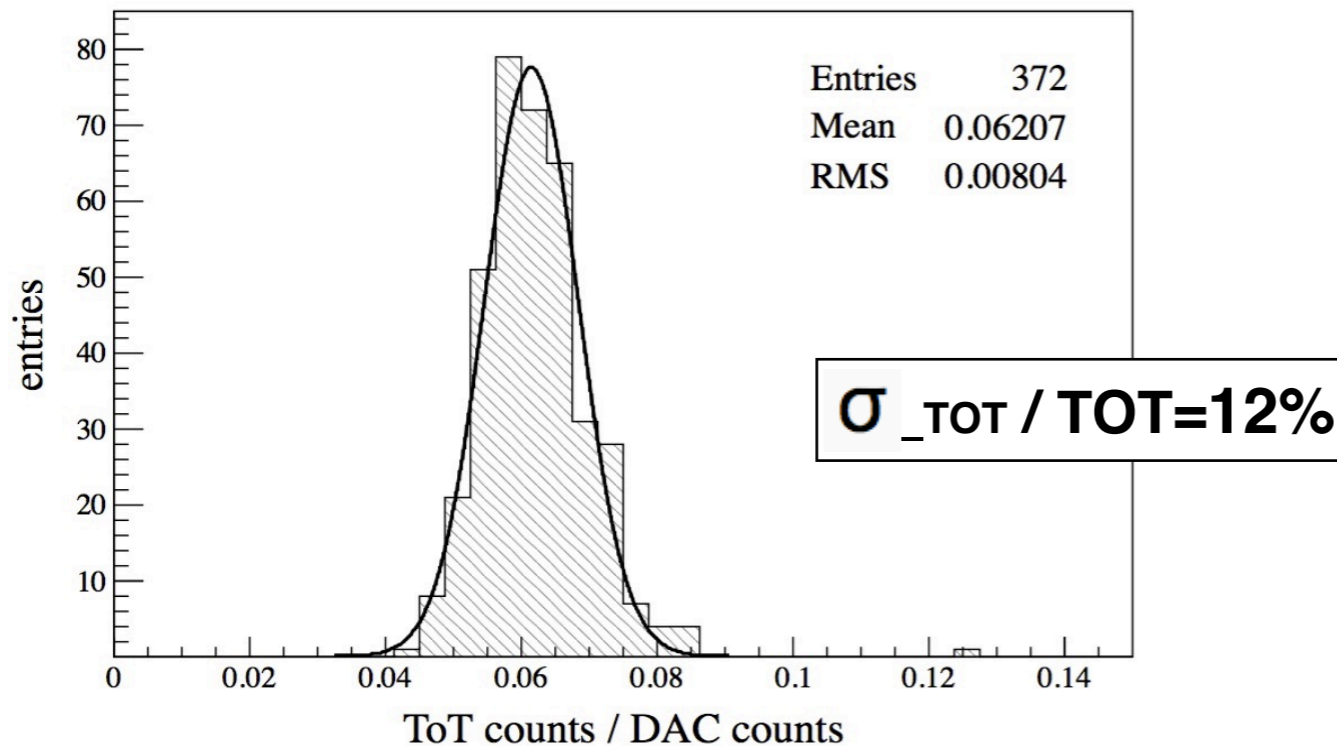- **Good ToT Linearity - 5 bit ToT**
- Measurement with **320MHz Fast ToT**
- Slope dispersion of about 12% expected from mismatch in I-Feed
- Decrease of <20% in frequency after 600 Mrad irradiation







Asynchronous VFE (Pv/Bergamo)




Threshold & Noise

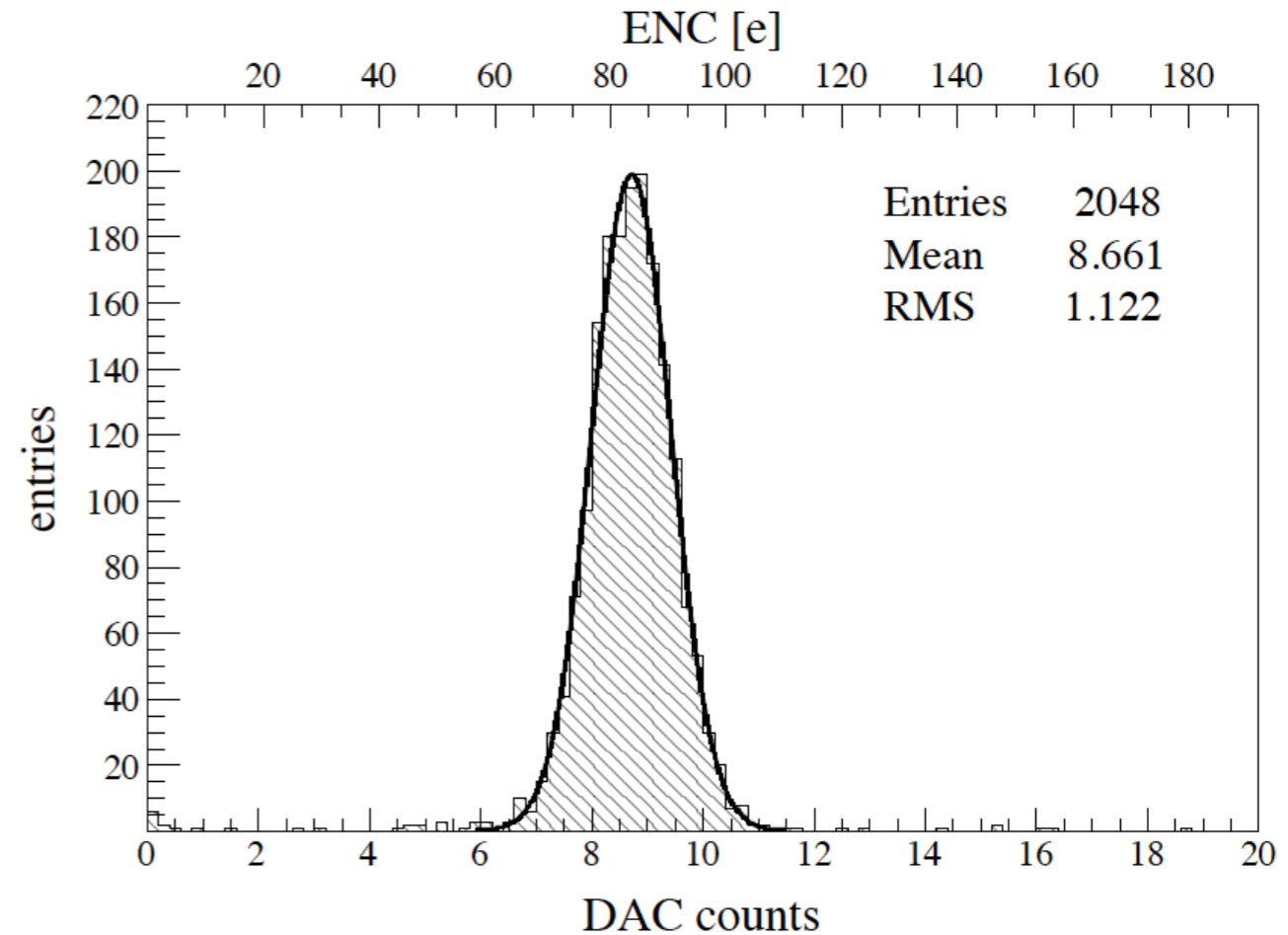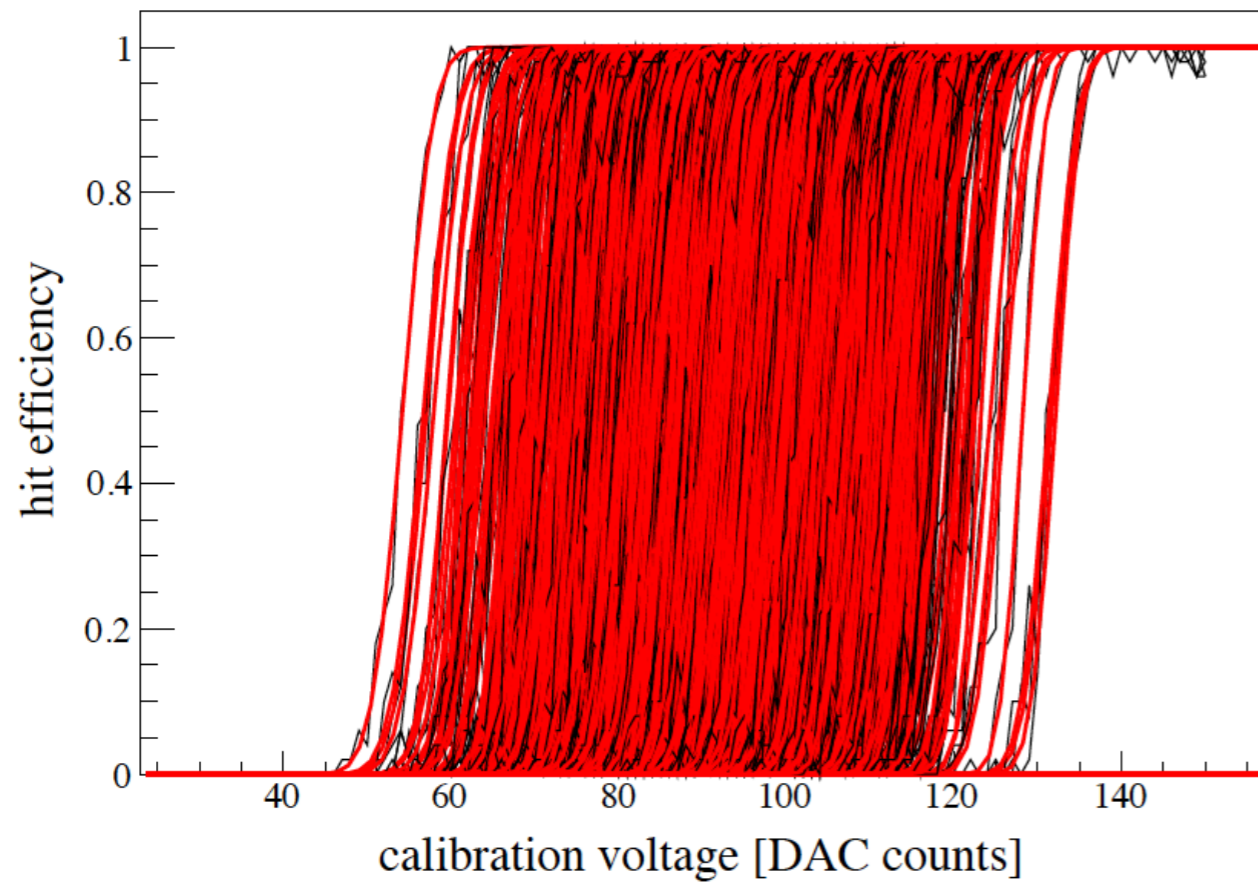

- About 450e- threshold dispersion before trimming
- Noise compatible with simulations $\sim 90e^-$





Threshold trimming

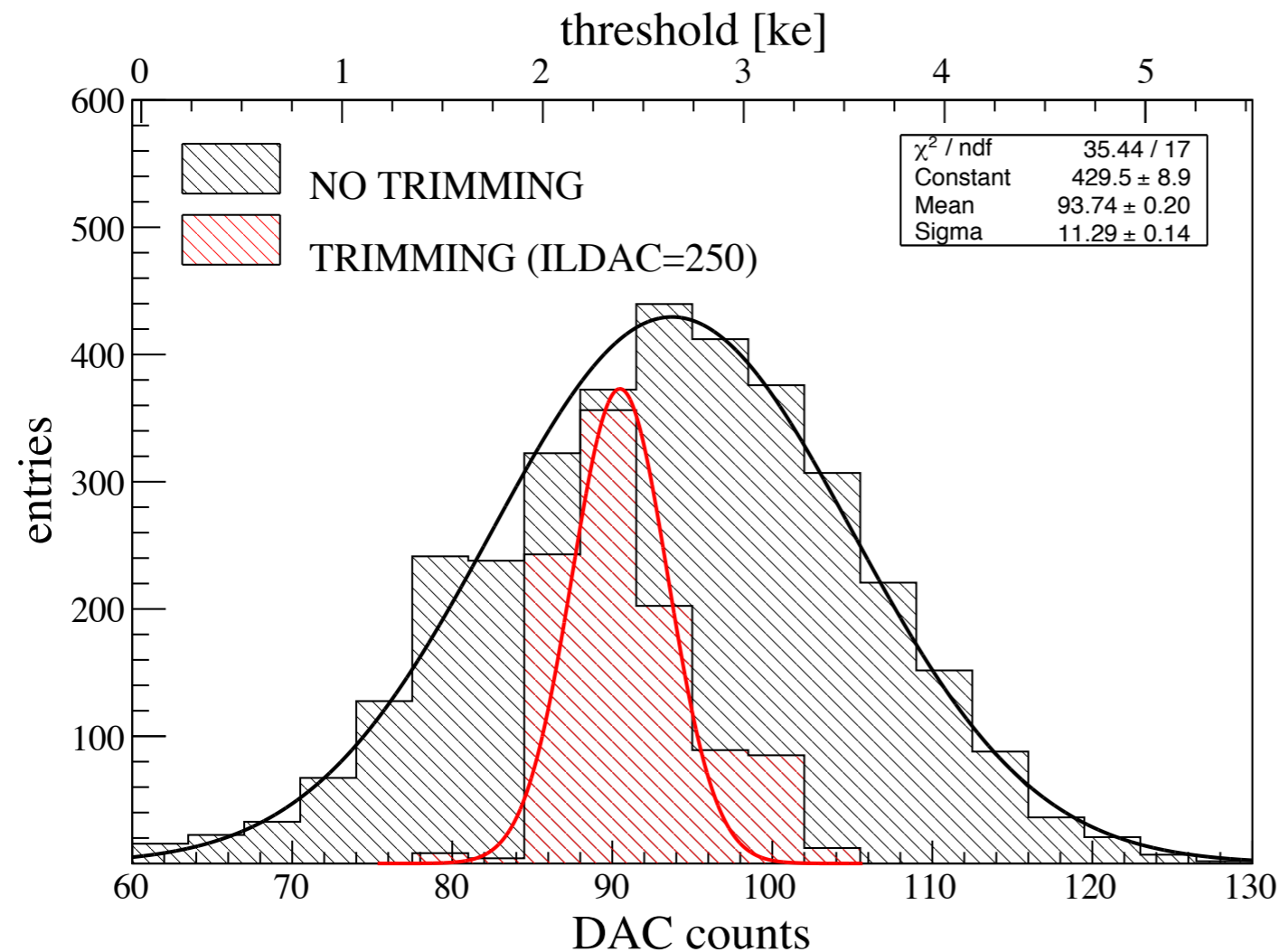

- The local DAC for trimming works fine,
- Here preliminary results: trimming tuning algorithm not optimised



Threshold

  

- Linear behaviour of Discriminator



Conclusions



- The CHIPIX65_demonstrator is a very sensible intermediate step before moving to the big prototype of RD53A. Several solutions studied in CHIPIX65 have been introduced into RD53A.
- CHIPIX65-FE0 is respecting the requirements imposed by Phase 2 HL_LHC pixel detectors : high efficiency for high particle flux, low-noise, high granularity
- The chip works fine, nothing found not to function well.
- CHIPIX65-FE0 resisted very well an irradiation test up to 600 Mrad (made at cold, -20C). Also digital logic, readout works perfectly. This is very promising !
- Excellent performance of Analog-VFE obtained.
- Next step will be to do bump-bonding with sensors (planar and 3D)






BackUp Slides




Radiation: Analog VFE

- No major worry: **two out of four analog-architectures tested under radiation** and no serious problem seen

Peaking time vs radiation

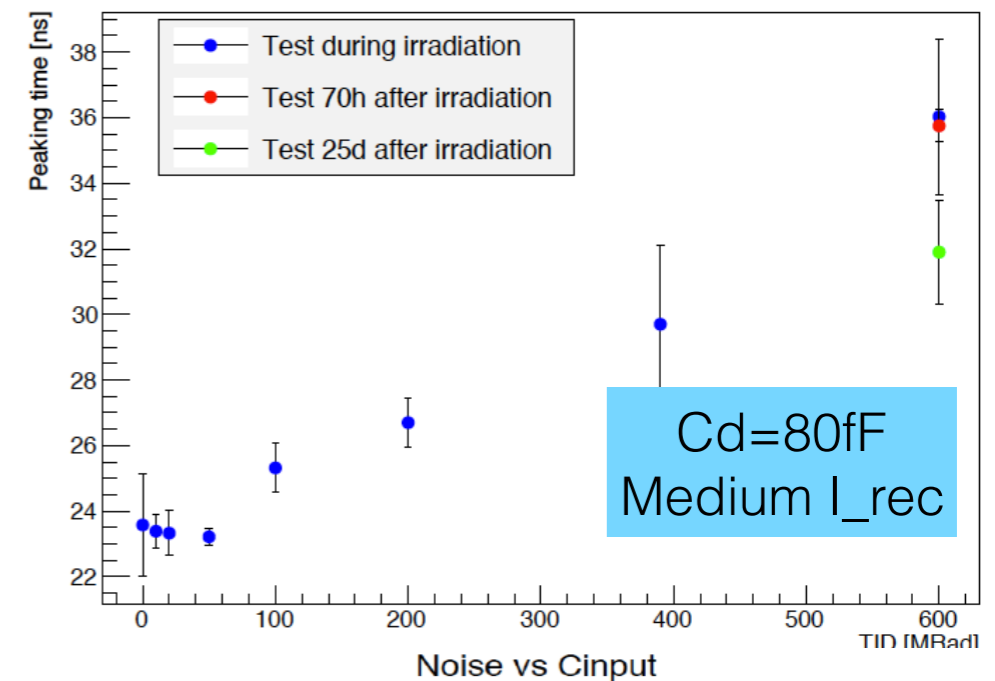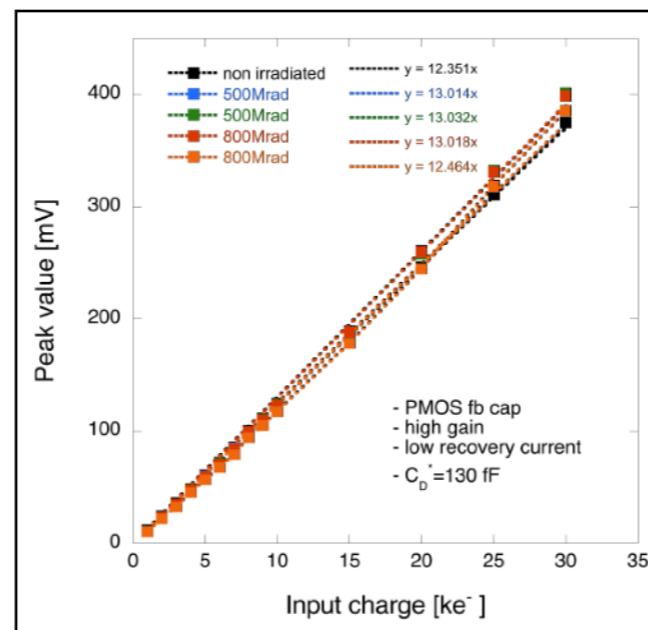 

 - Gain decrease of $\sim 5\%$
- Slower signal but looks ok
- 10-20% increase of noise






Asynch Analog FE



AIDA 2020

Pavia/Bg

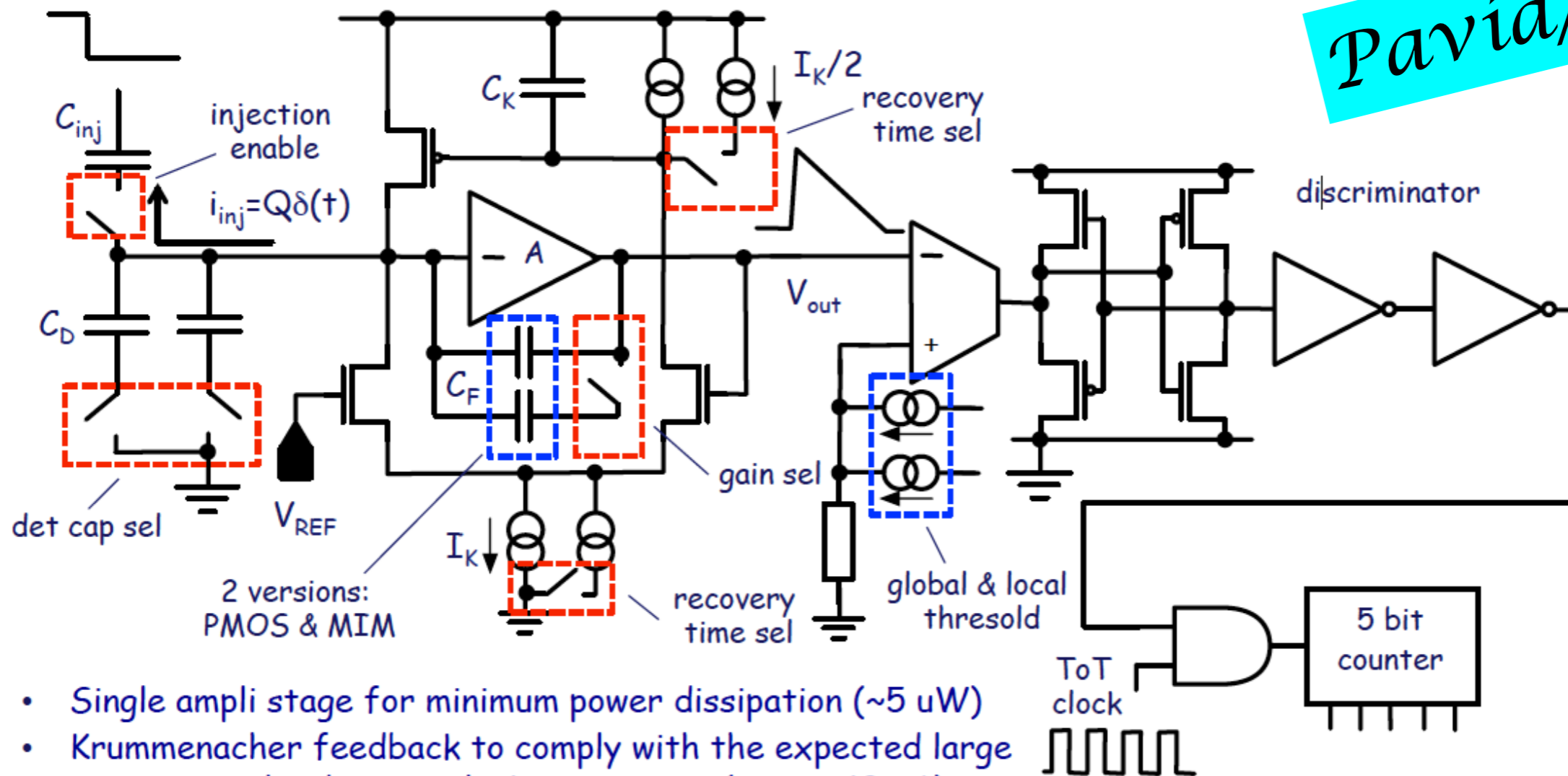


- Single ampli stage for minimum power dissipation (~5 uW)
- Krummenacher feedback to comply with the expected large increase in the detector leakage current (up to ~10 nA)
- 30000 electron maximum input charge expected, ~450 mV preampli output dynamic range
- Selectable gain, recovery current and detector emulating capacitance
- 40 MHz clock, 5 bit dual edge counter, 400 ns maximum ToT


TESTED after IRRADIATION



Synchronous Analog FE

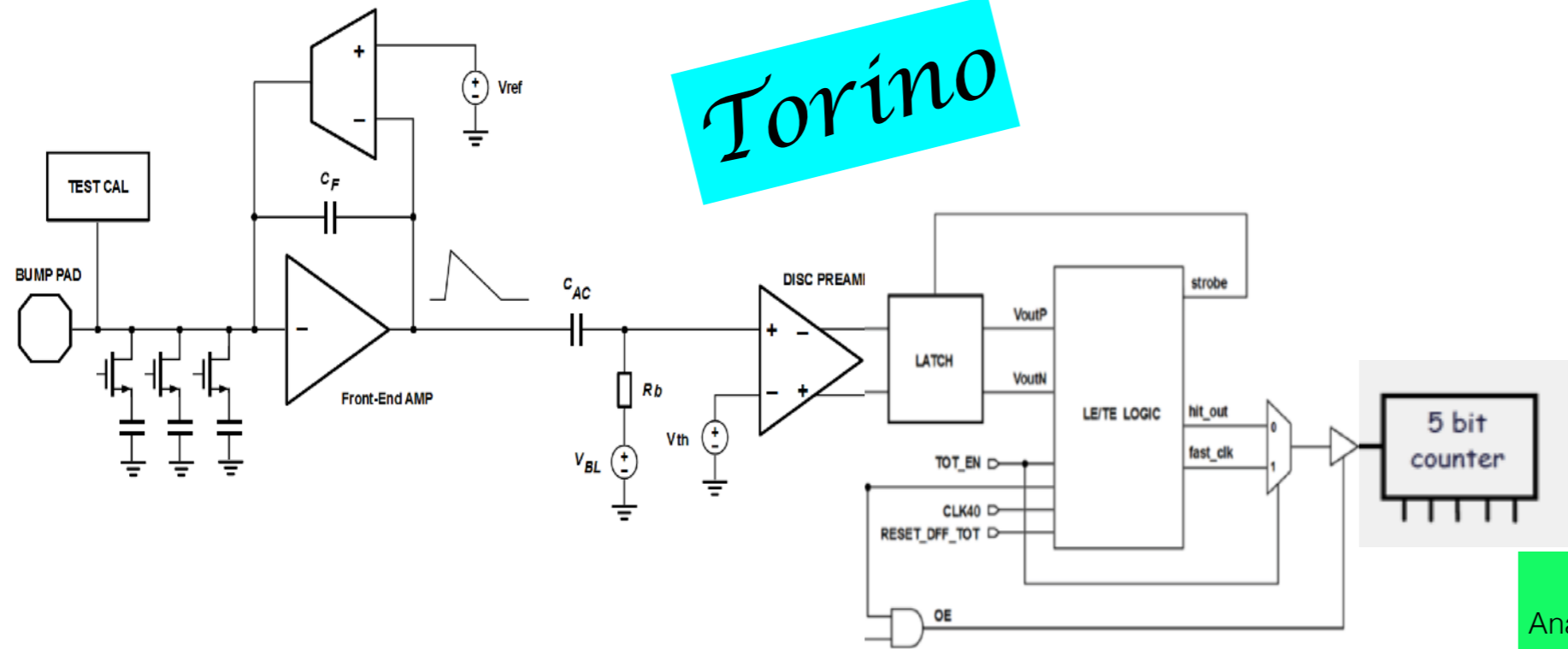

Torino

 

8x8 pixel matrix submitted and tested
Analog readout of CSA and Discriminator (via buffers)

- **PREAMPLIFIER**
 - One stage CSA with Krummenacher feedback
- **Synchronous DISCRIMINATOR**
 - (AC coupled to CSA)
 - off-set compensated diff.amplif. + latch;
 - **FAST Time-over-Threshold**
 - Local oscillator strobing Latch (to 800MHz)
- **Calibration circuit**
 - digital signal + DC calibration level

TESTED after IRRADIATION

Performance SUMMARY


- Compact: ~25um x 40 um
- Low power: < 5.5 uW (with ToT logic)
- Low noise: ENC=100e @C_{det}=100 fF
- Leakage compensation: up to 50nA/pixel
- Fast Charge measurement:
 - 10 ke in : 90 / 180 / 360 ns (Fast/Medium/Low recovery current)
 - up to 7-8bit (125-250e /ADC) - no ext clock
- NO Threshold-Trimming:
 - autozeroing made by hardware





Synch AFE



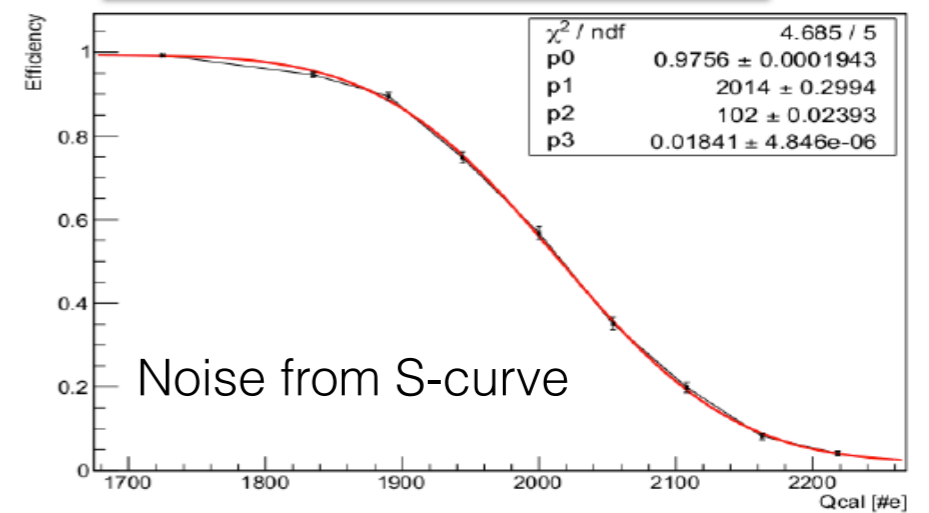- CSA: Triangular shape, discharge time (=dead-time) can be set. Krummenaker can stand up to 50nA.
 - 40nA = 90ns for 10ke => <0.3% ineff (FAST) ; ENC=110e-
 - 10nA = 360ns for 10ke => ~1% ineff (SLOW)




Analog signal (oscilloscope)

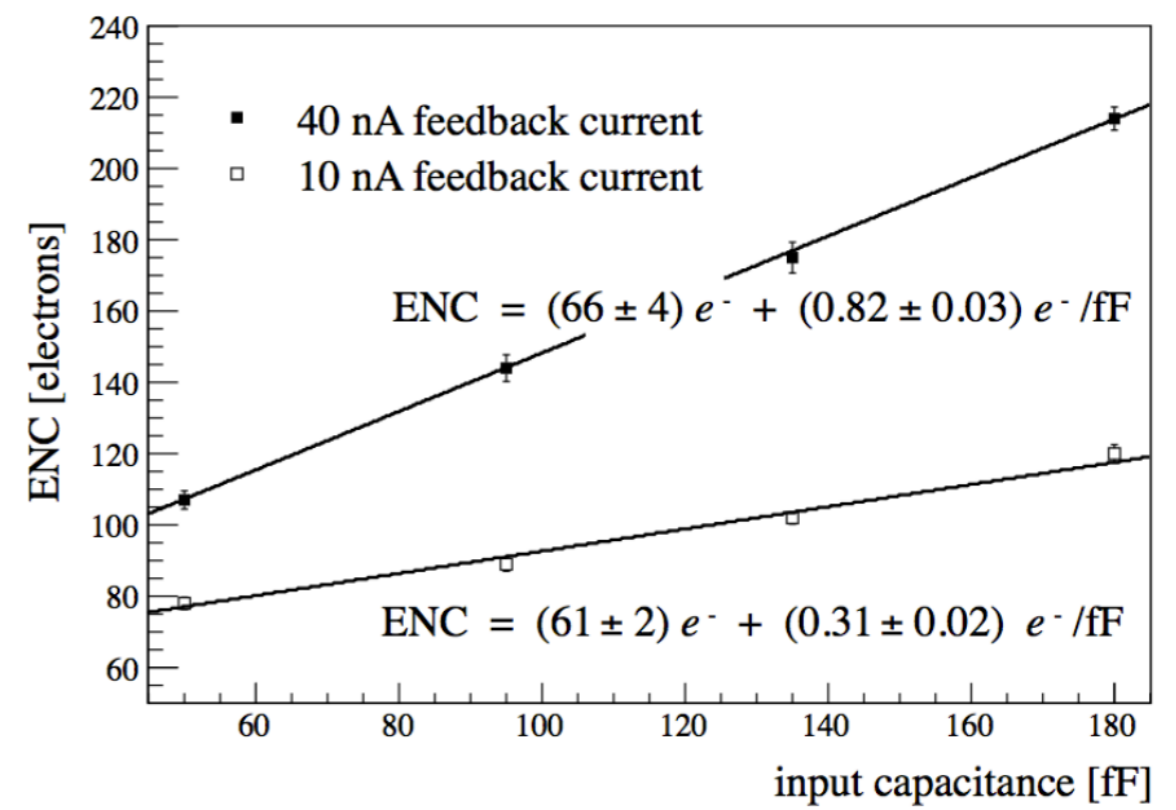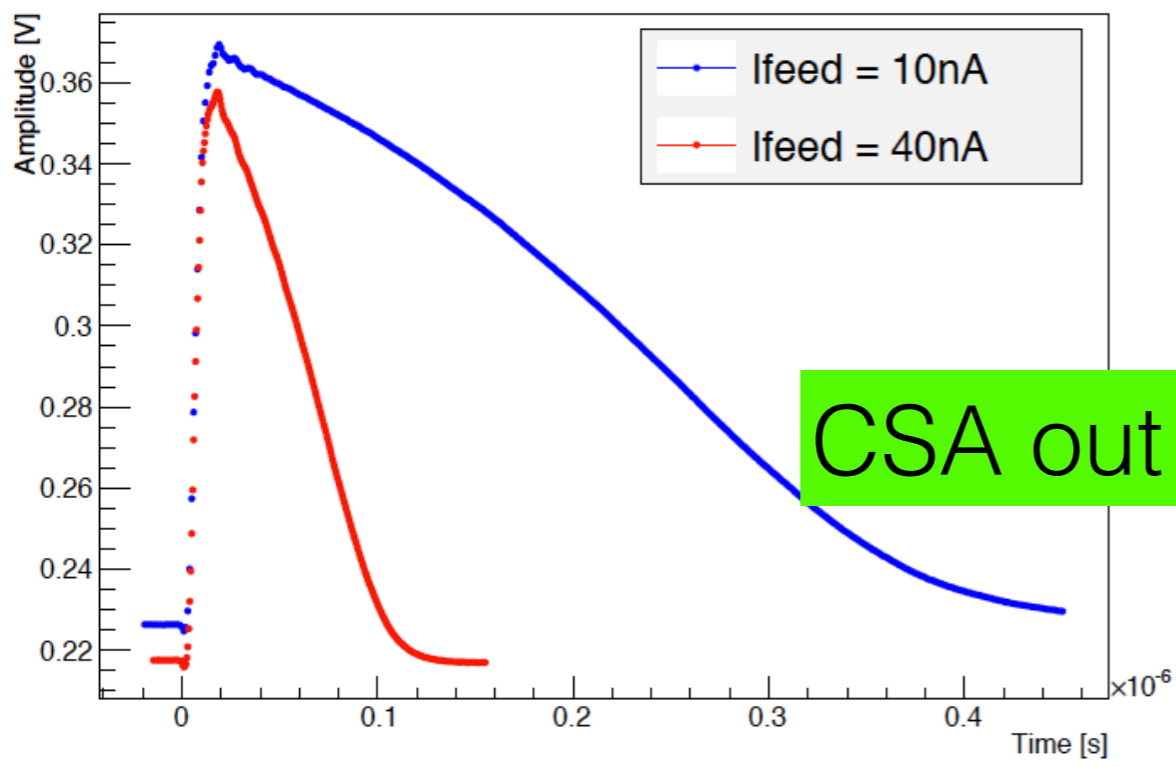





Synch AFE: Threshold variations

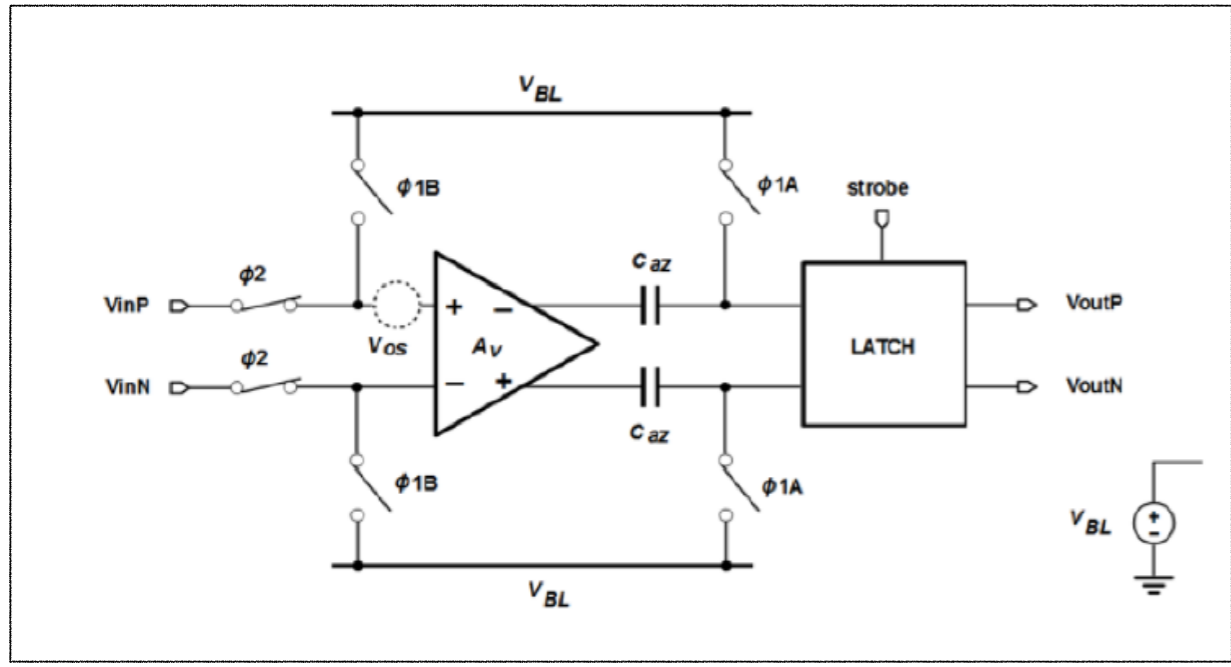

 - Comparator is AC coupled to CSA
- Differential amplifier is offset compensated every 100usec (still true after irradiation)
- **NO NEED for TRIMMING !**
- Latch dynamic offset dominates but is low: 70e-



offset compensation

 



No change after 600 MRad and 25d annealing

(a) Uncompensated

(c) Compensated - Second prototype




Synch AFE: Fast Oscillator

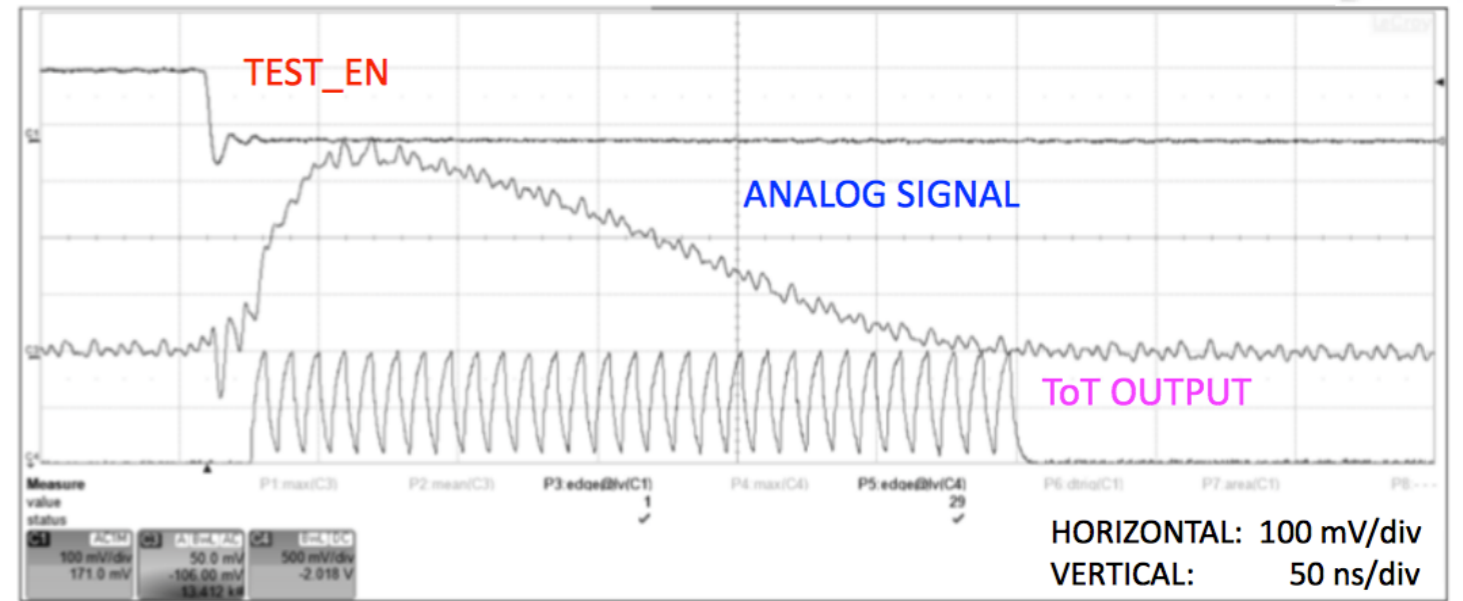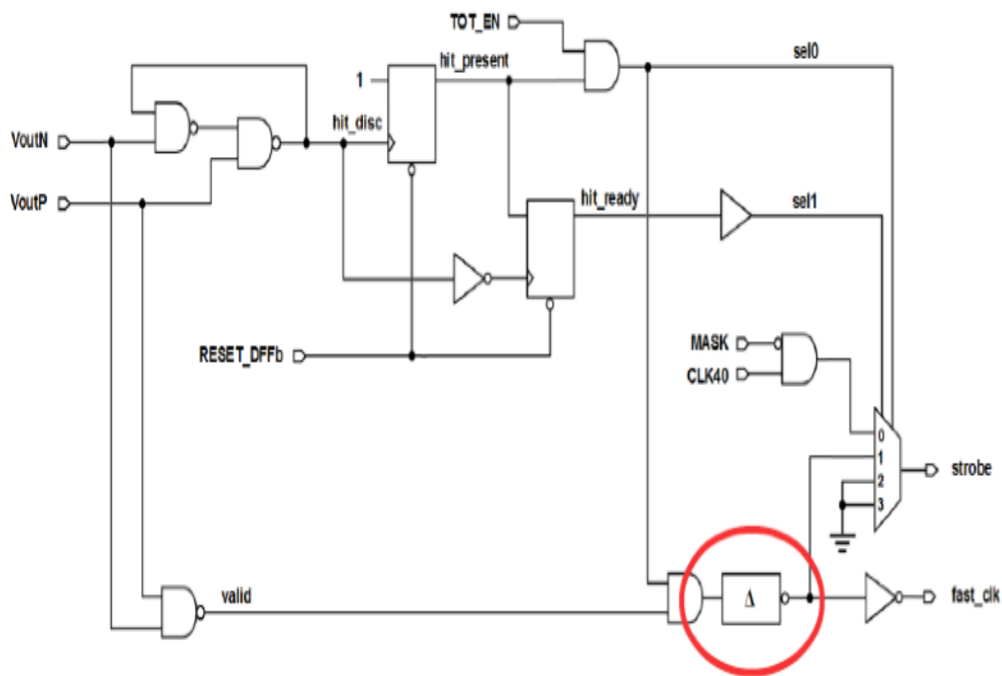

- Local oscillator set to 140 MHz
- Slow down with TID
- Partial recovery with time (annealing)
- Freq. rms ~ 1,8%
- Reminder: Freq. can be set to higher values

ToT frequency vs radiation

 



Synch VFE

