

Electronics, Trigger and Data Acquisition part 1

Summer Student Programme 2017, CERN

July 5, 2017

Roberto Ferrari
Istituto Nazionale di Fisica Nucleare



roberto.ferrari@pv.infn.it

Introduction

- Lectures will be concerned with Data Acquisition (DAQ) in High-Energy Physics ...
- Data acquisition is an **alchemy** of electronics, computer science, networking, physics
 - ..., resources and manpower matter as well, ...
- Topics are pretty much correlated → you will realise this in the lecture non-linearity

Credits: material and ideas come largely from my predecessor (Wainer Vandelli) and from the lectures of ISOTDAQ schools (<http://isotdaq.web.cern.ch/isotdaq/isotdaq/Home.html>)

General Overview

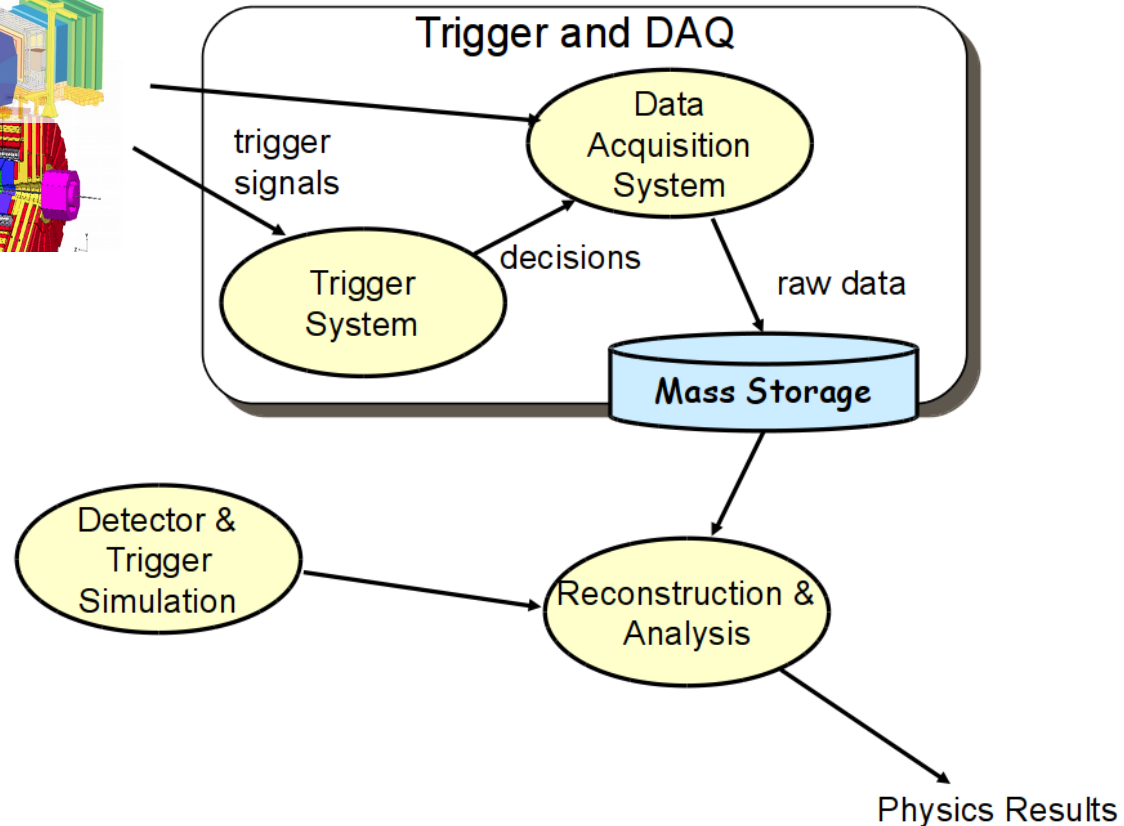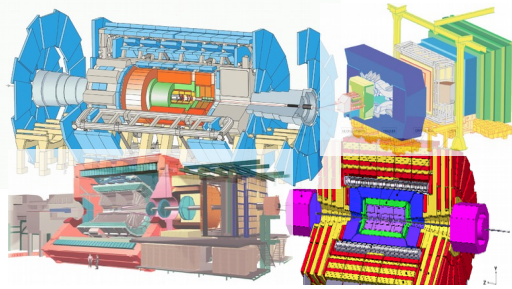

- main role of Electronics, Trigger & DAQ is to process signals generated in “a detector”, likely storing all useful information in some safe place

Signals ?

- Sometimes, somewhere in our detector, something (“one event”) happens, i.e. in some short time several particles interact within it.
- In High-Energy Physics, even a single event is composed by sequences of many different probabilistic (quantum-mechanics) processes → fluctuations are built-in
- At the end, “electrical” signals arrive at detector output terminals.

Different signals:

- a) have different characteristics (size, arrival time, duration, ...)
- b) carry different, (likely) independent, information
- c) need quite some **electronics** in order to become “**profitable**”


Electronics

[Horowitz & Hill, The Art of Electronics]

Role ?


- Sense, transform and collect electrical signals from detector(s) – very often short current/light pulses (i.e. bunches of electrons or photons)
 - you may be interested in total charge or in signal time or in both
- Adapt signals to optimize different, **conflicting**, characteristics → balance:
 - minimum detectable signal (min. noise and max. signal-to-noise ratio)
 - maximum detectable signal (dynamic range)
 - speed (signal rate)
 - timing
 - pulse shape dependence
- Digitize and preserve information
 - allow for subsequent processing, transmission, storage using digital electronics
→ computers, networks, ...

Read-Out Chain

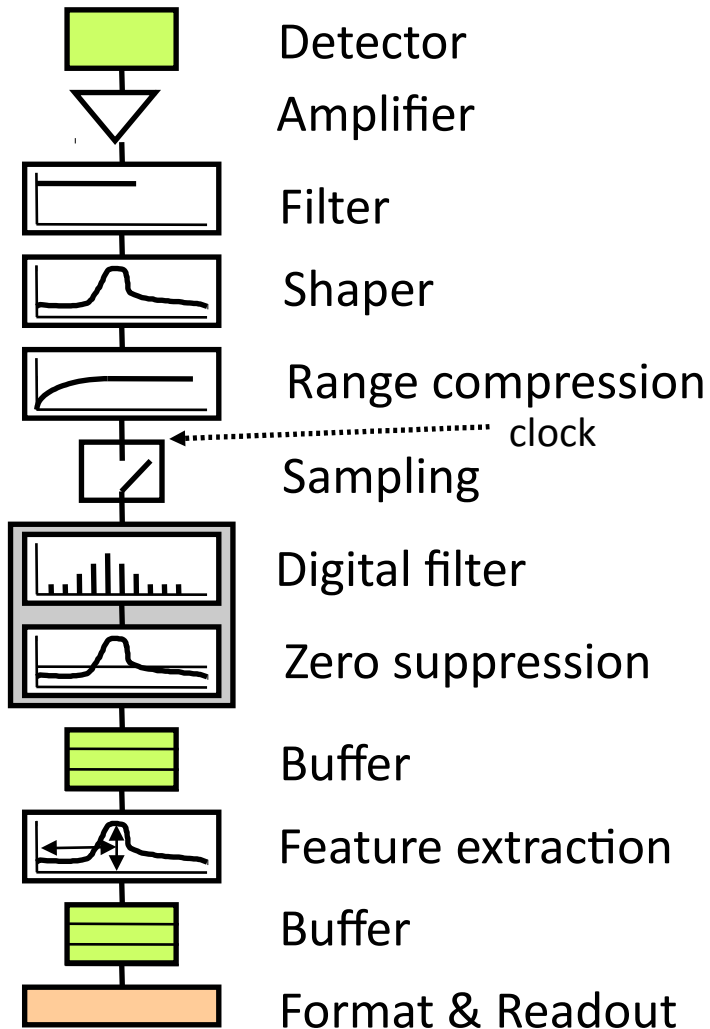

- **Front-end electronics very specialized**
 - custom-built to match detector characteristics
- **Cannot discuss all design and architecture details**
 - if you are into electronic design you already know more than me
- **Find yourself dealing or choosing commercial electronics**
 - provide you with base guidelines
- **Selected functions and principles**


Read-Out Chain

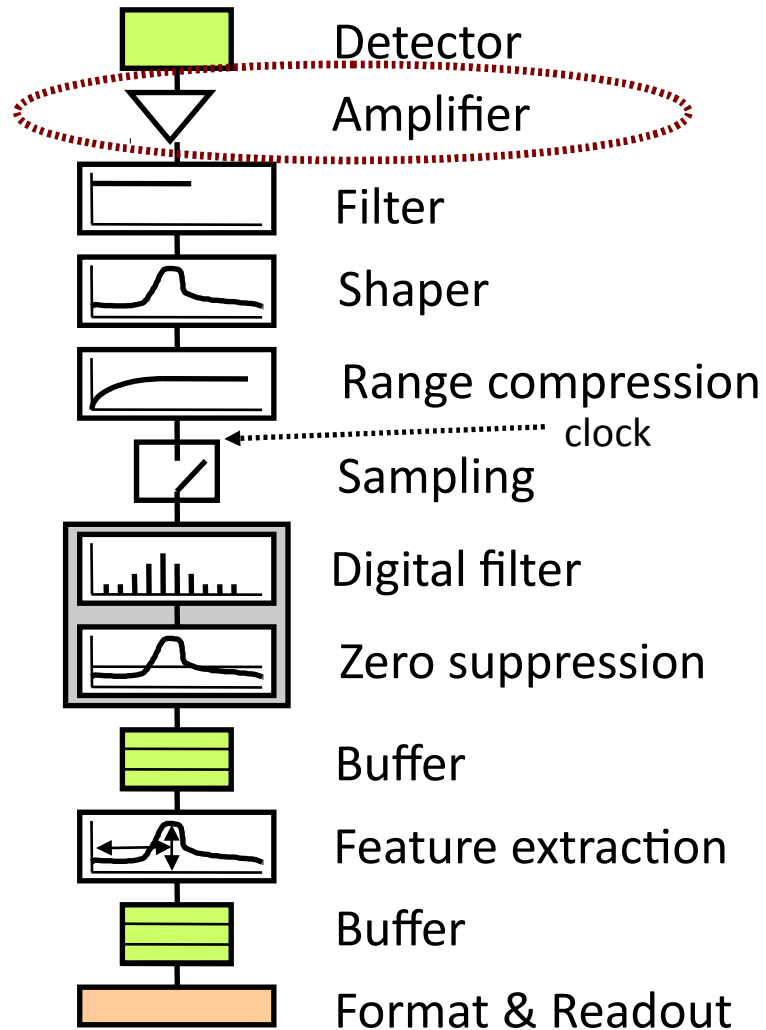

Amplifiers


Amplifier: *powered black box connected that receives an input signal with power P_0 and produces an output signal with amplified power P_1*

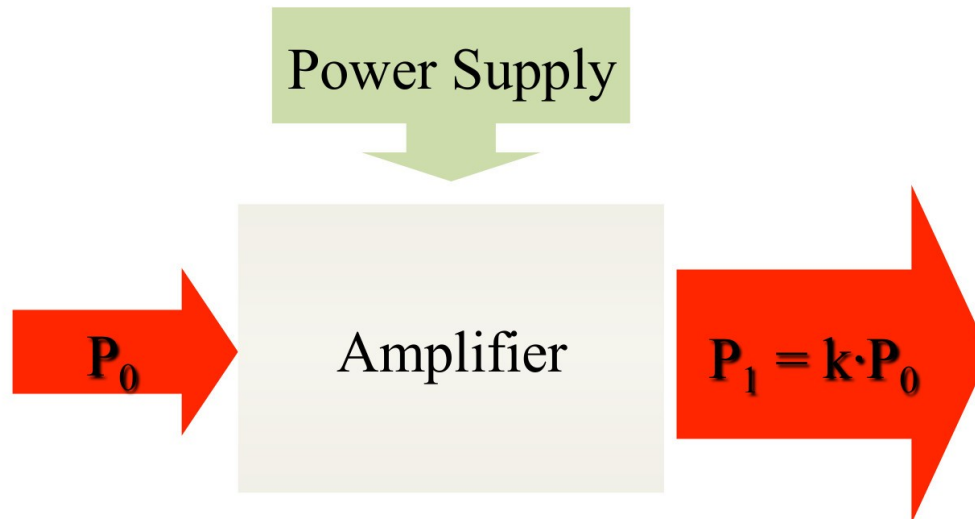Open loop gain: $k = P_1 / P_0$ (usually very large)



Negative Feedback

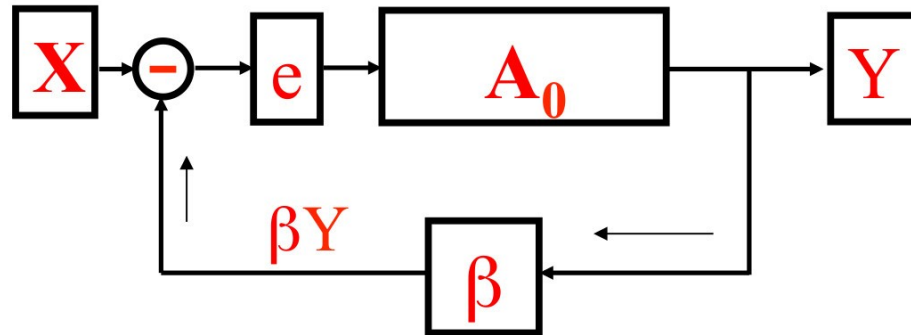Part of the output signal Y is sent back to cancel some of the input:



$$Y = A_0 e = A_0 (X - \beta Y) \rightarrow Y (1 + A_0 \beta) = A_0 X$$

$$Y = \frac{A_0}{1 + \beta A_0} X$$



If $A_0 \gg 1 \rightarrow Y = X/\beta$

\rightarrow stable and controlled gain ($1/\beta$)

Operational Amplifiers

Voltage amplifiers with:

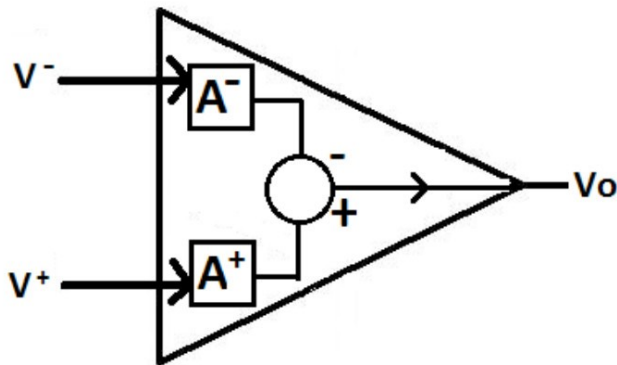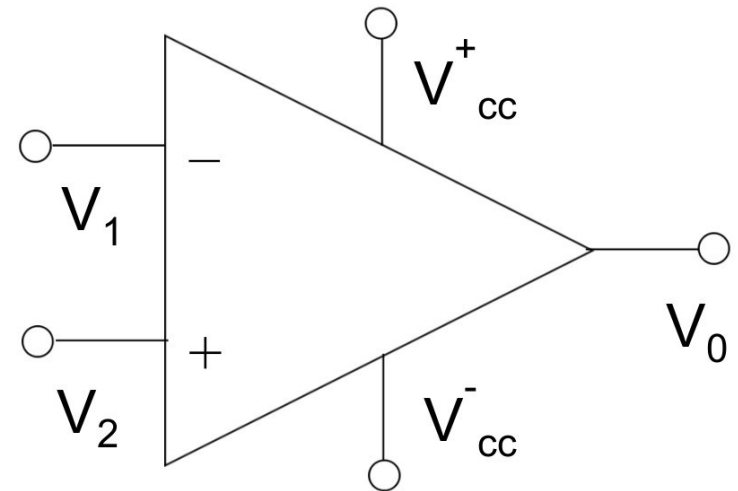- differential input
- high gain ($A^+ = A^- = \infty$)
- high input impedance ($Z_{in} = \infty$)
- low output impedance ($Z_{out} = 0$)








$$V_0 = A^+ V_2 - A^- V_1 = A^+ V^+ - A^- V^-$$



The output voltage V_0 is the sum of:

- the signal at the inverting input (-), V_1 , inverted and amplified by A^-
- the signal at the non-inverting input (+), V_2 , non-inverted and amplified by A^+


Open-loop Configuration: Comparator

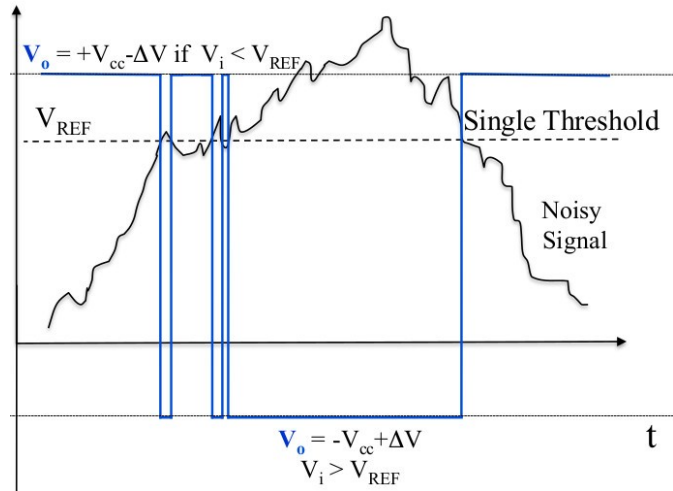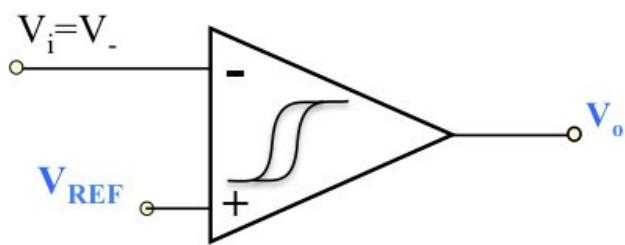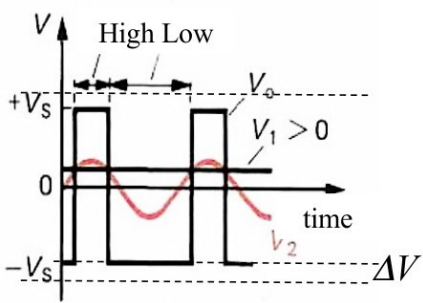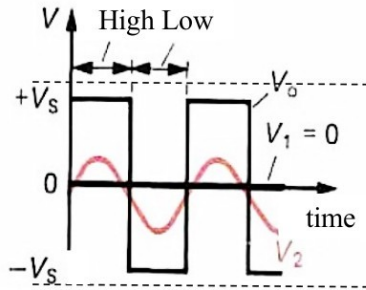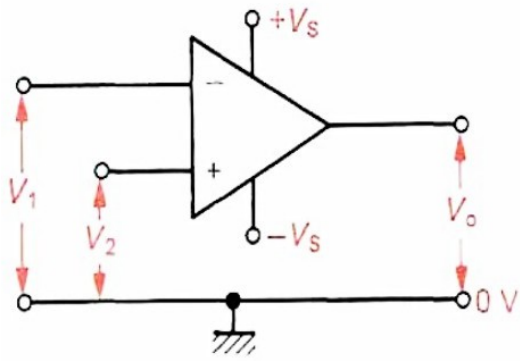

Positive Feedback → Schmitt Trigger

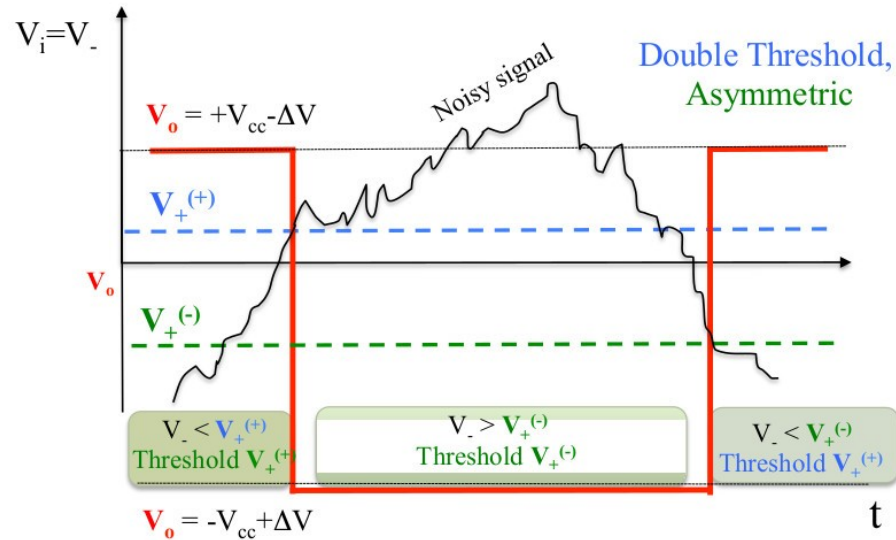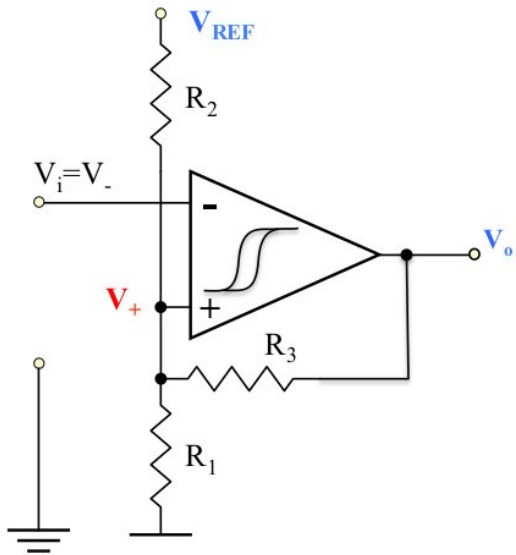

Hysteresis for the Inverting Trigger

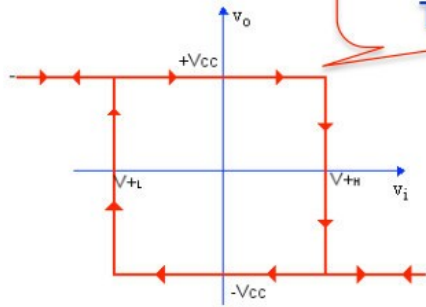

Positive feedback:


- *transition speedup*
- *hysteresis (both output and threshold depend on recent history)*

Negative Feedback ...

Golden rules:

- 1) output keeps zero voltage difference between inputs
- 2) inputs draw no current

Non-Inverting Amplifier

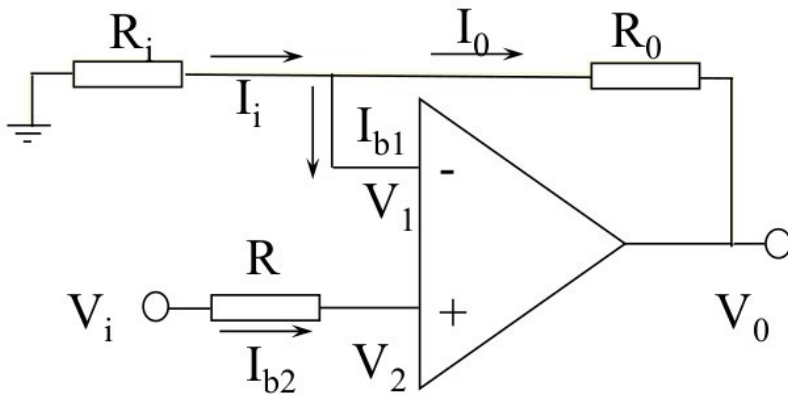

→

$$1: V_1 = V_2$$

$$2: I_{b1} = I_{b2} = 0; I_0 = I_i$$

→


$$V_1 = V_i$$

$$V_0 / (R_0 + R_i) = V_1 / R_i = V_i / R_i$$

→

$$G = V_0 / V_i = 1 + R_0 / R_i > 1$$

Inverting Amplifier

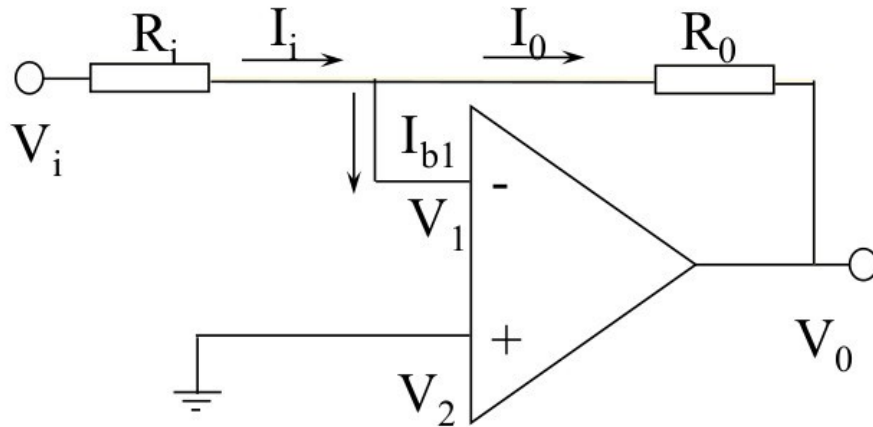

→

$$1: V_1 = V_2$$

$$2: I_{b1} = I_{b2} = 0 ; I_0 = I_i$$

→


$$V_1 = 0$$

$$V_0/R_0 = -V_i/R_i$$

→

$$G = V_0/V_i = -R_0/R_i$$

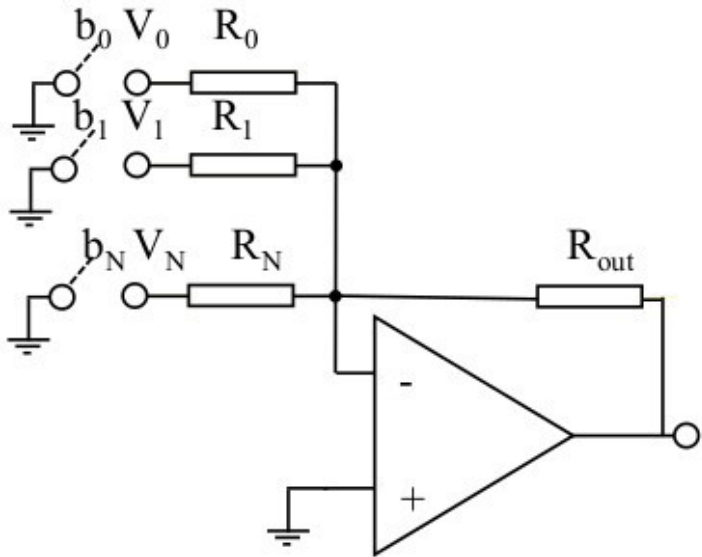Inverting Amplifier → Current Adder → DAC





If $V_N = 0$, then R_N is short-circuited (bit at 0)

Set $R_{out} = R_0$, $R_1 = 2R_0$, $R_2 = 4R_0$, etc. etc.


$$V_0 = -R_{out} \left(\frac{1}{R_N} V_N + \frac{1}{R_1} V_1 + \frac{1}{R_0} V_0 \right) \quad \dots \text{case } N=3$$

$$V_0 = -V_{REF} \sum_{i=0}^{N-1} \frac{b_i}{2^{N-i}} = -V_{REF} \left(\frac{b_2}{2} + \frac{b_1}{4} + \frac{b_0}{8} \right)$$
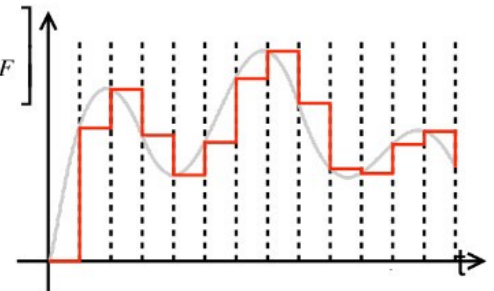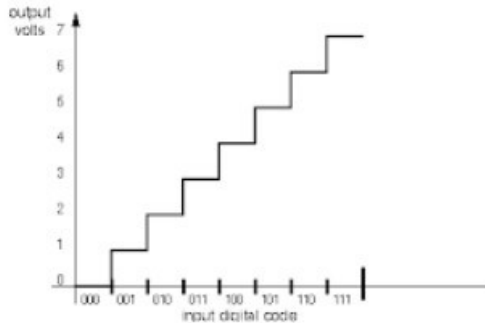
$$V_0 \in \left[0, \frac{1}{8} V_{REF}, \frac{2}{8} V_{REF}, \dots, \frac{7}{8} V_{REF} \right]$$



Differential Amplifier

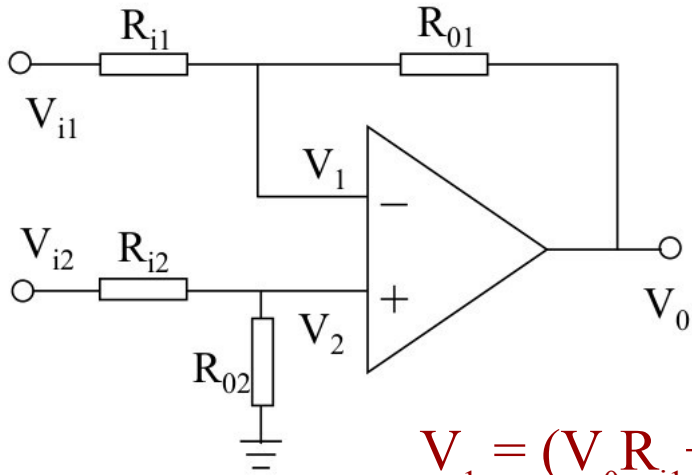

$$V_1 = (V_0 R_{i1} + V_{i1} R_{o1}) / (R_{i1} + R_{o1})$$

$$V_2 = V_{i2} R_{o2} / (R_{i2} + R_{o2})$$


$$\rightarrow V_0 = (1 + R_{o1} / R_{i1}) \cdot V_{i2} R_{o2} / (R_{i2} + R_{o2}) - V_{i1} R_{o1} / R_{i1}$$

$$\text{if } R_{o2} / R_{i2} = R_{o1} / R_{i1} = G$$


$$\rightarrow V_0 = G \cdot (V_{i2} - V_{i1})$$

Some Magics ...


Band-pass Filter

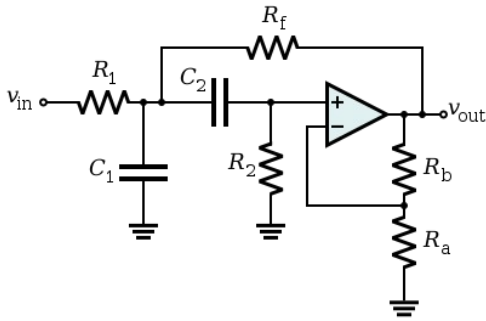


Phase Shifter

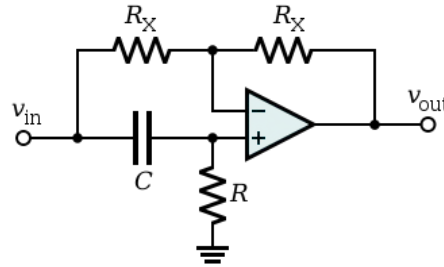


Voltage-to-Current Converter

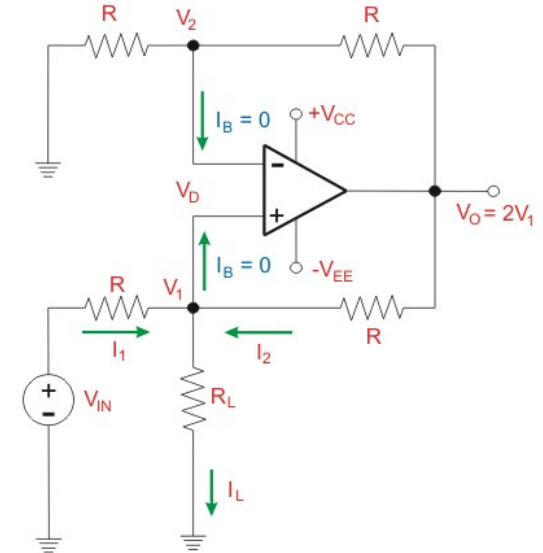


Band-stop Filter

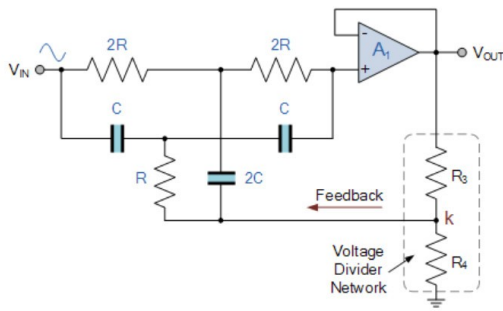

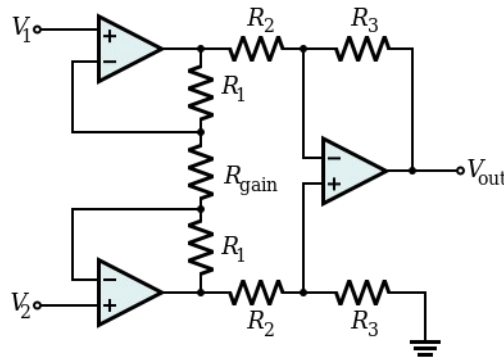*Instrumentation Amplifier
(High CMRR amplifier)*





Buffer!

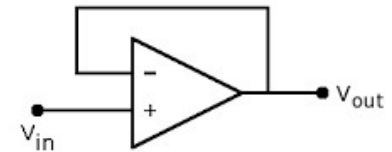


and billions of others ...

Back to signals: what can a signal be ?

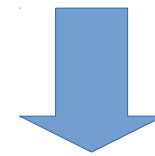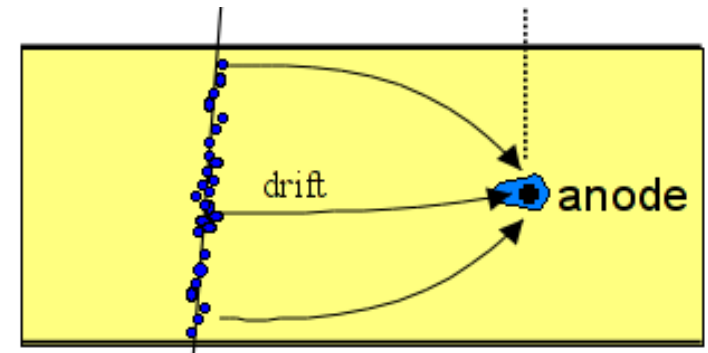- Detectors may be electrically represented as a capacitor (C_d)
 - more realistic schemes will include other contributions
- Interactions of passing particle \rightarrow energy release $E \rightarrow$ short current pulse i_s



DETECTOR

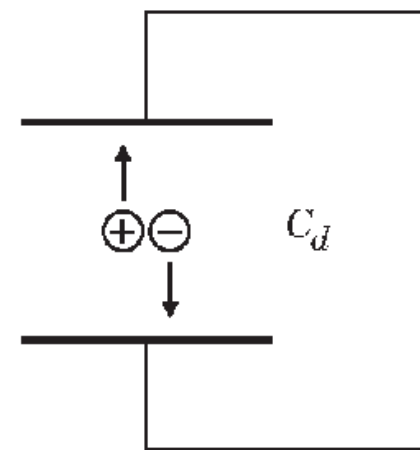

$$E \propto Q_s = \int i_s(t) dt$$

- Pulse duration may range from $O(100 \text{ ps})$ up to $O(10 \text{ } \mu\text{s})$


Voltage-Sensitive Amplifier

- Signals are possibly very small, amplify to:
 - improve signal resolution, adapt it to next stages
 - avoid SNR degradation ...

Using a simple voltage amplifier, the sensed **input voltage V_i** depends on the **detector capacitance**.

Detector capacitance could be a function of the operation point (e.g. high voltage) and/or detector dimension.


Additional **calibration** efforts

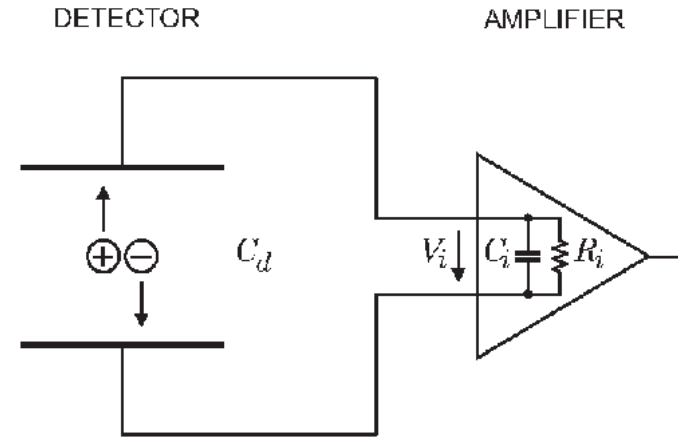

$$V_i = \frac{Q_s}{C_d + C_i}$$

A red arrow points from the text 'Additional calibration efforts' to the C_d term in the denominator of the equation.

Charge-Sensitive Amplifier

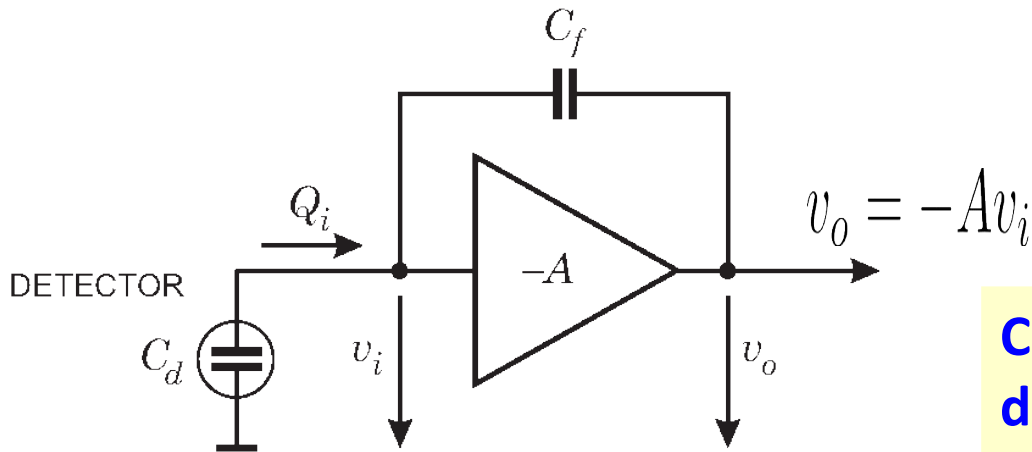

Charge amplification only depends on a well-controlled component

Effective (dynamic) input capacitance:

$$C_i = \frac{Q_i}{v_i} = C_f (A + 1)$$

Gain:

$$A_Q = \frac{v_o}{Q_i} = \frac{Av_i}{C_f(A+1)v_i} = \frac{A}{A+1} \frac{1}{C_f} \approx \frac{1}{C_f} \quad (A \gg 1)$$

Charge Transfer

$$C_i = \frac{Q_i}{v_i} = C_f (A + 1)$$

What total-charge fraction is measured ?

$$\frac{Q_i}{Q_s} = \frac{C_i v_i}{Q_{\text{det}} + Q_i} = \frac{C_i}{Q_s} \cdot \frac{Q_s}{C_i + C_{\text{det}}} = \frac{1}{1 + \frac{C_{\text{det}}}{C_i}} \approx 1 \quad (\text{if } C_i \gg C_{\text{det}})$$

Need **large input capacitance** to maximize charge transfer

Signal-to-Noise Ratio (SNR)

- Improving SNR improves sensitivity (minimum detectable signal)
- Electronic noise does not necessarily dominate each measurement

$$\Delta E = \sqrt{\Delta E^2_{fluc} + \Delta E^2_{noise}}$$

Fluctuations due to physical detection process (e.g. energy deposition) or detector readout (e.g. photomultiplier)



Electronic noise

- Thermal noise: velocity fluctuations in charge carriers
- Shot noise: fluctuations in carrier number (e.g. diode barrier crossing)

Signal-to-Noise Ratio (SNR)

- Improving SNR improves sensitivity (minimum detectable signal)
- Electronic noise does not necessarily dominate each measurement
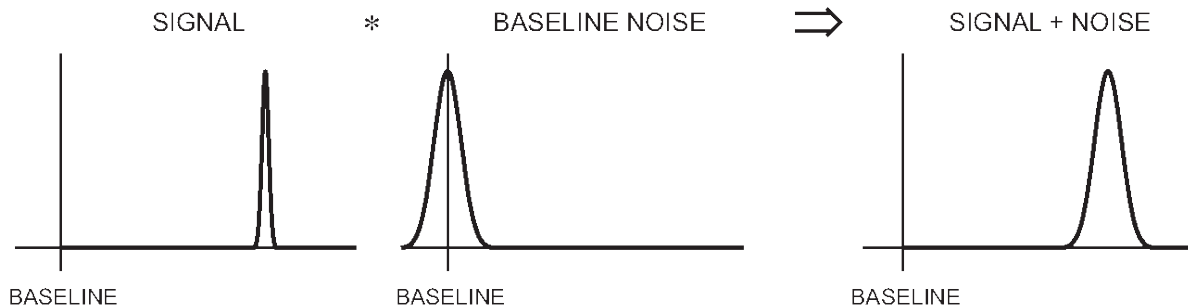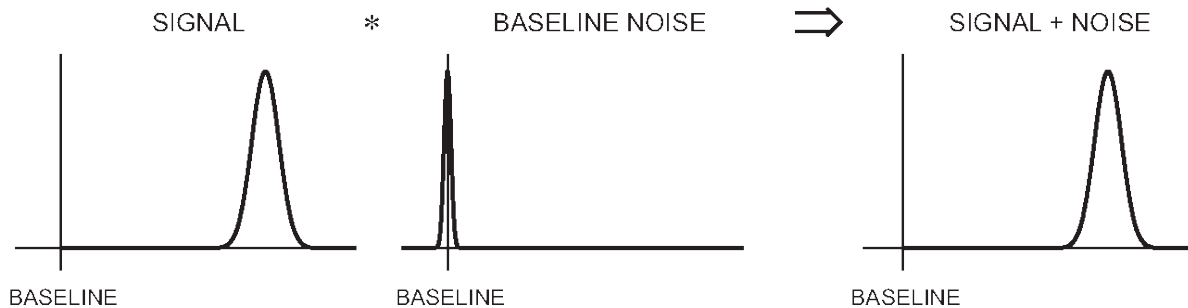
$$\Delta E = \sqrt{\Delta E^2_{fluc} + \Delta E^2_{noise}}$$



S/N needs optimization

SNR .vs. Detector Capacitance

voltage-sensitive amplifier

→ given signal charge Q_s

$$V_s = \frac{Q_s}{C_d + C_i}$$


→ assuming input noise V_n

$$\frac{V_s}{V_n} = \frac{Q_s}{V_n \underbrace{(C_d + C_i)}}_1$$


SNR inversely proportional to total input capacitance



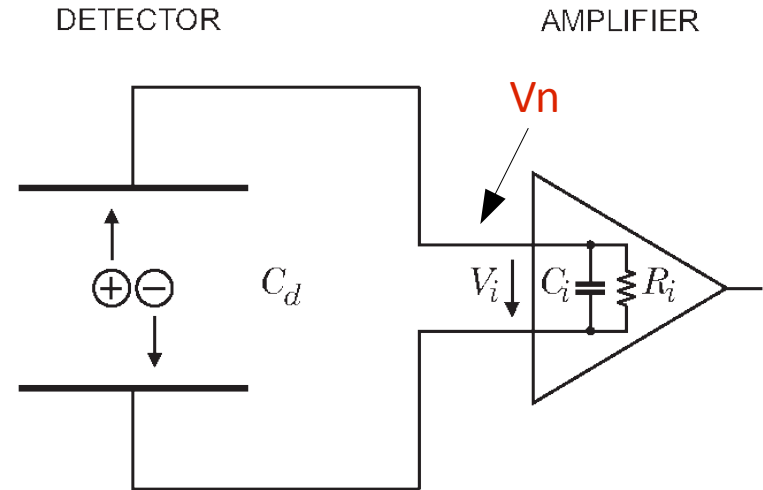Thick detectors normally provide larger signals **and noise**




Read-Out Chain

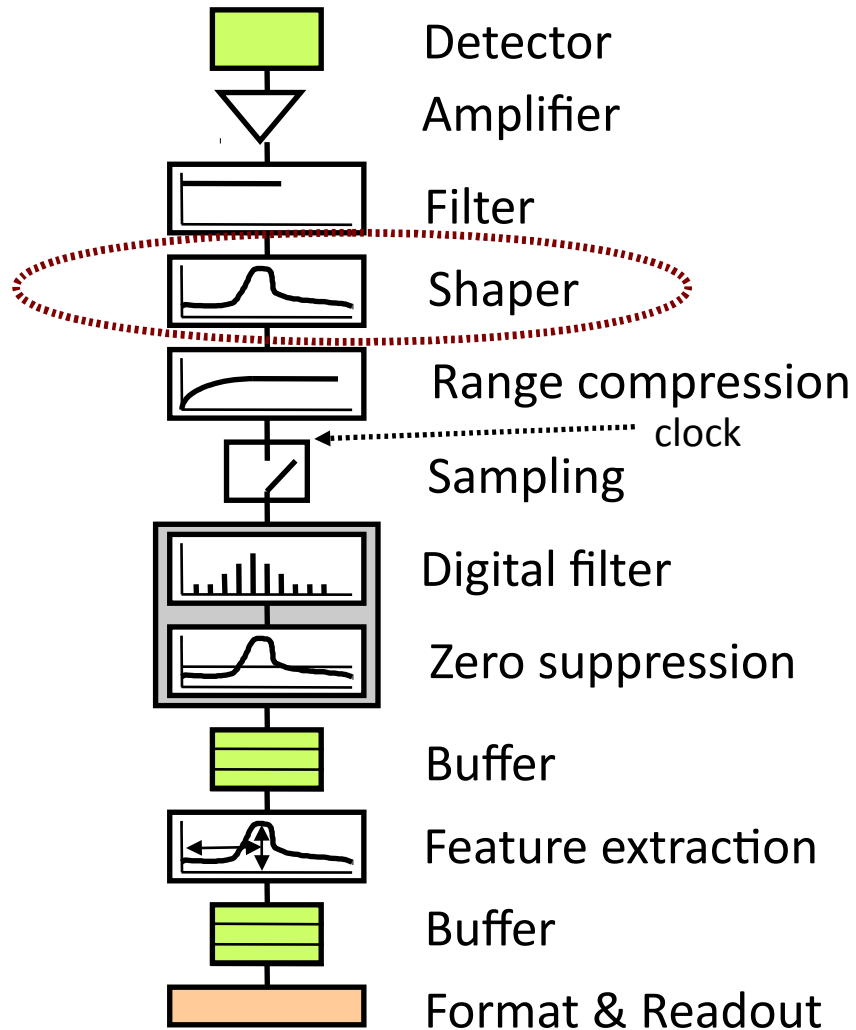


Pulse Shaping

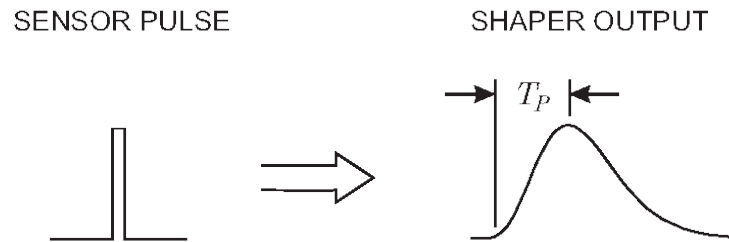- Reduce signal bandwidth (low-pass filter) → improve SNR
 - fast rising signals have large bandwidth
 - shaper broadens signals




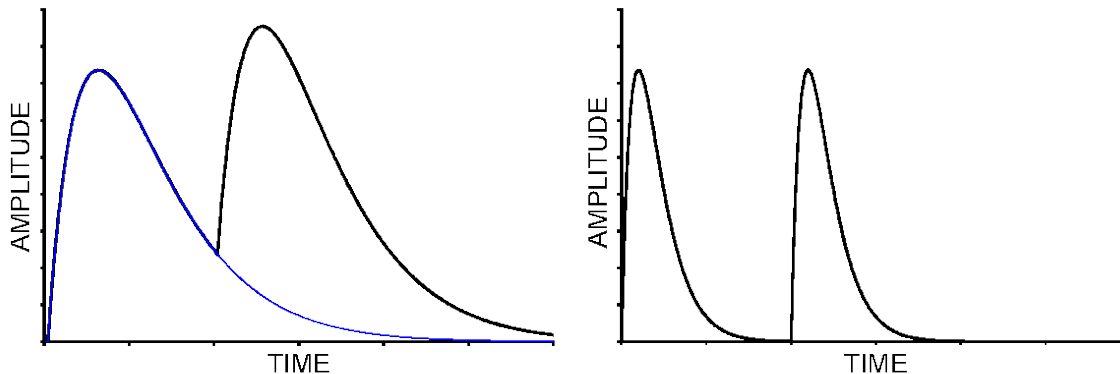- Limit pulse width (high-pass filter) → avoid overlap of successive pulses
 - increase maximum signal rate at the cost of more noise




Pulse Shaping

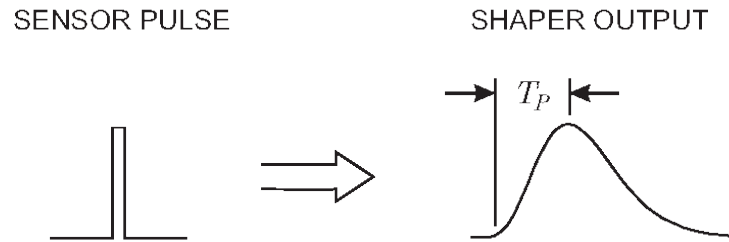- Reduce signal bandwidth (low-pass filter) → improve SNR
 - fast rising signals have large bandwidth
 - shaper broadens signals



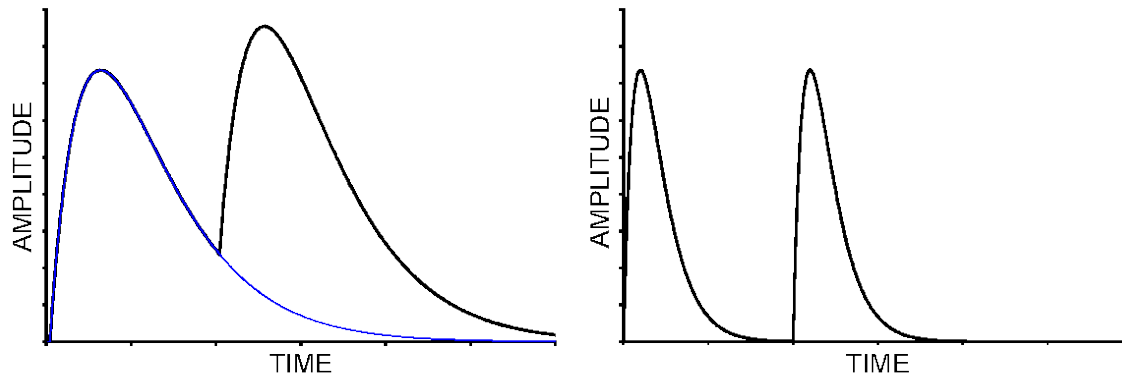
- Limit pulse width (high-pass filter) → avoid overlap of successive pulses
 - increase maximum signal rate at the cost of more noise



Shaping is often a compromise

$CR-(RC)^n$ shaping is often a good compromise

Read-Out Chain

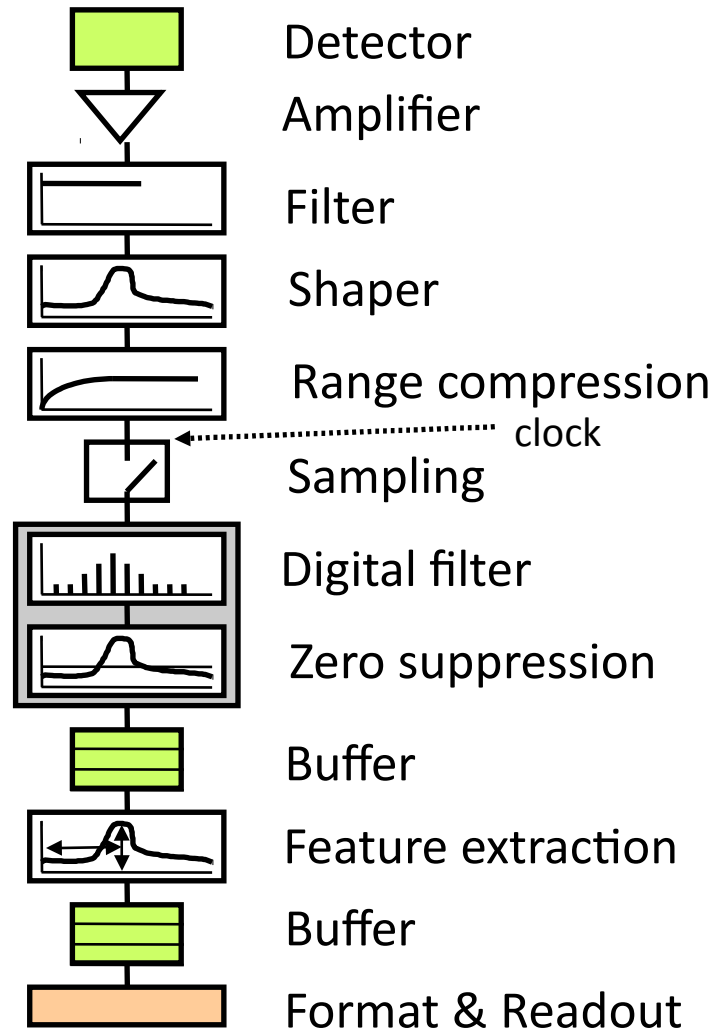


Analog-to-Digital Conversion Introduction


Digitization → encode analog information into a numerical (discrete) format

Why ? Much easier to handle and preserve

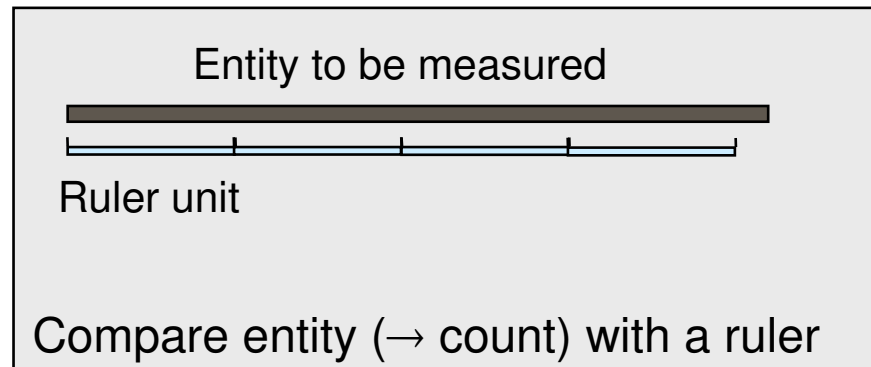Which format ? Usually binary, sometimes BCD




Electrical Symbol:

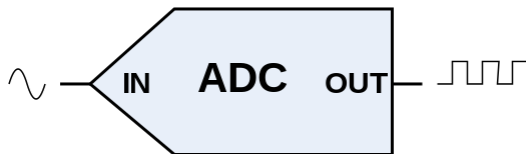

Allow further processing and storage in digital electronics
and **computers**

Flash ADC

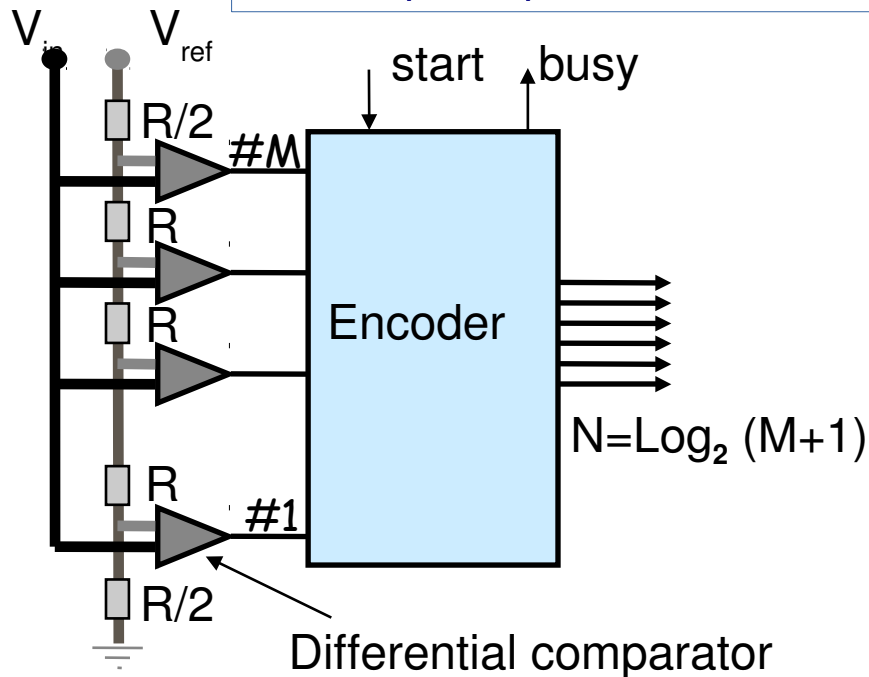- Simplest and fastest implementation
- Performs M comparisons in parallel
 - input V compared with M fractions of a reference voltage:
 $0.5 * V_{ref}/M, 1.5 * V_{ref}/M, \dots (M-0.5) * V_{ref}/M$
in step of V_{ref}/M
- Result encoded into compact N -bit binary value
- Sample input at fixed rate and fixed sample depth




- Simple ? Yes
- Fast ? Yes
- Could be non-linear ? Yes
- Cheap ? Oopss ...

Flash ADC

- Simplest and fastest implementation
- Performs M comparisons in parallel
 - input V compared with M fractions of a reference voltage:
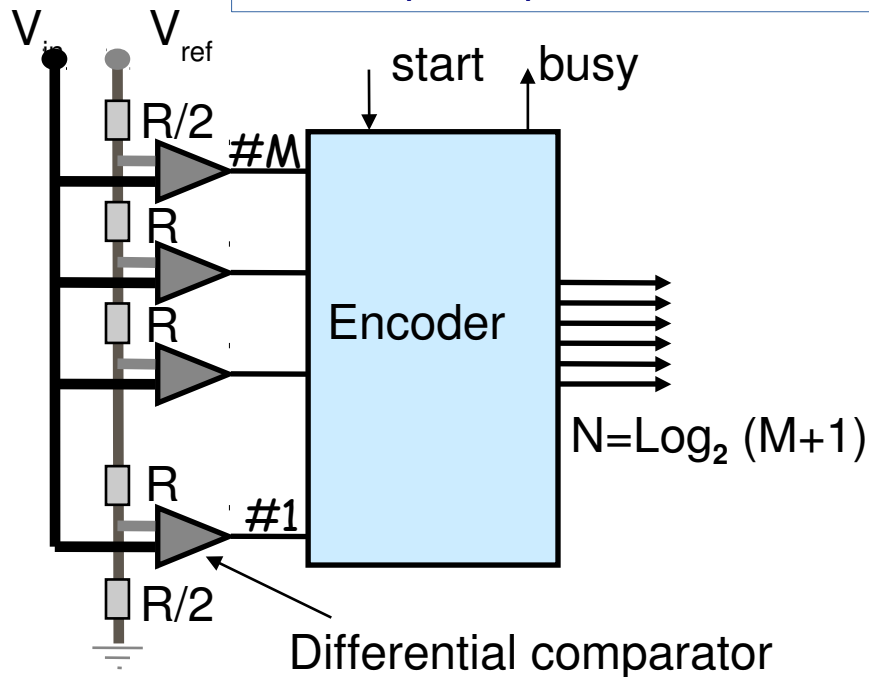
$$0.5 * V_{ref}/M, 1.5 * V_{ref}/M, \dots (M-0.5) * V_{ref}/M$$
 in step of V_{ref}/M
- Result encoded into compact N -bit binary value
- Sample input at fixed rate and fixed sample depth




Example $M=3 \rightarrow N=2$

V_{in}/V_{ref}	Comparison results	Encoded form
$<1/6$	000	00
$1/6 \leq <3/6$	001	01
$3/6 \leq <5/6$	011	10
$5/6 \leq$	111	11

ADC Characteristics

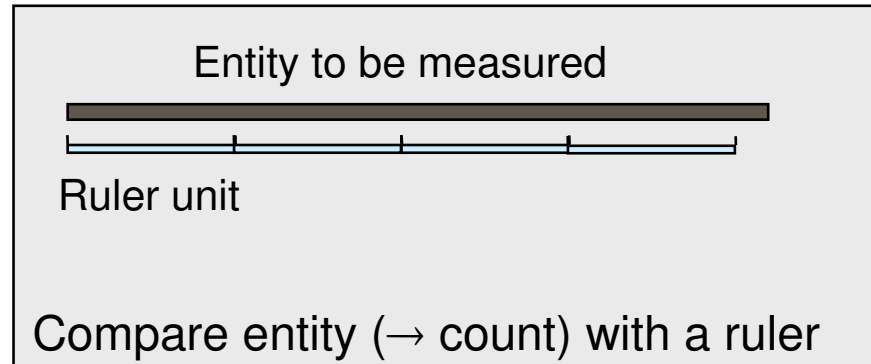
Digitization → encode analog information into a numerical (discrete) format



- Resolution (LSB), the ruler unit: $V_{\max}/2^N$
 - 8bit, 1V → LSB=3.9mV
- Quantization error: $\pm\text{LSB}/2$
- Dynamic range: V_{\max}/LSB
 - N for linear ADC
 - >N for non-linear ADC; if logarithmic:
constant relative resolution on the valid input range


ADC Phase-Space

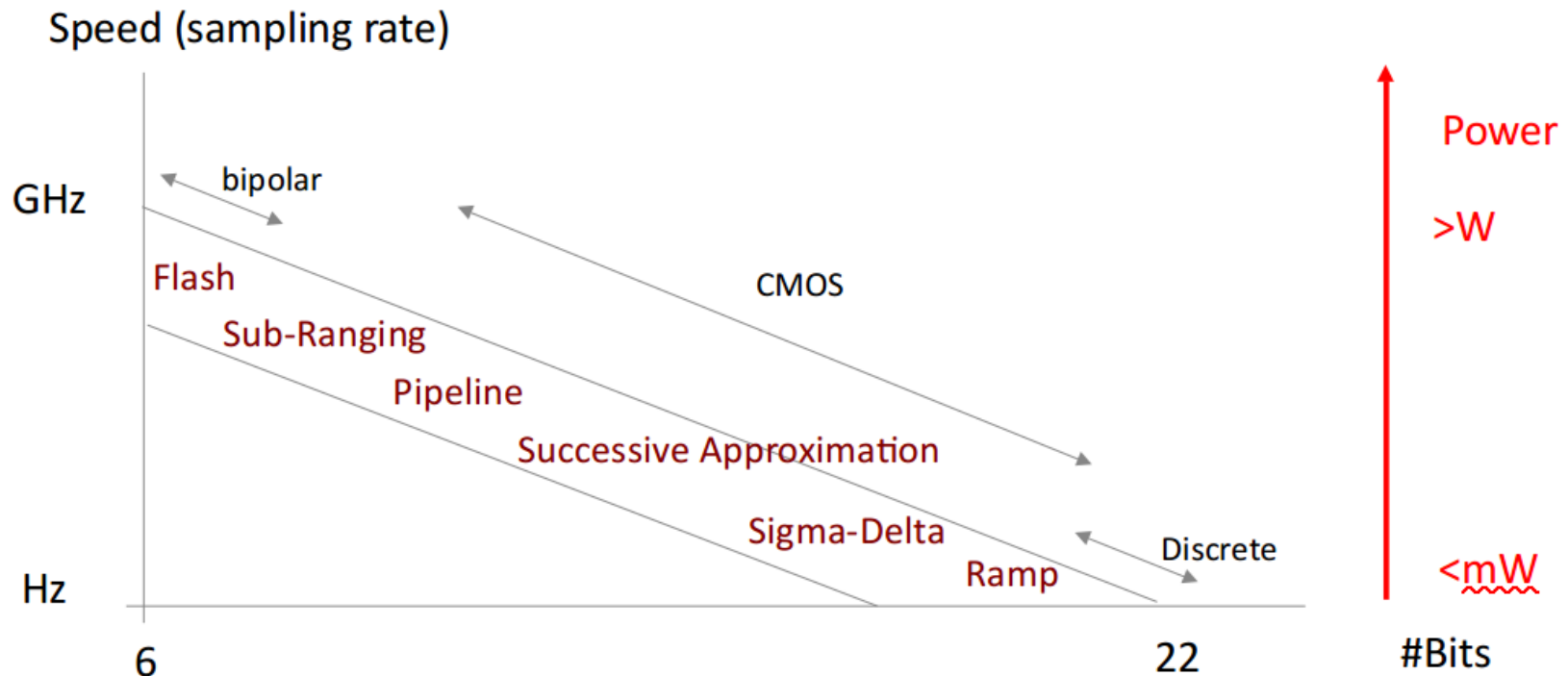Many different ADC techniques exist, with different trade-offs between speed, resolution, power consumption, cost, ...





ADC (In)Accuracies

ADC Transfer function

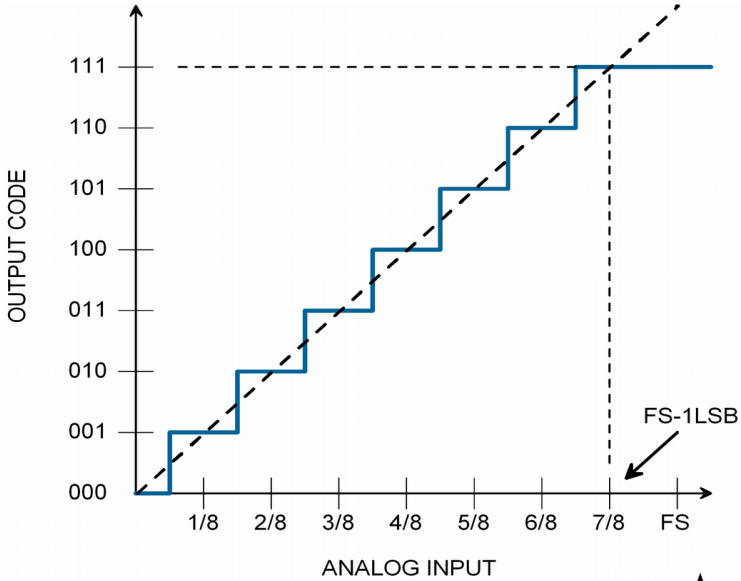



Integral & Differential Non-Linearity

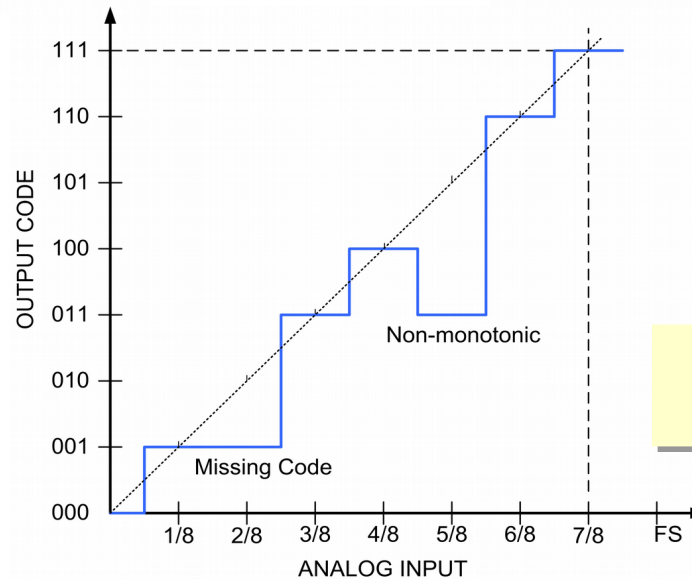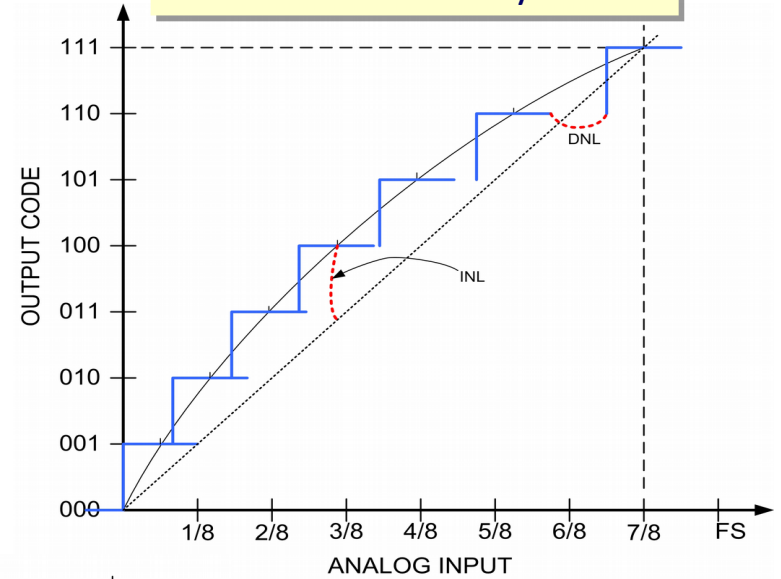

Extreme Differential Non-Linearity



Real ADC.s at Work

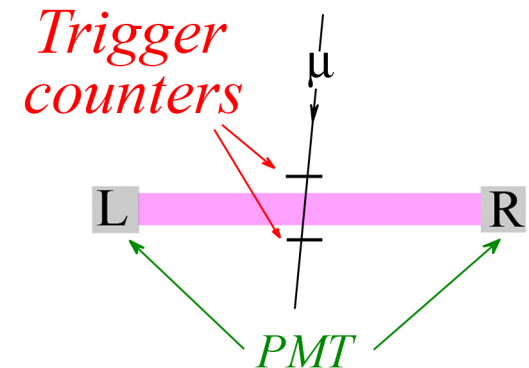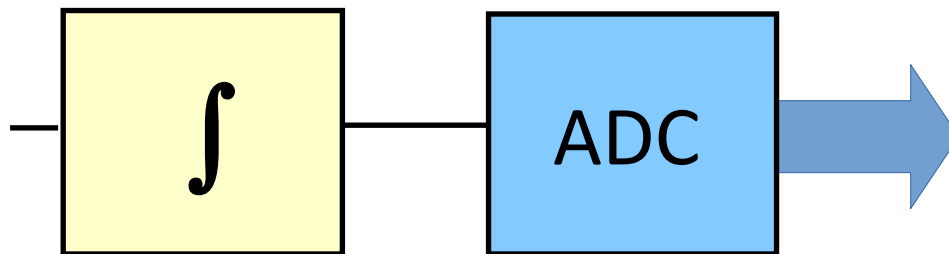- Real data from a beam test @CERN
- PbWO_4 (scintillating) crystal equipped with two PMTs and exposed to e , μ and π beams
- QDC \rightarrow (gated) charge integrator followed by ADC
 - \rightarrow (fixed-duration) gate opened after trigger
 - \rightarrow digital conversion started after gate closing
 - \rightarrow integrator discharged after conversion





Real QDC.s at Work

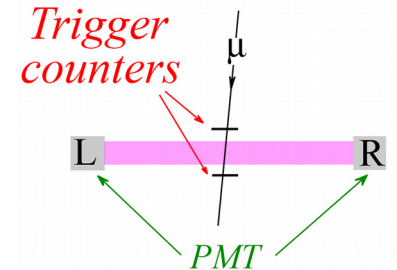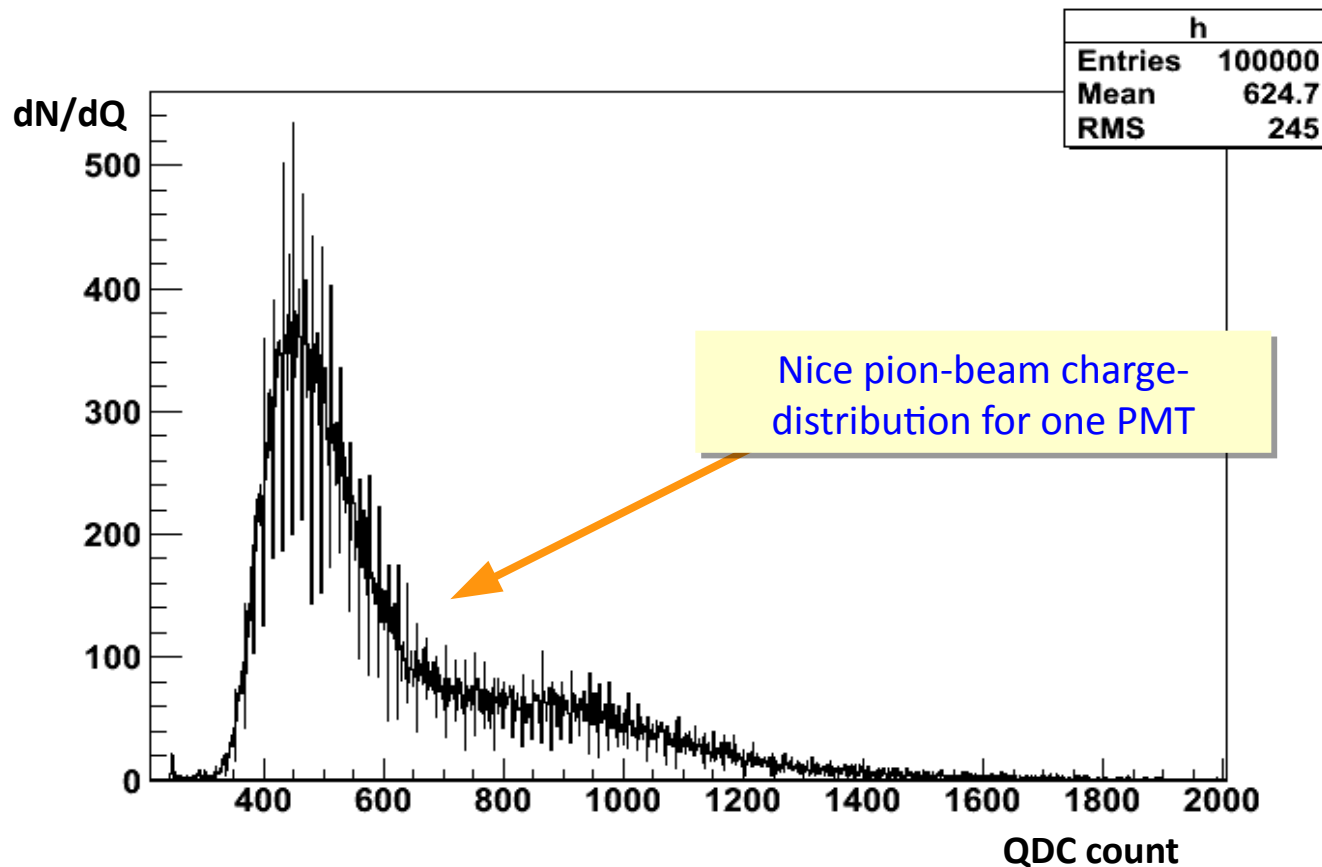PbWO₄ crystal equipped with two PMTs and exposed to e, μ and π beams




Real QDC.s at Work

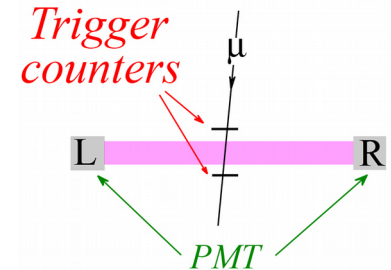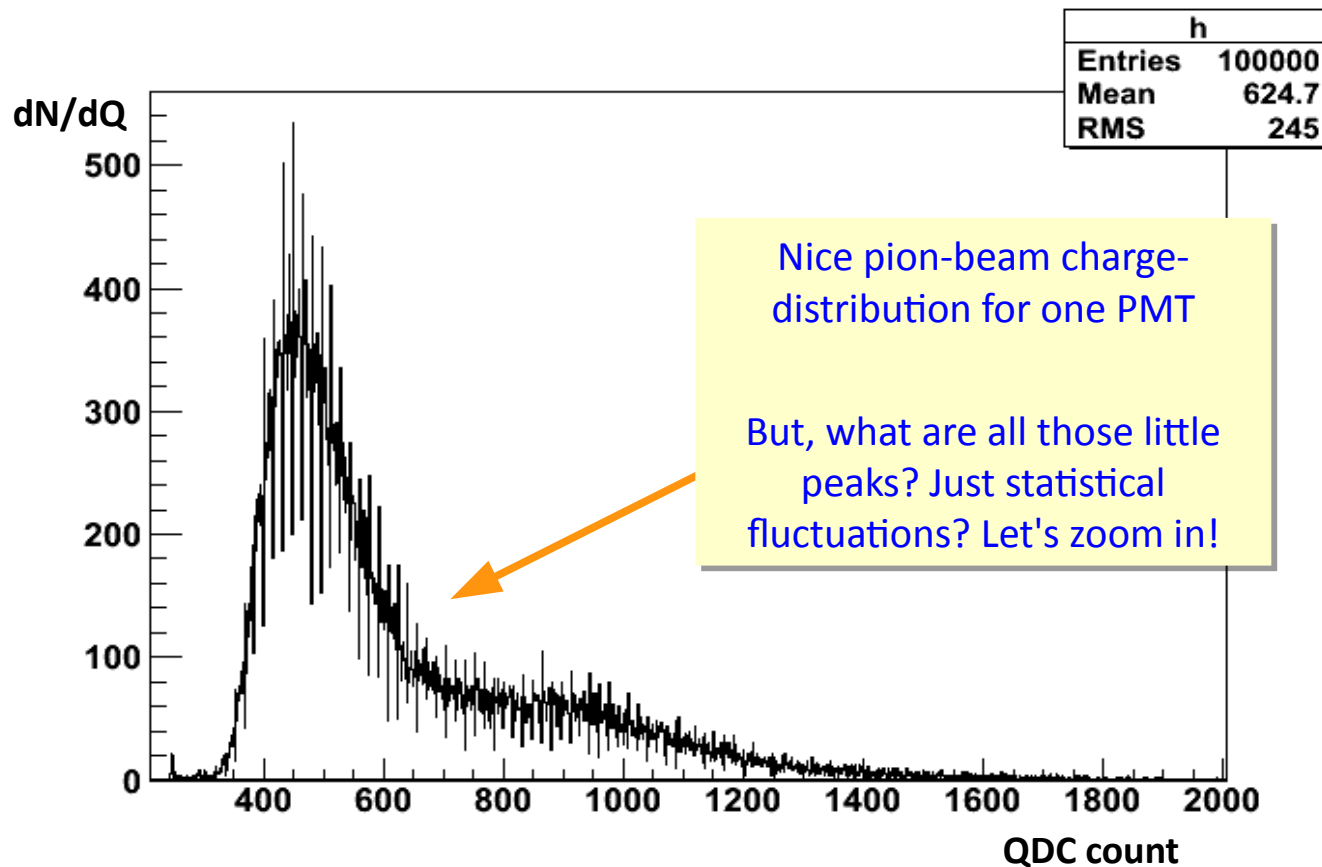
PbWO₄ crystal equipped with two PMTs and exposed to e, μ and π beams



Real QDC.s at Work

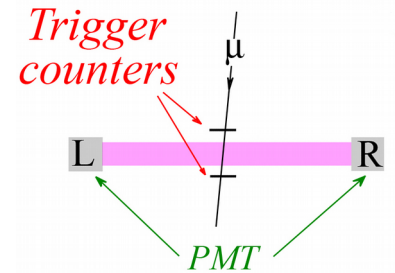

h	
Entries	100000
Mean	541.3
RMS	130

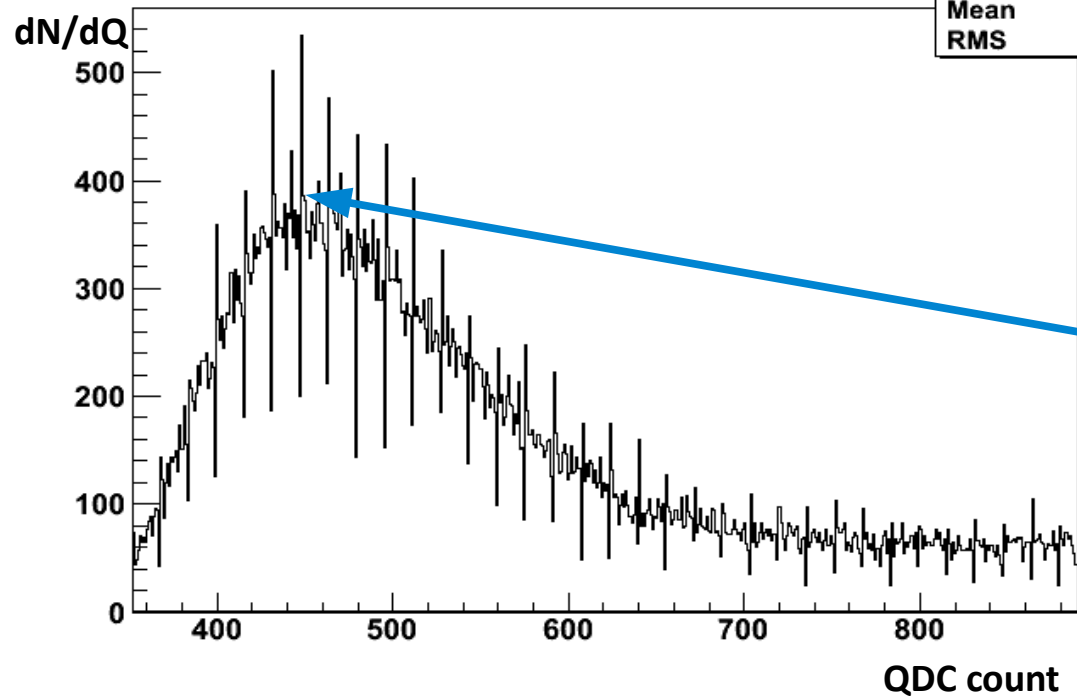

Bin with N entries shall fluctuate with:

- $\sigma = \sqrt{N}$

$$\sqrt{360} \sim 19 \rightarrow (540 - 360) / 19 \sim 10$$



Spikes are regularly distributed

- some systematic effect is taking place

Let zoom in a bit more!

Real QDC.s at Work

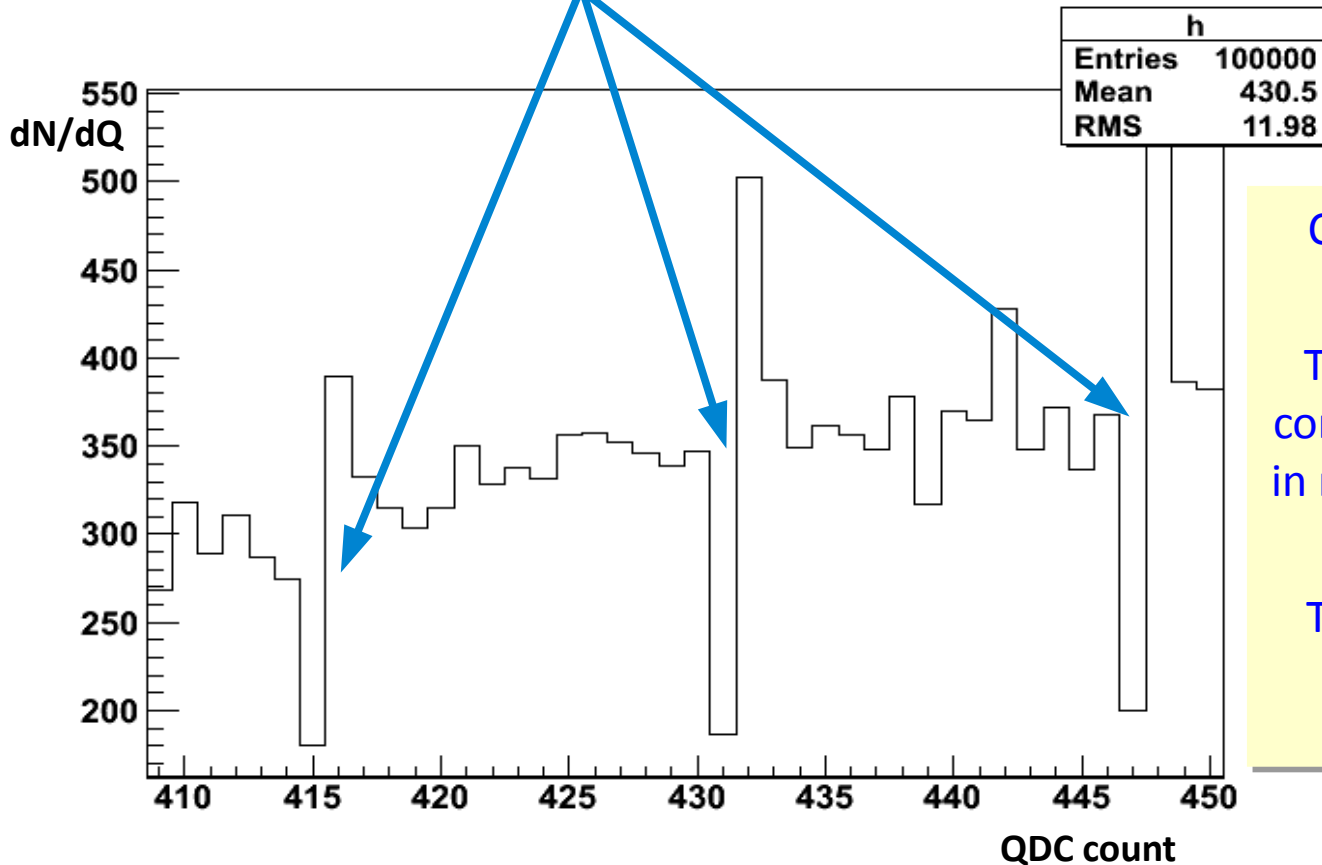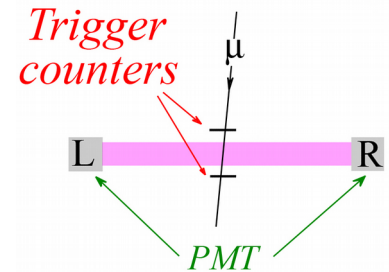415 & 416 → 0x19f & 0x1a0
 431 & 432 → 0x1af & 0x1b0
 447 & 448 → 0x1bf & 0x1c0



Can you see the effect?

The QDC prefers output configurations of type xxx0 in respect of those like xxxf

Typical differential non-linearity of successive approximation ADCs

Homework: can you find a simple way to fix this problem in the data? What the cost?

Some more ... Peak-Sensing ADC

- QDC signals need to be fully integrated, gate need not to be too long
→ need precise and stable timing .vs. gate:
- high-rate unipolar pulses may suffer of baseline drift

→ to overcome such problems:


1) charge amplifier + shaper:

- signal shape stable
- peak value proportional to Q

2) peak-sensing ADC:


- find V_{max} within a gate (rise-time shouldn't be too fast)
- at end-of-gate, convert

Time Measurements → TDC

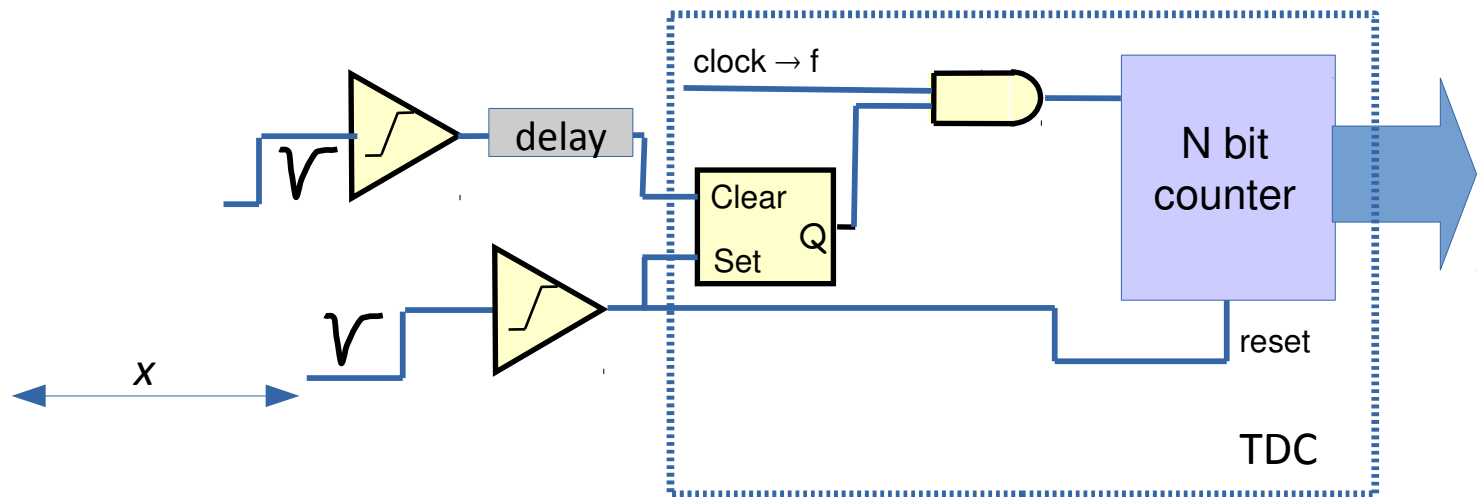


- Time-to-Digital Converter
- Resolution: $1/f$
- Dynamic range: N
- Single-hit TDC:
 - e.g. noise spike arriving just before the signal → measure lost

Multi-Hit TDC

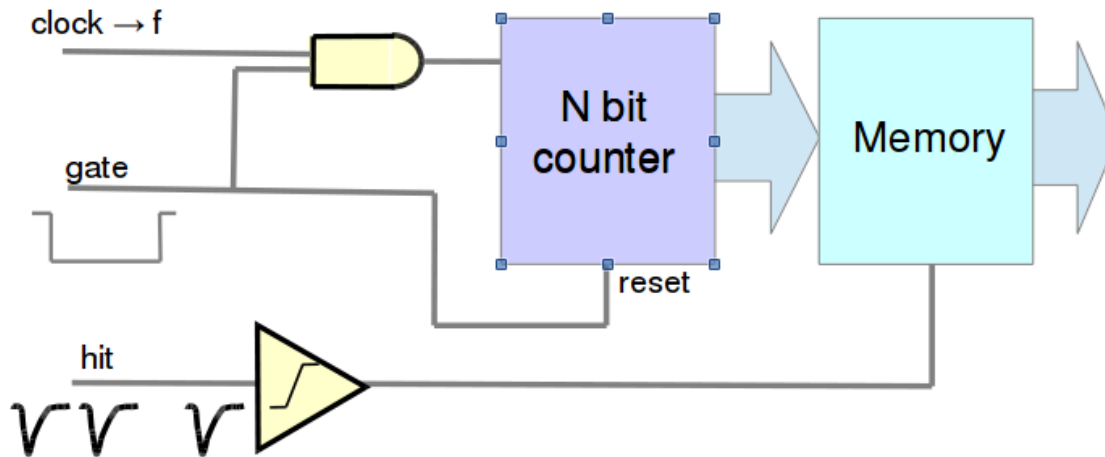

- Gate resets and starts counter. Also provides measurement period
- Gate duration $< \sim 2^N/f$
- Each “hit” (i.e. signal) forces memory (FIFO) to load current counter value, that's delay wrt. gate opening
 - in order to distinguish hits belonging to different gates, some additional logic needed to tag data (end/start-of-gate marker)
- Common-start configuration

Real TDC.s

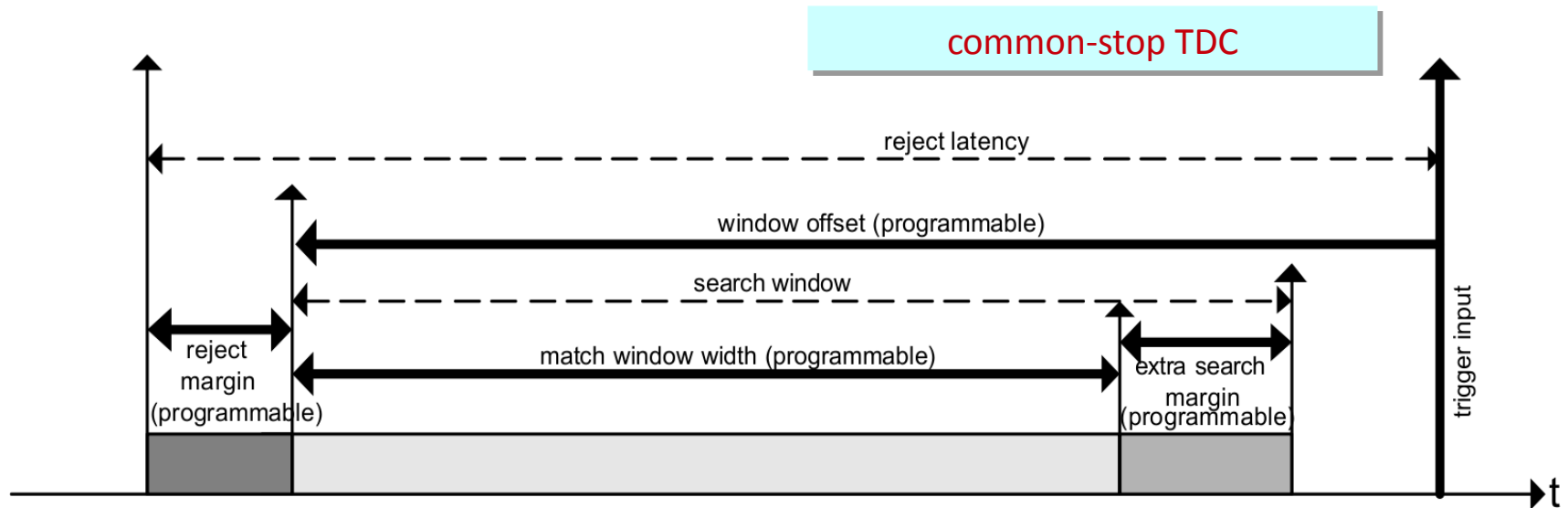

- Real TDCs provide advanced functionalities for fine-tuning hit-trigger matching
 - internal programmable delays
 - internal generation of programmable gates
 - programmable rejection frames

Digital Converters - Summary

Speaking about measuring fast (short) pulses ...

- Flash ADC: high-speed sampling, measure V
- QDC: pulse integration, measure Q , pedestal* proportional to gate length
- Peak Sensing ADC: measure $V(\text{peak})$
- TDC: measure time intervals
- **conversion (dead) time of commercial VME boards \sim few μs**

*pedestal = measurement of input noise (absence of signal)

to be continued...