

Development of an rf-waveform synthesizer with quantum-based accuracy

EUCAS 2017

Manuel A. Castellanos-Beltran

David Olaya, Christine A. Donnelly, Peter Hopkins, Paul Dresselhaus,
and Sam Benz



Create quantum-based signal sources

Spanning the entire RF frequency spectrum from 100 kHz to 100 GHz

- Near-perfect signal purity
- Quantum-accurate amplitude (up to 100 mV)
 - Voltage level: 0.2 V at 1 MHz demonstrated by J. Brevik⁽¹⁾
- Programmable

Customers

- Metrology labs worldwide
- Wireless communications industry
- RF spectrum users including defense applications

[1] (4EP2-24) Megahertz Waveform Synthesis with the Josephson Arbitrary Waveform Synthesizer


Quantum accurate waveform synthesis

NIST Josephson arbitrary waveform synthesizer (JAWS) with arrays of pulse-driven Josephson Junctions

10Hz to 1MHz Frequencies (>1 V)



PPM accuracy ($f < 20$ kHz)

Great SFDR performance

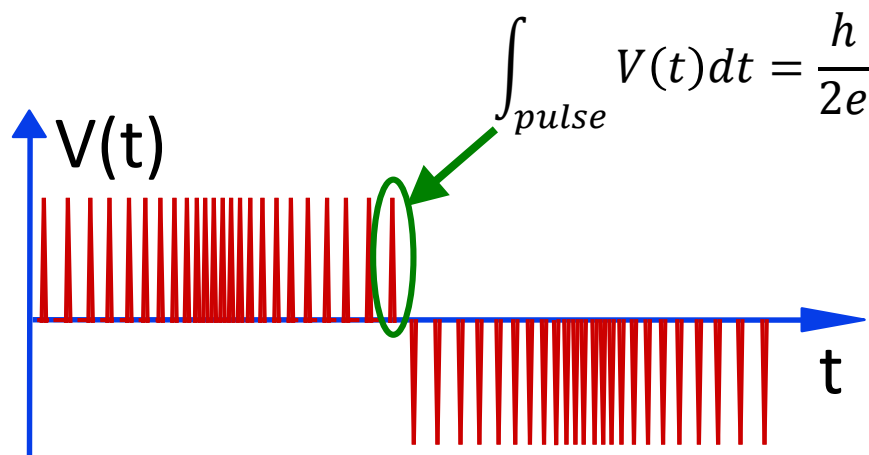

(2E02-07) Quantum Voltage Standard
Developments at NIST



S. Benz

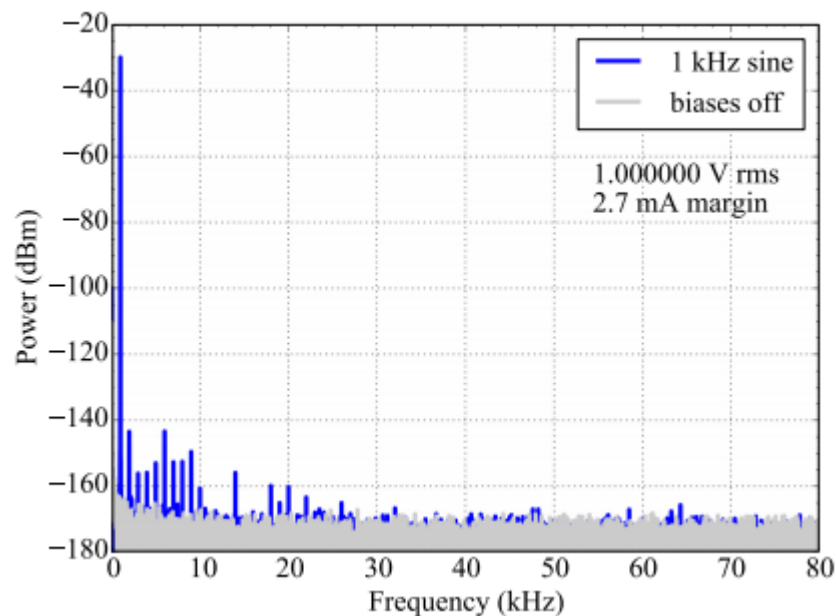 

Quantum accurate waveform synthesis

NIST Josephson arbitrary waveform synthesizer (JAWS) with arrays of pulse-driven Josephson Junctions

  - 10Hz to 1MHz Frequencies (>1 V)
- PPM accuracy ($f < 20$ kHz)
- Great SFDR performance



Several suggestions for SFQ-based-DACs


- Frequency modulation of output SFQ pulse train V. K. Semenov, C. Hamilton.
- Switching of multiplication factor in a voltage multiplier. M. Maezawa, F. Hirayama, and M. Suzuki (AIST)
- Use of RSFQ voltage drivers for biasing of large junction arrays. Niemeyer, *et. al.* (PTB)
- Direct Digital Synthesizer (Gigahertz output) O. Mukhanov, *et. al.* (HYPRES)

All suggested implementations imply maximum frequencies in the megahertz!

rf Arbitrary Waveform Synthesizer requires fundamental redesign

Goals

 - Near-perfect signal purity
- Quantum-accurate amplitude (up to 100 mV)
- Output frequencies at the tens of gigahertz



Challenges

- 1. Faster Clocking:** SFQ circuits, higher current density junctions
- 2. Signal Purity:** ⁽¹⁾ $\Sigma-\Delta$ modulation scheme, Low-pass \rightarrow Bandpass
- 3. Amplification:** Preserve quantized amplitude, timing, and signal purity
- 4. Signal Transmission:** ⁽²⁾ 4K \rightarrow 300K, 50 ohms loading
Collaboration with Communications Technology Laboratory.


[1] (1EP1-10) C. Donnelly

[2] (4EP2-24) J. Brevik

NIST Starting Point

Milestone #1: 1 GHz , 1 mV



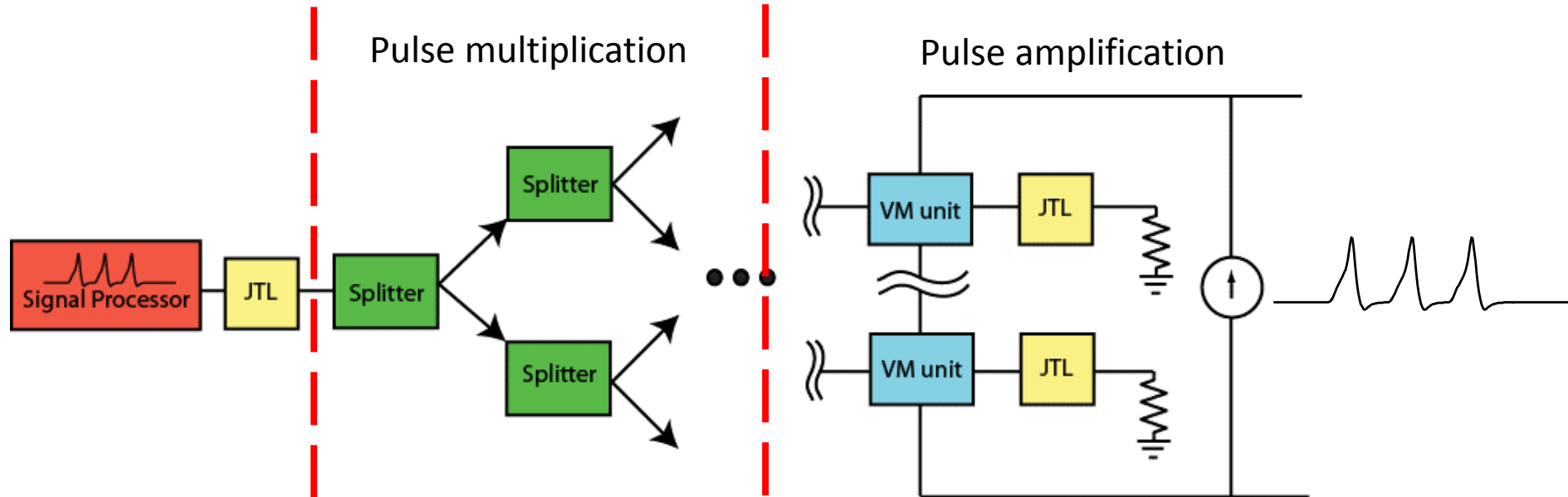
First Step: Δ - Σ SFQ pulse train generation + Voltage Multiplier



 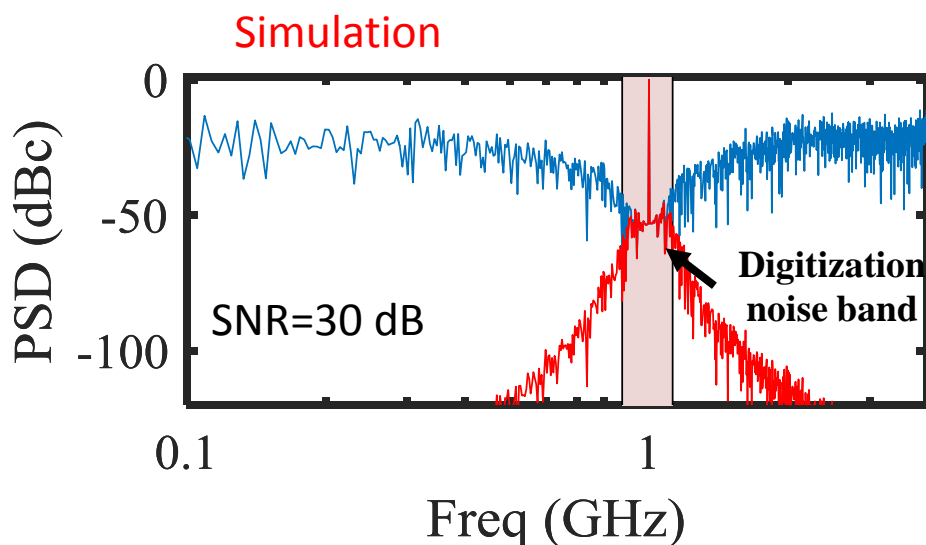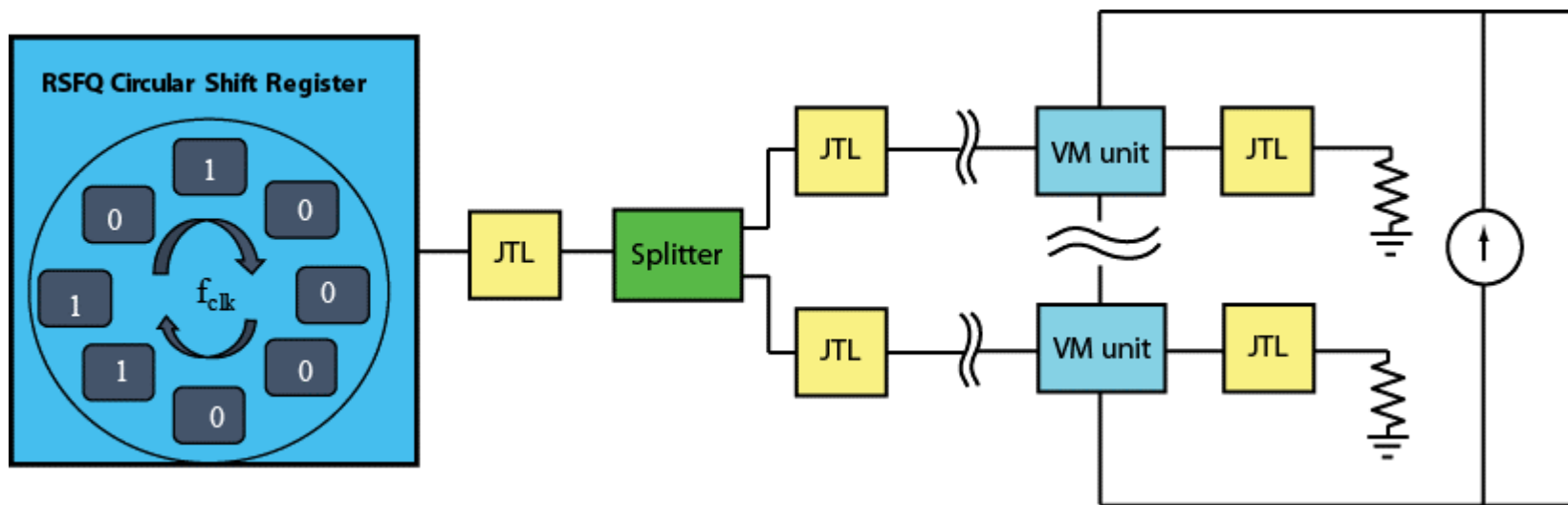1. Clock speed limit
2. Signal purity, Σ - Δ modulation scheme
3. Quantum-accurate amplification
 - pulse timing/synchronization
4. Signal transmission to 50 ohm load

Full Implementation of RSFQ Synthesizer

Plan: for now we will just worry about a unipolar signal loaded into a circular shift-register. Pulse density technique using Σ - Δ modulation



Requires
gain of 64

Shift register size of 2048 bits
Clocked at 8 GHz
Signal frequency 1 GHz
Noise band 250 MHz


NIST Fabrication Process

NIST cell library using self-shunted Josephson junction: fabrication process includes Nb electrodes with tunable Nb-doped silicon barrier junctions.

Process details

- Nb wiring and ground layers
- Nb-doped Si junction barriers close to metal-insulator transition
- 4 metal layers
- Slightly underdamped junctions ($\beta \sim 1.5$)
- Target $I_c R = 250 \mu\text{V}$
- $J_c = 4.5 \text{ kA/cm}^2$ (capable of doing up to 100 kA/cm^2)

4-layer process with CMP

 


NIST Fabrication Process

NIST cell library using self-shunted Josephson junction: fabrication process includes Nb electrodes with tunable Nb-doped silicon barrier junctions.

Process details

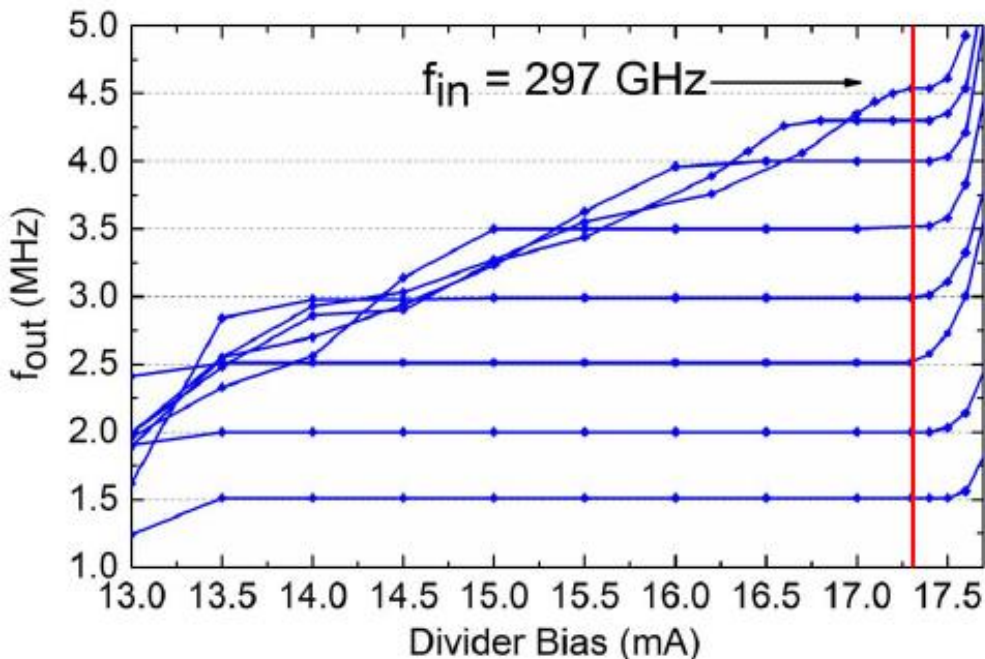- Nb wiring and ground layers
- Nb-doped Si junction barriers
- 4 metal layers.
- Slightly underdamped junctions ($\beta \sim 1.5$)
- Target $I_c R = 250 \mu\text{V}$
- $J_c = 4.5 \text{ kA/cm}^2$ (capable of doing up to 100 kA/cm^2)



David Olaya, *et al.* "300-GHz Operation of Divider Circuits Using High- J_c Nb/Nb_xSi_{1-x}/Nb Josephson Junctions." IEEE Trans. Appl. Supercond, VOL. 25, NO. 3, JUNE 2015

RSFQ circuits for waveform synthesis

NIST cell library so far:

- *DC-to-SFQ*
- *JTL*
- *SFQ-to-DC*
- *Splitters*

DC-to-SFQ



JTL



SFQ-to-DC



C-BUFFER



-100 -50 0 50 100

- *Confluence Buffers*
- *T flip-flops*
- *D flip-flops (for shift registers)*
- *Voltage multipliers*

SPLITTER



TFF



DFF





-100 -50 0 50 100

Expected margins (%)

Measured margins (%)



8-bit Shift Register

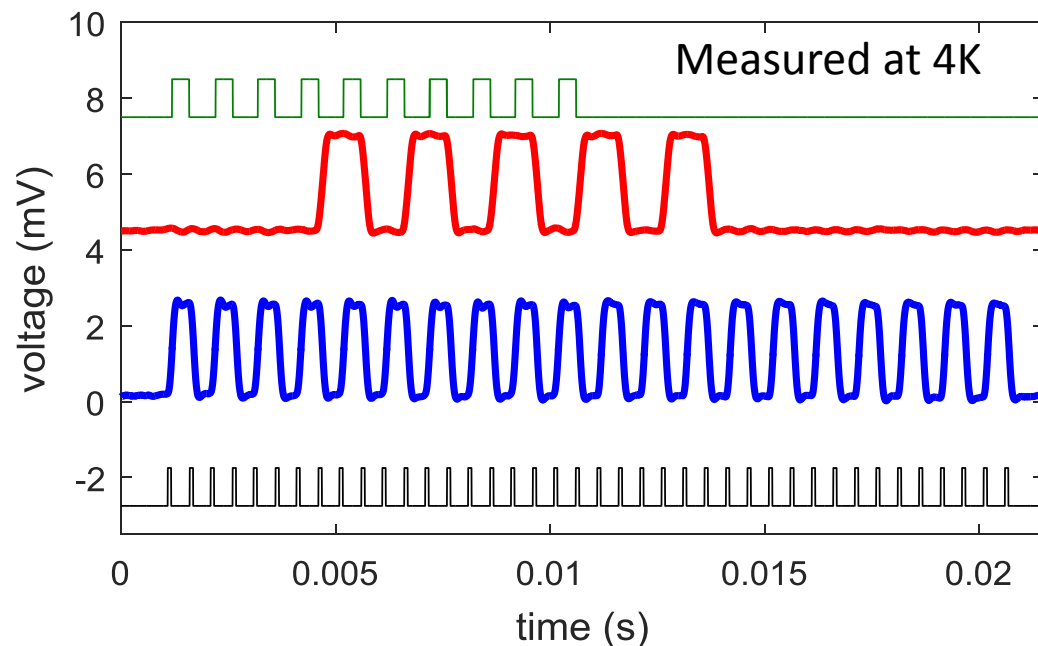 

$|Margins| > \pm 25\%$
 Tested at 1 kHz, not expected
 degradation up to $f = 50 \text{ GHz}$
 Showing no degradation from
 single D F-F to an 8-bit SR

(scaled) Data in
 Data out
 Clk out
 (scaled) Clk in


Voltage multiplier

  

S. Polonsky and D. Schneider IEEE Transactions on Applied Superconductivity, vol. 7, no. 2 (1997)

F. Hirayama, *et al.* Characteristics of a voltage multiplier for a RSFQ digital-to-analog converter, Superconductor Science and Technology, 15, 4 (2002).



How does the voltage multiplier work?

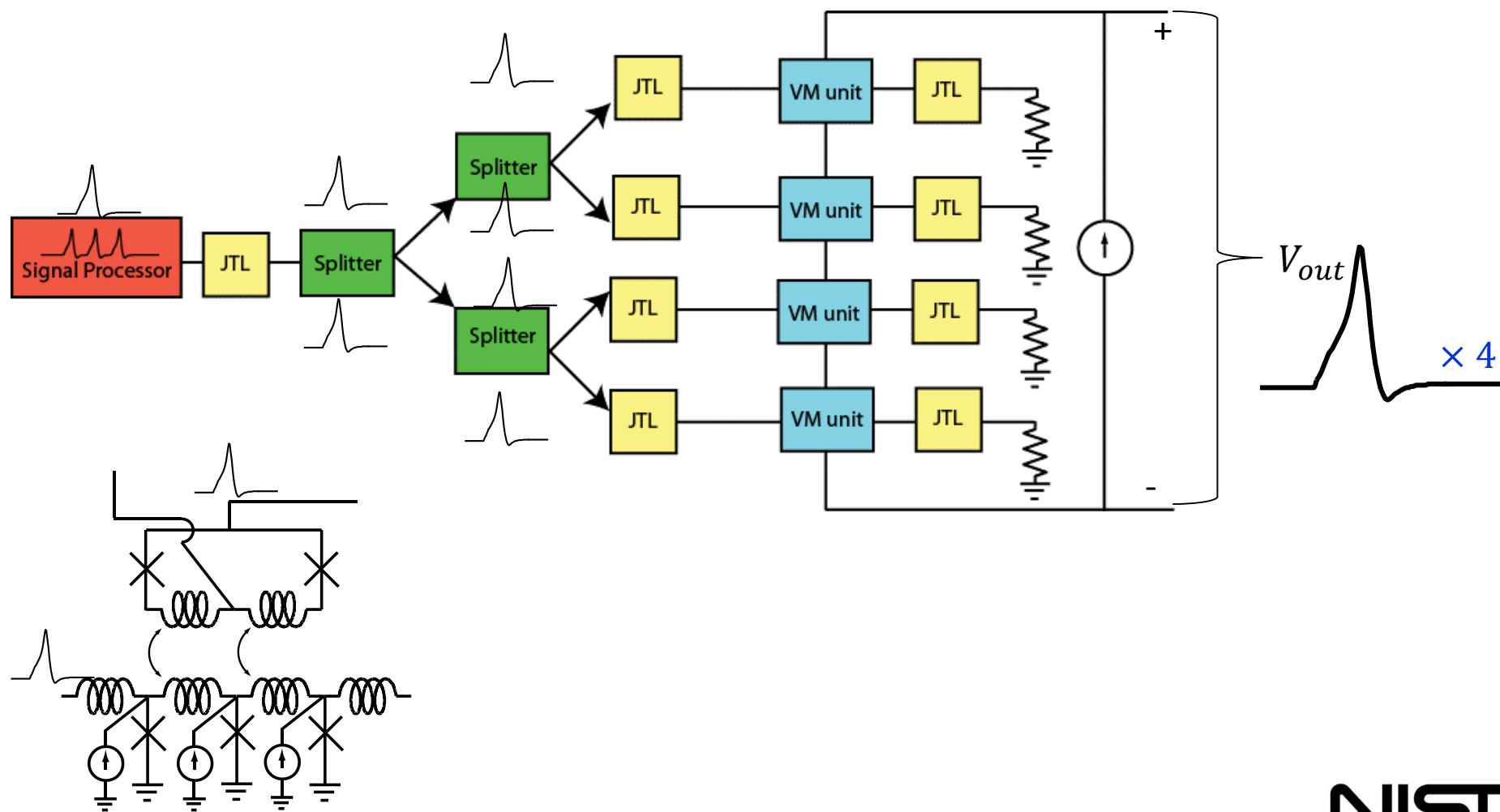

Expected performance of Voltage Multiplier

WRSPICE simulations for margins analysis of circuit

Over-biased junction method

 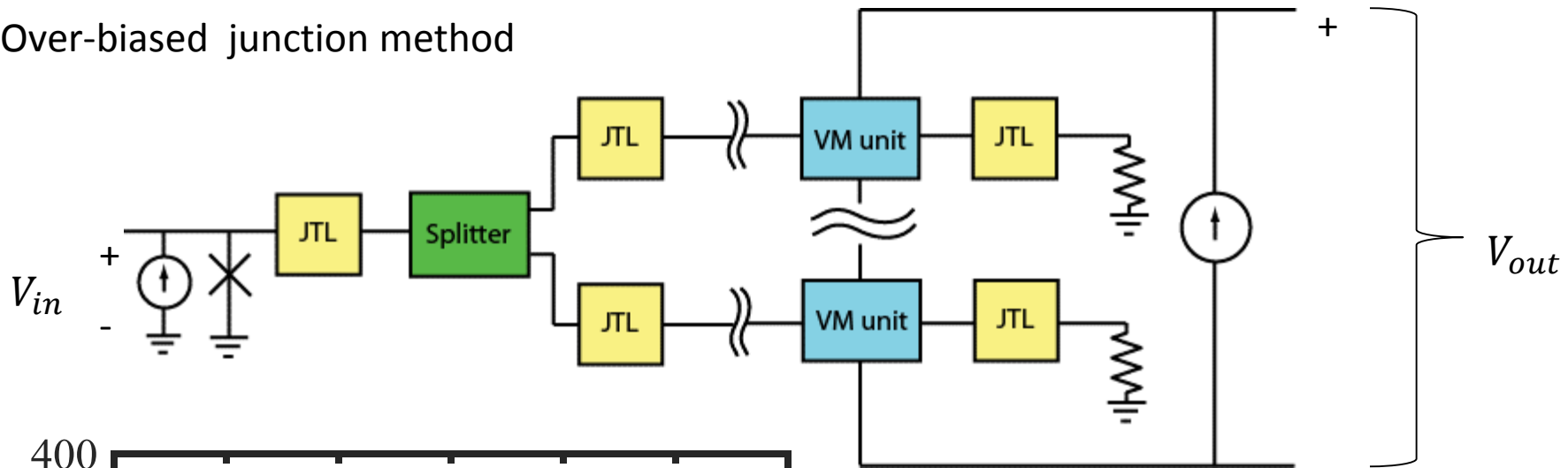


Issues:

- Frequency-limited by $I_c R = 250 \mu V$
- Margins reduced to $\pm 10\%$ at 20 GHz

Progress and Future Work

 - Building RSFQ infrastructure at NIST: fabricated and characterized basic SFQ circuits
- Fabricating building blocks of our high-frequency synthesizer (shift registers and voltage multipliers)
- Increase intrinsic speed of voltage multipliers
- Understand limitations of finite size circular shift registers
- Fix margin limitations due to $50\ \Omega$ impedance loading on voltage multipliers




END

Voltage multiplier $\times 8$

Measured margins.

Over-biased junction method.

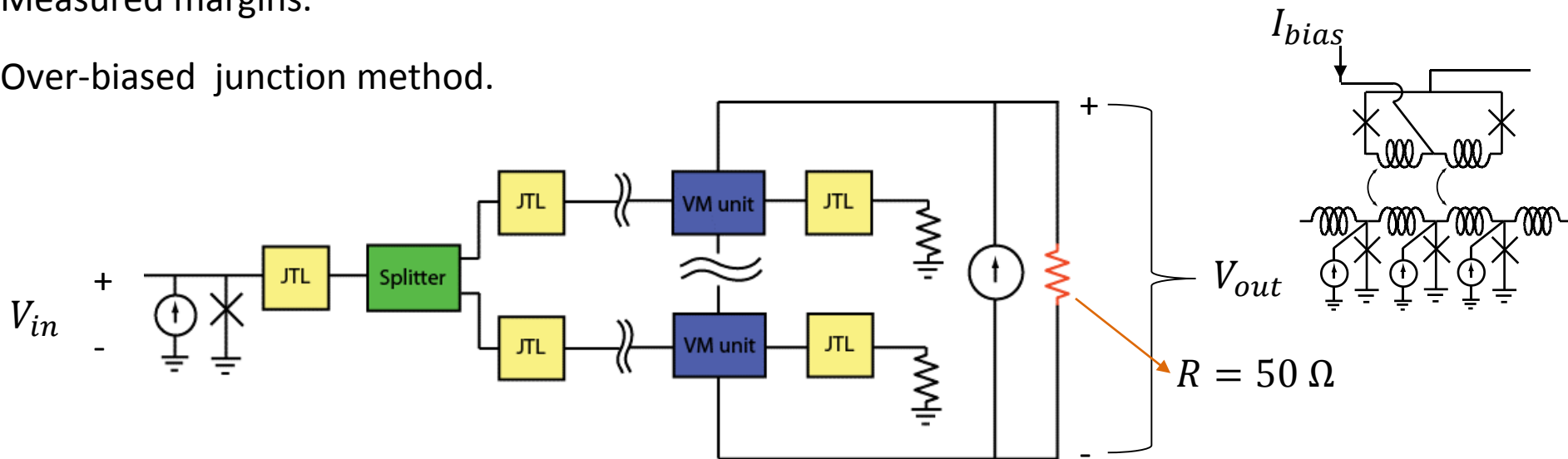


**Data.
Still
working
on it.**

Issues:


- Frequency-limited by $I_c R = 115 \mu\text{V}$ due to issues in fabrication
- We have not tested yet the effect of 50Ω loading

Near-future work

“Low” frequency implementation

 

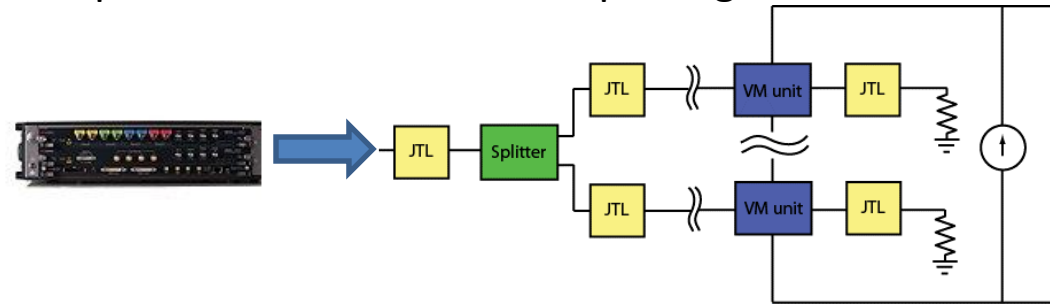Replace it with off-the-shelf pulse generators




Voltage multiplier $\times 8$

Clocked at 8 GHz
Signal frequency 1 GHz

Voltage multiplier

Voltage multiplier based on inductively-coupled SQUID-stack voltage reproducers.


Name	Value
LT1	1.3 pH
LT2	4.0
LT3	4.0
LT4	1.3
LS1	4.0
LS2	4.0
M1	1.4
M2	1.4
Ic1	240 μA ($\beta = 0.15$)
Ic2	135
Ic3	360
Ic4	400
Ic5	420

 


Polnsky, Schneidr (1997)

Characteristics of a voltage multiplier for a RSFQ digital-to-analog converter. Fuminori Hirayama, Masaaki Maezawa, Shogo Kiryu, Hitoshi Sasaki and Akira Shoji. Superconductor Science and Technology, 15, 4.

RSFQ circuits for waveform synthesis

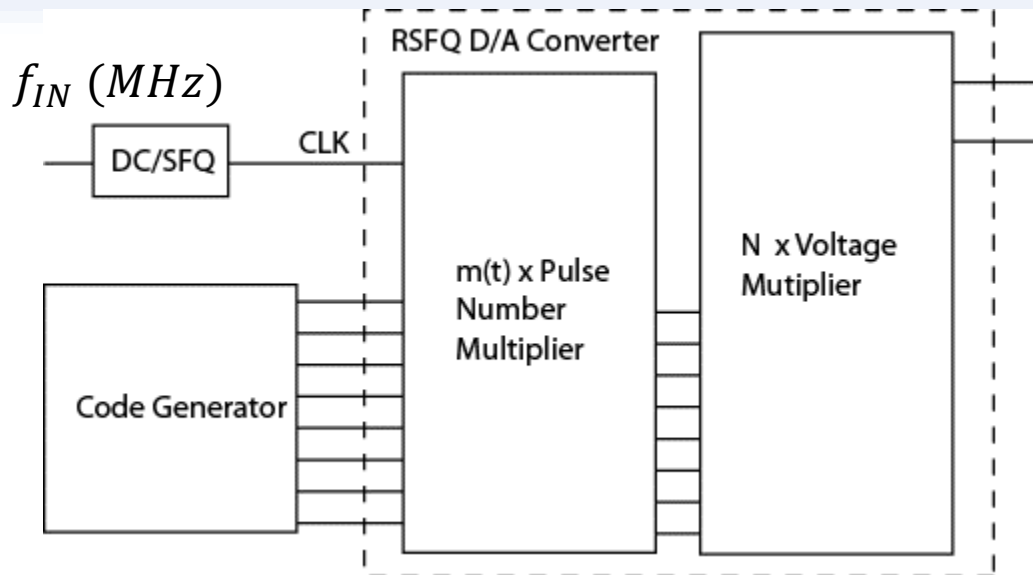
 
$$V_{out}(t) = \Phi_0 N \times m(t) \times f_{IN}$$



Several suggestions for SFQ-based-DACs

- **Frequency modulation of output SFQ pulse train**


V. K. Semenov (SUNY)

C. Hamilton (NIST).


- **Switching of multiplication factor in a voltage multiplier**

M. Maezawa, F. Hirayama, and M. Suzuki (AIST)

RSFQ circuits for waveform synthesis

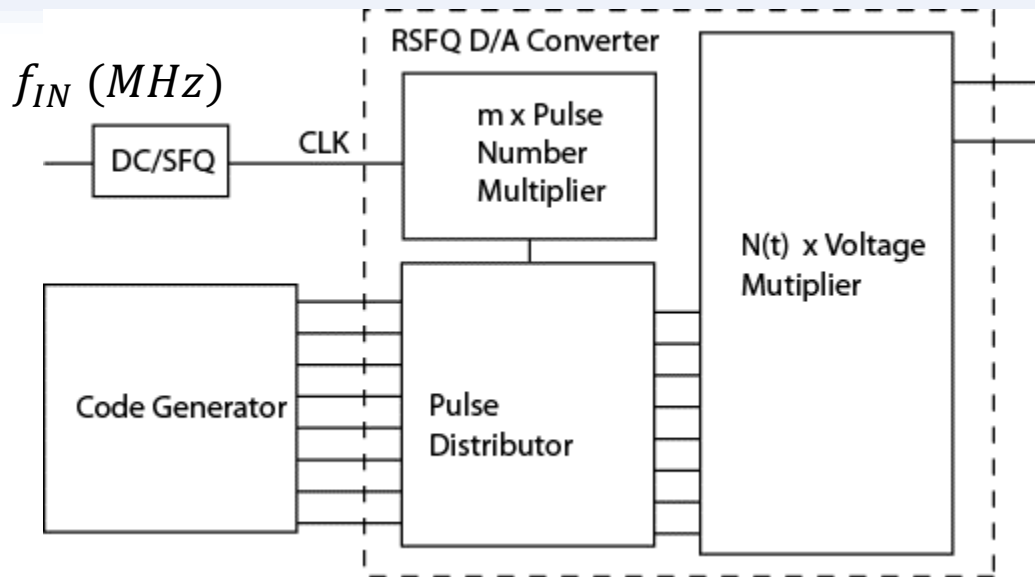
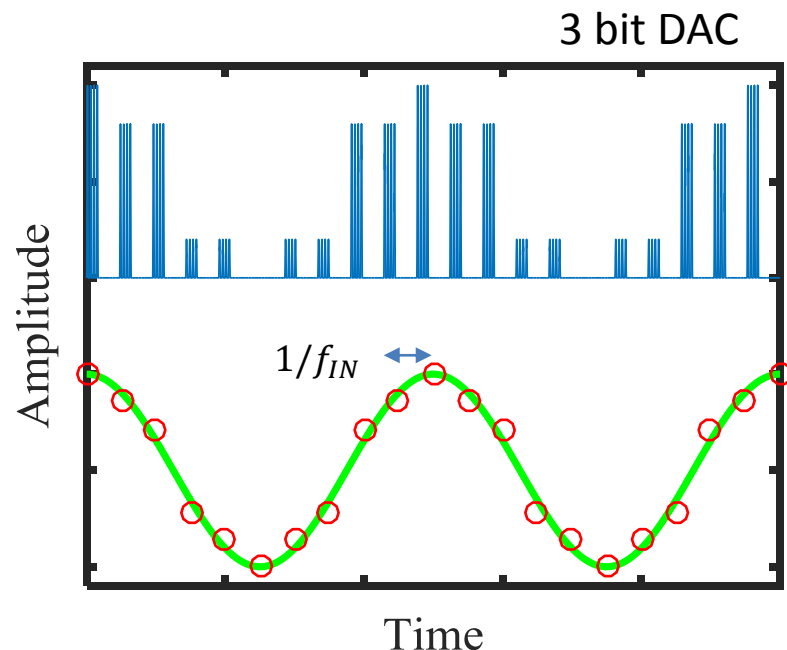
$$V_{out}(t) = \Phi_0 N(t) \times m \times f_{IN}$$



Several suggestions for SFQ-based-DACs

- Frequency modulation of output SFQ pulse train

V. K. Semenov (SUNY)

C. Hamilton (NIST).

- Switching of multiplication factor in a voltage multiplier

M. Maezawa, F. Hirayama, and M. Suzuki (AIST)