



CMS Upgrade Workshop –  **Fermilab** , 28th of October, 2009

DC-DC Conversion for the Pixel System at Phase I

Lutz Feld, Rüdiger Jussen, Waclaw Karpinski,
Katja Klein, Jennifer Merz, Jan Sammet

I. Physikalisches Institut B – RWTH Aachen University



Federal Ministry
of Education
and Research



RWTHAACHEN
UNIVERSITY

- Plans for Phase I pixel upgrade
- DC-DC Powering Scheme for the CMS Tracker

- Challenges
- Timeline
- Test System

- Choise of Converter ASICs
- Aachen Buck Converters with CERN-ASICs

- Efficiency Measurements
- Converter Noise Measurements (EMC)
- Infrared Camera Setup

- Implementation into the CMS pixel detector

- Summary




Pixels at Phase I: $2 \cdot 10^{34} \text{ cm}^{-2}\text{s}^{-1}$ | ~2014

- Detector will grow: 3 → **4 barrel layers**, 2 x 2 → **2 x 3 forward disks**
- More read-out chips per cable and PS, **total power consumption will increase**
→ Current in the cables to the Tracker will increase
- The upgraded pixel detector for Phase I cannot be powered with (modified) existing power supplies ⇒ Massive upgrade of PS would be needed
- DC-DC conversion scheme would allow to power the upgraded pixel detector with existing power supplies and cables
- Buck converters with conversion ratio $r = 2$ could be combined with light PS upgrade
→ First use case of DC-DC converters in the tracker

We will develop / test converters, based on ASICs of CERN group!

→ A new powering scheme is mandatory: **DC-DC conversion:**

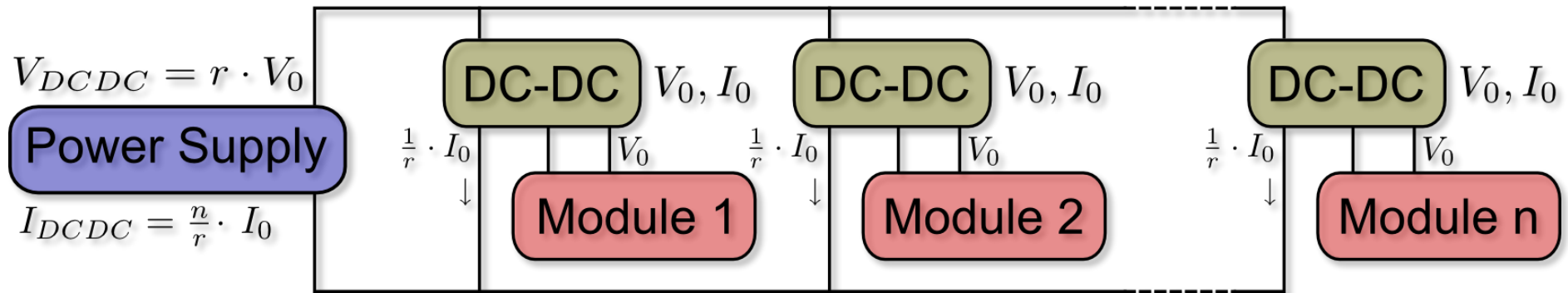Conversion ratio
 $r = V_{IN} / V_{OUT} (r > 1)$



Example for the Tracker:
 Cable losses: ($r = 2$, Efficiency $\eta = 80\%$)
 → without converter: $P_{Cable} = 30.0 \text{ kW}$
 → with converter: $P_{Cable} = 9.4 \text{ kW}$

- n modules are powered in parallel

- DC-DC Buck Converters:

- Convert higher input voltage to a lower output voltage
 “**Step-down Converter**” $U_{in} > U_{out} \rightarrow I_{in} < I_{out}$
- Losses without DC-DC: $P_{cab} = R \cdot I^2$
- Losses with DC-DC Conversion: $P_{cab,DCDC} = R \cdot (n \cdot I_0)^2 \cdot (1/r)^2 = R \cdot I^2 \cdot (1/r)^2$

- **High-voltage tolerant (up to 12V) and radiation-hard ASICs needed:**

- Up to $\sim 2-3 \cdot 10^{14}$ n/cm² (1MeV neutron equivalent) and ~ 150 kGy
→ **CERN AMIS2: Prototype** for radiation hard Converter [F. Faccio, S. Michelis, ...]

- **Efficiency:**

- $$\eta = \frac{P_{out}}{P_{in}} = \frac{V_{out} \cdot I_{out}}{V_{in} \cdot I_{in}} \quad (r \approx 2, I < 2.8A)$$

→ **Efficiency Measurements**

- **Inductors:**

- CMS Tracker: B=3.8T
→ Converters have to be magnetic field resistant
- Ferrite material saturates in a strong magnetic field
→ Use of air-core coils inevitable

→ **Magnetic Field Tests**

- **Converter switching noise ($f_{SWITCH} \sim$ MHz):**

- Additional source of noise in the system
- Has to be compatible with PSI46 ROC

→ **Spectrum Analysis (Converter Noise)**

→ **System Test Measurements (with pixel detector hardware)**

→ **Susceptibility Measurements**

- **Material budget:**

- Material budget of the new CMS pixel detector should decrease, even with converters

→ $\eta \approx 4 \leftrightarrow$ **uncritical**

- **Space constraints:**

- Length = 3.2cm ; width = 2cm; height < 1.4cm

→ **Piggy-boards with board-to-board connectors**

- **Specific requirements:**

- Very fast load variations due to the orbit gaps. Long pixel cables and the CAEN A4603 modules
- Quantity → 944 pieces required for FPIX + BPIX; 1400 including spares and prototypes

→ **Stability Test System w/ switched load**

1st qrt.
2010

- Development and System Test of a (non rad-hard) converter
- Start with commercial converters to commission setup
- In time for the Phase I upgrade TDR

1st qrt.
2011

- Development and test of the final rad-hard converter (CERN Group has agreed to develop required ASIC)

1st qrt.
2012

- Pre-production of 100-200 of fully qualified converter boards

1st qrt.
2013


- Delivery of full quantity (1300 pieces) of fully qualified converter boards

Stability Test of the whole power supply chain:

Pulsed load that emulates the varying load condition in the pixel digital current due to the orbit gaps (3 μs every 90 μs): $I_{\text{DIG}}(L) = 1.9\text{A} + L \cdot 0.4\text{A} / 10^{34}\text{cm}^{-2}\text{s}^{-1}$ for 4 pixel modules



 System Test with several pixel modules to fully qualify the converters



Components:	Quantity:	Origin:	Status:
CAEN SY1527 Mainframe	1	CERN Pool	in Aachen
CAEN Branch Controller	1	PSI	at CERN
CAEN EASY 4000 Crate	1	PSI	at CERN
CAEN A4603 PSM	1	PSI	not modified yet
CAEN Backboard	1	PSI	at CERN
48 V AC-DC	1	CERN Pool	in Aachen
50 m LIC Cable	1	PSI	in Aachen
Converter Prototypes with AMIS2 chip	5	Aachen	in Aachen
Motherboard	1	Aachen	under development
Load Box	1	Aachen	under development
Pixel Modules	4	PSI	at CERN
Read-out System	1	PSI	at CERN

Modification has to be done by CAEN:

Channel	1	2	3	4
Vset:	1.8 ÷ 3 V	1 ÷ 2.3 V	0 ÷ -600 V	0 ÷ -600 V
Vmax software:	1.8 ÷ 3 V	1 ÷ 2.3 V	0 ÷ -600 V	0 ÷ -600 V
Vset / Vmax sw resolution:	5 mV	5 mV	100 mV	100 mV
Vconn:	Up to 7 V	Up to 5.8V	N.A.	N.A.
Vmon Resolution:	5 mV	5 mV	100 mV	100 mV
Vconn Resolution	5 mV	5 mV	N.A.	N.A.
Iset:	0 ÷ 13 A	0 ÷ 6 A	0 ÷ 20 mA	0 ÷ 20 mA
Iset / Imon Resolution: ¹	10 mA	10 mA	1 μA	1 μA

Increase Vconn to ~10V

Increase Vset to ~8V for sensing at converter input

Adapt regulation to negative impedance load

Modification is organized by W. Bertl:

→ A modified CAEN A4603 Power Supply will be available in December




Choice of Converter ASIC

- Reminder: We started with commercial converters to commission set-up and took reference data
- Developed of radiation hard converters using a custom ASIC developed by F. Faccios group at CERN
- 2 different rad-hard technologies have been identified by CERN group
→ 3 different ASICs produced:


AMIS I3T80, ON Semiconductor	AMIS1 – 1 st submission	→ Tested – low efficiency (understood); system tests showed unsatisfactory EMI behaviour (high noise level)
	AMIS2 – 2 nd submission	→ ASICs delivered to CERN and after packaging to Aachen → Converter boards have been produced → Repeat system tests, efficiency measurements,
SGB25V GOD, IHP Frankfurt/Oder	IHP1 – 1 st submission	→ Radiation hardness of LDMOS transistors proven (F. Faccio, S. Michelis, ..) → 1 st submission: ASICs have been delivered to CERN, (re-)processing problems
	IHP2 – 2 nd submission	→ 2 nd run will be in January 2010 – Chips available May 2010

- Package: QFN48 (7mm x 7mm)
- No on-chip protection (over-V, over-I, over-T)
- Tested up to 300 Mrad = 3000 kGy with only 2% efficiency loss (after annealing) (→ backup slides)
- Integrated feedback loop with bandwidth of 20kHz
- Internal voltage reference
- Lateral HV transistors are used as power switches
- Noise and efficiency on upcoming slides

AMIS2 – Picture:

 


AMIS2 – Pinout:

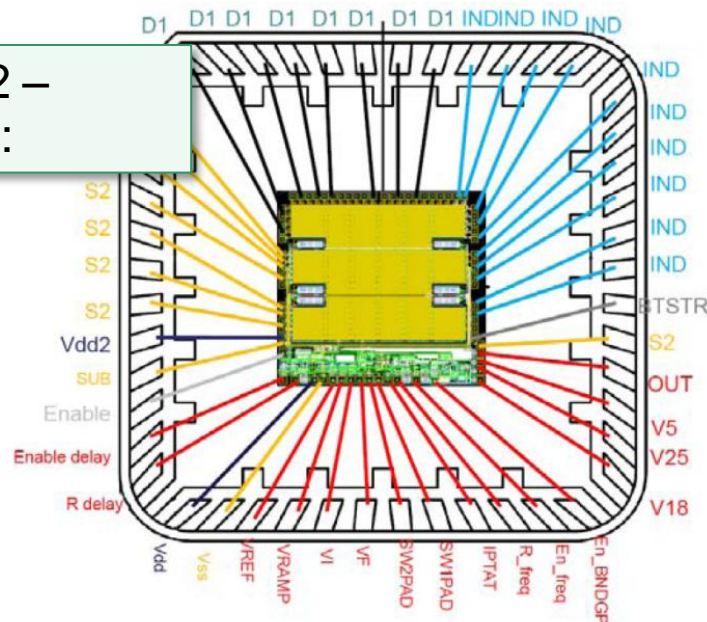

- Most chips will be delivered with a smaller package: QFN32 (5mm x 5mm)
- Delivery date not yet known!

We observed some problems with this chip (thermal instability, regulation problems) so we cannot use this chip for the 1st milestone in 2010

Picture:

 

PCB:

2 copper layers a 35 μ m
FR4 1mm
 $V = 19 \times 30 \text{mm}^2 \times 10 \text{mm}$
 $m = 2.5 \text{g}$


Chip: AMIS2 by CERN

$V_{IN} = 6-11 \text{V}(\text{rec.}) / 12 \text{V}(\text{max.})$
 $I_{OUT} < 3 \text{A}$
 $V_{OUT} = 3.3 \text{V}$ (but also 1.2V, 1.8V, 2.5V, 5V)
 $f_S = 600 \text{kHz}..3 \text{MHz}$

External air-core inductor:

Custom-made toroid, $\varnothing \approx 6 \text{mm}$,
height = 7mm, $L = 550 \text{nH}$, $R = 80 \text{m}\Omega$

Schematic:

 


Input and output π -filters


$L = 12.1 \text{nH}$, $C = 22 \mu\text{F}$

Cooling contact

$$\eta = \frac{P_{out}}{P_{in}} = \frac{V_{out} \cdot I_{out}}{V_{in} \cdot I_{in}}$$

 


AMIS2-PIX; $V_{OUT} > 3.2V$

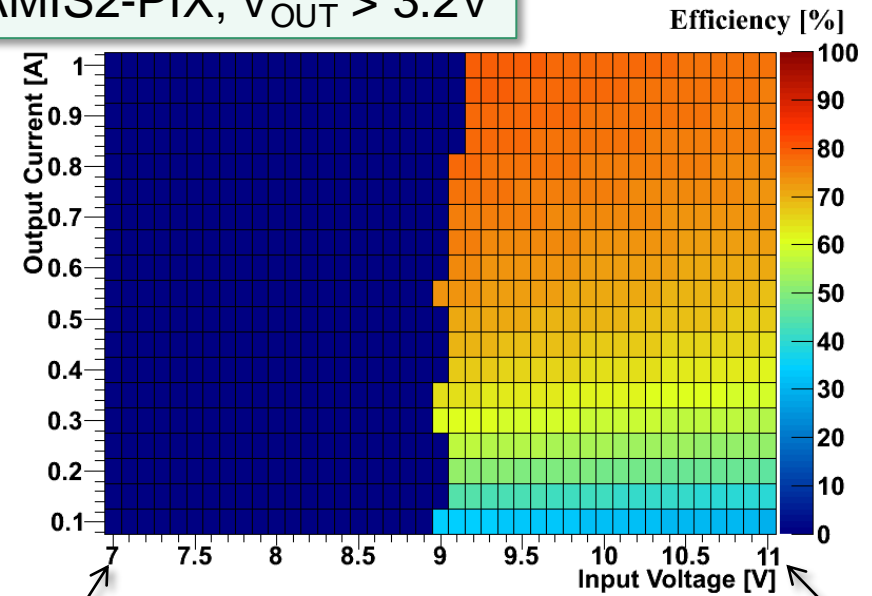

$r = 2.1$

$r = 3.3$



AMIS2-PIX: $V_{OUT} = 3.3V$

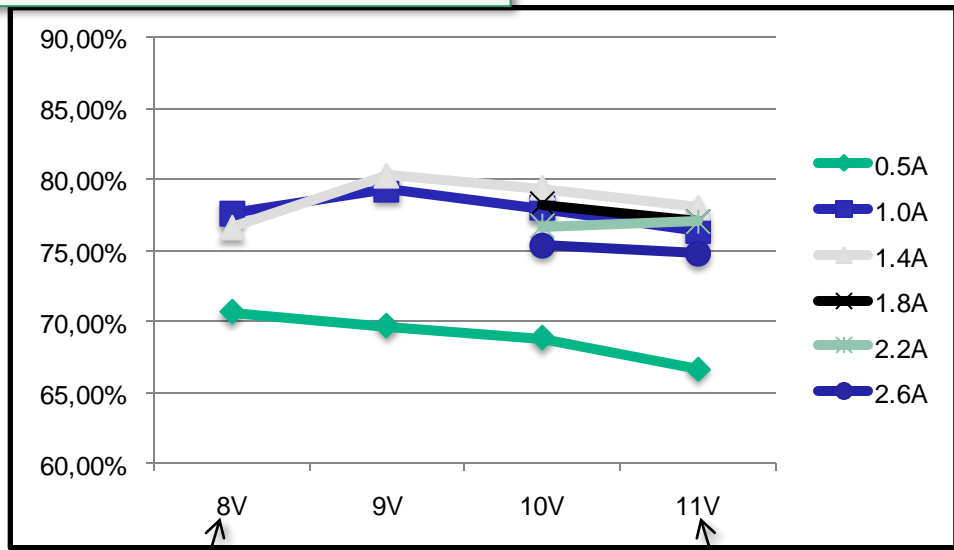

$r = 2.4$



$r = 3.3$

  - Inductor: Mini Toroid ($L = 600nH$)
- Efficiency is 75-80% for $I_{OUT} > 1A$
- Regulation does not work properly for low conversion ratios
- Poor thermal stability (bandgap reference, high I_{OUT})




LISN = Filter Network

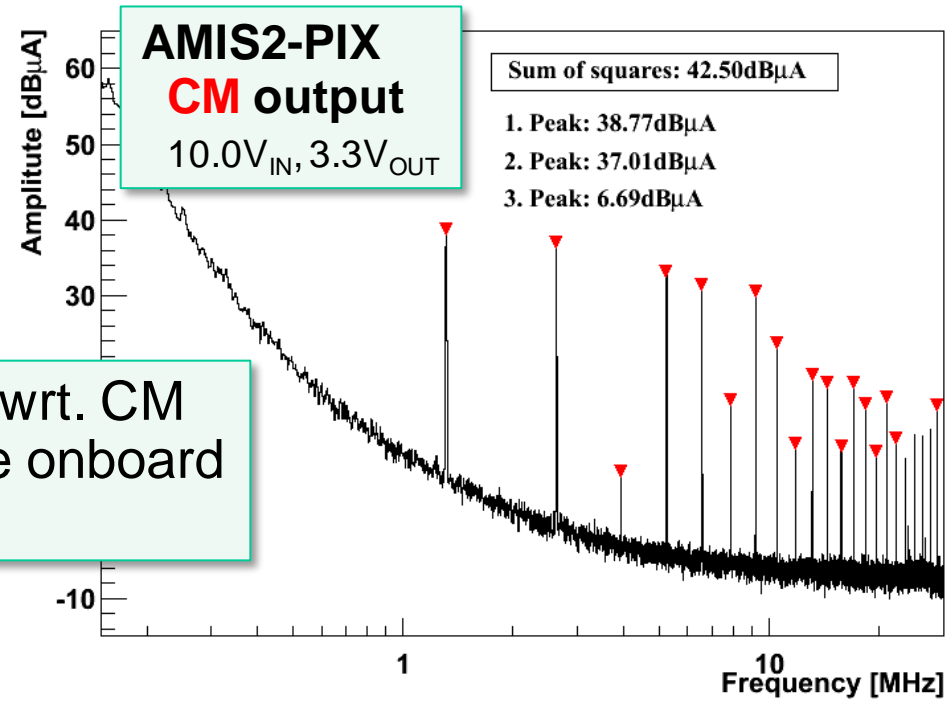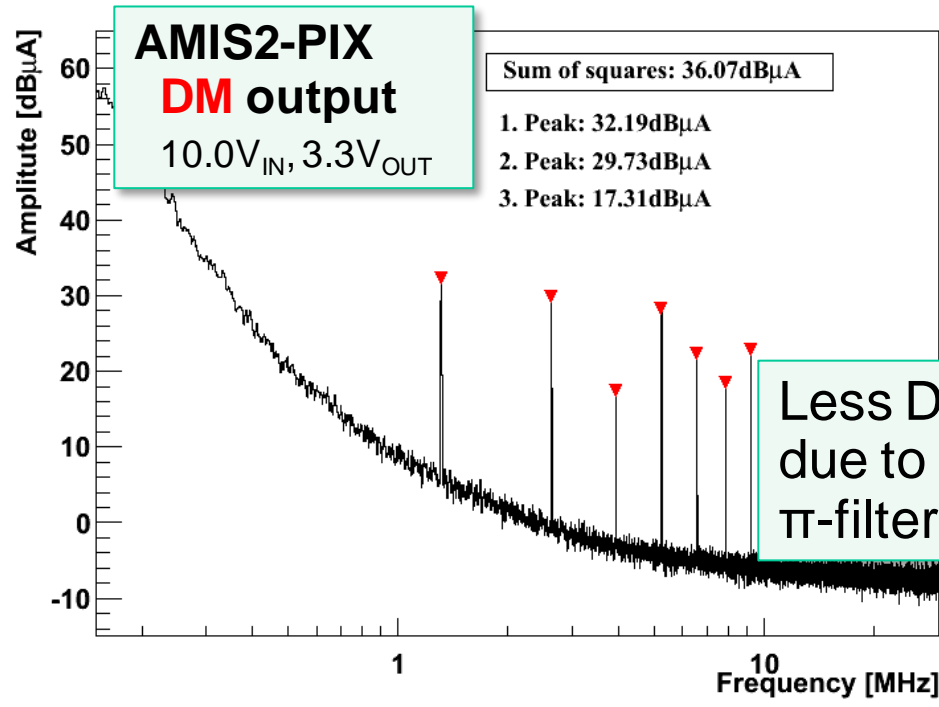- Suppresses external noise
- Avoids reflection of the noise currents inside the test system



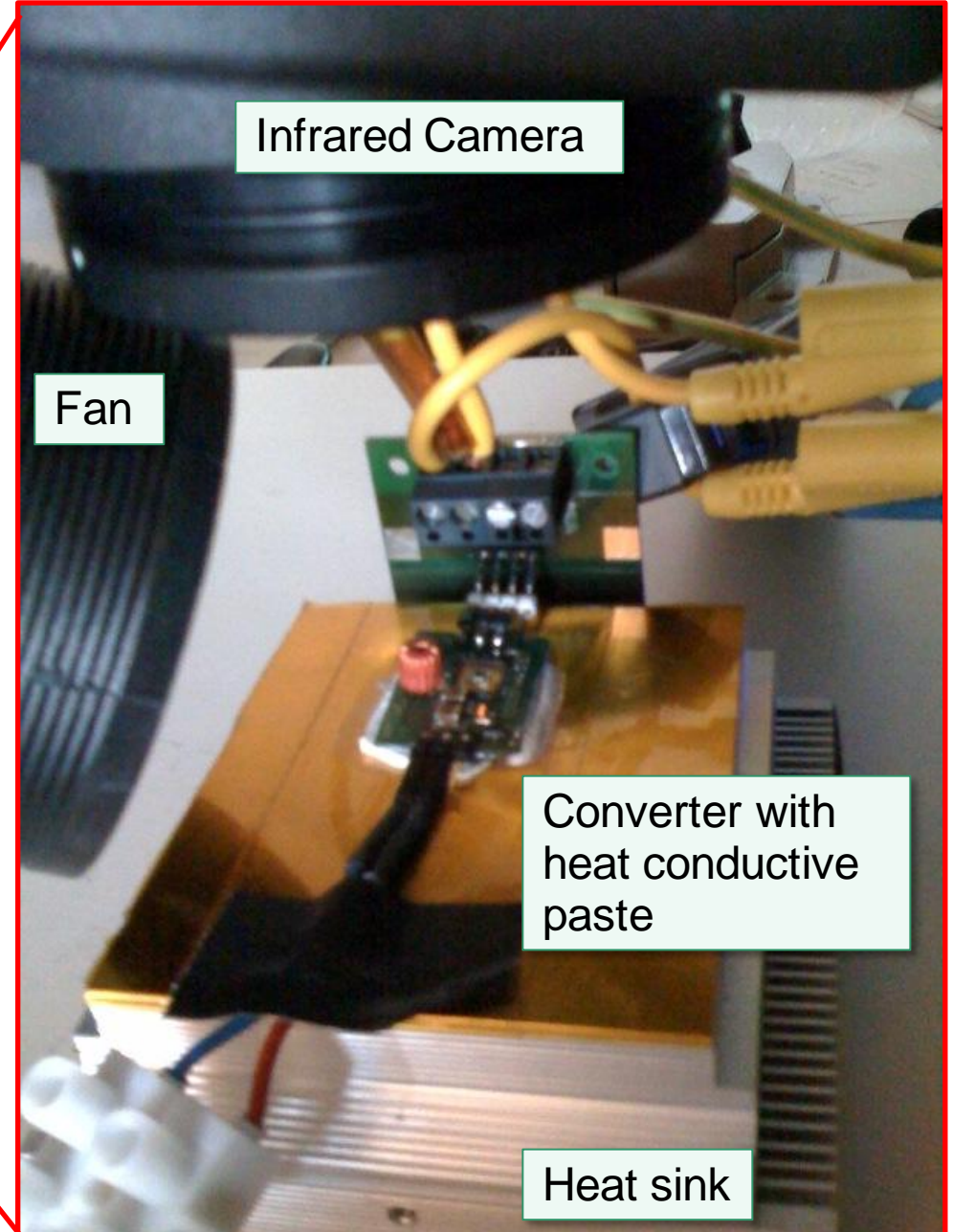Less DM wrt. CM due to the onboard π -filters



Converter w/ AMIS2:

- w/ fan and heat sink at room temperature
- $V_{IN} = 11V$
- $f_{SWITCH} = 1.27MHz$
- Load = 2A, stable
- $R_L = 80m\Omega$

AR04

Converter Avg: 38.3 C


Chip: 49.8 C

AR03

AR01


Coil: 55.2 C

AR02

 


Analysis Position Obj. Par Image Text comment

Label	Value [°C]	Min	Max	Max - Min	Avg	Stdev	Result	Expression
Image		26,3	62,8	36,5				
AR01		44,0	51,8	7,8	49,8	1,4		
AR02		43,5	62,8	19,3	55,2	4,8		
AR03		39,1	43,0	3,9	41,7	0,9		
AR04		28,8	62,8	34,0	38,3	6,0		

 

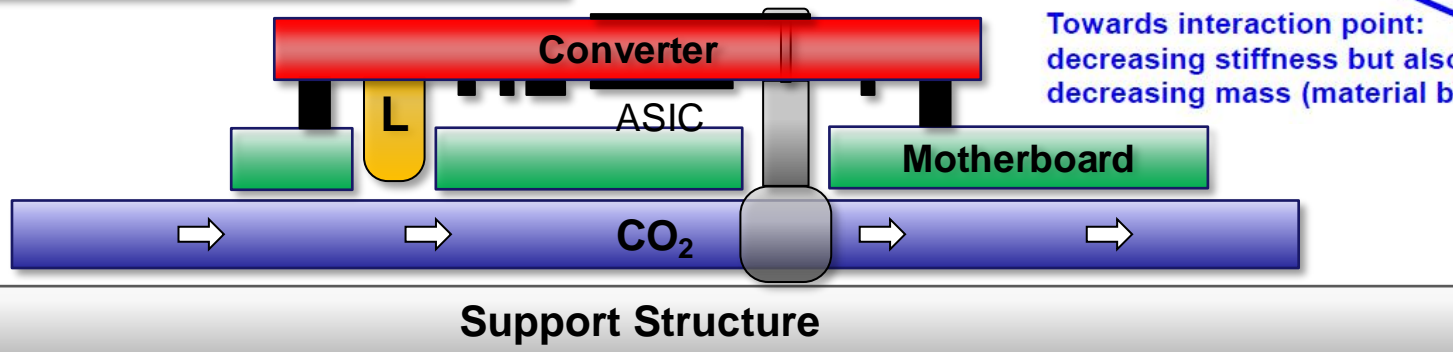→ BPIX needs 608 converters
 Volume available
 $\approx 12\text{cm}^3 / \text{converter}$






- The CMS Tracker plans to implement buck converters in the pixel system at Phase I (and in the outer tracker at Phase II)
- System test measurements with current pixel detector hardware will be performed in Aachen. Check converter behaviour under fast load variations and possible interference with CAEN power supply
- Buck Converters with ASICs from CERN have been developed
- PCBs are equipped with small, low-mass $0.6\mu\text{H}$ air-core toroids with low R_L and π -filters on the in- and output of the converter
- The efficiency is up to 80%. Impact of emitted noise has to be tested with pixel test system
- We also develop new Converters with commercial Chips (Enpirion 5336QI) for cross checking the test system
- AMIS2 Chip does not yet fulfill the Phase I specifications (Conversion ratio, thermal instability, ..) so we cannot use this specific chip for the 1st milestone in 2010




BACKUP – SLIDES

Specification	
radiation level	up to $2\text{-}3 \times 10^{14} \text{ cm}^{-2}$ (fast hadrons) up to 150 kGy (?)
magnetic field	4 T
voltage conversion	6.6 V \rightarrow 3.3 V (2:1)
current capabilities	< 2.8 A
volume	length = 3.2cm , width = 2cm, height < 1.4cm
form factor	piggy-board with board-to-board connectors
material budget	uncritical
output ripple	compatible with PSI46 ROC
specific requirements	<ul style="list-style-type: none"> • behaviour for very fast load variations due to the orbit gaps • stability of operation together with long pixel cables and the CAEN A4603 modules
quantity	944 pieces required for FPIX + BPIX 1400 including spares and prototypes

Efficiency vs TID

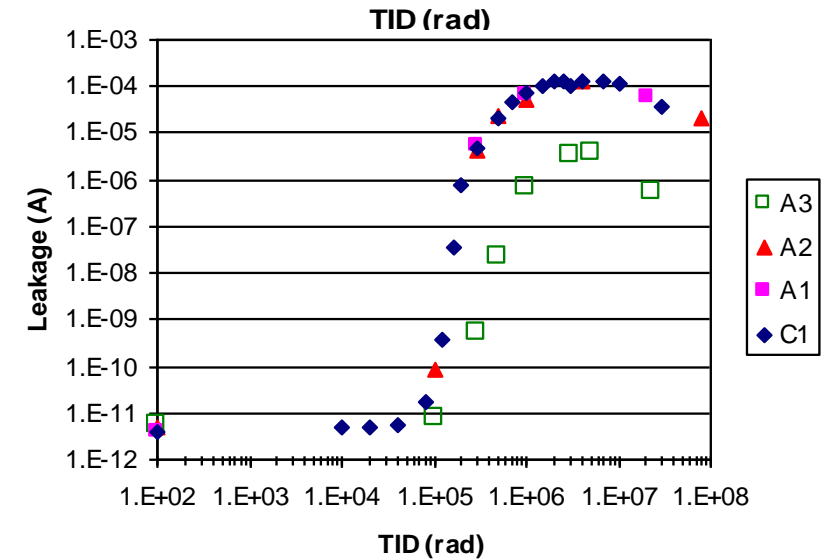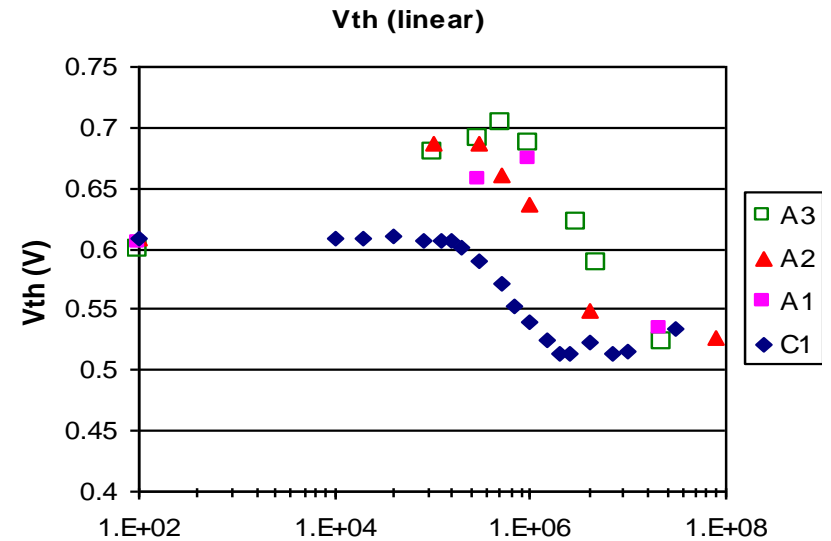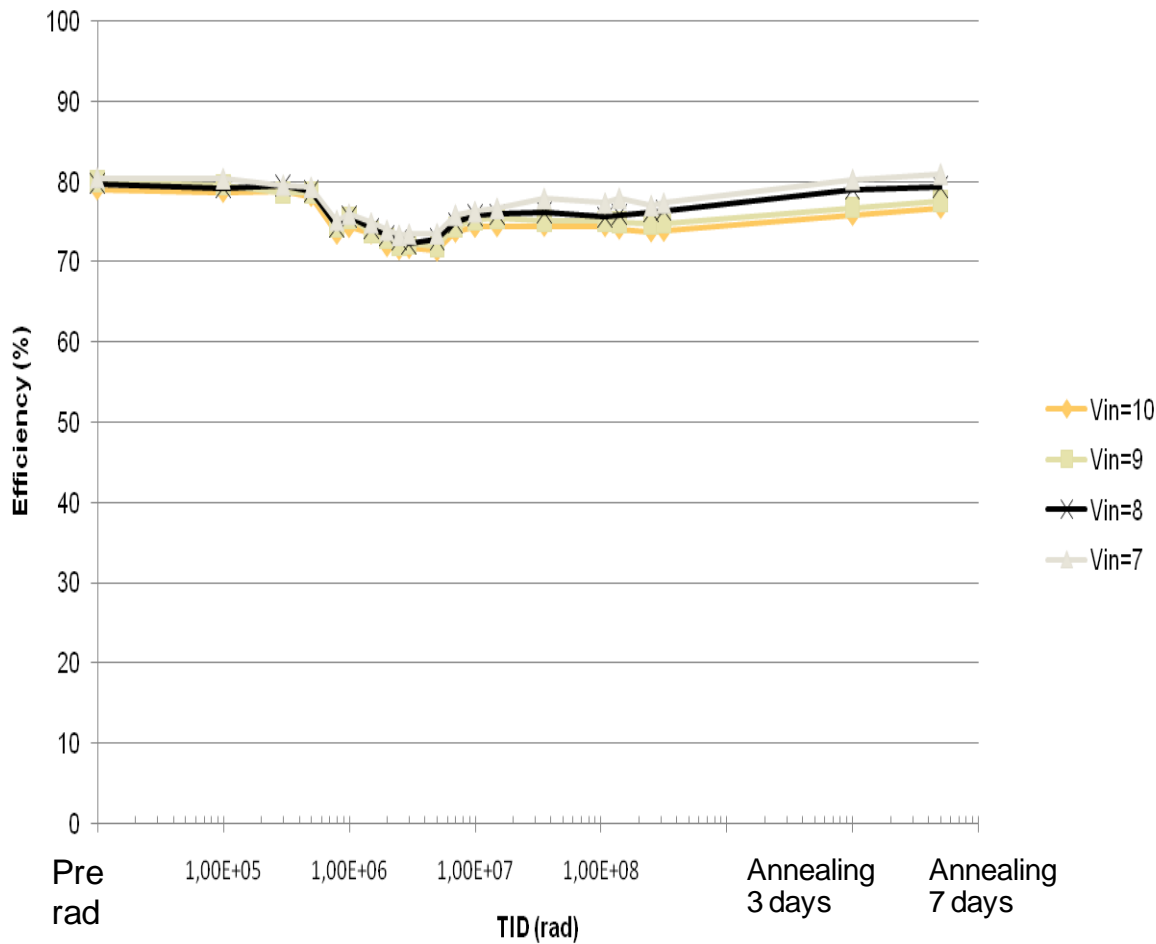

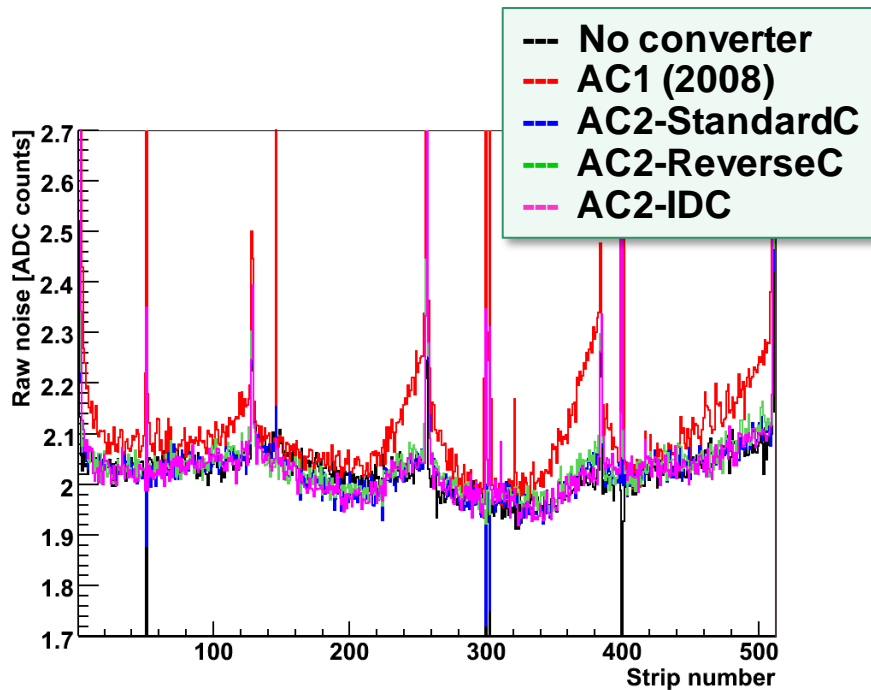
X-ray radiation tests shows a decrease of the efficiency mostly due to the radiation induced leakage current, compensated by the threshold voltage shift






Sensitive variable chosen for all following comparisons:

$$N = \sqrt{N_1^2 + N_{512}^2}$$

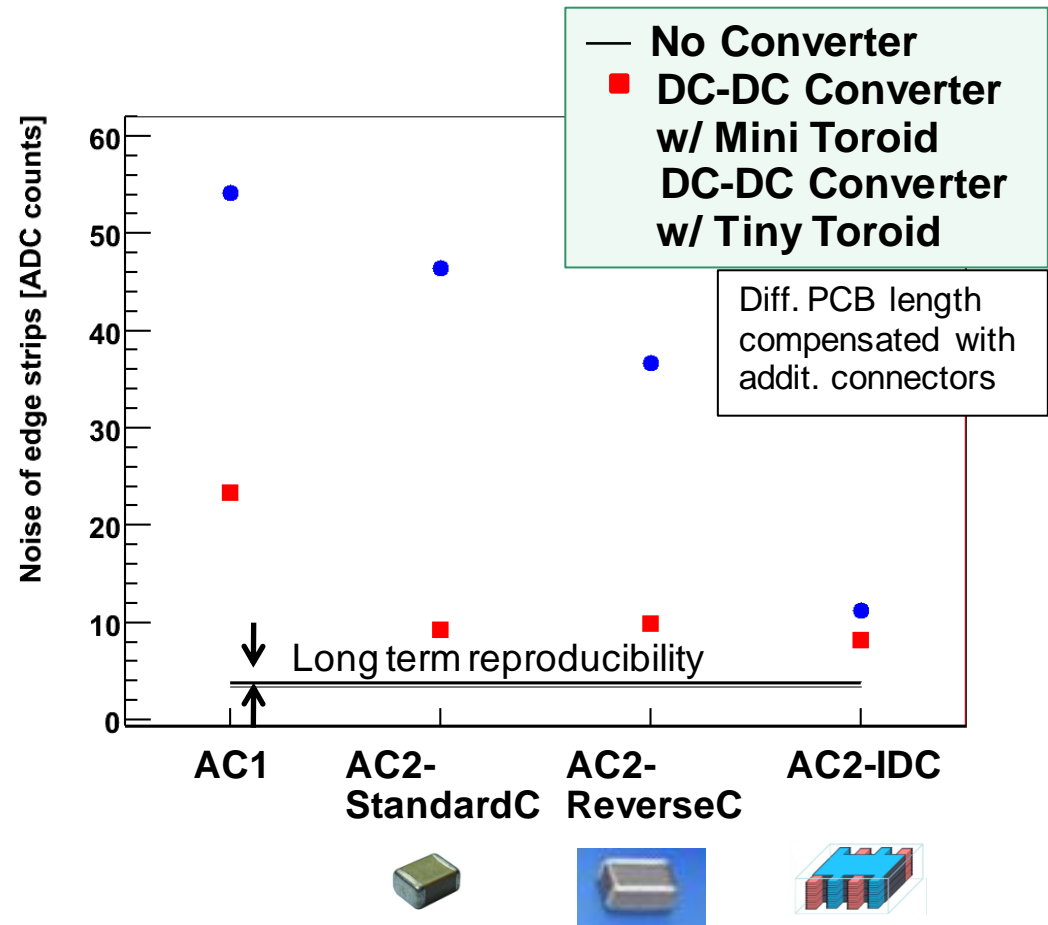- Lower noise than with 2008 boards
- Mini Toroid shows lower noise and 5-30% higher efficiency ($\Delta I_L = V_L \cdot t_{ON} / L$)
- Boards with IDCs perform best



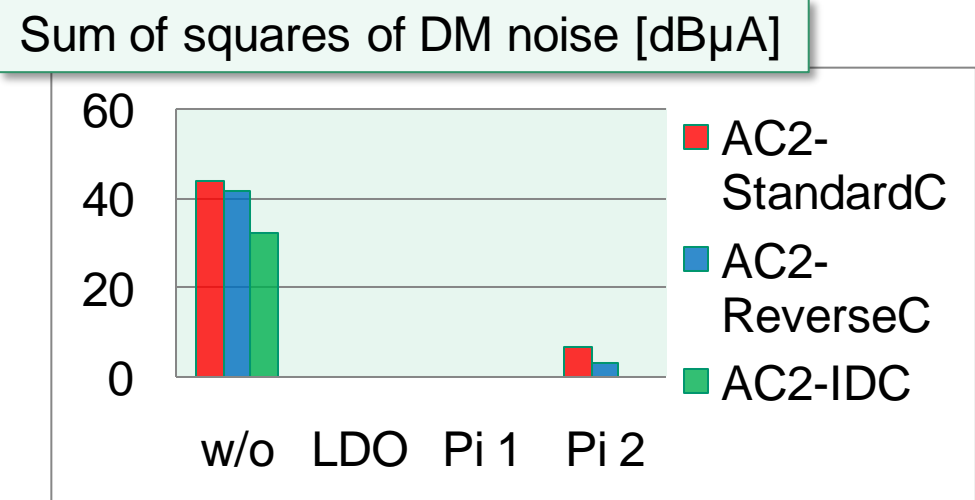 
 


- π -filters are as effective as LDO regulator!
- AC2-IDC performs “worst” with filters/LDO; likely reason: higher CM

π -Filters vs. LDO: What about Efficiency?

Ratio of the efficiency with LDO / π -Filter and the efficiency without LDO / π -Filter

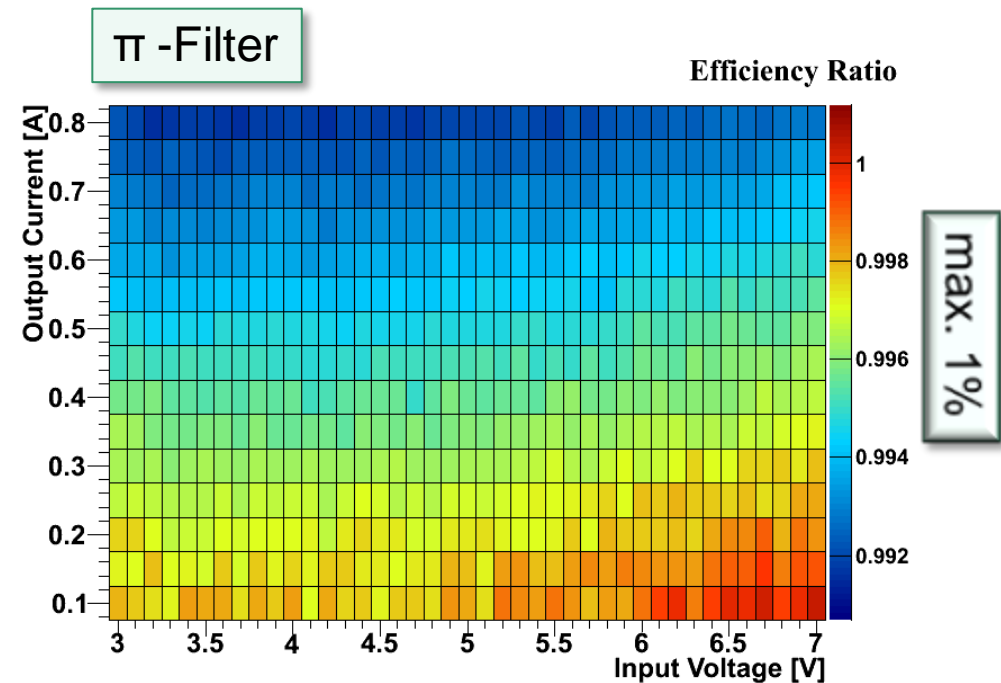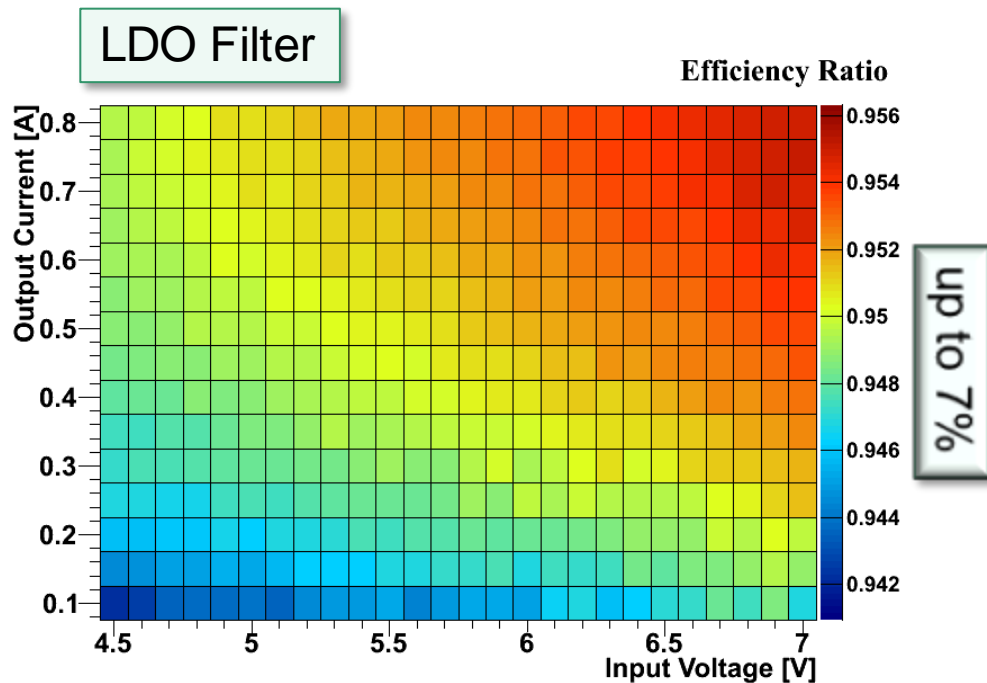→ was measured for all board types, filters and $V_{OUT} = 1.25V$ and $2.50V$;
e.g. standard capacitors, $1.25V$:



- Losses of up to 7% observed with LDO regulator (50mV drop out voltage)
- Losses with our π -Filters stay below 1%
- π -filter clearly preferred