

# IpGBT

## design and status

Szymon KULIS, CERN  
on behalf of the IpGBT design team

# IpGBT Design Team

---

## Design team:

- CERN: David Porret, Jose Fonseca, Ken Wyllie, Paulo Moreira, Pedro Leitao, Rui Francisco, Sophie Baron, Szymon Kulis, Daniel Hernandez
- AGH UST: Marek Idzik, Mirosław Firlej, Jakub Moroń, Tomasz Fiutowski, Krzysztof Swientek
- KU Leuven: Bram Faes, Jeffrey Prinzie, Paul Leroux
- UNL – FCT: João Carvalho, Nuno Paulino
- SMU Physics: Datao Gong, Di Guo, Dongxu Yang, Jingbo Ye, Quan Sun, Wei Zhou
- SMU Engineering: Tao Zhang, Ping Gui

## IP Cores:

- Czech Technical University Prague: Mirosław Havranek, Tomas Benka
- CERN: Stefano Michelis, Iraklis Kremastiotis, Alessandro Caratelli

# IpGBT: High Speed SerDes

- Data transceiver with fixed and “deterministic” latency both for up and down links.

- Down link:

- 2.56 Gb/s, FEC12
- E-links outputs:
  - Up to 16
  - Data rates : 80/160/320 Mb/s
- E-link clocks outputs:
  - Up to 28
  - Clock frequencies: 40/80/160/320/640/1280 MHz
- Phase aligned clocks – 4 channels
  - 50 ps resolution
  - Clock frequencies: 40/80/160/320/640/1280 MHz

- Up link:

- 5.12 Gb/s or 10.24 Gb/s, FEC5 or FEC12
- E-Links inputs:
  - Up to 28
  - Data rates 160 /320 / 640 / 1280 Mb/s


- Power dissipation:

- Target:  $\leq 500$  mW @ 5.12 Gb/s
- Target:  $\leq 750$  mW @ 10.24 Gb/s

- Compact package

- Radiation tolerance:


- 200 Mrad
- SEU robust

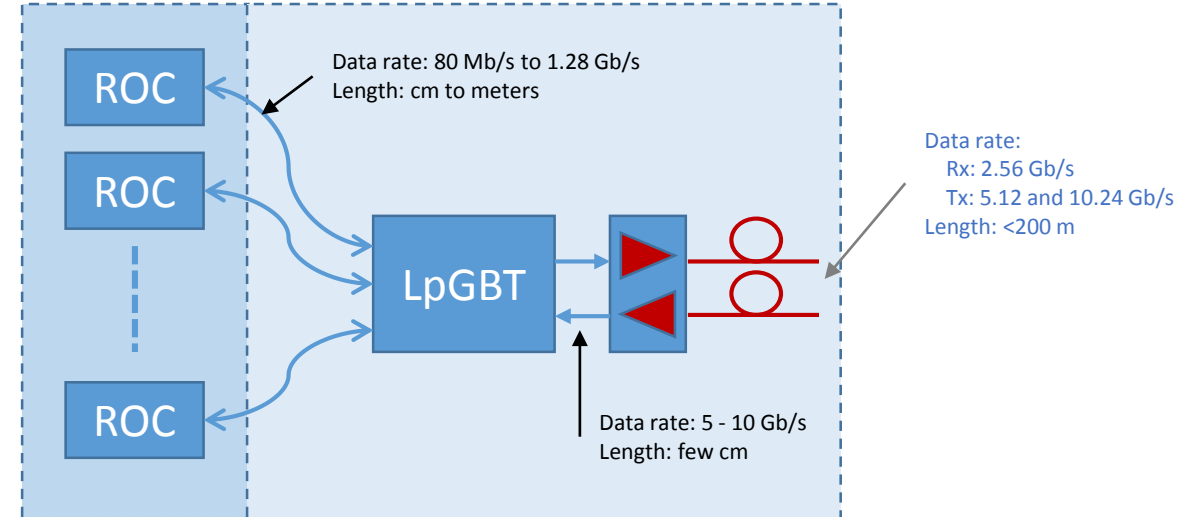

## Agenda


- IpGBT – architecture
- Architecture and performance of (selected) blocks
- Design status
- Package / PCB

# IpGBT: Block Diagram (simplified)

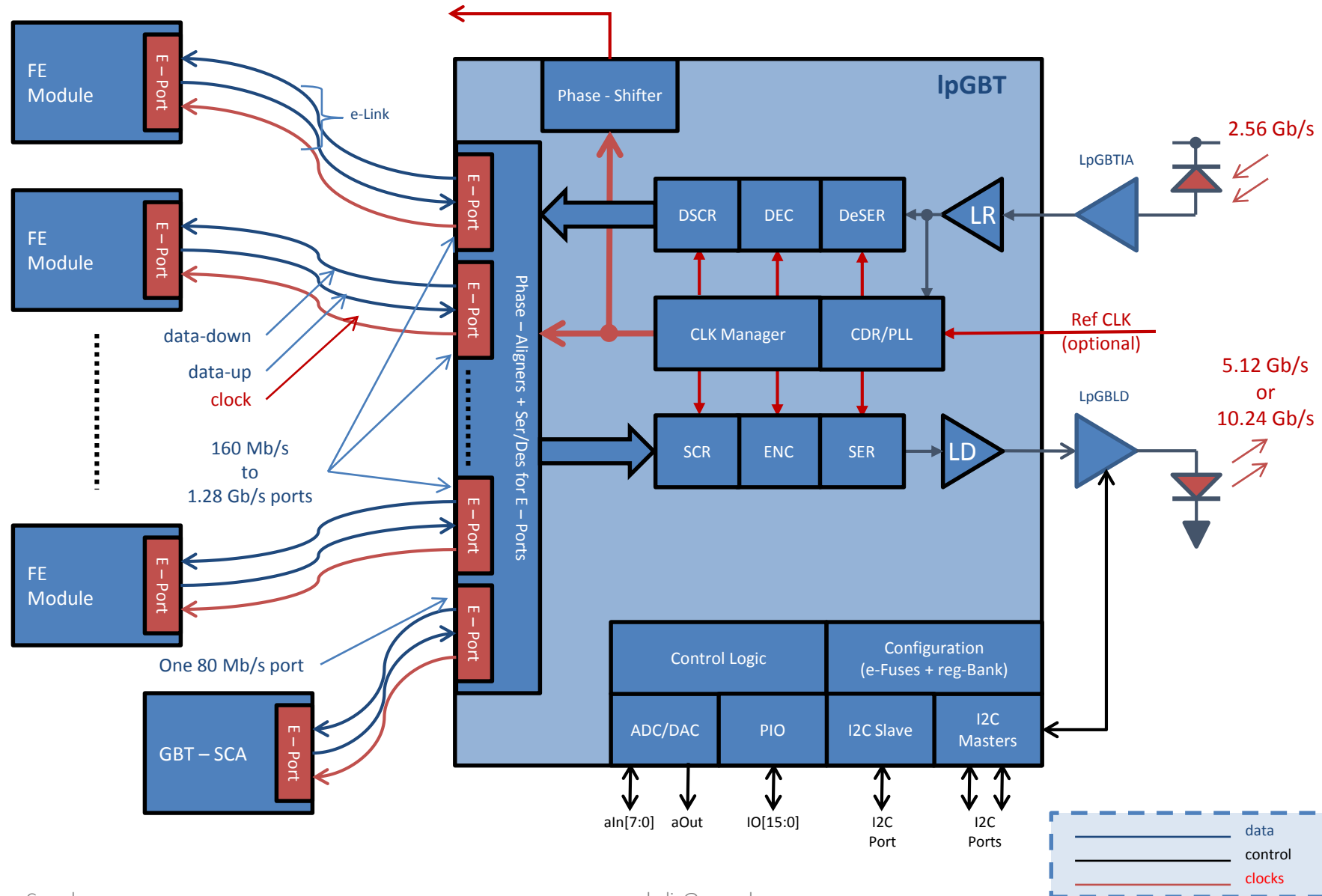

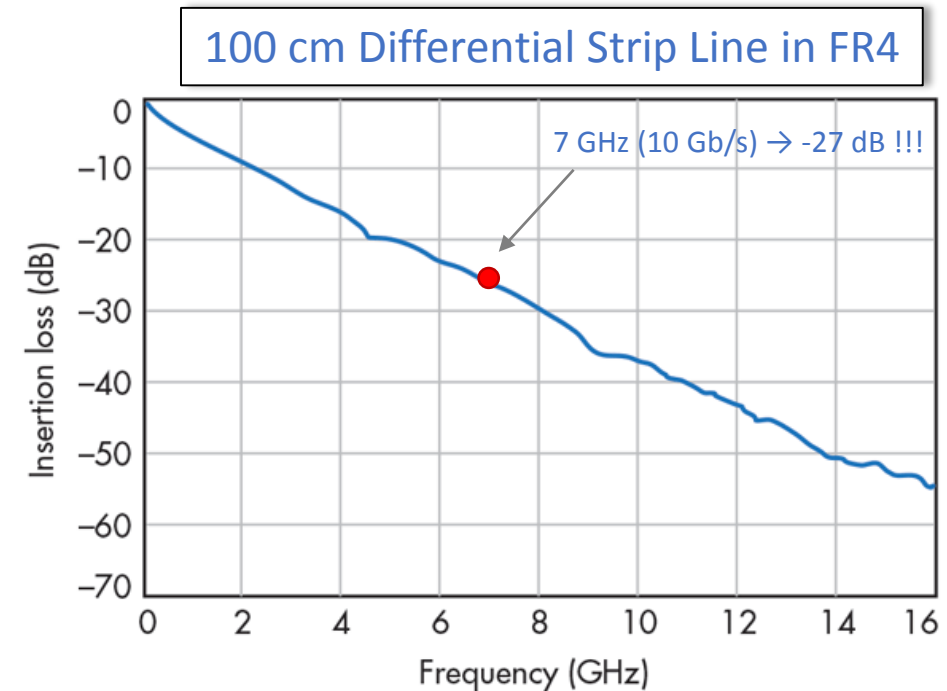
# Foreword: Transmission line, Equalization and Pre-Emphasis


- Bandwidth of transition lines used in HEP is limited because of material budget constraints
- Both pre-emphasis and Equalization are attempts to restore the baseband signal spectrum
- Pre-emphasis (done at the transmitter):
  - Tries to generate a wave shape with an “exaggerated” spectral contents at the frequencies that are most attenuated by the channel [typically the high frequencies]
  - No degradation of the SNR
- Equalization (done at the receiver):
  - Amplifies more the high frequency contents of the spectrum than the low frequency. It is an attempt to achieve a combined response of the channel and equalizer that will approach a channel that has no inter-symbol interference
  - Degradation of the SNR
- Because of the SNR degradation resulting from equalization, the best approach is to combine pre-emphasis and equalization:
  - Enhance the transmitted high frequency content rather than do all the high frequency peaking at the receiver side



# IpGBT: Down link: Line receiver


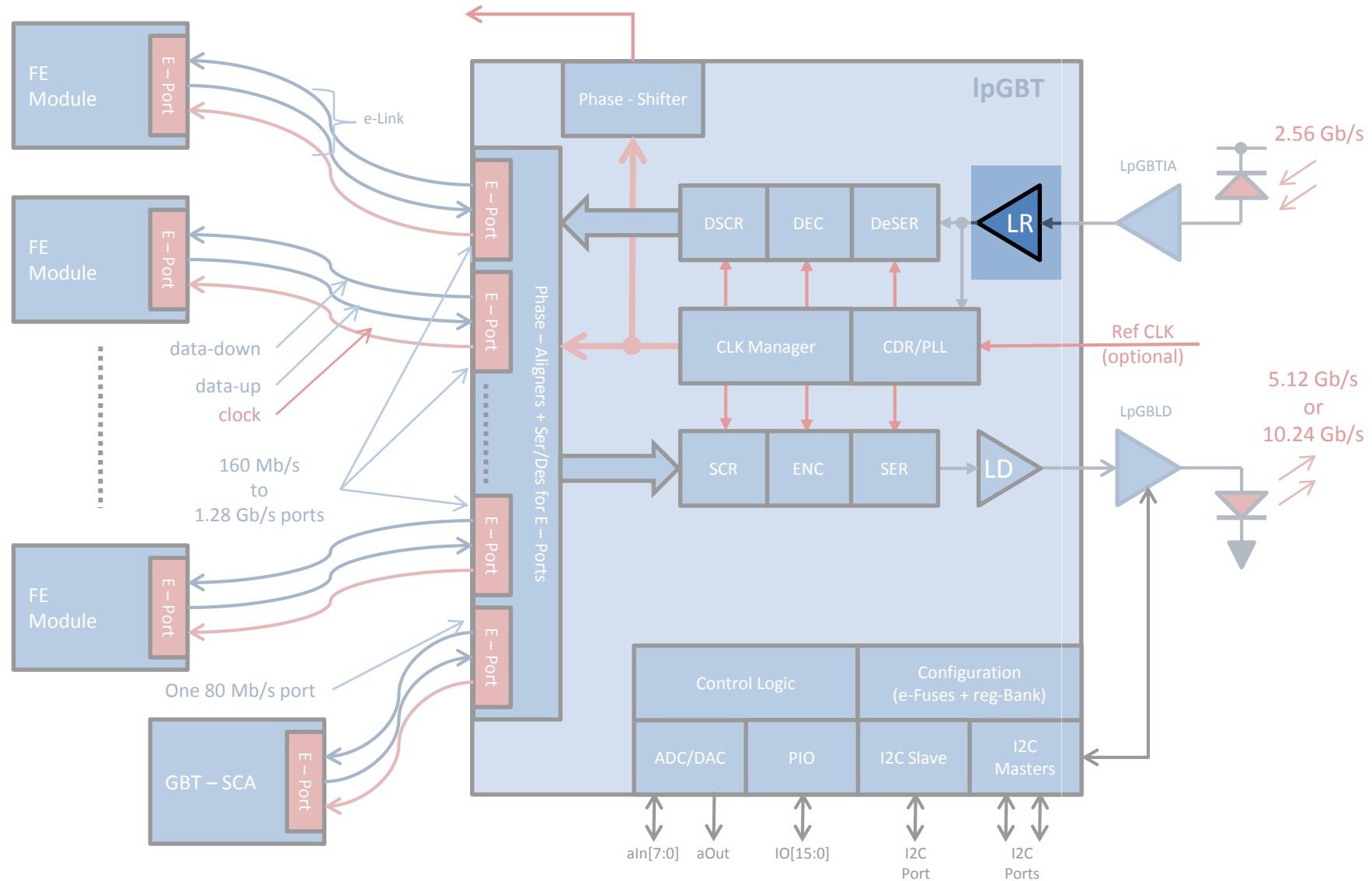

 
# IpGBT: Down link: Line receiver architecture (@2.56Gbps)




Four (independently controlled) equalizing stages allow to flexibly control the shape of the transfer function.

  - $f_z$  1<sup>st</sup> and 2<sup>nd</sup> stage: 81MHz – 758 MHz
- $f_z$  3<sup>rd</sup> stage: 237MHz – 3789 MHz
- $f_z$  4<sup>th</sup> stage: 355 – 5684 MHz



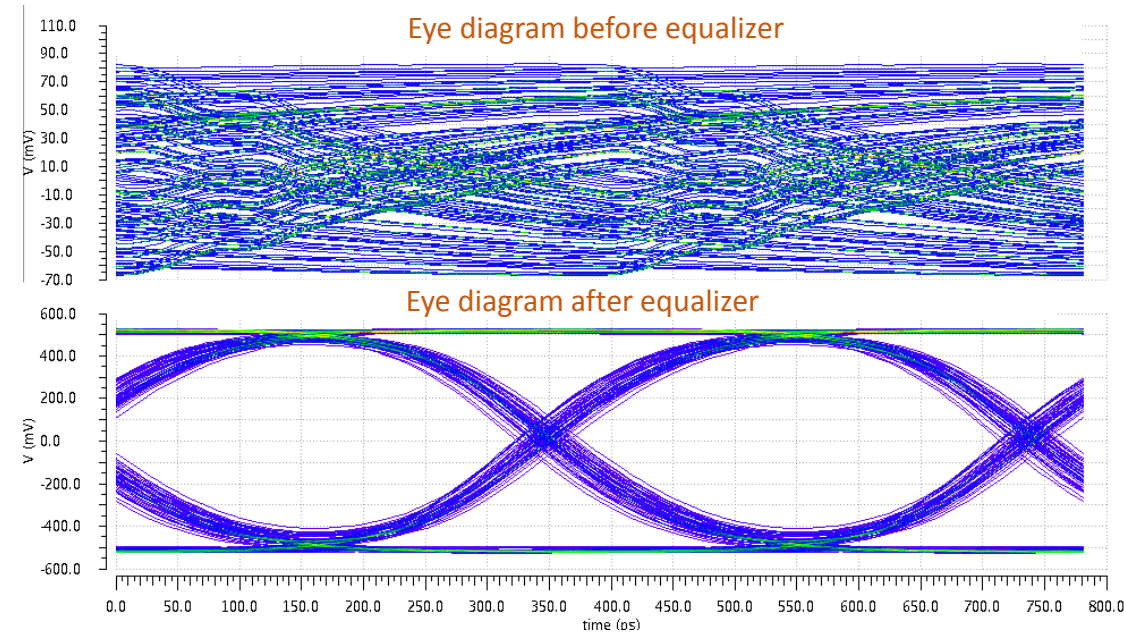
## 2.56Gbps after 75 cm low mass coaxial cable


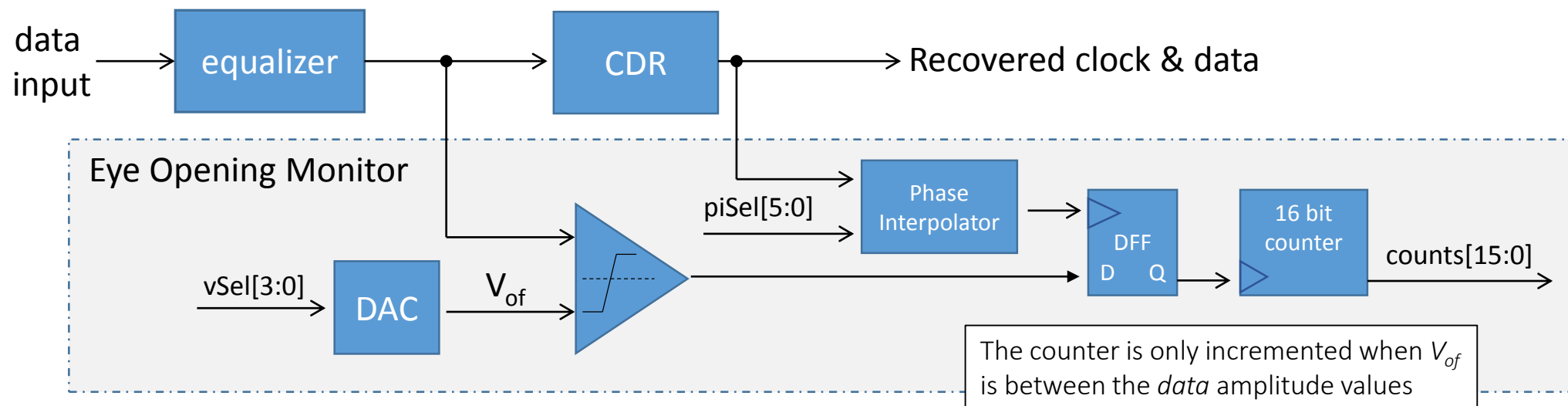
# IpGBT: Down link: Eye Opening Monitor architecture




- Goal: Monitor the opening of the received data eye diagram and tune the equalizer's settings
- Provides an "eye diagram picture" by using a "signal-scan" approach
- The scan is performed across the time (x-axis) and across the amplitude (y-axis), yielding a "signal density" per point
  - The input signal [data] is compared with a reference voltage " $V_{of}$ "
  - The comparator's result is sampled by the rising edge of a clock synchronous to the incoming data
  - The sampled result drives a ripple counter to accumulate statistics
  - The counter is enabled for a well defined period.





  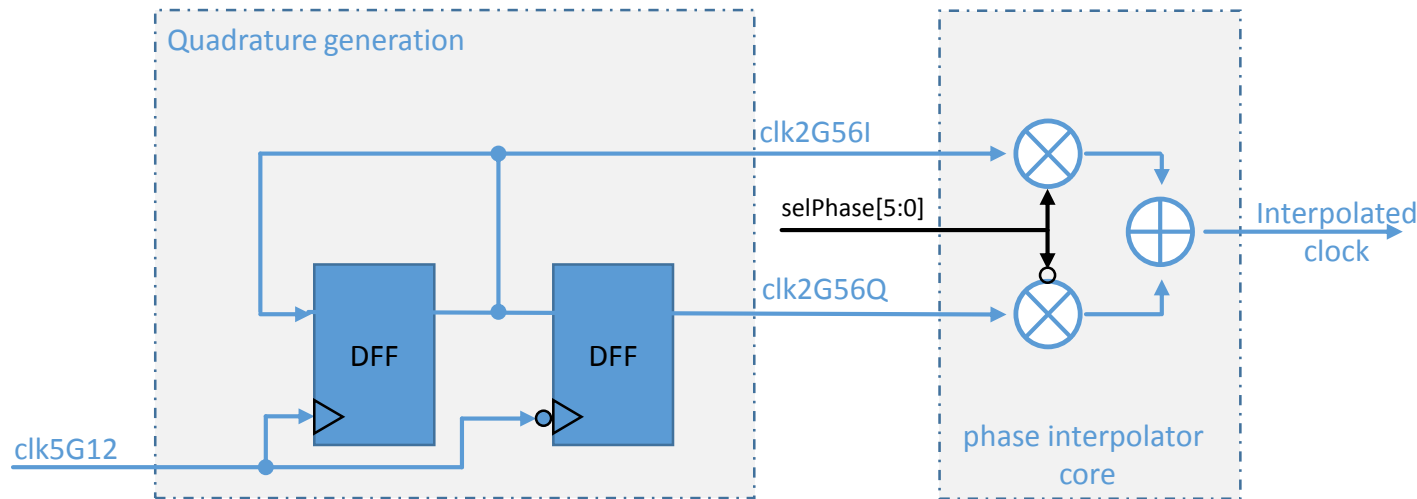
# IpGBT: Down link: Eye Opening Monitor

- Y-axis:
  - 5 bit resistive DAC
  - 31 points, step =  $\sim 20$  mV (covers from  $V_{DD}/2$  up to  $V_{DD}$ )
- X-axis:
  - Phase interpolator uses 5.12 GHz clock to generate in-phase I and quadrature Q clocks at 2.56GHz
  - 64 points, step =  $\sim 6.1$  ps in typical




# IpGBT: clocks manager

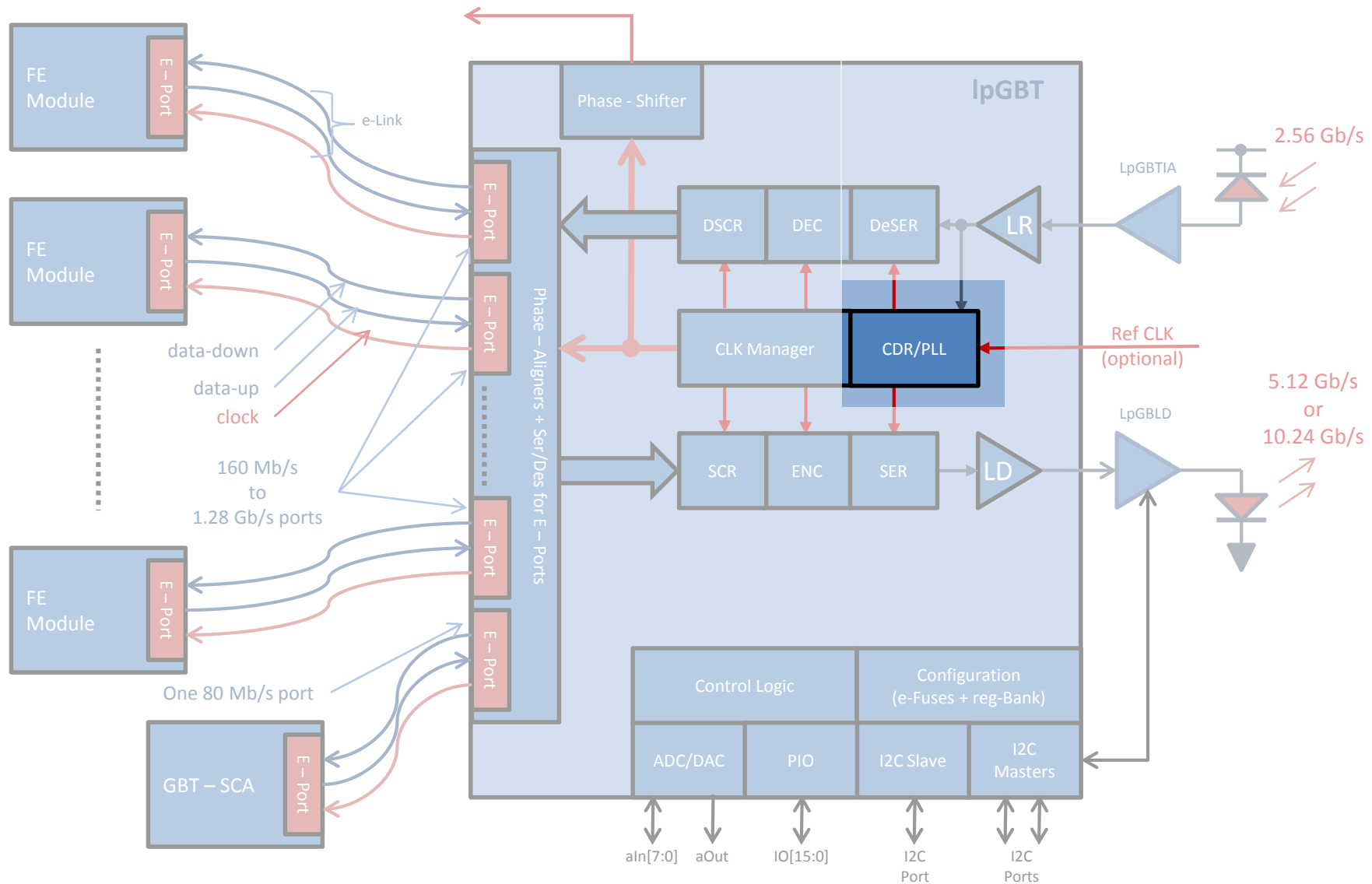


# Low jitter PLL: architecture matters

- Two PLLs working at 2.5 GHz, same circuits (power dissipation, loop dynamic) except the VCO:
  - LC VCO
  - Ring oscillator VCO
- Pre/post-rad jitter (rms):
  - LC: 0.3 / 1.0 ps
  - RO: 5.6 / 22 ps
- 600 Mrad + Annealing:
  - LC:  $\Delta f < 5\%$  (Passives set the frequency)
  - RO:  $\Delta f < 40\%$  (Actives set the frequency)


LC VCO

 


Ring oscillator VCO

 

Free running oscillation frequency



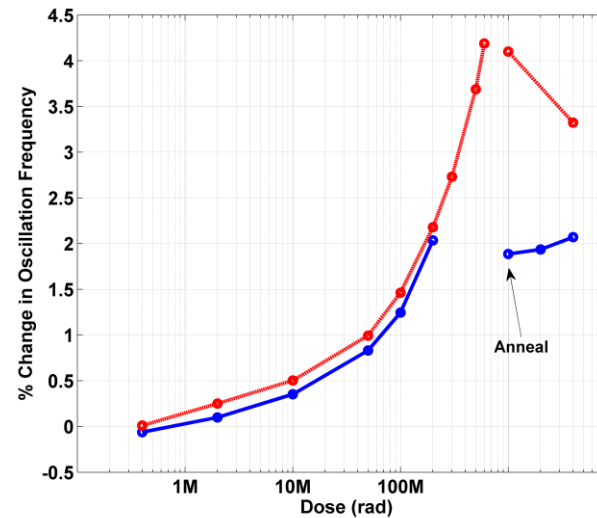


Free running oscillation frequency

 

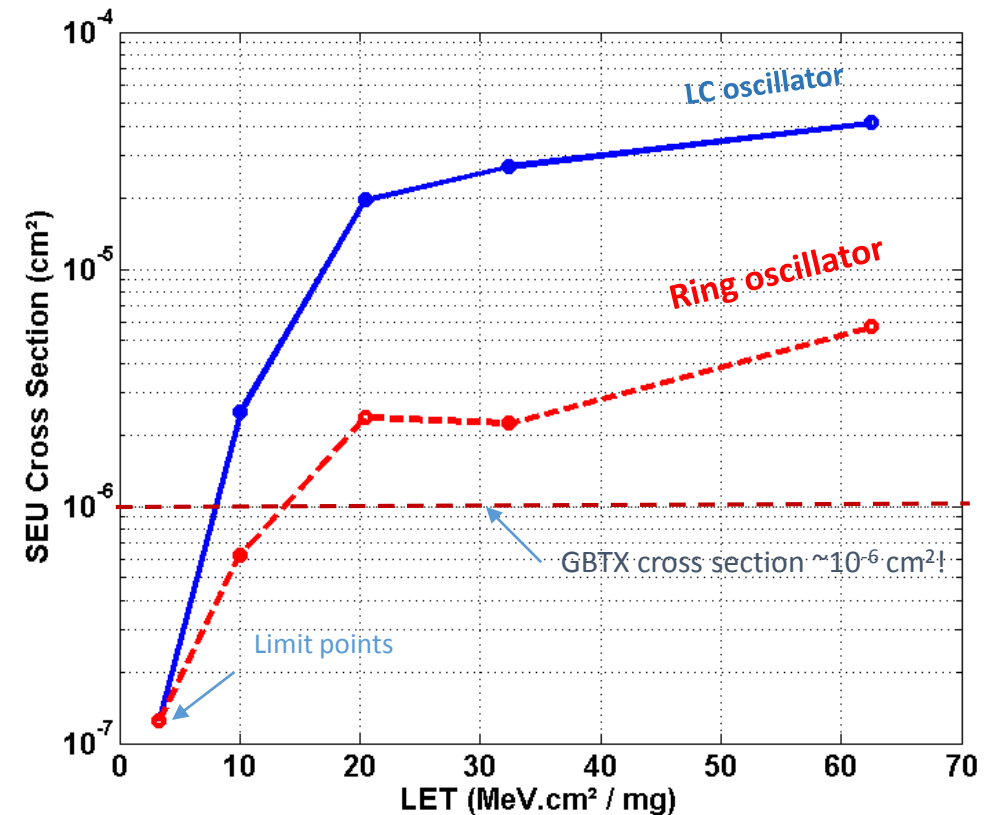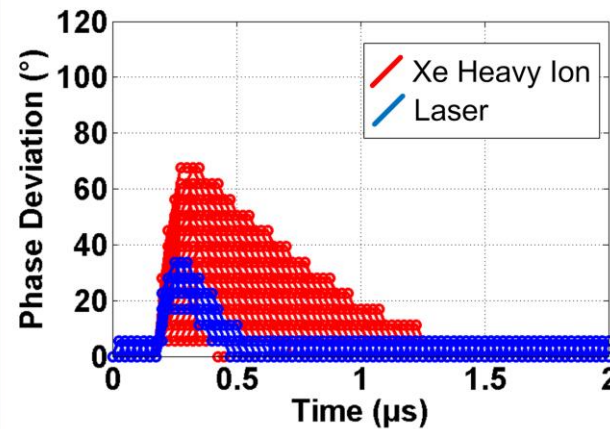 
# Low jitter PLL: architecture matters

- Heavy ion testing:
  - LET: 3.2 to 69.2 MeV.cm<sup>2</sup>/mg
- LC oscillator displays a significantly higher sensitivity than the ring oscillator!
  - Contrary to expectations!
- SEU Phase jumps (unlock):
  - Ring oscillator: both polarities
  - LC: Mainly positive
- Two-Photon Absorption (TPA) laser tests point to the VARACTOR as the main culprit!
  - Total cross section of the LC-oscillator is  $4 \cdot 10^{-5} \text{cm}^2$  from which 70% is contributed by the varactor area!



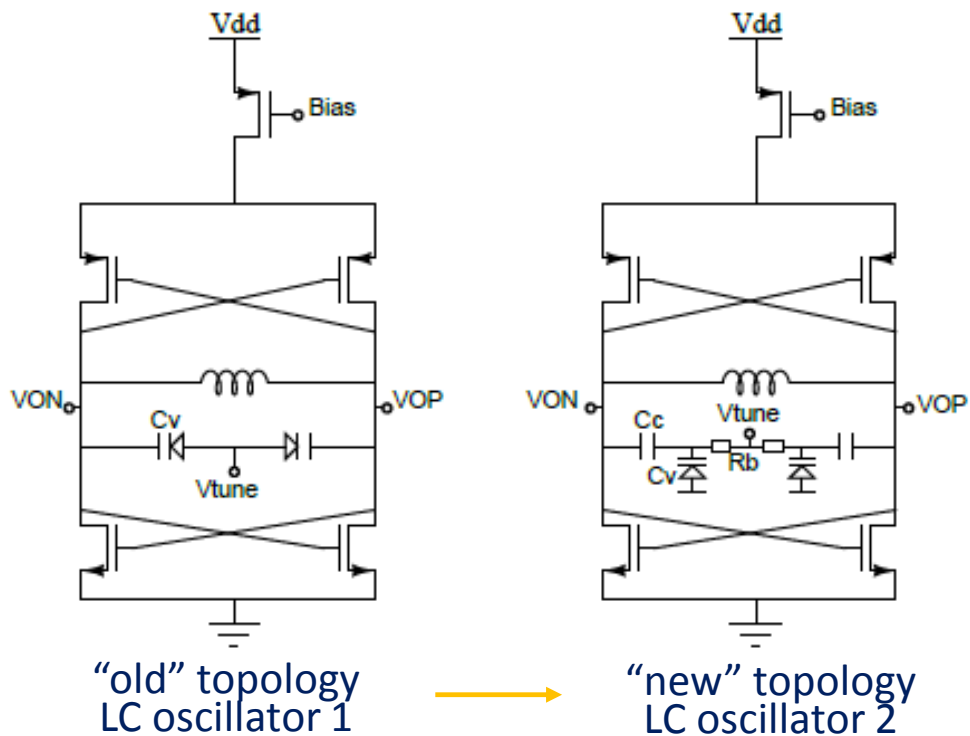
# Low jitter PLL: topology matters


- A new design prototyped to test the hypothesis:
  - Smaller varactor area
  - Different frequency tuning topology:
    - Grounded vs floating well!




Varactor cross section

 

SEE cross section

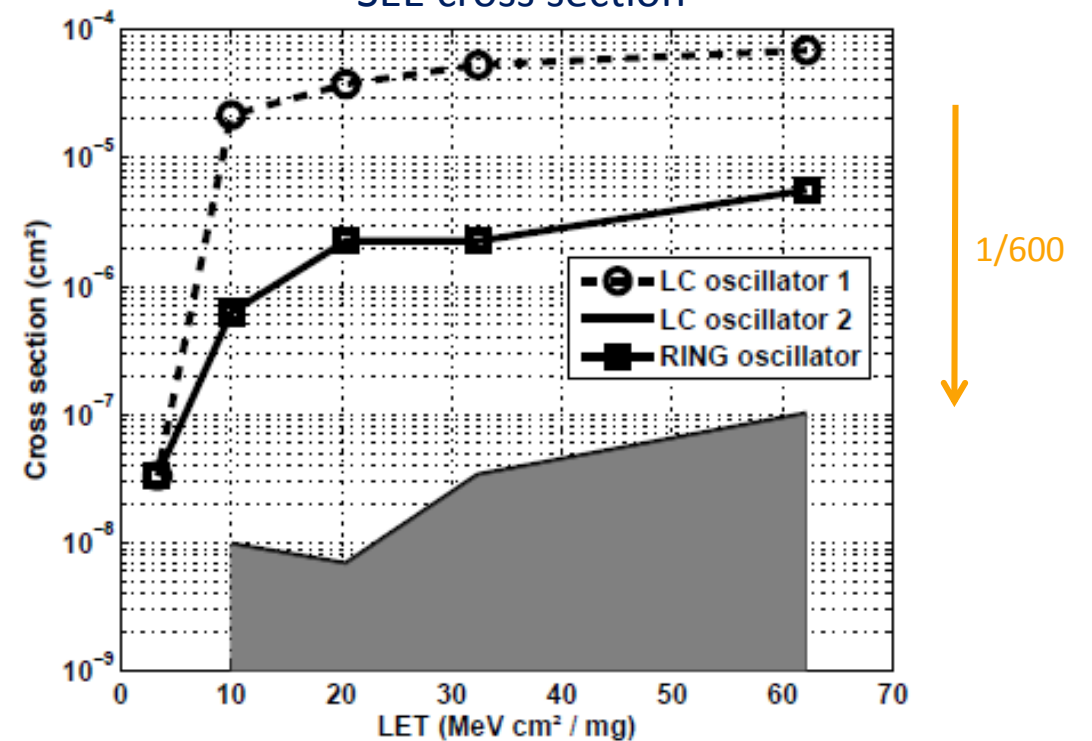

# IpGBT: clocks manager

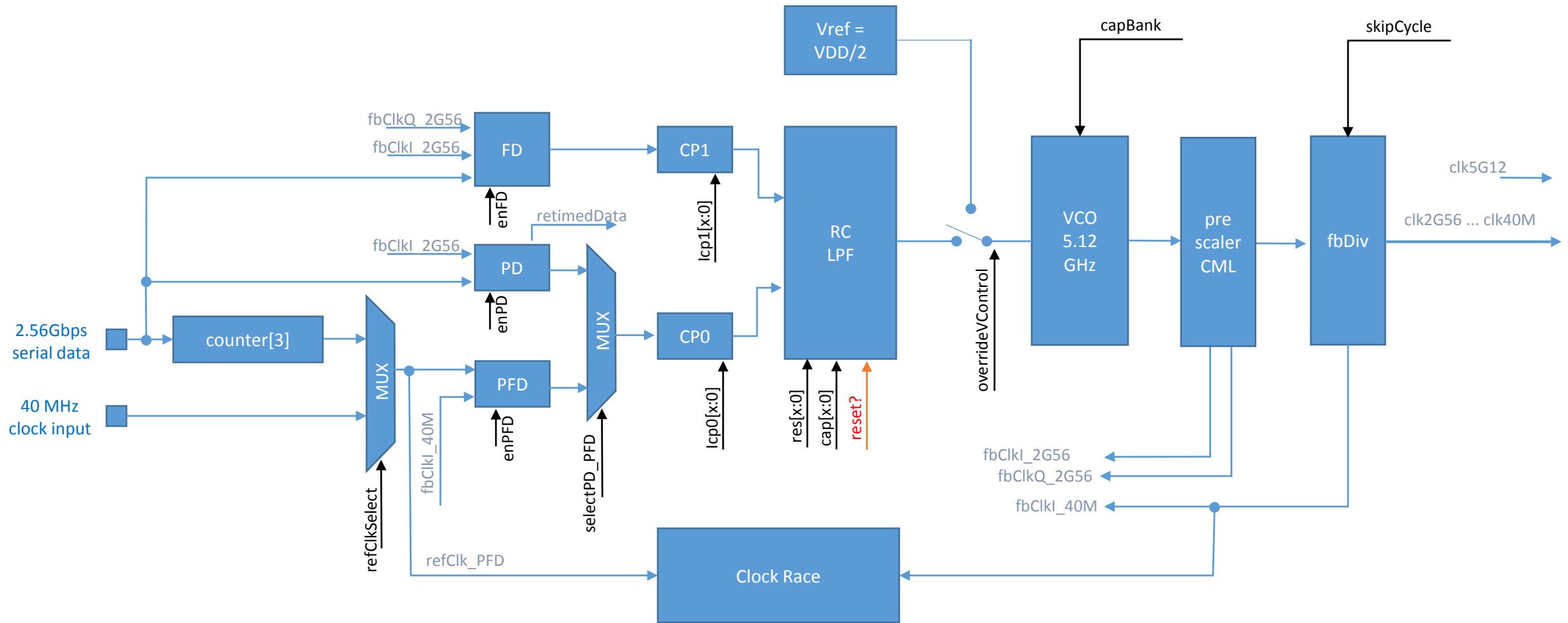


- Two modes of operation:

- PLL
- CDR
  - Locking with external reference
  - Reference-less locking (using data)

- Generated clocks:

- 40MHz / 80MHz / 160MHz / 320MHz / 640MHz / 1.28GHz/ 2.56GHz/ 5.12GHz (In phase!)
- + inverted clocks
- + triplicated clocks (A/B/C)

# IpGBT: Down link: eTx - eLink Driver

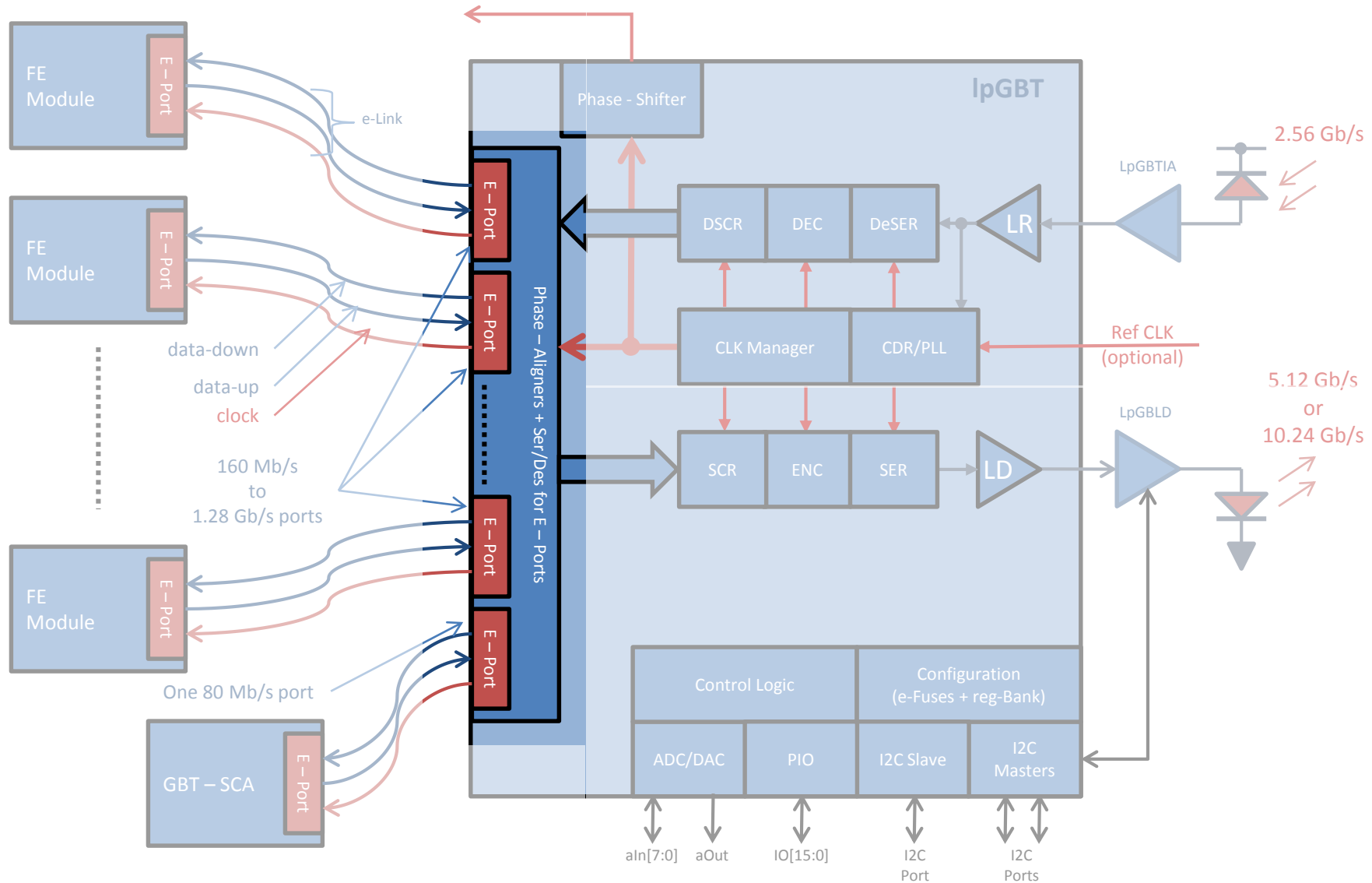


# lpGBT: Down link: eTx - eLink Driver

- Specs

- Data rate: Up to 1.28 Gb/s
- Clock frequency: Up to 1.28 GHz
- Driving current: 1 to 4 mA in 0.5 mA steps
- Receiving end termination: 100  $\Omega$
- Voltage amplitude : 200 mV to 800 mV (DIFF PP amplitude in 100  $\Omega$ )
- Common mode voltage: 600 mV
- Pre-emphasis:
  - Driving current: 1 to 4 mA in 0.5 mA steps
  - Pulse width:
    - Self timed: 120 ps to 960 ps in steps of 120 ps
    - Clock timed:  $T_{bit} / 2$

- Design - driven by radiation tolerance considerations:

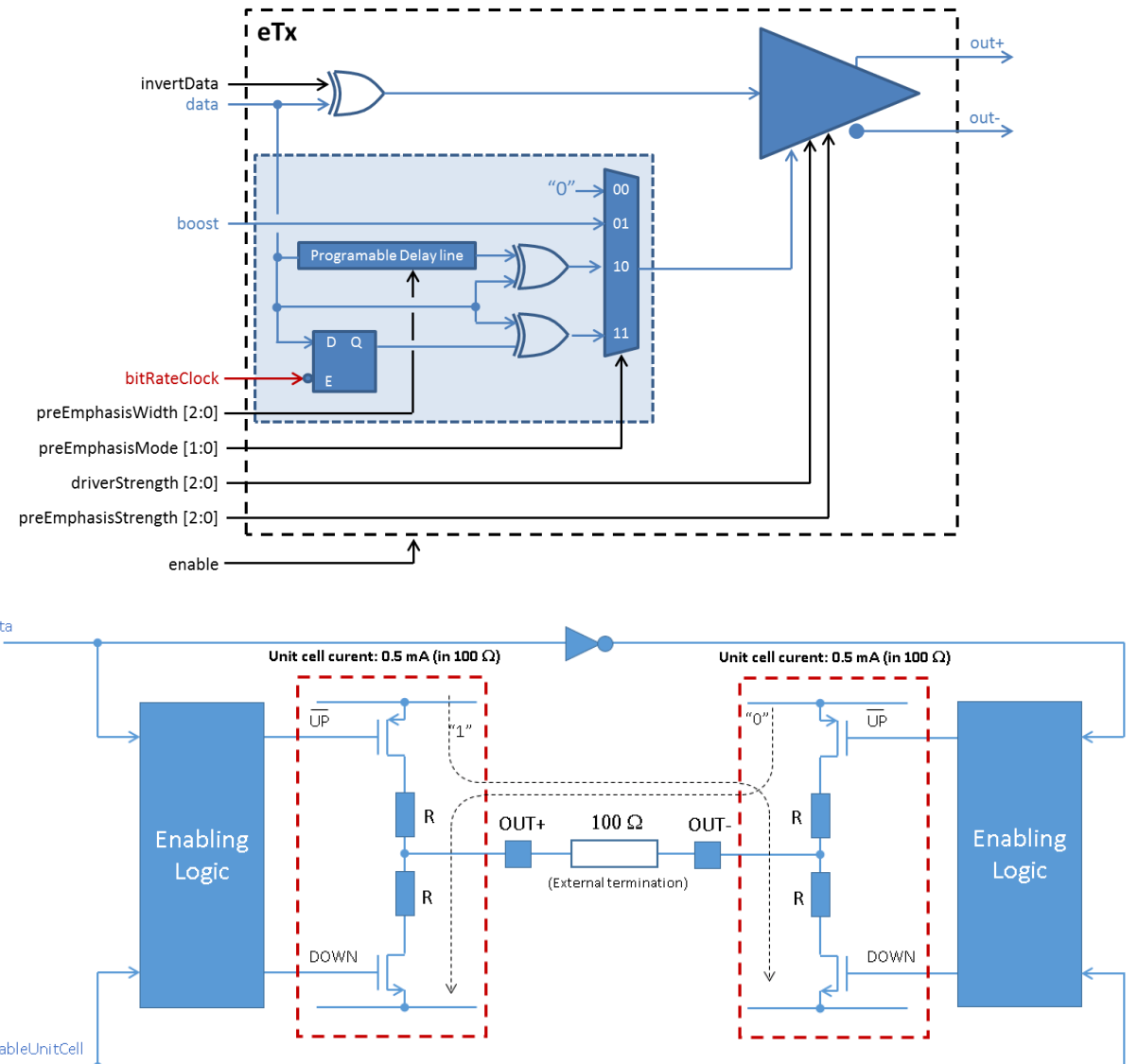- The circuit relies on having the resistors setting the current and not the transistors (Poly resistors are insensitive to TID)





# IpGBT: Down link: eTx – Pre-Emphasis



## No Pre-Emphasis

Driver Strength = 2 mA  
Pre-Emphasis Strength = 0 mA  
Pulse width = n.a.


Data: PRBS 7  
Data rate: 2.56 Gb/s  
 $C_L = 2 \times 5 \text{ pF}$
  
## With Pre-Emphasis

Driver Strength = 2 mA  
Pre-Emphasis Strength = 2 mA  
Pulse width = T/2




# IpGBT: Up link: eRx - eLink Receiver

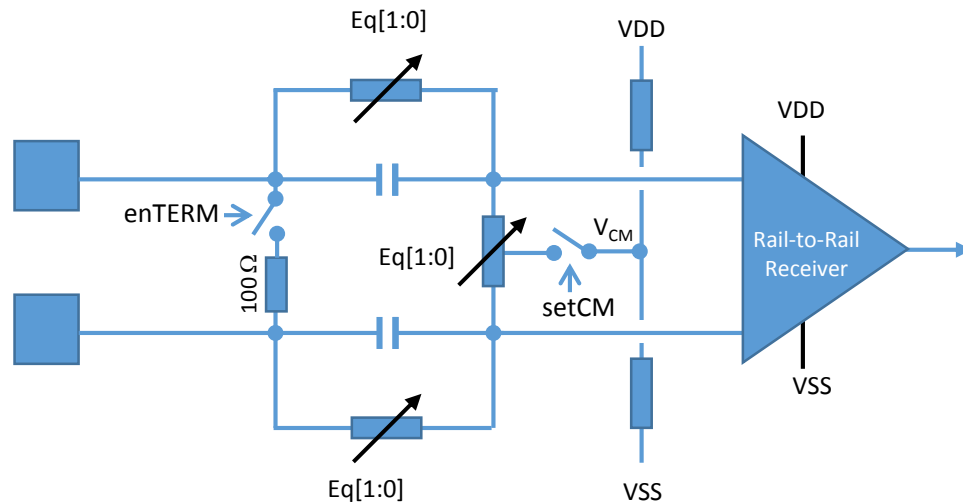

- Specs


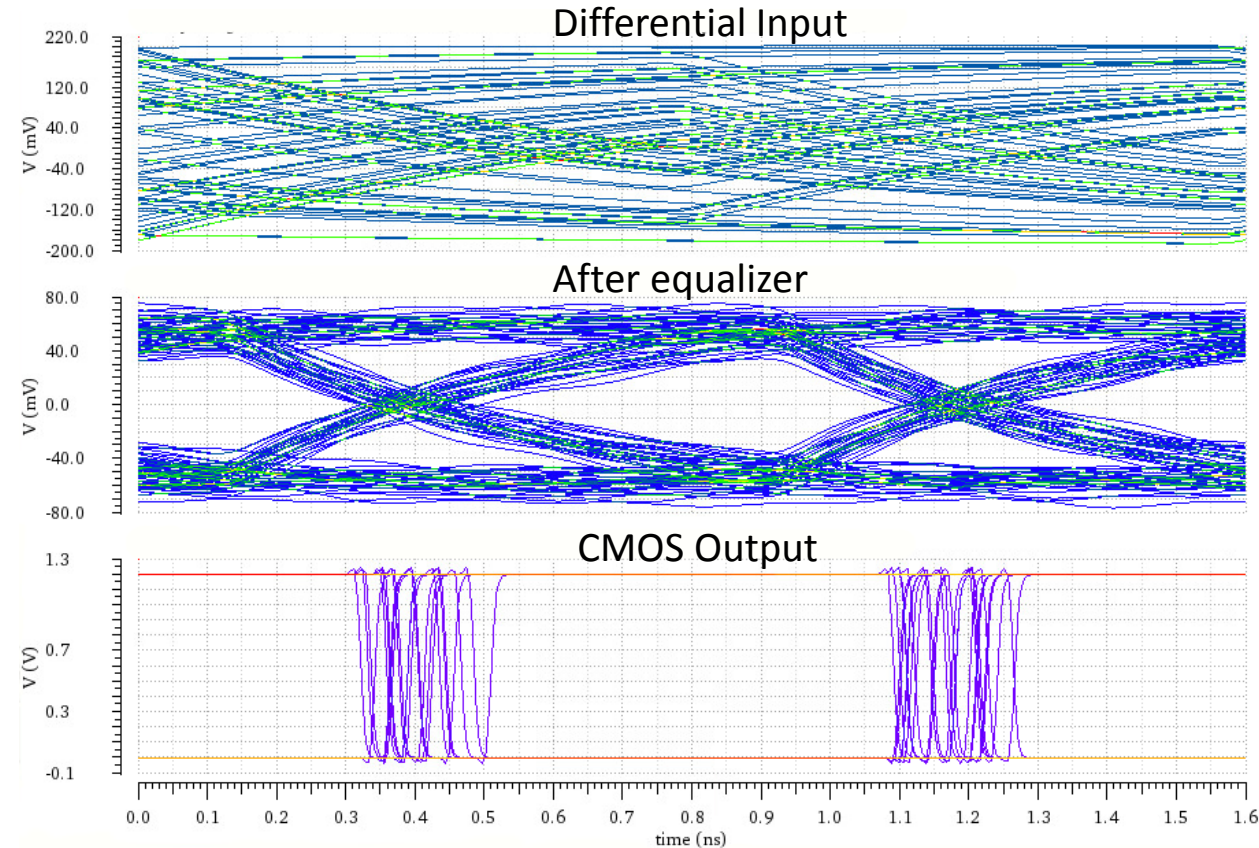
- Data rate: Up to 1.28 Gb/s
- Optional termination: 100  $\Omega$
- Optional bias generator for AC coupled signals ( $V_{DD}/2$ )
- Common mode voltage range: 70 mV – 1.13V
- Differential input voltage :140mV – 450mV
- Passive equalizer:
  - Optimized for cables with bandwidths of 448, 299 and 224 MHz
  - Attenuates low frequency signals



- Simulation conditions:


- 70 MHz channel
- Data rate: 1.28 Gb/s
- Signal amplitude: 200 mV
- Process: TT,  $V_{DD} = 1.2$  V,  $T = 25$   $^{\circ}$ C

# IpGBT: Up link: Phase Alignment

 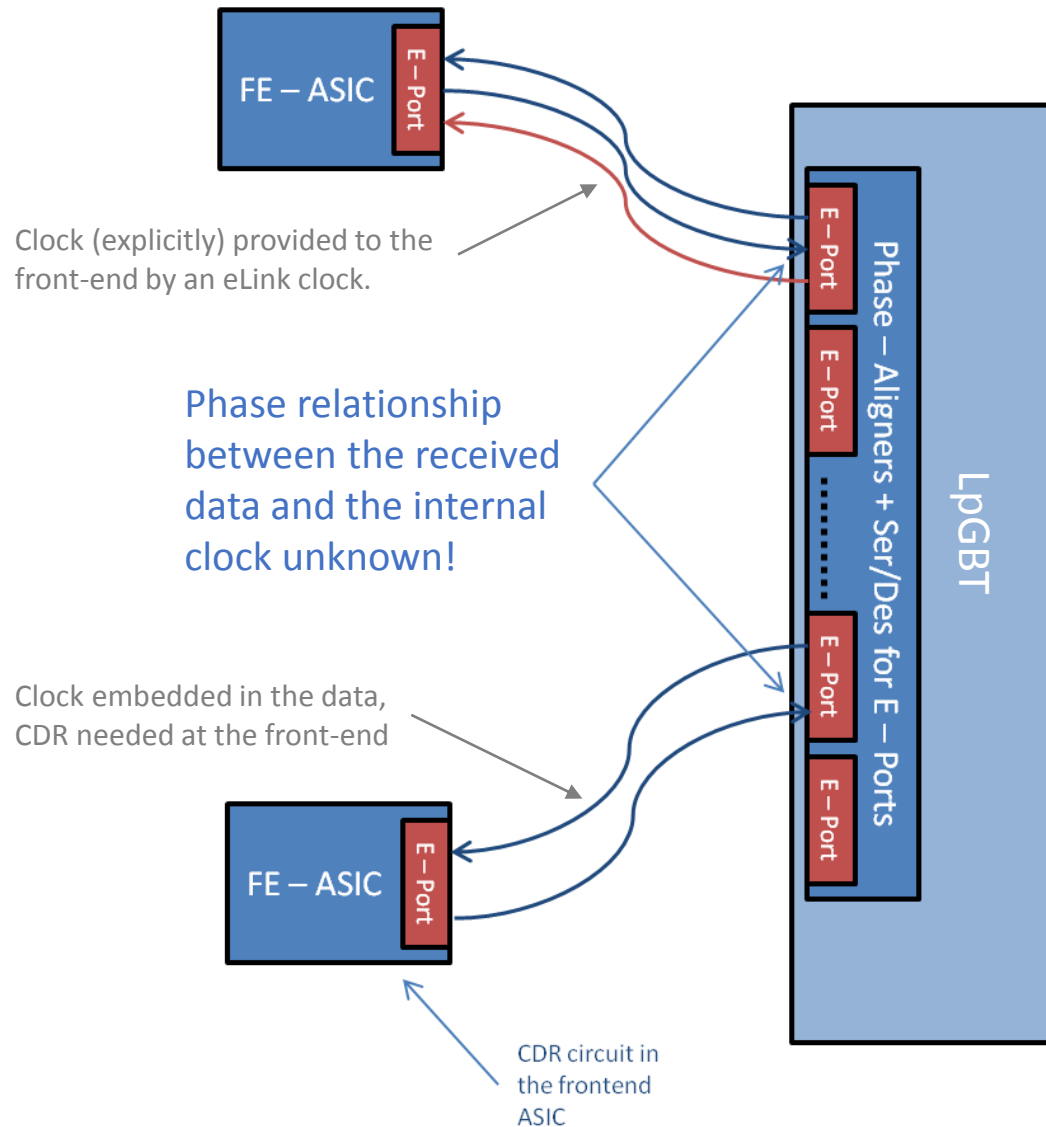

- The LpGBT is the clock source to the front-end modules;
  - All the clocks generated by the LpGBT are synchronous with the LHC machine clock; Thus the LpGBT “knows” exactly the frequency of the incoming data! A CDR circuit is thus not needed for each ePort.
- The phase of the incoming data signals is “unknown” in relation to the internal sampling clock!
- There are up to 28 eLink inputs (potentially) all with random phase offsets
- The solution:
  - “Measure” the phase offset of each eLink input
  - Delay individually each incoming bit stream to phase align it with the internal sampling clock
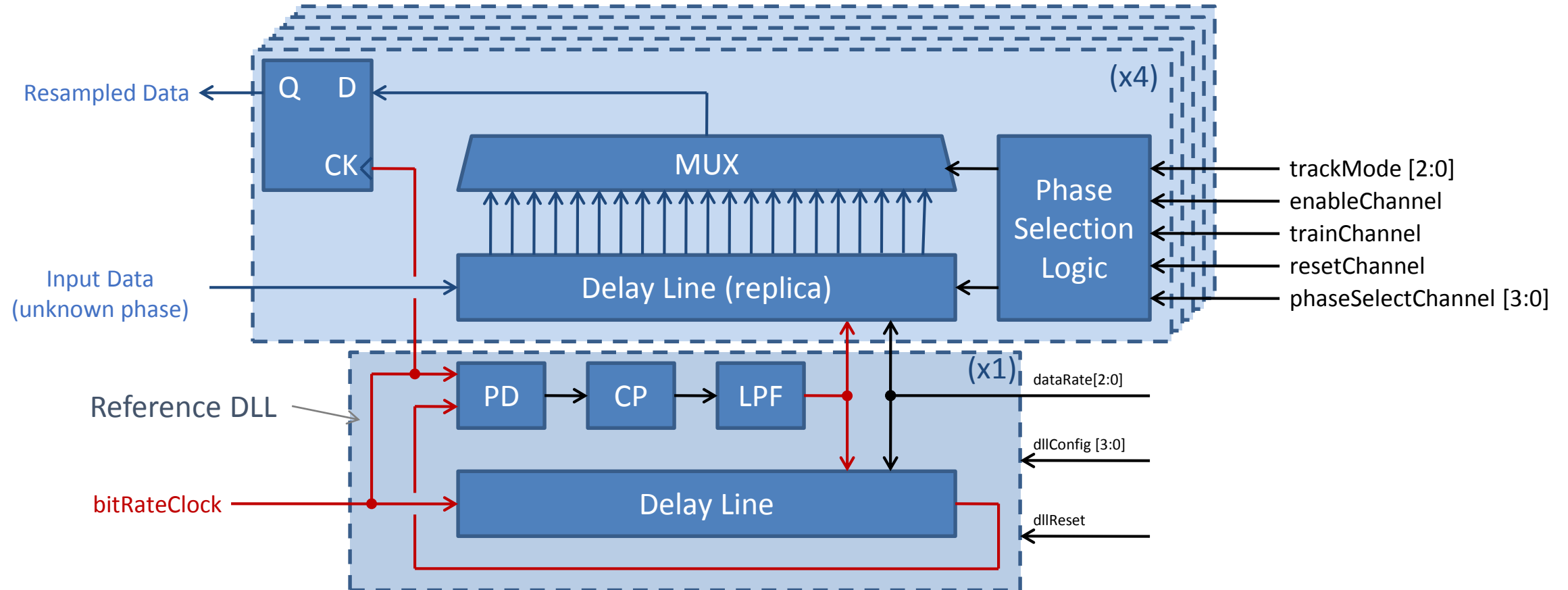
# IpGBT: Up link: Phase aligner - architecture




## Building blocks:

- Reference DLL tunes control voltage for delay elements
- “Open loop” delay lines for data channels

## Three modes of operation:


- Automatic phase tracking - tracks any phase drifts during operation
- Static phase selection - requires the operator to select the proper phase (reduced power consumption)
- Training with learned static phase - combines two above mentioned modes

# IpGBT: Data encoding

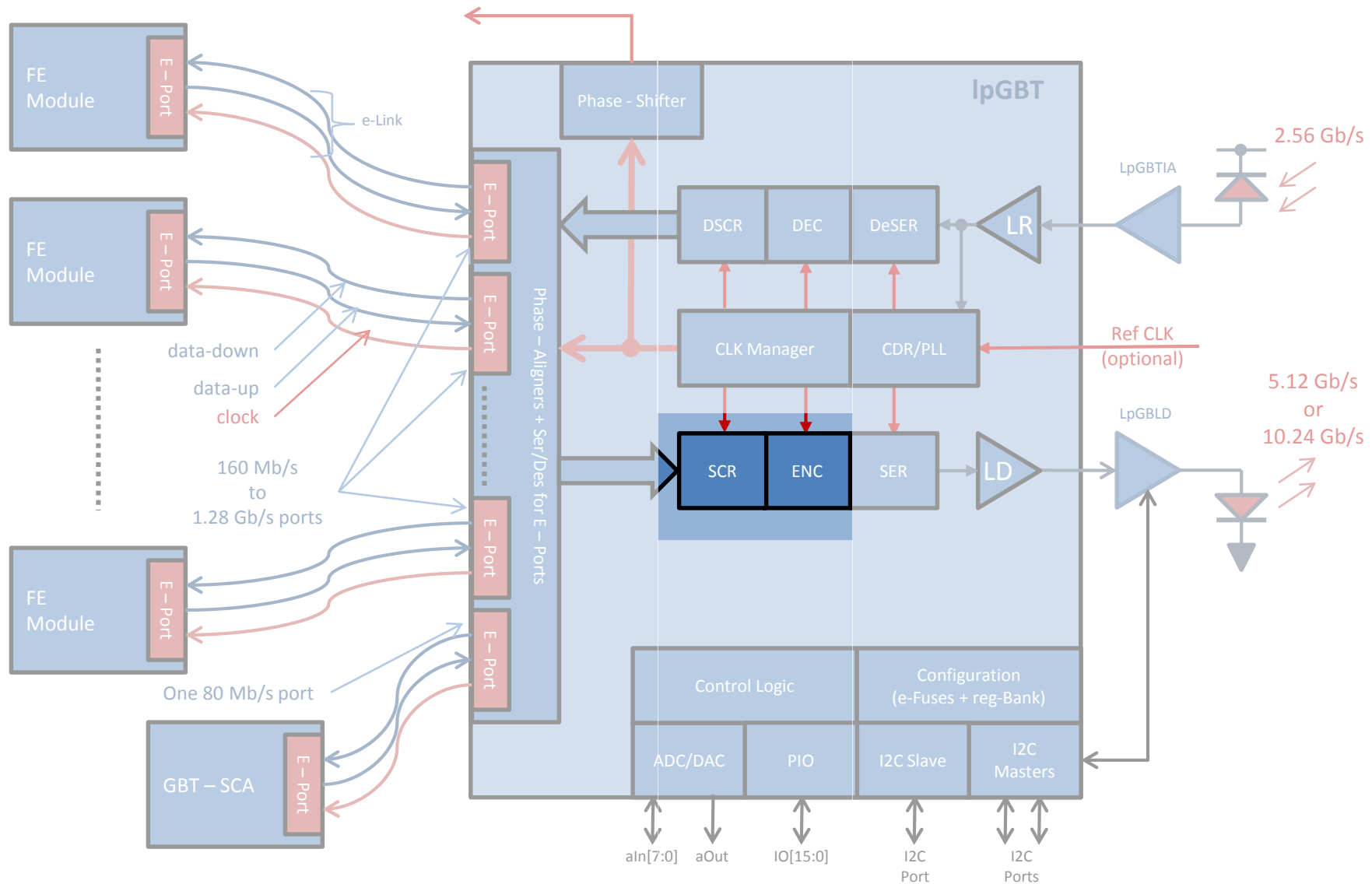

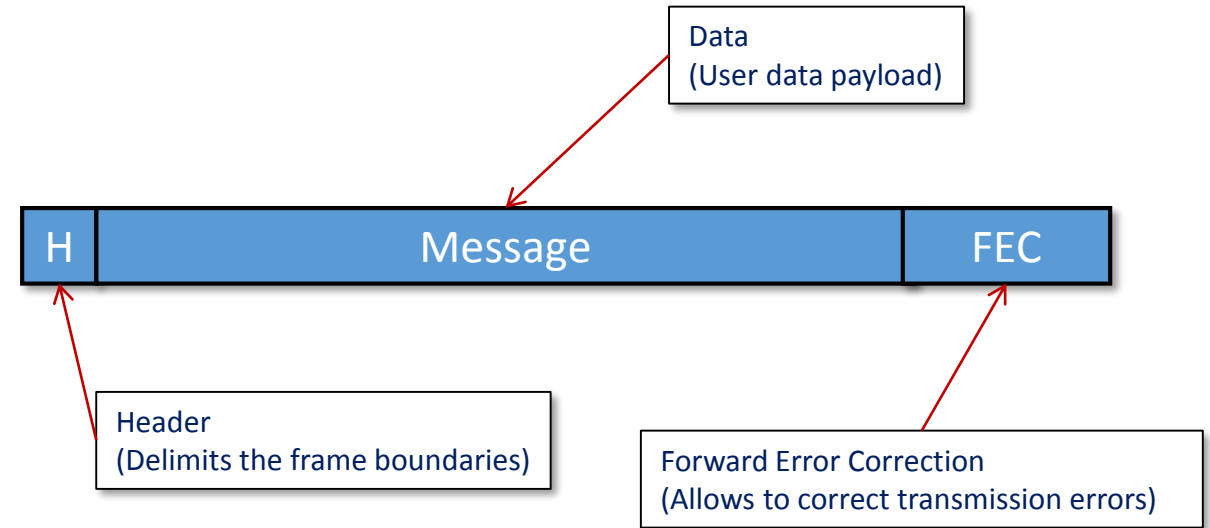
# IpGBT: Data encoding

- The IpGBT supports the following data rates:
  - Down link: 2.56 Gb/s
  - Up-link: 5.12 / 10.24 Gb/s
- In all cases data is transmitted as a frame composed of:
  - Header
  - The data field
  - A forward error correction field: FEC5 / FEC12
- The data field is scrambled to allow for CDR at no [additional] bandwidth penalty
- Efficiency = # data bits/# frame bits




	Down-link 2.56 Gb/s	Up-Link			
		5.12 Gb/s		10.24 Gb/s	
		FEC5	FEC12	FEC5	FEC12
Frame [bits]	64	128		256	
Header [bits]	4	2		2	
Data [bits]	36	116	102	232	204
FEC [bits]	24	10	24	20	48
Correction [bits]	12	5	12	10	24
Efficiency	56%	91%	80%	91%	80%

# IpGBT: Up link: Serialzier

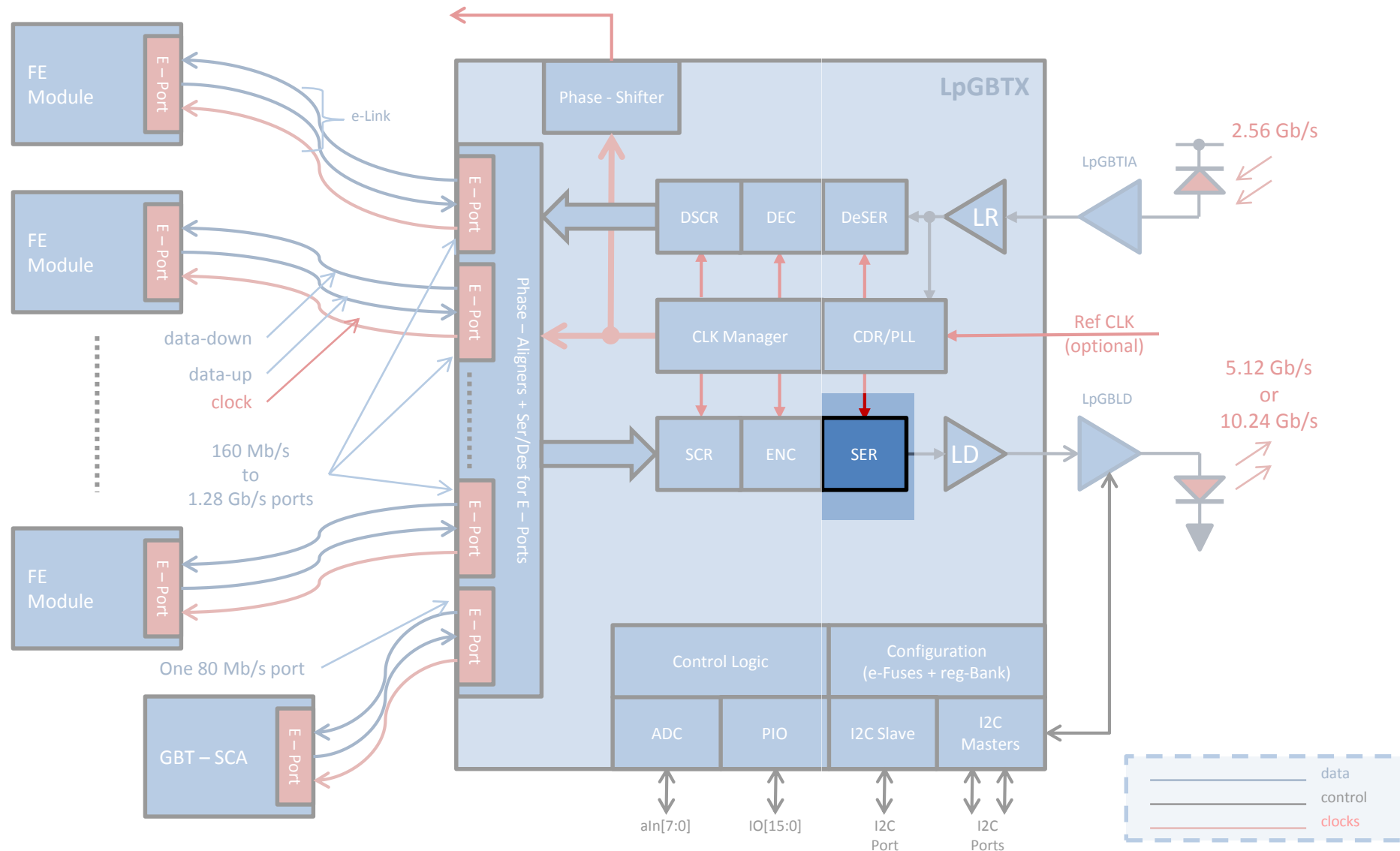

# lpGBT: Up link: Serialzier

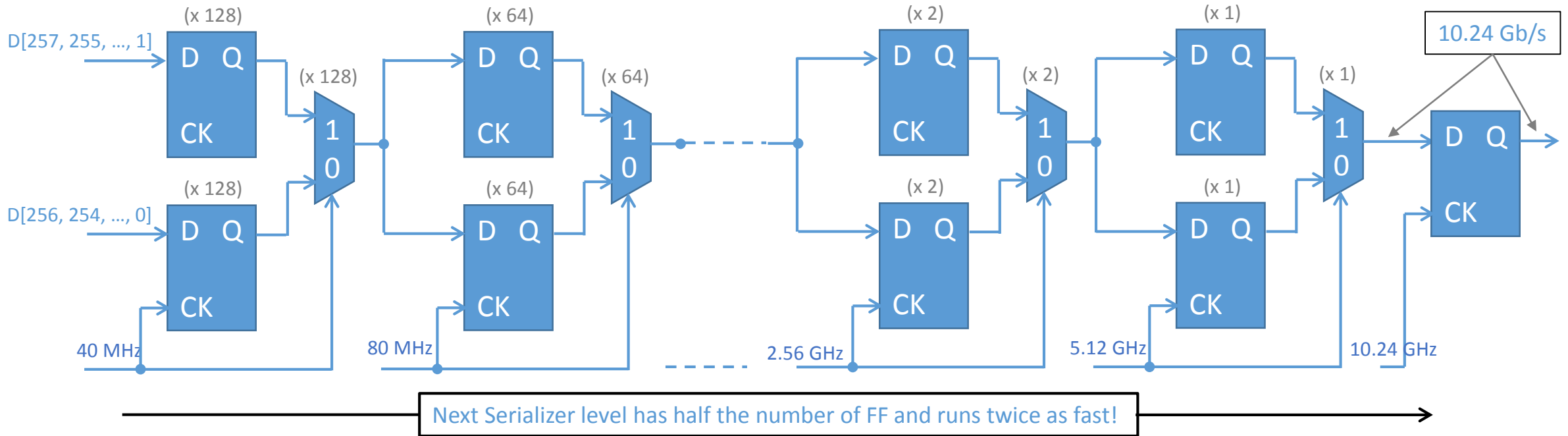

- The power per serialization level remains constant:

$$P_L = 10.24 \text{ GHz} \times P_0$$

- The serializer power is:

$$P = 10 \times 10.24 \text{ GHz} \times P_0$$


Ten levels are needed to go from 40 MHz to 10.24 GHz

- Although this architecture requires “twice” as much FFs (1023) as a simple shift register based serializer (512), it only requires  $10/257 = 3.9\%$  of the power consumption!!!


- Since the clock frequency increases with the serialization level, it is possible to optimize the speed-power at each level (Not possible for the simple shift register)
- The lpGBT does not use the last “resampling” stage at 10.24 GHz.
  - At the output of the last MUX the signal is already at 10.24 Gb/s (Double data rate)
  - Low jitter requires thus the last MUX to be fast and the 5.12 GHz clock to have “perfect” duty-cycle



# IpGBT: Up link: Line Driver


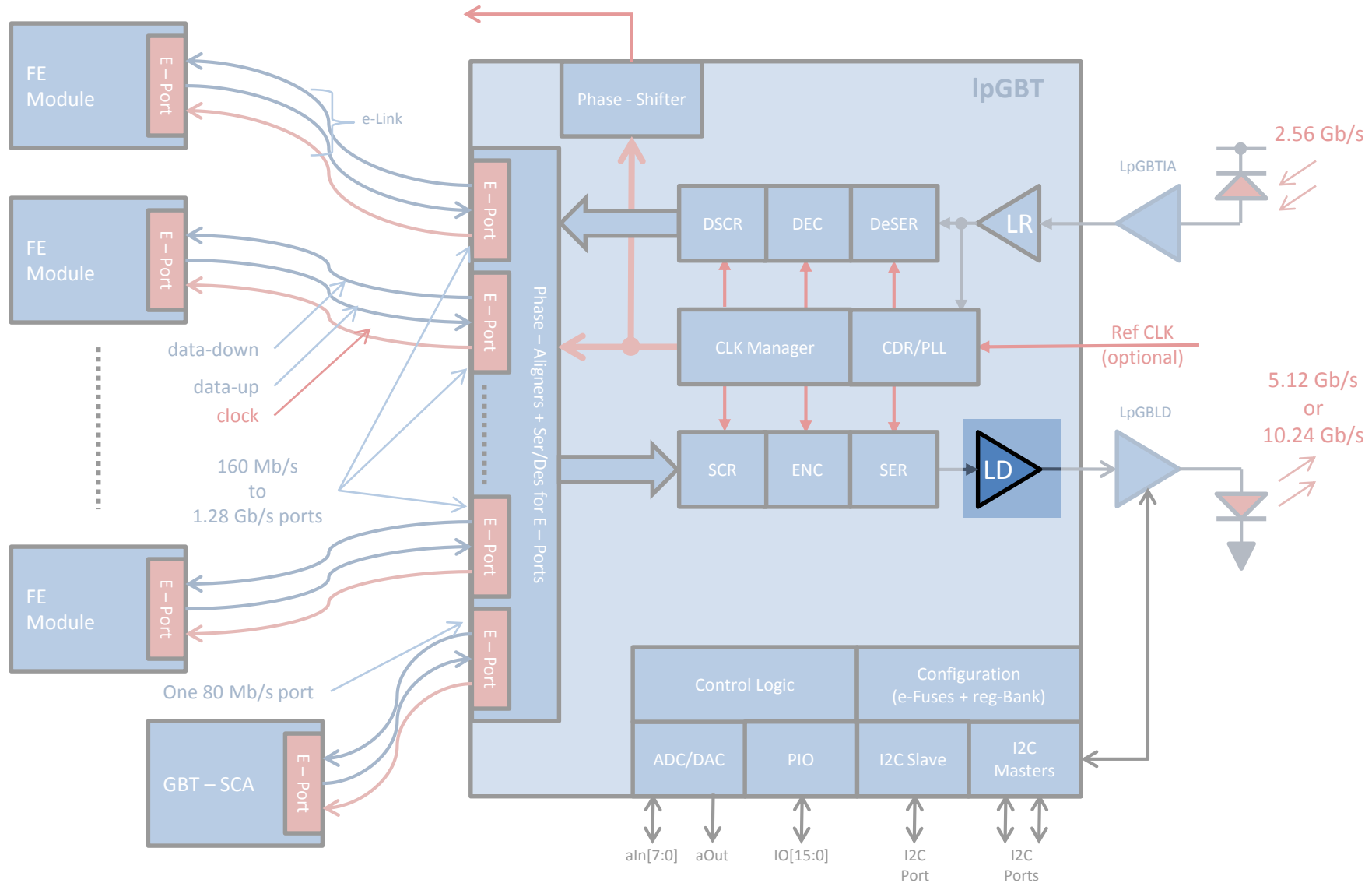


# IpGBT: Up link: Line Driver Topology

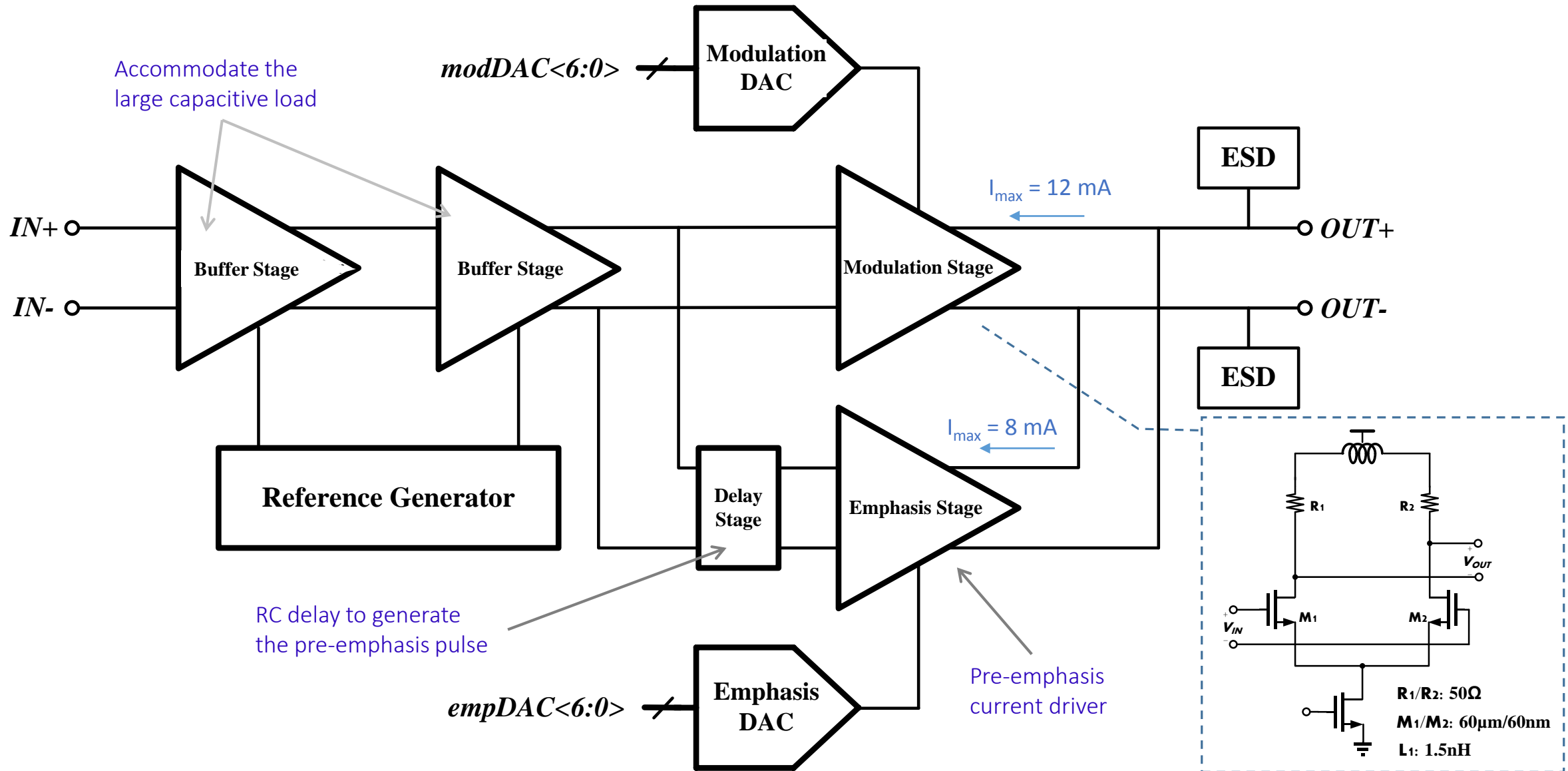
 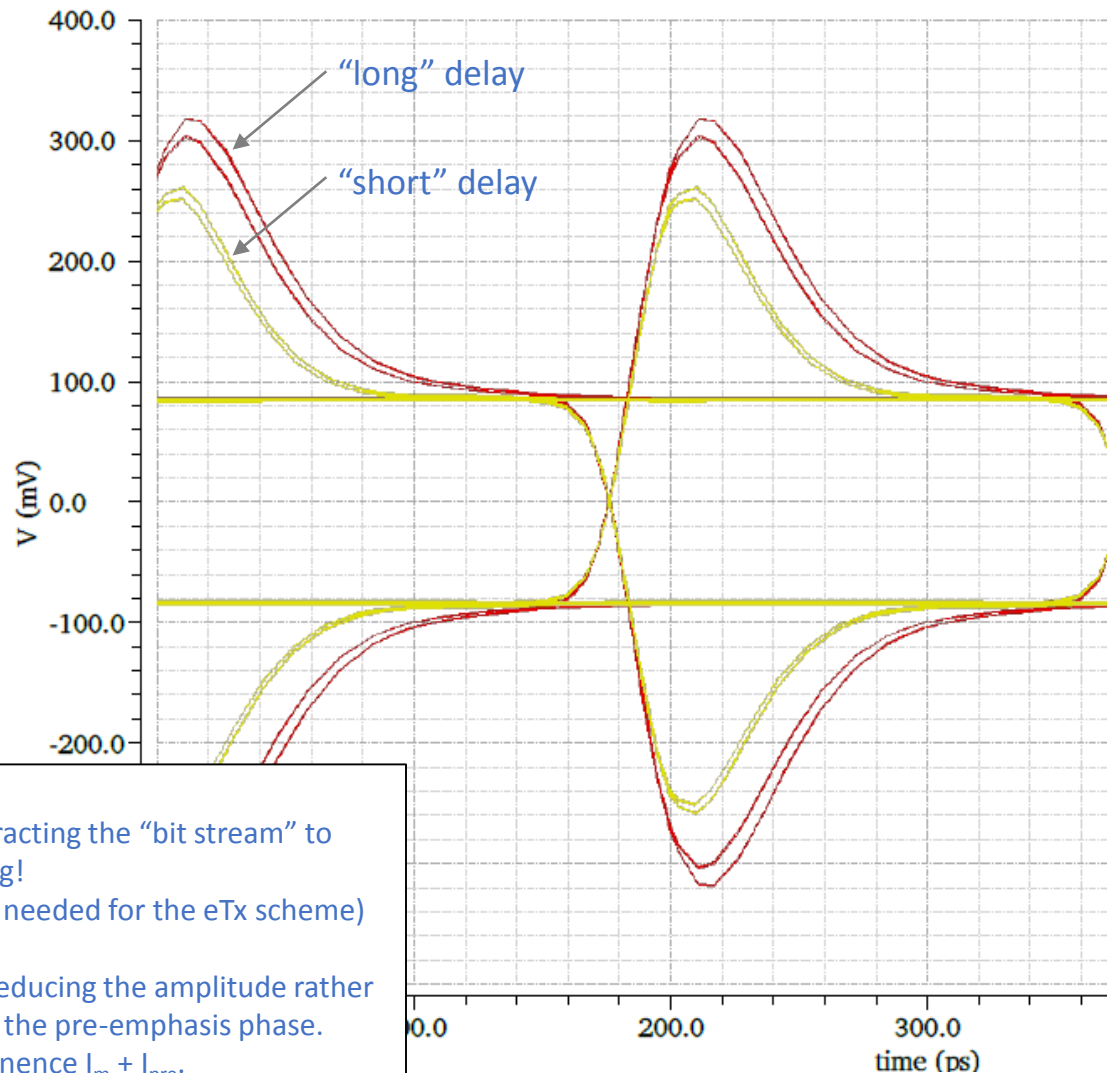
# IpGBT: Up link: Line driver simulations (@5.12Gbps)

$I_{cc} = 40 \text{ mA}$   
 $I_{mod} = 12 \text{ mA}$   
 $I_{pre} = 8 \text{ mA}$   
 $C_{out} = 500 \text{ fF}$   
Process: SS\_100C\_1.2V




## Advantage:

- Pre-emphasis is made by subtracting the "bit stream" to itself after inversion and scaling!
- No narrow pulses required (as needed for the eTx scheme)

## Disadvantage:


- The pre-emphasis is done by reducing the amplitude rather than peaking the signal during the pre-emphasis phase.
- The driver consumes in permanence  $I_m + I_{pre}$ .

# IpGBT: Analog and other peripherals

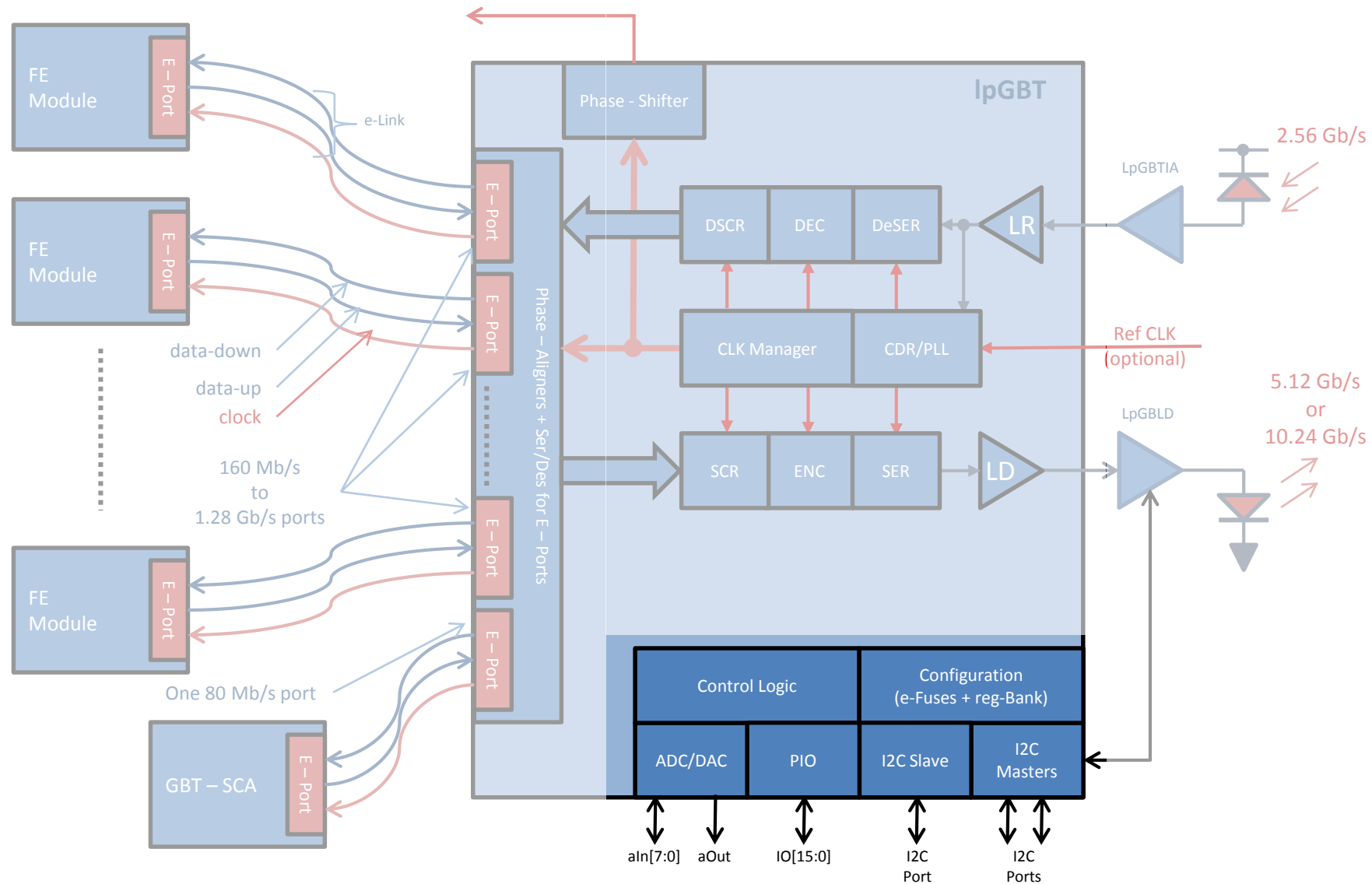
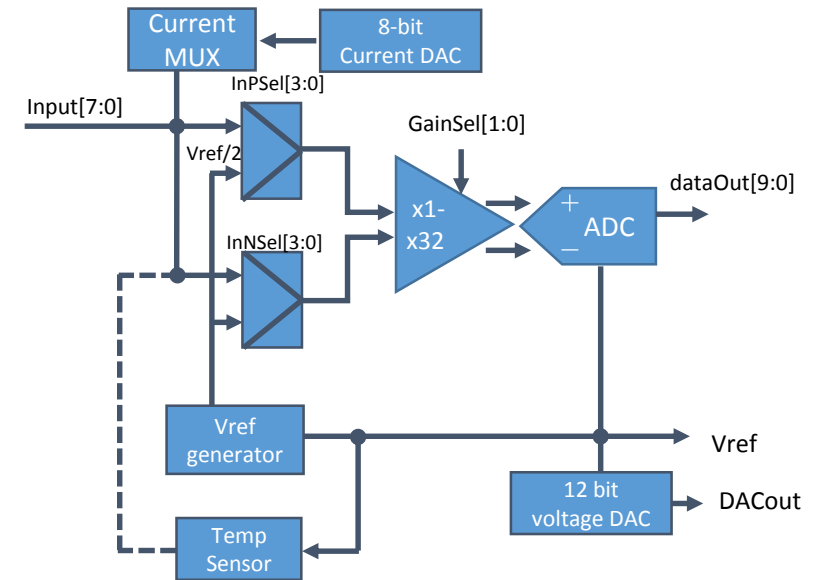
# IpGBT: Other features/blocks

- 28 multi mode deserializers:
  - Data rates: 160Mbps, 320Mbps, 640Mbps, 1280Mbps
- 16 multi mode serializers:
  - Data rates: 80Mbps, 160Mbps, 320Mbps
- 28 independent frequency programmable eLink clocks
  - Frequency: 40MHz – 1.28GHz
  - Two phases: 0 and 180 deg
- 4 independent phase/frequency programmable clocks:
  - Frequency: 40 MHz – 1.28GHz
  - Phase: 50ps resolution
- 3 independent I2C master channels
- 16 PIO
  - Configurable pull up/down
- Watchdog
- SEU calibrator
- Process monitors (ring oscillators)
- Test pattern generators and checkers
- Configuration memory (eFuses)
  - ... ~450 8-bit registers



- 10 bit ADC
  - 8 channels (single ended or differential)
  - Voltage amplifier (x1 .. x32)
  - Sampling rate up to ~ 1MSps
- 12 bit voltage DAC
- 8 bit current DAC
  - can be attached to any analog input
  - range: 0-1mA (8bit)
- Temperature sensor
- Power on reset generator
- Brown out detector
  - Programmable levels : 0.7, 0.75, ... 1.1V


# IpGBT: Status

- All blocks ready

Blocks	Blocks
10 Gb/s line driver	ePort Rx DLL
2.5 Gb/s line receiver	ePort Rx Delay Lines
HS LVT ELT Library	ePort TX
CML Library	ePort Clk
I/O Library	IC Channel
Bandgap	I2C Master
Power On Reset	I2C Slave
10-bit SAR ADC	Frame Alignment
8-bit ADC	Lock Control, PLL
Temperature Sensor	Lock Control, CDR
Programmable Current	Auto Reset
5/10 Gb/s Serializer	Power Up FSM
Deserializer	Watchdog
PLL/CDR	Timeout
CML Divider by 2	Scrambler
Eye Scan	FEC Codec
Loopback Multiplexer	Self Test BERT Tx
Fine Phase Shifter	Descrambler
Coarse Phase Shifter	Frame Deinterleaver
ePort Deserializer	Self Test BERT Rx

- Chip integration in progress

 - Integration of high speed blocks in the full custom macro
- Top level PNR : advanced (almost DRC and LVS clean)
- Whole chip timing and power verification




- Package is designed and ready for manufacturing
- Test system advanced

---

# Backup slides

# IpGBT: Analog peripherals

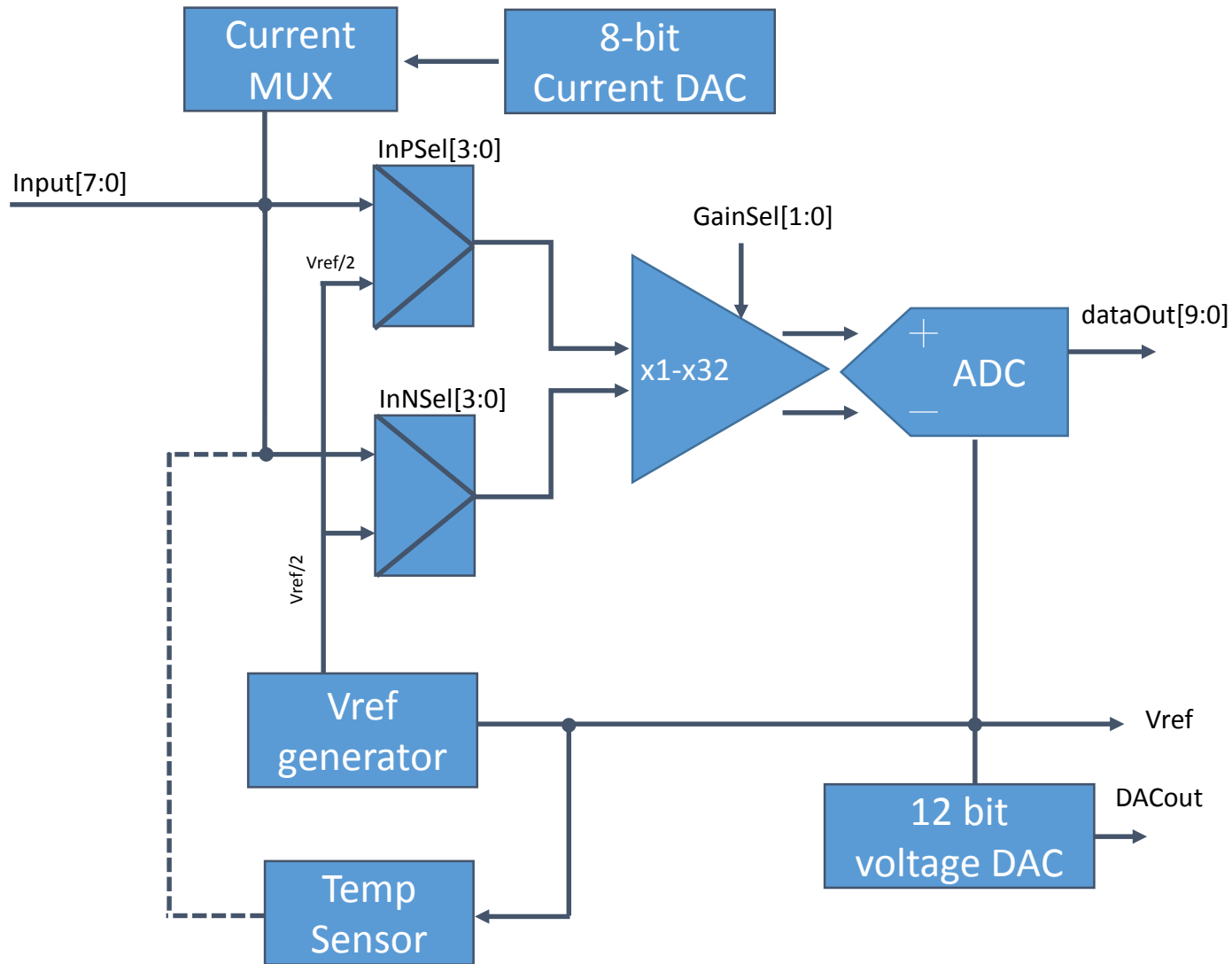


- 10 bit ADC
  - Core: fully differential SAR
  - 8 channels (single ended or differential)
  - Voltage amplifier (x1 .. x32)
  - Sampling rate up to ~ 1MSps (limited by the control channel)
  - Monitoring of internal signals (like VDD)
- 12 bit voltage DAC
- 8 bit current DAC
  - can be attached to any analog input
  - range: 0-1mA (8bit)
- Temperature sensor



 
# IpGBT: Package


- Small Footprint BGA package:
  - Size: 9 mm x 9 mm x 1.25 mm
  - Fine Pitch: 0.5 mm
  - Pin count: 289 (17 x 17)
- Designed by STATS ChipPAC
- Routing of high speed signals optimized and simulated
  - Very small loss @ 10GHz
  - models used for line driver simulations
- Status: ready for production




rxOutp, rxOutn

 



txOutp, txOutn

 

S12 for txOut(p/n)

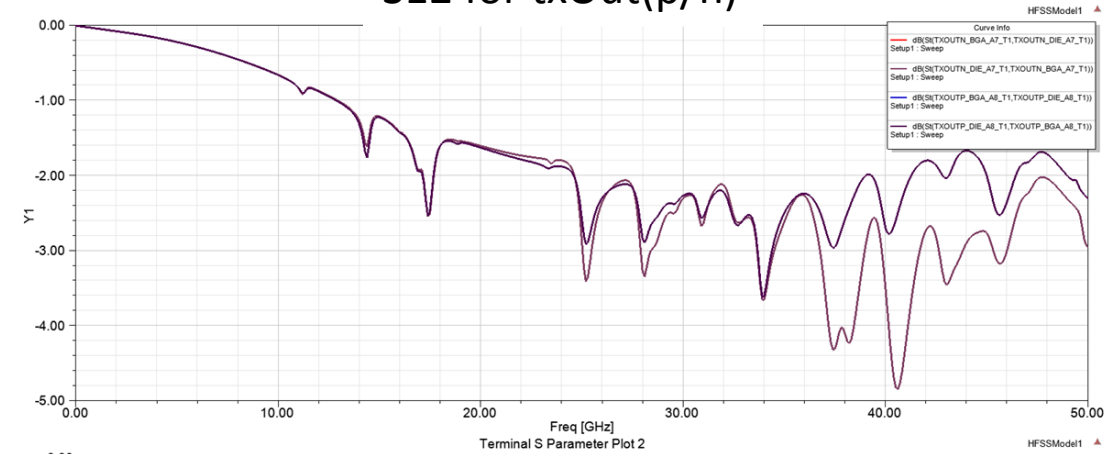

# IpGBT: Test Board and test firmware

  

## PCB

- 2 High Count FMC connectors
  - Access to ALL signals (79x2 differential, 4xHigh speed, 42 CMOS, 10 Analog)
  - Compatible with VC707
- Low jitter PLL for timing reference
- Software configurable LDO's with current monitoring
- Full custom socked already produced
- Status: final routing and simulation of high speed nets

## Firmware

- IP Bus based
- High speed part already tested
- Slow control interfaces ready (I2C)

# LpGBT Project Schedule

---

- Q2 2018:
  - Currently working towards the ASIC tapeout
    - MPW 2018 June
  - Package procurement and engineering completed
  - Test system currently under development
- Q4 2018
  - Prototypes available (~300 ASICs)
- Q4 2018 – Q3 2019:
  - Prototype functional testing
  - Radiation qualification
  - Production testing development
- Q4 2019:
  - Engineering run
- Q3 2020
  - Engineering ASICs (~40k) available to the users
- Q3 2021:
  - Production completed (~100k ASICs)