



INTEGRATED CIRCUITS
UNIVERSIDAD CATÓLICA



BeamCal ASIC v3 Design

Angel Abusleme

32nd FCAL HW Meeting

May 11th 2018, IFJ PAN Krakow

Outline

- Specs – a reminder
- General readout concept
- Filter conceptual design
- Transistor-level design
- Future tasks

SPECS – A REMINDER


Specifications

Specification	Value
Q_{in}	> 2.8 fC
ENC	< 1000 - 1500 e ⁻ rms
Number of channels	8
Maximum input rate	1 / 554ns
Baseline restoration	1%

- These specs are intended for **testbeam** purposes only
- Specs for **calibration** and **data taking** will be defined when the sensors are fixed
 - This ASIC will be a preliminary proof-of-concept

GENERAL READOUT CONCEPT

Timing diagram

 

1. CSA gets input charge
2. CSA integrates charge
3. Filter produces semi-gaussian shape
4. After peaking time, both filter and CSA are reset
 - a. CSA returns to baseline instantaneously
 - b. Filter returns to zero output instantaneously
5. Reset is released
 - a. Noise charge is produced and decays due to CSA time constant
 - b. Filtered noise charge decays before next input due to filter time constant

FILTER CONCEPTUAL DESIGN

Gm-C filters

- Suitable for VLSI
- Tunable
- Better than switched capacitors for higher bandwidth applications
- Continuous-time Gm-C filters are based on one building block: the integrator, which includes:
 - A tunable transconductor
 - A capacitor
- Direct circuit realization from block diagram


Filter implementation

- Cascade connection of:
 - Single-pole highpass filter
 - Two-pole lowpass filter
- Intended transfer function should look like this:

$$H(s) = K \cdot \frac{s\tau}{1 + s\tau} \cdot \frac{1}{(1 + s\tau)^2}$$

Single-pole highpass filter


- Block diagram:

 

- Transfer function:

$$T_{\text{HP}}(s) = k_1 \cdot \frac{s\tau}{1 + s\tau} \quad \tau = \frac{1}{\omega_0}$$

 Fully-differential Gm-C implementation of first-order bandpass filter



$$T_{\text{HP}}(s) = k_1 \cdot \frac{s\tau}{1 + s\tau}$$


Design equations:

$$k_1 = \frac{C_x}{C_x + C_A}$$

$$\tau = \frac{C_x + C_A}{G_{m2}}$$

Two-pole lowpass filter (KHN)


- Block diagram:

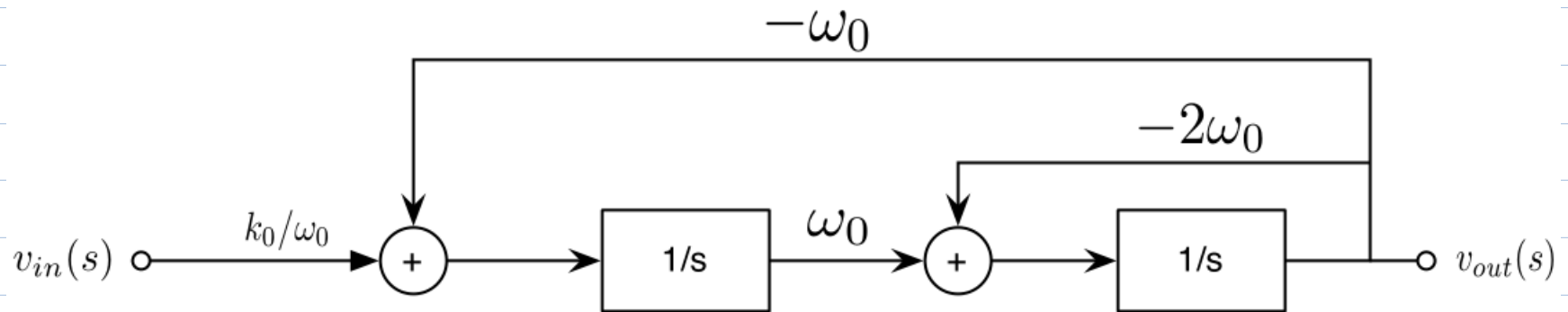

- Transfer function:

$$T_{LP}(s) = \frac{k_0 \tau^2}{(1 + s\tau)^2} \quad \tau = \frac{1}{\omega_0}$$

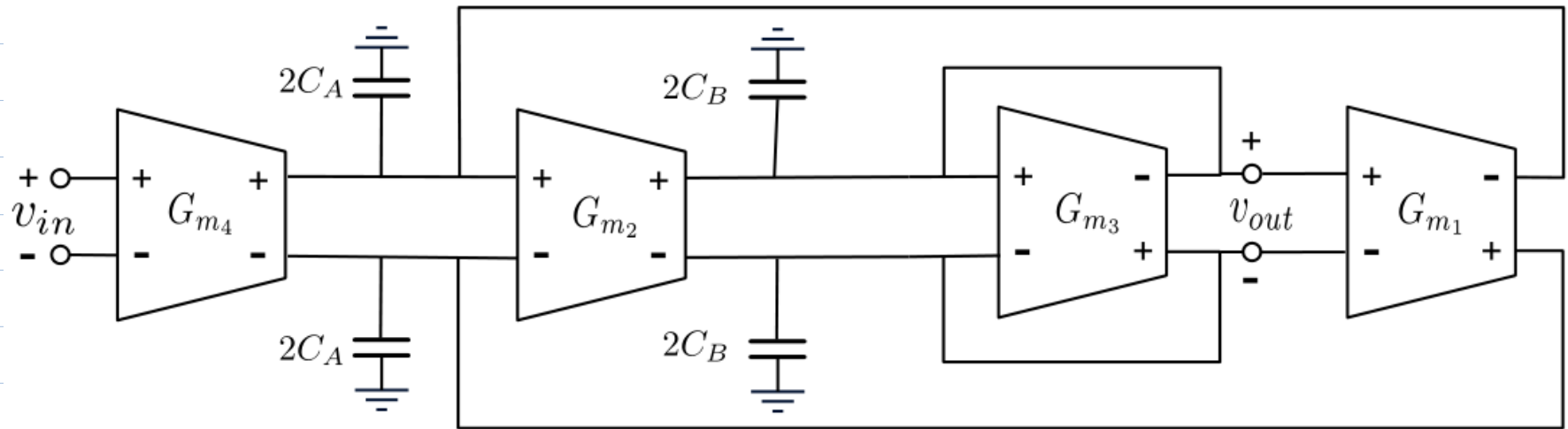
Fully-differential Gm-C implementation of second-order lowpass filter



$$T_{LP}(s) = \frac{k_0 \tau^2}{(1 + s\tau)^2}$$

Design equations: $\tau^2 = \frac{C_A C_B}{G_{m1} G_{m2}}$ $k_0 \tau^2 = \frac{G_{m4}}{G_{m1}}$ $Q = \sqrt{\frac{G_{m1} G_{m2}}{G_{m3}^2} \frac{C_B}{C_A}} = 0.5$

Gm-C implementation of CR-RC² filter

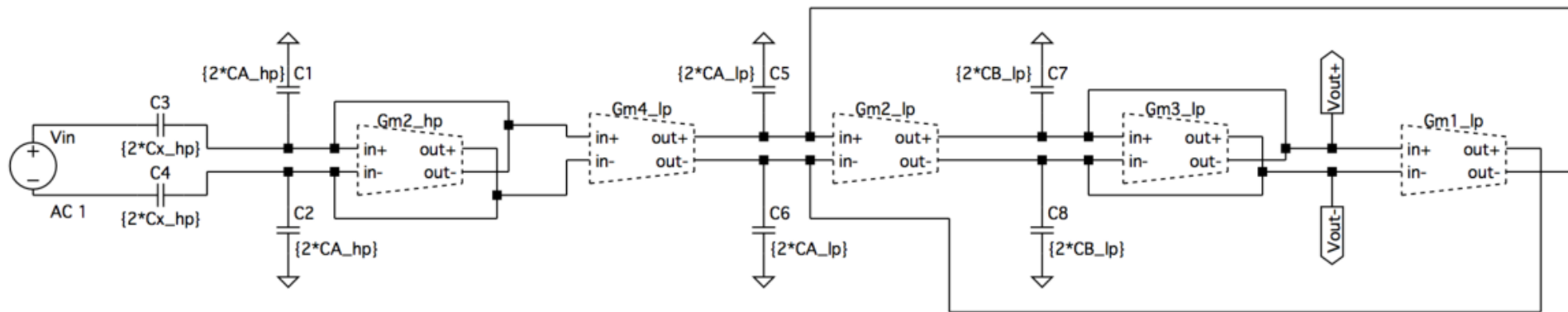

$$H(s) = K \cdot \frac{sT}{1 + sT} \cdot \frac{1}{(1 + sT)^2}$$


TRANSISTOR-LEVEL DESIGN

Challenges

- Constant value of G_m over the entire input range
 - Linearity
- High input range
- High output swing
- Wide tuning capabilities

Transconductor design

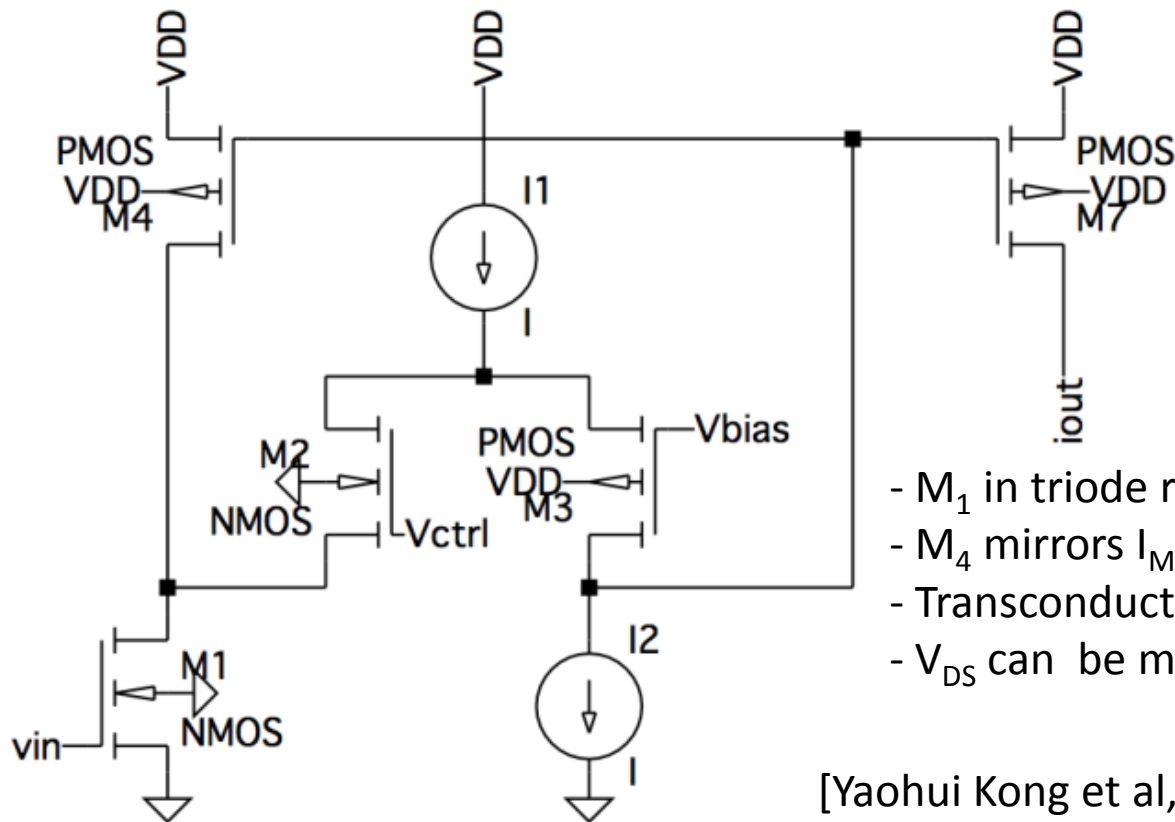
Highly linear transconductor with a wide tuning capability for low voltage and low power applications



- M_1 in triode region
- M_4 mirrors I_{M1} excess in M_7
- Transconductance is proportional to its V_{DS}
- V_{DS} can be modified by V_{ctrl}

[Yaohui Kong et al, "A highly linear low voltage CMOS triode transconductor", 2007]

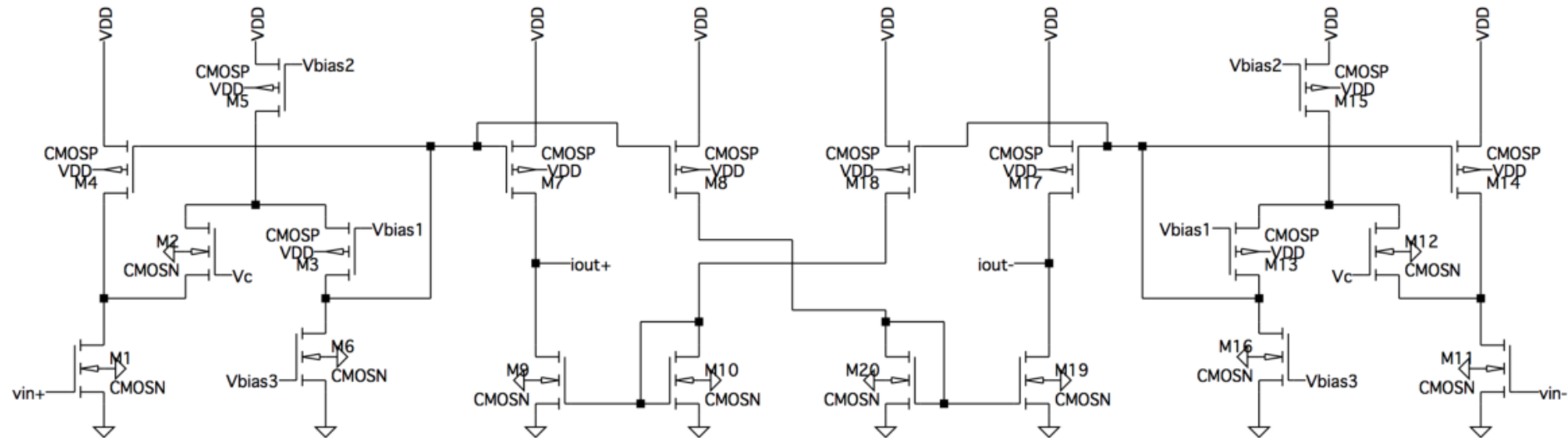
Transconductor fully-differential implementation (CMFB not shown)



The transconductance is

$$G_m = g_{m1} \cdot \frac{g_{m7}}{g_{m4}}$$

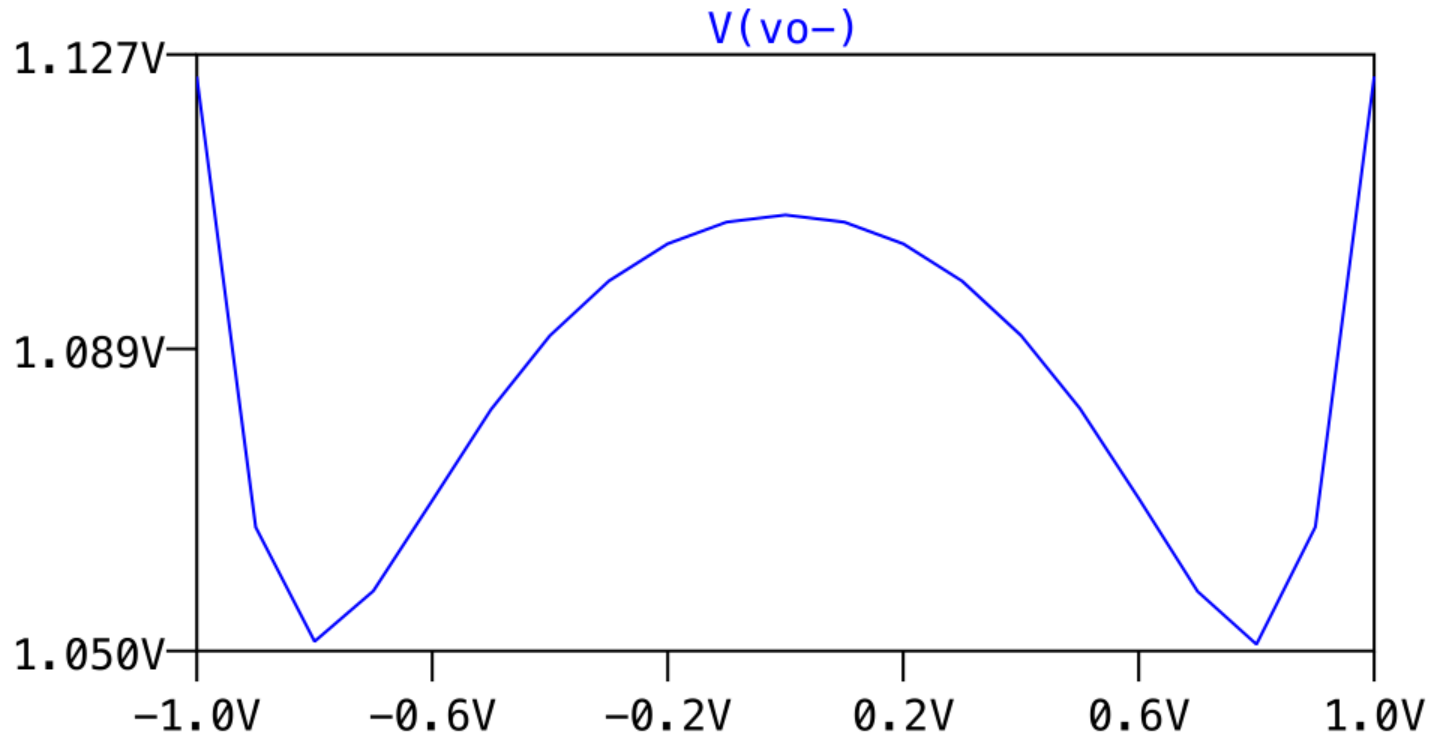Output common-mode voltage simulation (CMFB included)



FUTURE TASKS

What's next?

- Verify filter through SPICE simulations
- Edit CSA from The Bean V1
- Edit auxiliary blocks from The Bean V1
- Complete layout
- Tape-out in September 12 2018, TSMC 180nm
- Design and test board: Sept - Nov 2018
- Get chips by mid Dec
- Test for electrical stimuli between Dec 2018 - Feb 2019

Thanks for your attention