

Serial powering for pixels

F. Hüggling, D. Arutinov, M. Barbero, A. Eyring, L.
Gonella, M. Karagounis, H. Krüger, N. Wermes


SLHC-PP Annual Meeting,
CIEMAT, Madrid, 04-Feb-2010

- Introduction
- Serial Powering concept
- Serial Powering for ATLAS Pixel
 - Power Converters & Regulators
 - Protection Issues
 - System Aspects



Pixel powering for sLHC

- Current ATLAS Pixel Tracker burns 70% power in cables!
 - ASIC supply voltages: 2.0V & 1.7V.
 - Total front-end power: 6kW.
 - Total current: 3.5kA
 - Loss in cables: 17kW.
 - Situation is getting worse at SLHC since total cable cross section is fixed:
 - Services are dominating the material budget in certain areas and no more space for cables left.
 - FE power stays roughly the same while current is going up (130nm technology).
 - Cable loss scales with *current*².
- need to transmit **power at lower current!**

 

ATLAS Inner Det. Material Distribution




ATLAS Inner Det. Cables



ATLAS pixel detector services


Serial Powering Concept

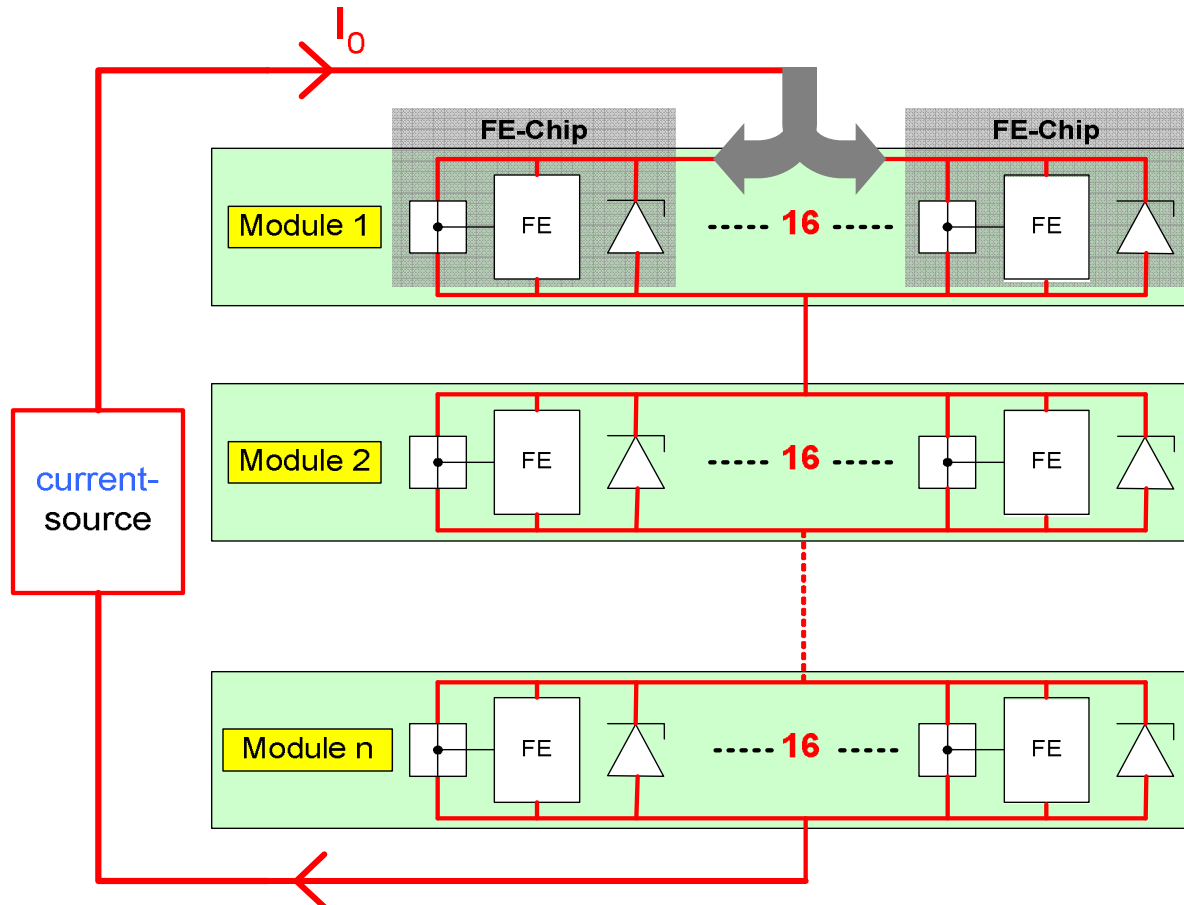

- $V_{\text{mod}} = V/n$ with n modules in a chain supplied with constant current I_{mod} .
 - Current through cables only $I = I_{\text{mod}}$ instead of $I = nI_{\text{mod}}$.
- $P_{\text{cable}}(\text{serial powering})/P_{\text{cable}}(\text{parallel powering}) = R_{\text{cable}} I_{\text{mod}}^2 / R_{\text{cable}} (nI_{\text{mod}})^2 = 1/n^2$




Serial Powering: proof of principle for pixels

 - Proof of principle has been demonstrated with a serially powered dummy half stave of the ATLAS Pixel Detector using 6 production like FE-I3 modules with internal shunt and linear regulators.
 - No performance degradation w.r.t. the parallel powering
 - High rejection capability against noise pickup injected into chain




Stockmanns, Ta, Hügging, Bonn 2005
 D.B. Ta et al., NIM A557 (2006) 445-459

   - sLHC outer layers baseline:
 - 32 4-chip-modules using the new FE-I4 chip.
 - Modules are arranged on both sides of the stave.
 - 8 modules (half stave on one side) connected to a 1 End-of-Stave card.
- Serial power module group of 8 (could be 16 or 32 modules depending on the needs).
- Power is provided together with the signals on one flex hybrid which serves as module HDI as well.



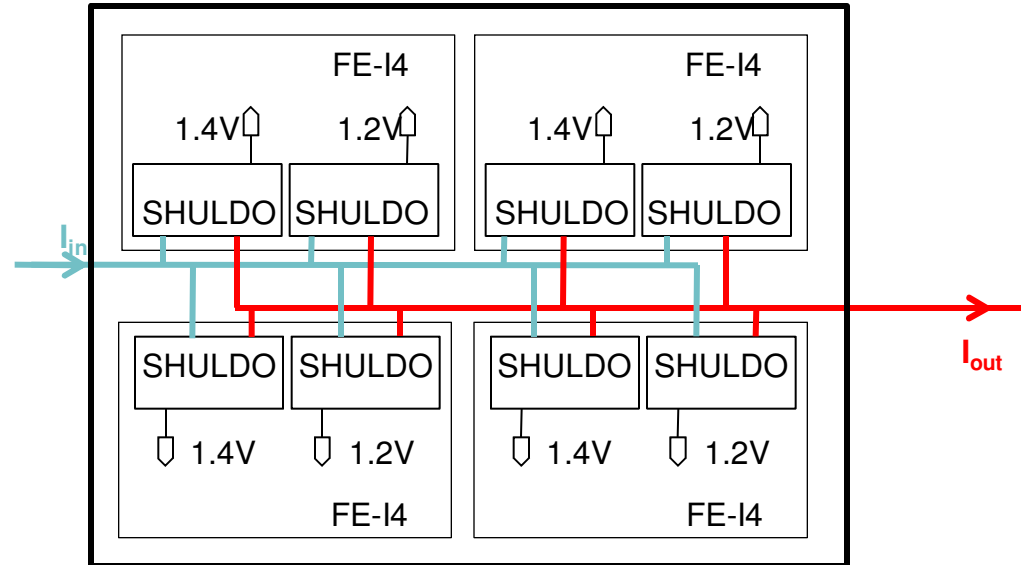
- FE-I4 power needs:
 - VDA = 1.4V
 - VDD = 1.2V
 - I = 600mA
- **voltage regulators** to generate a constant voltage out of the current supply.
- **integrated** regulation circuitry in every FE-I4.
 - avoid additional components on the module.
- 4-chip-module uses 8 regulators in **parallel**.
 - Redundancy.



- 2 SHULDOs/FE-I4
 - can operate in parallel and generate 2 different output voltages at the same time

ShuntLDO: Working Principle


- combination of a LDO and a shunt transistor:
 - R_{slope} of the shunt is replaced by the LDO power transistor.
 - shunt transistor is part of the LDO load.
- **shunt regulation circuitry** ensures constant I_{load} :
 - I_{ref} set by R3, depends on V_{in} ($\rightarrow I_{\text{in}}$).
 - I_{M1} mirrored and drained in M5.
 - I_{M1} and I_{ref} compared in A3.
 - M4 shunts the current not drawn by the load.
- **LDO regulation loop** sets constant output voltage V_{out} :
 - LDO compensates output potential difference.

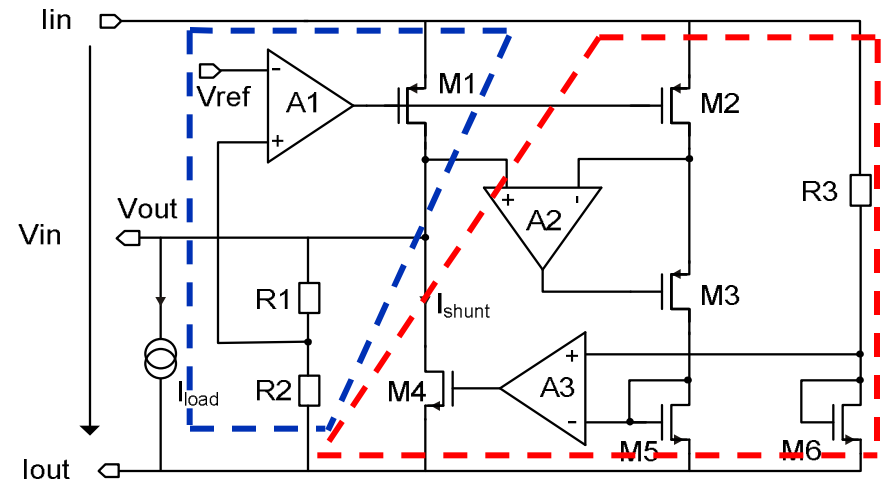

ShuntLDO: Features



- ShuntLDO regulators having different output voltages **can be placed in parallel** without any problem regarding mismatch & shunt current distribution.
 - resistor R3 mismatch will lead to some variation of shunt current (10-20%) but will not destroy the regulator.
- ShuntLDO **can cope with an increased supply current** if one FE-I4 does not contribute to the regulation e.g. disconnected wire bond.
 - I_{shunt} will increase
- can be **used as an ordinary LDO** when shunt is disabled.
- test results and more details: **see L. Gonella's talk.**

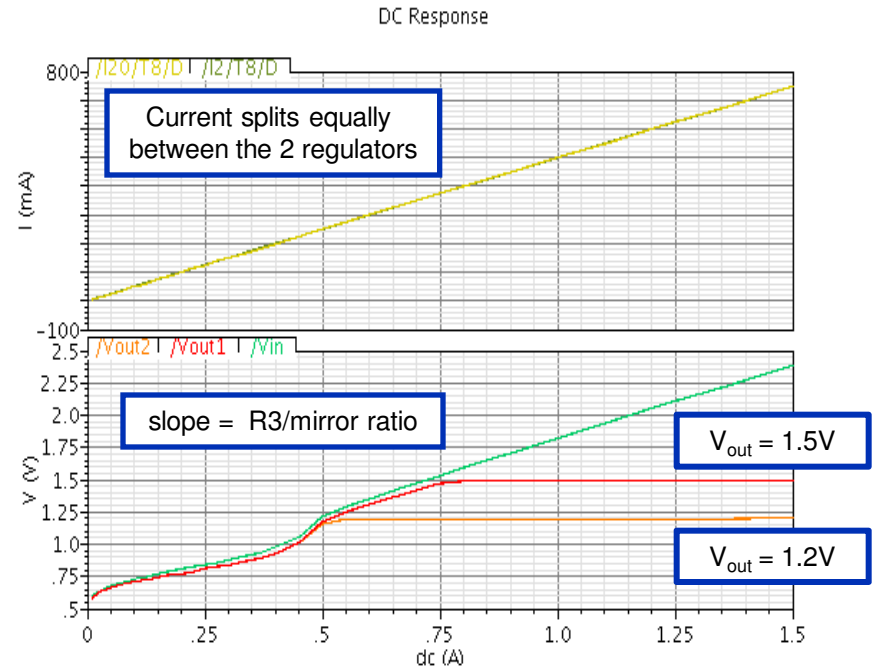Parallel placed regulators with different output voltages - simulation results -




- Crucial point for SP is the power efficiency of the power converter.
- For the ShuntLDO 3 sources of inefficiency:
 - Dropout voltage V_{drop}
 - Shunt current I_{shunt}
 - Difference between the 2 output voltages ΔV needed by the FE.
- Calculations with conservative assumptions for ATLAS Pixel:
 - $V_{\text{drop}} = 200\text{mV}$, $I_{\text{shunt}} = 30\text{mA}$, $\Delta V = 200\text{mV}$
 - Total current of the FE is 600mA with 250mV for the digital part at the lower output voltage of 1.2V.
- Power efficiency for single ShuntLDO is around 80% at realistic currents.
- Power efficiency for parallel operation of 2 ShuntLDOs at 1.2 and 1.4V is ~75%.


Power Efficiency of 2 parallel ShuntLDOs

 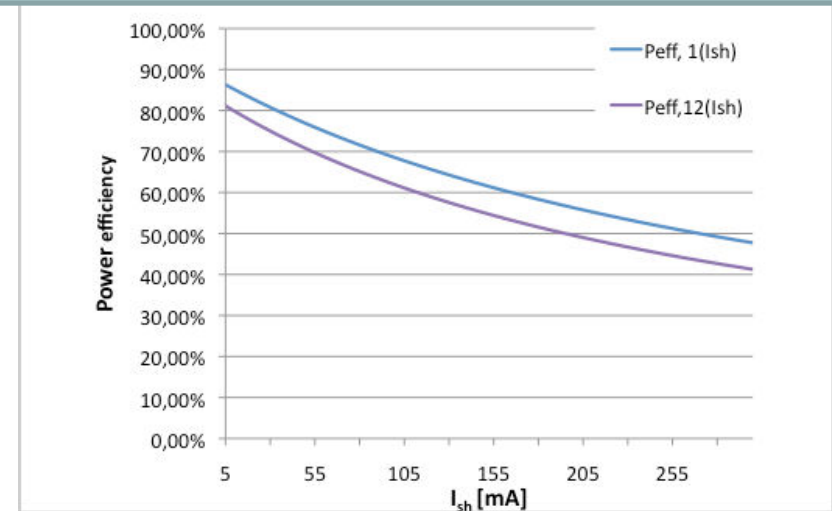

Protection for Serially Powered Staves



- Purpose:
 - Assure supply of power to the serially powered chain in case of failures.
 - Broken wire bonds, overvoltage.
 - Allow power to arbitrary selection of modules.
 - Switch off a noisy module.
- Requirements:
 - Slow Control: DCS should be able to switch off selected modules.
 - Fast Response: Over-voltage protection.
 - Residual voltage (when module off) < 100mV
 - During normal operation (module on) protection draws no power.
 - Minimise number of components, area of components and bus-cable lines.
 - Radiation hardness.
- Implementation for Pixel Stave:
 - Module Protection Chip.

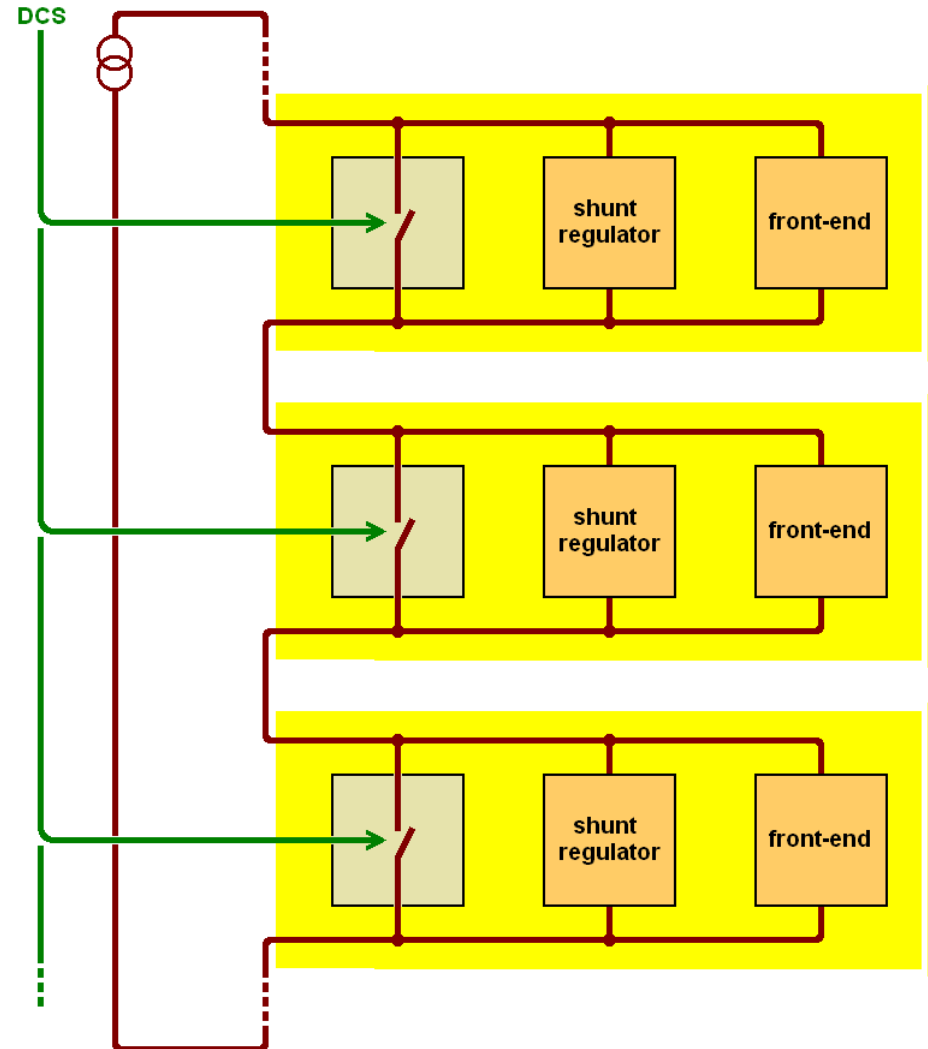

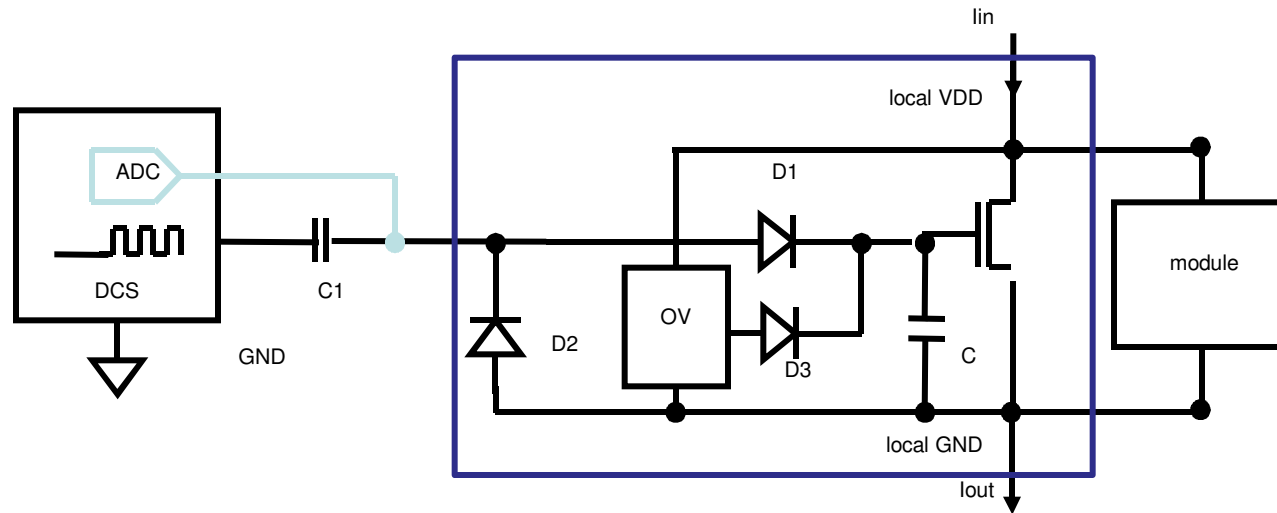


- 130nm CMOS technology.
- bypass transistor.
- AC-coupled slow control line:
 - can be used to monitor module voltage when idle.
- independent over voltage protection circuitry.
- development status (see L. Gonella's talk):
 - bypass transistor and slow control simulations completed.
 - over voltage protection circuitry in development.

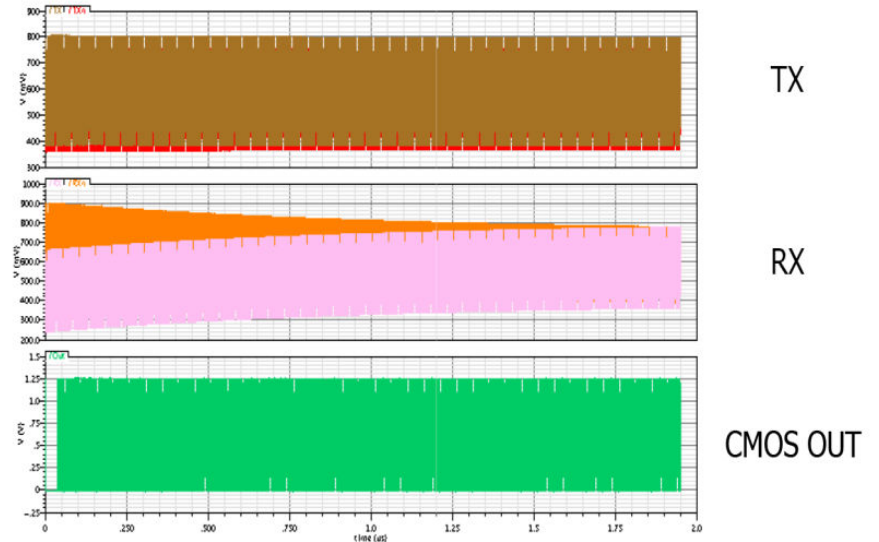 
- AC-coupling at LVDS TX/RX level:
 - Simple and less material.
 - Requires DC-balance and self-biased RX inputs.
 - Integrated self-biasing circuitry for LVDS RX input will be added in FE-14.
 - design finished.



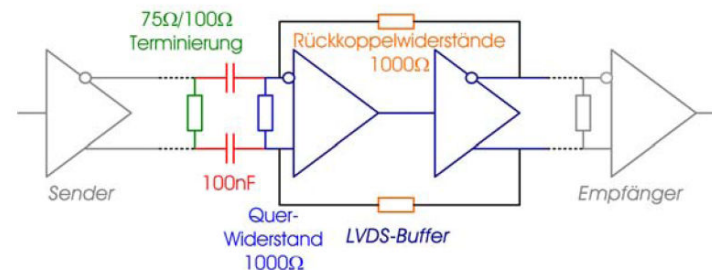- Otherwise usage of a link with feedback:
 - Used successfully in SP Proof of Principle.
 - No need for DC balancing and self-biasing.
 - Acts also as well as a fail safe (keeps the last state).



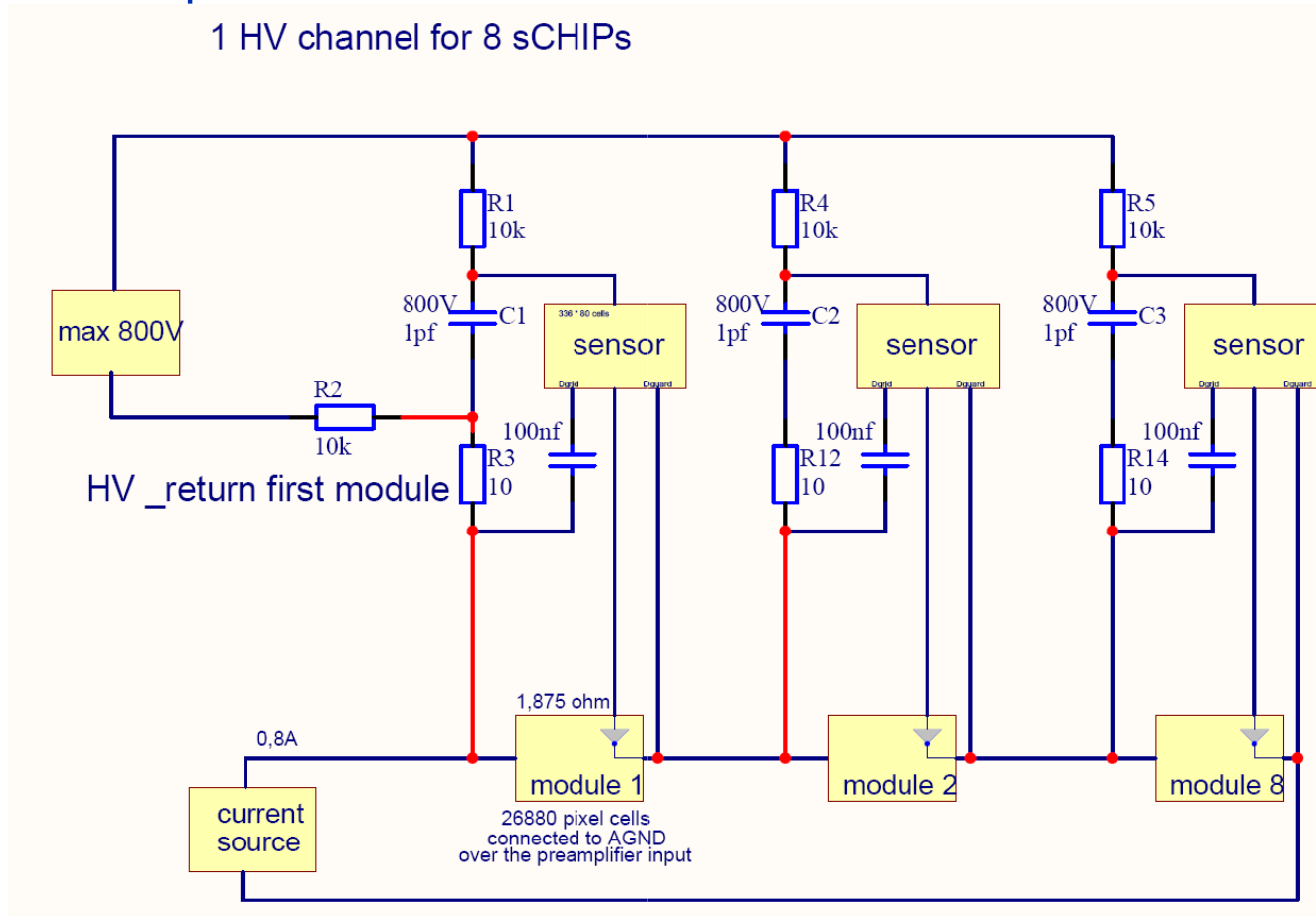- Use one floating HV supply per module → no problem.
- Use 1 HV supply per power group → several schemes possible, e.g. using the serial power line as HV return.



- A **serial powering scheme** for the ATLAS pixel detector for sLHC is being developed in Bonn:
 - A new regulator concept, the **SHULDO**, has been successfully prototyped and tested, with a **nominal power efficiency of 75%** for 2 SHULDO in parallel generating different output voltages.
 - A **protection scheme** for the SP chain of modules is being developed which includes both slow control and real time response.
 - **AC-coupling** at TX/RX level is preferred and thus a self-biasing LVDS RX input circuitry will be implemented in FE-I4.
 - **HV distribution** options have been proposed and will be tested.
- **Realistic SP system tests** will start as soon as FE-I4 module prototypes are available.
- Systems tests can (and have) already start with the **pixel stave emulator**, see L. Gonella's talk.