



Stave Emulator and Regulator Test


L. Gonella, D. Arutinov, M. Barbero, A. Eyring, F. Hügging, M. Karagounis, H. Krüger, N. Wermes
Physikalisches Institut, Uni Bonn

Stave Emulator Test Bench

- ▶ The stave emulator is a **test system** which allows to evaluate system aspects and custom developed hardware for the ATLAS Pixel Detector for sLHC, such as
 - ▶ physical layer data transmission: LVDS drivers/receivers, cables, connectors, ...
 - ▶ data coding schemes: raw, 8B/10B, 64B/66B, ...
 - ▶ powering concepts: serial, dc-dc, switched cap, ...
 - ▶ DCS concepts: voltage monitoring, control of bypass switch, reset, ...
 - ▶ data management of the End-Of-Stave controller, ...
 - ▶ ...
- ▶ It uses
 - ▶ FPGAs to emulate the modules and the end-of-stave controller
 - ▶ interconnection boards to provide support for different cable and connector options, LVDS transceiver chips, power supply options (parallel, DC/DC or SP), AC-coupling
 - ▶ a DCS test board (COBOLT) developed in Wuppertal providing multi-channel ADC and GPIO to test DCS functionalities



→ flexible and realistic test bench

Stave Emulator

 

End-Of-Stave emulator unit

Module emulator unit

  

Hardware

▶ FPGA Boards

▶ Module → Spartan 3E FPGA

- ▶ Commercial FPGA board (Trenz TEO300B)
- ▶ Spartan XC3S1600E, 64 Mbyte DDR RAM, 32 Mbit Flash, USB interface
- ▶ Approx. size of a 2x2 FE-I4 module


▶ End-Of-Stave Controller → Virtex4 FPGA

- ▶ FPGA board developed in Bonn for read-out of DEPFET modules
- ▶ XILINX Virtex 4 LX40-1148, 288Mbit RLDRAM – Should be able to handle >14.4Gbit/s, μ C-based system monitor (ADMI062), USB 2.0 connector, 16Mbit async. SRAM, EUDET TLU connection, Multiple high speed connectors


▶ Interconnection boards

- ▶ Custom developed
- ▶ Tailor different test wishes (data transmission, powering option, ...)
- ▶ Define successive stave emulator versions
 - ▶ Iterate the design of interconnection boards to add more functionalities and custom developed hardware when available

Spartan 3E board

 

VIRTEX4 board

 


Firmware and Software

- ▶ Firmware for data transmission tests
 - ▶ PRBS of different length, 8b10b encoded data
 - ▶ FE-I4 code for Spartan3E
 - ▶ Bit Error Rate firmware for Virtex4
 - ▶ uses PRBS;
 - ▶ clock frequency synthesized with Digital Clock Manager;
 - ▶ compares data out with data in;
 - ▶ delay adjustment between data out and data in done in 2 steps: coarse delay = 1 clk period, fine delay = 75ps



- ▶ Software
 - ▶ Application developed with C++ and Qt (GUI) allows to download firmware on the FPGA, read/write data from/to FPGA

Baseline Design

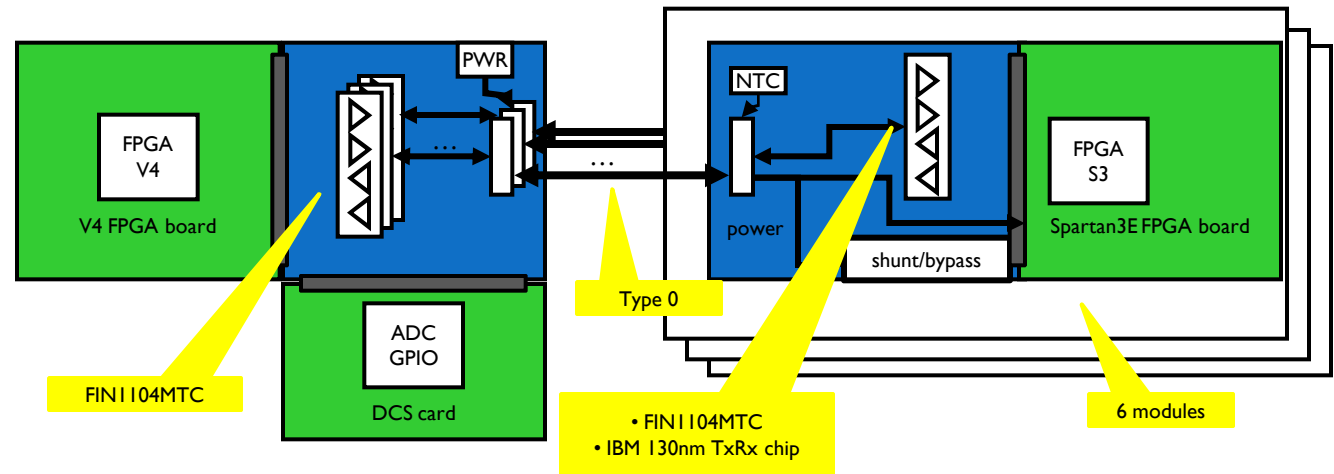

- ▶ “6 modules-stave”
- ▶ Connection EoS - module using **Type 0** cable
- ▶ Powering
 - ▶ parallel
 - ▶ serial using commercial shunt regulator
 - ▶ commercial bypass transistor on modules to test protection option
- ▶ DC-coupled data transmission with different **LVDS** transceiver chips
 - ▶ on End-Of-Stave side: commercial FINI I04MTC transceiver chip
 - ▶ on module side: commercial FINI I04MTC or IBM I30nm transceiver chip (i.e. FE-I4 LVDS TX and RX)
- ▶ **NTC** to measure module temperature

Tests with Baseline Design

▶ Bit Error Rate Tests

- ▶ study the performance of the LVDS TX and RX for FE-I4
 - ▶ Comparison with commercial transceiver chip
 - ▶ $V_{dd} = 1.2-1.5V$
 - ▶ I_{bias} higher than nominal
 - ▶ parallel powering, DC coupled data transmission, PRBS8-16-24, 160Mbps
- IBM 130nm transceiver chip runs error free with PRBS24 at 160Mbps with $V_{dd} = 1.2V$ ($38e^{12}$ bits transmitted)

		Nominal	1.2V	1.5V
RX	I_{bn}	-35uA	-100uA	-150uA
	I_{bp}	35uA	60uA	90uA
TX	I_{bp}	60uA	60uA	90uA
	U_{bias}	600mV (1.2V) 750mV (1.5V)	600mV	750mV



▶ Tests with COBOLT

- ▶ Serial powering chain
- ▶ Some DCS functionalities have been successfully tested
 - ▶ module temperature measuring with NTC
 - ▶ control of bypass transistor
 - ▶ monitoring of module voltage through bypass control line

Next Stave Emulator Version

- ▶ Second version of interconnection board for module emulator unit available
 - ▶ more custom-developed hardware
 - ▶ IBM I30nm LVDS transceiver chip
 - ▶ External biasing circuitry for RX inputs (→ AC-coupled data transmission)
 - ▶ IBM I30nm LVDS tri-state driver
 - ▶ ShuntLDO regulator
- ▶ Test plan
 - ▶ AC-coupling at TX/RX level with FEI4 LVDS transceiver chip
 - ▶ Multiplexing of data out of different FEs
 - ▶ w/ tri-state driver
 - ▶ FEs in master-slave configuration
 - ▶ Test of ShuntLDO regulator in a real serially powered system
 - ▶ Test of ShuntLDO pure LDO regulator operation with shunt capability switched-off

  
possible RX inputs self-biasing integrated circuit for FE-I4



Goal: Set up a serially powered stave with AC-coupled data transmission and FE data output multiplexing, using real FE-I4 components

ShuntLDO: Working Principle


- ▶ combination of a LDO and a shunt transistor
 - ▶ R_{slope} of the shunt is replaced by the LDO power transistor
 - ▶ shunt transistor is part of the LDO load
- ▶ **shunt regulation circuitry** ensures constant I_{load}
 - ▶ I_{ref} set by R3, depends on V_{in} ($\rightarrow I_{\text{in}}$)
 - ▶ I_{M1} mirrored and drained in M5
 - ▶ I_{M1} and I_{ref} compared in A3
 - ▶ M4 shunts the current not drawn by the load
- ▶ LDO regulation loop sets constant output voltage V_{out}
 - ▶ LDO compensates output potential difference

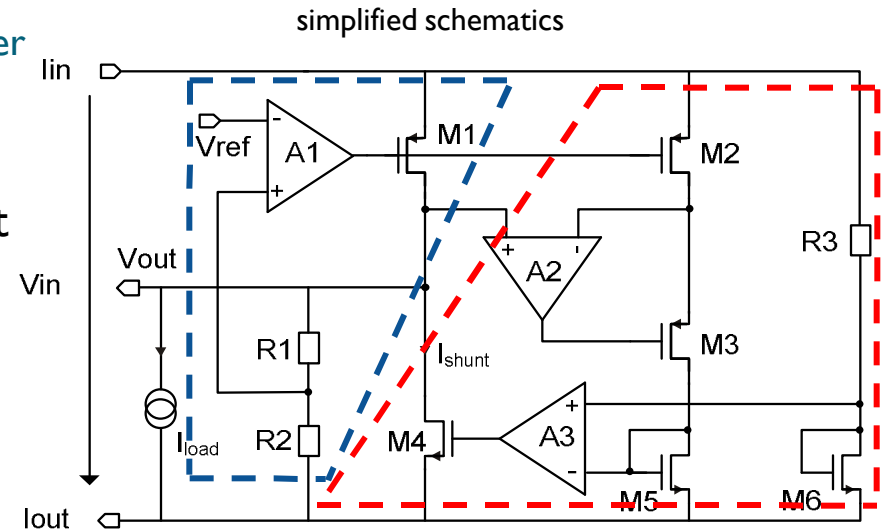

ShuntLDO : Features



- ▶ ShuntLDO regulators having different output voltages **can be placed in parallel** without any problem regarding mismatch & shunt current distribution
 - ▶ resistor R3 mismatch will lead to some variation of shunt current (10-20%) but will not destroy the regulator
- ▶ ShuntLDO **can cope with an increased supply current** if one FE-I4 does not contribute to the regulation e.g. disconnected wire bond
 - ▶ I_{shunt} will increase
- ▶ can be **used as an ordinary LDO** when shunt is disabled

 Parallel placed regulators with different output voltages
- simulation results -





ShuntLDO : Prototypes and Test System

- ▶ 2 prototypes submitted and tested
 - ▶ September 2008, March 2009
 - ▶ $V_{out} = 1.2-1.5V$, $V_{dropout} MIN = 200mV$, $I_{shunt} MAX = 0.5A$, $R_{in} = 4\Omega$, $R_{out} = 30m\Omega$
- ▶ test setup
 - ▶ two ShuntLDO regulators connected in parallel on the PCB
 - ▶ biasing & reference voltage is provided externally
 - ▶ input & load current is provided by programmable Keithley sourcemeter
 - ▶ input & output voltages are measured automatically using a Labview based system
 - ▶ shunt current is measured by $10m\Omega$ series resistors and instrumentation opamp

 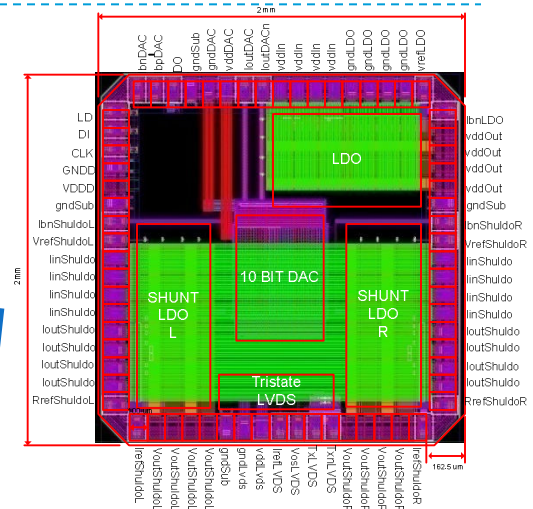

2 ShuntLDO in Parallel



- ▶ Load Regulation Measurement
 - ▶ 1.5(1.2)V output sees fix $I_{load} = 0.4A$
 - ▶ 1.2(1.5)V output has variable I_{load}
 - ▶ V_{in} and V_{out} collapse when the overall I_{load} reaches I_{supply} ($= 0.8A$)
 - ▶ effective output impedance $R = 60m\Omega$ (incl. wire bonds and PCB traces)
- ▶ Generation of different V_{out}
 - ▶ V_{out} settles at different potentials
 - ▶ V_{out1} and V_{out2} slightly decrease with rising input current (V drop on ground rails leads to smaller effective reference voltages)
 - ▶ non constant slope of V_{in}
 - ▶ $R_{in} \approx 2\Omega$ (after saturation)

  

Shunt Current Distribution at Start-Up

- ▶ unbalanced I_{shunt} distribution at start-up
 - ▶ more I_{shunt} flows to the regulator which saturates first (i.e. to the regulator with lower V_{out})
 - ▶ however $I_{shunt,MAX}$ is not exceeded
- ▶ improvement of shunt distribution as soon as both transistors are saturated
- ▶ non - constant slope of V_{in} closely related to I_{shunt} distribution
- ▶ bad mirroring accuracy for non saturated transistors due to offset at the input of A2
 - ▶ wrong current is compared to the reference
- ▶ hypothesis confirmed by simulations and second prototype
 - ▶ scaling of input transistor of A2 by factor 4 halves the unbalance

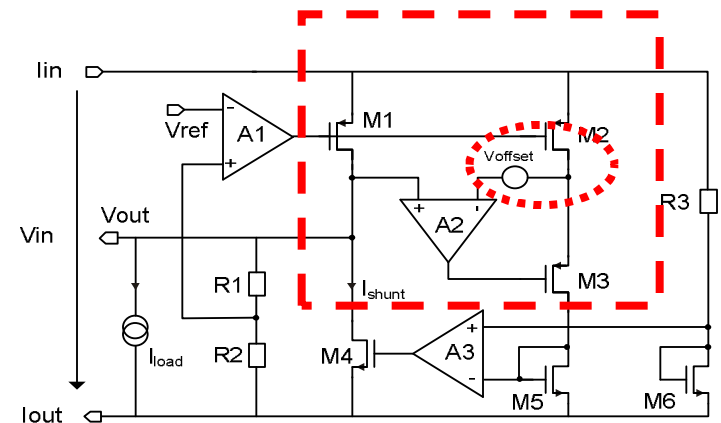
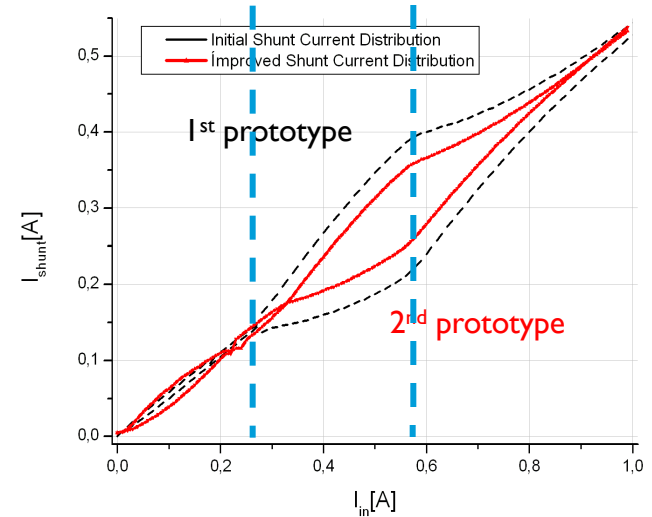
2 SHULDOS in parallel with different V_{out}



Shunt Current Distribution

- ▶ no problem at start-up if the 2 ShuntLDOs generate the same V_{out}
 - ▶ they saturate at the same time
 - ▶ if V_{out} is changed with both regulators being saturated the shunt current changes of about 1.4%
- Unbalanced I_{shunt} at start-up can be avoided completely by choosing the same V_{out} at start-up and setting different V_{out} afterwards

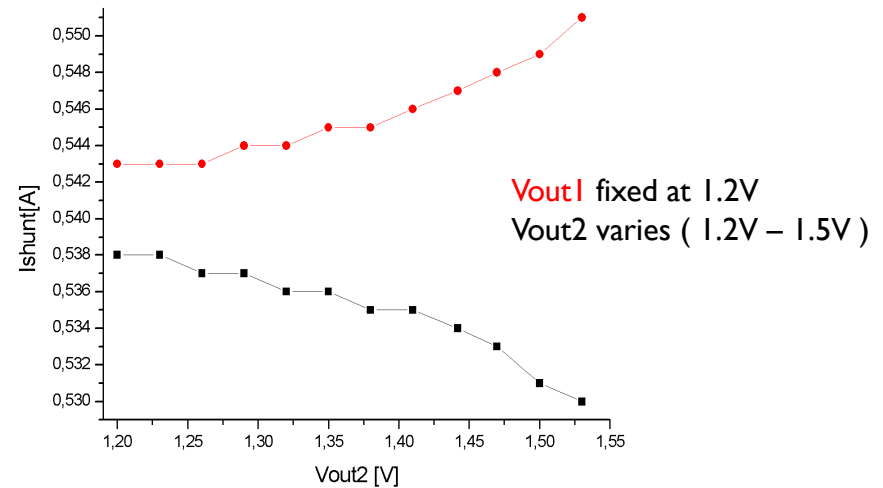 
2 ShuntLDOs in parallel with same V_{out} at start-up



ShuntLDO Efficiency


- ▶ Crucial point for SP is the power efficiency of the power converter
- ▶ 3 possible sources of inefficiency for the ShuntLDO
 - ▶ Dropout voltage V_{drop}
 - ▶ Shunt current I_{shunt}
 - ▶ ΔV between the 2 V_{out} needed by the FE
- ▶ Calculation for ATLAS Pixels

	nominal	worst case	best
V_{out1} [V]	1.4	1.4	1.4
V_{out2} [V]	1.2	1.2	1.2
I_{out1} [A]	0.36	0.4	0.36
I_{out2} [A]	0.24	0.27	0.24
V_{drop} [V]	0.2	0.2	0.1
I_{shunt} [A]	0.03	0.05	0.01
ΔU [V]	0.2	0.3	0.2
I_{TOT} [A]	0.6	0.67	0.6
$P_{\text{eff, 1}}$	80.77%	77.78%	90.81%
$P_{\text{eff, 2}}$	66.67%	59.56%	76.80%
$P_{\text{eff, 1-2}}$	79.55%	76.14%	90.32%
$\Delta P_{\text{eff, 1-2}}$	4.55%	6.57%	5.16%
$P_{\text{eff, 1-2g}}$	75.00%	69.56%	85.16%

 

Module Protection Chip


- ▶ 130nm CMOS technology
- ▶ Bypass transistor
- ▶ AC-coupled slow control line
 - ▶ can be used to monitor V_{mod} when idle
- ▶ Independent over voltage protection circuitry
- ▶ Specs for 4-chip FE-I4 module^(*)
 - ▶ $I_{\text{nom}} = 2.4\text{A}$, $I_{\text{MAX}} = 3.5\text{A}$
 - ▶ AC-signal frequency = 100k – 1MHz
 - ▶ AC-signal amplitude = V_{gs} bypass
 - ▶ OV protection threshold: $V_{\text{thMIN}} = 2\text{V}$ – $V_{\text{thMAX}} = 2.5\text{V}$
 - ▶ OV protection time response = 100ns

 

^(*) preliminary

Bypass Transistor

- ▶ $I = 3.5A, V \geq 1.6V$ (max 2.5V)
→ DG NMOS
- ▶ Radiation hardness
 - ▶ ELT to cut leakage current path
 - ▶ Positive V_{th} shift at $TID \geq 1Mrad$
 - ▶ Account for $\Delta V_{th} = 200mV$ in simulations
- ▶ Operational temperature
 - ▶ Not yet defined, will depend on the sensor
 - ▶ Simulations with $T = (-27 \div +27)^\circ C$
- ▶ Low power consumption when on
- ▶ Process Corners
→ $W = 48mm, L = 0.24\mu m$

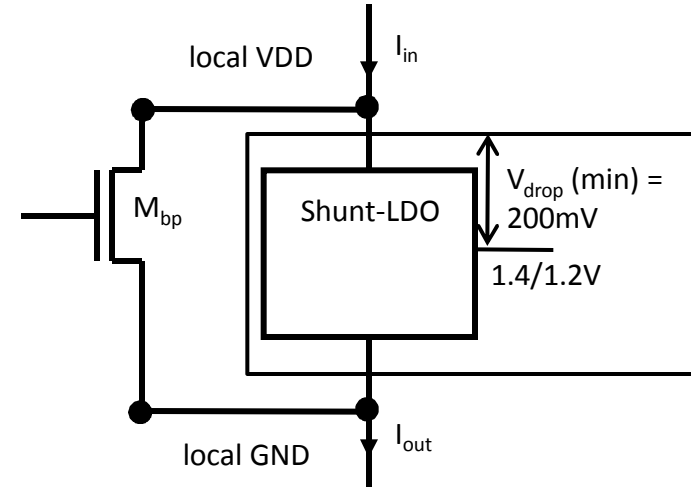


- ▶ Power consumption (worst case)
 - ▶ Bypass on → 335.1mW
 - ▶ Bypass off → 25 μ W

Control Line



▶ Rectifier

- ▶ In a diode connected MOSFET $V_{ds} = V_{gs} \approx V_{th}$
- ▶ To increase the power conversion efficiency
 - ▶ $V_{sb} < 0$ when diode is forward biased $\rightarrow V_{th}$ smaller $\rightarrow V_{ds}$ smaller
 - ▶ $V_{sb} > 0$ when diode is reversed biased $\rightarrow V_{th}$ higher \rightarrow smaller leakage current \rightarrow use PMOS or triple well NMOS (allow to connect bulk in the “forward direction”)
- ▶ Thin oxide transistor
 - ▶ $W = 10\mu\text{m}$ for radiation hardness
 - ▶ 2 PMOS in series to avoid gate oxide breakdown (AC-signal amplitude $> 2.5\text{V}$)

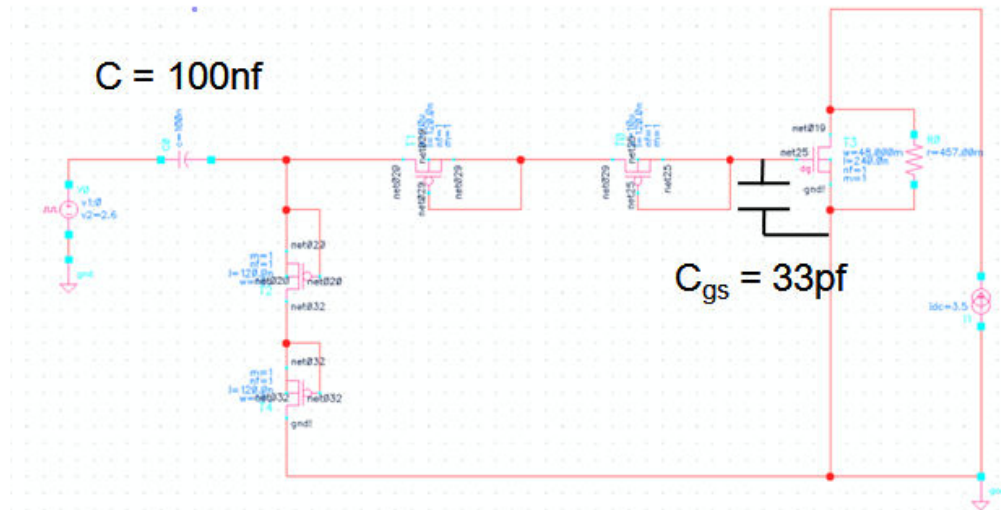

Control Line: Simulation Results

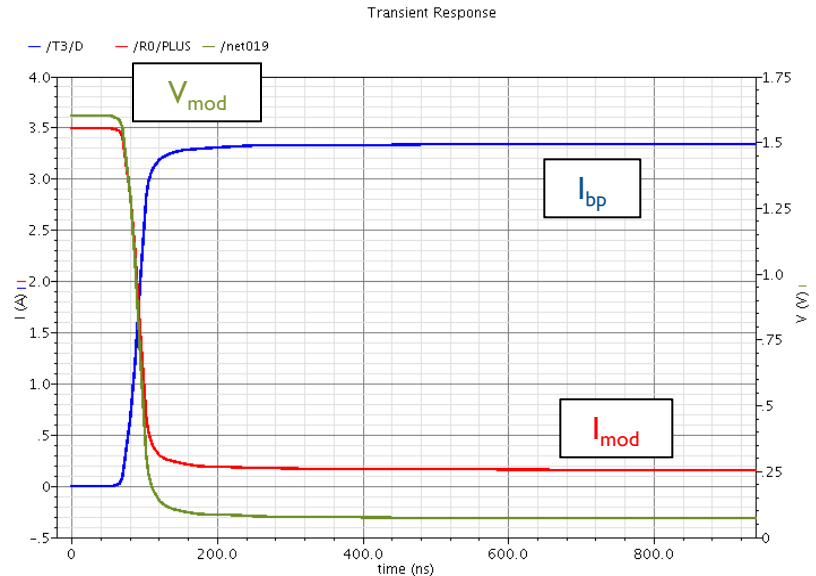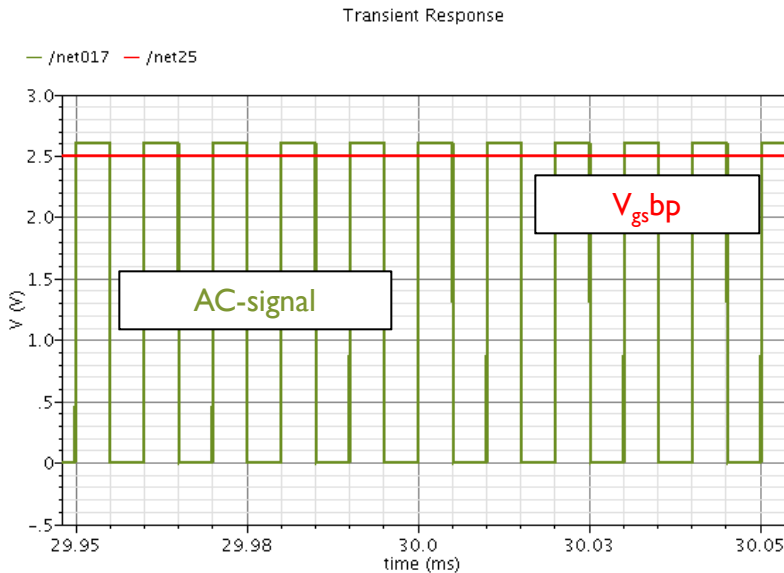
- ▶ AC-signal: 2.6V, $f = 100\text{k} - 1\text{MHz}$
 - ▶ V_{gs} bypass: 2.5V
 - ▶ V_{mod} : 1.6V $\rightarrow \sim 60\text{mV}$
 - ▶ I_{mod} : 3.5A $\rightarrow \sim 100\text{mA}$
- Control from DCS works fine




Over-Voltage Protection

▶ Silicon Controlled Rectifier

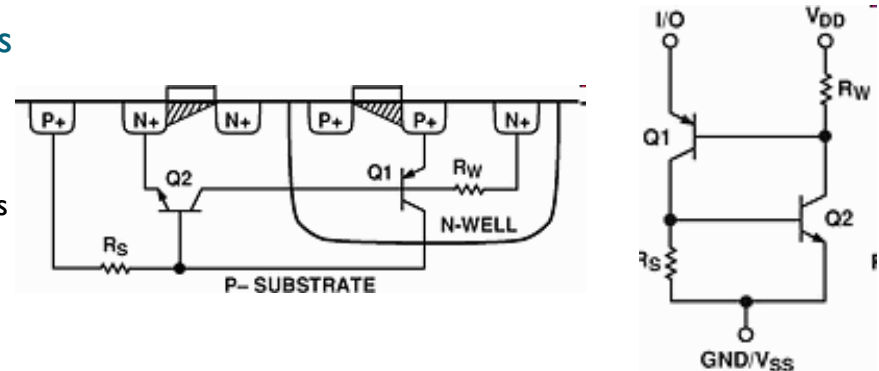- ▶ Parasitic elements (BJTs) in CMOS technologies (inverter in IO pads)
- ▶ Latch-up condition: I/O voltage ($U_{E^{Q1}}$) $>$ VDD
 - ▶ Q1 begins to conduct \rightarrow Q2 switches on \rightarrow Q1 draws even more current
- ▶ Shorts the supply rails when triggered
- ▶ That is exactly what we want!




 - ▶ Use MOSFETS instead of parasitic BJTs for better control of operation parameters
- ▶ Trigger threshold defined by $R2/R1$
- ▶ Want to draw high currents
 - ▶ $R1$ small
 - ▶ or use additional 'power' NMOS \rightarrow bypass



SCR: Simulation Results

- ▶ Sweep of $R_{\text{mod}} \rightarrow V_{\text{mod}}$ increases, I_{mod} constant
- ▶ The voltage across the module is effectively clamped down when the SCR activates, however
 - ▶ $V_{\text{ds,bp}} = V_{\text{gs,bp}} \rightarrow$ impossible to get $V_{\text{mod}} = 100\text{mV}$ and $V_{\text{gs,bp}} = 2.5\text{V}$
 - ▶ $V_{\text{mod}} = 850\text{mV}$ & $I_{\text{bp}} \approx 3\text{A} \rightarrow$ too high power density
- ▶ A SCR is not the optimal solution for our needs and a different OV protection scheme has to be studied

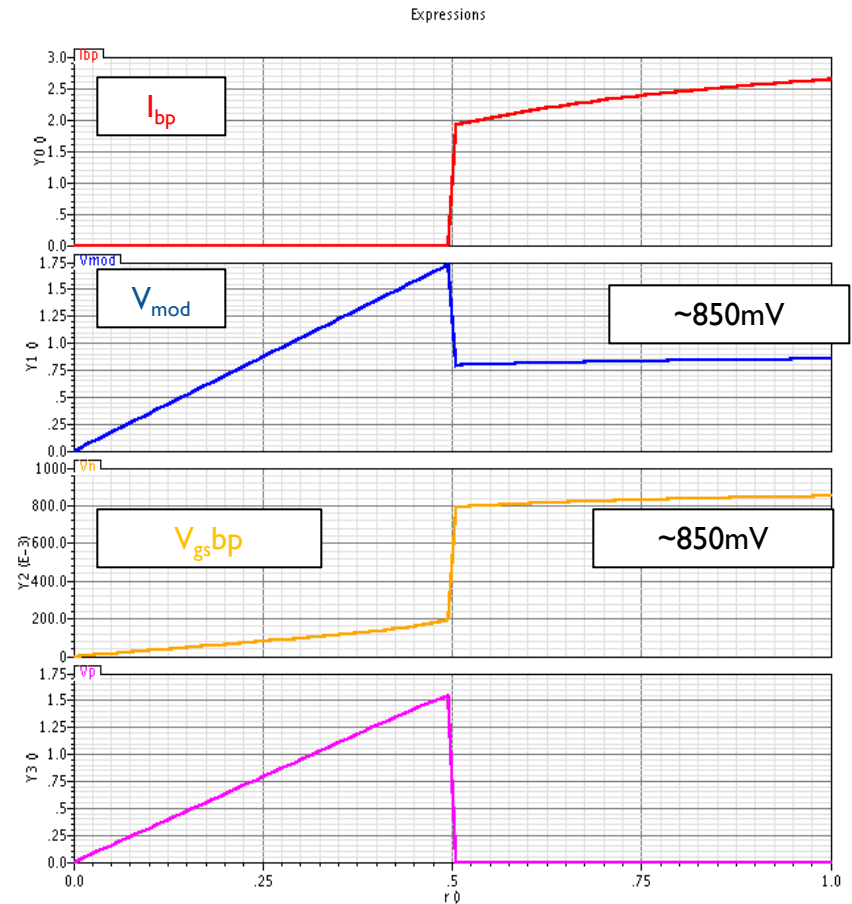


Summary


- ▶ A stave emulator has been developed which allows study of system aspects related to serial powering
 - ▶ A baseline design has been set up and the FE-I4 LVDS transceiver has been tested, as well as some DCS functionalities
 - ▶ A serial powered emulator stave is under development to study ShuntLDO performance and AC-coupled data transmission
- ▶ Characterization of the ShuntLDO has been performed on single devices, with nominal current and voltage values
 - ▶ Results show that the ShuntLDO performs according to specifications with a nominal power efficiency of 75%
 - ▶ Problems with shunt current distribution have been understood and corrected in next version
- ▶ Work is ongoing on the Module Protection Chip

SHULDO: Load Transient Behavior

 - ▶ I_{load} pulse of 150mA (15mV measured across 100m Ω)
- ▶ 10mV output voltage change



SHULDO Efficiency

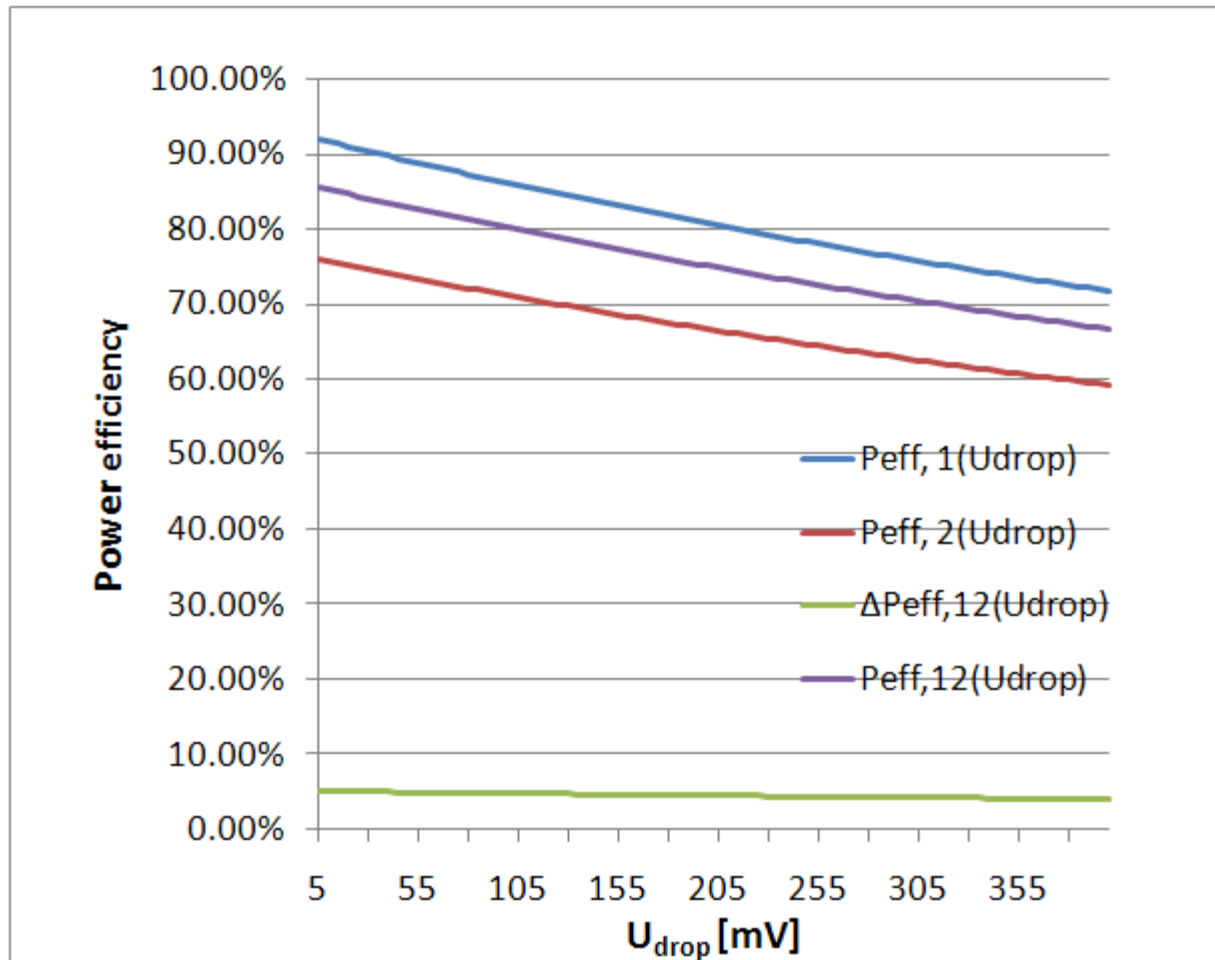

SHULDO Efficiency

