



COMPARATIVE STUDY OF TWO-QUADRANT DC/DC STAGE IN POWER SUPPLY FOR SUPERCONDUCTING MAGNETS

E. Coulinge - J-P. Burnet - S. Pittet

CERN - Electrical Power Converter (EPC)
Low Power Converter (LPC)



OUTLINE

Introduction

- From LHC to HL-LHC
- HL-LHC operation

Output DC/DC stage

- 2-quadrant 18 kA converter
- 2 kA sub-converter modulation strategies
- 2 kA sub-converter loss map
- 2 kA sub-converter performance comparison


Conclusions

- Ongoing activities


FROM LHC TO HL-LHC



▲ Actual 1-quadrant 6 kA converter

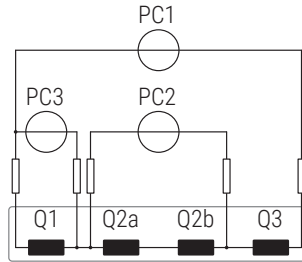


▲ LHC powering scheme

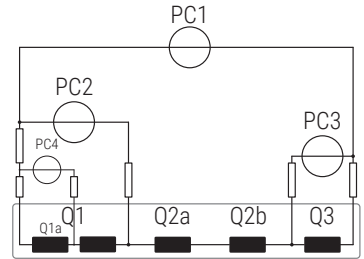

▲ HL-LHC powering scheme

HL-LHC OPERATION

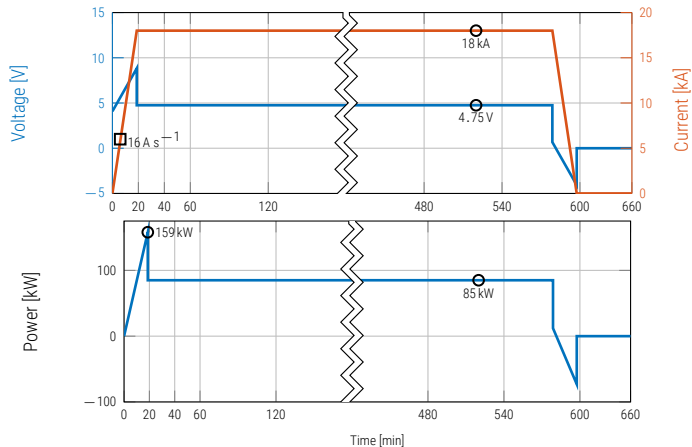- Minimal resistance to the load:
 - Superconducting link
- Cycling operation:
 - Constraint on ramp-down time
- Minimal power taken from the grid:
 - Philosophy for new developments




■ Key numbers:

$$I_{\text{RATED}} = 18 \text{ kA}$$
$$V_{\text{RATED}} = \pm 10 \text{ V}$$


$$L_{\text{LOAD}} = 255 \text{ mH}$$
$$R_{\text{LOAD}} \leq 0.26 \text{ m}\Omega$$
$$P_{\text{LOAD[peak]}} = 159 \text{ kW}$$

$$I_{\text{uncertainty}} = 18 \text{ mA (1 ppm)}$$

2-QUADRANT 18 KA CONVERTER

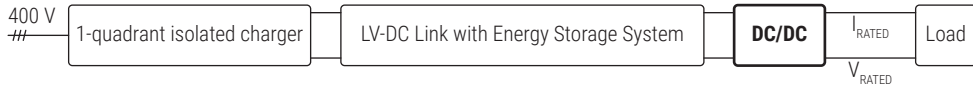

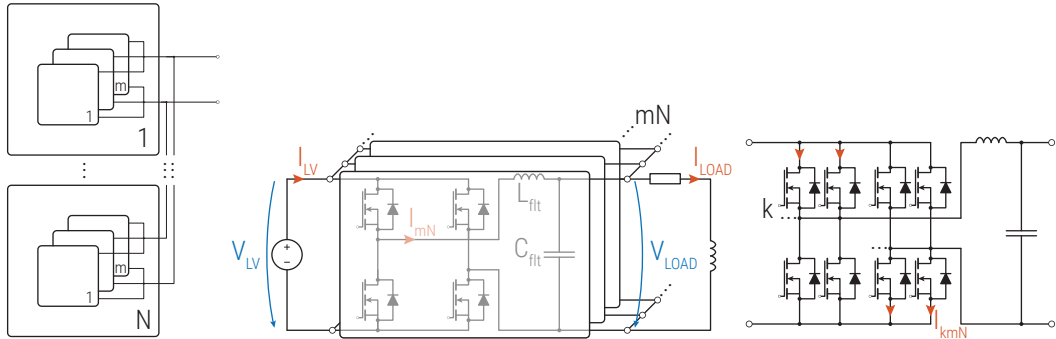
- Paralleling is needed to reach 18 kA
- Converter modularity:
 - The converter is divided in N sub-converters rated 2 kA each, $N + 1 = 9 + 1$
 - The sub-converter is divided in m branches, m to be defined
 - Each sub-converter composed of a charger, an energy storage system and an output DC/DC will be integrated in a rack
 - The branch is composed by k devices in parallel, k to be defined



▲ Topology and modularity concept


2 KA SUB-CONVERTER MODULATION STRATEGIES

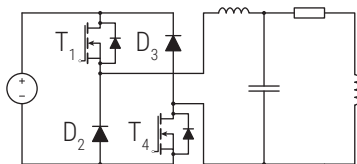- 2-quadrant operation required:
 - Four different modulation strategies are compared:
 - 2-quadrant with diode (2Q)
 - 2-quadrant with synchronous rectification (2QSR)
 - 4-quadrant with bipolar modulation (4QBI)
 - 4-quadrant with unipolar modulation (4QUNI)
 - Different performances
 - Different controllability



Mode	T ₁	D ₂	D ₃	T ₄
$V_{LOAD} \geq 0$	d	$1 - d$	blk	on
$V_{LOAD} \leq 0$	off	cond	$1 - d$	d

▲ 2-quadrant operation with diode

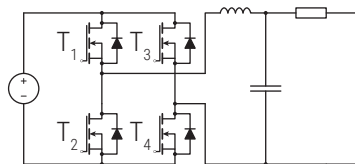

Mode	T ₁	T ₂	T ₃	T ₄
$V_{LOAD} \geq 0$	d	$1 - d$	off	on
$V_{LOAD} \leq 0$	off	on	$1 - d$	d


▲ 2-quadrant operation with synchronous rectification

Mode	T ₁	T ₂	T ₃	T ₄
bipolar	d	$1 - d$	$1 - d$	d
unipolar	d	$1 - d$	d	$1 - d$


▲ 4-quadrant bi-/uni-polar modulation

2 KA SUB-CONVERTER LOSS MAP

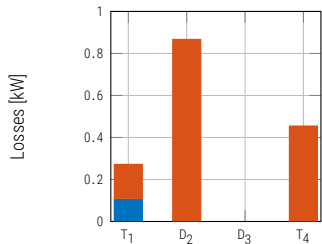
- Depends on the modulation strategy
- Given for one configuration:
 - Operating point: flat-top, 4.75 V; 2 kA; 9.5 kW
 - Switching frequency: 50 kHz
 - Number of MOSFETs:
 - $m \times k = 14$
 - Total for the *sub-converter* $14 \times 4 = 56$
 - Reference device: IXYS GigaMOS 75 V; 500 A@25 °C



▲ 2-quadrant operation with diode

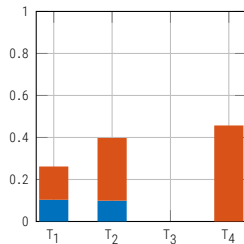


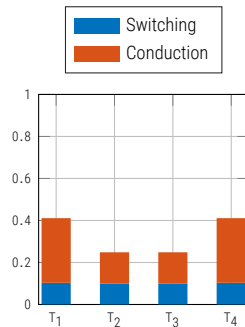▲ 2-quadrant operation with synchronous rectification



▲ 4-quadrant bi-/uni-polar modulation


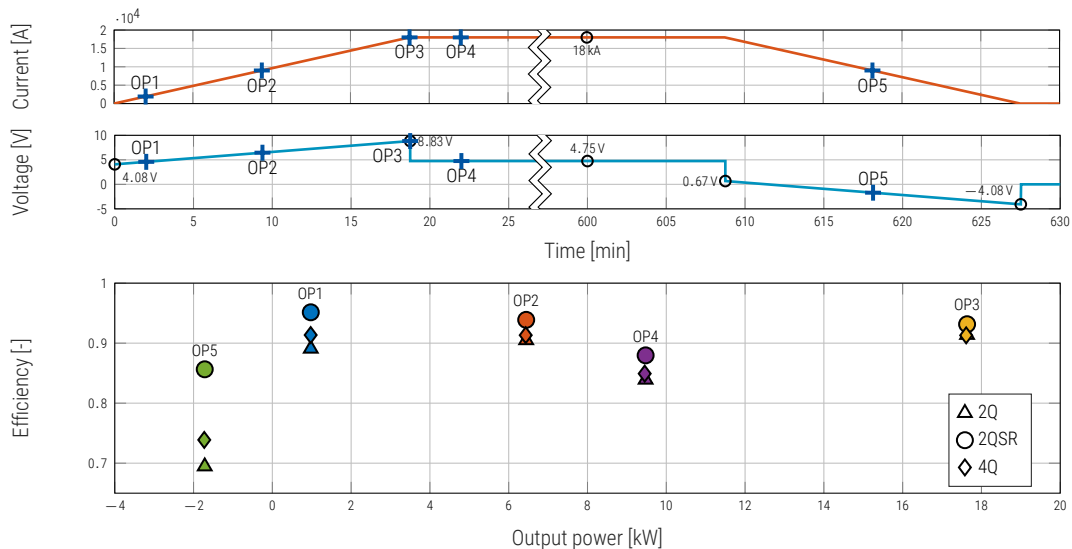
2 KA SUB-CONVERTER PERFORMANCE COMPARISON



ONGOING ACTIVITIES

■ MOSFET characterization setup:

- Follow device selection process:
 - Electrical performances
 - Mechanical integration
- Selected component:
 - V_{DSS} : 60 V
 - I_{D25} : 260 A
 - PowerFLAT package
 - Above 95 % efficiency
 - 400+ MOSFETs per *sub-converter*
- Up to 10 devices in parallel:
 - Setup rated for 200 A
- Used to verify:
 - Parallel switching of several devices
 - Current sharing
 - Current limit
 - Switching frequency limit
 - Thermal behavior
- Carried out at EPFL

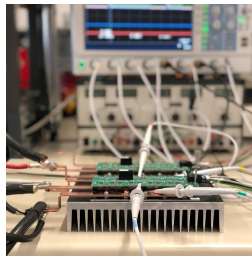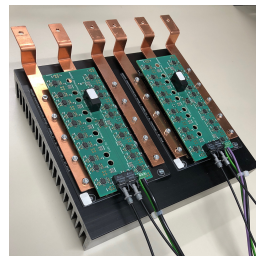

CONCLUSIONS

- Modulation strategy comparison:
 - Efficiency
 - Selected modulation is **2-quadrant with synchronous rectification**

- Next steps:
 - Complete MOSFET study using characterization setup:
 - Number of devices
 - Switching frequency
 - Magnetic components
 - Mechanical integration

- References:
 - E. Coulinge, J. P. Burnet and D. Dujic, "High-current low-voltage power supplies for superconducting magnets", 2017 International Symposium on Power Electronics (Ee), Novi Sad, 2017, EDMS 1832844
 - E. Coulinge, J. P. Burnet, D. Dujic and S. Pittet, "Comparative study of two-quadrant DC/DC stage in power supply for superconducting magnets", 2018 IEEE International Conference on Industrial Technology (ICIT), Lyon, 2018, EDMS 1918772
 - E. Coulinge, "18 kA Converter for HL-LHC Inner-Triplet, MOSFET Characterization Setup", internal presentation, EDMS 1887908

THANK YOU

Thank you for your attention



Any questions ?



COMPARATIVE STUDY OF TWO-QUADRANT DC/DC STAGE IN POWER SUPPLY FOR SUPERCONDUCTING MAGNETS

E. Coulinge - J-P. Burnet - S. Pittet

CERN - Electrical Power Converter (EPC)
Low Power Converter (LPC)

