

ESD Diode protection integration on chamber design


Hans Muller CERN PH

MM ATLAS 2008/9 Test setup

BAV 99 diodes to protect a “discrete-component” preamplifier

Summary

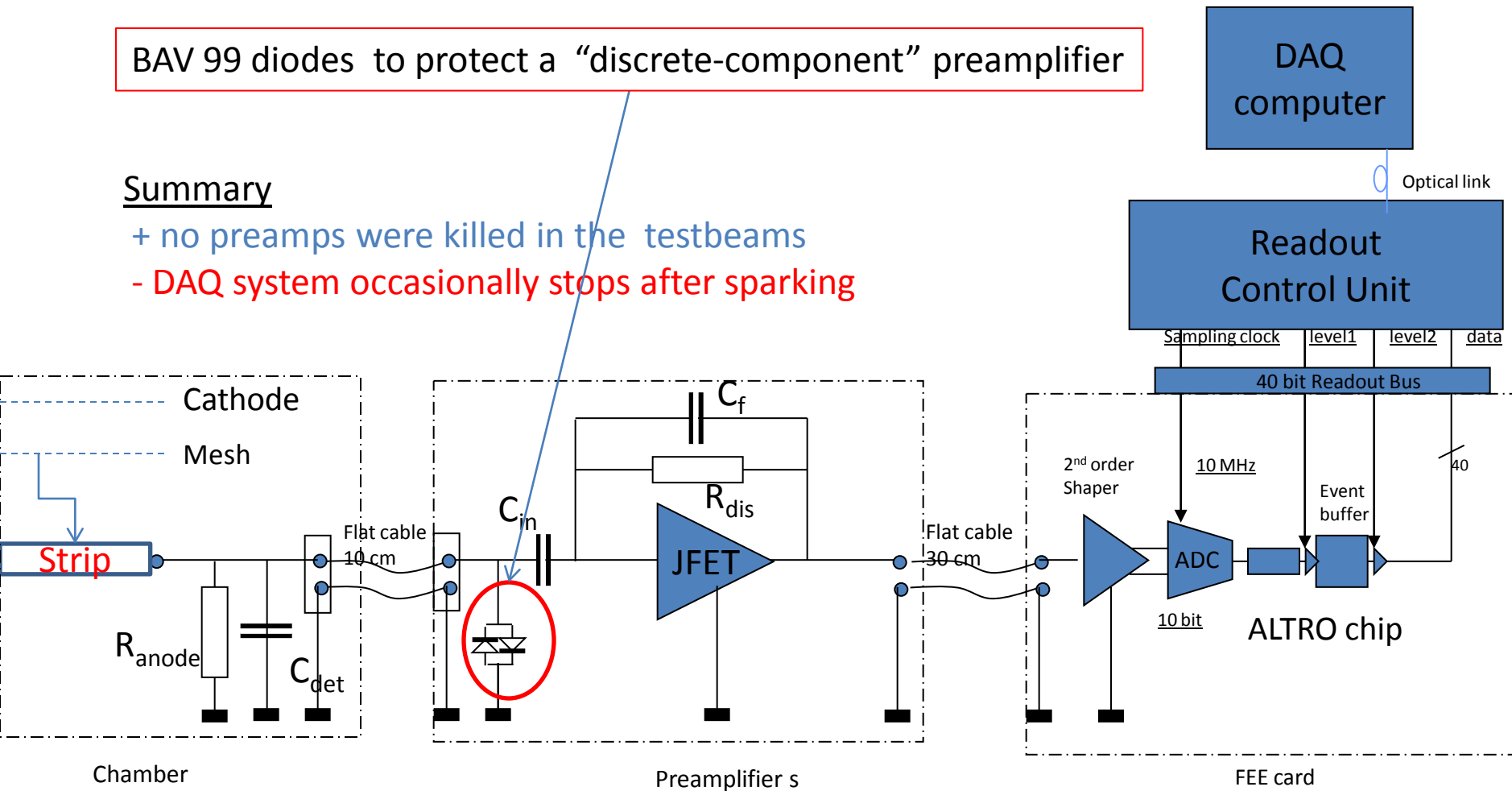- + no preamps were killed in the testbeams
- DAQ system occasionally stops after sparking



Lessons learnt from the 2008/9 system

A.) VITAL for commissionable operation

- Sparc protection: does it reliably protect chip-resident preamp inputs ?
- Spark protection to include readout immunity
- Crosstalk to be reduced
- Detector capacitance not to be altered by sparc protection
- real estate is a problem for discrete diodes

Proposed solution: ESD diodes on chamber +

- Capacitive coupling to preamp
- low impedance common grounding to chamber GND
- no signal cables to pre-amps
- chamber and pre-amp ground connected via low impedance plug
- new Industry ESD diodes made for sparc protection of Gigabit chips
- ESD diode ground must be quasi inductance-free to chamber ground
- reverse biased ESD diodes do not add more than $\sim 1\text{pF}$


B.) DESIRABLE for smooth operation

- Spark monitoring channel
- Test pulse for all channels

Proposed solution: pickup strip

- capacitive coupled common pickup strip for groups of strips
- pulse injection either via pickup strip or via Chip test feature

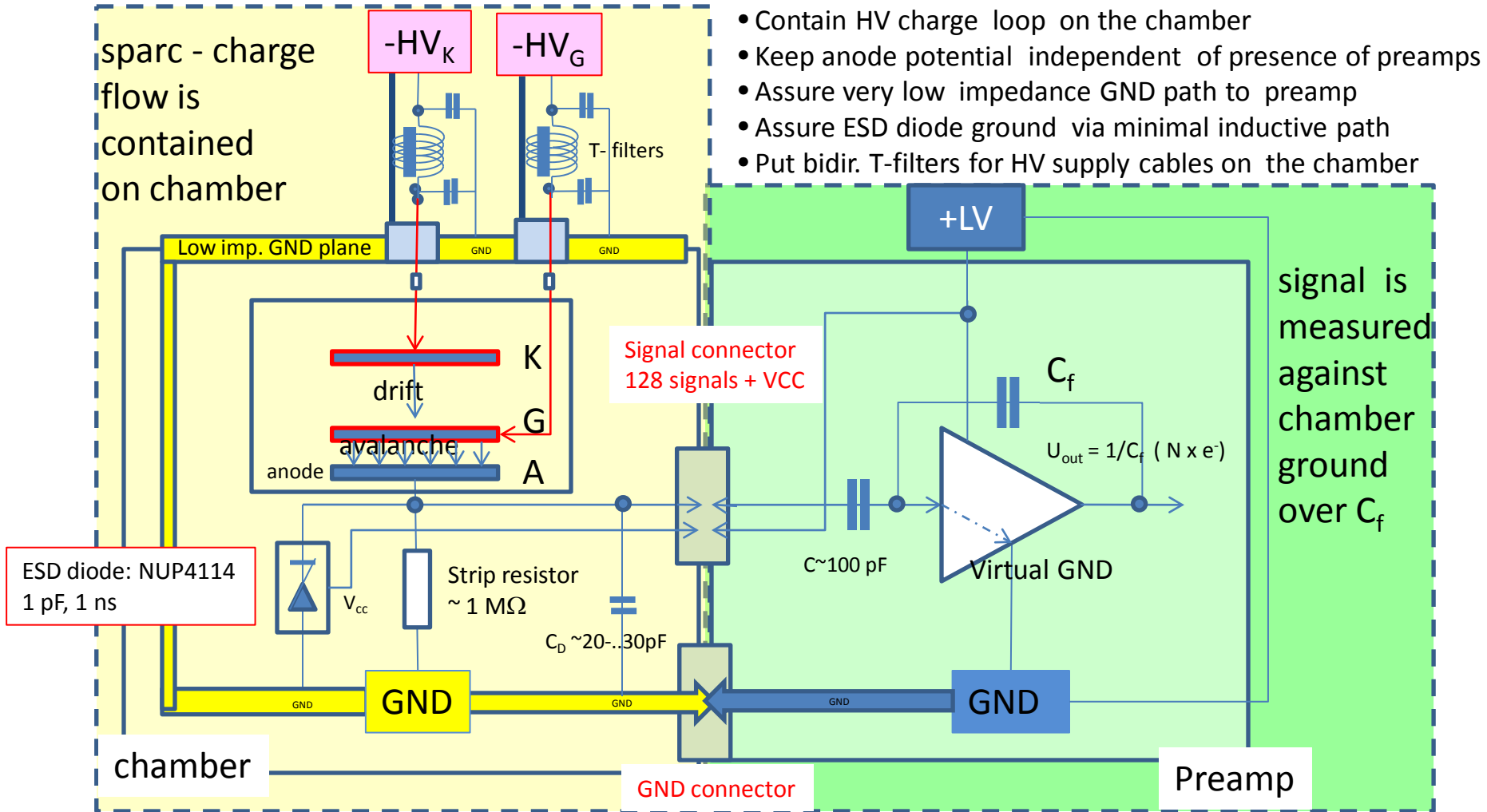Equivalent circuit for an optimized protection




MM chamber: Integrate coupling capacitor in double strip design

Double Strip: capacitive coupling
estimated 100 pF/m


Strip resistor
on top strip only

Non capacitor !

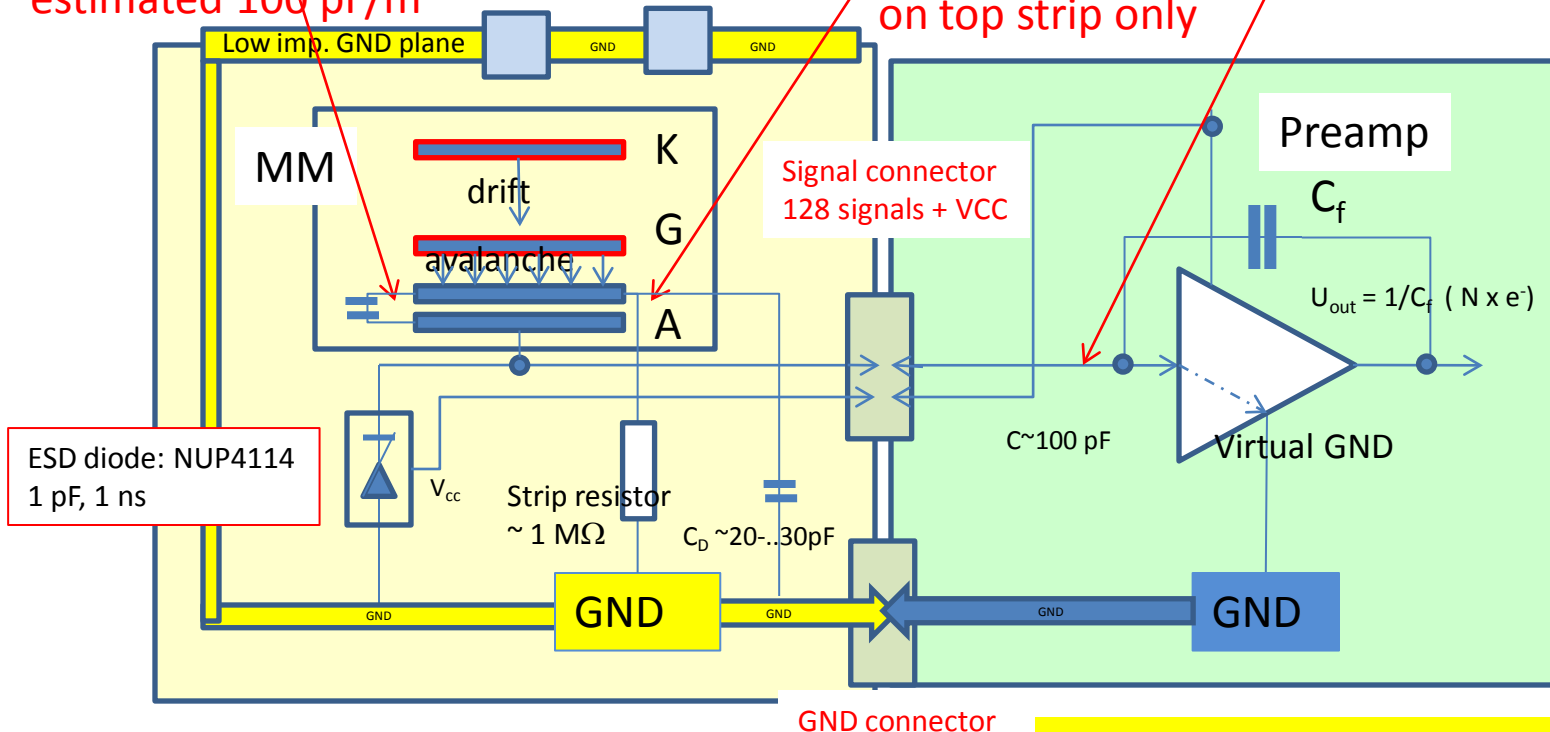


High sparc immunity expected:
Sparc-charge contained on chamber
Capacitively induced charge clipped by
ESD diode on chamber

Model for Dual Strip MM chamber

 


ESD diode arrays

NUP4114UPXV6

 


4 channels in 1.6 x 1.6 mm²

 

ELECTRICAL CHARACTERISTICS (T_J=25°C unless otherwise specified)



Parameter	Symbol	Conditions	Min	Typ	Max	Unit
Reverse Working Voltage	V _{RWM}	(Note 1)			5.0	V
Breakdown Voltage	V _{BR}	I _T = 1 mA, (Note 2)	6.0			V
Reverse Leakage Current	I _R	V _{RWM} = 5 V			1.0	μA
Junction Capacitance	C _J	V _R = 0 V, f = 1 MHz between I/O Pins and GND		0.8	1.0	pF
Junction Capacitance	C _J	V _R = 0 V, f = 1 MHz between I/O Pins		0.4	0.5	pF

ESD clipping performance

 

IEC 61000-4-2 Spec.


Level	Test Voltage (kV)	First Peak Current (A)	Current at 30 ns (A)	Current at 60 ns (A)
1	2	7.5	4	2
2	4	15	8	4
3	6	22.5	12	6
4	8	30	16	8

 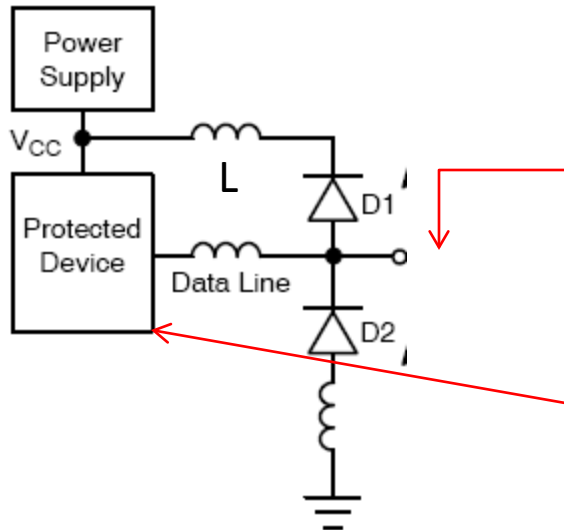


Negative clipped: $V_n = -V_f - L \times di_{esd}/dt$
 Positive clipped: $V_p = V_{cc} + V_f + L \times di_{esd}/dt$

Minimize the inductive part L !

MM chamber edge

 


ESD Implementation on chamber

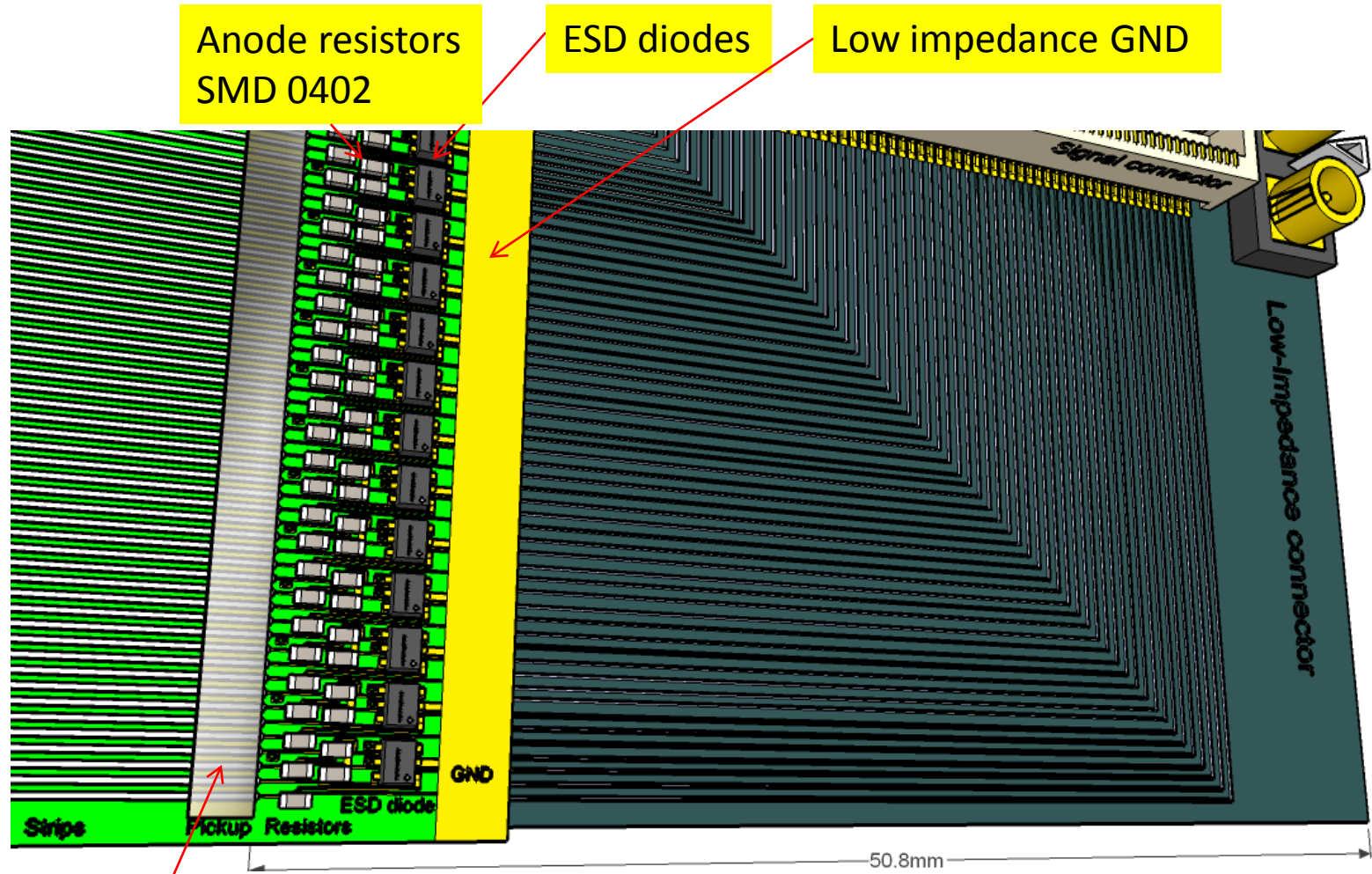


Pickup strip, capacitive pickup from groups of 64 channels

Connectors on chamber

 

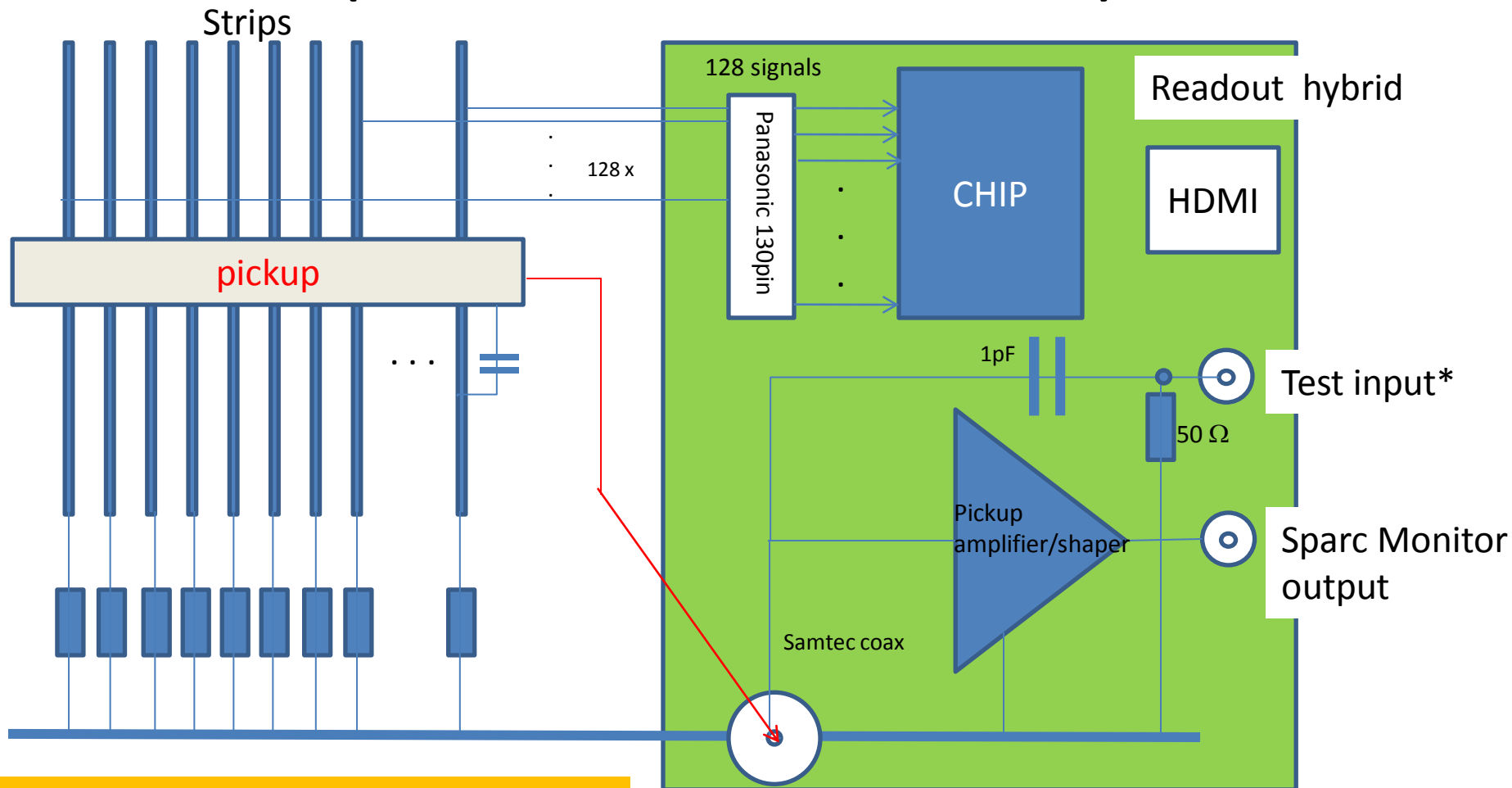Sparc monitor output and test input (under consideration)




Note: may also be used for generating a trigger
If chamber pulses are sufficiently strong

* Only required if chip has no test feature

Summary

- Vital and Desirable solutions for sparc protection needed
 - Component damage protection and readout immunity are vital
 - Sparc monitoring and test pulses are desirable
- Discrete protection diodes may work with AC coupling
 - but have too much capacitance and require too much space
- New ESD diodes are made for protection and combine a few advantages
 - very low capacitance $\sim 1\text{pF}$
 - very fast $\sim 1\text{ns}$
 - very small packages $\sim 1.5\text{ mm}^2$
 - better than IEC standard ESD protection
- Implementation requires low impedance ground and V_{cc} bias
- MM chamber layout exercise with ESD, R and dual strip looks OK
- Sparc monitoring and test signals look like an easy addition

Backup

 

HV connectors and filters

X-ray through MM edge and carrier

