



# **General considerations for the crowbar design of the HL-LHC circuits**

Hugues THIESEN (CERN)

On behalf of WP6B Warm Powering



8<sup>th</sup> HL-LHC Collaboration Meeting – Geneva - 15-18 October 2018


# Contents

- Power converter crowbar
- Crowbar for superconducting circuits
- Crowbar for HL-LHC circuits
- Conclusion

# *Power converter crowbar*

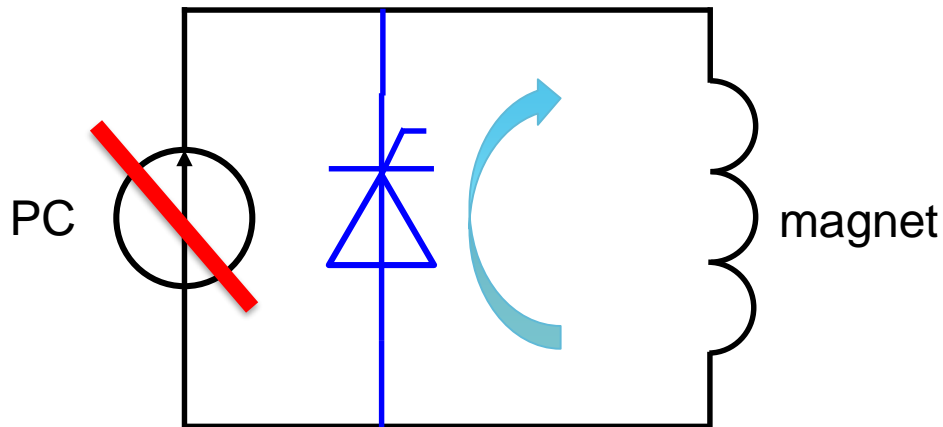
# Power converter crowbar

- The main function of the crowbar is to **protect the electrical circuit** (PC, DC cables and magnet) by giving a **path for current** in case of PC trip



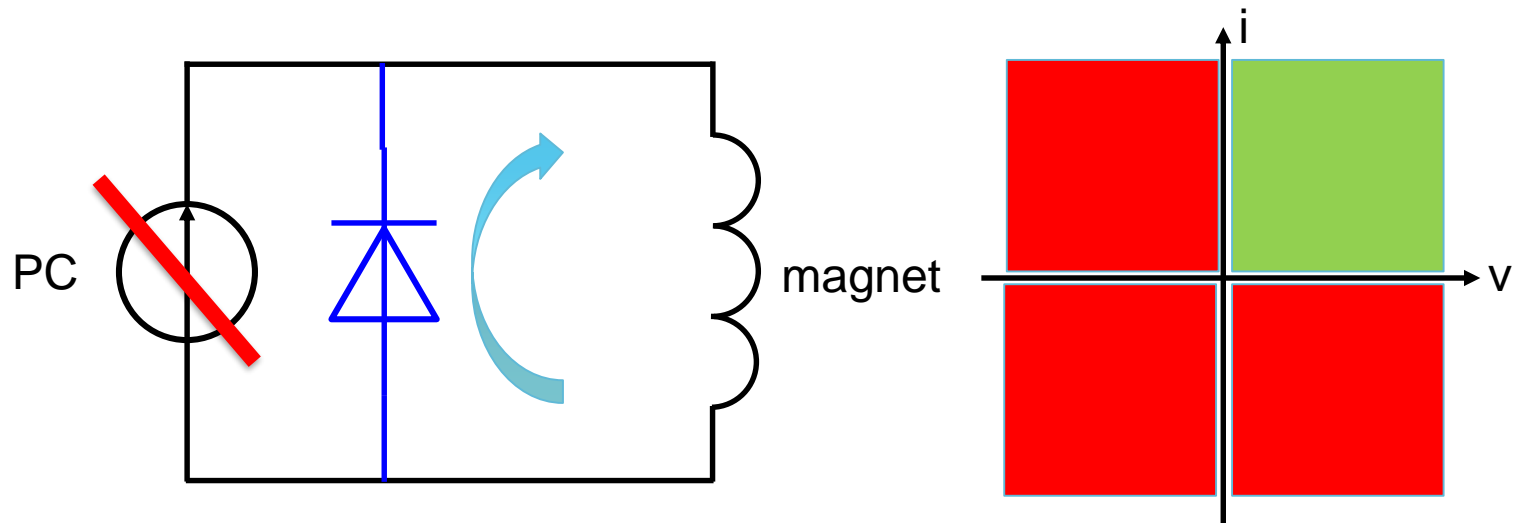
# Power converter crowbar

- Different types of crowbar
  - 1Q power converter => Diode



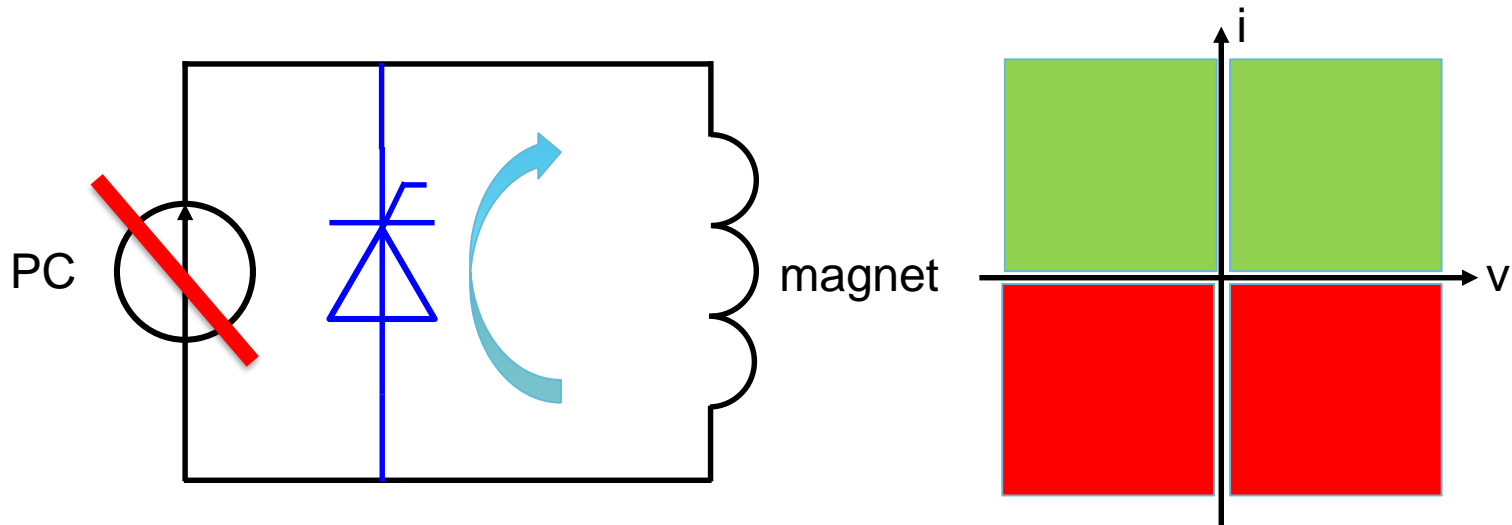
# Power converter crowbar

- Different types of crowbar
  - 1Q power converter => Diode
  - 2Q (bipolar in V) power converter => Thyristor


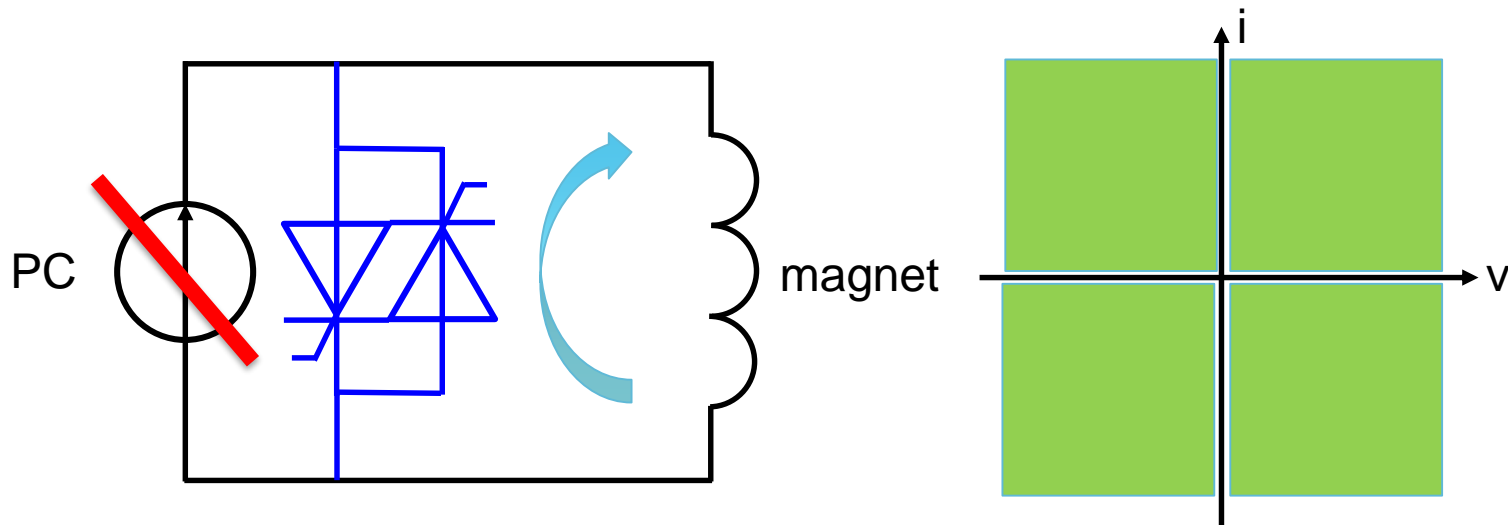
# Power converter crowbar

- Different types of crowbar
  - 1Q power converter => Diode
  - 2Q (bipolar in V) power converter => Thyristor
  - 4Q power converter => 2 thyristors back2back





# Power converter crowbar

- The main parameters for the crowbar design:
  - $V_{\text{peak}}$ ,  $I_{\text{peak}}$  and  $P_{\text{peak}}$  are defined by the power converter
  - Energy and current decay ( $\tau$ ) are defined by the magnet
  - Crowbar has to be natural air cooled (in case of water fault)
  - Auto-maintain (not need of external energy to maintain the crowbar ON)


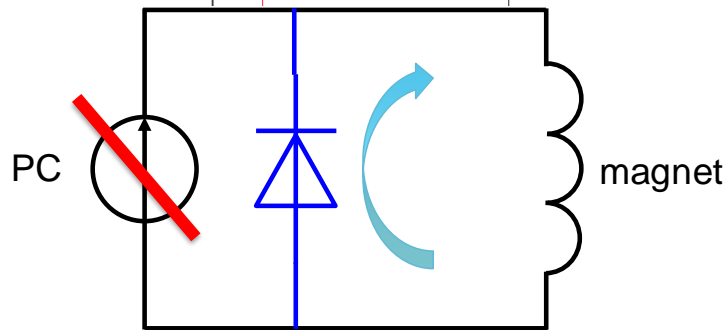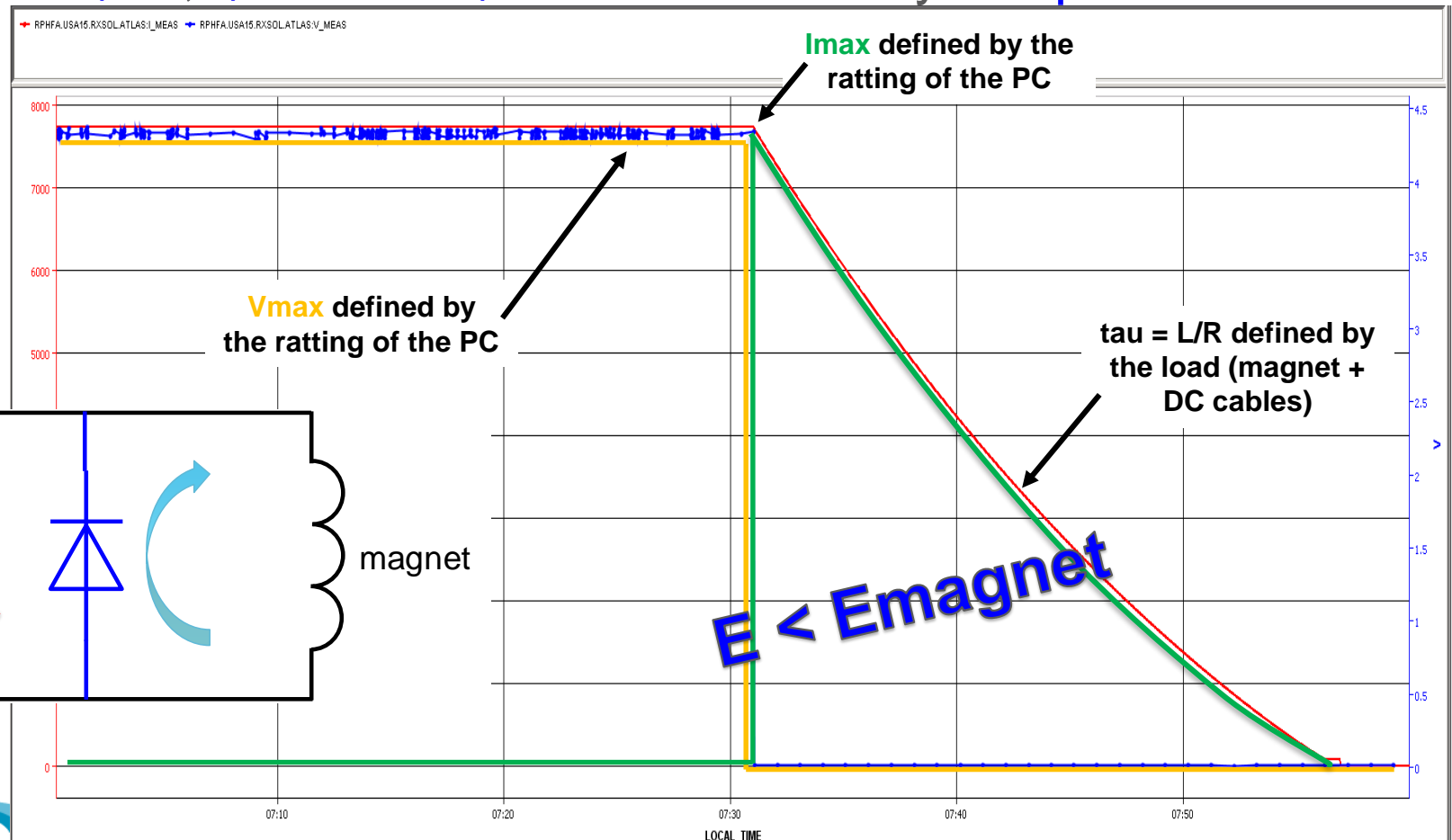
# Power converter crowbar

- The main parameters for the crowbar design:
  - $V_{peak}$ ,  $I_{peak}$  and  $P_{peak}$  are defined by the power



# ***Crowbar for superconducting circuits***


# Crowbar for superconducting circuits

- Superconducting circuits can have
  - High current ( $>1$  kA) and high inductance ( $>1$  H)
  - Low resistance ( $<10$  m $\Omega$ , only DC cables)
- main part of the magnet energy is dissipated in the crowbar

**Series resistor can be added to reduce the constraints ( $E$  and  $\tau$ ) for the crowbar (diodes or thyristors)**

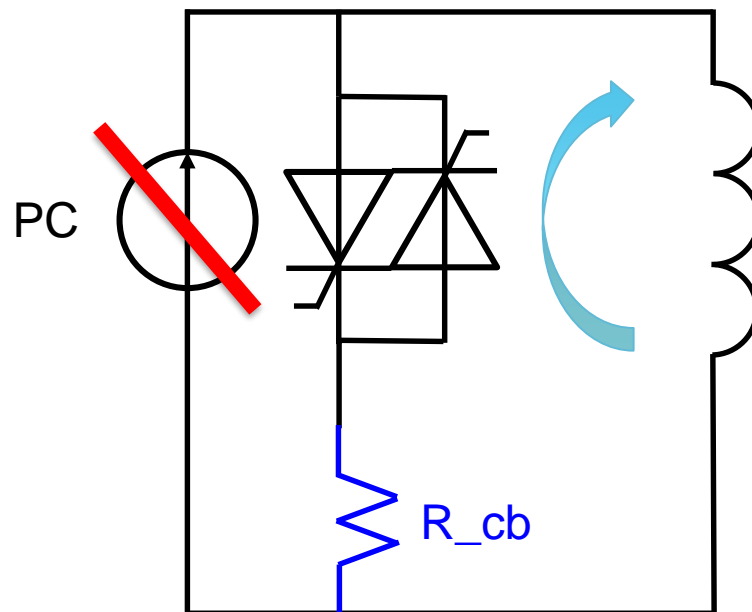
# Crowbar for superconducting circuits

- Crowbar resistor
  - The **series resistor** absorbs a part of **magnet energy** and reduces the **time constant** of the discharge (positive point for the magnet)



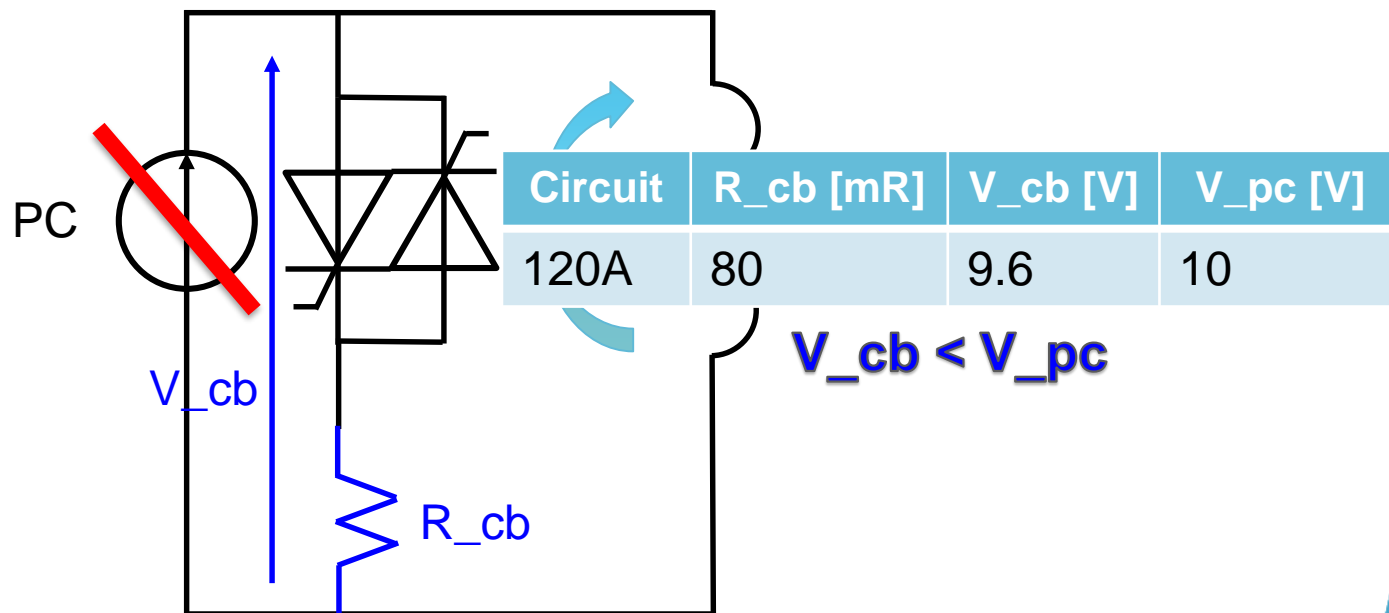
# Crowbar for superconducting circuits

- Crowbar resistor
  - Example: Crowbar resistor is used for the LHC 120A power converters.


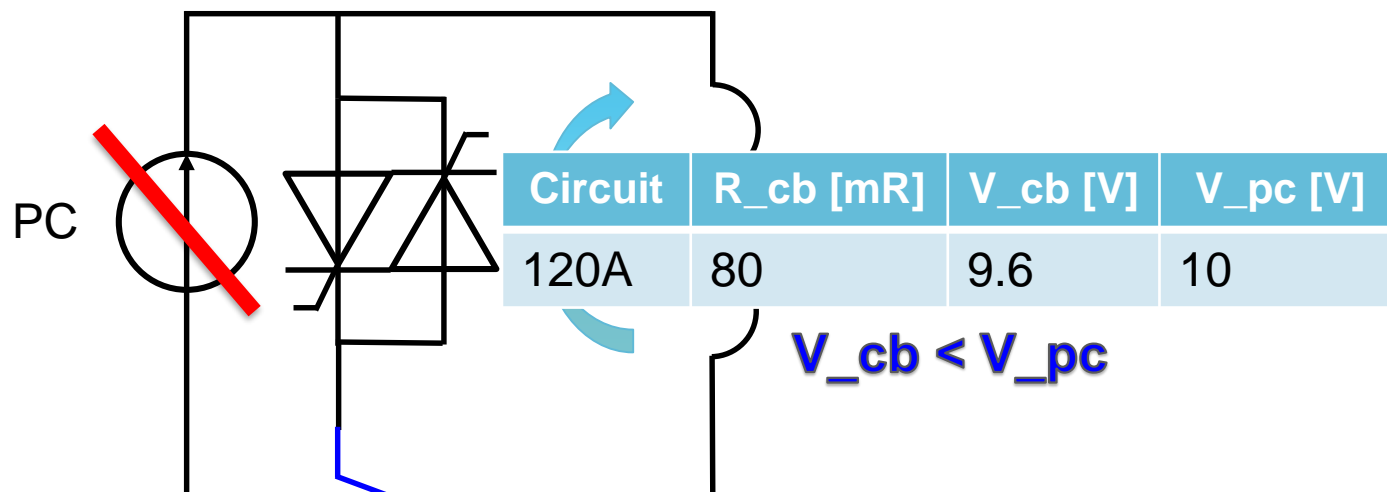
# Crowbar for superconducting circuits

- Crowbar resistor
  - Example: Crowbar resistor is used for the LHC 120A power converters.




**Can we go above nominal voltage of the power converter ?**

# Crowbar for superconducting circuits

- Crowbar resistor
  - The [600A/10V] PCs power superconducting circuits with huge inductance and huge time constant (eg. RU circuits with 4.8 H and 1000 s)
  - The crowbar resistor is **50 mΩ** and the voltage across the PC during the discharge is **30V**.
    - Constraints for the power converter (over voltage)
    - Constraints for the superconducting circuit ( $di/dt > \text{nominal } di/dt$ )
    - Constraints for the QDS (protection by global voltage)
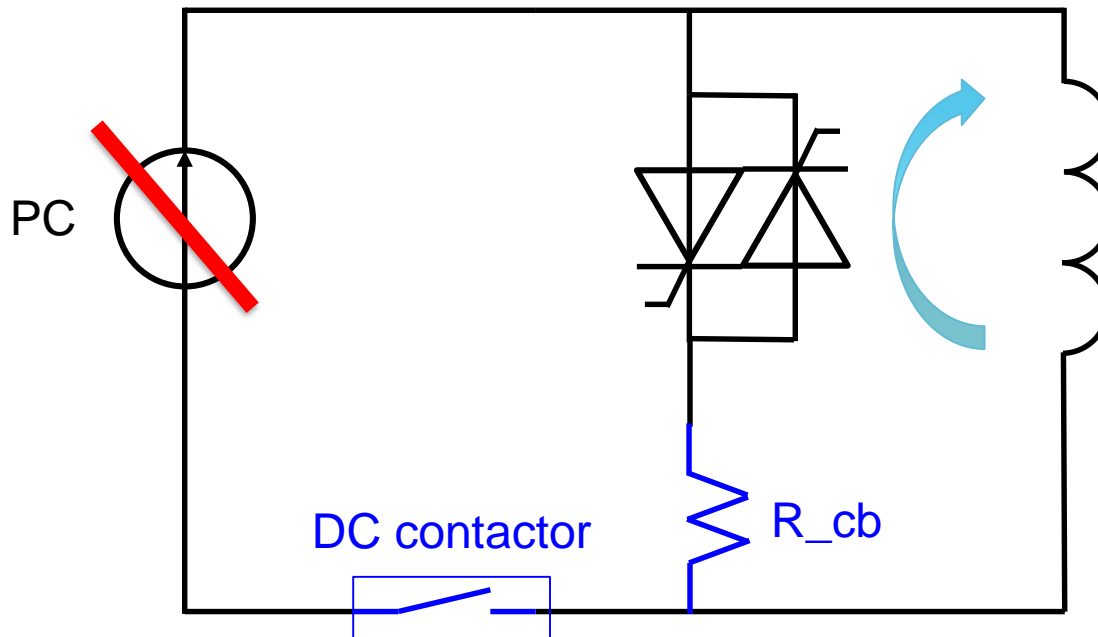
# Crowbar for superconducting circuits

- SC busbar can be protected by the Crowbar ?
  - Risk to bypass the crowbar in case of PC short circuit
  - DC contactor added in series with the PC to increase the safety level of the discharge system






# ***Crowbar for HL-LHC circuits***


# Crowbar for HL-LHC circuits

## ■ HL-LHC circuits

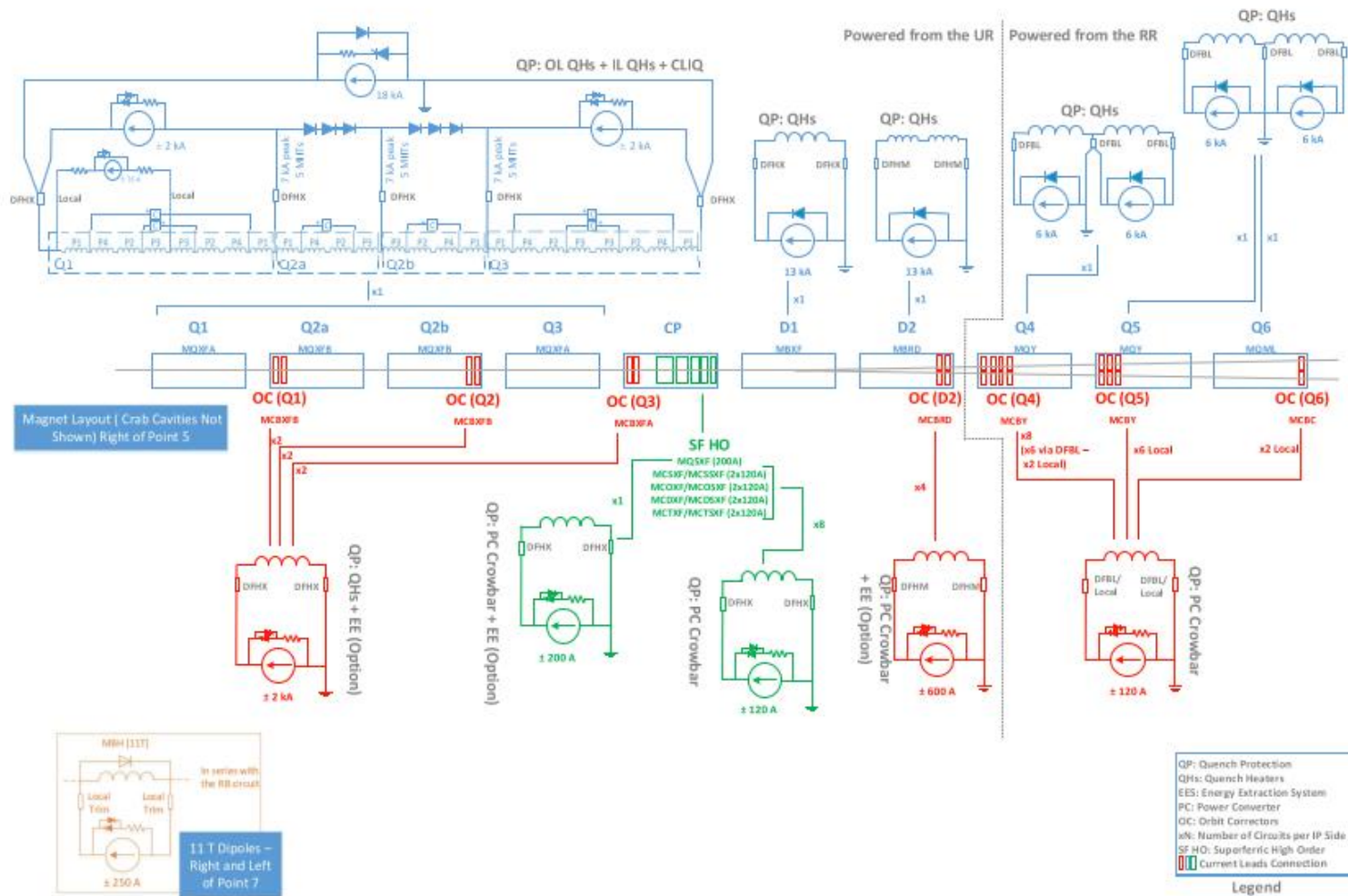


# Crowbar for HL-LHC circuits

## HL-LHC circuits

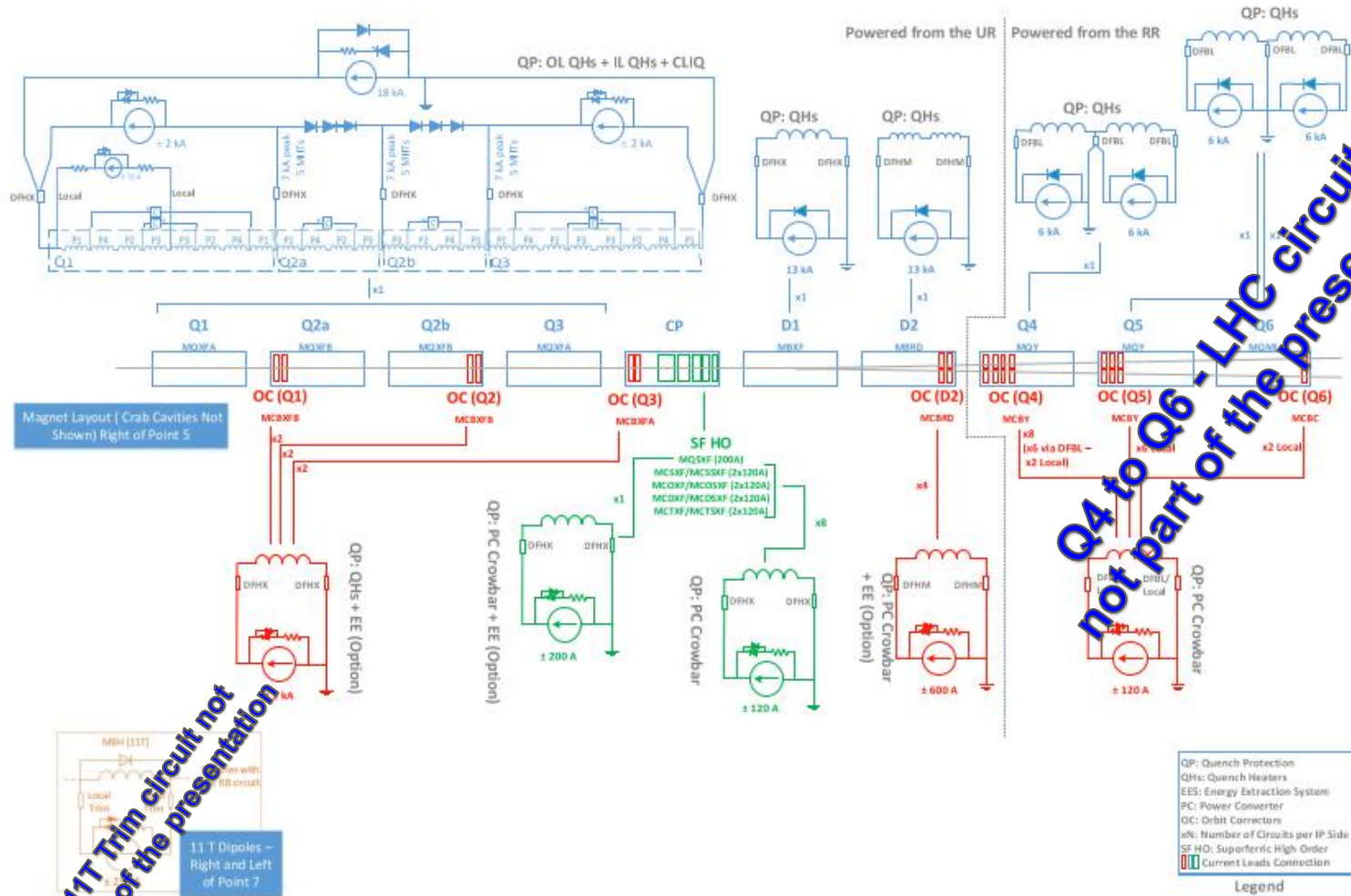

# Crowbar for HL-LHC circuits


## ■ HL-LHC circuits

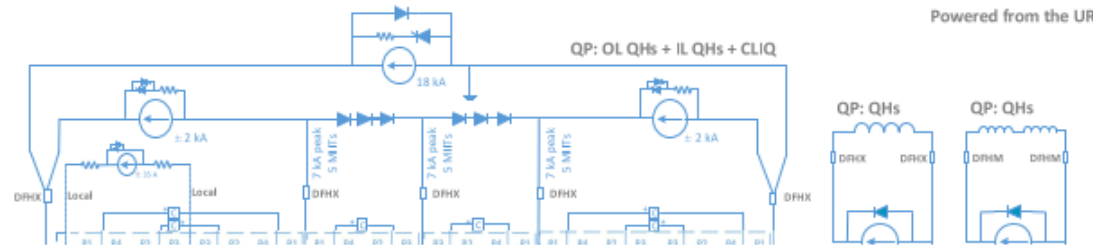

Circuit	I <sub>pc</sub> [A]	V <sub>pc</sub> [V]	Quadrant	Magnet	Crowbar	R <sub>cb</sub> [mΩ]	V <sub>cb</sub> [V]	Based on
120A	120	10	4Q	CP	Thy_B2B	80	9.6	LHC
200A	200	10	4Q	CP	Thy_B2B	50	10	LHC R2E
600A	600	10	4Q	OC(D2)	Thy_B2B	50	30	LHC R2E
2kA	2'000	10	4Q	OC(Q1toQ3)	Thy_B2B	7	14	New
13kA	13'000	8	1Q	D1/D2	Diode	-	0	LHC R2E
IT Main	18'000	10	2Q	Q1toQ3	Thy	0.5	9	New
IT Trim	2'000	10	4Q	Q1/Q3	Thy_B2B	7	14	New
IT kmod	35	8	4Q	Q1a	Thy_B2B	??	??	LHC
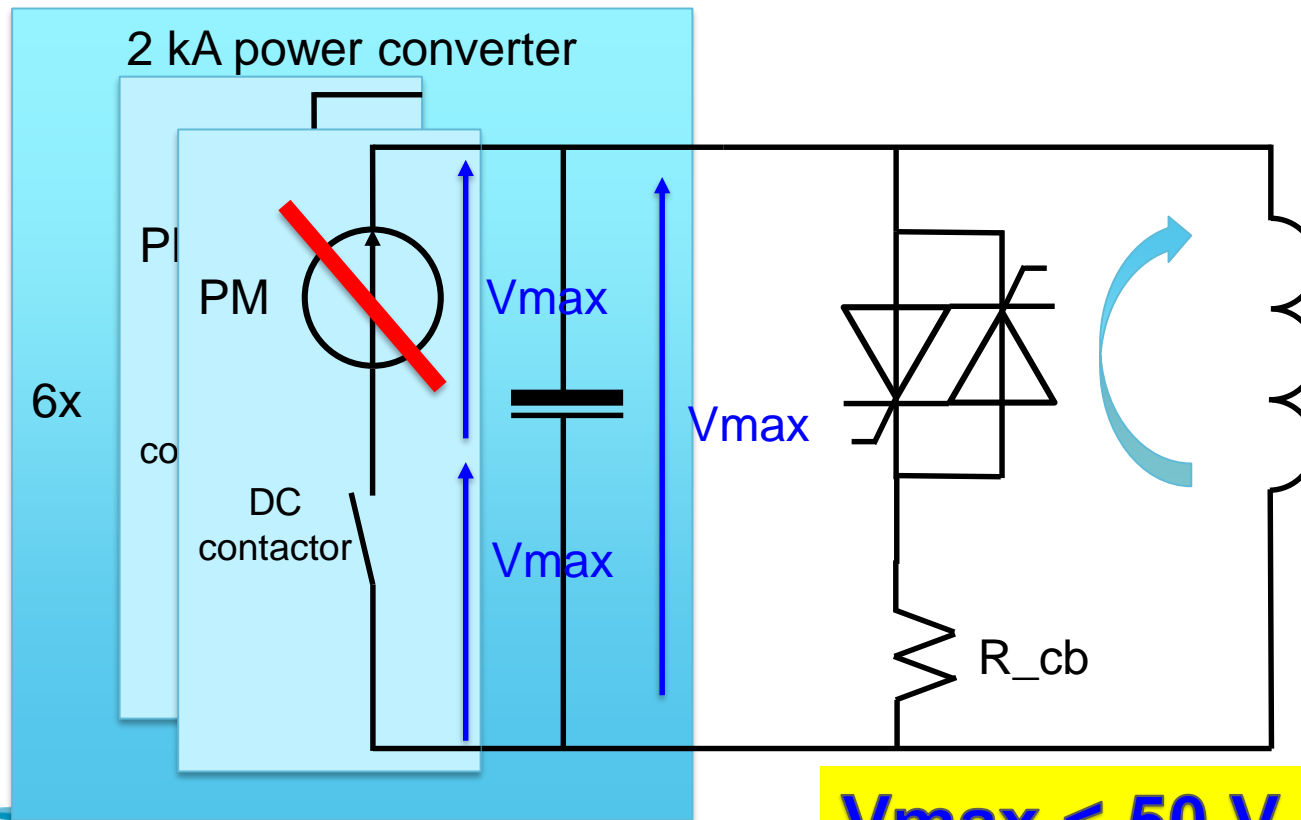
# Crowbar for HL-LHC circuits

- 2kA power converter
  - Redundant power converter with 6 sub-PC in parallel



$$V_{max} < 50 \text{ V}$$

# Crowbar for HL-LHC circuits


- 2kA power converter
  - 2 cases to take in account to design the 2 kA crowbar resistor
    - Power converters for OC(Q1toQ3)
    - Power converters for IT TRIM

PC	Over Current [A]	R_cb [mΩ]
OC(Q1toQ3)	2'000	< 25
TRIM(Q1&Q3)	7'000	< 7

# Crowbar for HL-LHC circuits


- 2kA power converter
  - 2 cases to take in account to design the 2 kA crowbar resistor
    - Power converters for OC(Q1toQ3)
    - Power converters for IT TRIM

PC	Over Current [A]	R_cb [mΩ]
OC(Q1toQ3)	2'000	< 25
TRIM(Q1&Q3)	7'000	< 7

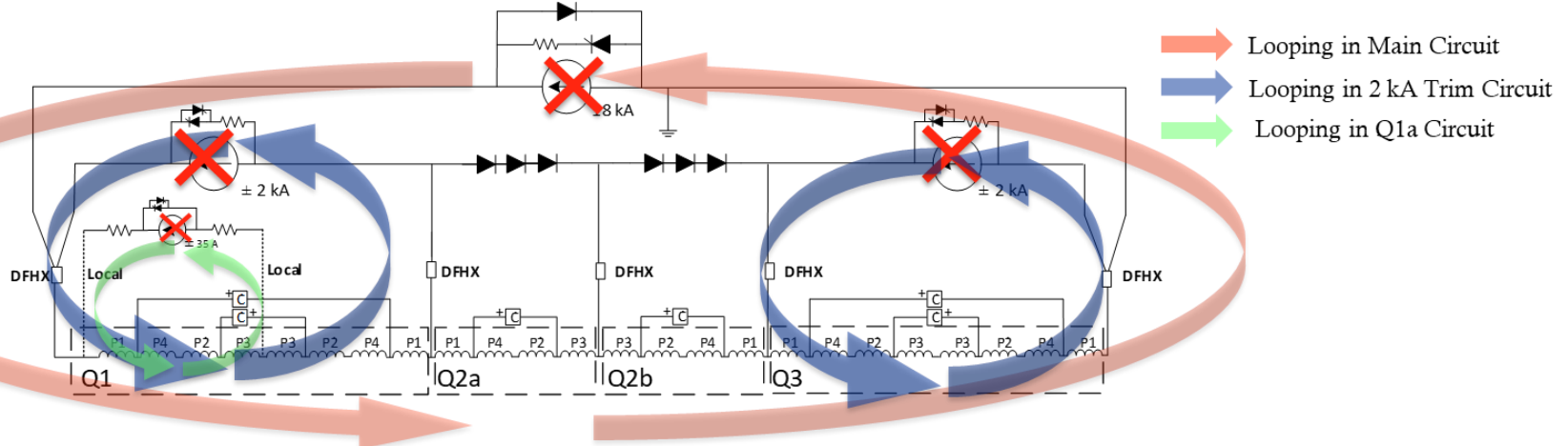
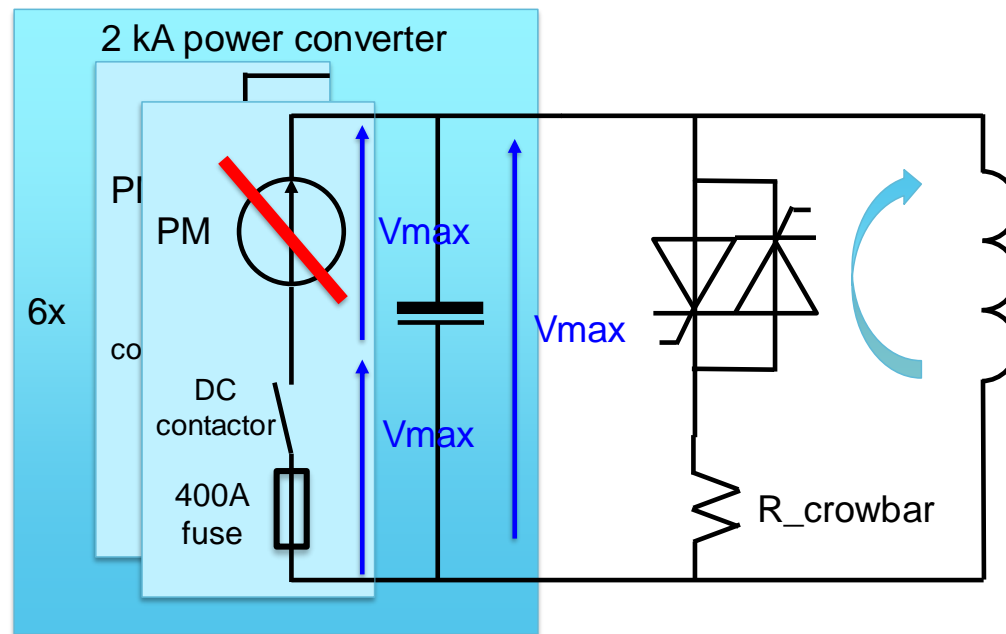
# Crowbar for HL-LHC circuits


- 2kA power converter
  - If the crowbar is critical for the protection of the SC busbar then 400A fuses can be added in series with the DC contactor of each sub converter





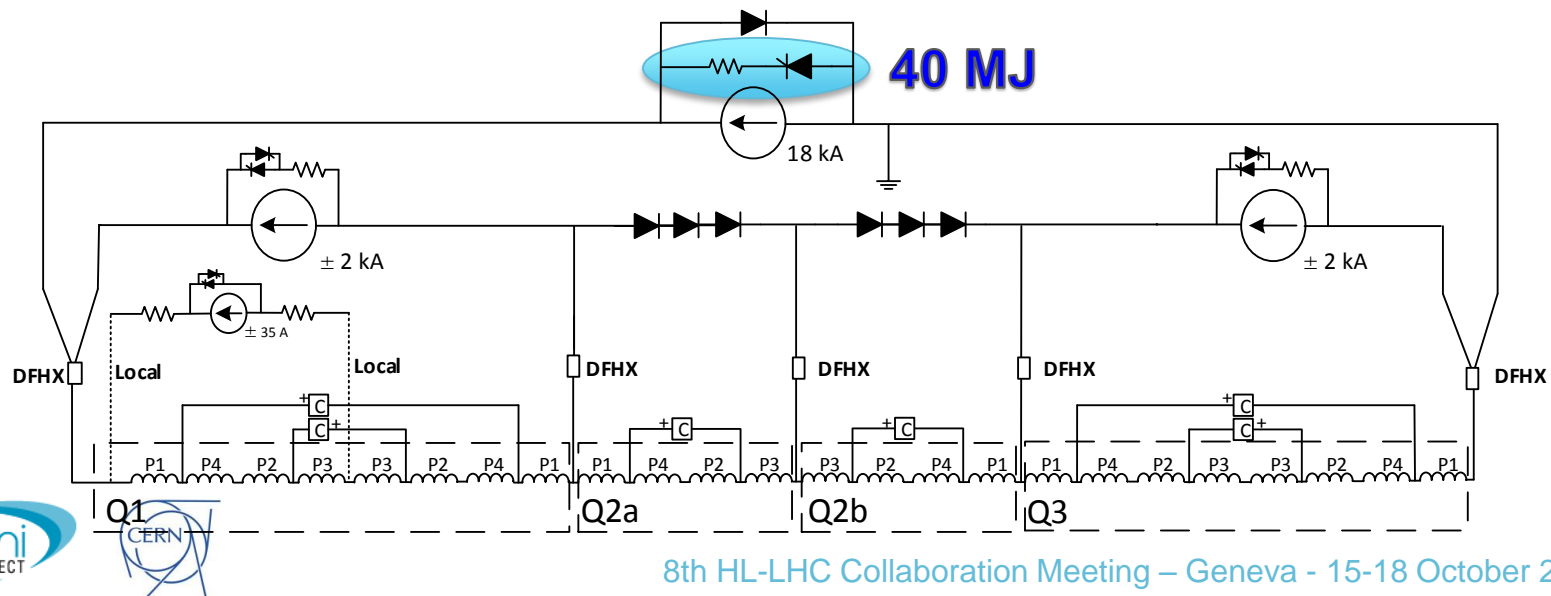
# Crowbar for HL-LHC circuits

- 18kA power converter
  - Huge energy stored in the circuit (Q1, Q2a, Q2b and Q3)
  - No DC cables
    - Time constant  $> 500$  s
    - Full magnet energy dissipated in the crowbar


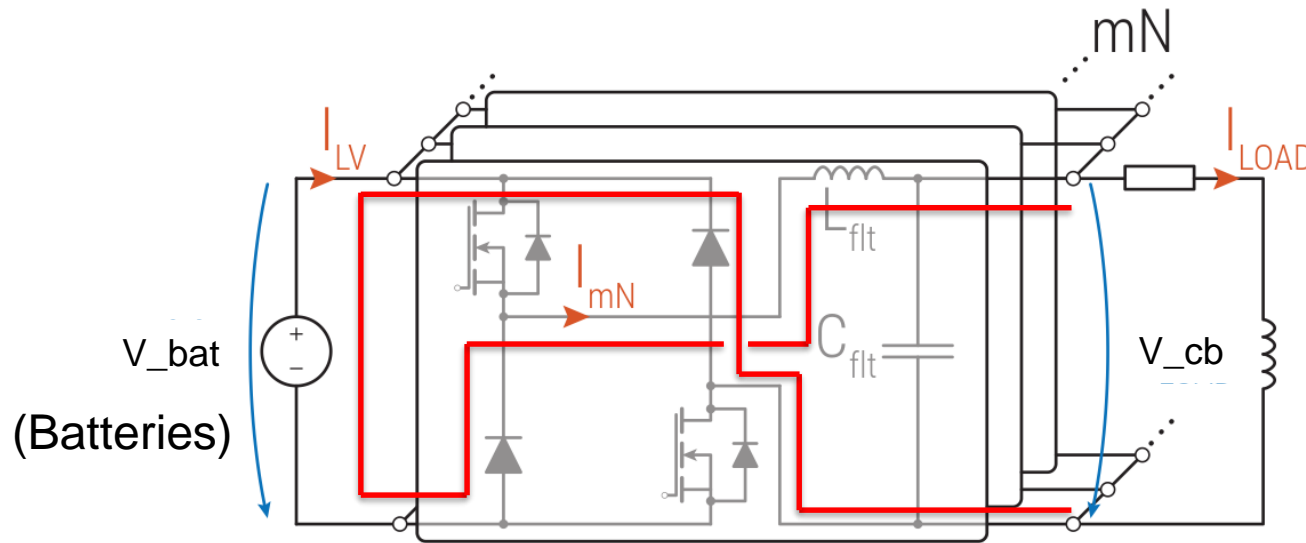
# Crowbar for HL-LHC circuits


- 18kA power converter
  - N sub-converters with M sub-module in parallel
  - Diodes of the output stage in parallel with the crowbar



$$V_{cb} < V_{bat} (24 \text{ V})$$
$$\tau > 250 \text{ s}$$
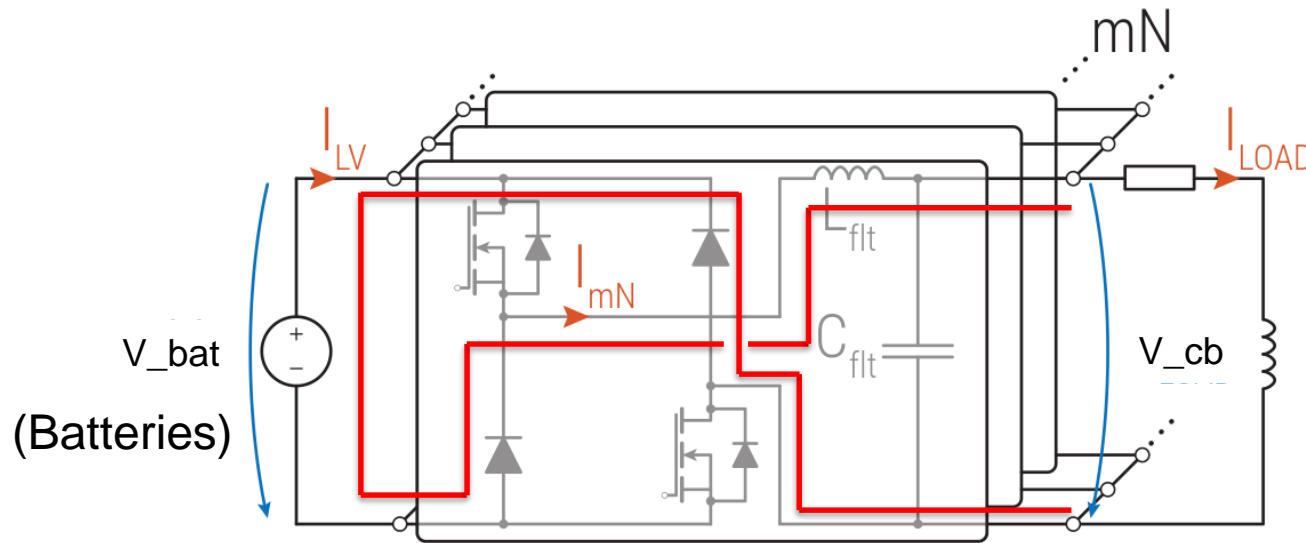
# Crowbar for HL-LHC circuits

- 18kA power converter
  - If  $V_{cb} > 24$  V is requested then external 18 kA EE system is mandatory



# *Conclusion*

# Conclusion

- The function of the crowbar is to protect electrical circuit (PC, DC cables and magnet) by giving a path for current when the power converter is OFF (normal or fault off)
- Resistor in series with the crowbar can be added to reduce the time constant of the discharge but in this case the  $V_{cb}$  shall be close to the  $V_{pc}$
- For high discharge voltage, EE system must be used



***Thank you for your attention...***

