

Design of matrix 1 for RD50-ENGRUN1 - Analog sampling


O. Alonso, S. Moreno, N. Franch, J. Canals, V. Moro and A. Diéguez

SIC, Electronics and Biomedical Eng. Department, University of Barcelona, Spain

oononso@el.ub.edu



ENGRUN1: Design

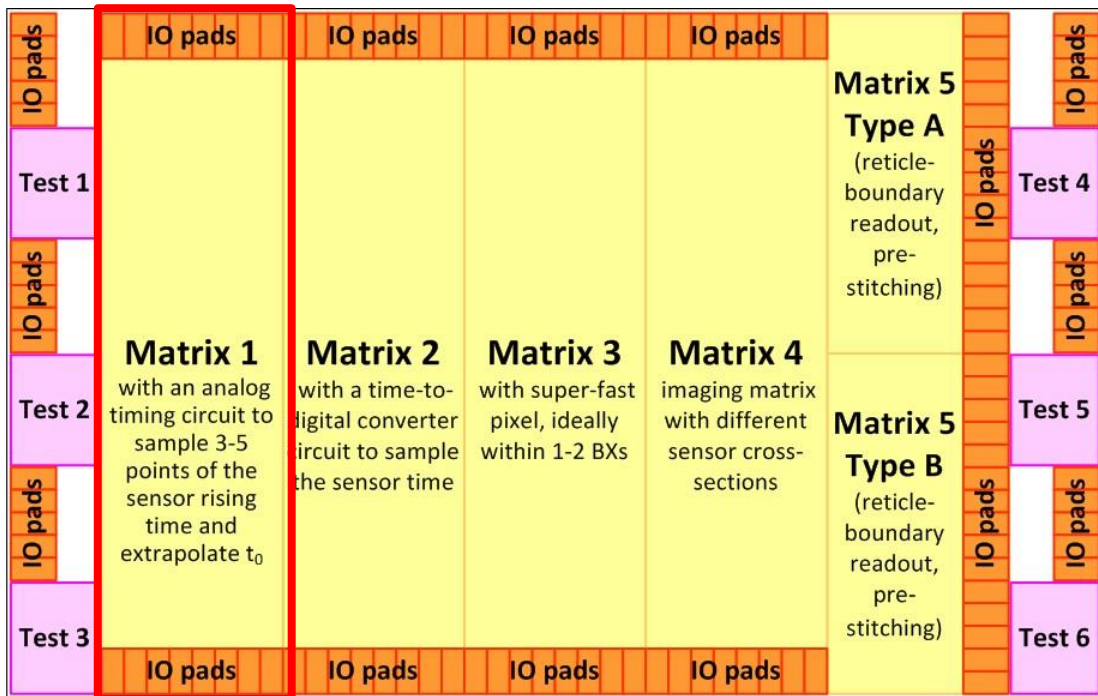

Test structure 1

Simple CMOS capacitors to study oxide thickness

Test structure 2

10 x 10 matrix of very small pixels with passive readout

Test structure 3

10 x 10 matrix of very small pixels with 3T-like readout

Test structure 4

Small matrix of pixels for TCT, e-TCT and TPA-TCT measurements

Test structure 5

Single pixels for sensor capacitance measurements

Test structure 6

...

CERN/RD50 collaboration:

- International project to develop radiation hard semiconductor devices for very high luminosity colliders

Target of this submission:

- Improve the timing resolution of HV-CMOS sensors with different solutions implemented at the readout circuit level
- Study new sensor cross-sections
- Study pre-stitching options (increase the device area beyond the reticle size limitation)

Technology:

- 150 nm HV-CMOS from LFoundry

Design effort:

- IFAE (R. Casanova)
- Uni. Barcelona (O. Alonso)
- Uni. Liverpool (S. Powell, E. Vilella and C. Zhang)
- FBK (N. Massari and M. Perenzoni)




ENGRUN1: Design



The pixel in Matrix 1 includes:



- **Sensor** → $50\ \mu\text{m} \times 50\ \mu\text{m}$ ($\sim 200\ \text{fF}$ parasitic capacitance)
- **Analog readout electronics** → CSA, shaper, filter and comparator.
- **Digital readout electronics** → Electronics that sense the leading edge of the comparator and store the corresponding time-stamp in an 8-bit memory. The electronics also store the pixel address in another 8-bit memory (this info is not needed for the analysis presented in these slides).
- **Sampling electronics** → Chain of delay elements and sample & holds to store 5 analog voltages. The sample & holds sample the output voltage of the shaper. The delay elements put the sample & hold in hold mode when there is an event in the pixel. We can tune the delay with an external voltage (i.e., $1.04\ \text{ns}$ @ $1\ \text{V}$, $1.94\ \text{ns}$ @ $1.1\ \text{V}$).

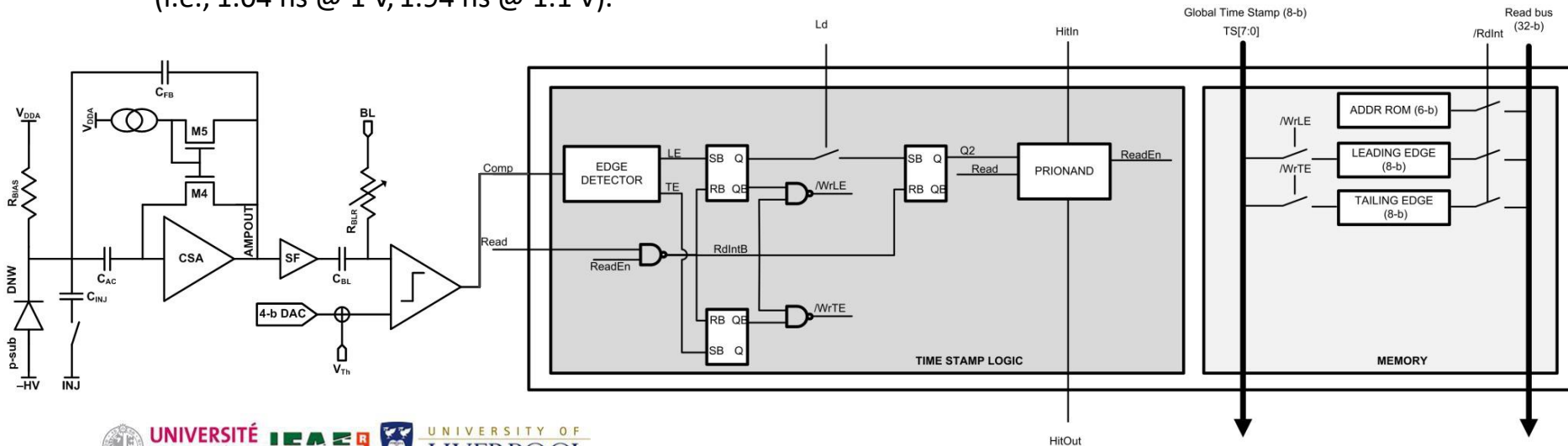

ENGRUN1: Design




Simplified schematic and functionality

 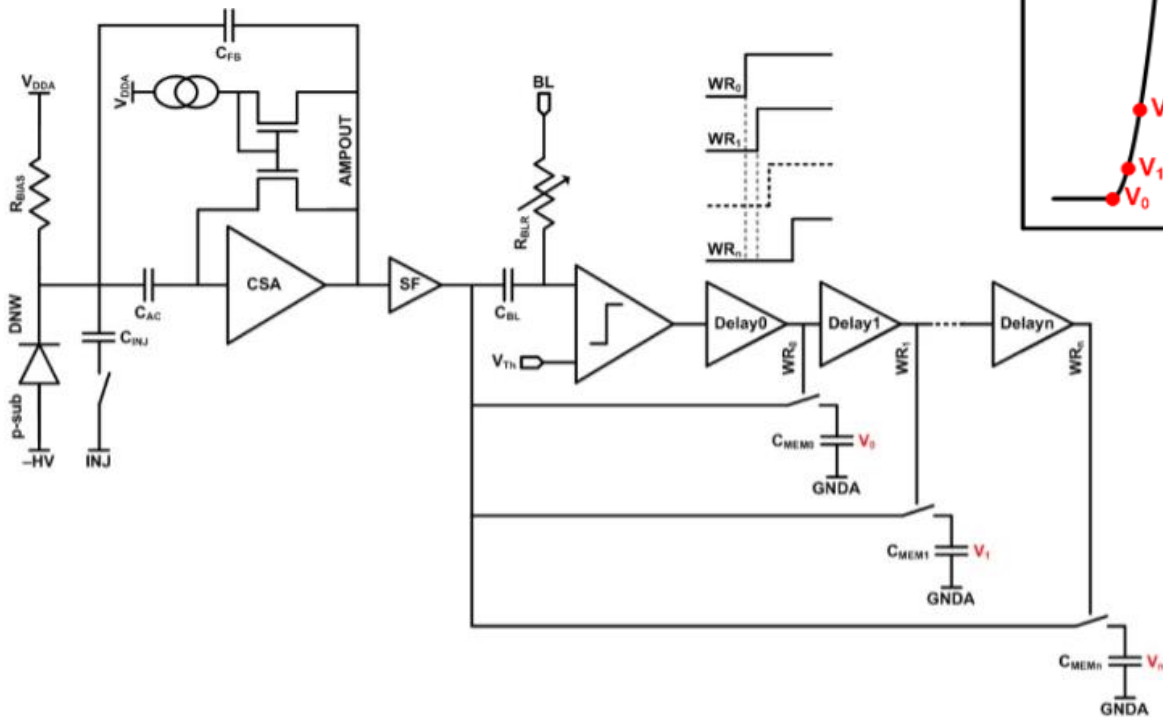


The main idea is to store up to 5 analog voltages.

ENGRUN1: Design

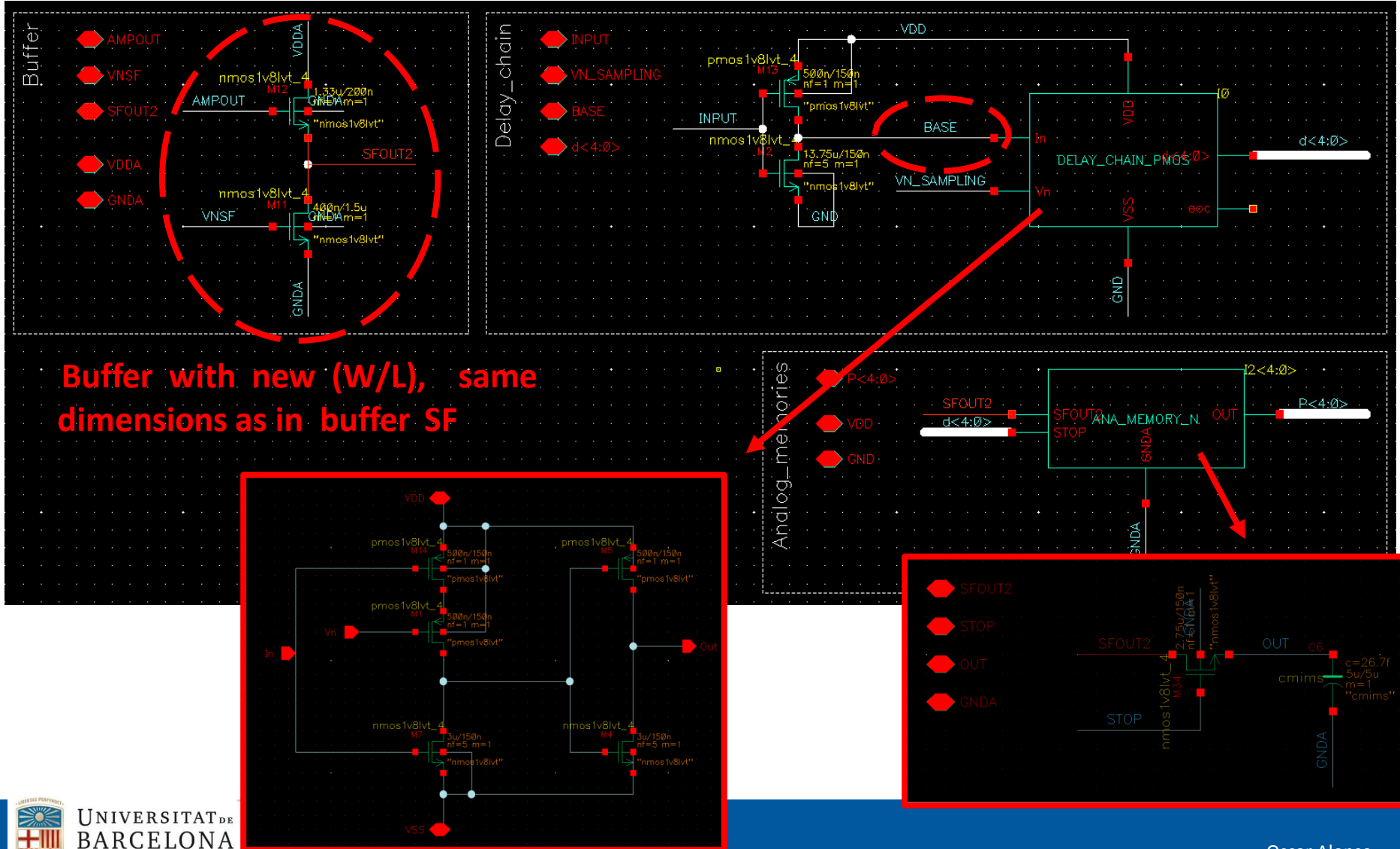


Buffer with new (W/L), same dimensions as in buffer SF

ENGRUN1: Design

 


ENGRUN1: Design

 

Baseline + th




ENGRUN1: Design

 


Input charge 2k - Power consumption = 25.72 μ W

ENGRUN1: Design

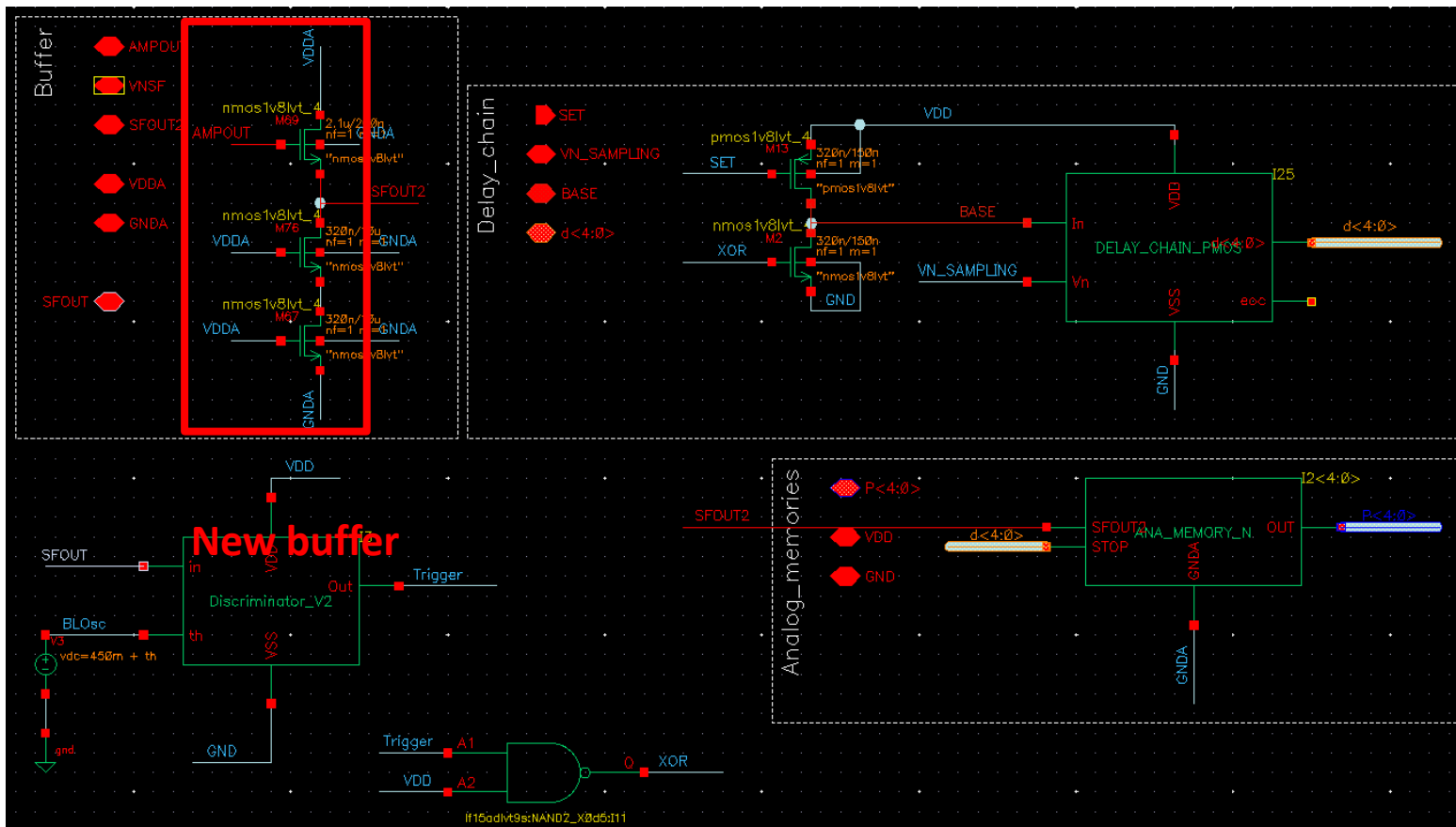

ENGRUN1: Design

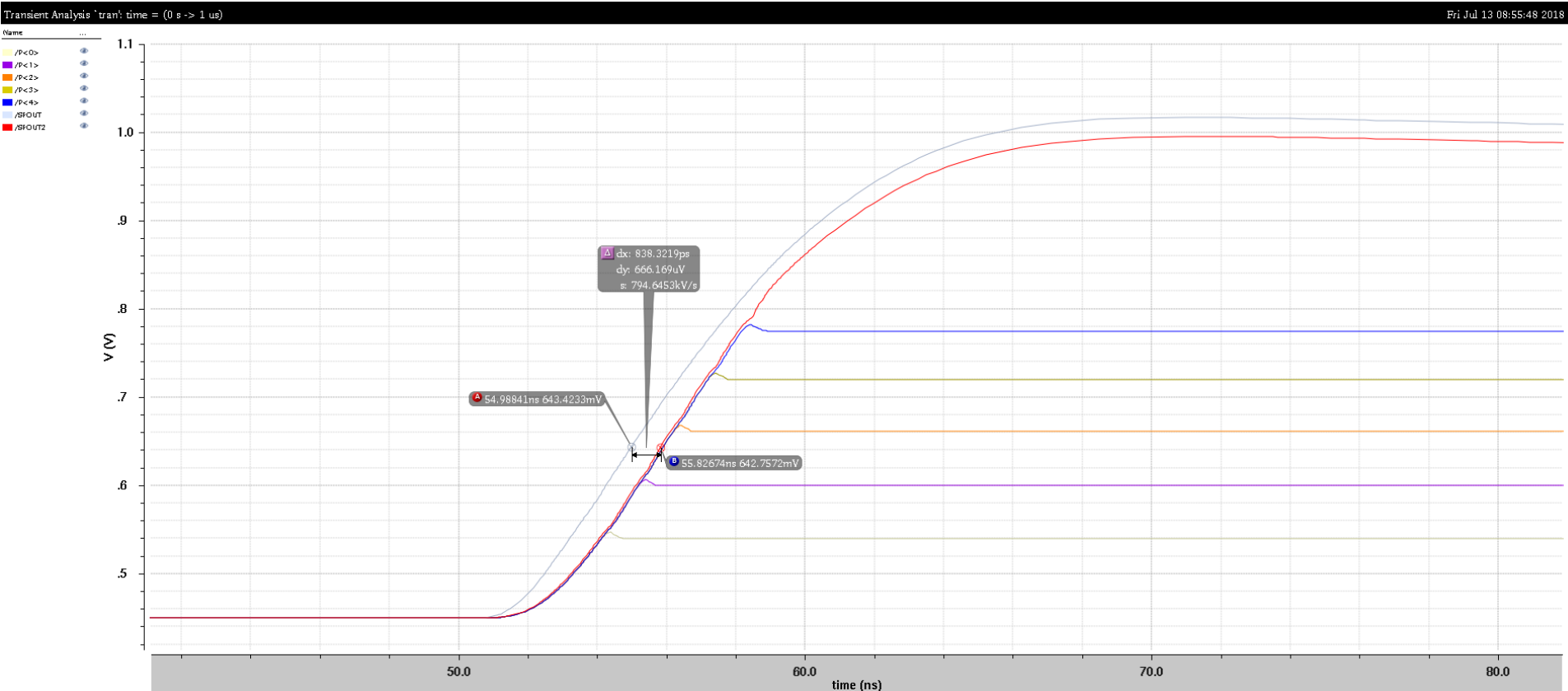

Input charge 9k - Power consumption ~ 28 μ W




Conclusion



- The quality of the method depends on:
 - Value of VN → How do we choose the appropriate value of VN?
 - Comparator time response
 - It also depends on the amount of input electrons
 - Better time resolution at larger amounts of input electrons
 - It also depends on the proximity of the real event time to the Cadence/chip time-stamp
 - An event happening at $1.022 \mu\text{s}$ gives a better time resolution than an event happening at $2.385 \mu\text{s}$, as $1.022 \mu\text{s}$ is closer to the time-stamp ($1 \mu\text{s} = 20 * 50 \text{ ns}$) than $2.385 \mu\text{s}$ ($2.35 \mu\text{s} = 47 * 50 \text{ ns}$).
 - Time-stamp period
- Power consumption of $28 \mu\text{W}$ per pixel with the possibility to reduce it to $22 \mu\text{W}$
- Other solutions under study

Conclusion

 

- Instead of defining time axis we define the voltage axis
=> We are designing a TDC