 


Matching issues on the bias voltages



- Serious mismatch of bias voltages has been observed from the measurement of RD50-MPW1. Although, there is suspicious issue with the measurement set-up, it is still worth to look into this matter.
- From the schematic design level:
 - All bias voltages are based on a reference voltage VP generated on chip. Variations of the transistor M1 and the resistors R2, R3 contribute to the mismatch of all bias voltages
 - Optimise the size of M1 and replace the rppolyh resistors (high resistivity, high variation) with rppolyl resistors (low resistivity, low variation) for better matching.
 - distribute the current I_VP instead of the voltage VP to generate different bias voltages.
- From the layout design level:
 - re-arrange transistors for better matching.



Comparison based on Monte Carlo simulations



| | Before modification | | | | After modification | | | |
|-----------------|---------------------|---------------|--------------|-------------------------|--------------------|---------------|---------------|------------------------|
| | Min | Max | Mean | Std Dev | Min | Max | Mean | Std Dev |
| VP | 927 mV | 1.06 V | 1 V | 24.7 mV | 478 mV | 620 mV | 541 mV | 22.5 mV |
| I_VP | 26.9 μ A | 48.8 μ A | 36 μ A | 4.14 μ A (11.5%) | 29.2 μ A | 44.4 μ A | 35.8 μ A | 2.76 μ A (7.7%) |
| VPCOMP | 1.14 V | 1.31 V | 1.23 V | 28.2 mV (2.29%) | 1.15 V | 1.31 V | 1.23 V | 27.7 mV (2.25%) |
| I_VPCOMP | 7.27 μ A | 12.99 μ A | 9.95 μ A | 1.16 μ A (11.7%) | 7.7 μ A | 13.13 μ A | 10.33 μ A | 0.95 μ A (9.2%) |
| VNFB | 503 mV | 671 mV | 583 mV | 27.3 mV (4.7%) | 519 mV | 653 mV | 586 mV | 22.8 mV (3.9%) |
| I_VNFB | 277 nA | 602 nA | 396 nA | 57.2 nA (14.4%) | 294 nA | 550 nA | 411 nA | 48.5 nA (11.8%) |

- Modifications are on schematic design level by now.
- Standard deviations of generated currents are 20% - 30% smaller after modification. Smaller currents have higher variation (I_VNFB), larger currents have lower variation (I_VPCOMP).

- use a Low Dropout (LDO) regulator to minimise the variation on the transistor?
- Options?