



RaToPUS: A Generic Radiation Tolerant Power Supply for Distributed I/O Tier Project




Lalit Patnaik


lalit.patnaik@cern.ch

Objective

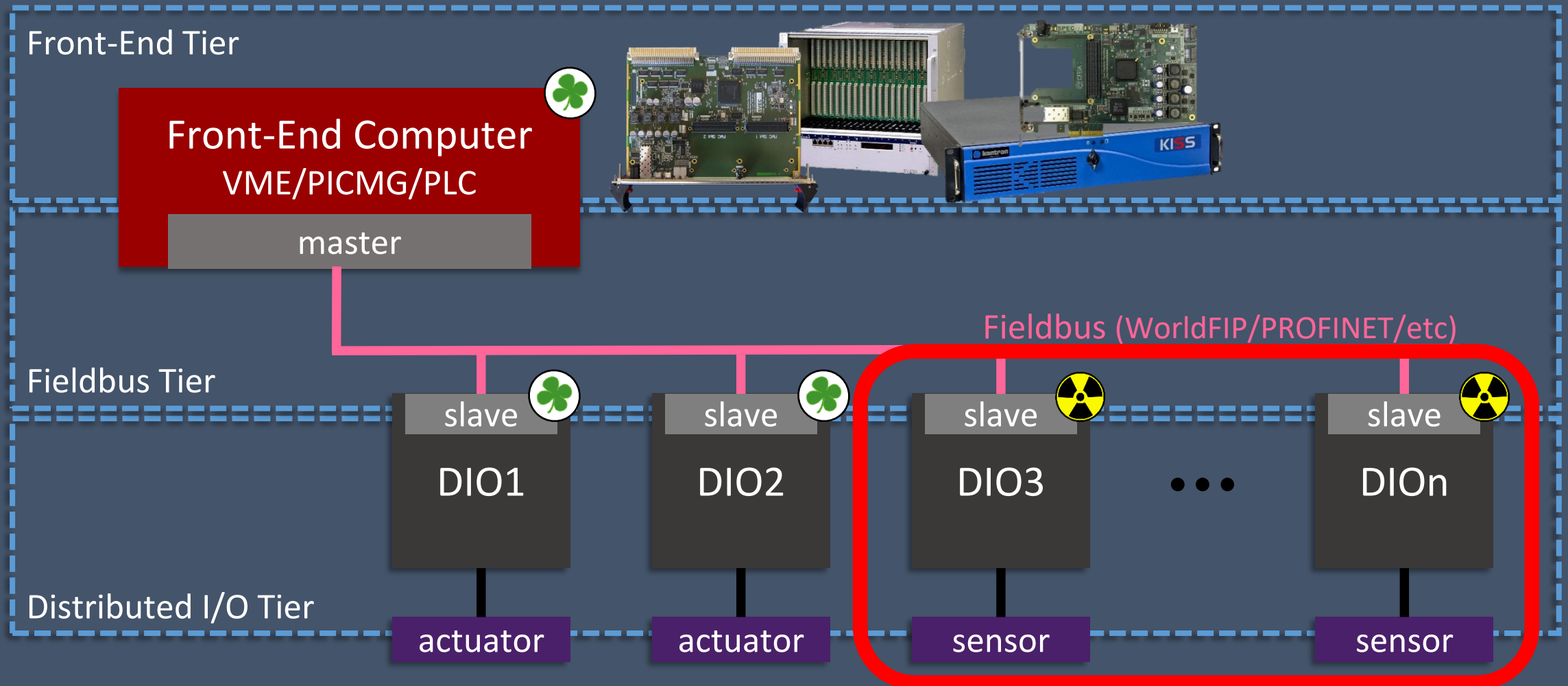Design and test a generic PSU for Distributed I/O Tier (DIOT) crates to be used under radiation environment by various CERN user groups.



DIOT crate mockup

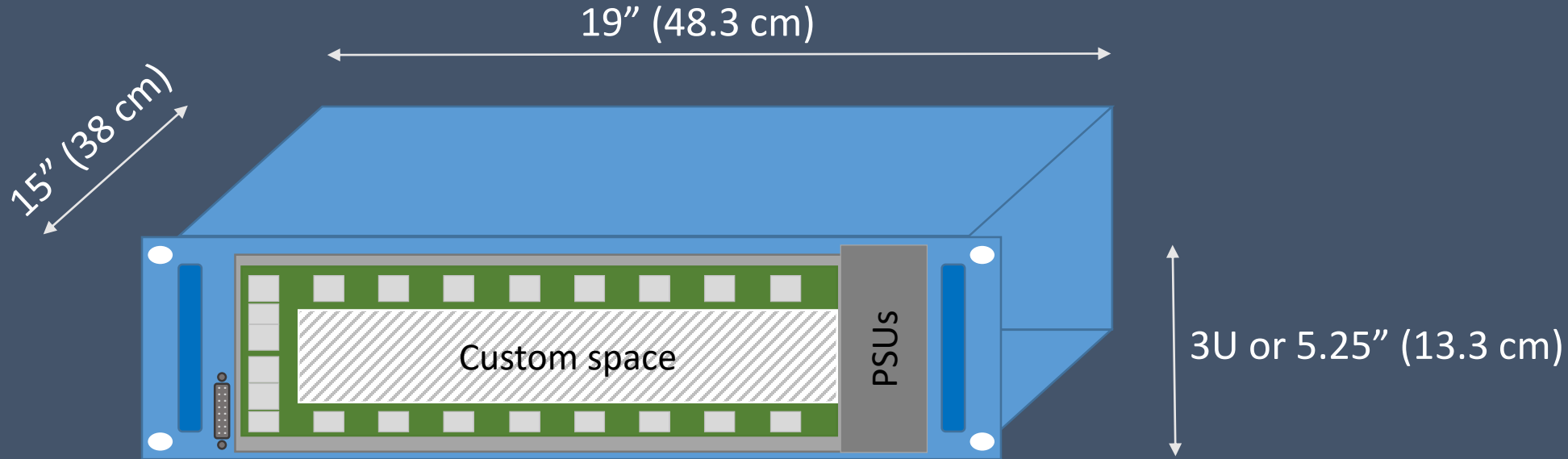

- Each PSU: 3U x 170 mm x 8HP
- Two PSUs in redundant/load-sharing mode
- Accessible from front side

Target user groups in CERN

- Beam instrumentation (BE-BI)
- Magnet positioning (EN-SMM)
- Machine protection (TE-MPE)
- Electrical power converters (TE-EPC)
- More ...?


Assumptions

1. All PCBs in the crate (system and peripheral) have POL regulators for low voltage digital circuits (1-3.3V)
2. Power for high performance analog circuits (<10mV ripple + noise) is provided by dedicated linear regulators external to RaToPUS.

Project schedule

Task	YEAR #1				YEAR #2			
	2018 Q4	2019 Q1	2019 Q2	2019 Q3	2019 Q4	2020 Q1	2020 Q2	2020 Q3
Define specifications; Survey existing solutions								
Design and simulation								
Radiation effects training								
Laboratory prototyping								
Define test specifications and test plan								
Non-radiation testing and improvements								
Radiation testing and improvements								

Project workflow

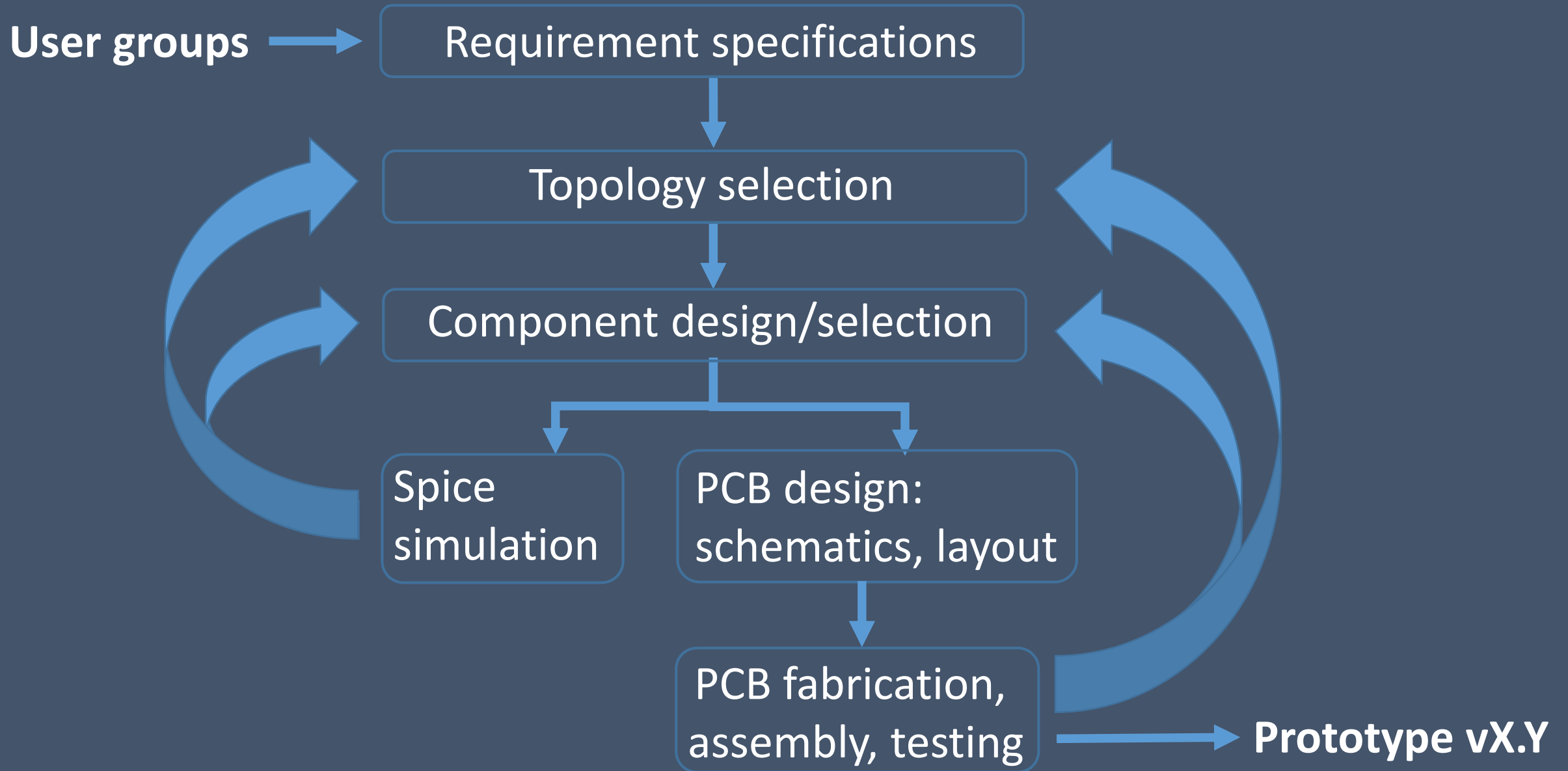

Requirement specifications (tentative)

Parameter	Value
Input: V_{in}, f, I_{in}	230 Vac, 50 Hz
Outputs: $V_{o1}, I_{o1} (P_{o1})$ $V_{o2}, I_{o2} (P_{o2})$	12 V, 8.33 A (100 W) 5 V, 2 A (10 W)
Output voltage ripple + noise, ΔV_{o1} ΔV_{o2}	100 mVpp for 12 V 20 mVpp for 5 V
TID	>500 Gy (1000 Gy?)
PCB dimensions	100 mm x 160 mm x 37 mm
PSU dimensions (including packaging)	3U x 170 mm x 8HP i.e. 133 mm x 170 mm x 40 mm
Switching frequency, f_s	250 kHz - 1 MHz
External monitoring/control	PMBus and PS_ON (for remote switching ON/OFF)
EMI specifications	EN55022 Class B
Thermal environment:	
- Ambient temperature	40°C
- Fan tray available	Yes

Existing Rad-Tol PSU solutions at CERN

7-15Vac 10-20Vdc
50 Hz Transformer → Bridge Rectifier → LDO

7-15Vac 10-20Vdc
50 Hz Transformer → Bridge Rectifier → DC/DC



- BE-BI-BL (25W)
- TE-MPE-EP (40W)
- TE-CRG-CI (100W)

Advantages

- Simple and robust design
- No higher voltage switching

Disadvantages


- Large and costly transformer
- Large heat dissipation in crate
- No PFC ⇒ Large EMI filter

35Vac 48Vdc
50 Hz Transformer → Bridge/PFC Rectifier → DC/DC




- TE-EPC-CCE (70W)

RaToPUS power architecture: Option-1

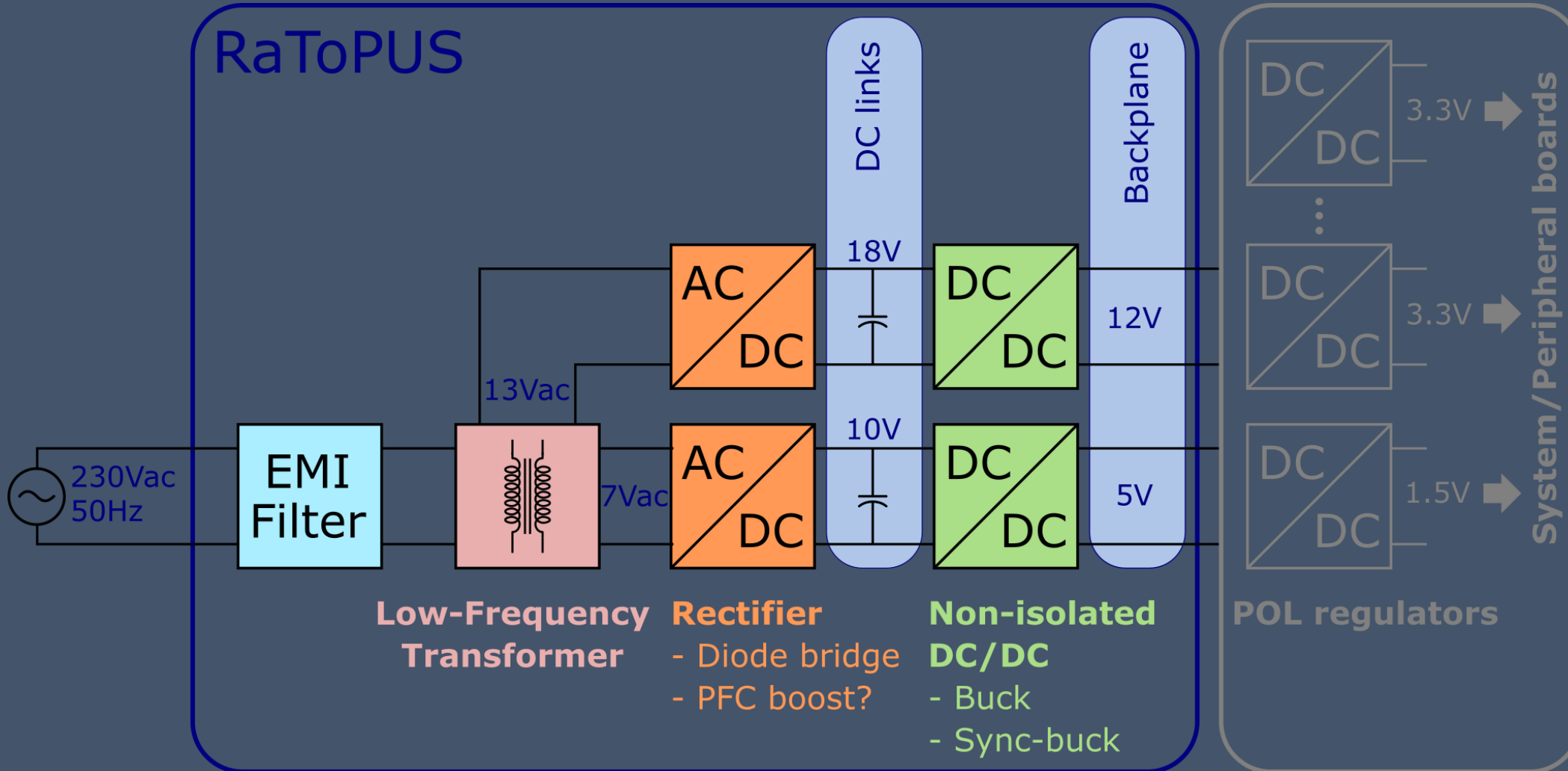

- Large low-frequency transformer
- MOSFETs switching at lower voltage
- Large EMI filter?

RaToPUS power architecture: Option-2

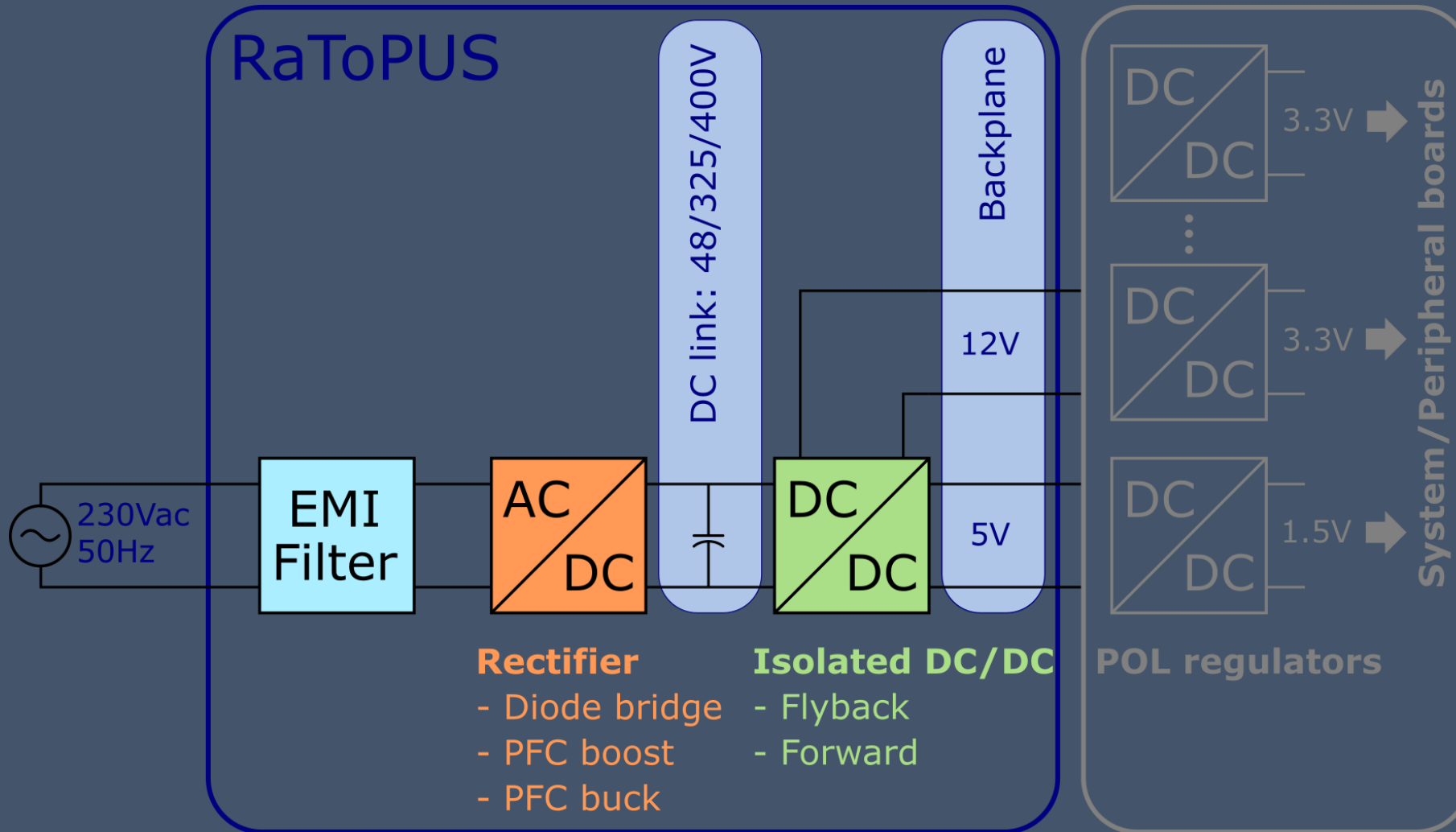

- Small high-frequency transformer (part of isolated DC/DC converter)
- MOSFETs switching at higher voltage
- Small EMI filter

Radiation hardness: Power stage components

Component	Options	Rad hardness (TID)
EMI Filter	Schurter FMLB-41	✓
Bridge rectifier diodes	Multicomp ABS8	TBD
Power MOSFETs	Infineon IRLI540N Infineon IRH NJ67C30 Infineon IRFB4310 Vishay IRFL110	TBD 1000 Gy [†] 300 Gy* 300 Gy*
Filter and DC link capacitors:	Ceramic Aluminium electrolytic Tantalum electrolytic	TDK C Series -- --
Filter inductor	Bourns SRP1038A Series	✓
HF transformer	Coilcraft	✓
LF transformer	Toroidal	✓

Radiation hardness: Other components



Component	Options	Rad hardness (TID)
Analog controllers for power stages: For DC-DC stage	FEAST	2 MGy*
	ST1845	1000 Gy [†]
For PFC stage	UCC28056	TBD
House-keeping bias (power supply for controllers): Extra flyback winding + diode on HF transformer	STPS10H100C Schottky	TBD
MOSFET gate drivers (+12V, -3V)	NCP5901	TBD
	RHRPM4424	1000 Gy [†]
Isolated voltage sensing	HCNR200	150 Gy*
	ACPL-C87B	TBD
Isolated current sensing: Hall-effect sensors	ACS712	TBD
PWM pulse isolation: High-speed optocouplers	FOD8012A	TBD
Temperature sensing: Solid-state sensors	LM45	1000 Gy*
Thermocouple/RTD	PT100	✓
MCU/DSP/FPGA for PMBus implementation	TBD	TBD

Feasibility study: FEAST as controller for DC/DC stage

Typical configuration: Up to 10W



Modified configuration: Up to 100W

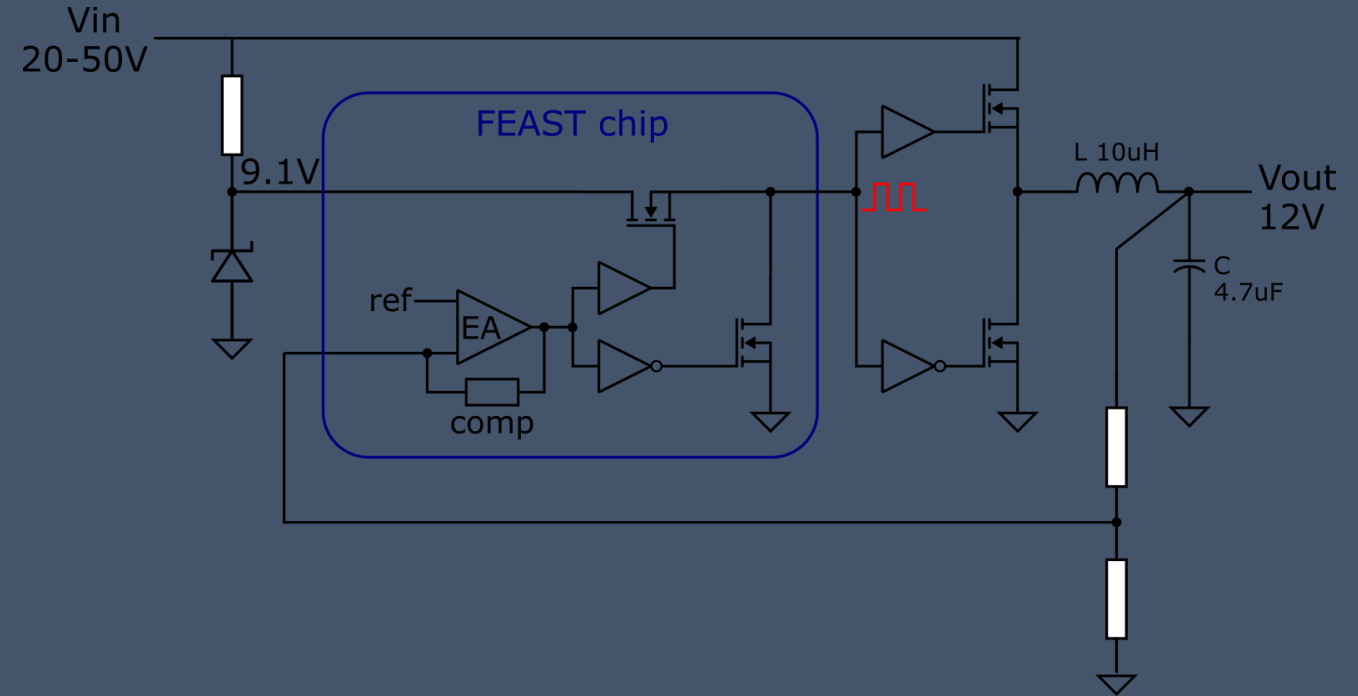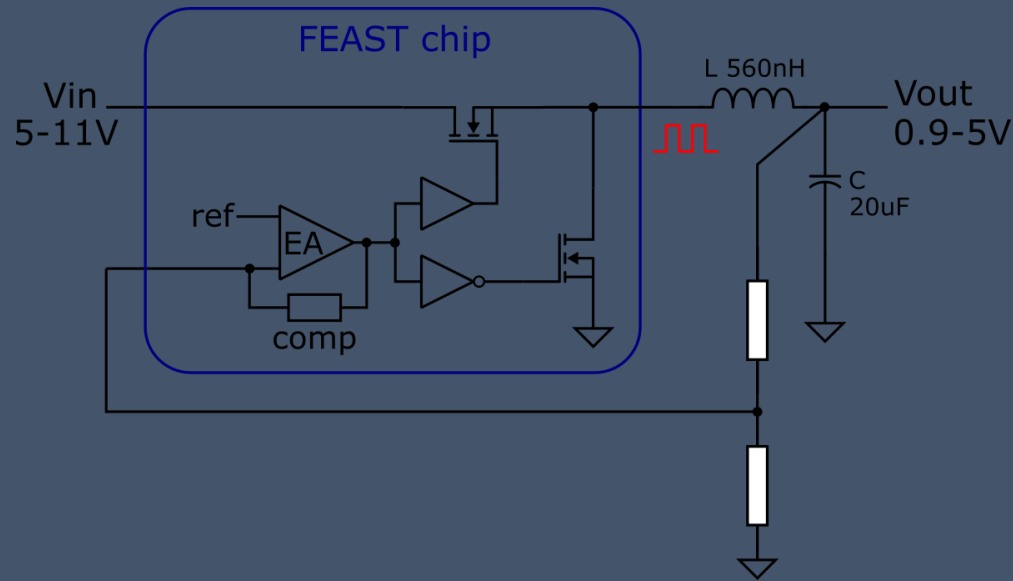




- External MOSFETs of higher V and I rating
- Larger LC filter on output side
- 9-12V HKB (house-keeping bias)
- Delayed EN for bootstrap capacitor charging

Feasibility study: FEAST as controller for DC/DC stage

Typical configuration: Up to 10W



Modified configuration: Up to 100W

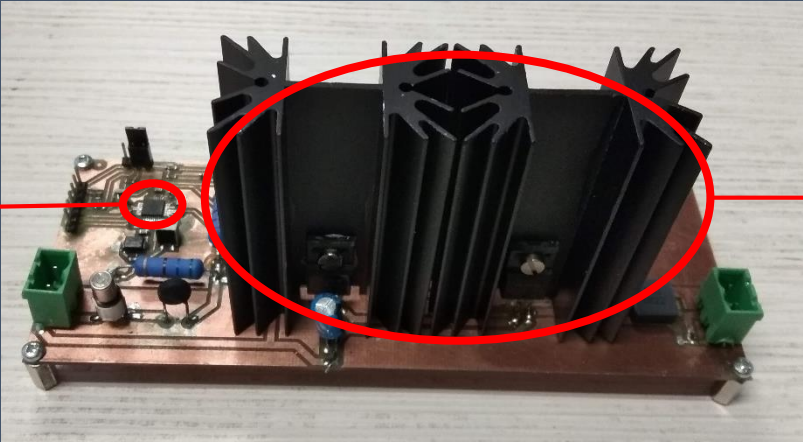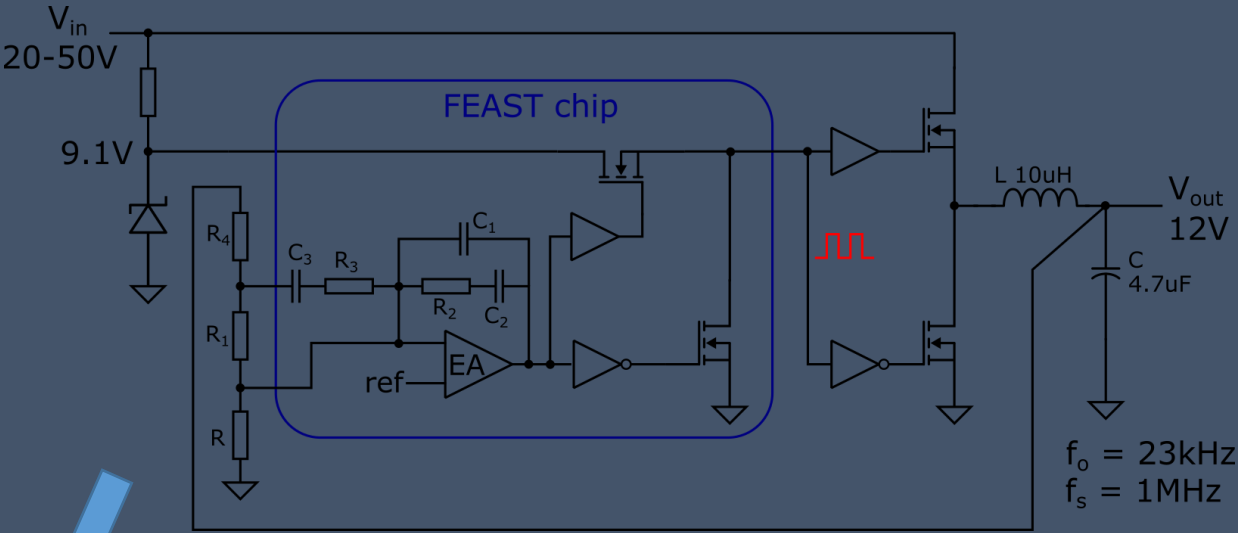
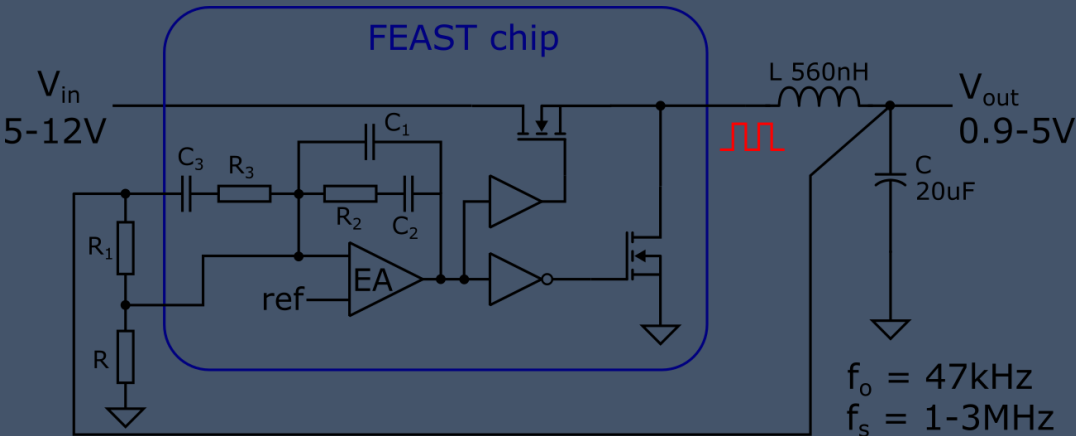


FEAST chip

External MOSFETs with heatsinks

- Lab prototype
- Loop stability issues

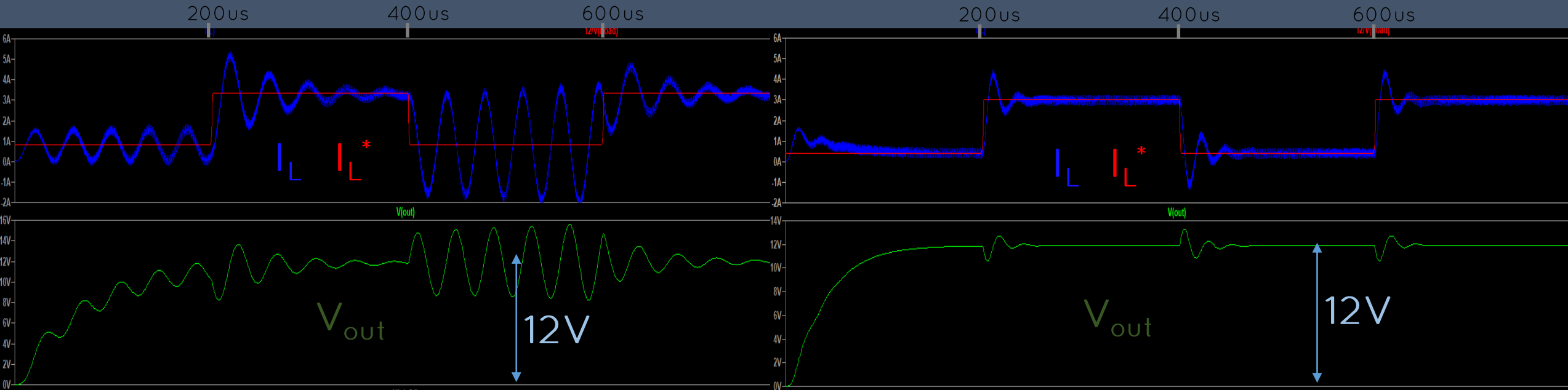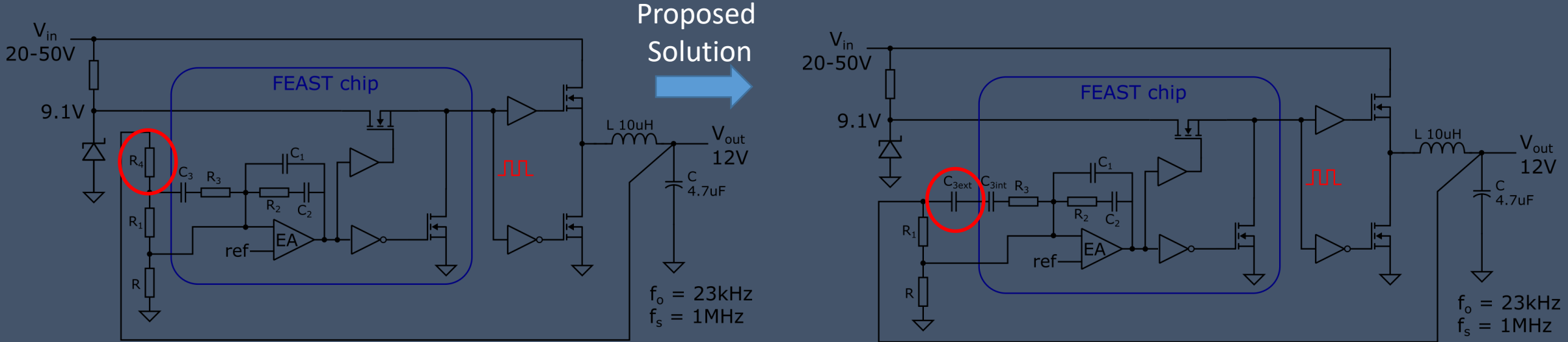Feasibility study: FEAST as controller for DC/DC stage



Spice simulation results:

With R_4

With C_{3ext}

Future work and open questions

- Can compensation network of FEAST be externally modified for stable operation with up to 100W load? Provisional answer: Yes
- Can the switching frequency of FEAST be pushed under 1 MHz? (Typical 1-3 MHz)
- Rad-hard isolated DC/DC converter: Design and implementation
- Rad-hard PFC converter: Design and implementation
- Can GaN/SiC FETs be reliably used in radiation environment?
- Effect of switching high voltage MOSFETs (600/700V) under radiation?
 - Threshold voltage
 - Leakage current
 - Single Event Effects/Burnout

<https://wikis.cern.ch/display/DIOT/Rad-tol+power+supply>