

Simulation of SET/SEU in microelectronics: AFTU software


F.R. Palomo¹, F.Muñoz¹, F.Márquez¹, E.López-Morillo¹
Mohsine Menouni²

fpalomo@us.es


¹Departamento Ingeniería Electrónica, Escuela Superior de Ingenieros
Universidad de Sevilla, Spain

²CPPM Centre de Physique des Particules de Marseille
Marseille, France

Radiation effects in Electronics

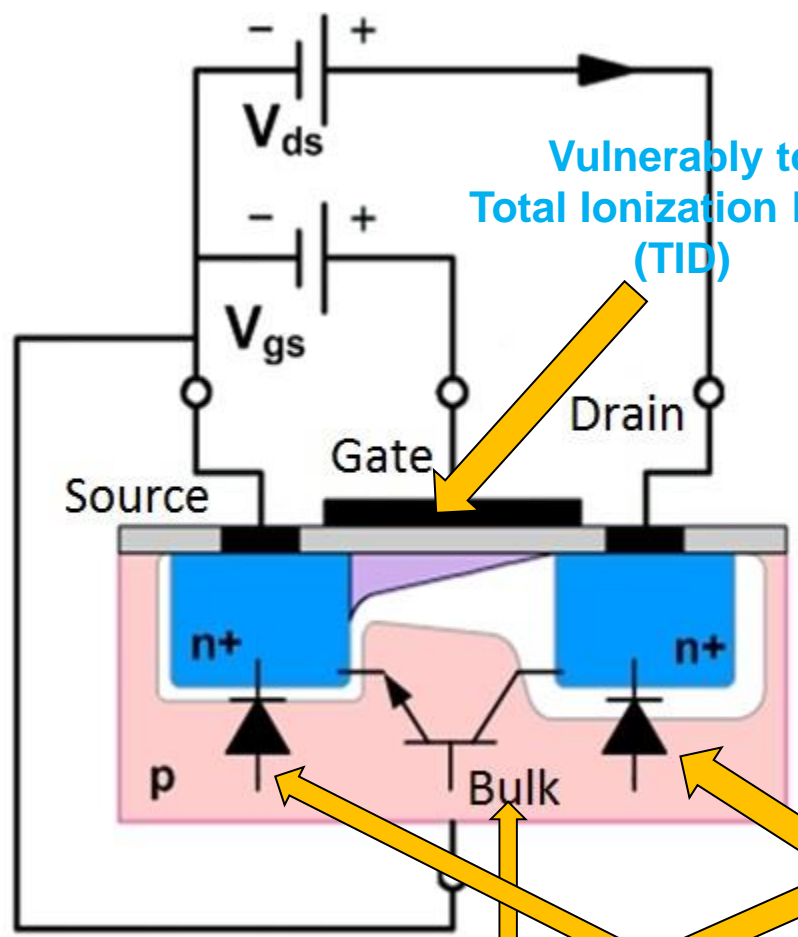


Vulnerably to Displacement Dose Damage

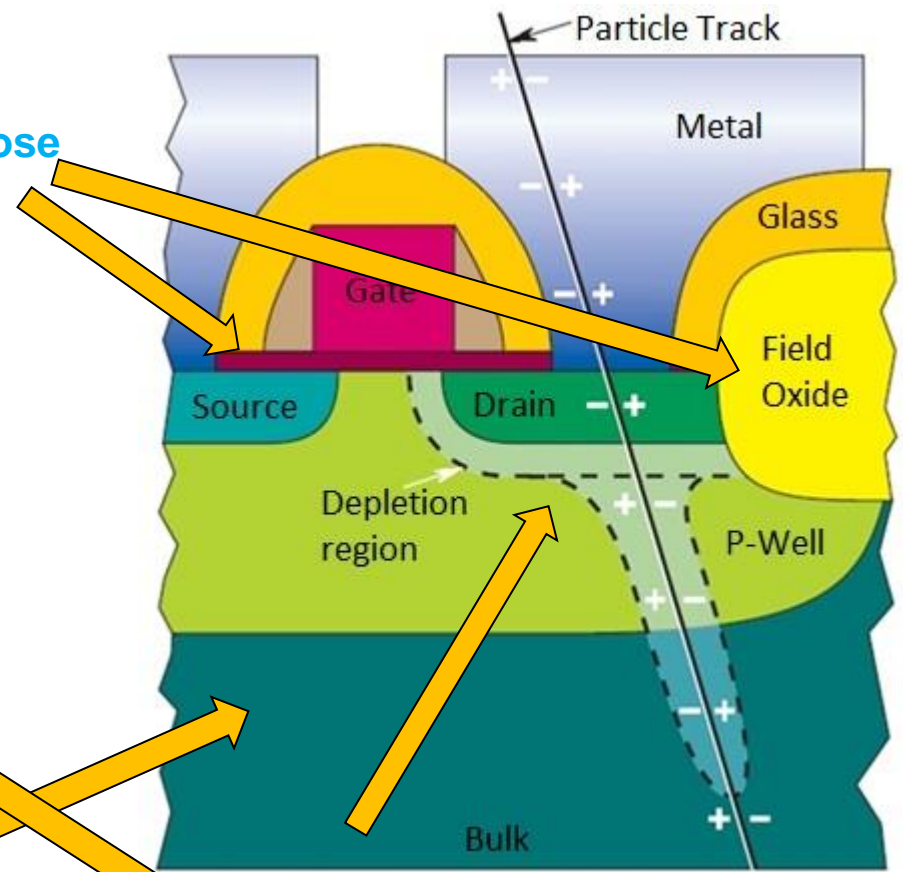

Vulnerably to Transient Ionization (Single Event Currents)

SEU (bitflips) and SET (glitches)

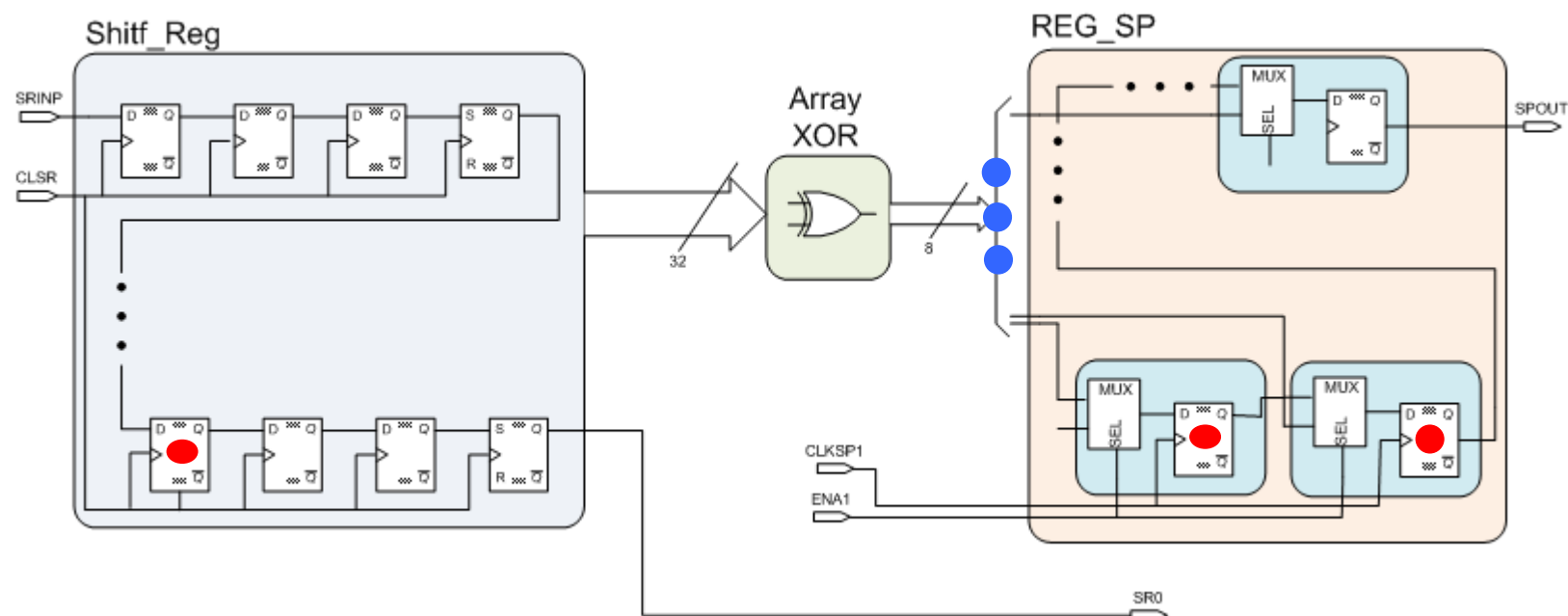


Single Event Upsets (Red) affect to memory cells producing bit flips

Single Event Transients (Blue) affect to any transistor, producing glitches

SETs effects are harder to detect and can produce Cascade Bitflips

SEE and Critical Charge

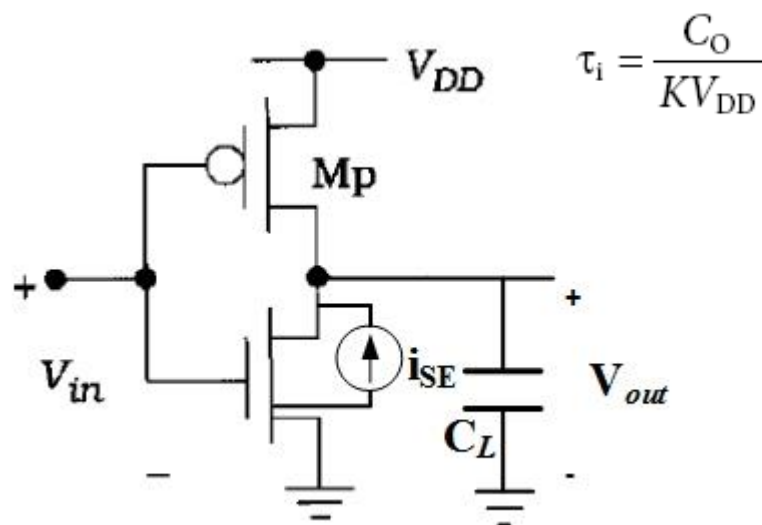

τ_i : inverter intrinsic time constant
 C_O is the total output capacitance
 V_{dd} is the power rail voltage

τ_e : charge collection single event
 time constant ($< 1\text{ps}$)

$\tau_e \ll \tau_i$ implies Single Event Effect (switching)

So at Critical node (V_{out}) the SEE induced ΔV is:

$$\Delta V = \int \frac{i_{SE}(t)}{C_N} dt = \frac{Q_{\text{collected}}}{C_N}$$

$$Q_{\text{crit}} = C_N \cdot \Delta V_{\text{nm}}$$

$i_{SE}(t)$ is the single event photocurrent
 $Q_{\text{collected}}$ is the total charge delivered to/from
 the node by the single event photocurrent
 C_N is the total nodal capacitance


Q_{crit} is the total charge delivered to/from
 the node by the single event photocurrent
 C_N is the total nodal capacitance
 ΔV_{nm} is the node voltage

What is AFTU?

The Analog FTU Hardware Debugging System is a software tool to evaluate the **SEE sensitivity** of analog/mixed signal circuits at **transistor level**

How does it work?




AFTU parses a Spectre design netlist...

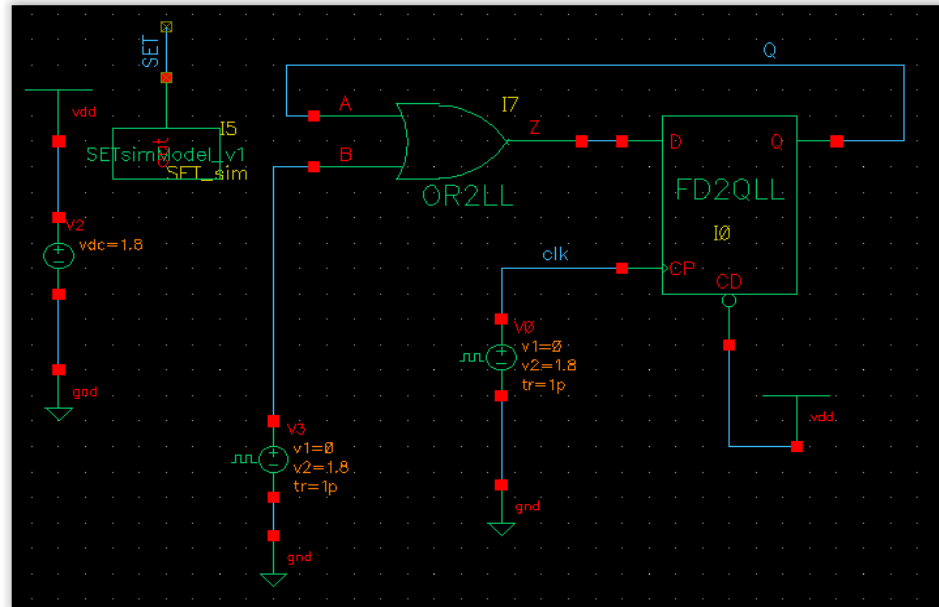

...to generate a parametric simulation Ocean script

- Analysis of Transient Effects in Analogue Topologies, F.Marquez, F.Muñoz, F.R.Palomo, M.A.Aguirre and M.Ullán, AMICSA 2012, Noordwijk, Netherlands 26th -28th August 2012, <http://microelectronics.esa.int/amicosa/2012/amicosa2012.htm>
- Automatic inspection of SET sensitivity in analog cells, F.Márquez, F.Muñoz, M.A.Aguirre, F.R.Palomo and M.Ullán, SMACD'12, Sevilla, Spain, 19th-21st Sept. 2012 http://www2.imse-cnm.csic.es/~smacd2012/SMACD_2012/HOME.html
- AFTU, an analog single event effects automatic analysis tool, F.Marquez, L.Sanz, F.R.Palomo, F. Muñoz and M.A.Aguirre, AMICSA 2014, CERN, Switzerland, 30th June-1st July 2014, <https://indico.cern.ch/event/277669/>
- Automatic Single Event Effects Sensitivity Analysis of a 13-Bit Successive Approximation ADC, F.Márquez, F.Muñoz, F.R.Palomo, L.Sanz, E.López-Morillo, M.Aguirre and A.Jiménez, **IEEE Transactions on Nuclear Science**, **62(4)** 2015, pp.1609-1616

...emulates Single Event Effects...

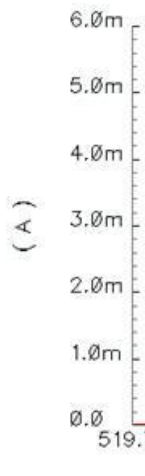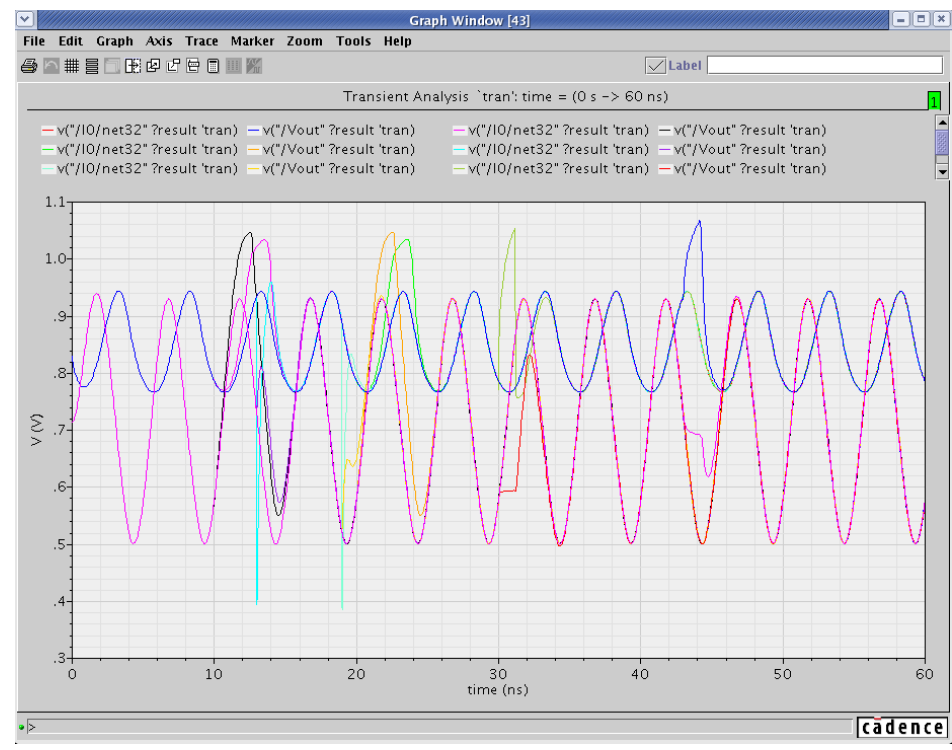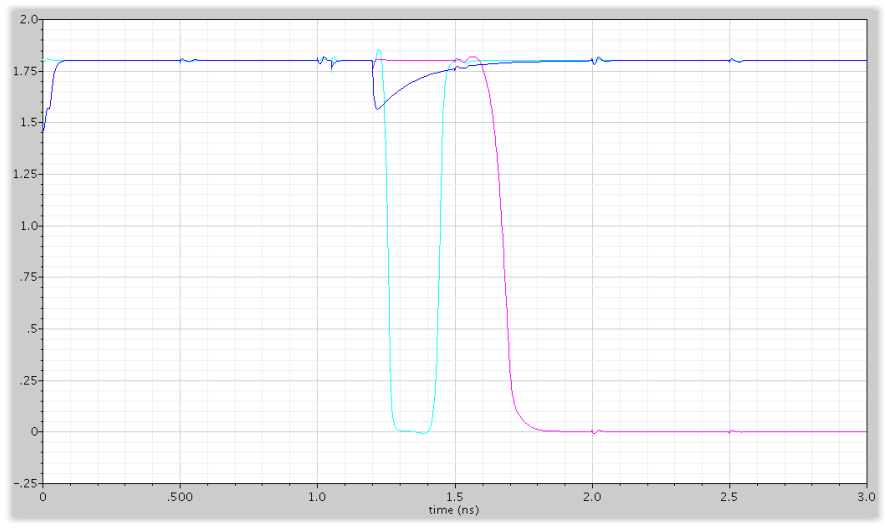


$$I_{rad} = \frac{Q_c}{\tau_d - \tau_r} \left(e^{-\frac{\tau}{\tau_d}} - e^{-\frac{\tau}{\tau_r}} \right)$$

$$Q_c = \frac{\rho \cdot LET \cdot d}{3.6}$$

Injection Current
Default Model

An injection current source at every node or at user selected nodes is the way to emulate the SEE. The injection source model can be changed.


... and evaluates vulnerabilities

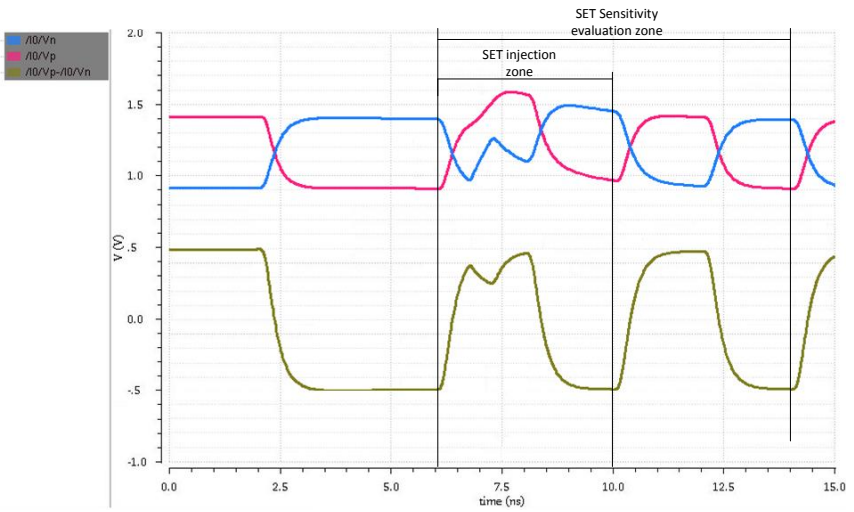

- The user defines injection and evaluation zones
- and select the appropriate hard coded heuristic to analyze the parametric simulation results

D-latch circuit, STMicroelectronics 130 nm

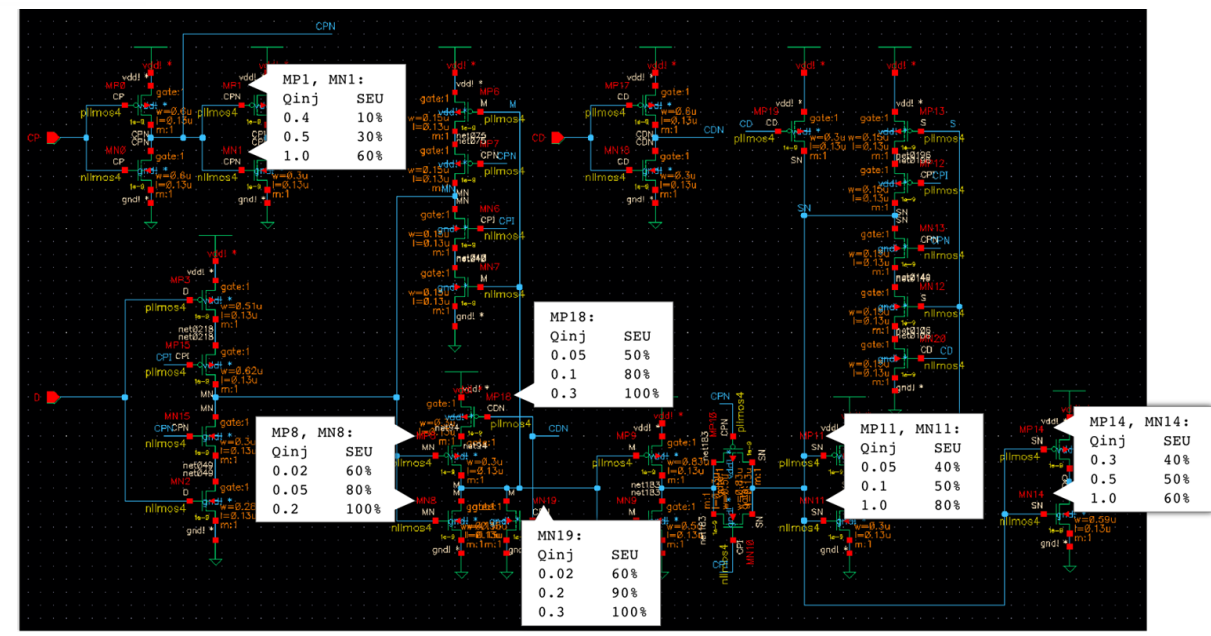- The final result is a list of vulnerabilities (in terms of the heuristic) for each user selected node in the design.




User Web Interface (Fault Injection Campaign)

The screenshot shows a web browser window with the address bar displaying 'ftu.us.es/uff/'. The page content is divided into two main sections:

- Left Panel (List of Fault Injection Points):** A scrollable list of identifiers for various fault injection points, including:
 - I1_18_I2_M_u1_2
 - I1_18_I2_M_u1_1
 - I1_18_I2_M_u2_1
 - I1_18_I2_M_u2_3
 - I1_18_I2_M_u2_0
 - I1_18_I2_M_u2_2
 - I1_18_I4_M_u1_0
 - I1_18_I4_M_u1_3
 - I1_18_I4_M_u1_2
 - I1_18_I4_M_u1_1
 - I1_18_I4_M_u2_1
 - I1_18_I4_M_u2_3
 - I1_18_I4_M_u2_0
 - I1_18_I4_M_u2_2
 - I1_18_I3_M3
 - I1_18_I3_M_u1
 - I1_18_I3_M4
 - I1_18_I3_M_u2
 - I1_18_M0
 - I1_18_M2
- Right Panel (Detailed View of Selected Point):** A scrollable view showing the configuration for a selected point, such as 'I1_19_I2_M_u1_0'. The configuration includes:
 - Charges (Q): 0.5p
 - Times (t): 2n:6n:1n


Hard Coded Heuristics

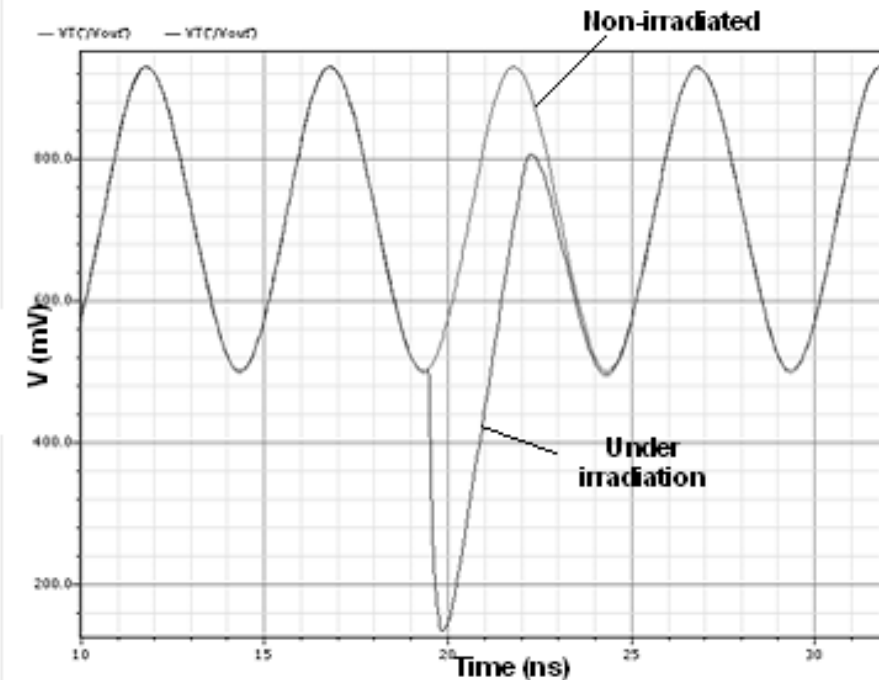Deviation Recovery
(ex. analog circuits SET's)




- Recovery Time
- Signal Voltage Deviation

 Time Ranges
(ex. digital SEU's & differential circuits SET's)



- Total time between up to 4 signal thresholds

User Web Interface (Heuristics)

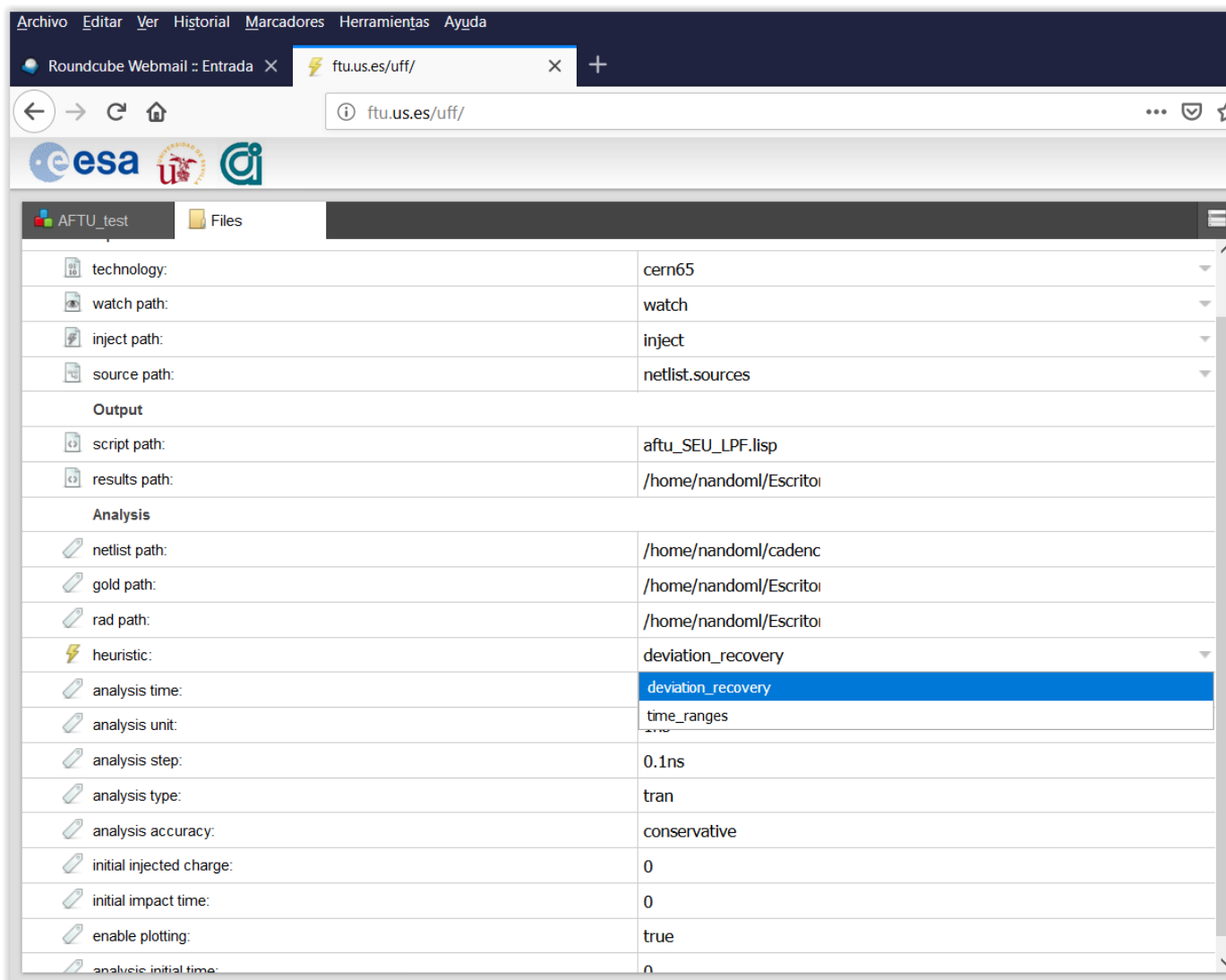


The screenshot shows a web browser window with the address bar displaying 'ftu.us.es/uff/'. The page content is a configuration interface for heuristics, organized into sections: 'technology:', 'Output', 'Analysis', and 'heuristic:'. Each section contains a list of parameters and their corresponding values.

technology:	cern65
watch path:	watch
inject path:	inject
source path:	netlist.sources
Output	
script path:	aftu_SEU_LPF.lisp
results path:	/home/nandoml/Escrito
Analysis	
netlist path:	/home/nandoml/cadenc
gold path:	/home/nandoml/Escrito
rad path:	/home/nandoml/Escrito
heuristic:	deviation_recovery
analysis time:	deviation_recovery
analysis unit:	time_ranges
analysis step:	0.1ns
analysis type:	tran
analysis accuracy:	conservative
initial injected charge:	0
initial impact time:	0
enable plotting:	true
analysis initial time:	0


Analysis of FE-I4 DICE structures

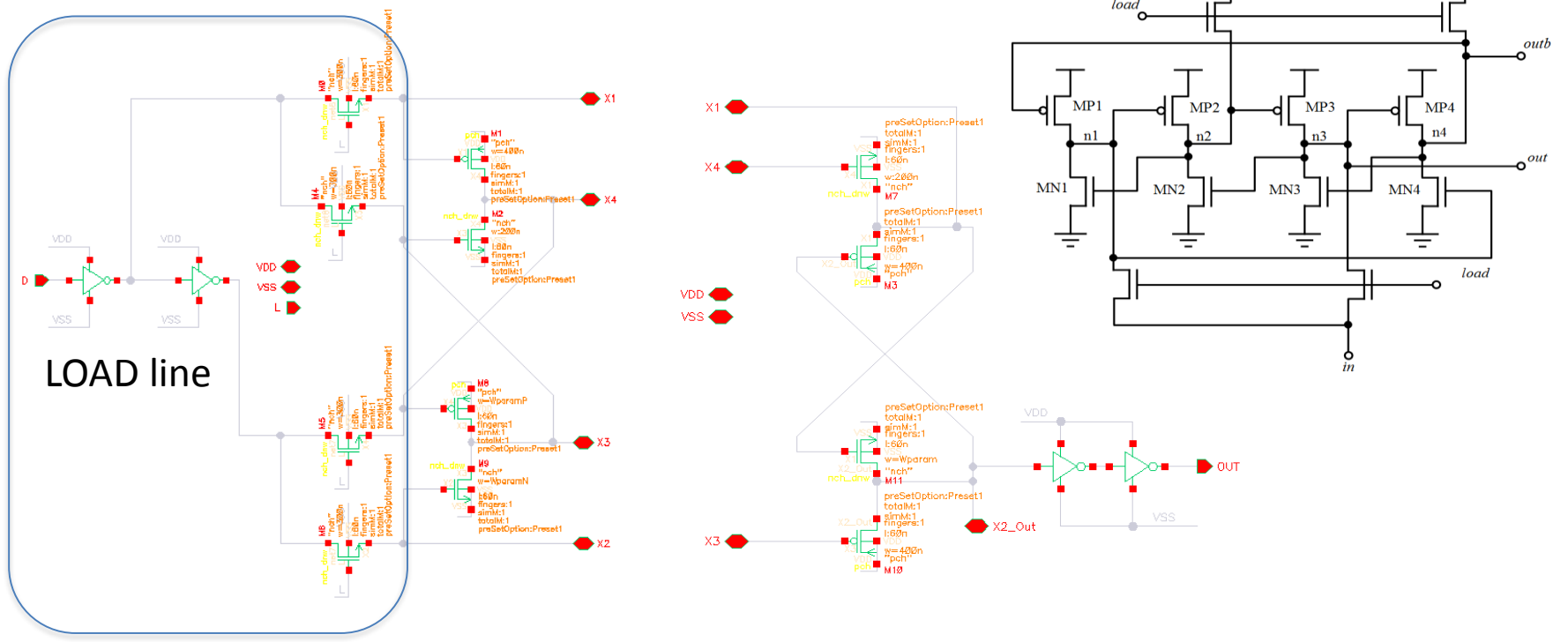- Circuit schematics (interleaved version)
 - Increased robustness against SET/SEU due to DICE structure
 - Only affected by simultaneous impacts at n1,n3 or n2, n4



DICE structure analysis with AFTU

 - Impacts at 4 different times (0.5, 1.25, 2.5, 3.25 ns) in every transistor of the DICE
 - Every possible input/output state is studied



DICE structure analysis with AFTU

- Impacts at 4 different times (0.5, 1.25, 2.5, 3.25 ns) in every transistor of the DICE
- According to results, there are 4 classes of transistors:
 - Class I: no effect on the latch output
 - Class II: transient glitch at the latch output, with no permanent effect (SET)
 - Class III: a change of the state at the output (SEU)
 - Class IV: a pair of transistors simultaneously impacted that generate a SEU at the latch output.

DICE structure analysis with AFTU

<i>Qinj</i>	<i>Class</i>	<i>Transistors</i>
0.05 pC	I	All except class II
	II	M10, M11, M9, M3
	III	None
	IV	(M11-M8), (M11-M2), (M10-M7), (M10-M1)
0.1 pC	I	All except class II
	II	M10, M11, M9, M3
	III	None
	IV	(M11-M8), (M11-M2), (M10-M7), (M10-M1), (M11-M6), (M11-M5), (M10-M0), (M10-M4), (M7-M9), (M7-M0), (M7-M4), (M9-M1), (M9-M0), (M9-M4), (M3-M2), (M3-M5), (M3-M6), (M8-M3), (M8-M6)
0.2 pC	I	M7, M8, M2, M1, MU1_X_M_u3
	II	M10, M11, M9, M3
	III	M0, M4, M6, M5, MU1_X_M_u2
	IV	(M11-M8), (M11-M2), (M10-M7), (M10-M1), (M11-M6), (M11-M5), (M10-M0), (M10-M4), (M7-M9), (M7-M0), (M7-M4), (M9-M1), (M9-M0), (M9-M4), (M3-M2), (M3-M5), (M3-M6), (M8-M3), (M8-M6)
0.3 pC	I	M7, M8, M2, M1, MU1_X_M_u3
	II	M10, M11, M9, M3
	III	M0, M4, M6, M5, MU1_X_M_u2
	IV	(M11-M8), (M11-M2), (M10-M7), (M10-M1), (M11-M6), (M11-M5), (M10-M0), (M10-M4), (M7-M9), (M7-M0), (M7-M4), (M9-M1), (M9-M0), (M9-M4), (M3-M2), (M3-M5), (M3-M6), (M8-M3), (M8-M6)


- Impacts in every transistor of the DICE for different values of injected charge
- “Secondary latch” seems safe when simple impacts are performed

DICE structure analysis with AFTU

<i>Qinj</i>	<i>Class</i>	<i>Transistors</i>
0.05 pC	I	All except class II
	II	M10, M11, M9, M3
	III	None
	IV	(M11-M8), (M11-M2), (M10-M7), (M10-M1)
0.1 pC	I	All except class II
	II	M10, M11, M9, M3
	III	None
	IV	(M11-M8), (M11-M2), (M10-M7), (M10-M1), (M11-M6), (M11-M5), (M10-M0), (M10-M4), (M7-M9), (M7-M0), (M7-M4), (M9-M1), (M9-M0), (M9-M4), (M3-M2), (M3-M5), (M3-M6), (M8-M3), (M8-M6)
0.2 pC	I	M7, M8, M2, M1, MU1_X_M_u3
	II	M10, M11, M9, M3
	III	M0, M4, M6, M5, MU1_X_M_u2
	IV	(M11-M8), (M11-M2), (M10-M7), (M10-M1), (M11-M6), (M11-M5), (M10-M0), (M10-M4), (M7-M9), (M7-M0), (M7-M4), (M9-M1), (M9-M0), (M9-M4), (M3-M2), (M3-M5), (M3-M6), (M8-M3), (M8-M6)
0.3 pC	I	M7, M8, M2, M1, MU1_X_M_u3
	II	M10, M11, M9, M3
	III	M0, M4, M6, M5, MU1_X_M_u2
	IV	(M11-M8), (M11-M2), (M10-M7), (M10-M1), (M11-M6), (M11-M5), (M10-M0), (M10-M4), (M7-M9), (M7-M0), (M7-M4), (M9-M1), (M9-M0), (M9-M4), (M3-M2), (M3-M5), (M3-M6), (M8-M3), (M8-M6)

- Impacts in every transistor of the DICE for different values of injected charge
- “Secondary latch” seems safe when simple impacts are performed
- DICE structure → No class III transistors expected

DICE structure analysis with AFTU

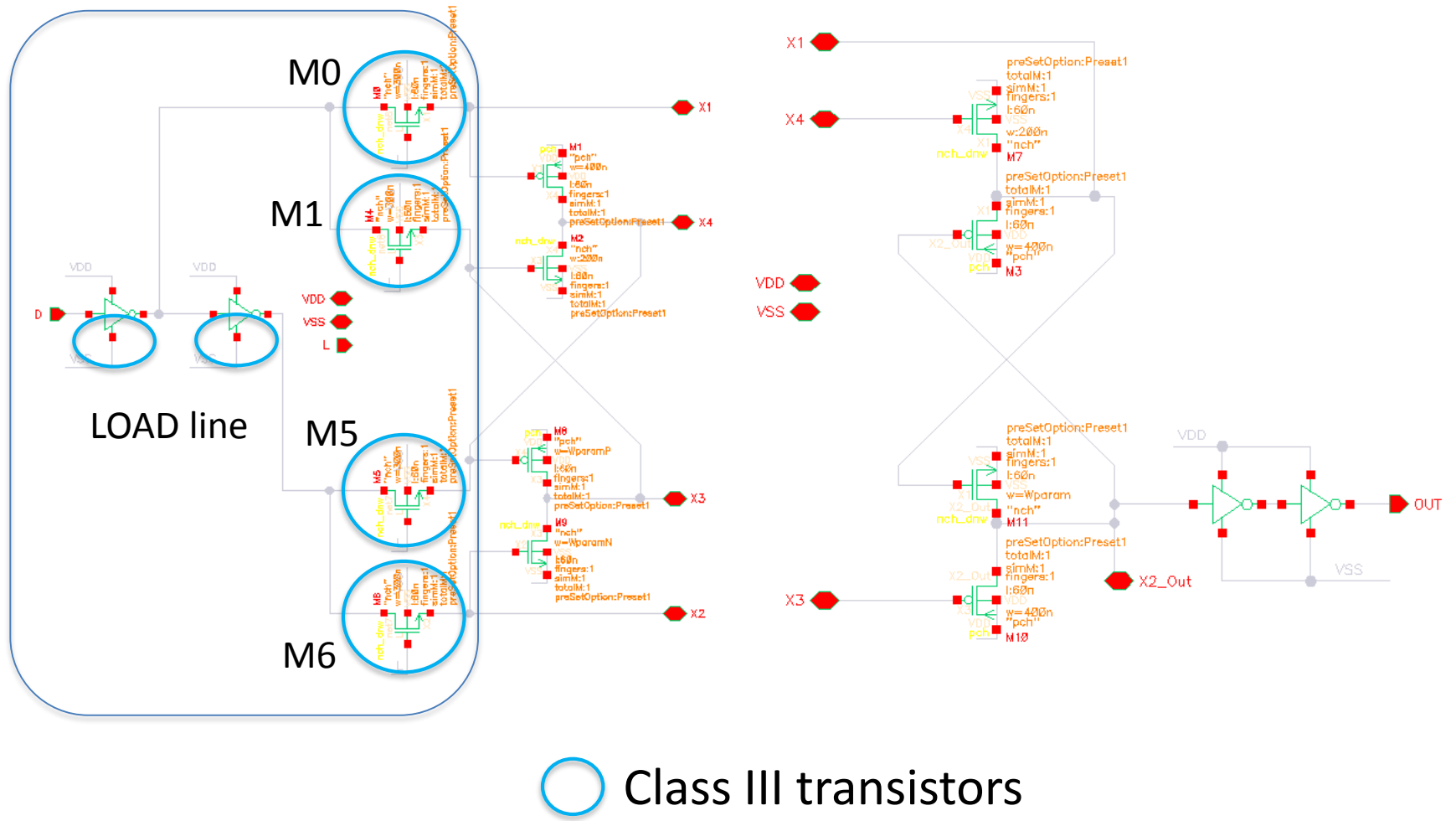

DICE structure analysis with AFTU



- A single impact in transistor M0 affects nodes 1 & 3 of DICE latch → SEU (class III)

A SET (glitch) in LOAD line produces a cascade of bitflips!

Results


- AFTU predicts that SETs in the LOAD line produce a SEU cascade downstream
- From experiments: they confirm AFTU predictions, see next talk, “SEU/SET results in ATLAS IBL FE-I4-B” by Marcello Bindi



Thanks for your attention

fpalomo@us.es


AFTU ToolChain

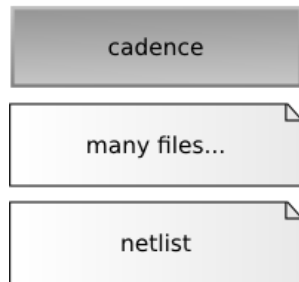

Before using AFTU:

- The user designs a circuit with Cadence as usual.
- The design is simulated through a testbench.
- Of all files generated by Cadence, we pick the **netlist**.


AFTU instrumentalize

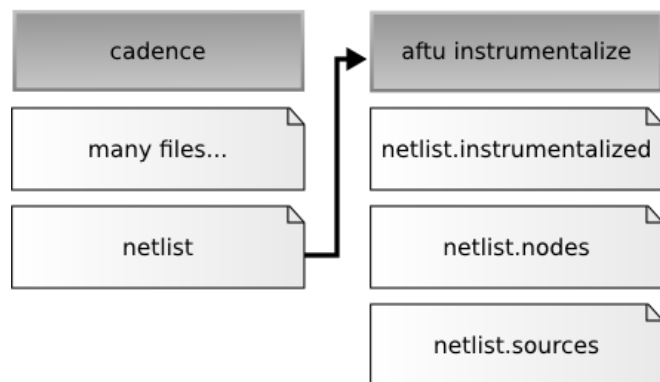

The **instrumentalizer** implements a parser for the SPECTRE language

- Replaces the **netlist** with a *functionally identical* one allowing SEE emulation.
- **netlist.nodes** lists all observable circuit nodes.
- **netlist.sources** lists all transistors where an impact can be emulated.


AFTU ocean init

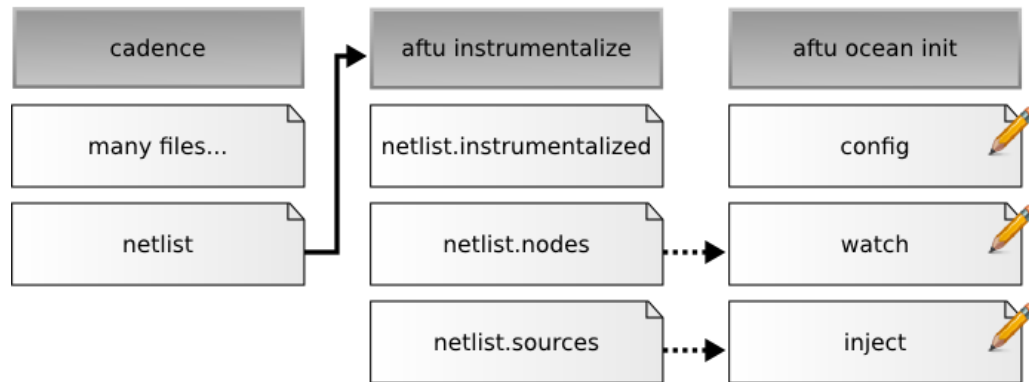

AFTU projects are flexible and give the user many options for analysis.

- **config** contains paths, times, heuristics parameters, initial values...
- **watch** defines all elements in the circuit to be observed during the simulation
- **inject** defines where, when and how much charge we inject (SEE emulation).


AFTU Ocean cook

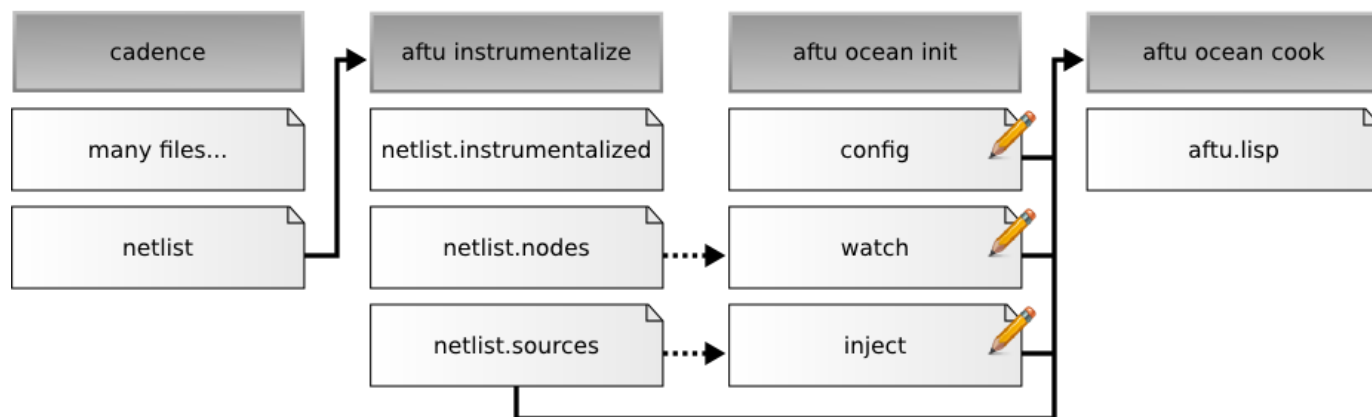

From all this data an Ocean simulation script is produced

- Includes all paths and required data.
- Describes the way to perform the user defined test campaign.
- Defines how to analyze the results of the campaign.

AFTU campaign

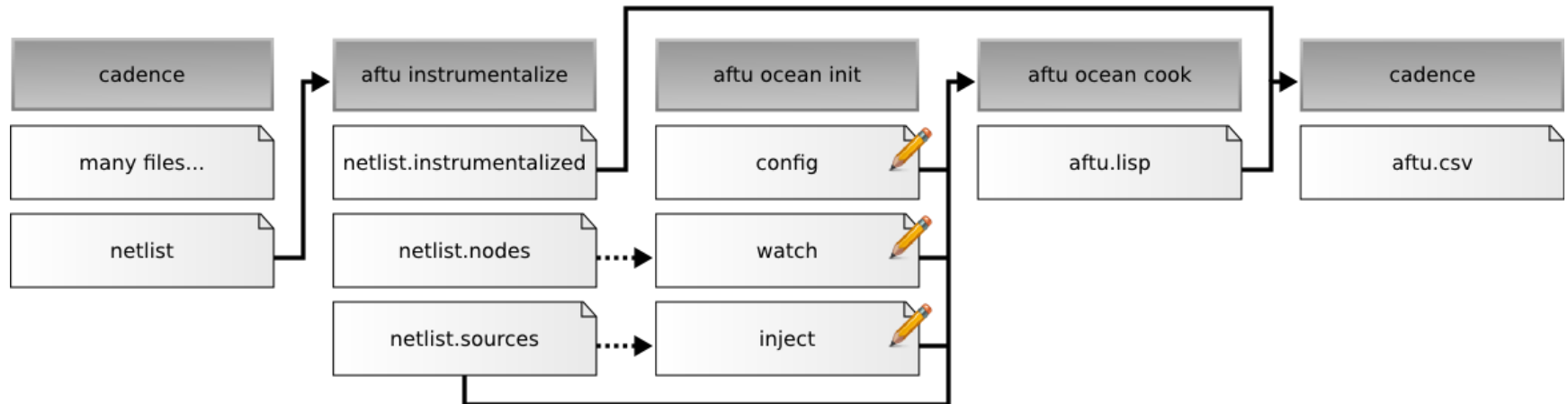


Cadence runs the provided script.

It produces a CSV file with the desired statistics.

This uncovers radiation vulnerabilities in the circuit.


A Practical Example

Let's say we have this circuit:


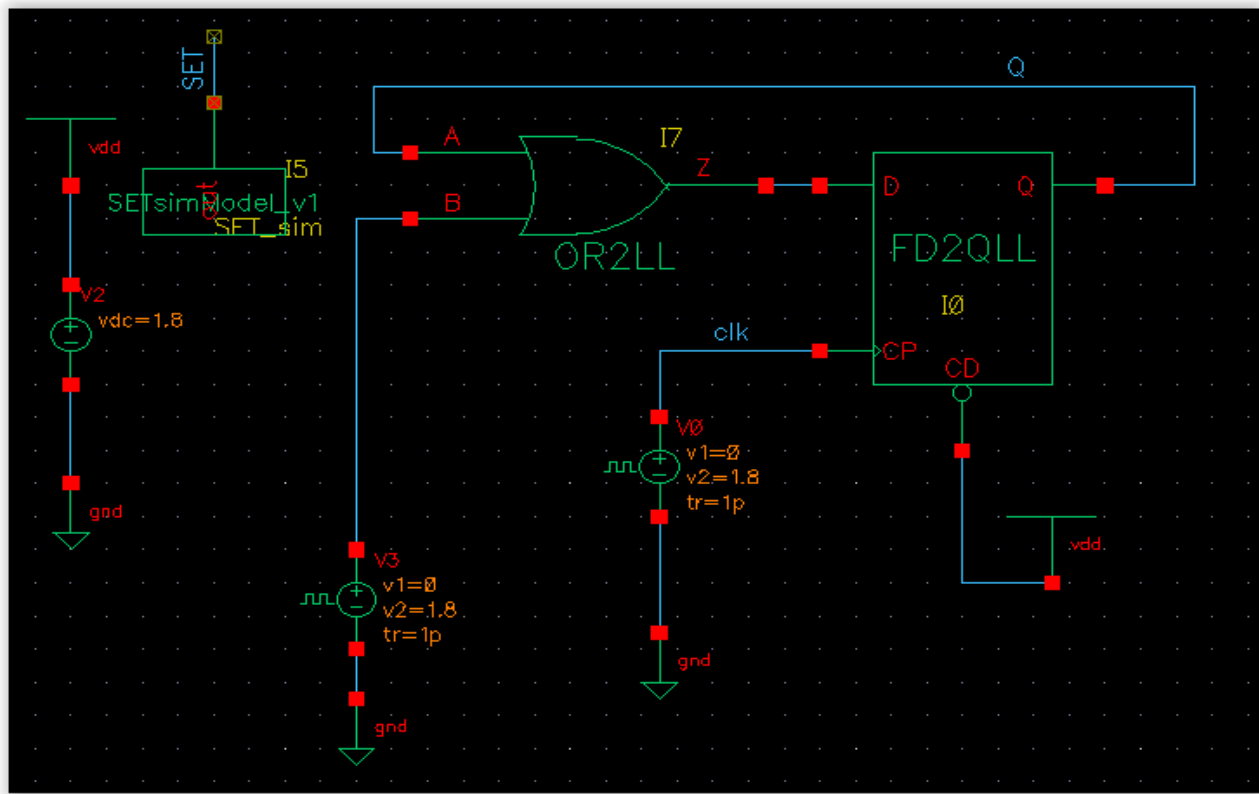


What is the critical charge to produce a SEU?


Netlist

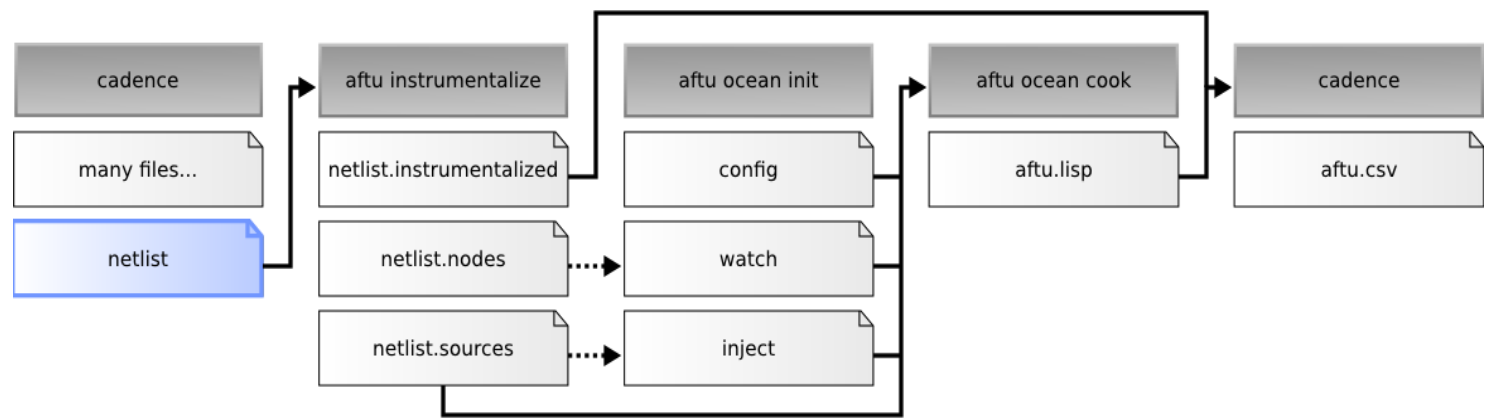

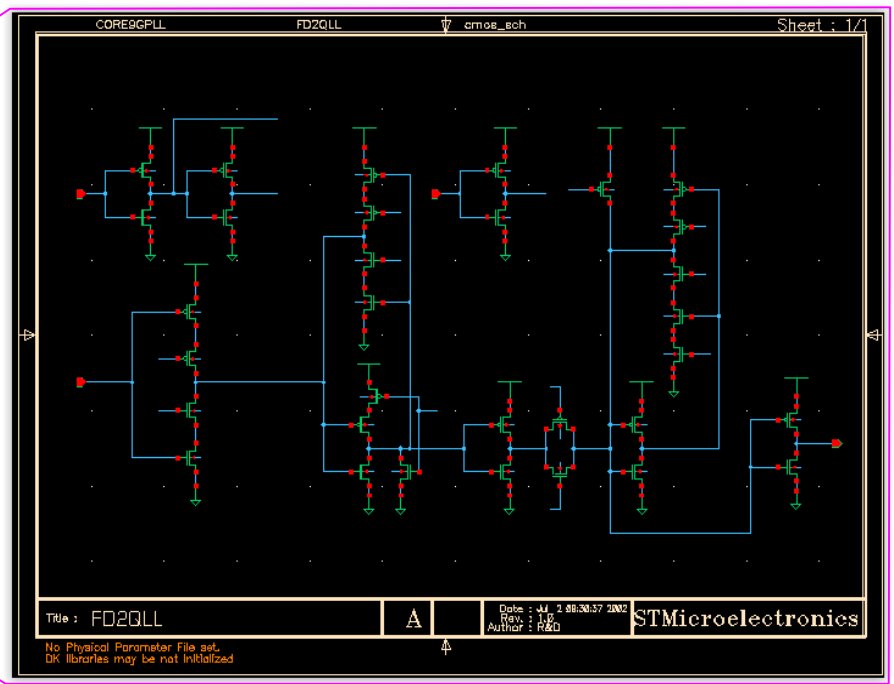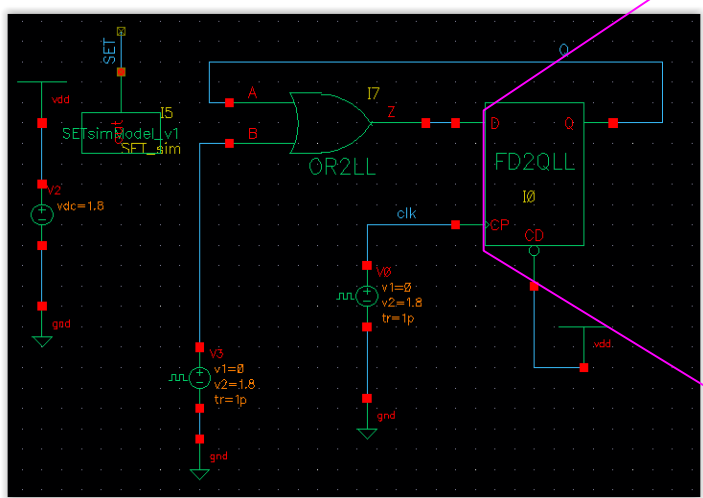D-latch transient testbench and schematic view of the digital cell
 STMicroelectronics 130 nm



Watch & Inject

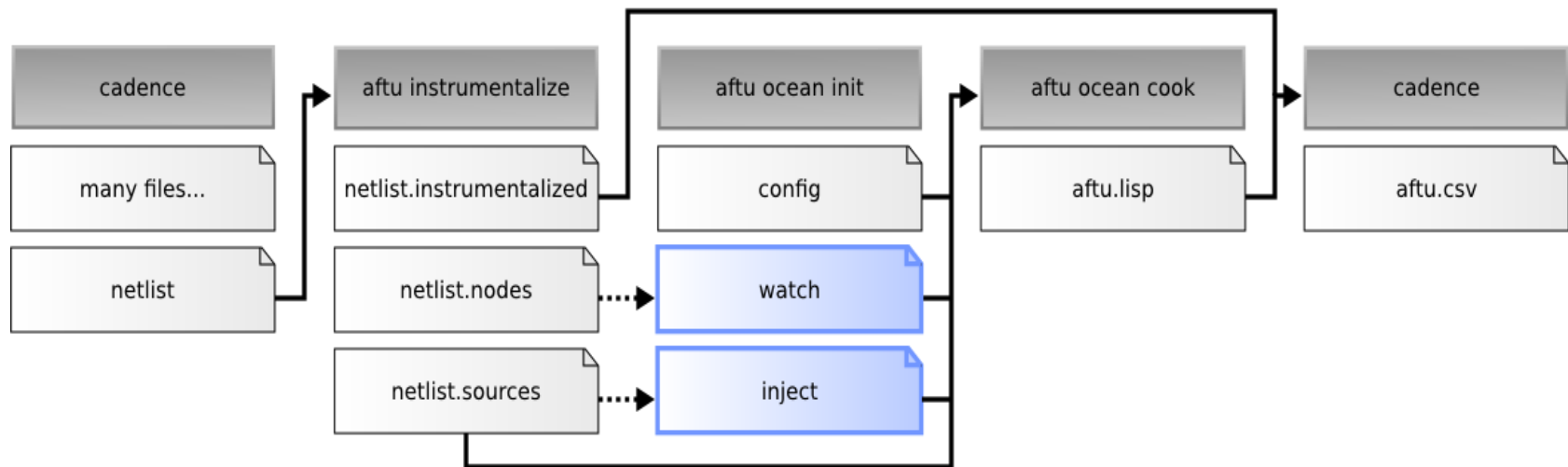

```

watch Q = /Q :
      threshold = 0.975 ;
  
```

```

inject I0_MP19:
  Q = .025p, .05p, 0.1p, .2p, .5p, .75p, 1p, 1.5p;
  t = 1.0n, 1.1n, 1.2n, 1.3n, 1.4n, 1.5n, 1.6n, 1.7n, 1.8n, 1.9n;
  
```


```

inject I0_MN19:
  Q = .025p, .05p, 0.1p, .2p, .5p, .75p, 1p, 1.5p;
  t = 1.0n, 1.1n, 1.2n, 1.3n, 1.4n, 1.5n, 1.6n, 1.7n, 1.8n, 1.9n;
  
```

```

inject I0_MP18:
  Q = .025p, .05p, 0.1p, .2p, .5p, .75p, 1p, 1.5p;
  t = 1.0n, 1.1n, 1.2n, 1.3n, 1.4n, 1.5n, 1.6n, 1.7n, 1.8n, 1.9n;
  
```

Results

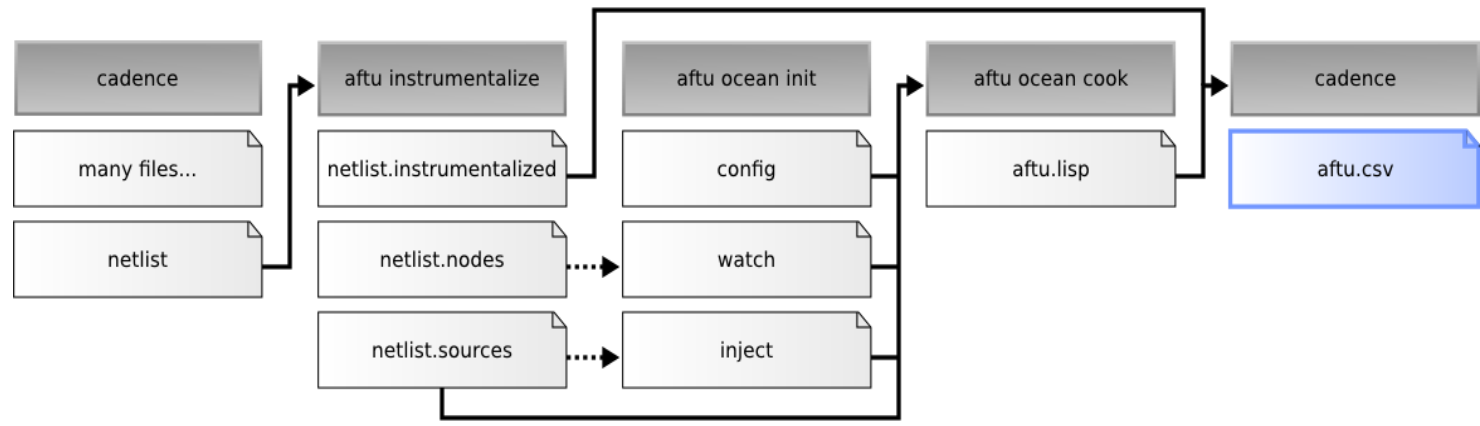


Output	ImpactNode	Qinj	Timp	Trec	Vmax
V_Q	I0_MP18	2.5e-14	1e-09	0.000000	0.001941
V_Q	I0_MP18	2.5e-14	1.1e-09	0.000000	0.00219
V_Q	I0_MP18	2.5e-14	1.9e-09	0.000000	0.003664
V_Q	I0_MP18	5e-14	1e-09	2.000000	1.807421
V_Q	I0_MP18	5e-14	1.1e-09	1.910000	1.807422
V_Q	I0_MP18	5e-14	1.2e-09	1.800000	1.807426
V_Q	I0_MP18	5e-14	1.3e-09	1.700000	1.807384
V_Q	I0_MP18	5e-14	1.8e-09	0.000000	0.519730
V_Q	I0_MP18	5e-14	1.9e-09	1.100000	1.803023

Output	ImpactNode	Qinj	Timp	Trec	Vmax
V_Q	I0_MN11	2.5e-14	1e-09	0.000000	0.006827
V_Q	I0_MN11	2.5e-14	1.9e-09	0.000000	0.016568
V_Q	I0_MN11	5e-14	1e-09	0.000000	0.017084
V_Q	I0_MN11	5e-14	1.3e-09	0.000000	0.005371
V_Q	I0_MN11	5e-14	1.4e-09	1.610000	1.806680
V_Q	I0_MN11	5e-14	1.5e-09	1.500000	1.806814
V_Q	I0_MN11	5e-14	1.6e-09	1.400000	1.805740
V_Q	I0_MN11	5e-14	1.7e-09	1.300000	1.802925
V_Q	I0_MN11	5e-14	1.8e-09	0.240000	1.404223

“Deviation Recovery” heuristic analysis

Results

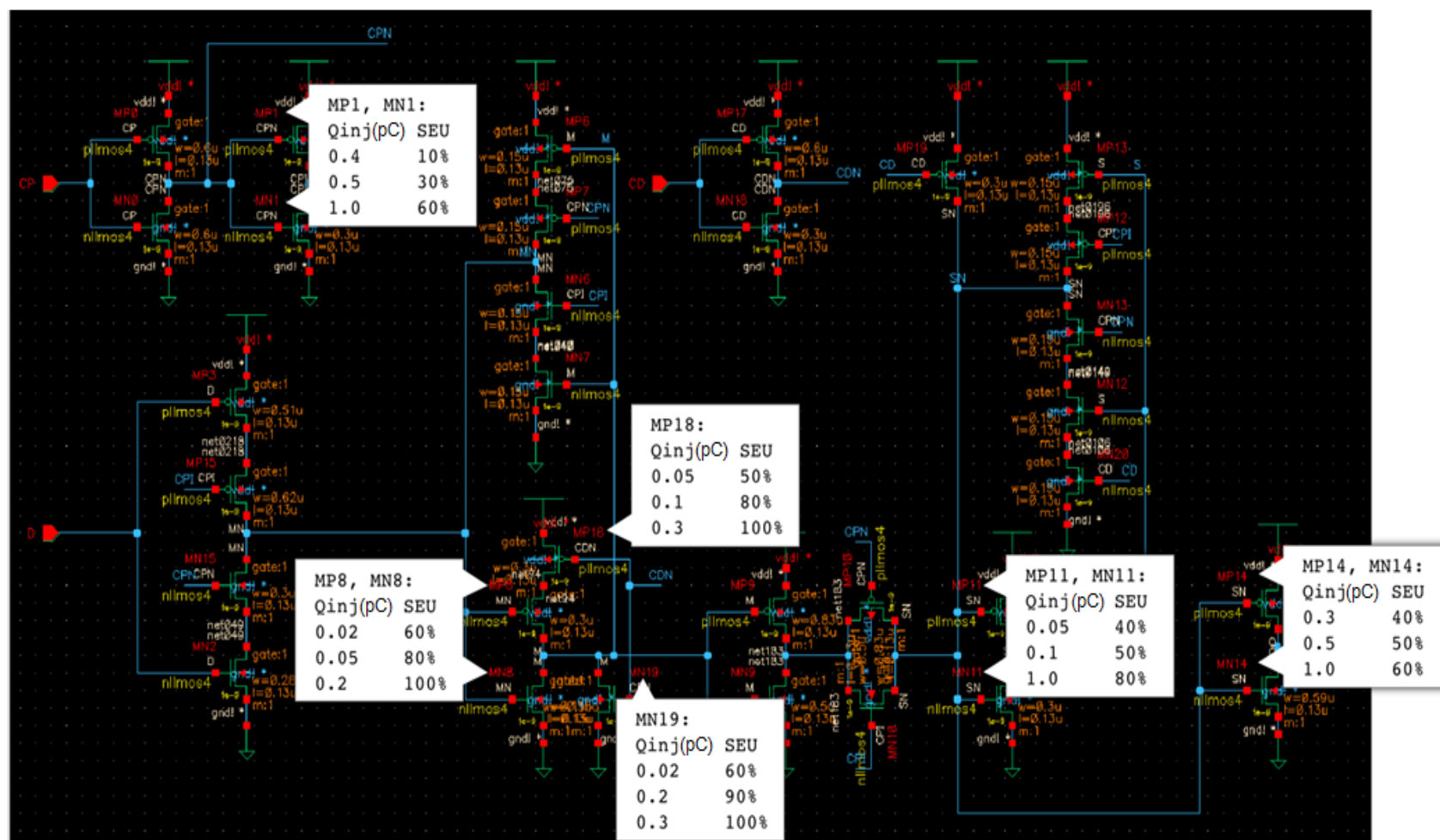D-latch circuit , STMicroelectronics 130 nm



For this particular test, we shot at 10 different instants per period to obtain a sensitivity percentage: for example if 7 impacts generate a SEU we have a sensitivity of 70%