

Stabilization and Protection of the Shunt-LDO regulator for the HL-LHC pixel detector upgrades


TWEPP 2019 – Santiago de Compostela

05.09.2019



Jeremias Kampkötter

Introduction

- Serial powering is necessary for the supply of the pixel sensors in the Atlas and CMS experiment
- A voltage regulator is integrated in the front-end chips and generates a constant supply voltage from a constant supply current
- To stabilize the LDO regulator a new compensation scheme is introduced
- In order to generate precisely defined reference values for the regulator, the new revised Bandgap scheme is presented
- A number of new circuits have been added to ensure robustness and security

 

Parallel vs. Serial Powering

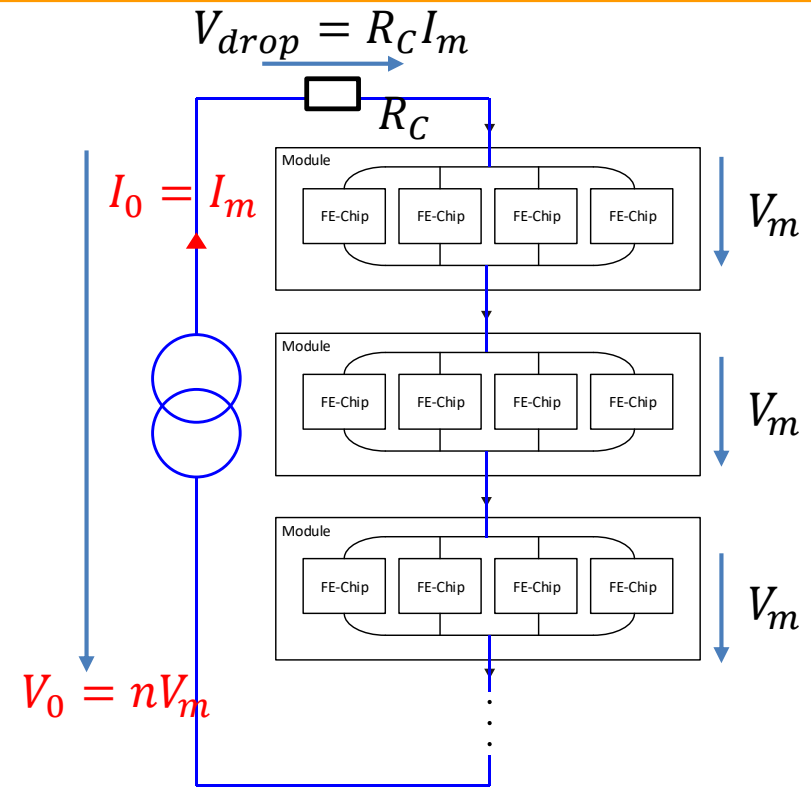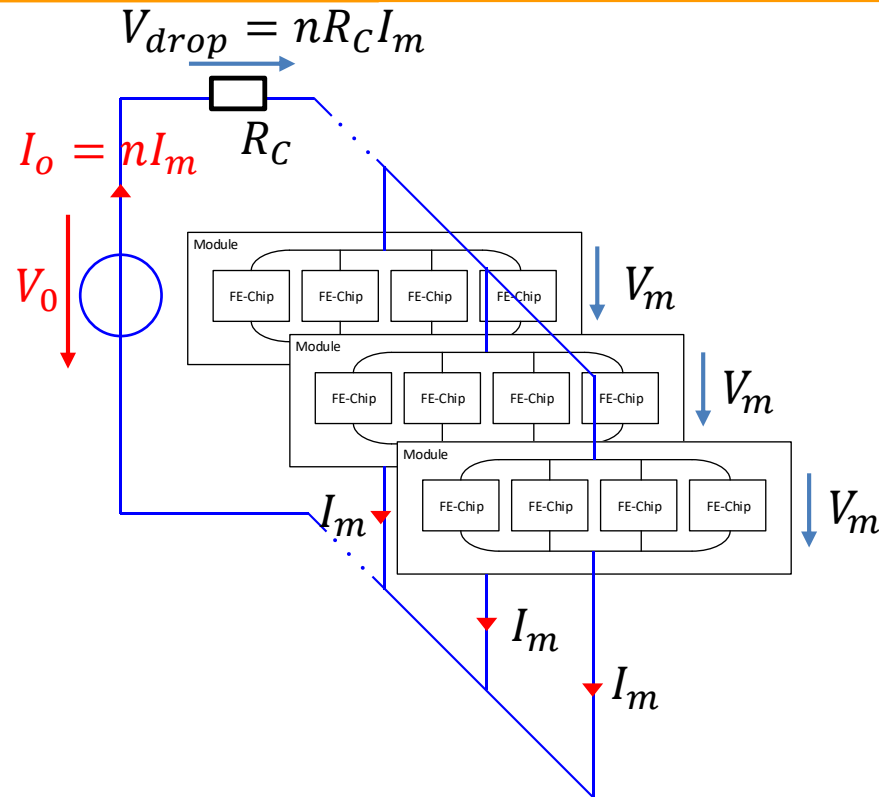

- Modules are connected in parallel and powered by a constant voltage source
- Total supply current scales with the number of modules


$$\eta = \frac{1}{1 + n \frac{R_C I_m}{V_m}}$$

- Modules are connected in series chain and powered by a constant current source
- Total supply current is defined by the highest feasible load current of a single module

$$\eta = \frac{1}{1 + \frac{R_C I_m}{n V_m}}$$



Shunt-LDO Regulator

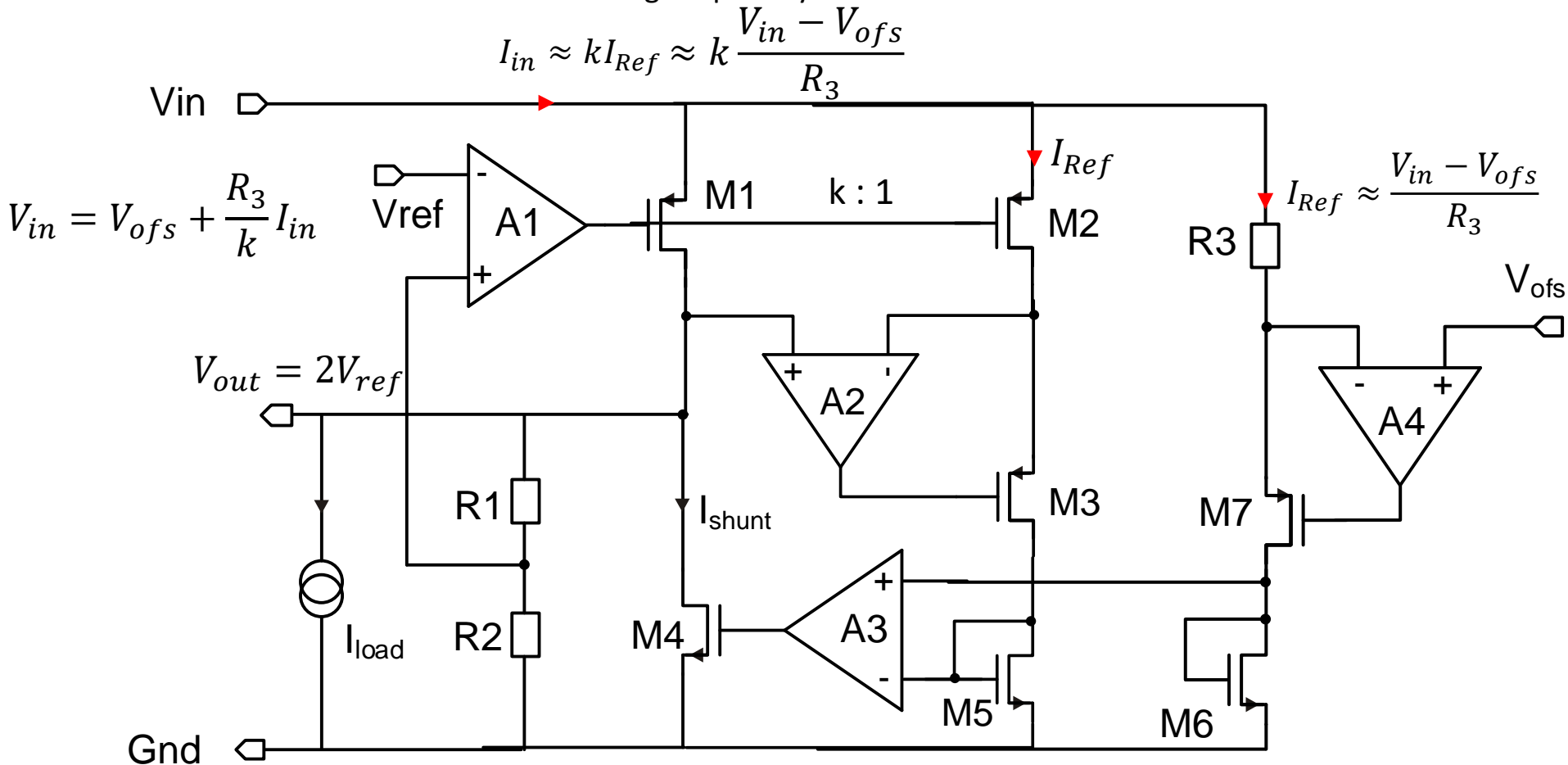- The Shunt-LDO regulator is a combination of a low-drop-out (LDO) voltage regulator and a shunt regulator
 - Two control loops: 1) constant output voltage 2) constant current flow through the regulator
- Core Transistors are used due to high radiation resistance → carry voltages up to 1.32V
 - Transistors are cascoded for overvoltage capability




I/V characteristics of the Shunt-LDO

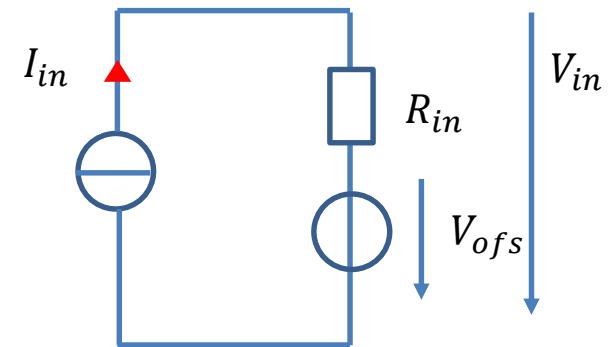 - Shunt-LDO is equivalent to a resistor in series with a voltage source
- Slope is defined by input impedance $r_{in} = \frac{R_3}{k}$
- Output voltage is reached at the point where the amplifier is saturated and the reference voltage is achieved
- The slope of the input voltage ensures a uniform current distribution to parallel regulators



Effect of the Double Zero

 

- Amplitude response of output pole (blue curve), zero (green curve) and both (red curve)
- First the pole is dominant and at high frequencies the zero
 - Zero dominates at the intersection point with the pole

Determination of the Zeros Frequency


- The frequency of the zero is determined at the intersection with the output pole

$$\omega_z = \frac{1}{\sqrt{2}C_{out}R_{LG}} \sqrt{-1 + \sqrt{1 + \frac{R_{LG}^4 g_m^2 C_{out}^2}{g_{ms}^2 R_o^2 C_s^2 R_x^2}}}$$


$$R_{LG} = R_{load} || (R_1 + R_2) || r_{DS}$$

$$R_x = R_1 || R_2$$

$$R_o = r_{DS2} || R_s$$

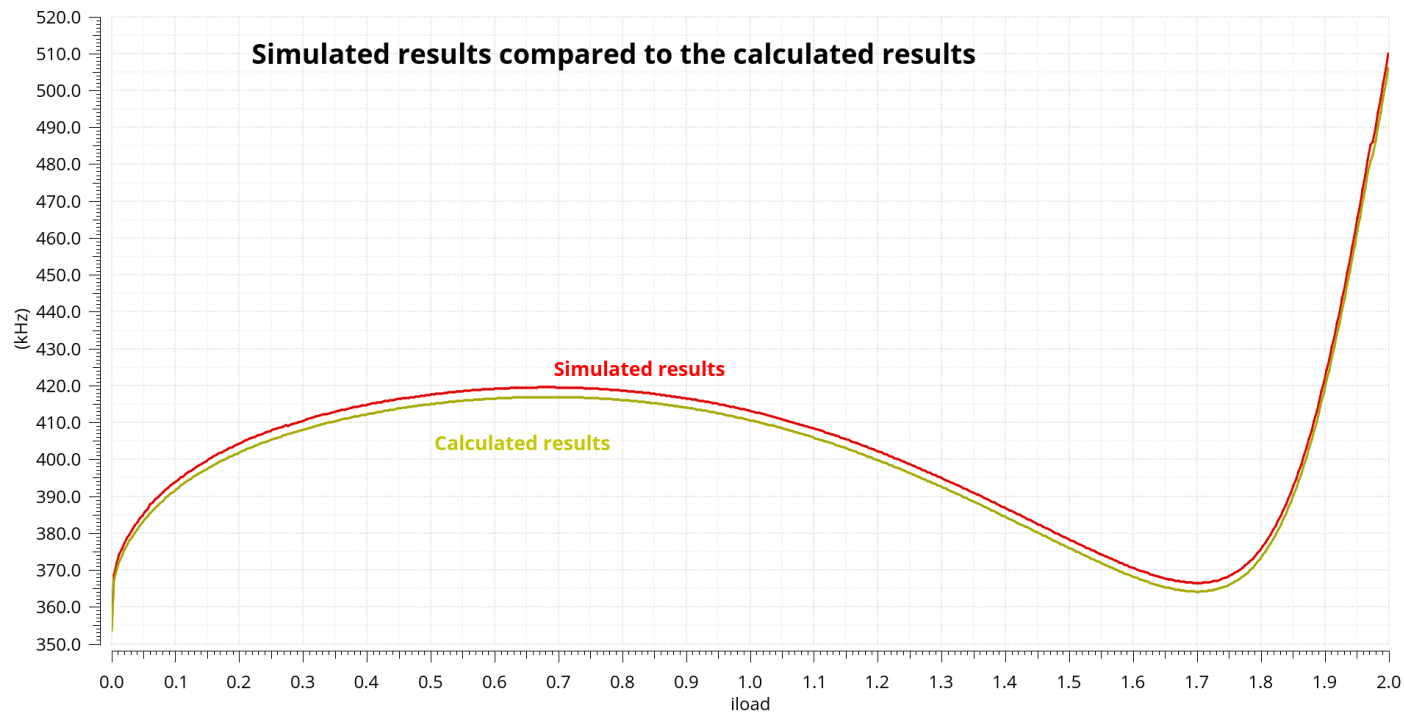


 Activation of the Under Shunt Protection Circuit



Overvoltage Protection (OVP)

 
- Protects the regulator from overvoltage
- During an overvoltage situation, the excess supply current is drawn to ground
 - Implemented with a shunt regulator
 - The OVP becomes active if the input voltage exceeds 2V
- Shunt-LDO is connected in parallel to the overvoltage protection



High & Low Power Mode


- The regulator operate with low supply currents during the installation phase
 - Since the cooling system is inactive
- Possibility to switch between two Offset voltages
 - High Power Mode is active in the nominal case
 - E.g. $V_{ofs} = 800\text{mV}$
 - Low Power Mode
 - E.g. V_{ofs} is increased to 1.3V
- Start-up circuit is integrated to ensure reliable start-up at small supply currents

Offset Voltage Configuration Capability

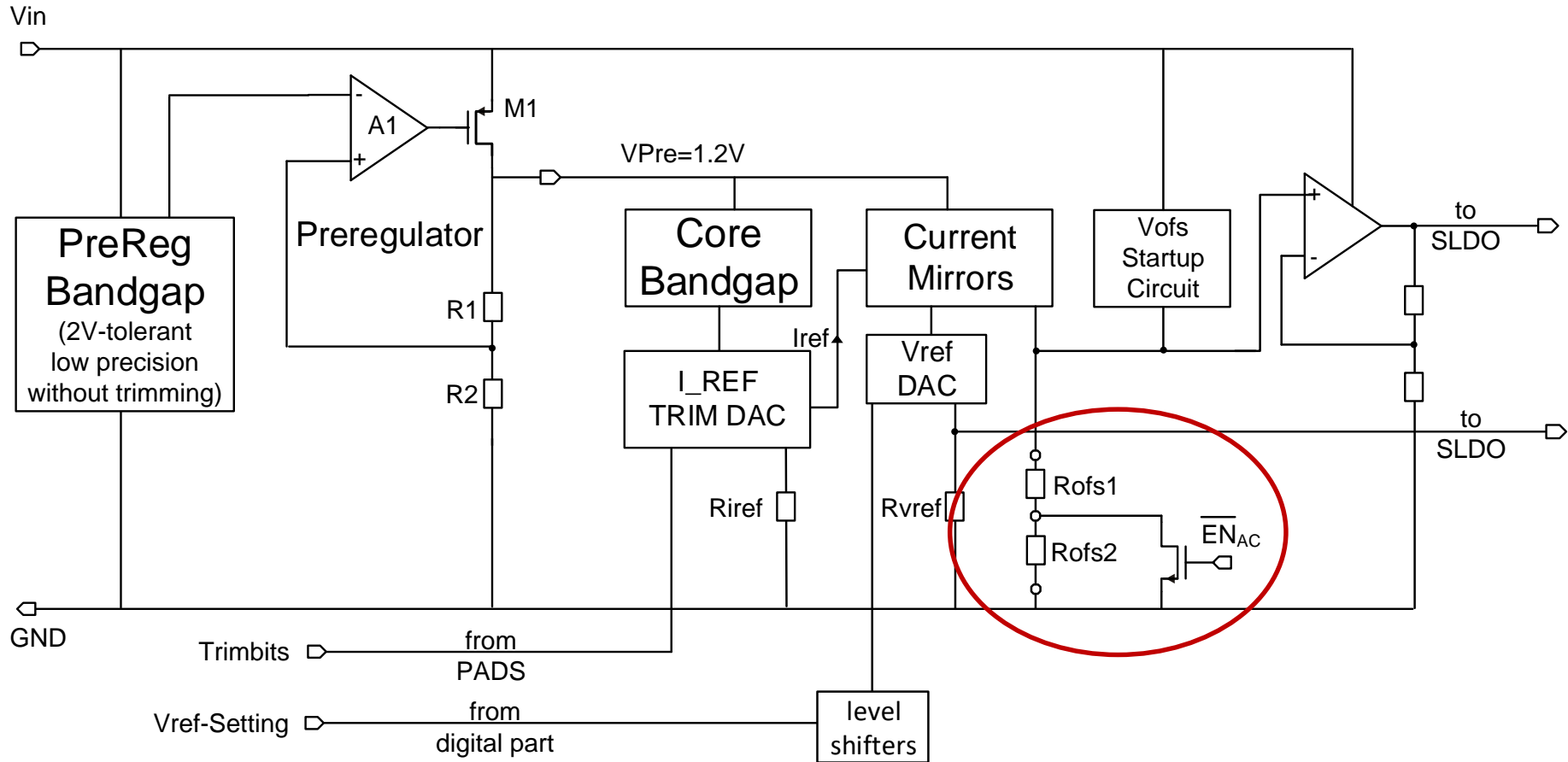


Rectification Circuit

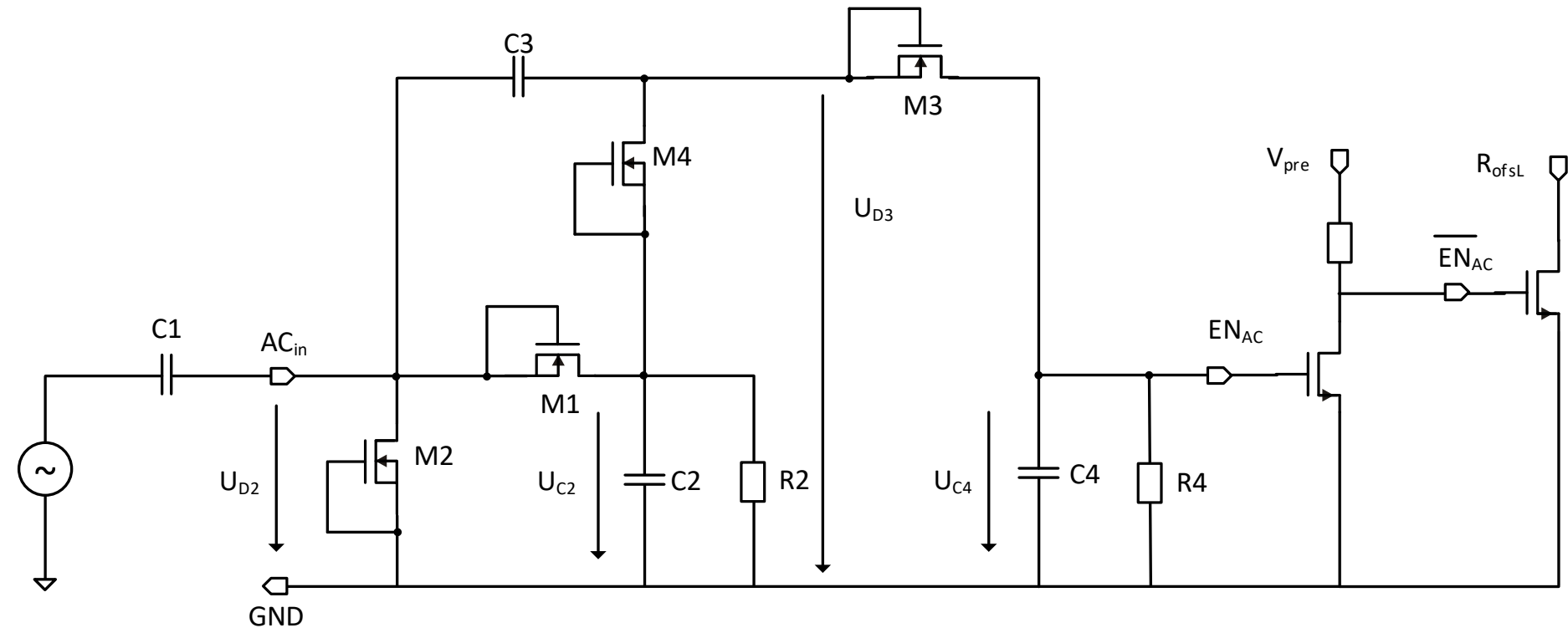
- Inverted rectified signal controls the transistor to switch into the Low Power Mode
- AC signal applied before power on
 - Two-stage rectifier circuit
- Rectifier generates supply voltage for a small digital configuration circuit



Activation of the Low Power Mode

 

Comparison High & Low Power Mode

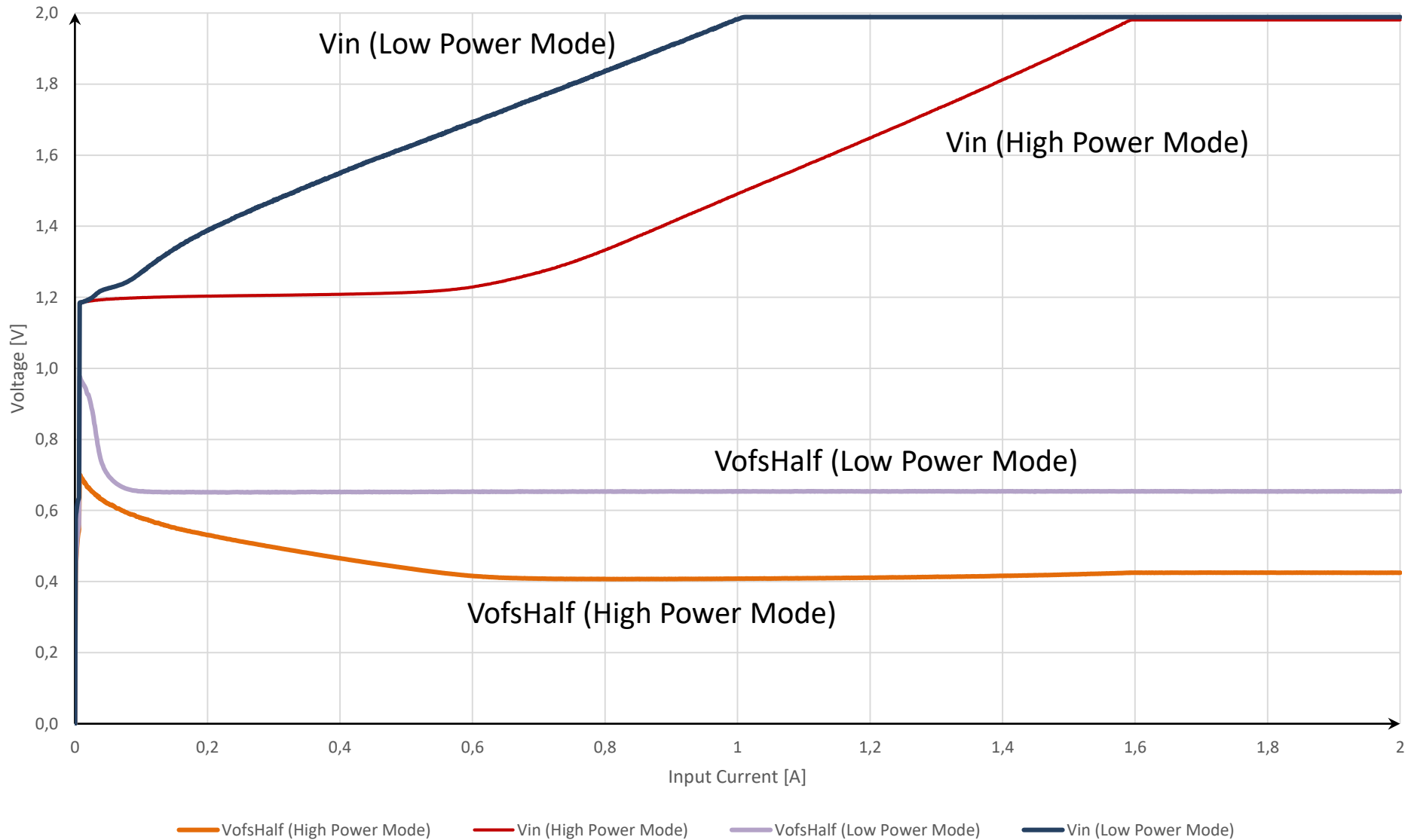


- Conclusion:
 - New compensation scheme stabilizes the LDO regardless of large on-chip capacitance
 - Accurate reference values due to new bandgap scheme
 - Improved PSRR
 - Trimming options
 - Protection circuits were integrated to protect the circuit for overload and overvoltage scenarios
 - The Low Power Mode was integrated for test purposes during the installation phase


Appendix

Startup Circuit

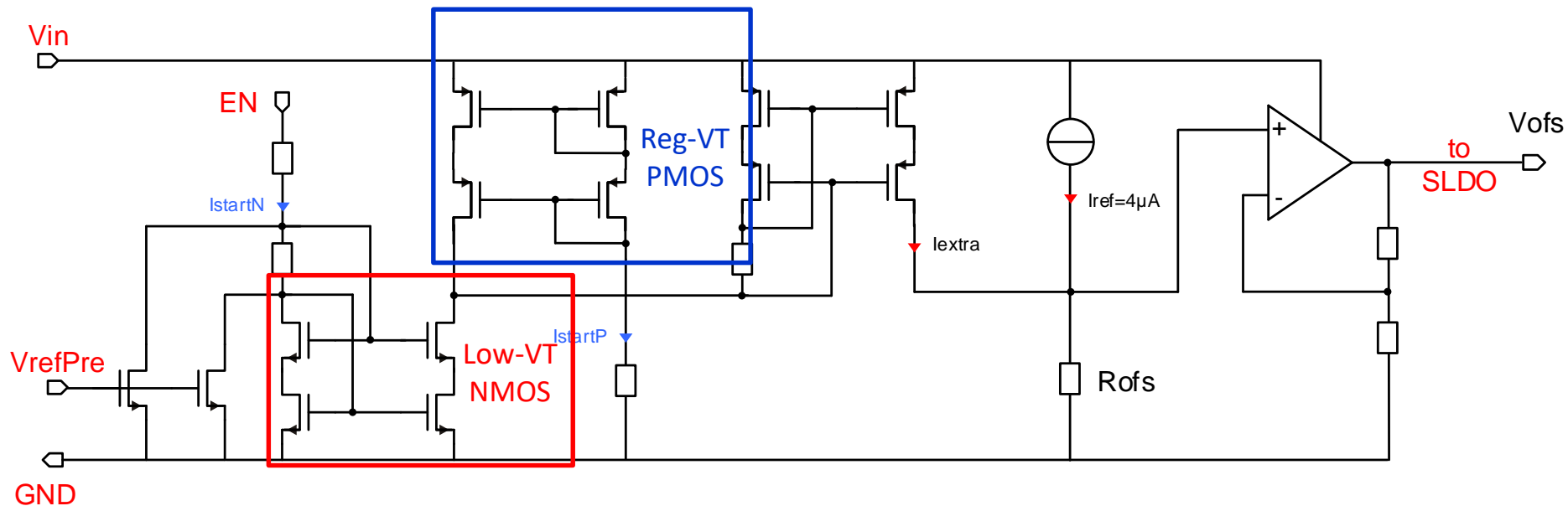- Improves start-up behaviour
 - Vofs & Vref follows Vin
- wide-swing cascode current mirror with low-VT NMOS transistors draw current first
- standard cascode current mirror with regular-VT PMOS transistors drain current later
 - difference between current is injected to R_{ofs}




Bandgap Circuit

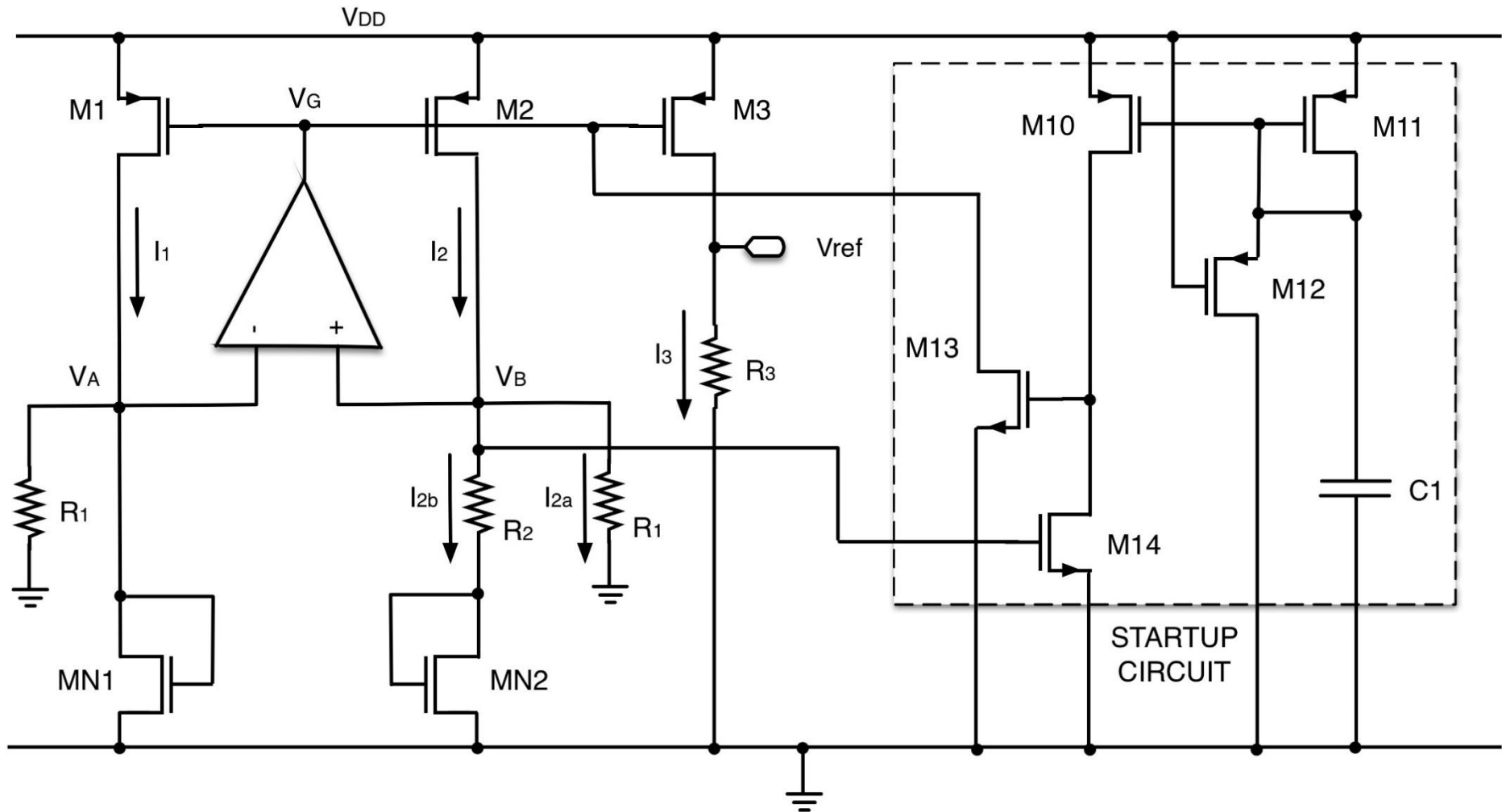

- Gianluca Traversi: *Characterization of bandgap reference circuits designed for high energy physics applications*

LPM Alvaro Circuit (LPM Signal Generation)

- I_{in} is measured with a current mirror of the LDO transistor + a resistor.
- If the I_{in} is below the threshold value, a current source is enabled and starts to charge a capacitor (external big capacitor).
- If this capacitor reaches the trigger voltage of the Schmitt trigger, it changes LPM_SIGNAL to HIGH, and LPM is enabled.
- **In case of High Power Mode**, the I_{in} is going to surpass $I_{threshold}$ very fast and C1 is not going to be charged at all (in this case this circuit is **almost “transparent” from outside point of view**, without any nasty transient)
- C charging time should be adjusted so that it is slower than the normal start-up time.

 

- By Alvaro Pradas

Comparison High & Low Power Mode (without activating the Start-up Circuit)

