

Serial Powering for the Tracker Phase-2 Upgrade

Dominik Koukola on behalf of the CMS Tracker Group



Lopud Island, Croatia October 13-18, 2019

Outline


Serial powering scheme

- Introduction and motivation
- Shunt-LDO regulator and RD53A readout chip
- System issues

Recent system tests and developments

- Serial powering chains with RD53A Quad modules

LHC Plan

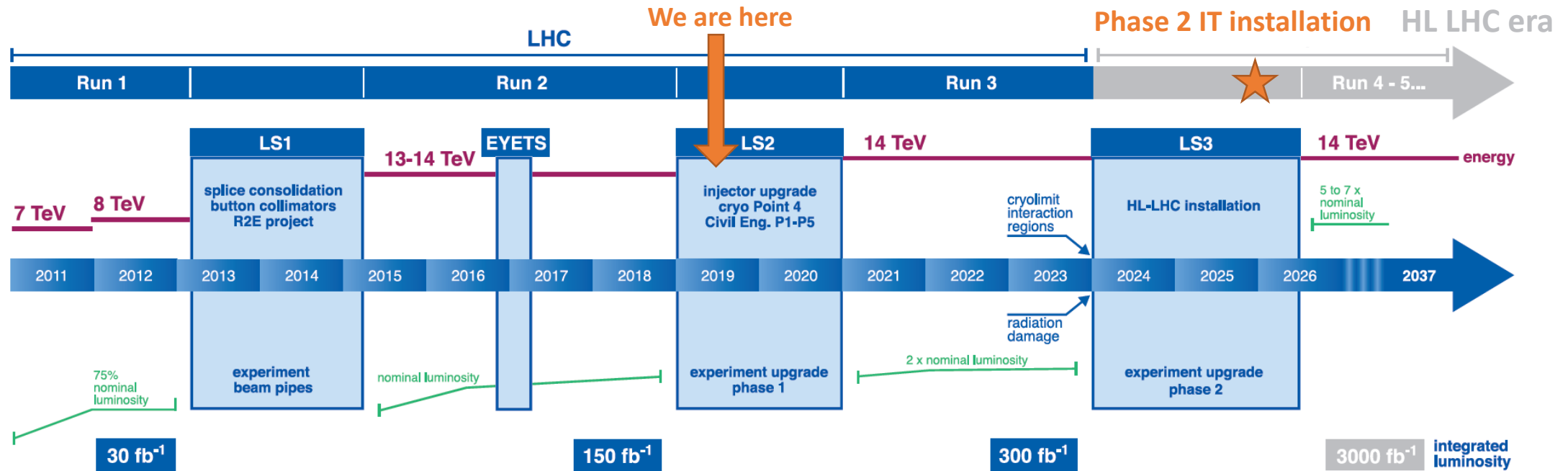

- ATLAS and CMS will upgrade their Inner Trackers for HL-LHC
- Both will use **Serial Powering** to power the pixel readout chips
=> Never been used in HEP experiments
- Presentation will give a CMS Inner Tracker biased view on Serial Powering
 - Largely also applicable for ATLAS Pixel ITk

Power related challenges for Phase 2 IT

HL LHC era will bring increased requirements for the Inner Tracker:

❑ High radiation levels up to:

- Fluence of $2.3 \times 10^{16} \text{ n}_{\text{eq}} \text{ cm}^{-2}$
- Total ionizing dose of 1.25 Grad

=> Radiation hard design

❑ Increased latency, granularity and hit rate:

- Big buffers, many pixels, high bandwidth


=> High supply current (~2A / chip)

❑ Minimize material budget for good tracking performance:

- Light cables and mechanical structures
- Tight space constraints
- CO₂ cooling


=> Compact and low mass design

Why serial powering?

 


Direct parallel powering

 - Requires many thick cables to maintain voltage



Parallel powering with DCDC converters

 - Not sufficiently radiation hard
- Space limitations



Serial powering


- Fewer ($n \approx 8$ times) and lighter cables

CMS Inner Tracker Phase 2 Overview

More in talk on “CMS Inner Tracker Upgrade ”
by Panja Luuka Tuesday 09:00


Serial powering requirements:

 - On-detector power $\sim 50\text{kW}$
- Supply current $\sim 3\text{kA}$
- 500 serial powering chains
- 3900 modules (Double and Quad modules)




Serial powering scheme

Serial powering scheme

 


- Serial chain is powered with a **constant input current**
- Up to 12 modules are connected in series in a **serial chain**
 - Modules have **different local grounds**
- Current based powering system => Insensitive to voltage drops on cables


Serial powering scheme

 

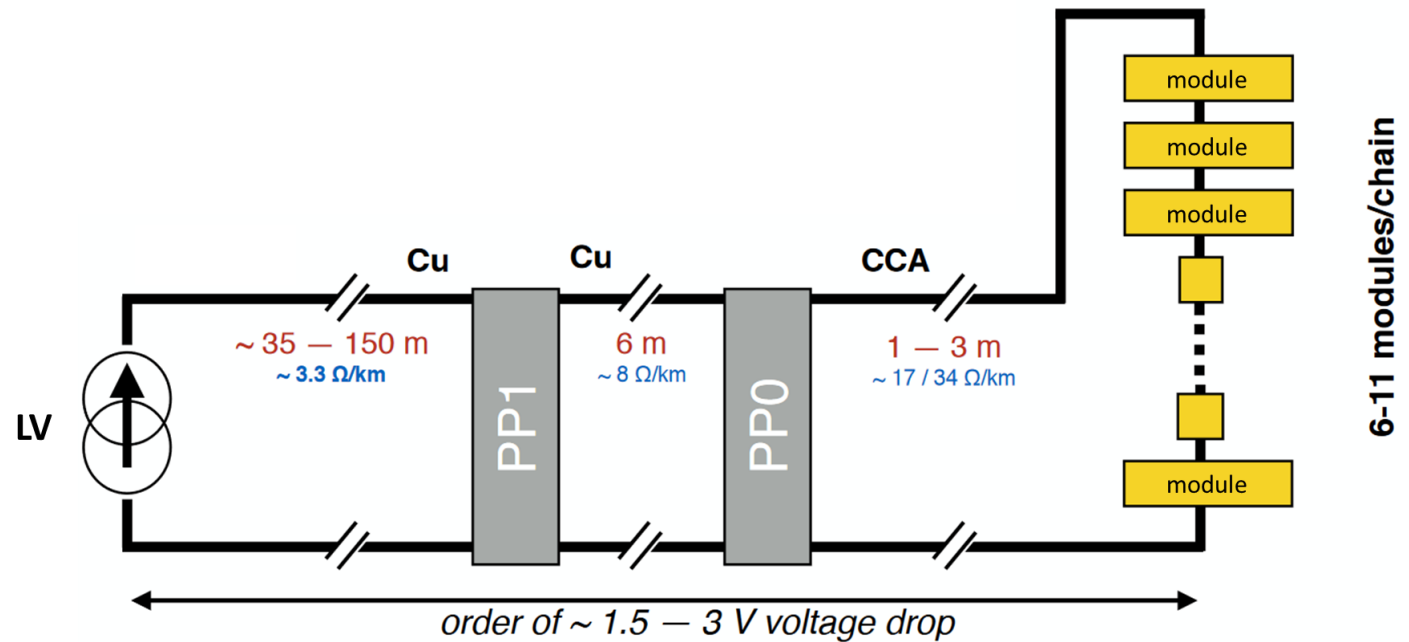
- Serial chain is powered with a **constant input current**
- Up to 12 modules are connected in series in a **serial chain**
 - Modules have **different local grounds**
- Current based powering system => Insensitive to voltage drops on cables
- No auxiliary on-detector electronics needed for serial powering
 - Only cabling between power supply and readout chips



Serial powering scheme

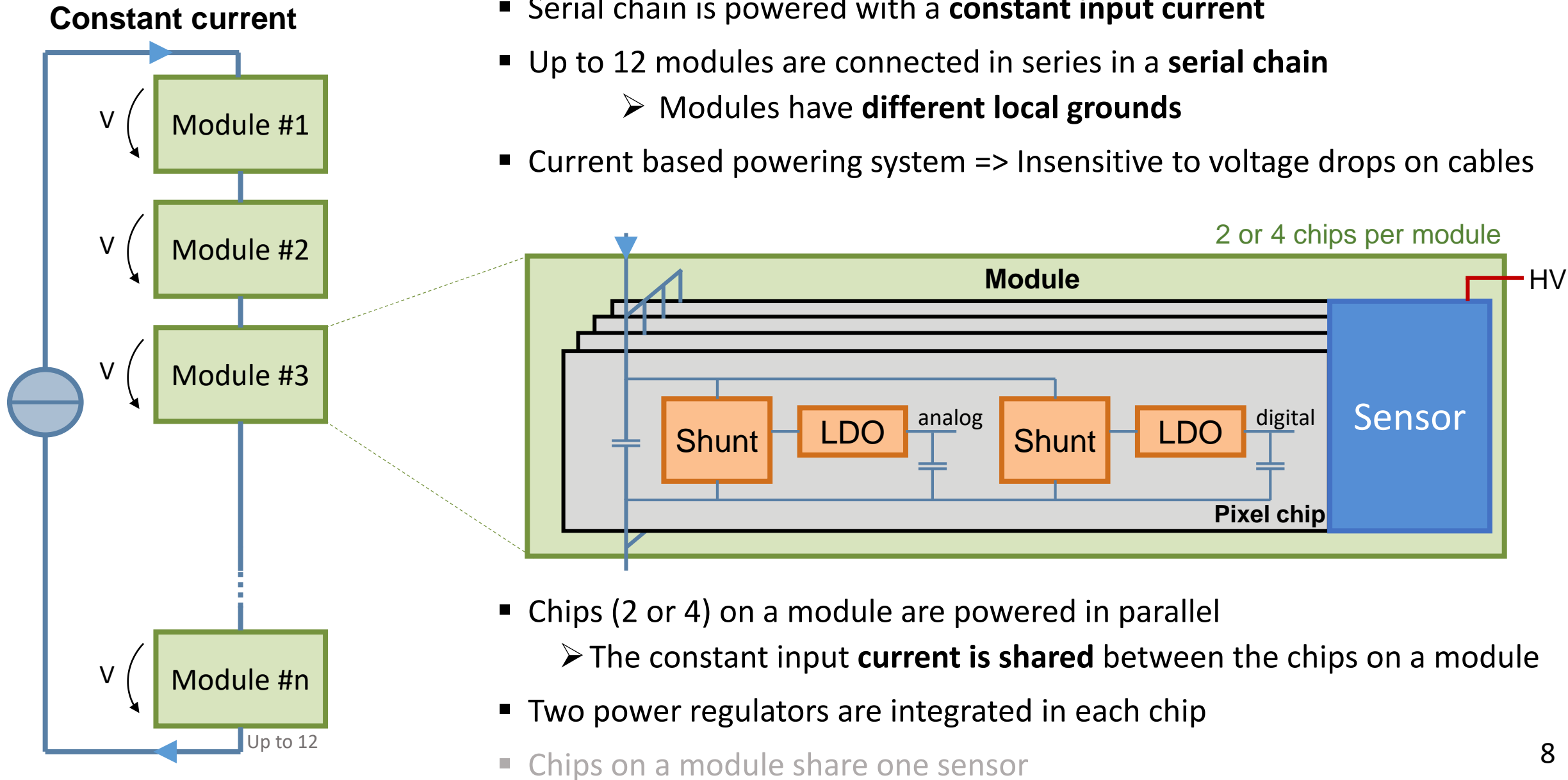


High voltage bias for Sensors

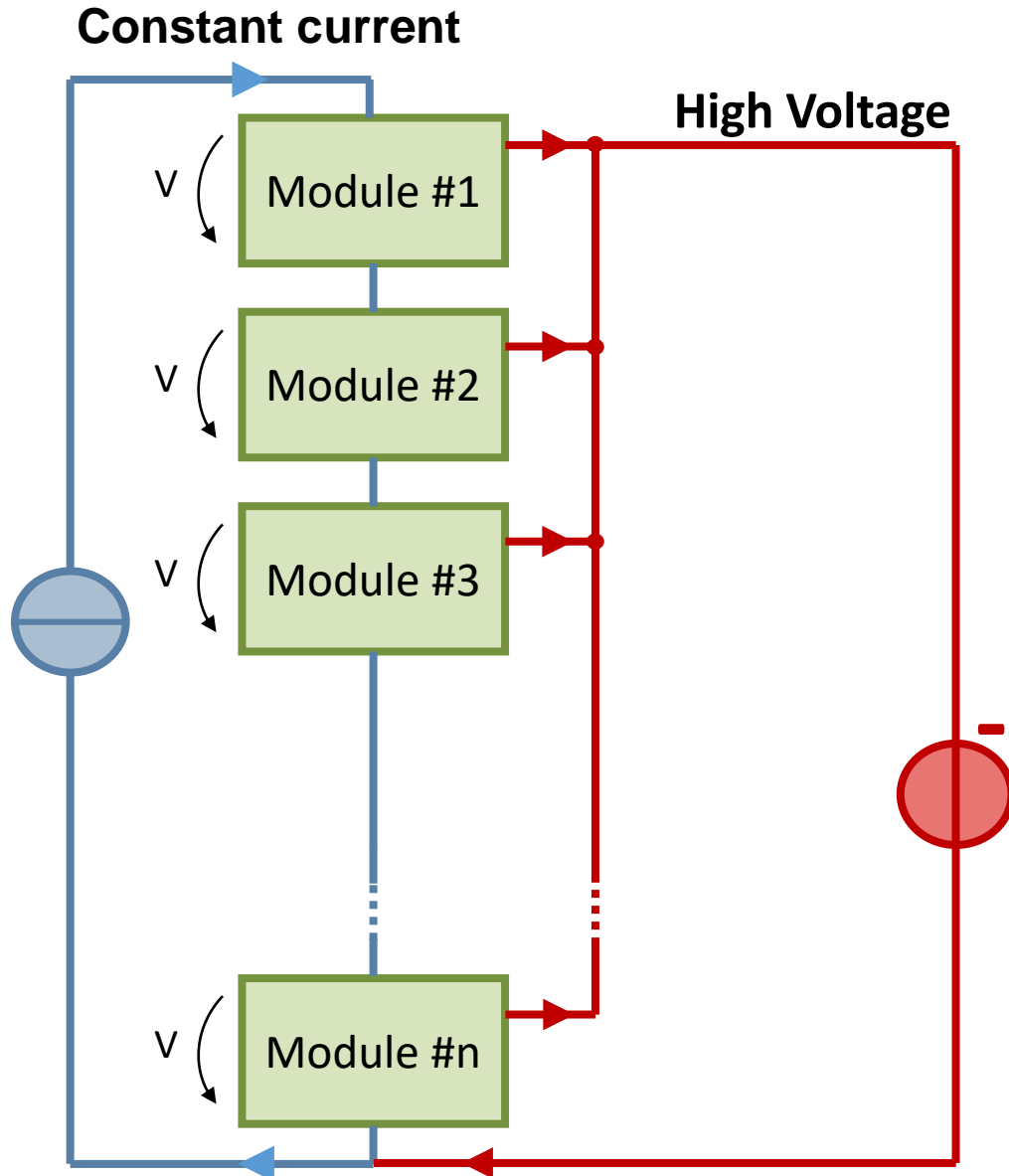

- High voltage is **provided in parallel**
 - Baseline choice is **one parallel HV supply line** per serial chain
- HV return path is through the serial chain
- Modules have different local grounds
 - Sensors see different HV due to different ground potential
 - **Up to 20V differences** in sensor HV in a chain
 - => Not problematic for planar sensors
 - => For 3D sensors higher HV granularity foreseen
 - **Sensor forward biasing possible when HV off and LV on**
 - => Several solutions to avoid this

On-detector readout electronics

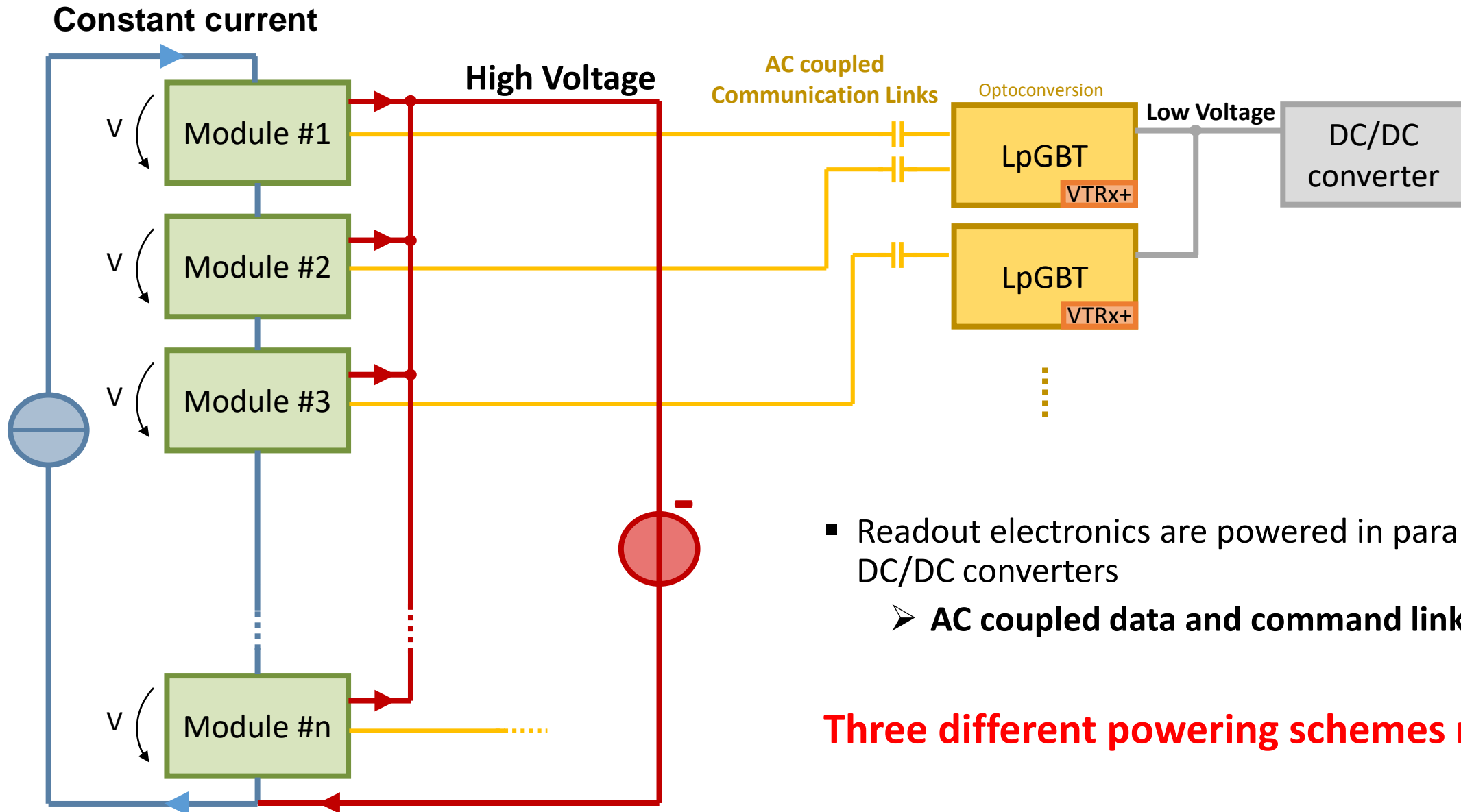


- Readout electronics are powered in parallel with DC/DC converters
 - AC coupled data and command links required

Shunt-LDO regulator & RD53A readout chip

Overview of recent chips with Shunt-LDO regulators

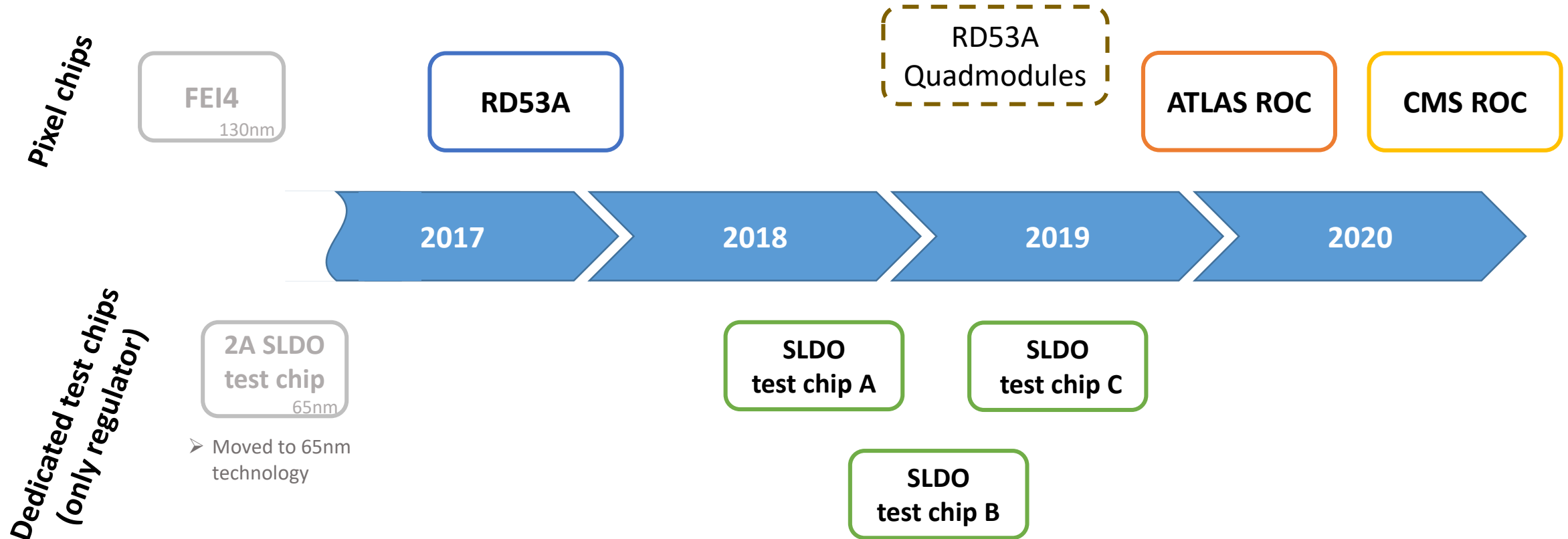- Date corresponds to the first (expected) availability




Improved performance (Startup, voltage accuracy, ..)
New features (Overvoltage/overload protection, ..)

Shunt-LDO regulator

“Constant current to constant voltage converter”

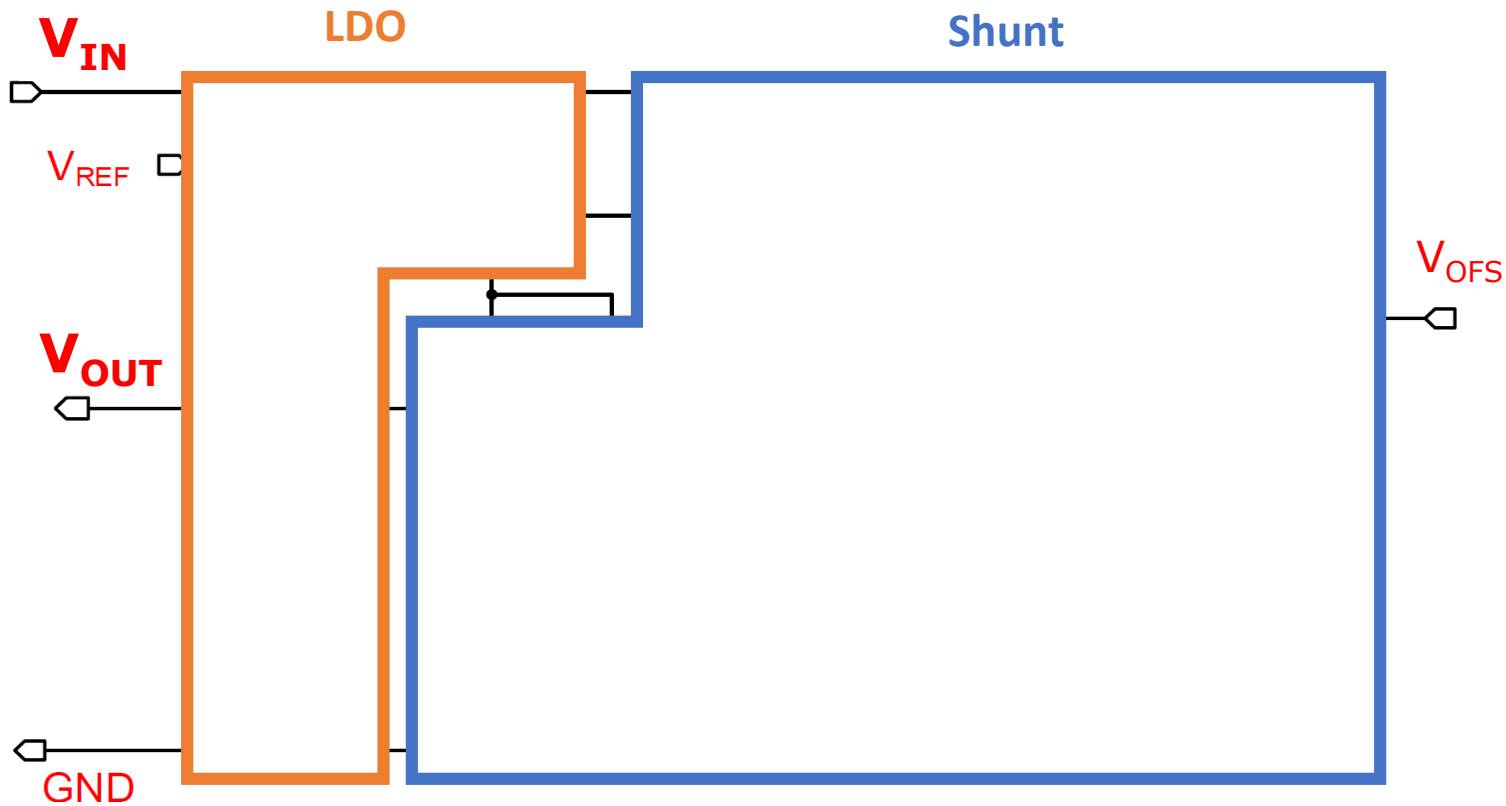
- Combines two functionalities: **Shunt** + **LDO**



Shunt-LDO regulator



Shunt part:

 - Regulates input voltage => resistive behavior
- Shunts not used current to ground



Relationships

 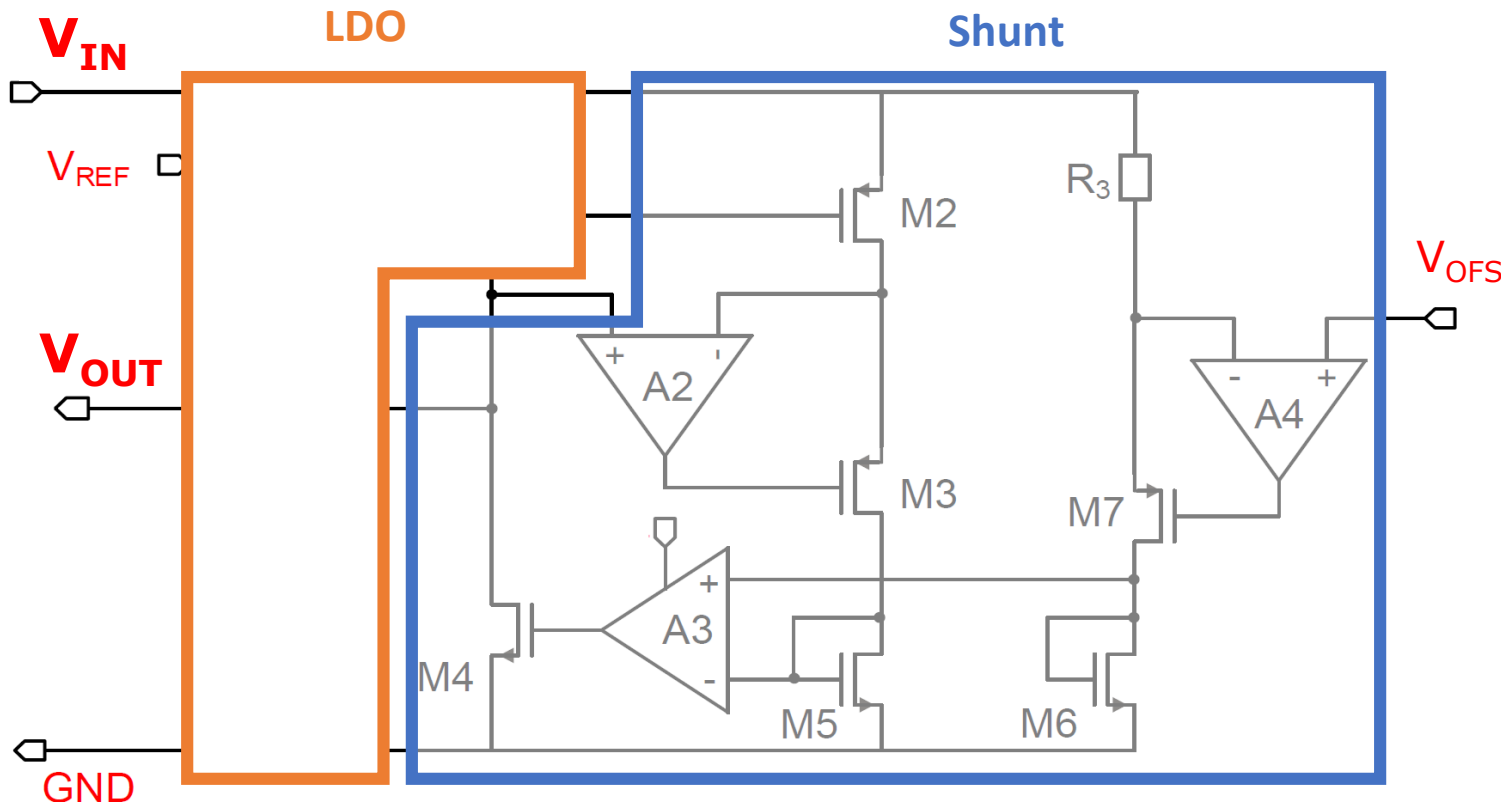
$$V_{in} = V_{ofs} + \frac{R_3}{1000} * I_{in}$$



Shunt-LDO regulator

LDO part:

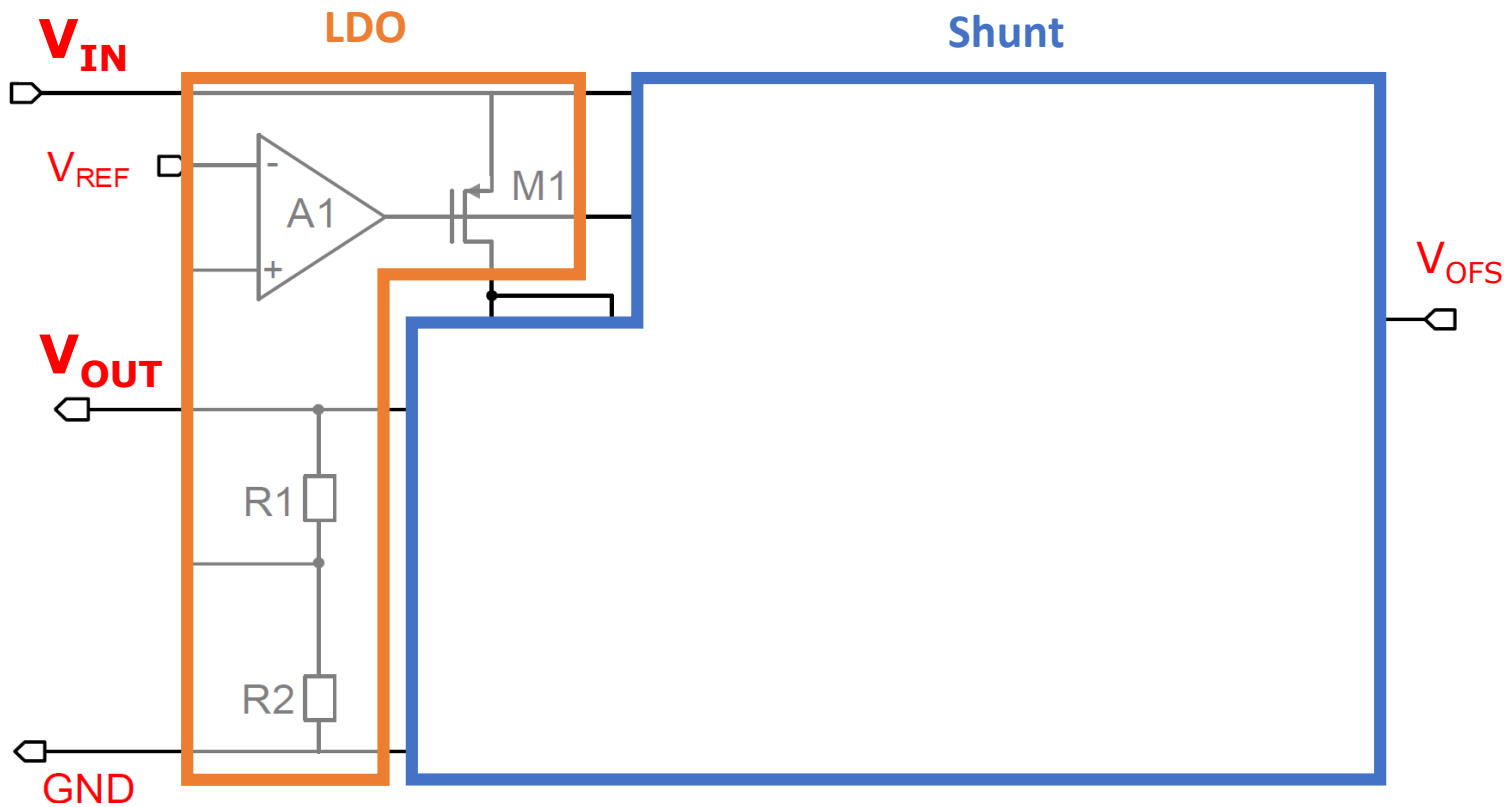
- Provides constant output voltage
- Requires 0.2 V drop out voltage $\Rightarrow V_{in} > V_{out} + 0.2V$



Relationships


$$V_{in} = V_{ofs} + \frac{R3}{1000} * I_{in}$$

$$V_{out} = 2 * V_{ref}$$

 

Shunt-LDO regulator

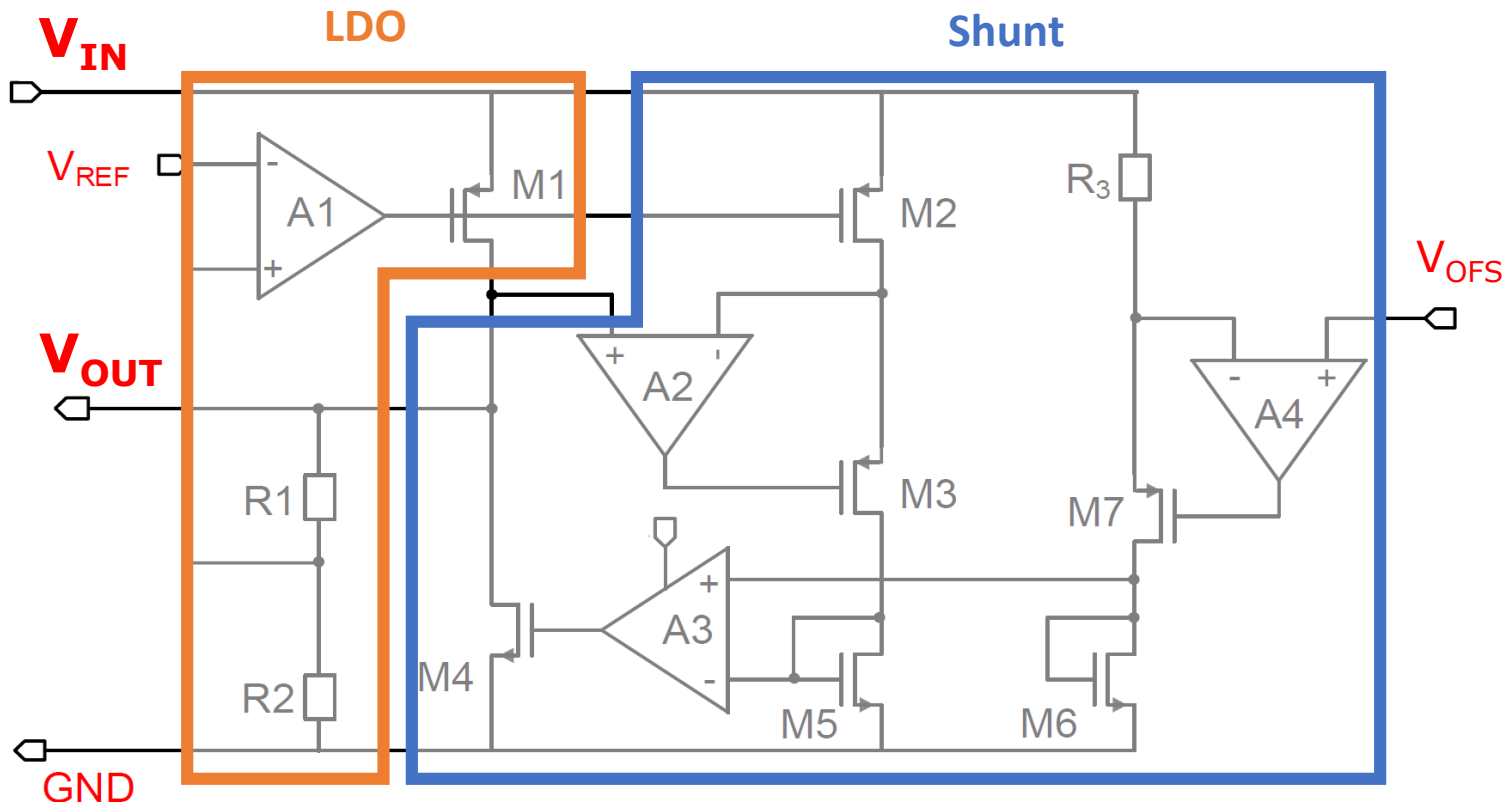
- Resistive input behavior
- Provides constant voltage to the chip
- Input impedance, Vofs and Vref are **configurable**



Relationships

$$V_{in} = V_{ofs} + \frac{R3}{1000} * I_{in}$$

$$V_{out} = 2 * V_{ref}$$

 


RD53A readout chip

Demonstrator pixel readout chip designed by the RD53 collaboration (22 institutes - ATLAS and CMS)


- 400x192 pixels ($50 \times 50 \mu\text{m}^2$ each)
- Three analog front end architectures
- $\frac{1}{2}$ size of final chip $\Rightarrow \sim \frac{1}{2}$ power ($\sim 1\text{A}$)
- 65nm CMOS technology $\Rightarrow 1.2\text{V}$ core voltage
- Radiation hardness $> 500 \text{ Mrad}$



 Final prototype of production chips expected in 2020:





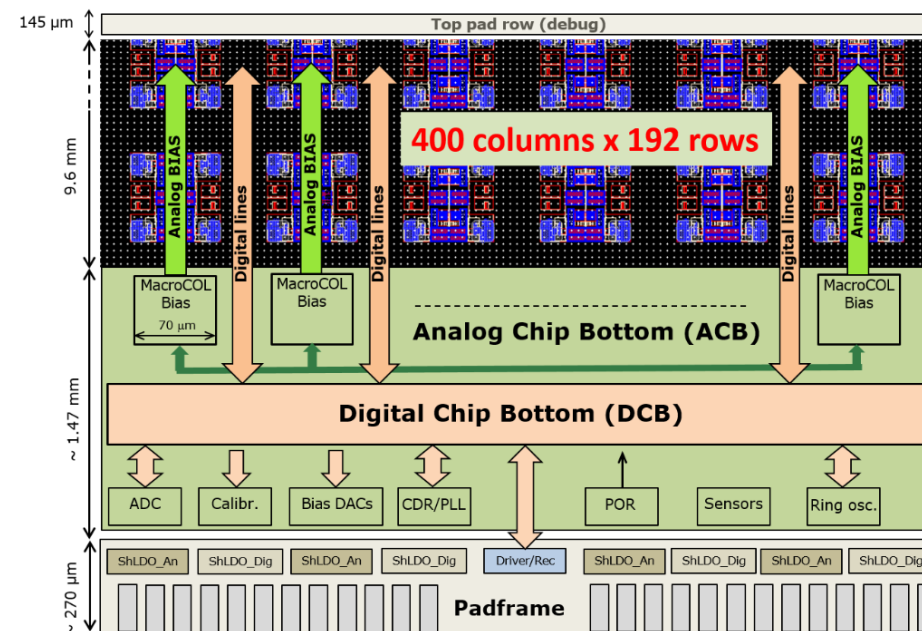More in talk on “RD53 analog front-end processors”
by Luigi Gaioni Tuesday 15:00




RD53A readout chip - Power

- ½ size of final chip $\Rightarrow \sim \frac{1}{2}$ power ($\sim 1\text{A}$)
- 65nm CMOS technology $\Rightarrow 1.2\text{V}$ core voltage
- **Two power domains** \Rightarrow one for **digital**, one for **analog**
 - To decouple noisy digital from sensitive analog
- **Two Shunt-LDO regulator integrated** (one per domain)
 - Dimensioned for production chip
 - Can take 2A each \Rightarrow more than twice the expected load of final chip
 - Maximum input voltage 2V
- **Three powering modes:**
 - Shunt-LDO mode (nominal mode)
 - LDO mode (Shunt disabled)
 - Direct (Shunt-LDO bypassed)

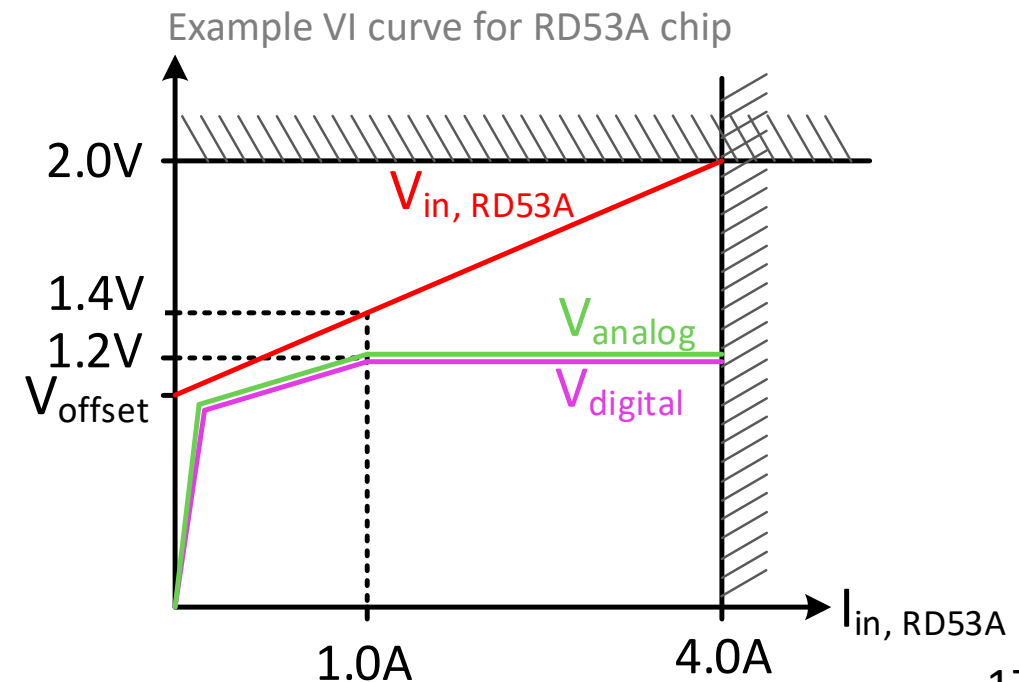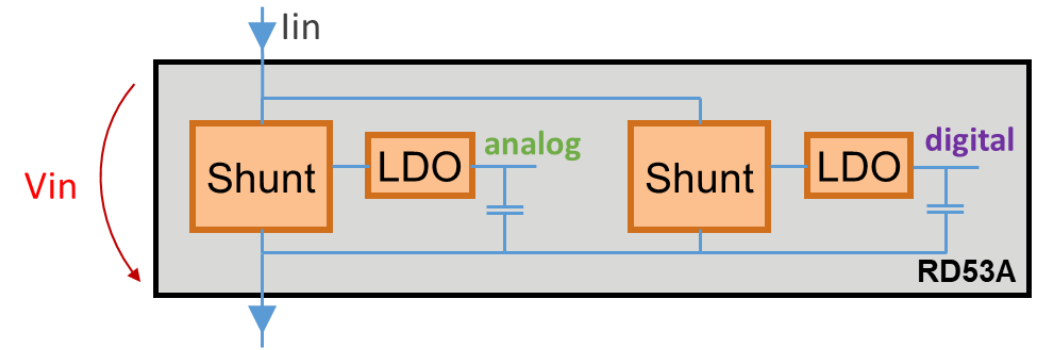

System issues

Constant supply current

 

Example current consumption of one readout chip

- Need to **provide enough constant current** for the chip to operate:

$$I_{constant} = I_{Max\ chip} + I_{headroom}$$

- **Surplus current is dissipated** in shunt part of regulator => **intrinsically inefficient**
- Load variations on chip are not propagated to power supply => resistive load to power supply
- If more current is drawn than provided (overload), regulator will fall out of regulation
=> Fast transients are filtered by external decoupling capacitors
- **Headroom also needed to cover imbalances in current sharing among parallel chips**


Optimizing the working point

- Optimize choice of: **Current headroom, Input behavior (slope, offset)**
- Goal is to have **power efficient and reliable powering** => compromise between the two

Low headroom


Sufficient current (> max load)
Sufficient voltage (> 1.4V)

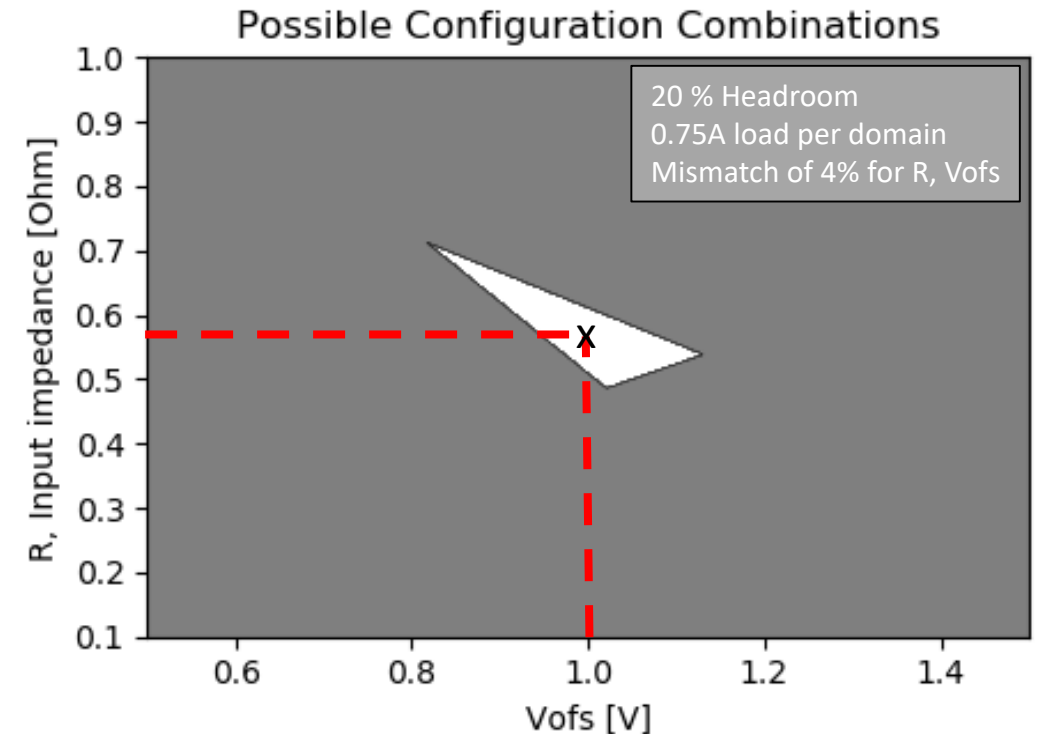- **Mismatches and parasitics need to be taken into account**
- First studies confirm that **20% headroom** is sufficient to cover estimated mismatches




Typical failure cases

Normal operation

 


- Current is shared equally between parallel chips

Open on one chip

 

- Remaining chip has to take **double the current**


Short on one chip

 

- All current goes through shorted chip
- Parallel chips don't receive power anymore


Typical failure cases

Normal operation

 


- Current is shared equally between parallel chips

Open on one chip

 

- Remaining chip has to take **double the current**

Short on one chip

 

- All current goes through shorted chip
- Parallel chips don't receive power anymore

➤ Serial powering chain stays operable when one chip of a module fails




- Shunt-LDO designed to take twice the nominal operation current

➤ Additional protection features have been added since RD53A

=> **Overvoltage & Overload protection**



Hotspots and possible temperature gradient

   - Shunt-LDO is located in **very small area** on the chip bottom
 - Excessive current and drop out voltage are “burned” there
 - **Up to 35% of power** in nominal operation!
- => Highly efficient CO2 cooling allows for this intrinsic inefficiency
- In case of one chip fails the power dissipated in the shunt parts can significantly increase



Recent system tests and developments

RD53A Quad modules

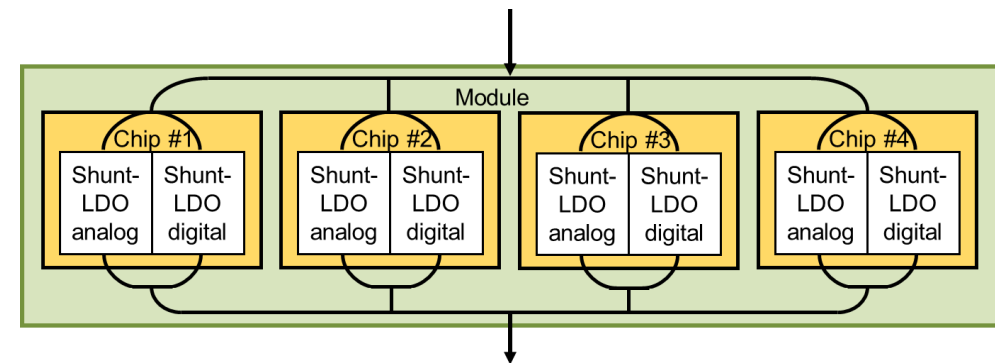 


- First RD53A Quad modules were produced (without sensor so far)
 - Four chips are powered in Shunt-LDO mode in parallel
- Successful operations (powering and readout) of all four chips
 - Including operation of multiple modules in a serial chain


More in poster on “Prototype module construction for the high luminosity upgrade of the CMS pixel detector ”
by Branislav Ristic

Two flavors of serial power chains in CMS

Ladder structure

 

 
TBPX: 1 chain for 2 consecutive ladders in Phi



Disk structure



TFPX/TEPX: 1 chain per ring

 

Prototyping detector-like structures for electrical tests


Ladder structure

Up to 5 modules in series





Disk structure

4 modules in series

 


- Electrical connections similar to final detector
- Aluminum structure with water cooling pipe inside
 - Cooling is essential: ~ 10 W per module are dissipated

  Measurements with Alu Power Flex for Disks



Picture with thermal camera

 

- Started electrical tests with disk structure
- Want to study RD53A power performance in detector like setup
- Demonstrate full chain operation (power + optical readout)

Conclusion

- Serial powering concept is **well established**
- Active R&D communities in ATLAS, CMS and RD53
 - Demonstrated **robust performance** in tests and simulations
 - Many **improvements** in Shunt-LDO regulator performance since RD53A
- System developments and tests are ongoing
 - Basic tests with **RD53A Quad modules** including chain operation were successful
 - Started tests with **detector like structures** for ladder and disk geometries
- Future challenges are still ahead
 - **Ensure efficient current sharing**
 - **Optimization** of serial powering parameters (working point, headroom)



Backup

Possible sensor forward bias issue

Setting a work point for the Shunt-LDO



Shunt-LDO evaluation

- Irradiation campaign
- Overvoltage protection
- Overload protection


Serial Powering system tests with RD53A chips

Possible sensor forward bias when HV off and LV on

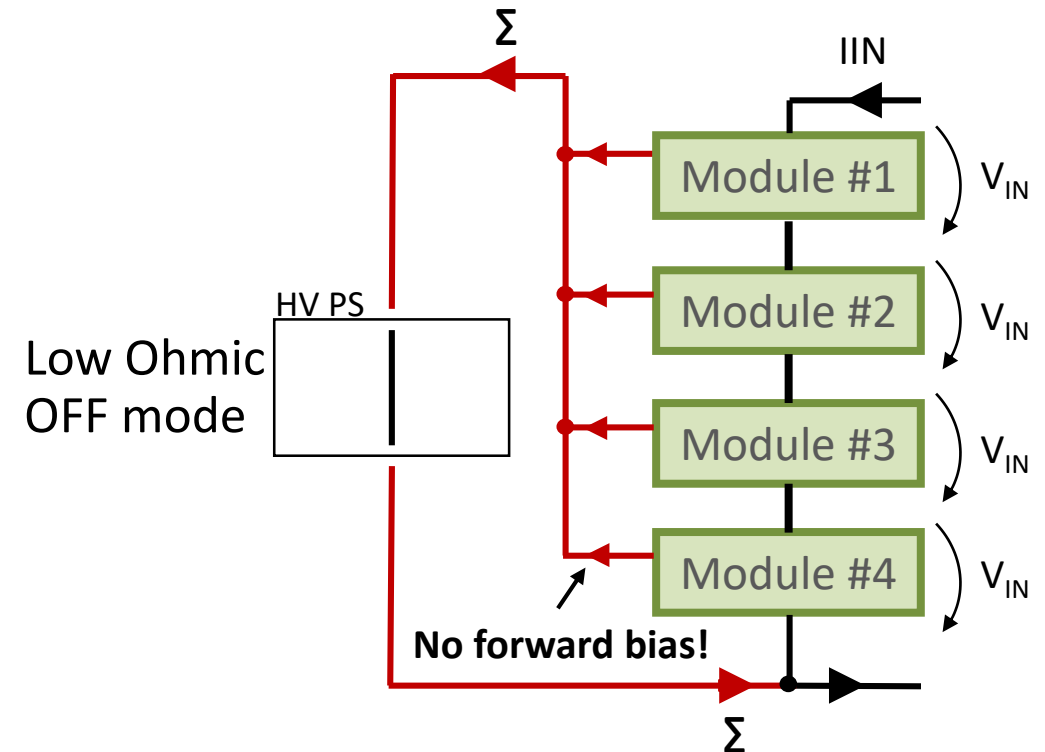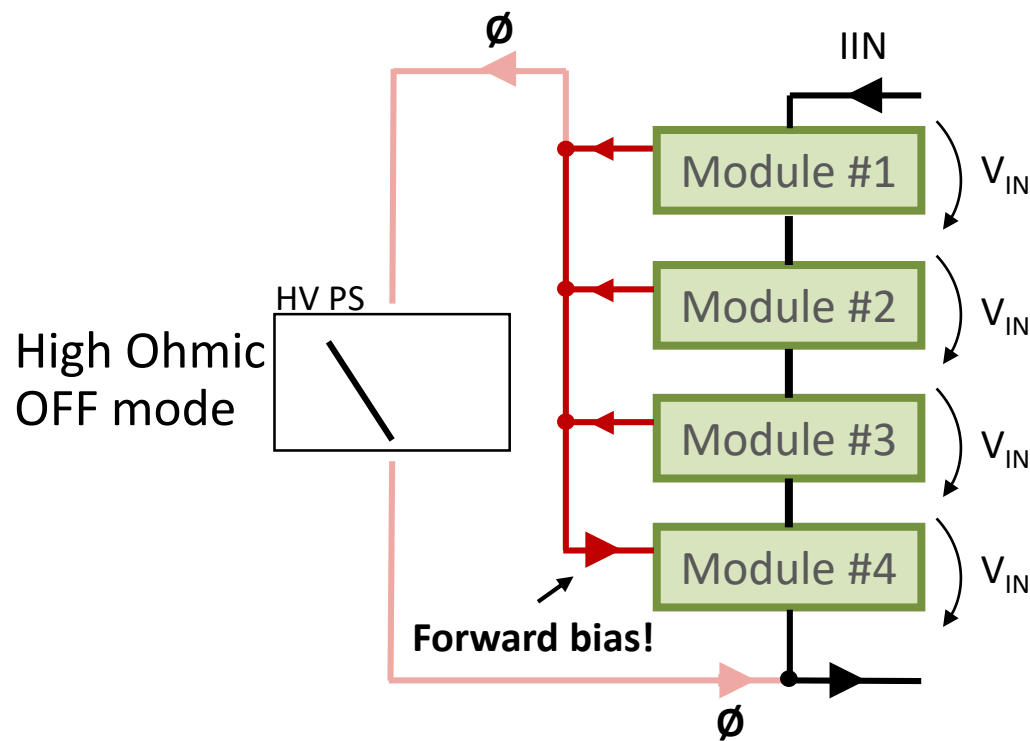- Can generate **forward bias** of sensors when HV off and LV on
- Different local ground on each module \Rightarrow HV OFF is not 0V on sensor when LV on
 \Rightarrow Biased sensors and leakage current in off mode possible
- Power supply off mode (high/low ohmic) important for leakage current path



 Setting a working point for the Shunt-LDO



Relationships

$$V_{in} = V_{ofs} + \frac{R3}{1000} * I_{in}$$

$$V_{out} = 2 * V_{ref}$$


- Choose V_{ofs} and Slope (with resistors) \Rightarrow For input behavior
- Trim V_{ref} (with trimbits) \Rightarrow For output behavior
- Provide constant input current
 - Shunt-LDO regulates input voltage accordingly
 - Has to be higher than maximum expected load
 - Limited by $1.4V < V_{IN} < 2.0V$ and $I_{IN,SLDO} < 2.0A$

Fixed after installation

Adjustable during operation


Shunt-LDO evaluation

 Irradiation campaign with Shunt-LDO testchips



Shunt-LDO is fully functional after 600Mrad at 0C:

 
- Output behavior is very stable
- Some variations of input behavior
- Reference voltages change due to internal resistor
=> New design with radiation harder resistor




Additional feature: Overload protection

- Decreases output voltage if load current gets too high
=> Reduces transients propagated to other chips in the chain

Protection off

 


Protection on

 

- Creating 1 ms overload pulse and comparing with and without protection
=> Without protection huge transient on **input voltage**
=> **With protection reduced transient on input voltage**

Additional feature: Overvoltage protection

 
➤ Acts like a voltage clamp => **Limits maximum voltage**



- Tested with different configured maximum voltages
- **Startup significantly improved** compared to RD53A

Serial powering system tests with RD53A chips

 Serial powering system tests with RD53A chips




8 RD53A chips without sensor

8 RD53A chips **with sensor**


- First serial powering tests based on single RD53A chip cards connected externally
- Emulated serial power chains of double and quad modules with 16 RD53A chips

Emulating Quad and Double modules



a) 8x “Double-chip modules”

 

VI curves for each module group

 


b) 4x “Quad-chip modules”

  

=> Successfully operated serial chains with up to 16 RD53A chips on Single Chip Cards

 Powering RD53A chips with new Shunt-LDO test chips



- Started to test new Shunt-LDO test chips with RD53A chip (By bypassing the RD53A Shunt-LDOs)
 - Want to evaluate new Shunt-LDO performance with RD53A chip