

S-Parameters – Introduction (1)

- ◆ **Light falling on a car window:**
 - Some parts of the incident light is reflected (you see the mirror image)
 - Another part of the light is transmitted through the window (you can still see inside the car)
- ◆ **Optical reflection and transmission coefficients of the window glass define the ratio of reflected and transmitted light**
- ◆ **Similar:**
Scattering (S-) parameters of an n -port electrical network (DUT) characterize reflected and transmitted (power) waves




S-Parameters – Introduction (2)

◆ Electrical networks

- 1... n -ports circuits
- Defined by **voltages** $V_n(\omega)$ or $v_n(t)$ and **currents** $I_n(\omega)$ or $i_n(t)$ at the ports
- Characterized by circuit matrices, e.g. ABCD (chain), Z, Y, H, etc.

◆ RF networks

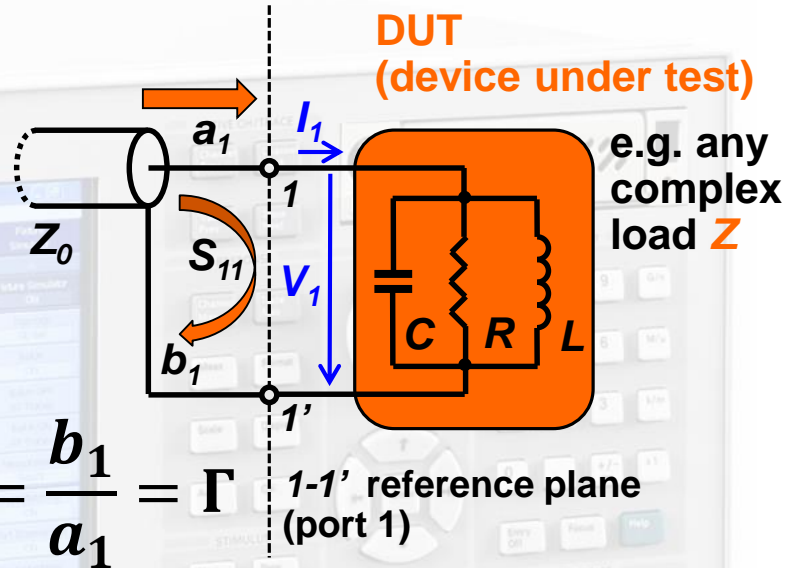
- 1... n -port RF DUT circuit or subsystem, e.g. filter, amplifier, transmission-line, hybrid, circulator, resonator, etc.
- Defined by **incident** $a_n(\omega, s)$ and **reflected waves** $b_n(\omega, s)$ at a **reference plane** s (physical position) at the ports
- Characterized by a scattering parameter (S-parameter) matrix of the reflected and transmitted power waves
- Normalized to a **reference impedance** $\sqrt{Z_0}$ of typically $Z_0 = 50 \Omega$



1-port DUT example

- ◆ S-Parameters allow to characterize the DUT with the measurement equipment to be located at some distance
- ◆ All high frequency effects of distributed elements are taken into account with respect to the reference plane

S-Parameters – Example: 2-port DUT

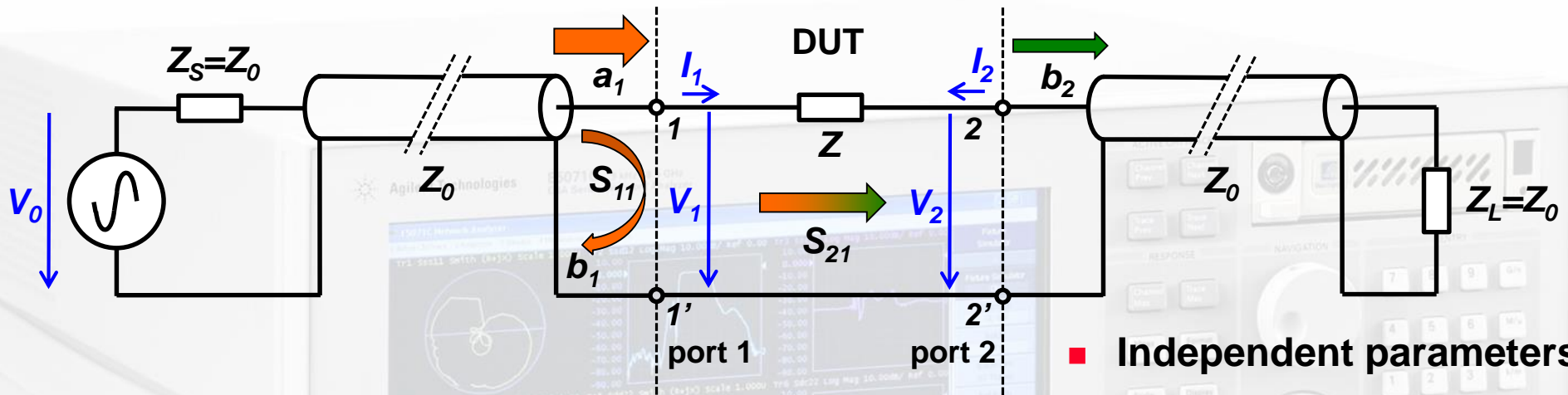

◆ Analysis of the forward S-parameters:

$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} \equiv \text{input reflection coefficient}$$

$(Z_L = Z_0 \Rightarrow a_2 = 0)$

$$S_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0} \equiv \text{forward transmission gain}$$

- Examples of 2-ports DUT: filters, amplifiers, attenuators, transmission-lines (cables), etc.
- **ALL ports ALWAYS need to be terminated in their characteristic impedance!**

■ Independent parameters:

$$a_1 = \frac{V_1^{inc}}{\sqrt{Z_0}} = \frac{V_1 + I_1 Z_0}{2\sqrt{Z_0}}$$


$$a_2 = \frac{V_2^{inc}}{\sqrt{Z_0}} = \frac{V_2 + I_2 Z_0}{2\sqrt{Z_0}}$$

■ Dependent parameters:

$$b_1 = \frac{V_1^{refl}}{\sqrt{Z_0}} = \frac{V_1 - I_1 Z_0}{2\sqrt{Z_0}}$$

$$b_2 = \frac{V_2^{refl}}{\sqrt{Z_0}} = \frac{V_2 - I_2 Z_0}{2\sqrt{Z_0}}$$

S-Parameters – Example: 2-port DUT

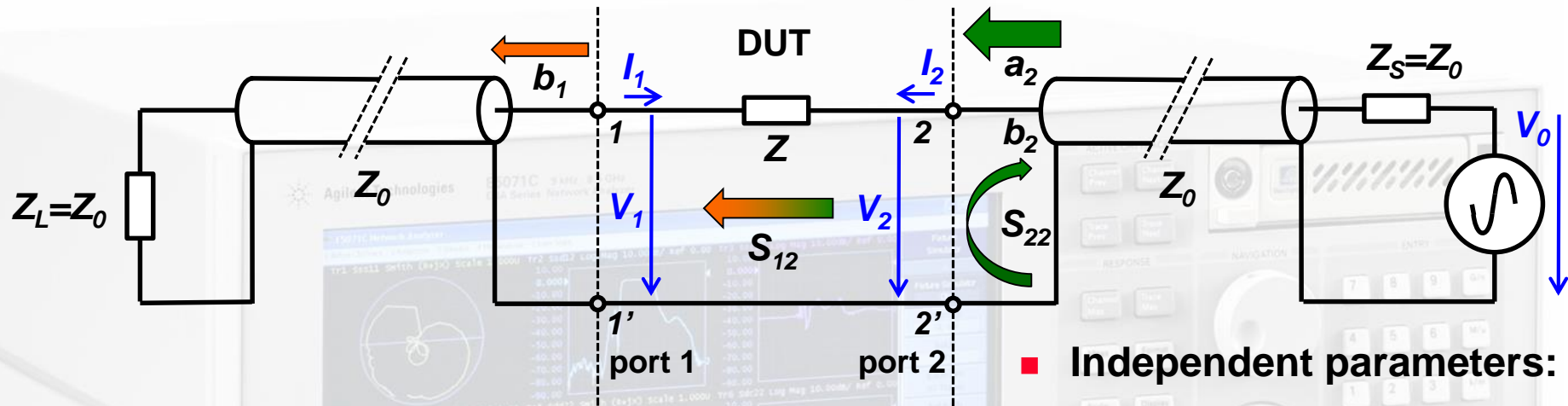

◆ Analysis of the reverse S-parameters:

$$S_{22} = \left. \frac{b_2}{a_2} \right|_{a_1=0} \equiv \text{output reflection coefficient}$$

$(Z_L = Z_0 \Rightarrow a_1 = 0)$

$$S_{12} = \left. \frac{b_1}{a_2} \right|_{a_1=0} \equiv \text{backward transmission gain}$$

- n -port DUTs still can be fully characterized with a 2-port VNA, but again: **don't forget to terminate unused ports!**

- Independent parameters:

$$a_1 = \frac{V_1^{inc}}{\sqrt{Z_0}} = \frac{V_1 + I_1 Z_0}{2\sqrt{Z_0}}$$

$$a_2 = \frac{V_2^{inc}}{\sqrt{Z_0}} = \frac{V_2 + I_2 Z_0}{2\sqrt{Z_0}}$$

- Dependent parameters:

$$b_1 = \frac{V_1^{refl}}{\sqrt{Z_0}} = \frac{V_1 - I_1 Z_0}{2\sqrt{Z_0}}$$

$$b_2 = \frac{V_2^{refl}}{\sqrt{Z_0}} = \frac{V_2 - I_2 Z_0}{2\sqrt{Z_0}}$$

S-Parameters – Definition (1)

◆ Linear equations for the 2-port DUT:

$$\begin{aligned} b_1 &= S_{11}a_1 + S_{12}a_2 \\ b_2 &= S_{21}a_1 + S_{22}a_2 \end{aligned}$$

■ with:

$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} \equiv \text{input reflection coefficient}$$

$$S_{22} = \left. \frac{b_2}{a_2} \right|_{a_1=0} \equiv \text{output reflection coefficient}$$

$$S_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0} \equiv \text{forward transmission gain}$$

$$S_{12} = \left. \frac{b_1}{a_2} \right|_{a_1=0} \equiv \text{backward transmission gain}$$

S-Parameters – Definition (2)

- ◆ Reflection coefficient and impedance at the n^{th} -port of a DUT:

$$S_{nn} = \frac{b_n}{a_n} = \frac{\frac{V_n}{I_n} - Z_0}{\frac{V_n}{I_n} + Z_0} = \frac{Z_n - Z_0}{Z_n + Z_0} = \Gamma_n$$

$$Z_n = Z_0 \frac{1 + S_{nn}}{1 - S_{nn}} \text{ with } Z_n = \frac{V_n}{I_n} \text{ being the input impedance at the } n^{\text{th}} \text{ port}$$

- ◆ Power reflection and transmission for a n -port DUT


$$|S_{nn}|^2 = \frac{\text{power reflected from port } n}{\text{power incident on port } n}$$

$$|S_{nm}|^2 = \text{transmitted power between ports } n \text{ and } m$$

with all ports terminated in their characteristic impedance Z_0
and $Z_S = Z_0$

Here the US notion is used, where power = $|a|^2$.
European notation (often): power = $|a|^2/2$
These conventions have no impact on the S-parameters,
they are only relevant for absolute power calculations

How to measure S-Parameters?

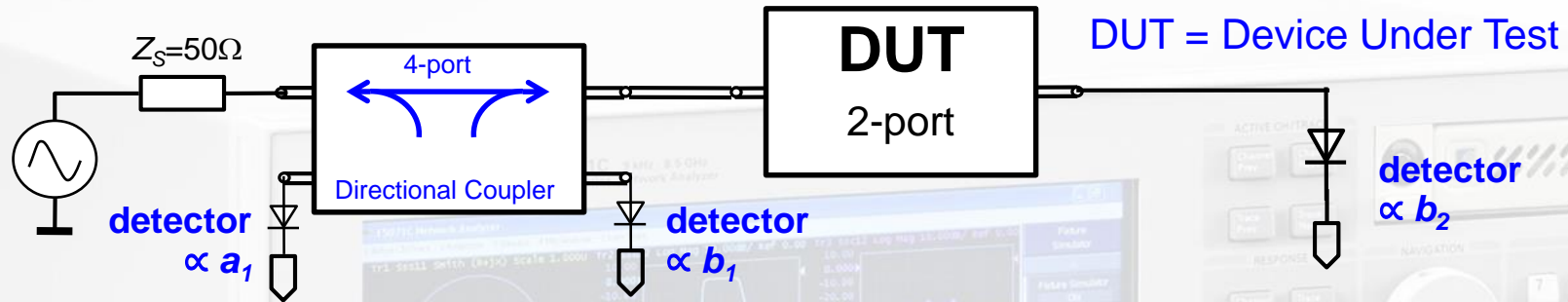


- ◆ **Performed in the frequency domain**
 - Single or swept frequency generator, stand-alone or as part of a VNA or SA
 - Requires a **directional coupler** and RF detector(s) or receiver(s)
- ◆ **Evaluate S_{11} and S_{21} of a 2-port DUT**
 - Ensure $a_2=0$, i.e. the detector at port 2 offers a well matched impedance
 - Measure incident wave a_1 and reflected wave b_1 at the directional coupler ports and compute for each frequency
 - Measure transmitted wave b_2 at DUT port 2 and compute
- ◆ **Evaluate S_{22} and S_{12} of the 2-port DUT**
 - Perform the same methodology as above by exchanging the measurement equipment on the DUT ports

$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0}$$
$$S_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0}$$

The *Smith Chart* (1)

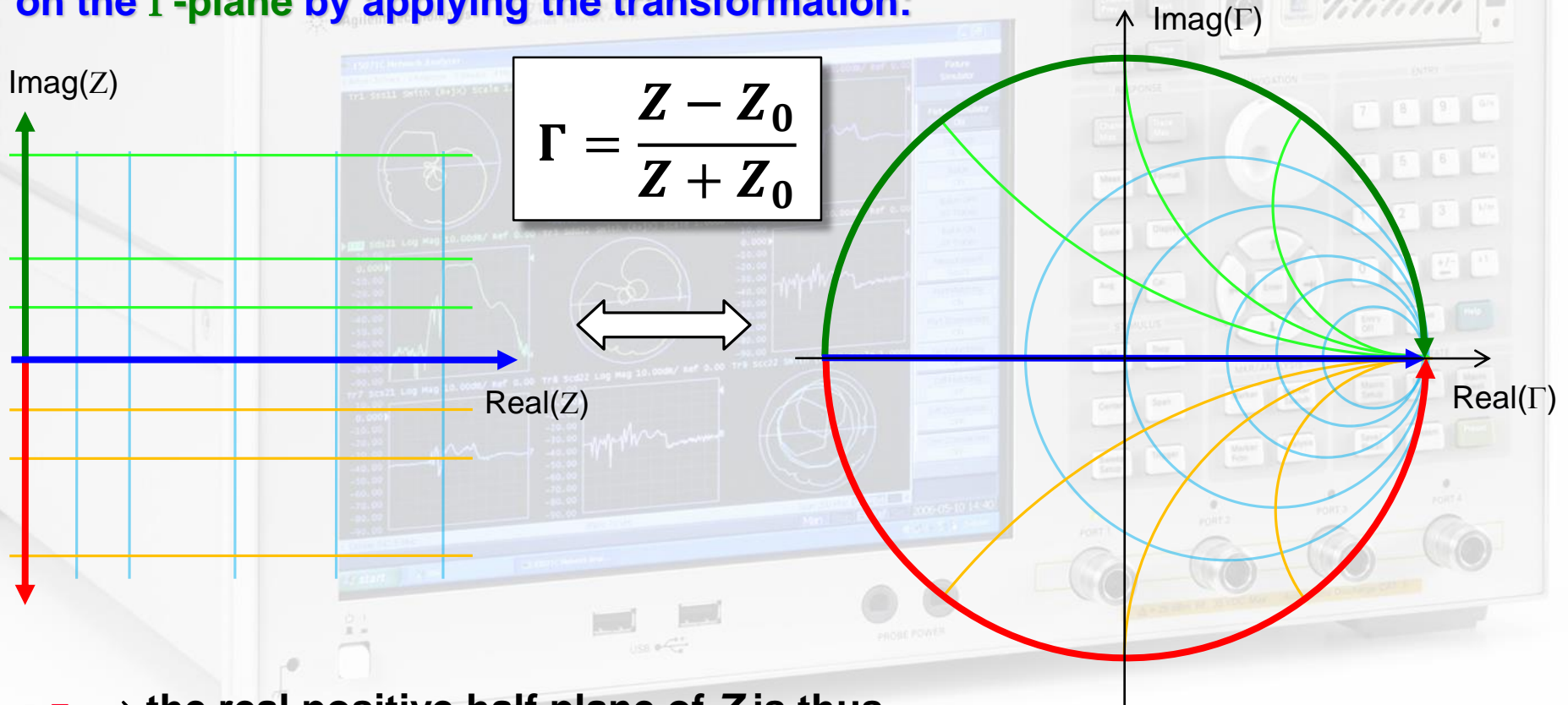- ◆ The *Smith Chart* (in impedance coordinates) represents the complex Γ -plane (in polar coordinates) within the unit circle.
- ◆ It is a conformal mapping of the complex Z -plane on the Γ -plane by applying the transformation:



- \Rightarrow the real positive half plane of Z is thus transformed (*Möbius*) into the interior of the unit circle!

The *Smith Chart* (2)

- ◆ The Impedance Z is usually normalized to a reference impedance Z_0 , typically the characteristic impedance of the coaxial cables of $Z_0=50\Omega$.
- ◆ The normalized form of the transformation follows then as:


$$z = \frac{Z}{Z_0}$$

$$\Gamma = \frac{z - 1}{z + 1} \quad \text{resp.} \quad \frac{Z}{Z_0} = z = \frac{1 + \Gamma}{1 - \Gamma}$$

This mapping offers several practical advantages:

- ◆ The diagram includes all “passive” impedances, i.e. those with positive real part, from zero to infinity in a handy format.
 - Impedances with negative real part (“active device”, e.g. reflection amplifiers) would be outside the (normal) *Smith* chart.
- ◆ The mapping converts impedances or admittances into reflection factors and vice-versa. This is particularly interesting for studies in the radiofrequency and microwave domain where electrical quantities are usually expressed in terms of “incident” or “forward”, and “reflected” or “backward” waves.
 - This replaces the notation in terms of currents and voltages used at lower frequencies.
- ◆ Also the reference plane can be moved very easily using the *Smith* chart.

The Smith Chart (3)

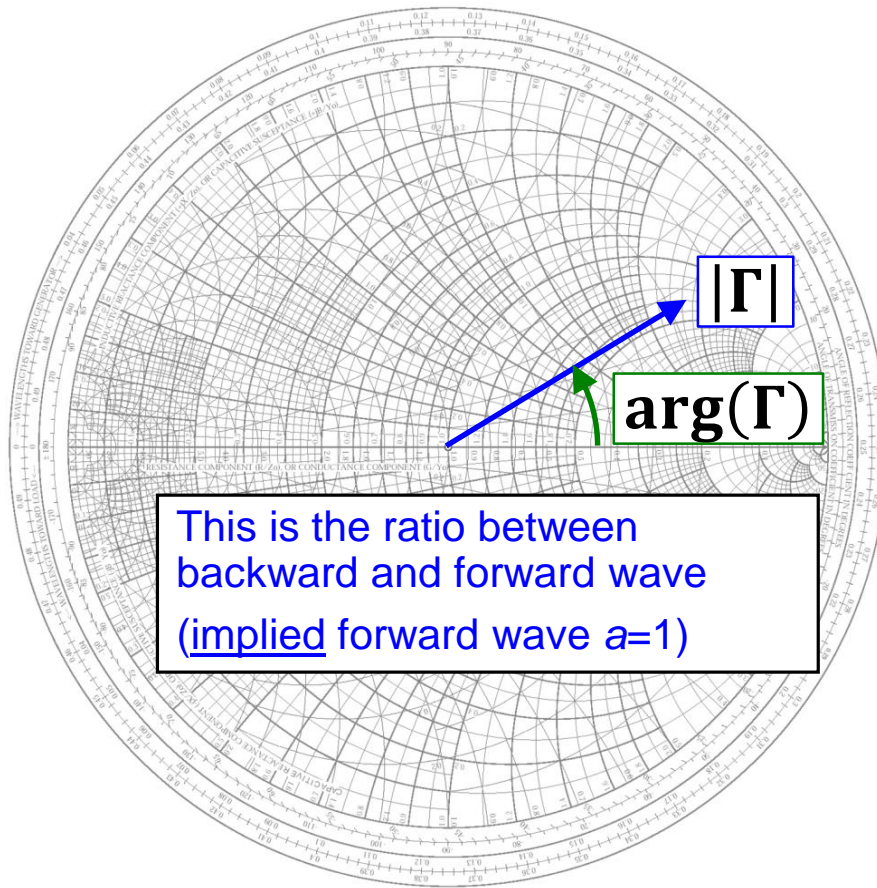

- ◆ In the *Smith* chart, the complex reflection factor

$$\Gamma = |\Gamma|e^{j\varphi} = \frac{b}{a}$$

is expressed in linear cylindrical coordinates, representing the ratio of backward vs. forward traveling waves.


The Smith Chart (4)

- ◆ The distance from the center of the directly proportional to the **magnitude of the reflection factor $|\Gamma|$** , and permits an easy visualization of the **matching performance**.

- In particular, the perimeter of the diagram represents total reflection: $|\Gamma|=1$.
- (power dissipated in the load) = (forward power) – (reflected power)

$$\begin{aligned} P &= |a|^2 - |b|^2 \\ &= |a|^2 (1 - |\Gamma|^2) \end{aligned}$$

available source power mismatch losses

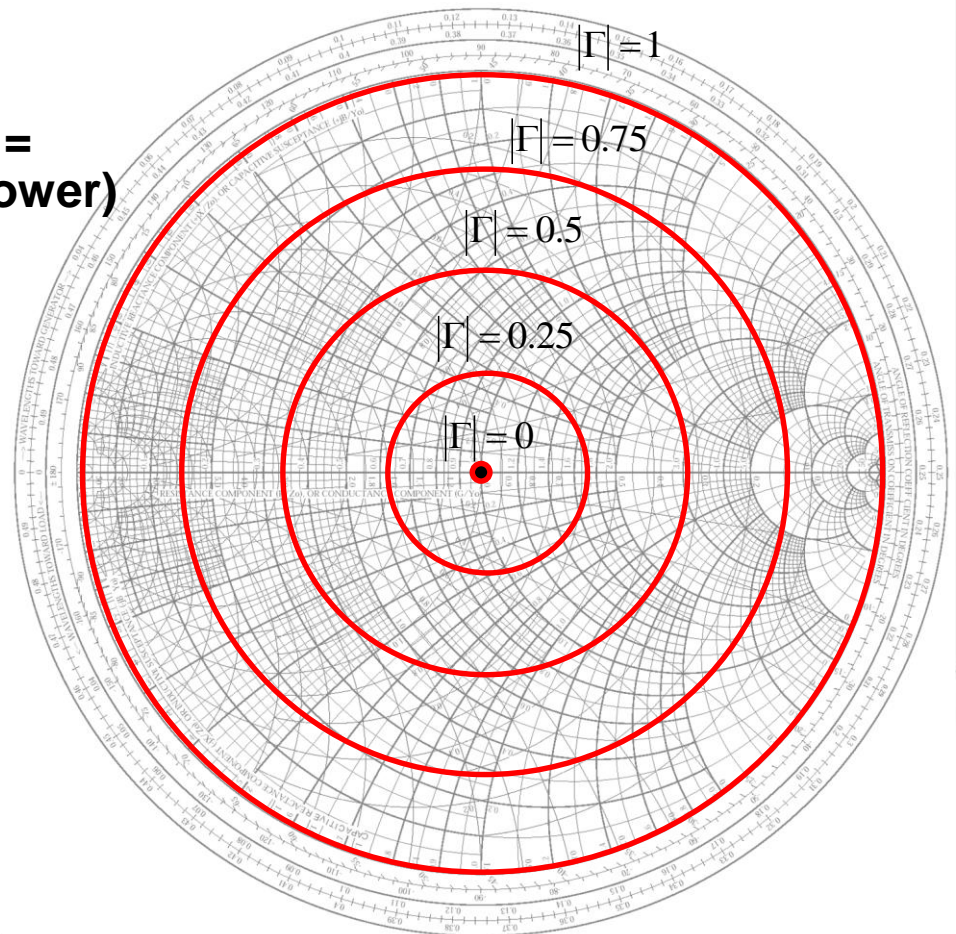

The *Smith Chart* – “Important Points”

Important Points:

- ◆ **Short Circuit**
 $\Gamma = -1, z = 0$
- ◆ **Open Circuit**
 $\Gamma = +1, z \rightarrow \infty$
- ◆ **Matched Load**
 $\Gamma = 0, z = 1$
- ◆ **On the circle $\Gamma = 1$:**
lossless element
- ◆ **Upper half:**
”inductive” =
positive imaginary part of Z
- ◆ **Lower half:**
”capacitive” =
negative imaginary part of Z
- **Outside the circle, $\Gamma > 1$:**
active element,
for instance tunnel diode reflection amplifier

Short Circuit

$$z = 0$$

$$\Gamma = -1$$

Open Circuit

$$z = \infty$$

$$\Gamma = +1$$

$$z = 1$$

$$\Gamma = 0$$

Matched Load

