

# JUAS 2020 – Tutorial 1

F. Caspers, M. Bozzolan, M. Wendt

$$\mu = \mu_0 \mu_r$$

$$\mu_0 = 4\pi \cdot 10^{-7} \text{ Vs/(Am)}$$

$$\varepsilon = \varepsilon_0 \varepsilon_r$$

$$\varepsilon_0 = 8.854 \cdot 10^{-12} \text{ As/(Vm)}$$

$$c_0 = 2.998 \cdot 10^8 \text{ m/s}$$

## 1.) Transmission-lines


Given is a coaxial transmission-line with an inner diameter of the outer conductor of 100 mm, the dielectric is air (so-called "air-line").

### Questions:

1. What is the outer diameter of the inner conduction to achieve a characteristic impedance of  $50 \Omega$ ?
2. With which velocity is a wave travelling in this line?
3. Specify the capacitance and inductance per meter length of this transmission-line?
4. Instead of an air dielectric this transmission line is now homogeneously filled with Teflon ( $\varepsilon_r = 2$ ). Determine the phase velocity, characteristic impedance, as well as capacitance and inductance per meter length?
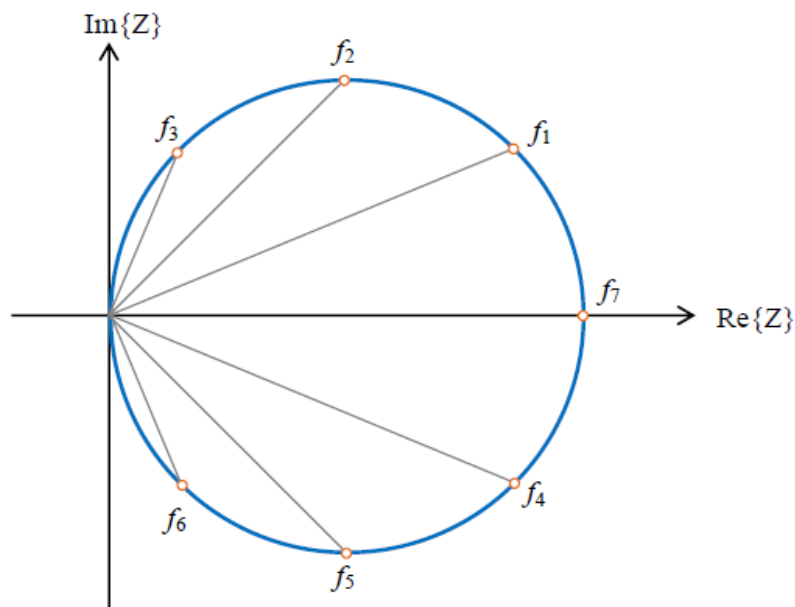
## 2.) Impedances in the complex plane (2)

The impedance of a resonant circuit is a function of frequency. For a given resonator the impedance was measured at 7 different frequencies,  $f_1 \dots f_7$ . The result is shown in the complex  $Z$ -plane:



	$f_1$	$f_2$	$f_3$	$f_4$	$f_5$	$f_6$	$f_7$
$f / \text{MHz}$	105.11	105.05	104.94	105.29	105.35	105.46	105.20
$Z / \text{k}\Omega$	$200.0 e^{j30^\circ}$	$162.6 e^{j45^\circ}$	$115.0 e^{j60^\circ}$	$200.0 e^{-j30^\circ}$	$162.6 e^{-j45^\circ}$	$115.0 e^{-j60^\circ}$	$230.0 e^{j0^\circ}$

## Questions:

1. Determine the resonant frequency.
2. Determine the 3-dB bandwidth ( $BW$ ) of this resonator.  
(Hint: The bandwidth of a resonator is defined as the frequency difference between the upper and lower 3-dB frequency points.)
3. Sketch the equivalent circuit for the measured resonator.
4. Determine  $R$ .
5. Draw the locus of admittance of this circuit in the  $Y$ -plane, and indicate lower and upper 3-dB points.
6. Determine the Q-value, as well as  $L$  and  $C$  for this circuit.

## 3.) Multiple choice questions

1. How will the resonant frequency  $f_{res}$  of the  $E_{010}$  ( $TM_{010}$ ) mode of a pill box cavity change if height of the cavity is doubled? (check 1)
  - The  $f_{res}$  decreases by a factor 2.
  - The  $f_{res}$  decreases by a factor  $\sqrt{2}$ .
  - The  $f_{res}$  increases by a factor 2.
  - The  $f_{res}$  increases by a factor  $\sqrt{2}$ .
  - The  $f_{res}$  will not change.
2. A critically coupled aluminum pill-box cavity is driven by an RF generator. The same pill-box cavity is now made out of copper, again with the generator operating at critical coupling, such that the gap voltage remains the same.  $\sigma_{Al} = 3.8 \cdot 10^7 S/m$ ,  $\sigma_{Cu} = 5.8 \cdot 10^7 S/m$ . What happens with the dissipated power in the cavity? (check 1)
  - The power dissipation decreases
  - The power dissipation increases
  - The power dissipation will not change
3. Calculate the thickness of a copper wall of 5 times the penetrations depth for 50 Hz signals.  $\sigma_{Cu} = 5.8 \cdot 10^7 S/m$ ,  $\mu = \mu_0 \mu_r$  with  $\mu_0 = 4\pi \cdot 10^{-7} Vs/Am$  (check 1)
  - 46.7 mm
  - 4.67 mm
  - 0.46 mm
  - 0.046 mm
4. A rectangular waveguide has a width (long side!) of  $a = 10$  cm. (check 2)
  - The mode  $TE_{10}$  or  $H_{10}$  has a cutoff frequency of 3 GHz.
  - The mode  $TE_{10}$  or  $H_{10}$  has a cutoff frequency of 1.5 GHz.
  - The electric field is parallel to the side with the larger dimension.
  - The electric field is orthogonal to the side with the larger dimension.

5. Which mode is the fundamental mode (lowest cut-off frequency) in a cylindrical waveguide of circular cross-section *without* inner conductor? (check 1)

- $TE$
- $TEM$
- $TM$

6. Adding capacitive loading to a cavity (check 1)

- lowers the resonance frequency
- does not affect the resonance frequency
- increases the resonance frequency

7. When you cover the antenna of your mobile with your hand, the attenuation caused is in the order of 20 dB. Human tissue is a rather good absorber, so you can neglect reflections for this calculation. How many percent of the mobile's output power stay in the hand? (check 1)

- 9 %
- 99 %
- 99.9 %
- 99.99 %

## 4.) Impedances in the complex plane

### Questions:

1. Plot the following impedances in the Z-plane, use the plot axes on the next page:

$Z = (3 + 4j) \Omega$	$ Z  = 2, \arg(Z) = \pi/4$	$Z = \text{short circuit}$
$Z = 2 \Omega$	$ Z  = 1, \arg(Z) = -\pi/2$	$Y = Z^{-1} = (0.16 + 0.12j) \Omega^{-1}$
$Z = (1 - 4j) \Omega$	$ Z  = 5, \arg(Z) = 53^\circ$	

2. Qualitatively, how would an inductor look like, plotted from DC to some arbitrary frequency, in the Z-plane? Hint:  $Z_L = j\omega L$

3. How would a capacitor look like? Hint:  $Z_C = 1/(j\omega C)$

4. The input impedance of a RLC circuit has been plotted in the Z-plane (blue circle).

Mark the points in the diagram describing:

- a. Impedance at the resonant frequency
- b. DC impedance
- c. 3-dB bandwidth
- d. Impedance at  $f \rightarrow \infty$

## 5.) Waves of a transmission line $Z = 50 \Omega$

Problem: Convert the circuit-based formats, voltage  $V$  and current  $I$  into the equivalent wave-based formats, forward wave  $a$  and backward wave  $b$  and vice versa using the relations:

$a = \frac{V + I Z}{2}$	$V = a + b$
$b = \frac{V - I Z}{2}$	$I Z = a - b$

### Questions:

- In a  $50 \Omega$  system, a directional coupler measured forward and reflected waves  $a$  and  $b$  at a certain plane as:  $a = 100 \angle 0^\circ$  and  $b = 60 \angle 45^\circ$ .
  - Calculate the corresponding voltage  $V$  and current  $I$
  - Sketch the "phasors" of  $V$ ,  $I Z$ ,  $a$  and  $b$ .
- At some plane in the  $50 \Omega$  system, a voltage of  $V = 100 \angle 0^\circ$  V and a current of  $I = 1.0 \angle -45^\circ$  A are measured.
  - Calculate the corresponding forward and backward waves  $a$  and  $b$ .
  - Sketch the "phasors" of  $V$ ,  $I Z$ ,  $a$  and  $b$ .

## 6.) Scaling laws

A cavity shall be scaled from existing designs for a frequency  $f_x = 318.32$  MHz and  $C_x = 10$  pF. There are three test designs, with the following parameters:

Cavity	$f_{res}$ / MHz	$C$ / pF	$Q$	Diameter / mm
<b>A</b>	100	7.957	10000	600
<b>B</b>	500	3.18	5000	200
<b>C</b>	3000	1.061	2000	25

### Questions:

- Which cavity is suitable as reference design?
- Calculate the diameter of the new design.
- Calculate the expected  $Q$  factor for the new design, provided it will be built out of the same

## 7.) Thermal expansion and scaling laws

An accelerator cavity heats up under high RF power load.

The cavity used is constructed from a material having a:

thermal expansion coefficient:  $\Delta l/l = 20\text{e-}6/^{\circ}\text{C}$  (per degree Centigrade)

thermal resistivity coefficient:  $\Delta\rho/\rho = 4\text{e-}3/^{\circ}\text{C}$  (per degree Centigrade)

At room temperature the cavities resonance frequency is  $f_1 = 100$  MHz and has a 3-dB bandwidth of  $BW_1 = 100$  kHz.

Under RF power the cavity temperature increases by  $100^{\circ}\text{C}$  (subscripts 2 apply).

### Questions:

Determine

- the ratio  $\lambda_2/\lambda_1$
- the ratio  $L_2/L_1$
- the ratio  $C_2/C_1$
- the ratio  $Q_2/Q_1$  (hint: the skin depth  $\delta$  is proportional to  $\sqrt{\rho/f}$ )
- the resonance frequency  $f_2$  under load
- and the 3-dB bandwidth  $BW_2$  of the resonance under load