

# JUAS 2020 – Tutorial 1

F. Caspers, M. Bozzolan, M. Wendt

$$\mu = \mu_0 \mu_r$$

$$\mu_0 = 4\pi \cdot 10^{-7} \text{ Vs/(Am)}$$

$$\varepsilon = \varepsilon_0 \varepsilon_r$$

$$\varepsilon_0 = 8.854 \cdot 10^{-12} \text{ As/(Vm)}$$

$$c_0 = 2.998 \cdot 10^8 \text{ m/s}$$

## 1.) Transmission-lines

Given is a coaxial transmission-line with an inner diameter of the outer conductor of 100 mm, the dielectric is air (so-called “air-line”).

### Questions:

1. What is the outer diameter of the inner conductor to achieve a characteristic impedance of  $50 \Omega$ ?

$$Z_0 = \sqrt{\frac{\mu_r}{\varepsilon_r}} 60 \Omega \ln\left(\frac{R}{r}\right) = 60 \Omega \ln\left(\frac{D}{d}\right)$$
$$d = \frac{D}{\exp\left(\frac{50}{60}\right)} = \frac{D}{2.3} = 43.46 \text{ mm}$$

see script page 10

2. With which velocity is a wave travelling in this line?

$$v = c = 2.998 \cdot 10^8 \text{ m/s}$$

3. Specify the capacitance and inductance per meter length of this transmission-line?

$$C' = \frac{1}{vZ_0} = 66.71 \text{ pF/m}$$

$$L' = \frac{Z_0}{v} = 166.78 \text{ nH/m}$$

see script page 10

4. Instead of an air dielectric this transmission line is now homogeneously filled with Teflon ( $\varepsilon_r = 2$ ). Determine the phase velocity, characteristic impedance, as well as capacitance and inductance per meter length?

$$v = \frac{c}{\sqrt{\varepsilon_r \mu_r}} = 2.12 \cdot 10^8 \text{ m/s}$$


$$Z_0 = \frac{60 \Omega}{\sqrt{\varepsilon_r}} \ln\left(\frac{D}{d}\right) = 35.36 \Omega$$

$$C' = \frac{1}{vZ_0} = 133.43 \text{ pF/m}$$

$$L' = \frac{Z_0}{v} = 166.78 \text{ nH/m}$$
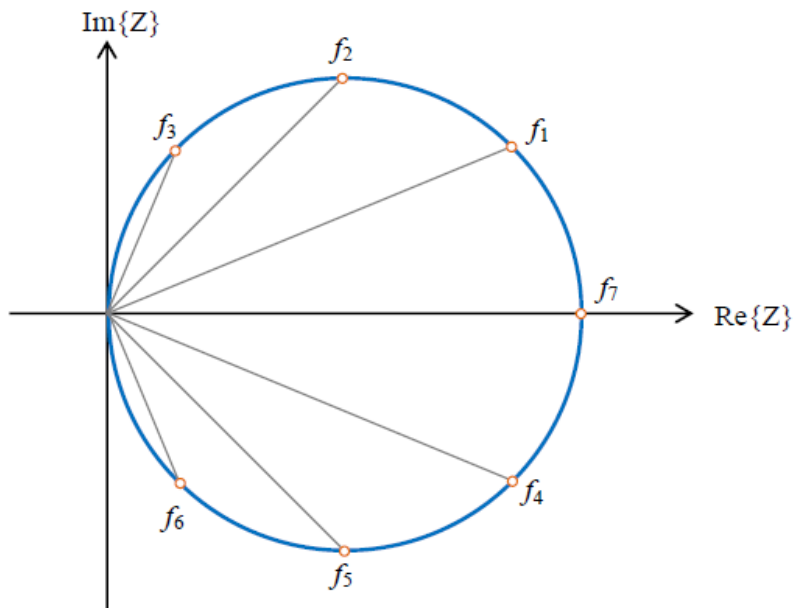
## 2.) Impedances in the complex plane (2)

The impedance of a resonant circuit is a function of frequency. For a given resonator the impedance was measured at 7 different frequencies,  $f_1 \dots f_7$ . The result is shown in the complex Z-plane:



	$f_1$	$f_2$	$f_3$	$f_4$	$f_5$	$f_6$	$f_7$
$f / \text{MHz}$	105.11	105.05	104.94	105.29	105.35	105.46	105.20
$Z / \text{k}\Omega$	$200.0 e^{j30^\circ}$	$162.6 e^{j45^\circ}$	$115.0 e^{j60^\circ}$	$200.0 e^{-j30^\circ}$	$162.6 e^{-j45^\circ}$	$115.0 e^{-j60^\circ}$	$230.0 e^{j0^\circ}$

### Questions:

1. Determine the resonant frequency.

$$f_{res} = f_7 = 105.20 \text{ MHz}$$

2. Determine the 3-dB bandwidth ( $BW$ ) of this resonator.


(Hint: The bandwidth of a resonator is defined as the frequency difference between the upper and lower 3-dB frequency points.)

$$BW = f_5 - f_2 = 300 \text{ kHz}$$

In order to evaluate the properties of a resonator,

it is common to model it as equivalent circuit with lumped RLC elements.

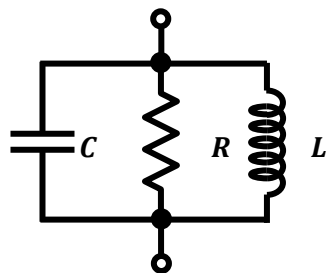
3. Sketch the equivalent circuit for the measured resonator.



4. Determine  $R$ .

$R = 230 \text{ k}\Omega$  (at  $f_{res} = f_7$ )

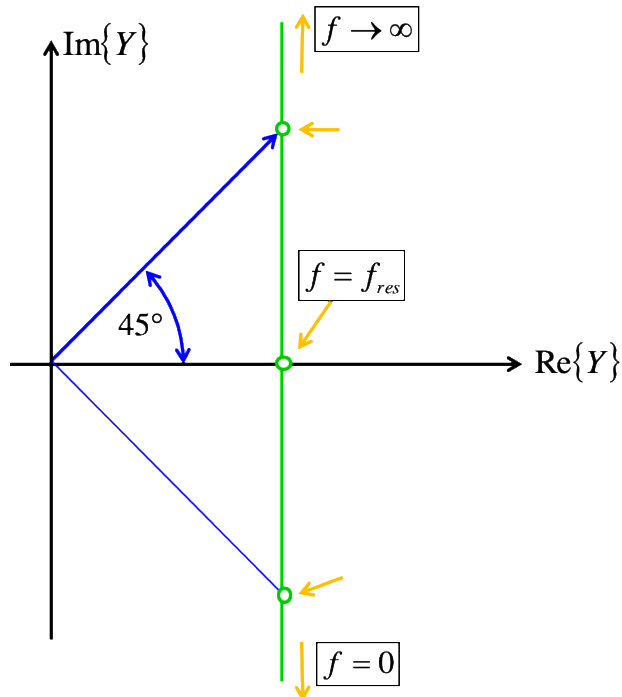5. Draw the locus of admittance of this circuit in the  $Y$ -plane, and indicate lower and upper 3-dB points.



Straight line parallel to the  $Im\{Y\}$  axes, crossing  $Re\{Y\}$  at  $1/230 \text{ mS}$ . The 3-dB points are located on the locus as points crossing with lines from the origin under  $\pm 45^\circ$ .

see script page 58

6. Determine the Q-value, as well as  $L$  and  $C$  for this circuit.

$$Q = \frac{f_{res}}{BW} = 350.667$$

$$L = \frac{R}{2\pi f_{res} Q} = 992 \text{ nH}$$

$$C = \frac{1}{(2\pi f_{res})^2 L} = 2.31 \text{ pF}$$

### 3.) Multiple choice questions

1. How will the resonant frequency  $f_{res}$  of the  $E_{010}$  ( $TM_{010}$ ) mode of a pill box cavity change if height of the cavity is doubled? (check 1)

- The  $f_{res}$  decreases by a factor 2.
- The  $f_{res}$  decreases by a factor  $\sqrt{2}$ .
- The  $f_{res}$  increases by a factor 2.
- The  $f_{res}$  increases by a factor  $\sqrt{2}$ .
- The  $f_{res}$  will not change.

2. A critically coupled aluminum pill-box cavity is driven by an RF generator. The same pill-box cavity is now made out of copper, again with the generator operating at critical coupling, such that the gap voltage remains the same.  $\sigma_{Al} = 3.8 \cdot 10^7 S/m$ ,  $\sigma_{Cu} = 5.8 \cdot 10^7 S/m$ . What happens with the dissipated power in the cavity? (check 1)

- The power dissipation decreases
- The power dissipation increases
- The power dissipation will not change

3. Calculate the thickness of a copper wall of 5 times the penetrations depth for 50 Hz signals.  $\sigma_{Cu} = 5.8 \cdot 10^7 S/m$ ,  $\mu = \mu_0 \mu_r$  with  $\mu_0 = 4\pi \cdot 10^{-7} Vs/Am$  (check 1)

- 46.7 mm
- 4.67 mm
- 0.46 mm
- 0.046 mm

4. A rectangular waveguide has a width (long side!) of  $a = 10$  cm. (check 2)

- The mode  $TE_{10}$  or  $H_{10}$  has a cutoff frequency of 3 GHz.
- The mode  $TE_{10}$  or  $H_{10}$  has a cutoff frequency of 1.5 GHz.
- The electric field is parallel to the side with the larger dimension.
- The electric field is orthogonal to the side with the larger dimension.

5. Which mode is the fundamental mode (lowest cut-off frequency) in a cylindrical waveguide of circular cross-section *without* inner conductor? (check 1)

- $TE$
- $TEM$
- $TM$

6. Adding capacitive loading to a cavity (check 1)

- lowers the resonance frequency
- does not affect the resonance frequency
- increases the resonance frequency

7. When you cover the antenna of your mobile with your hand, the attenuation caused is in the order of 20 dB. Human tissue is a rather good absorber, so you can neglect reflections for this calculation. How many percent of the mobile's output power stay in the hand? (check 1)

- 9 %
- 99 %
- 99.9 %
- 99.99 %

## 4.) Impedances in the complex plane

### Questions:


1. Plot the following impedances in the Z-plane, use the plot axes on the next page:

$Z = (3 + 4j) \Omega$	$ Z  = 5, \arg(Z) = \pi/4$	$Z = \text{short circuit}$
$Z = 2 \Omega$	$ Z  = 2, \arg(Z) = -\pi/4$	$Y = Z^{-1} = (0.16 + 0.12j) \Omega^{-1}$
$Z = (1 - 4j) \Omega$	$ Z  = 5, \arg(Z) = 53^\circ$	

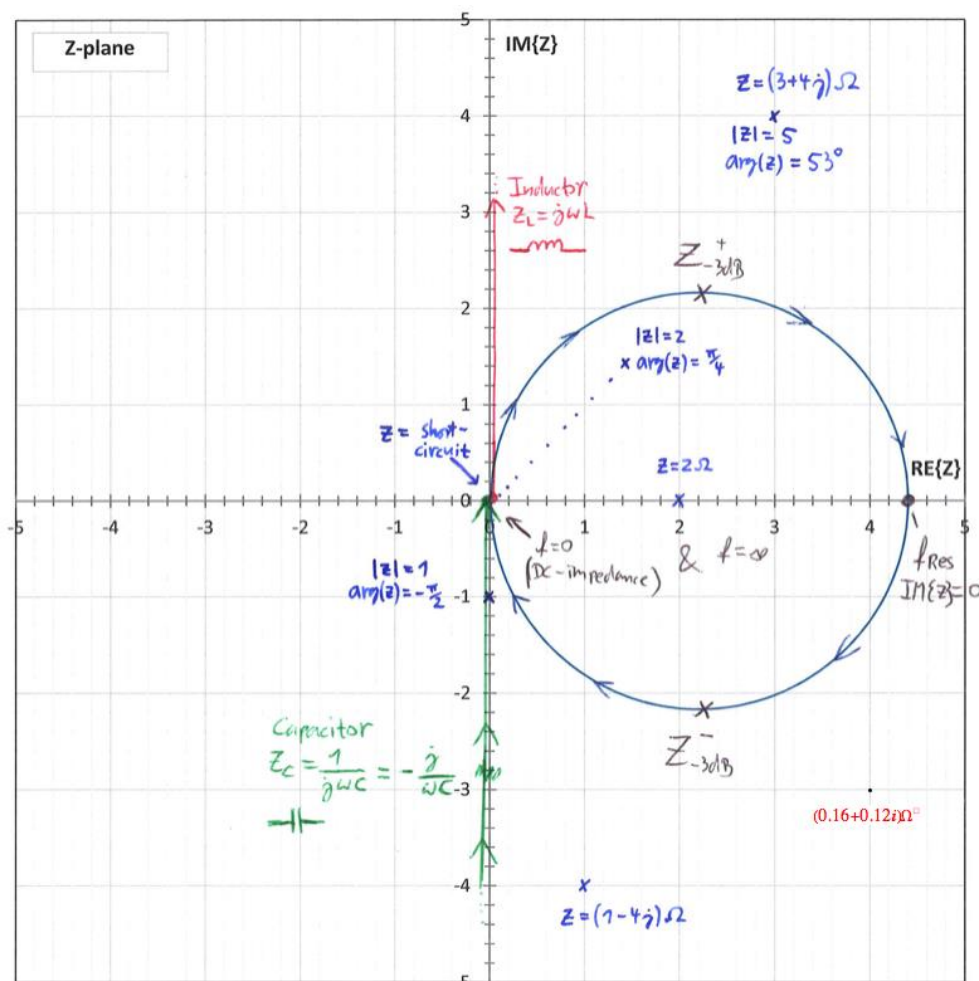2. Qualitatively, how would an inductor look like, plotted from DC to some arbitrary frequency, in the Z-plane? Hint:  $Z_L = j\omega L$
3. How would a capacitor look like? Hint:  $Z_C = 1/(j\omega C)$
4. The input impedance of a RLC circuit has been plotted in the Z-plane (blue circle).

Mark the points in the diagram describing:

- Impedance at the resonant frequency
- DC impedance
- 3-dB bandwidth
- Impedance at  $f \rightarrow \infty$



## 5.) Waves of a transmission line $Z = 50 \Omega$

Problem: Convert the circuit-based formats, voltage  $V$  and current  $I$  into the equivalent wave-based formats, forward wave  $a$  and backward wave  $b$  and vice versa using the relations:

$a = \frac{V + IZ}{2}$	$V = a + b$
$b = \frac{V - IZ}{2}$	$IZ = a - b$

### Questions:


- In a  $50 \Omega$  system, a directional coupler measured forward and reflected waves  $a$  and  $b$  at a certain plane as:  $a = 100 \angle 0^\circ$  and  $b = 60 \angle 45^\circ$ .

- Calculate the corresponding voltage  $V$  and current  $I$

$$V = a + b = (100 + 42.43 + j42.43) V = (142.43 + j42.43) V = 148.61 V e^{j16.59^\circ}$$

$$I = \frac{a - b}{Z} = \frac{(100 - 42.43 - j42.43) V}{50 \Omega} = (1.15 - j0.849) A = 1.43 A e^{-j36.39^\circ}$$

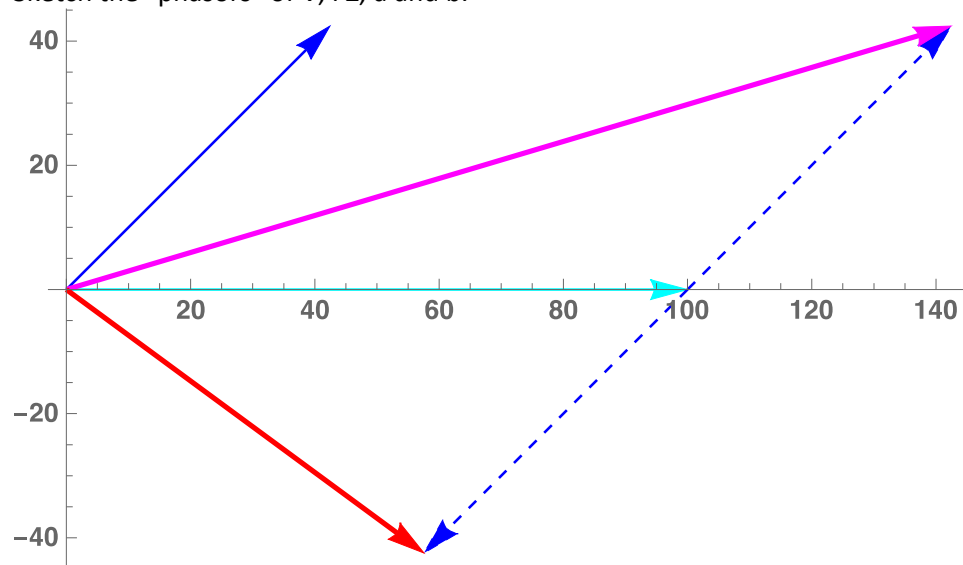- Sketch the "phasors" of  $V$ ,  $IZ$ ,  $a$  and  $b$ .




- At some plane in the  $50 \Omega$  system, a voltage of  $V = 100 \angle 0^\circ$  V and a current of  $I = 1.0 \angle -45^\circ$  A are measured.

- Calculate the corresponding forward and backward waves  $a$  and  $b$ .

$$a = \frac{V + IZ}{2} = \frac{100 V + (0.7 - j0.7) A 50 \Omega}{2} = (67.68 - j17.68) = 69.95 V e^{-j14.6^\circ}$$

$$b = \frac{V - IZ}{2} = \frac{100 V - (0.7 - j0.7) A 50 \Omega}{2} = (32.32 - j17.68) = 36.84 V e^{j28.68^\circ}$$

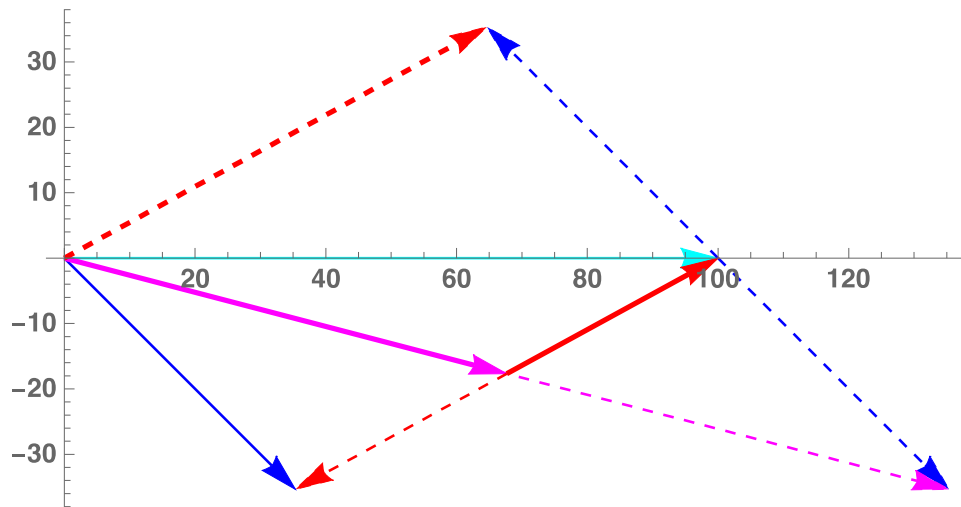- Sketch the “phasors” of V, I Z, a and b.



## 6.) Scaling laws

A cavity shall be scaled from existing designs for a frequency  $f_x = 318.32$  MHz and  $C_x = 10$  pF.

There are three test designs, with the following parameters:

Cavity	$f_{res}$ / MHz	$C$ / pF	$Q$	Diameter / mm
A	100	7.957	10000	600
B	500	3.18	5000	200
C	3000	1.061	2000	25

### Questions:

1. Which cavity is suitable as reference design?

For the optimal candidate design, the parameter  $r/Q$  has to agree with the one calculated for the actual cavity. Using:

$$r/Q = \frac{1}{\omega C}$$

we find  $r/Q = 50$  for the scaled cavity,

and  $r/Q = 200$  (cavity A), 100 (cavity B), 50 (cavity C) for the three design candidates.

Therefore, **cavity C** is chosen for scaling.

2. Calculate the diameter of the new design.

All physical dimensions of the cavity scale proportional to  $\lambda \propto 1/f$ .

$$D_x = D \frac{f}{f_x} = 0.236 \text{ m}$$

3. Calculate the expected  $Q$  factor for the new design, provided it will be built out of the same material as the reference design.

Using the 3<sup>rd</sup> scaling law:

$$Q \frac{\delta}{\lambda} = \text{const.}$$

we find  $Q \propto \lambda/\delta$ , with the skin depth  $\delta$  decreasing linear with the frequency  $f$ :

$$\delta = \sqrt{\frac{1}{\pi f \mu \sigma}} \propto \frac{1}{\sqrt{f}} \propto \sqrt{\lambda}$$

This results in:

$$Q \propto \sqrt{\lambda} \propto \frac{1}{\sqrt{f}} \Rightarrow Q_x = Q \sqrt{\frac{f}{f_x}} = 6140$$

## 7.) Thermal expansion and scaling laws

An accelerator cavity heats up under high RF power load.

The cavity used is constructed from a material having a:

thermal expansion coefficient:  $\Delta l/l = 20e-6/^{\circ}\text{C}$  (per degree Centigrade)

thermal resistivity coefficient:  $\Delta\rho/\rho = 4e-3/^{\circ}\text{C}$  (per degree Centigrade)

At room temperature the cavities resonance frequency is  $f_1 = 100$  MHz and has a 3-dB bandwidth of  $BW_1 = 100$  kHz.

Under RF power the cavity temperature increases by  $100$   $^{\circ}\text{C}$  (subscripts 2 apply).

### Questions:

Determine

- the ratio  $\lambda_2/\lambda_1$   
The wavelength  $\lambda$  scales proportional with the cavity dimension  $d$ , because  $\lambda$  is inverse proportional to  $f$ . Therefore:

$$\frac{\lambda_2}{\lambda_1} = \frac{d_2}{d_1} = \frac{d_1 \left(1 + \frac{\Delta l}{l} \Delta T\right)}{d_1} = 1 + \frac{\Delta l}{l} \Delta T = 1.002$$

- the ratio  $L_2/L_1$   
The characteristic impedance  $\sqrt{L/C} = R/Q$  stays constant, therefore:

$$\frac{L_2}{L_1} = \frac{R/Q}{\omega_2} = \frac{\omega_1}{R/Q} = \frac{\omega_1}{\omega_2} = \frac{\lambda_2}{\lambda_1} = 1.002$$

- the ratio  $C_2/C_1$   
Similar to the previous we get:

$$\frac{C_2}{C_1} = \frac{1}{R/Q\omega_2} = \frac{R/Q\omega_1}{1} = \frac{\omega_1}{\omega_2} = \frac{\lambda_2}{\lambda_1} = 1.002$$

- the ratio  $Q_2/Q_1$  (hint: the skin depth  $\delta$  is proportional to  $\sqrt{\rho/f}$ )  
The quality factor  $Q \propto \lambda_0/\delta$ , and the skin depth follows  $\delta \propto \sqrt{\rho/f}$ , therefore:



$$\frac{Q_2}{Q_1} = \frac{\text{const } \lambda_2}{\delta_2} = \frac{\delta_1}{\text{const } \lambda_1} = \frac{\lambda_2 \delta_1}{\lambda_1 \delta_2} = \frac{\lambda_2}{\lambda_1} \sqrt{\frac{\rho_1 f_2}{\rho_2 f_1}} = \frac{\lambda_2}{\lambda_1} \sqrt{\frac{\rho_1 \lambda_1}{\rho_2 \lambda_2}} = \sqrt{\frac{\rho_1 \lambda_2}{\rho_2 \lambda_1}} = 1.1844$$

with:  $\rho_1/\rho_2 = 1 + \Delta\rho/\rho \Delta T = 1.4$

- the resonance frequency  $f_2$  under load

$$\frac{f_2}{f_1} = \frac{\lambda_1}{\lambda_2} \Rightarrow f_2 = \frac{f_1}{\lambda_2/\lambda_1} = 99.8 \text{ MHz}$$

- and the 3-dB bandwidth  $BW_2$  of the resonance under load

$$\Delta f_1 = \frac{f_1}{Q_1}, \Delta f_2 = \frac{f_2}{Q_2} \Rightarrow \frac{\Delta f_2}{\Delta f_1} = \frac{f_1 Q_1}{Q_2 f_1}$$

$$\Delta f_2 = \frac{f_2}{f_1} \frac{1}{Q_2/Q_1} \Delta f_1 = 84.26 \text{ kHz}$$