

# SQUIDs


EASISchool 3, Genova, Italy

Mikko Kiviranta

# Overview


- Kirchoff laws with superconductors
- Weak link - flux quantization
- One-junction rf-SQUID - MISSING
- Two-junction dc-SQUID from SET – SQUID dualism
- Overdamped dc-SQUID, analytic solution
- Realistic dc SQUID characteristics
- A detour to 3-junction interferometer
- Different bias conditions
- Input coil, magnetometers and gradiometers
- SQUID readout, Flux-locked loop

## Kirchoffs 1. law

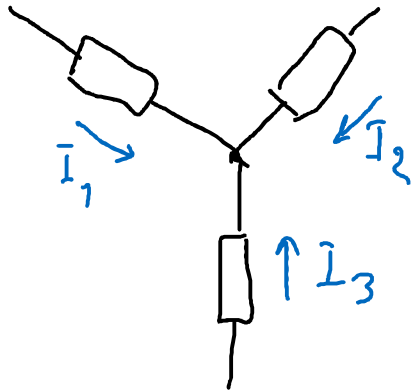


$$\sum_n I_n = 0$$

### Kirchhoff's 1. law

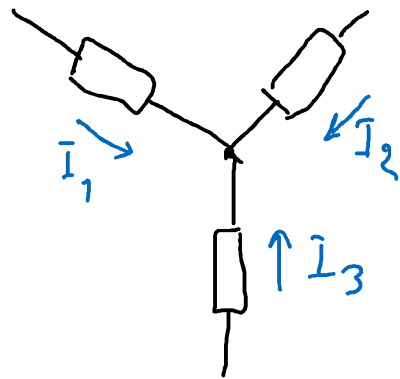



$$\sum_n I_n = 0$$

### Kirchhoff's 2. law

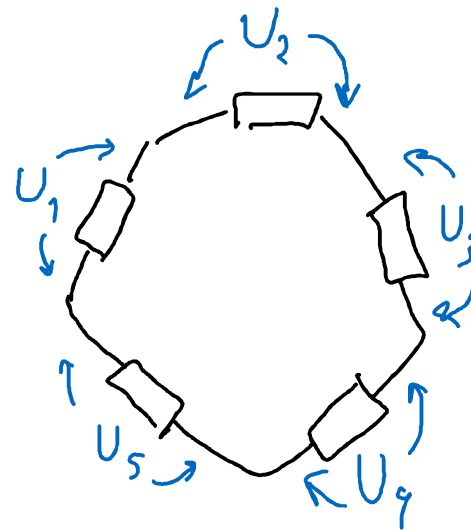


$$\sum_n U_n = 0$$

### Ohms law

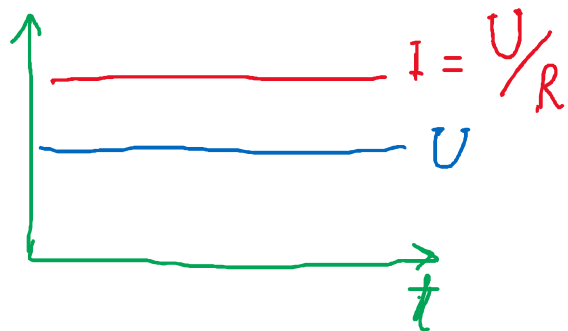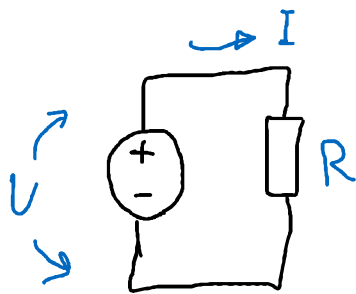


### Kirchoffs 2. law


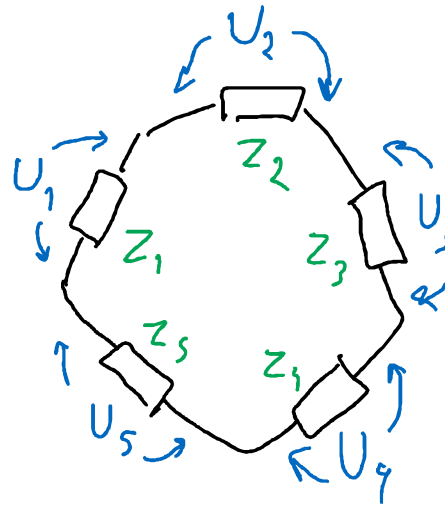





$$\sum_n U_n = 0$$




Ohms law

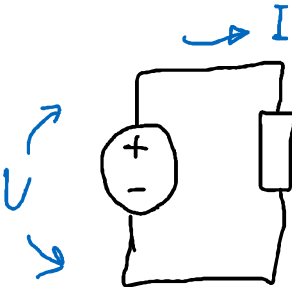



Superconductor  
?  
 $R = 0$  ?

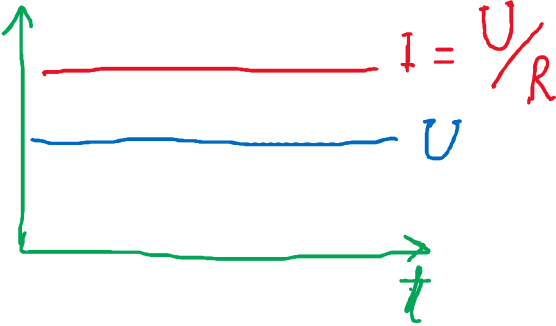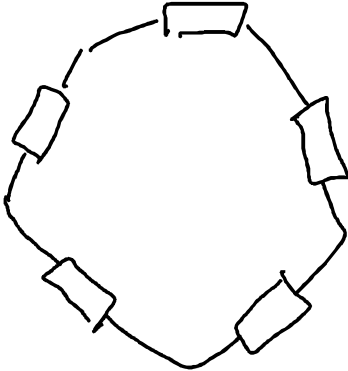

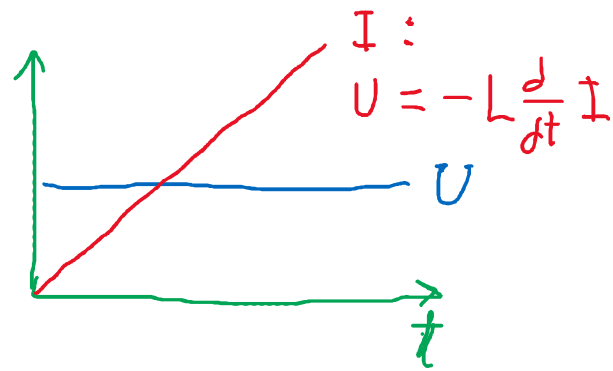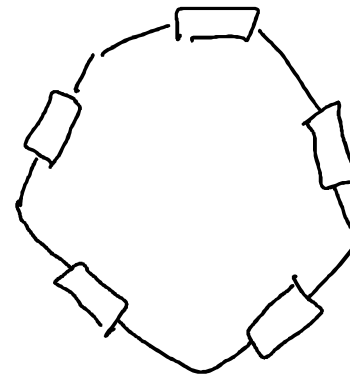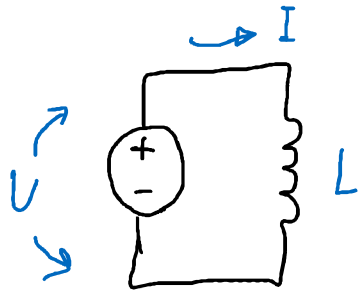

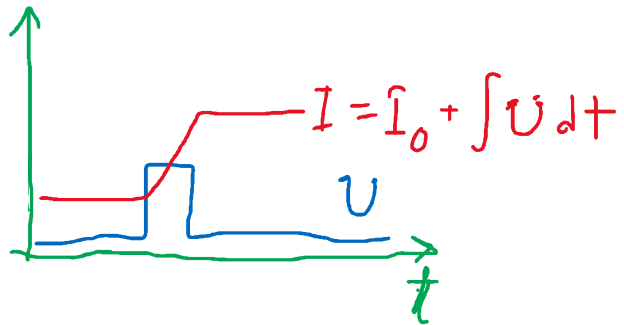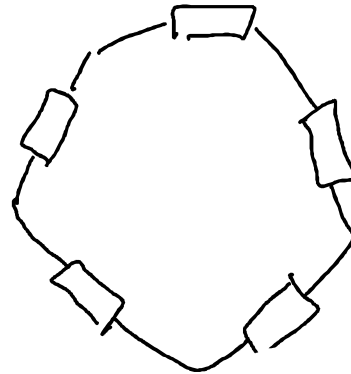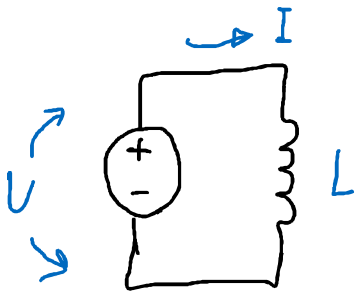




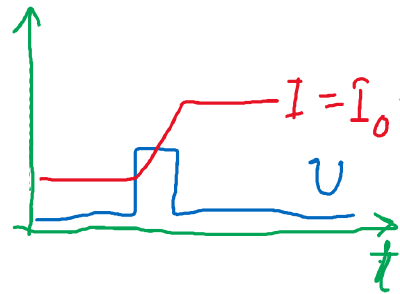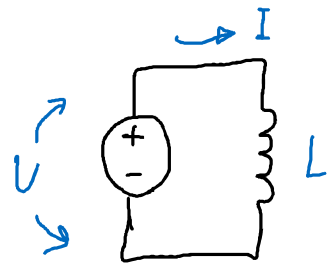

$$I = I_0 + \int U dt$$

Kirchoffs 2. law  
(integrated version)

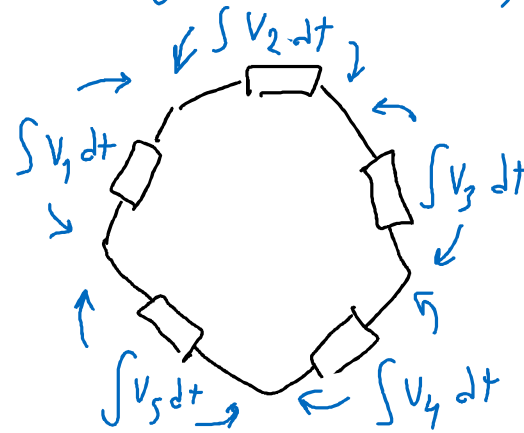


Integral of voltage

$$\int V(t) dt = \Phi$$


is called flux

Kirchoffs  
1. law

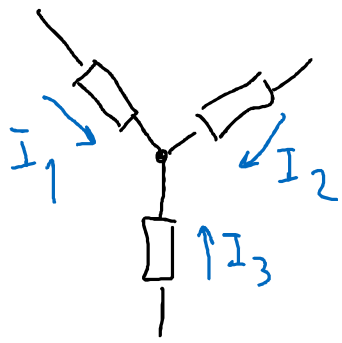

$$\sum_n I_n = 0$$


Kirchoffs 2. law  
(integrated version)

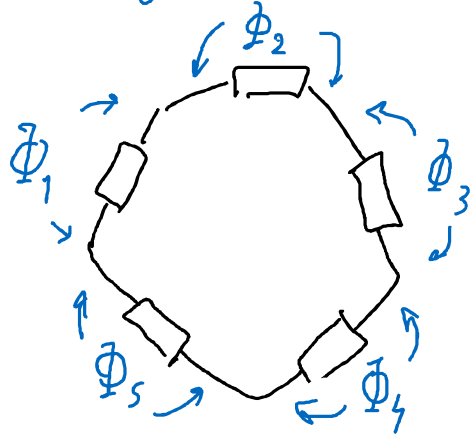


$$\sum_n \Phi_n = 0$$

Linear circuits are boring

Non-linear





Semi-  
conductors 

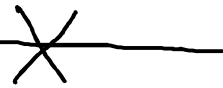Super-  
conductors 

# Linear circuits are boring

Non-linear

Two-port

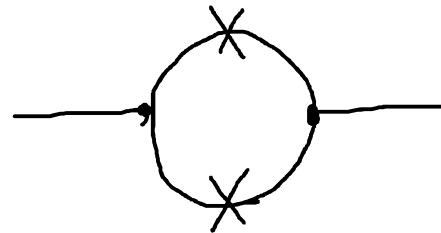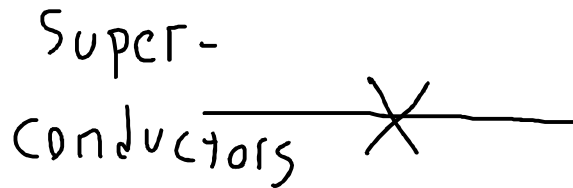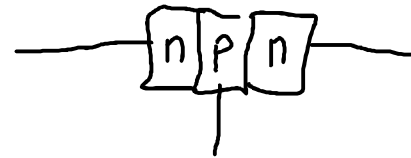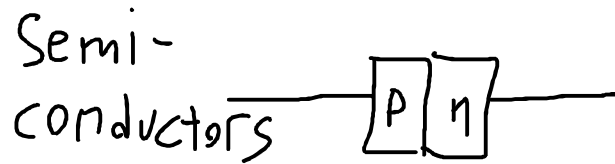

From Josephson relations




$$\begin{cases} I = I_c \sin \theta \\ U = \frac{\Phi_0}{2\pi} \frac{d}{dt} \theta \end{cases}$$

$$\Rightarrow U = \frac{\Phi_0}{2\pi} \cdot \frac{1}{\sqrt{1 - I^2/I_c^2}} \cdot \frac{d}{dt} I$$

← Derivative of arc sin


$$U = \frac{\Phi_0}{2\pi} \frac{1}{I_c \cos \theta} \frac{d}{dt} I$$

$L_J$ : Josephson inductance

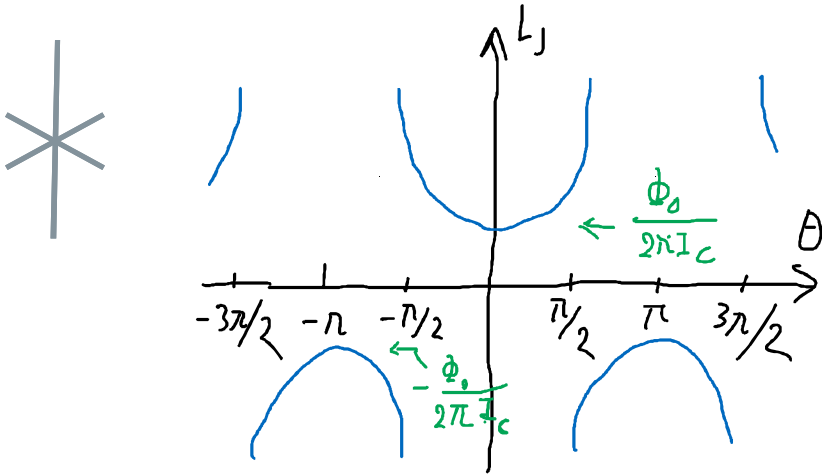

$$U = \frac{\phi_0}{2\pi} \underbrace{\frac{1}{I_c \cos \theta}}_{L_J} \frac{d}{dt} I$$

$L_J$ : Josephson inductance

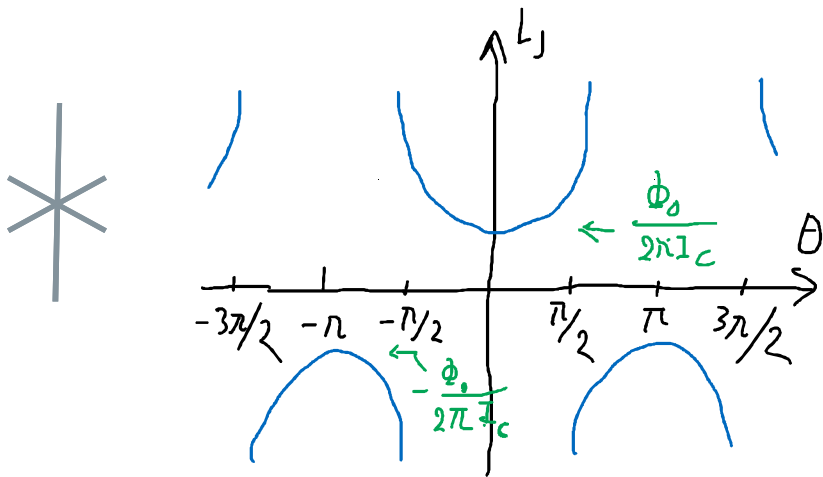

$$U = \underbrace{\frac{\Phi_0}{2\pi I_c}}_{L_J: \text{Josephson inductance}} \cos \theta \frac{d}{dt} I$$


Work done on the junction

$$\Delta E = W = \int U \cdot I \, d\theta$$

$$= - \frac{I_c \Phi_0}{2\pi} \cos \theta$$

is finite however


## Phase slip, a.k.a SFQ

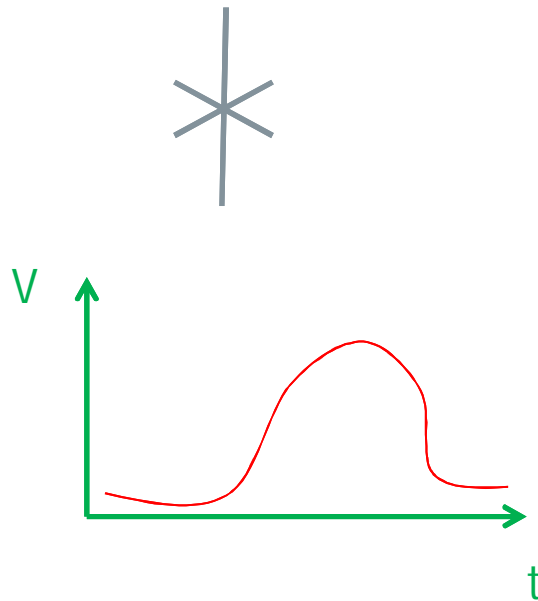

- When quantum phase advances by  $2\pi$  integral of voltage across junction is always 2.07 picosecond-millivolts.
- Such a pulse creates in any inductor the flux of 2.07 microampere-nanohenrys




Kirchoffs  
1. law

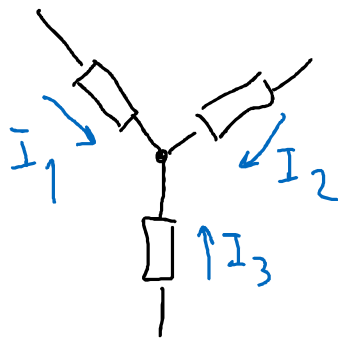

$$\sum_n I_n = 0$$

Kirchoffs 2. law  
(integrated version)

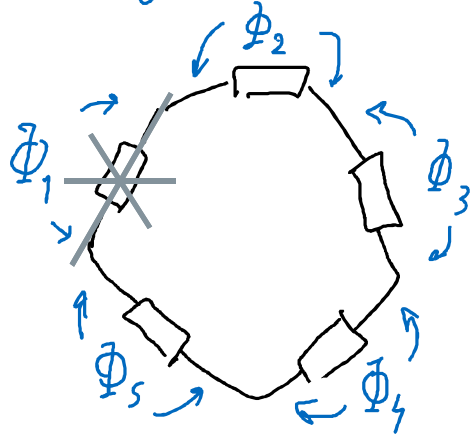


$$\sum_n \Phi_n = n\Phi_0$$


Version with  
weak links


# Single-junction SQUID





# Single electron transistor

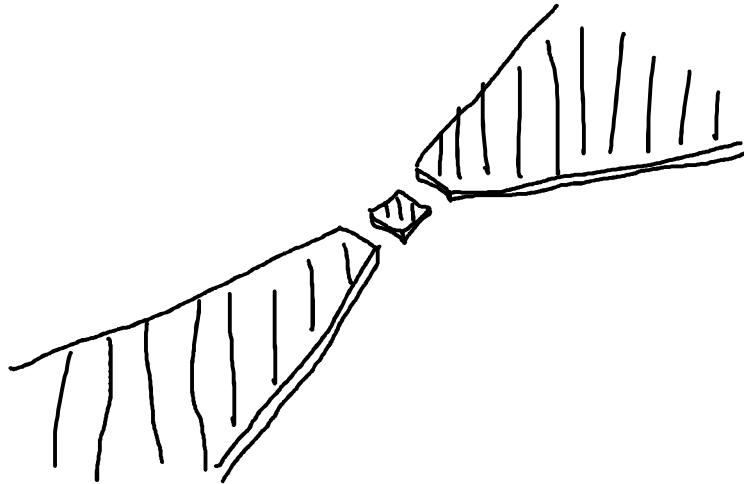


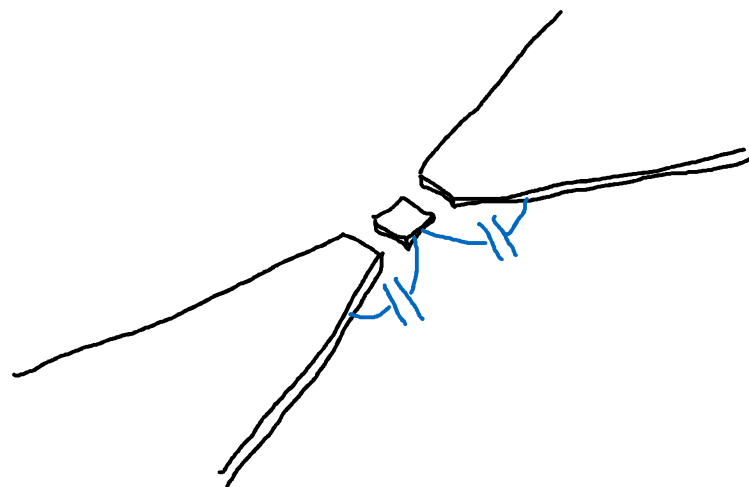

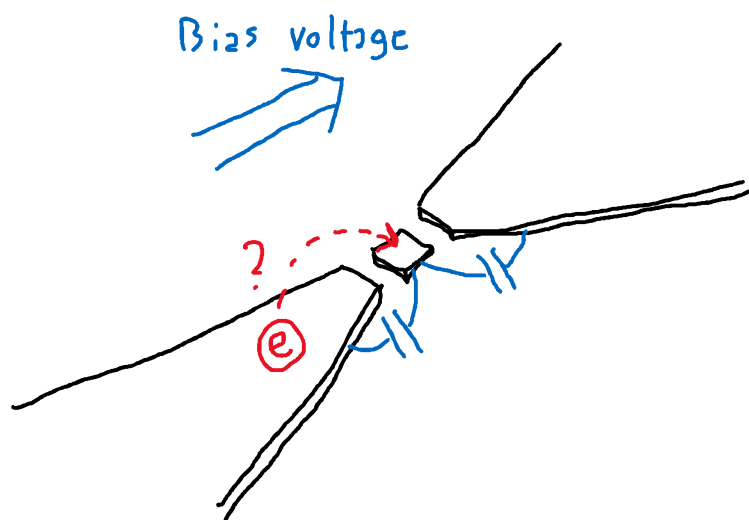

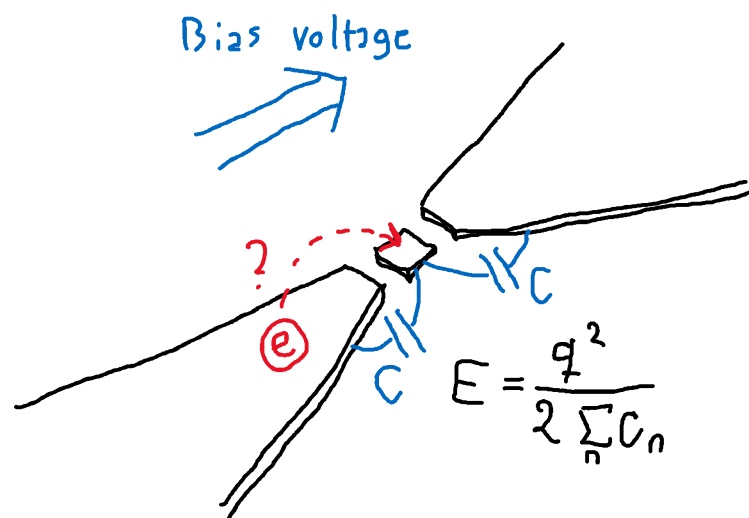


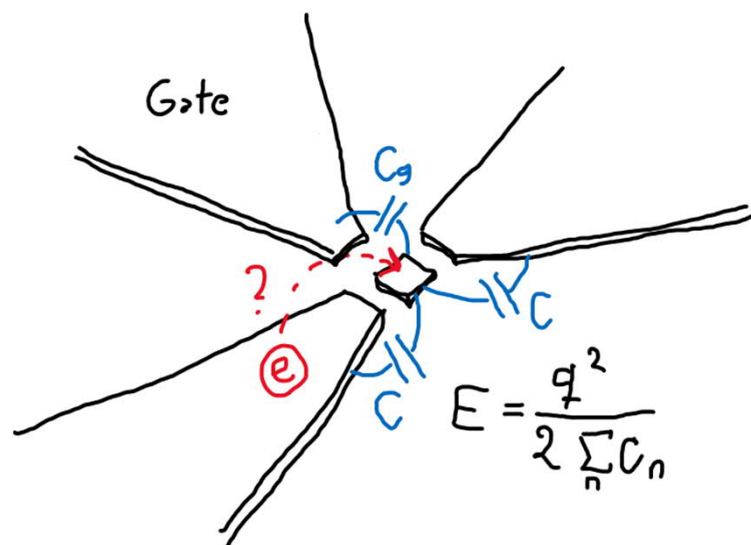

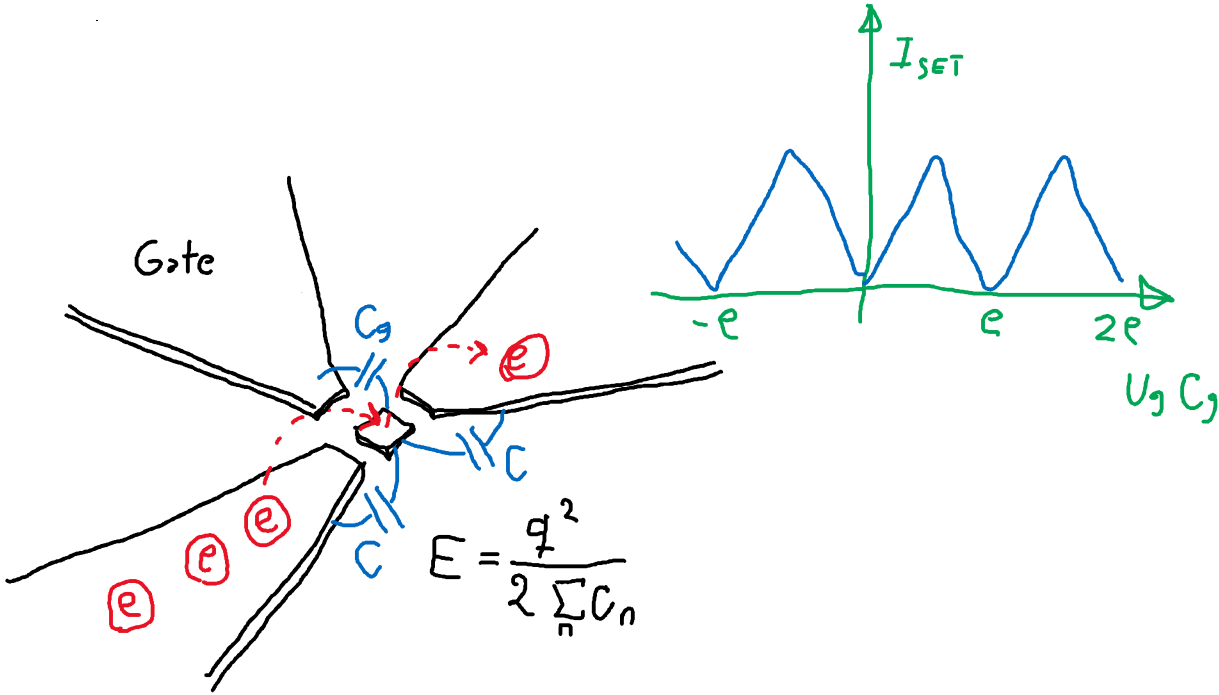





## Electrostatic dual of a SET

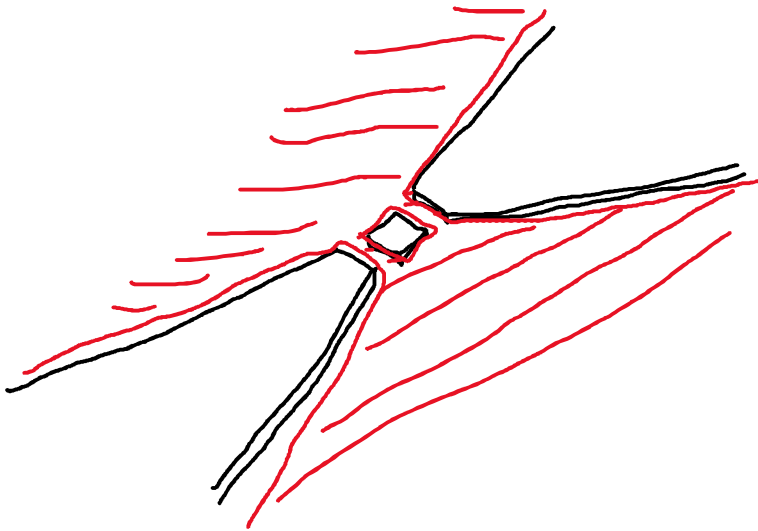


# Electrostatic dual of a SET

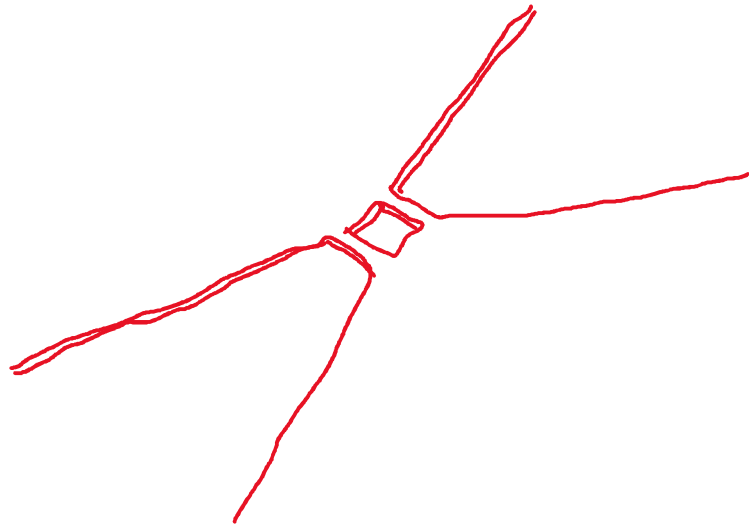


## Electrostatic dual of a SET

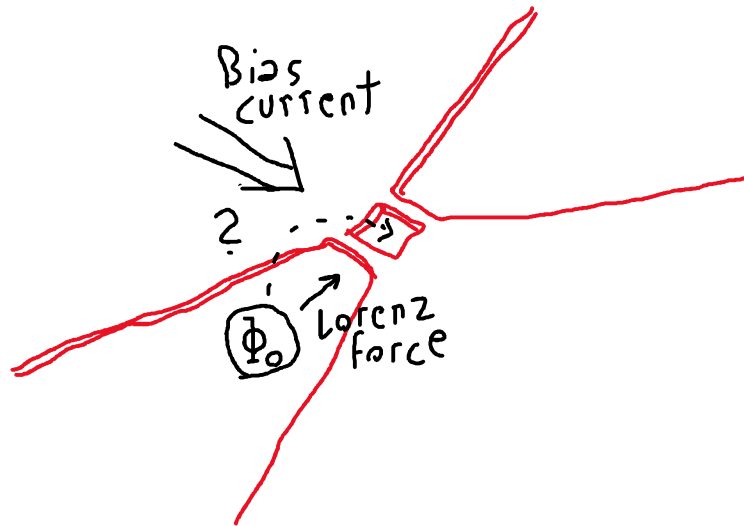


# Electrostatic dual of a SET

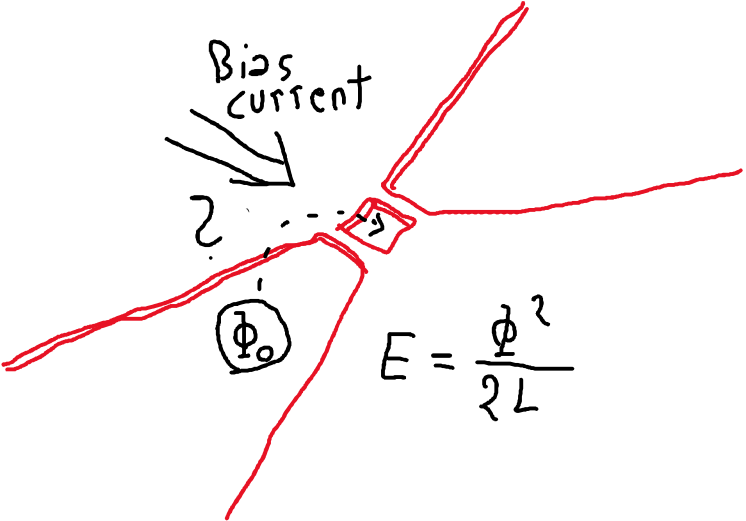


# Electrostatic dual of a SET

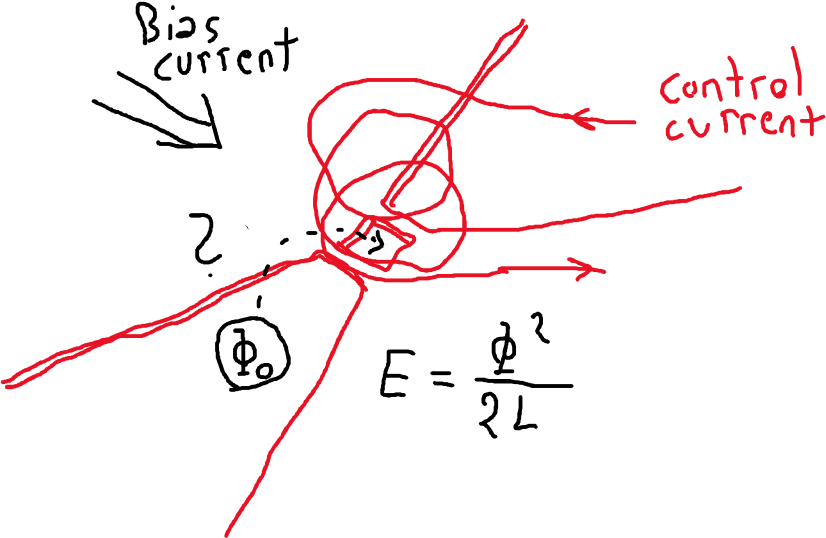

# Electrostatic dual of a SET = dc SQUID

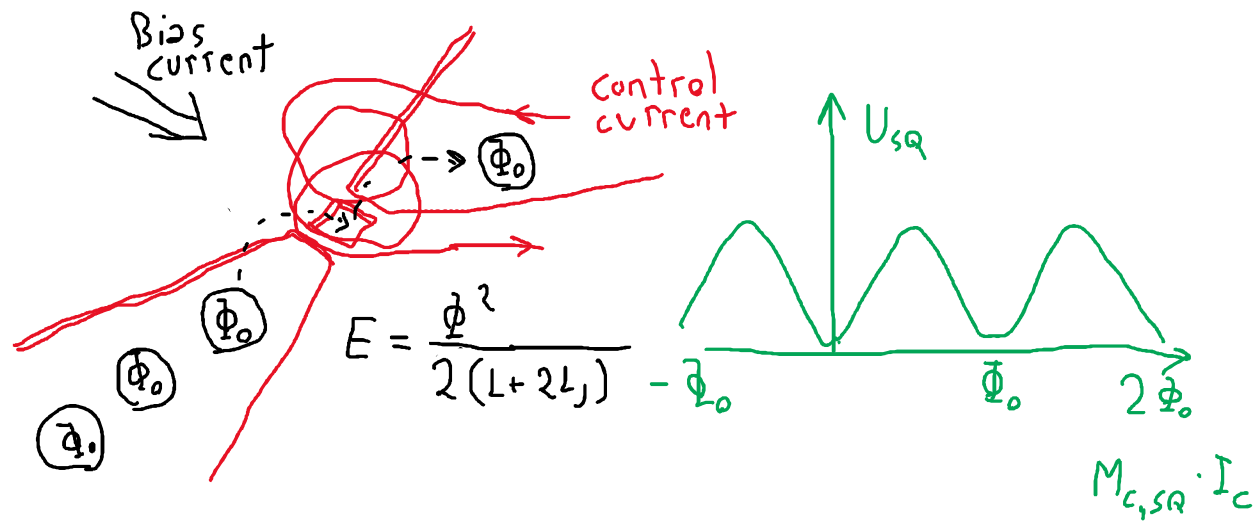

Lets take dc SQUID more quantitatively

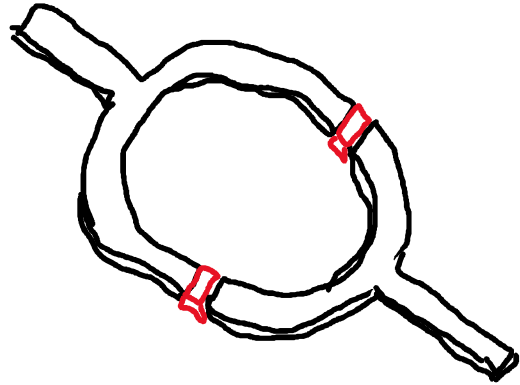


# Lets take dc SQUID more quantitatively



External flux  $\Phi$

Geometric inductance  $L_{sq}$

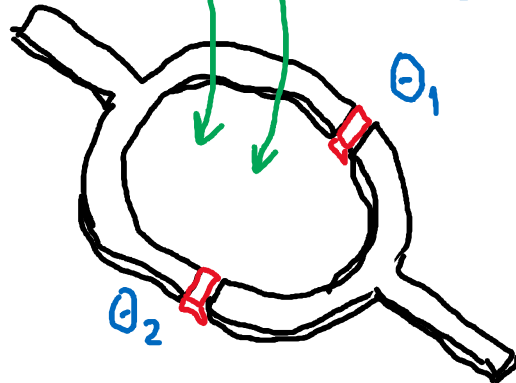


Josephson inductance  $L_J$



External flux  $\Phi_A$


Geometric inductance  $L_{sq}$

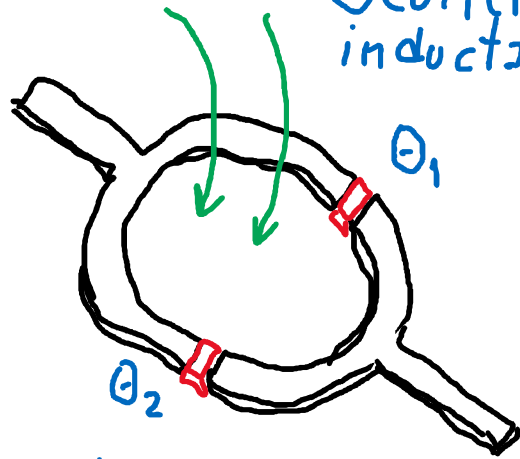

Josephson inductance  $L_J$

Limit  $L_{sq} \ll L_J$  :  
 Equation of motion  
 for  $\frac{1}{2}(\theta_1 + \theta_2)$  is the  
 same as the single JJ  
 whose crit. current is  
 not  $I_c$  but  $|\cos(\pi\Phi_A)| \cdot 2I_c$
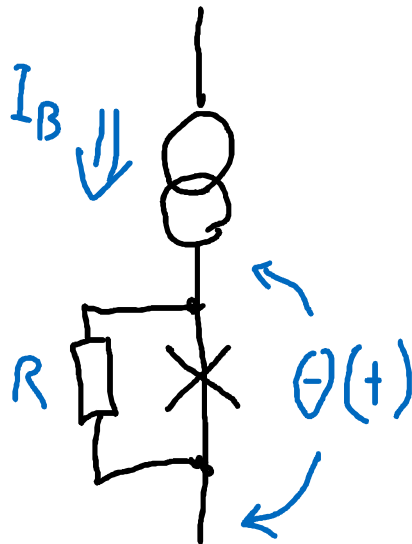
# Equation of motion of single J-junction




# Equation of motion of single J-junction


Dimensionless units

$$\lambda = I / I_c \quad \mu = U / R I_c \quad \tau = t \frac{2\pi R I_c}{\Phi_0}$$


---

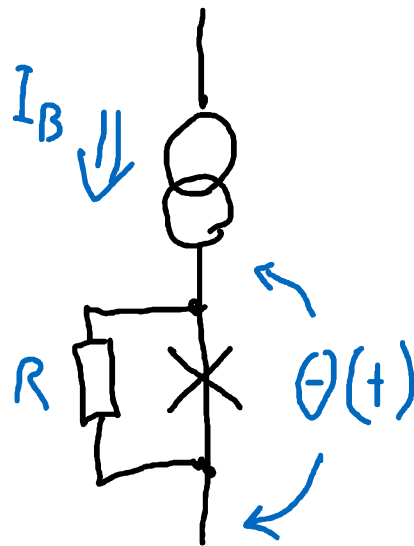
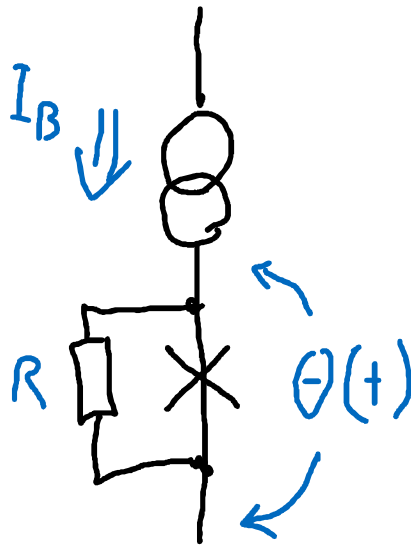
# Equation of motion of single J-junction




Dimensionless units

$$i = I / I_c \quad \mu = U / R I_c \quad \tau = t \frac{2\pi R I_c}{\Phi_0}$$


---
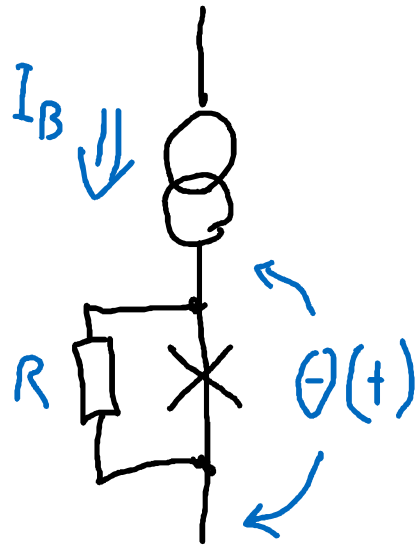
$$\frac{d}{dt} \theta = i_B - \sin \theta$$



Dimensionless units

$$\lambda = I / I_c \quad \mu = \frac{U}{RI_c} \quad \tau = t \frac{2\pi R I_c}{\Phi_0}$$

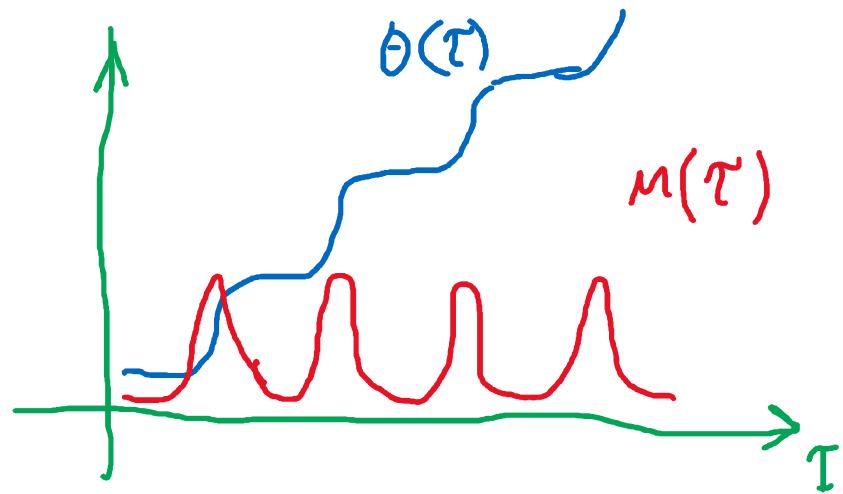
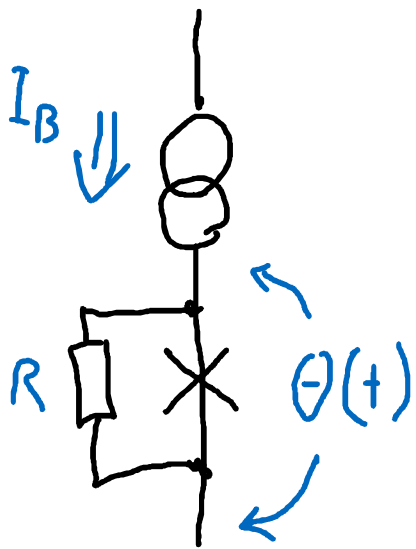

---

$$\frac{d}{dt} \theta = \lambda_B - \sin \theta$$

Asmaralozov-Larkin (or Maple):

$$\theta(t) = 2 \operatorname{atan}^{-1} \left[ \frac{\sqrt{\lambda_B^2 - 1}}{\lambda_B + 1} \operatorname{tanh} \left( \frac{1}{2} \sqrt{\lambda_B^2 - 1} t \right) \right] + \frac{\pi}{2}$$



$$\mu = \frac{d}{d\tau} \theta = \frac{\lambda_B^2 - 1}{\lambda_B + \cos(\sqrt{\lambda_B^2 - 1} \cdot t)}$$





Асмалязов-Ларкин (or Maple):


$$\theta(t) = 2 \tan^{-1} \left[ \frac{\sqrt{i_B^2 - 1}}{i_B + 1} \tanh\left(\frac{1}{2} \sqrt{i_B^2 - 1} t\right) \right] + \frac{\pi}{2}$$
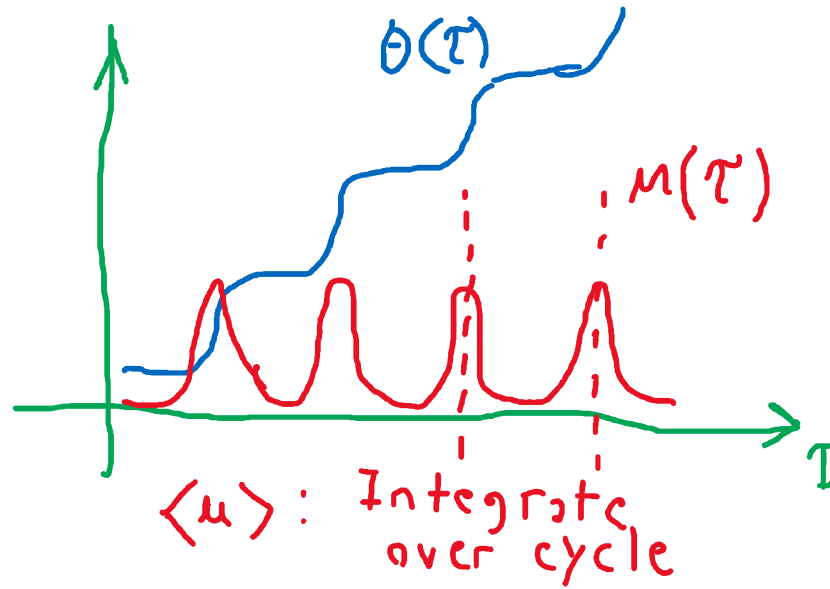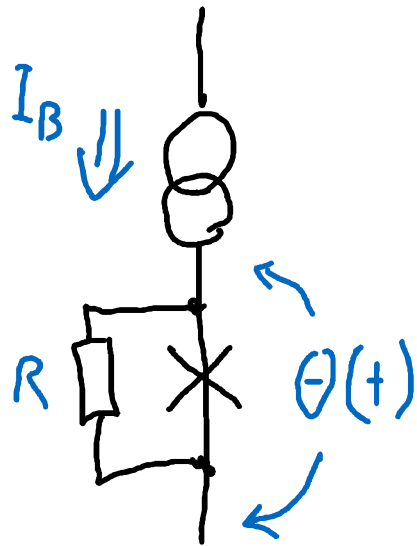
$$\mu = \frac{d}{d\tau} \theta = \frac{i_B^2 - 1}{i_B + \cos(\sqrt{i_B^2 - 1} \cdot t)}$$



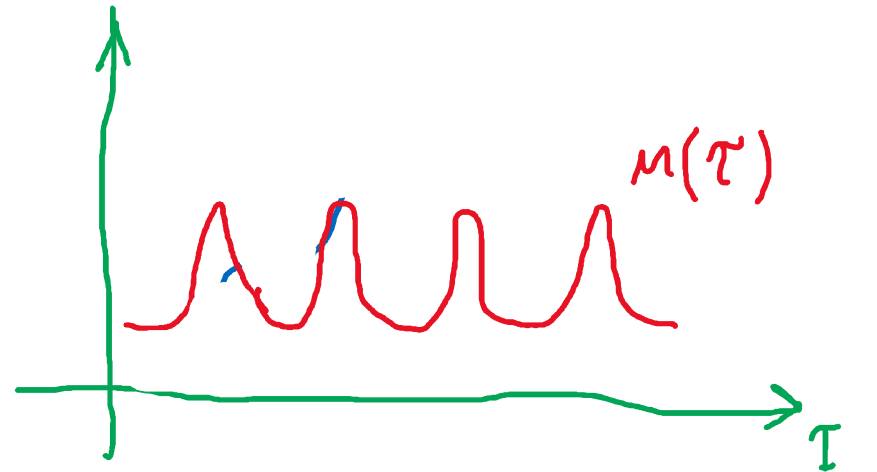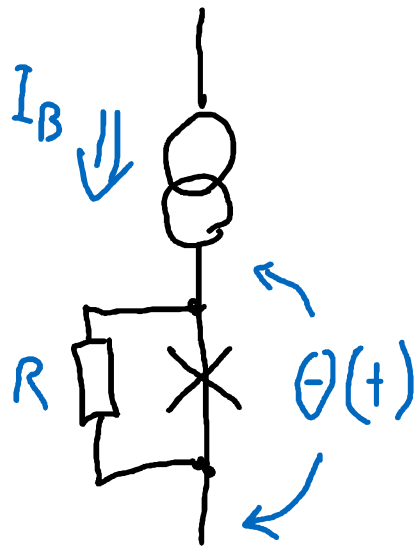

Back to dimensioned values


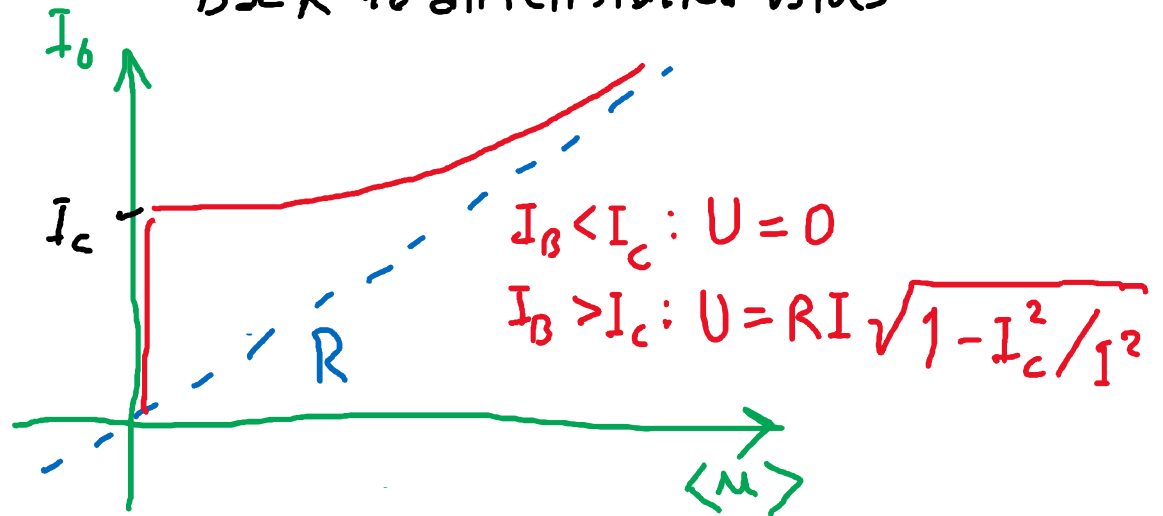




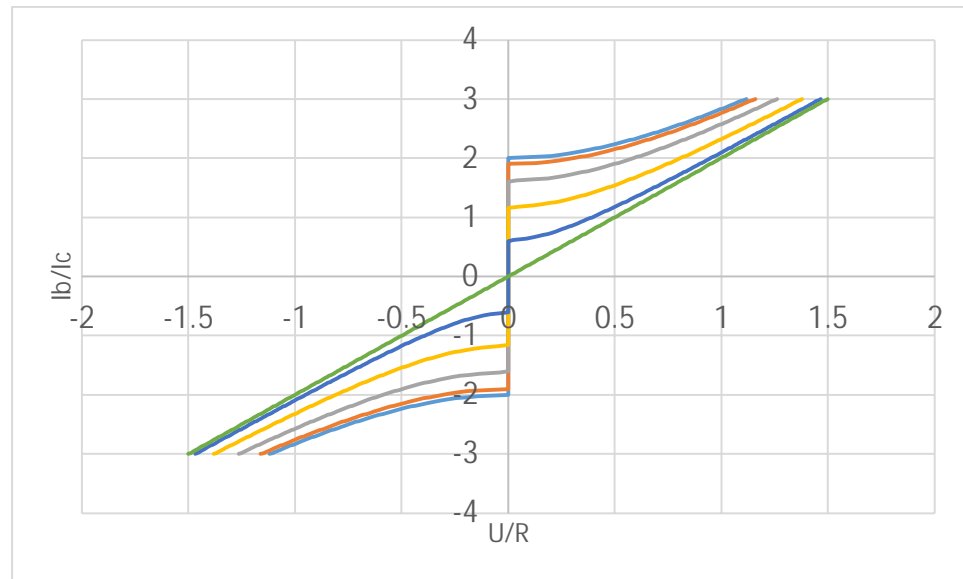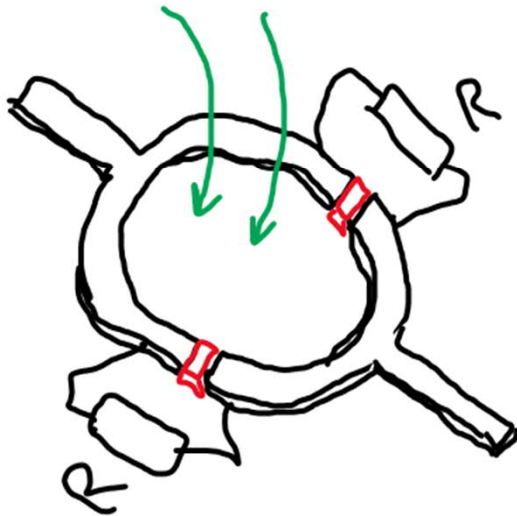
# DC SQUID is like single J-junction with flux-controllable critical current

External flux  $\Phi_A$

$$U = \frac{RI}{2} \sqrt{1 - \left( \frac{2I_c}{I} \cos \frac{\pi \Phi_A}{\Phi_0} \right)^2}$$


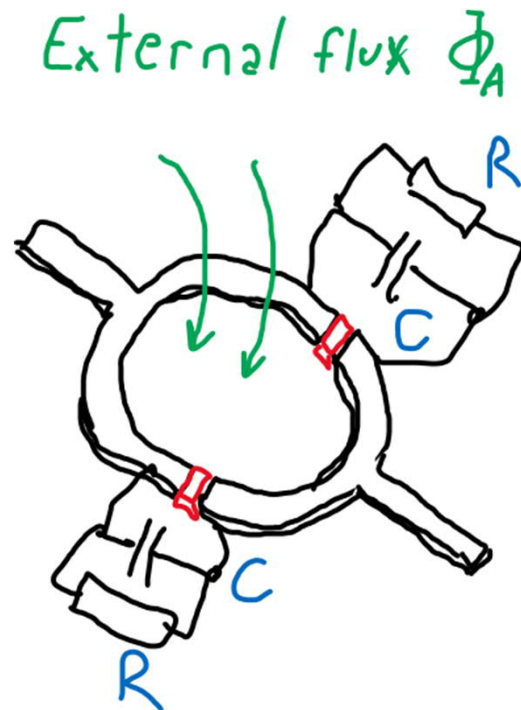
## Added complication: junction capacitance






- Makes characteristics hysteretic
- For single-valued response must add sufficiently small shunt resistors
- Johnson noise of the resistors is the main source of noise in dc SQUIDs

$$\beta_C = \frac{2\pi I_C C_J R_S^2}{\Phi_0} < 0.7$$

H. H. Zappe 1972, doi:10.1063/1.1662354
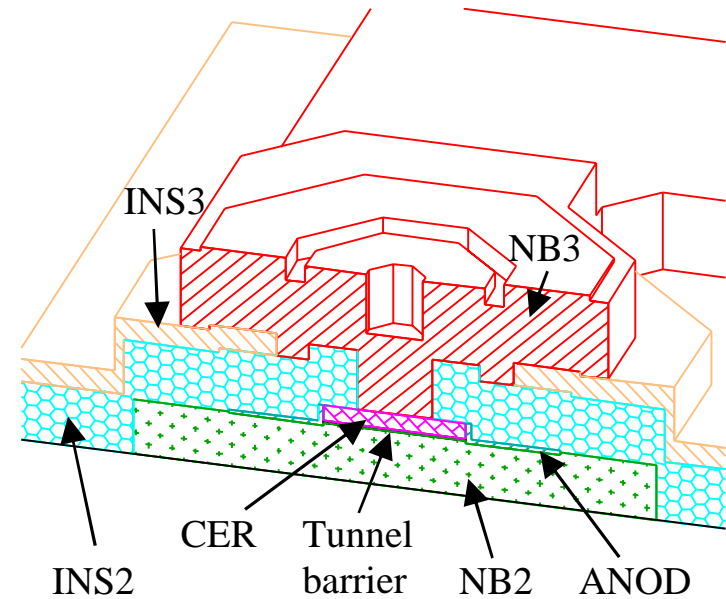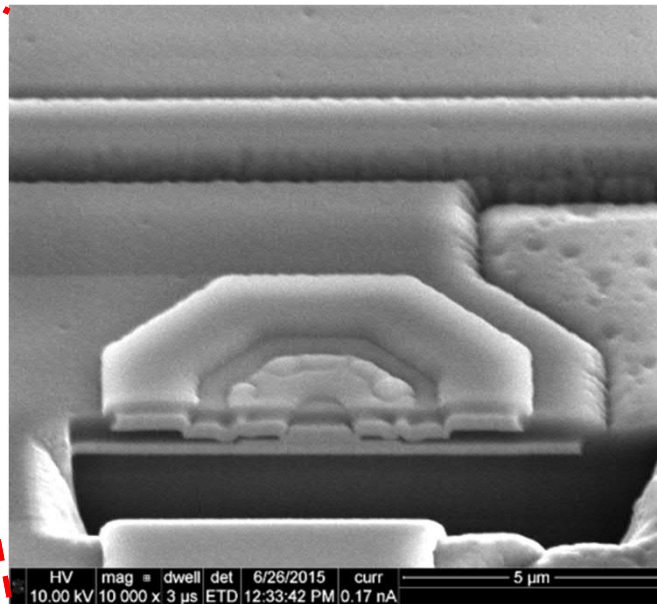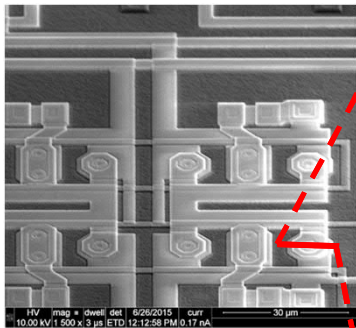
# Added complications: junction capacitance



# Phenomena due to junction capacitance



Josephson inductance forms an LC resonator

Inductance depends on oscillation amplitude -> anharmonicity

- Dynamical equations of DC SQUID.


$$\beta_c \frac{d^2 \nu}{d\tau^2} + \frac{d\nu}{d\tau} + \sin \nu \cos \phi = i$$

$$\beta_c \frac{d^2 \phi}{d\tau^2} + \frac{d\phi}{d\tau} + \cos \nu \sin \phi + \frac{2}{\beta_L} (\phi - \phi_a) = 0$$

External flux


$$\nu = \frac{\delta_1 + \delta_2}{2} \quad \phi = \frac{\delta_1 - \delta_2}{2}$$

$$\beta_L = \frac{2\pi L I_c}{\Phi_0}$$

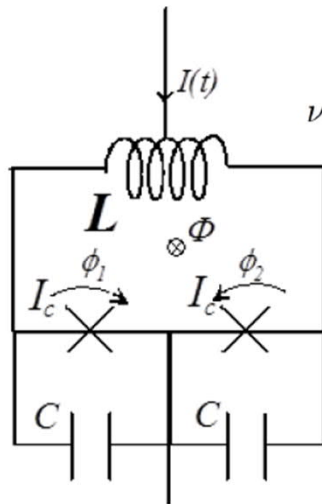



05/10/2020
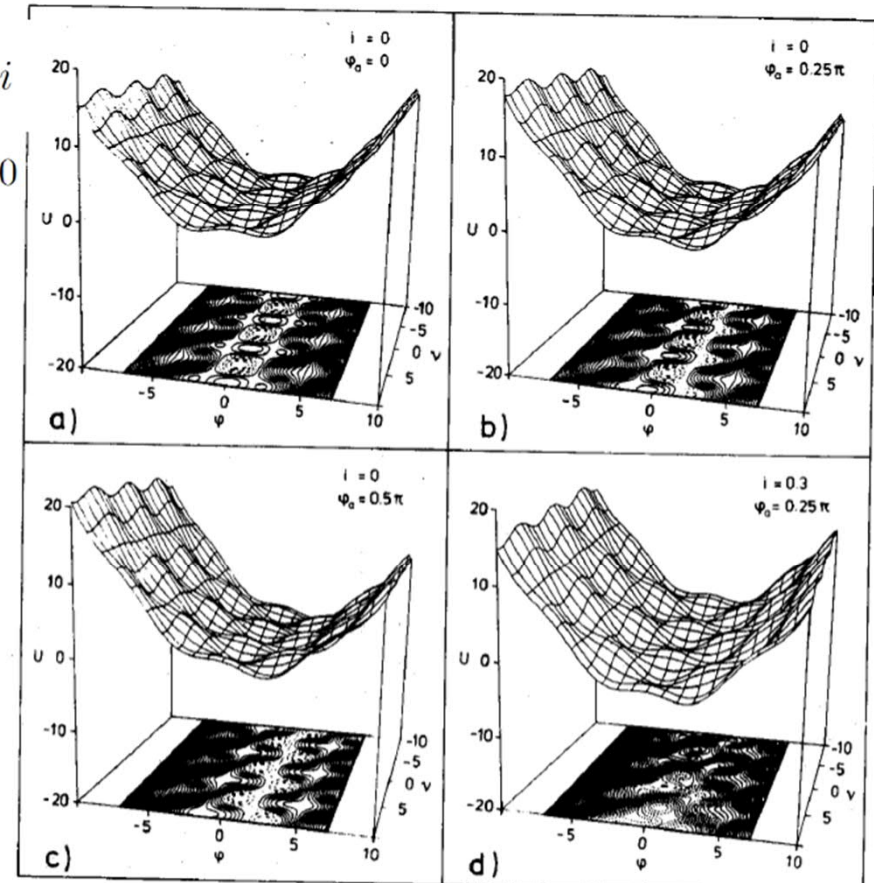
$$U(\nu, \phi) = \frac{1}{\beta_L} (\phi - \phi_a)^2 - i\nu - \cos \nu \cos \phi$$



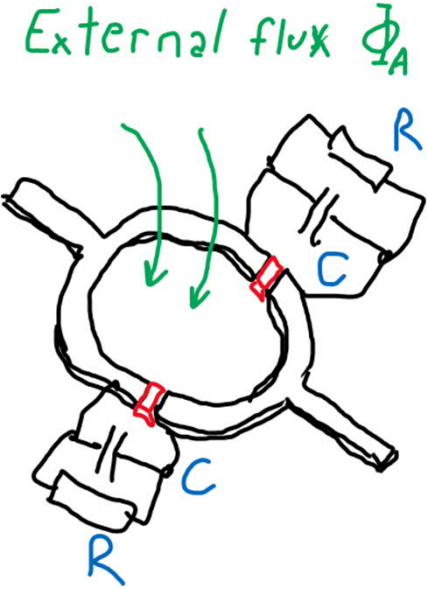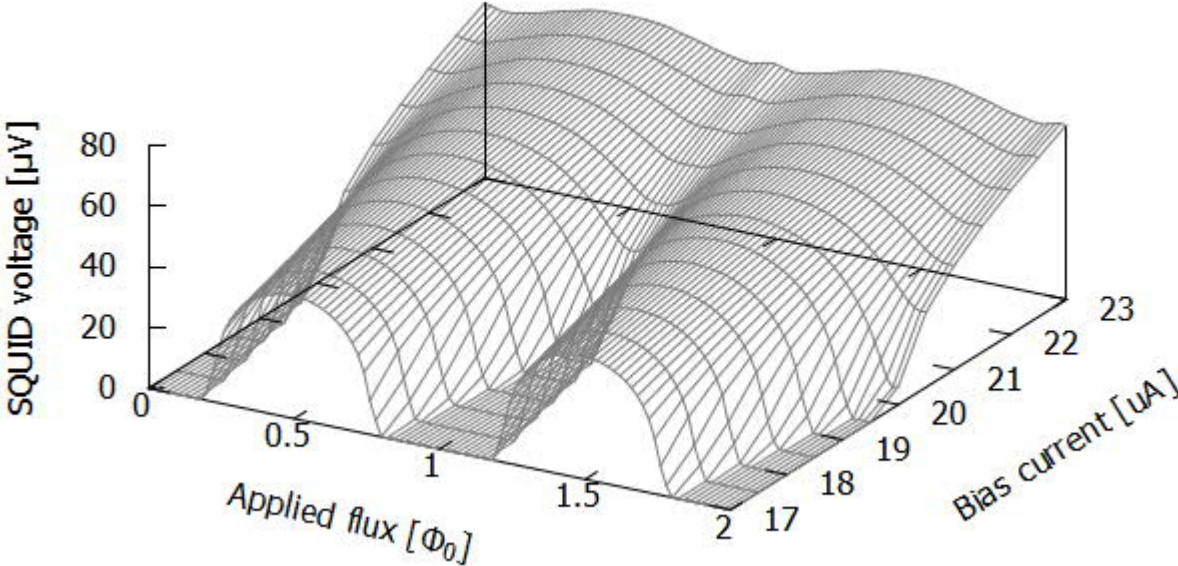
# Realistic dc SQUID characteristics


$$\beta_C = \frac{2\pi I_C C_J R_S^2}{\Phi_0} = 0.7 \quad \beta_L = \frac{2\pi L_S Q I_C}{\Phi_0} = 1.0$$



# Current bias

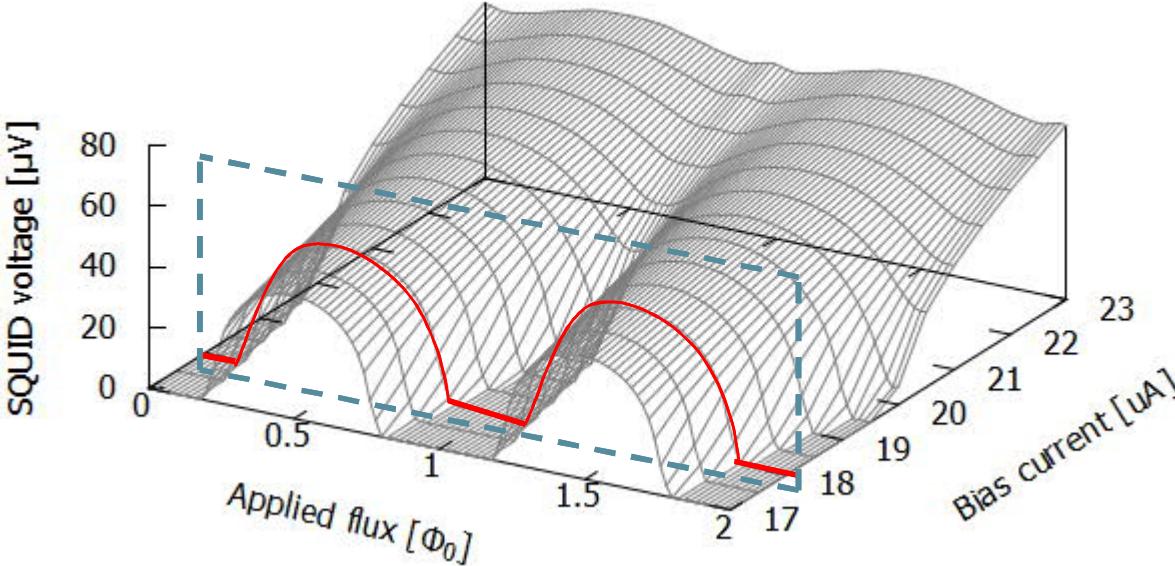


# Current bias, $I_B < 2I_C$

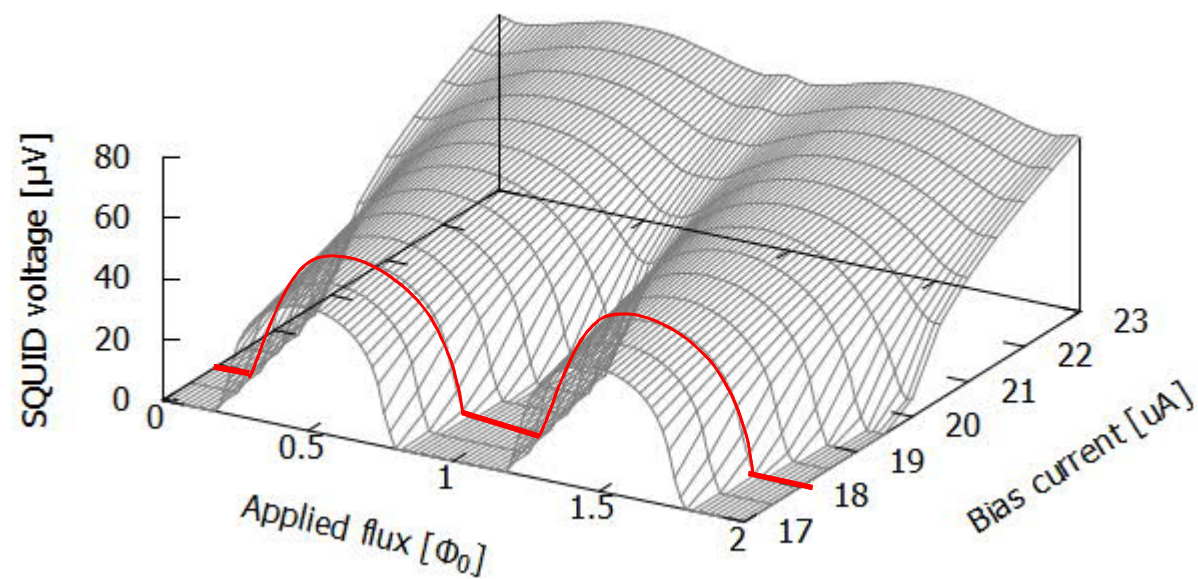


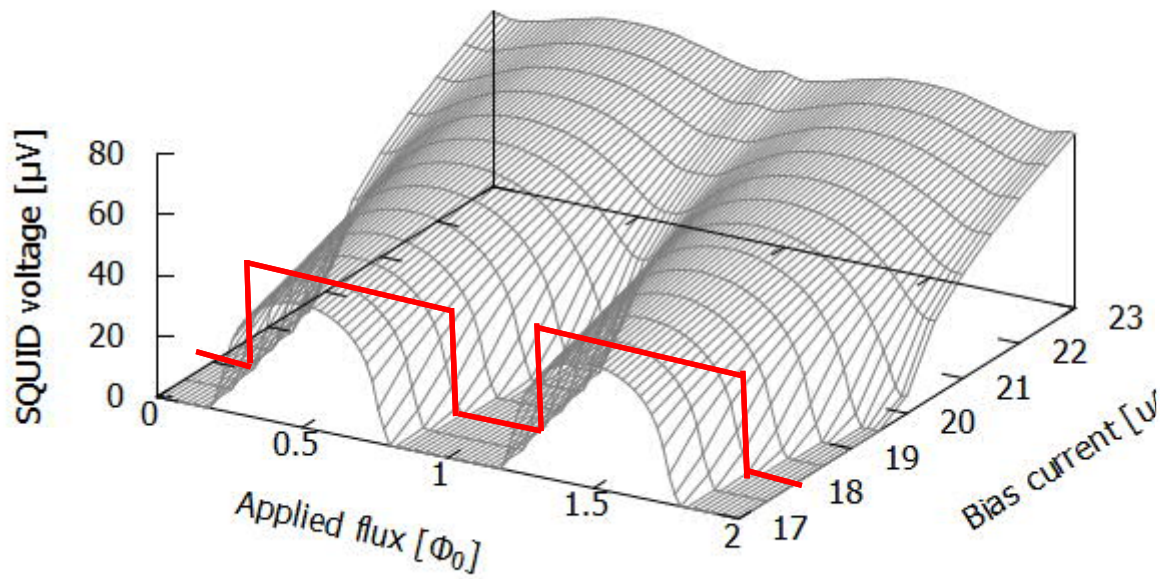
# Detour: 3-junction interferometer - Zappe switch



H. H. Zappe, IEEE Transactions on Magnetics, 1977

05/10/2020 VTT – beyond the obvious



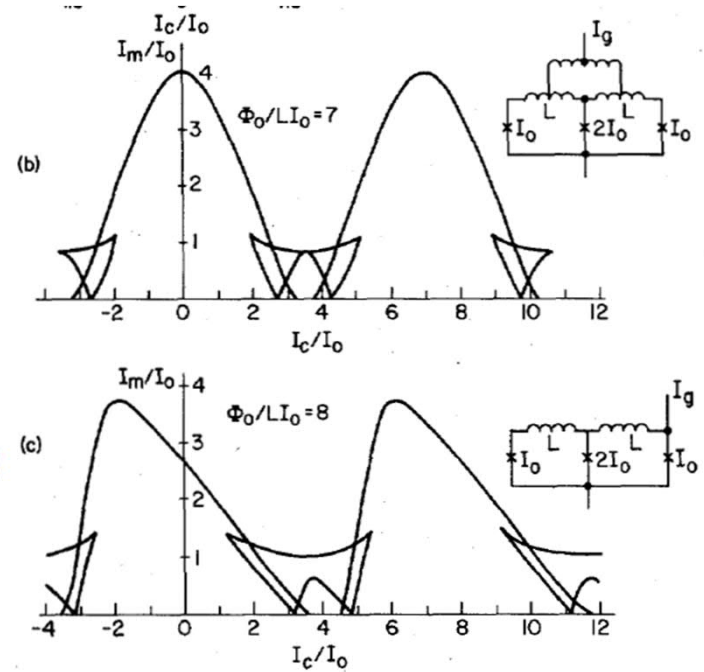


Fig. 5. Threshold curves of quantum interference devices. (a) is a two junction device. (b) and (c) are three junction interferometers with symmetric and asymmetric supply current feed respectively.


# Current bias, $I_B > 2I_C$

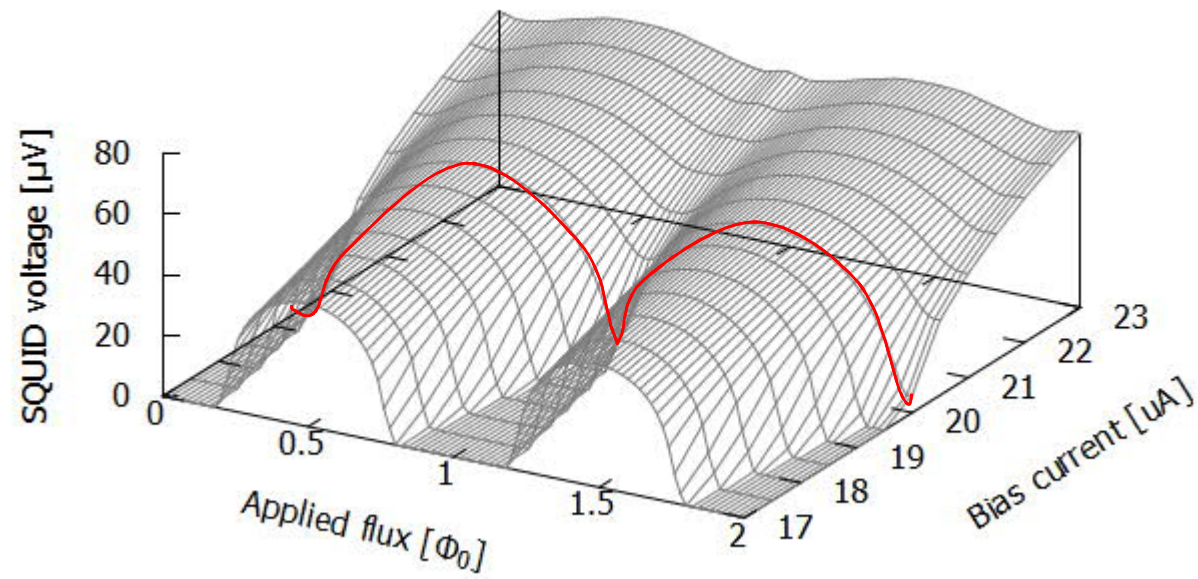


Current bias,  $I_B > 2I_C$

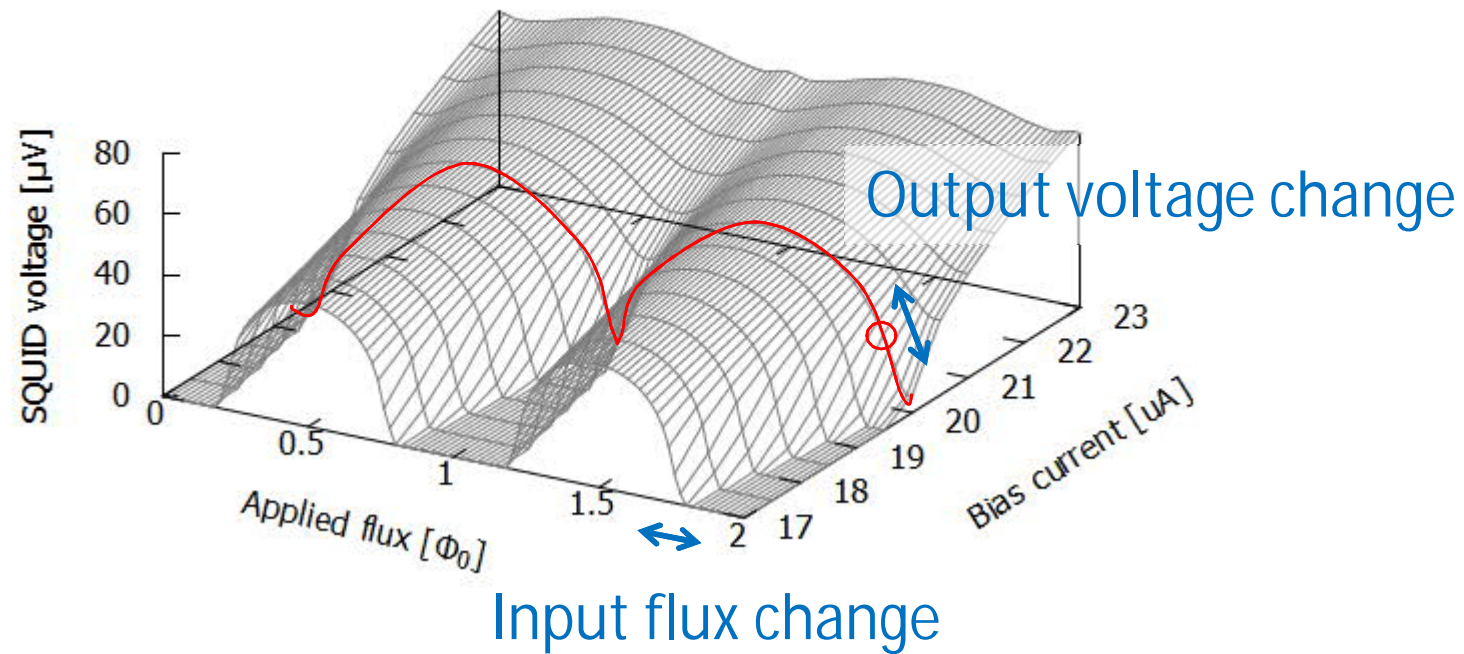


# Voltage bias

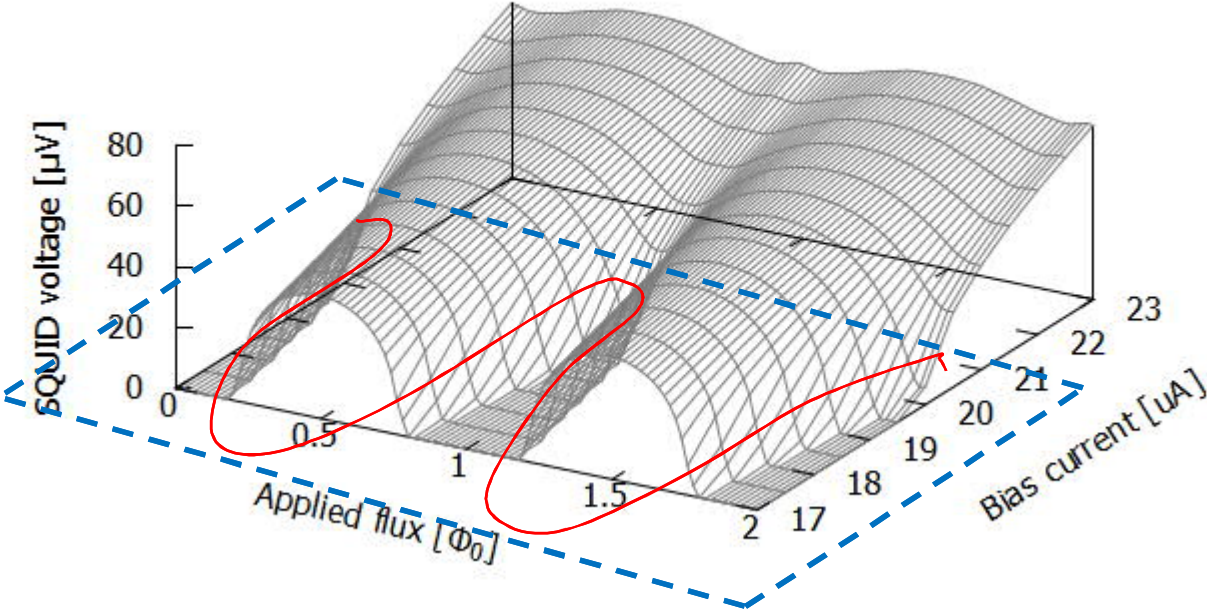


# Voltage biased SQUID characteristics

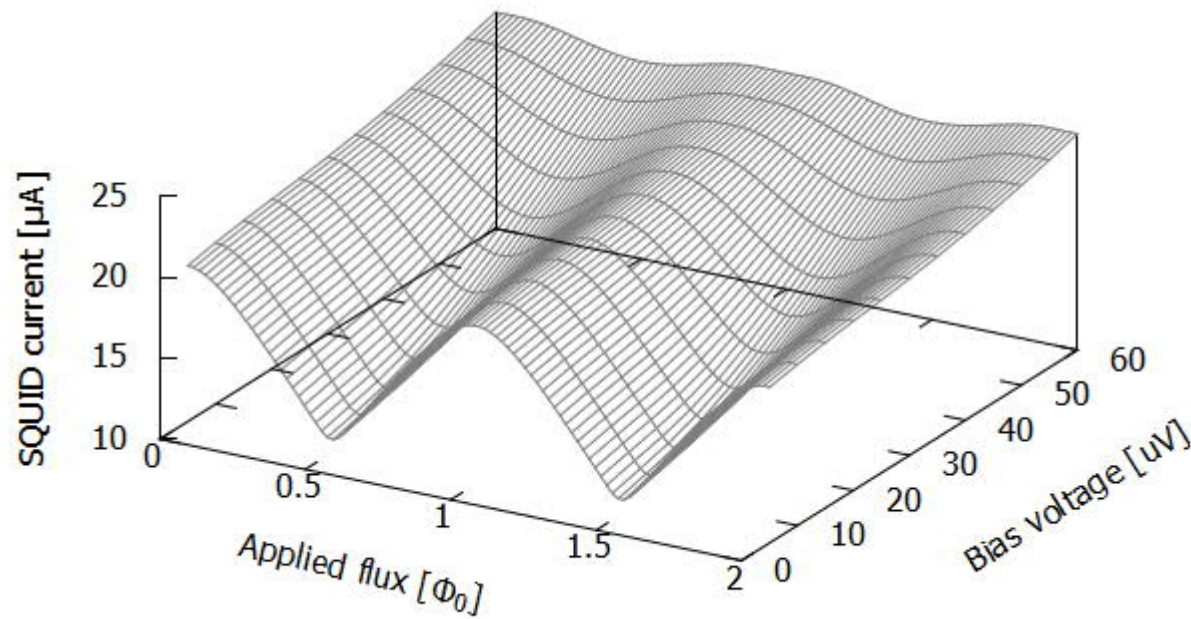


# Flux noise ( with current bias)

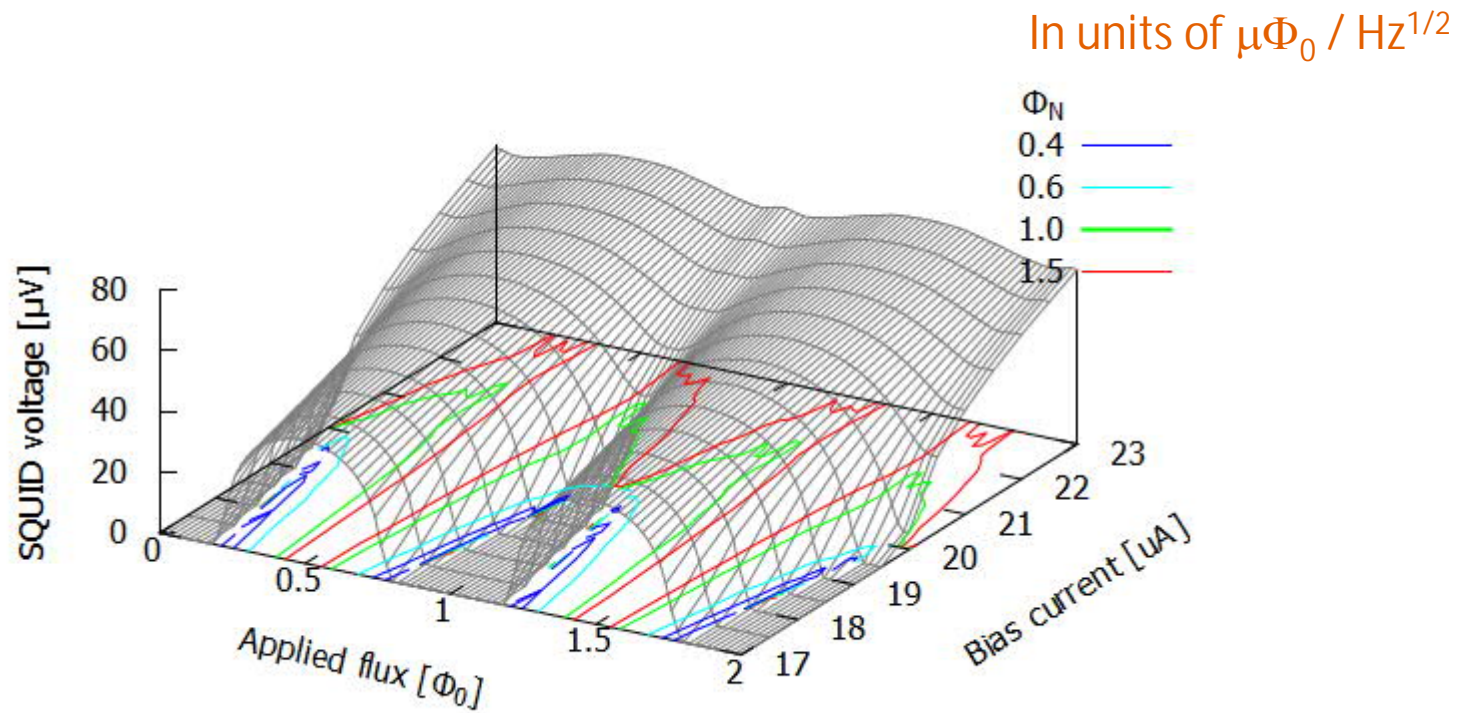

# Flux noise (with voltage bias)

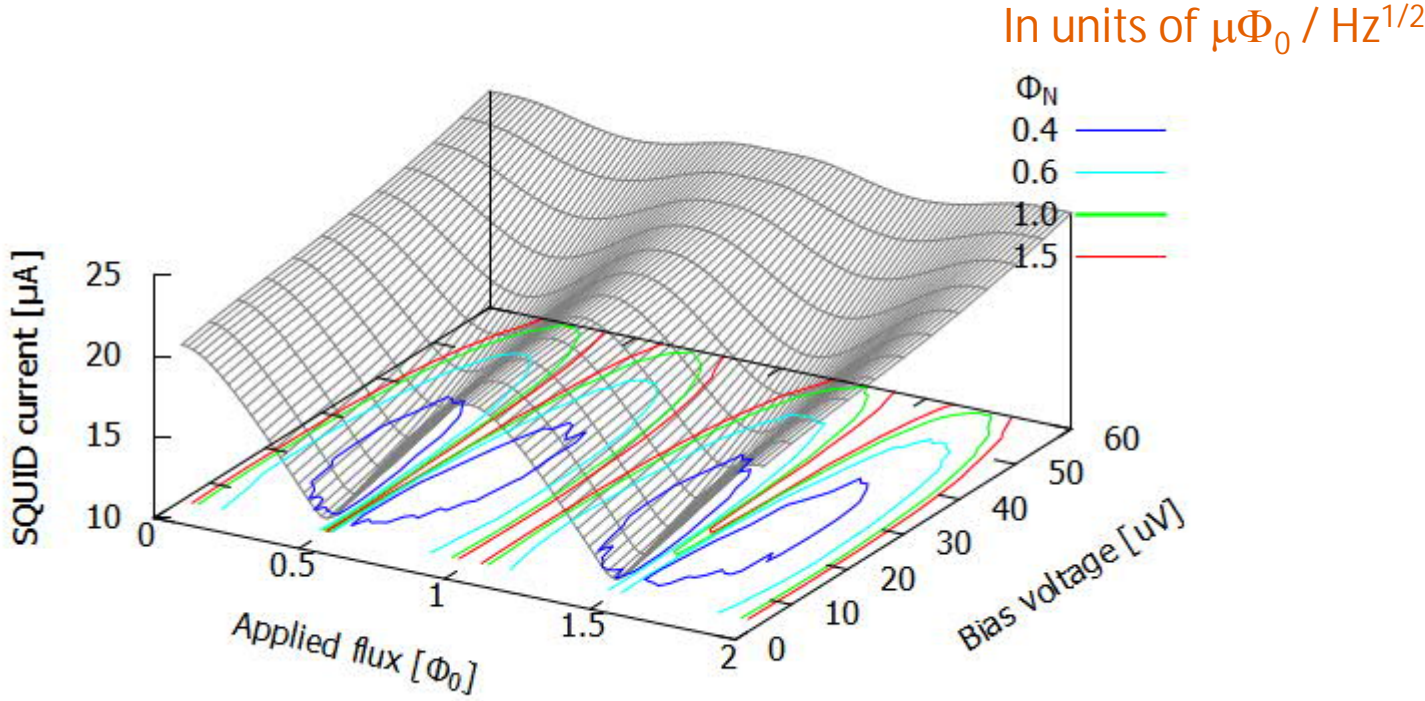


# Matched bias

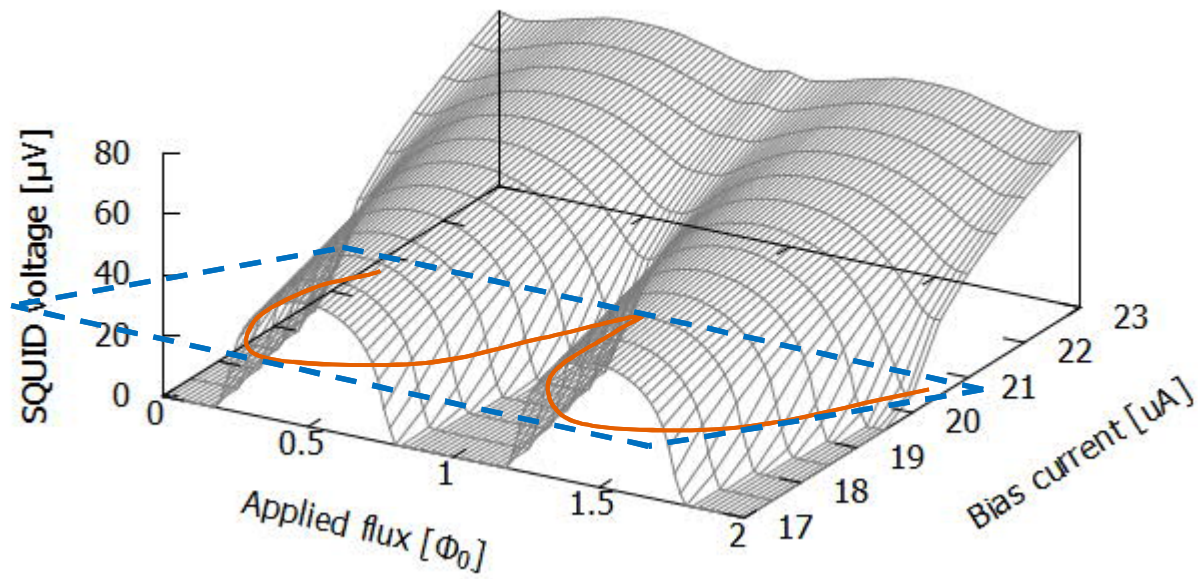


Load line:  
 $0 \Omega$  – voltage bias  
 $\infty \Omega$  – current bias  
SQUID  $R_D$  – matched bias




# Dc SQUID as a magnetometer

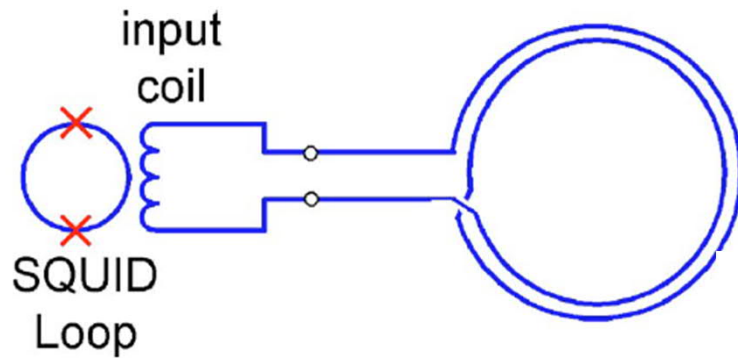

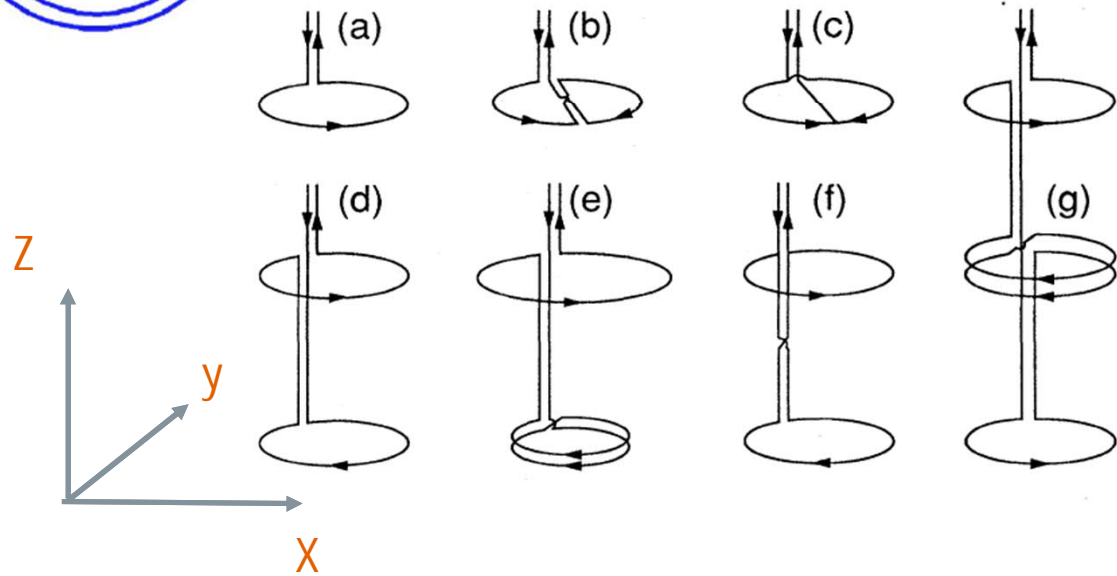Various pickup loops:  
magnetometers and  
gradiometers




# The thin-film stack of a washer SQUID

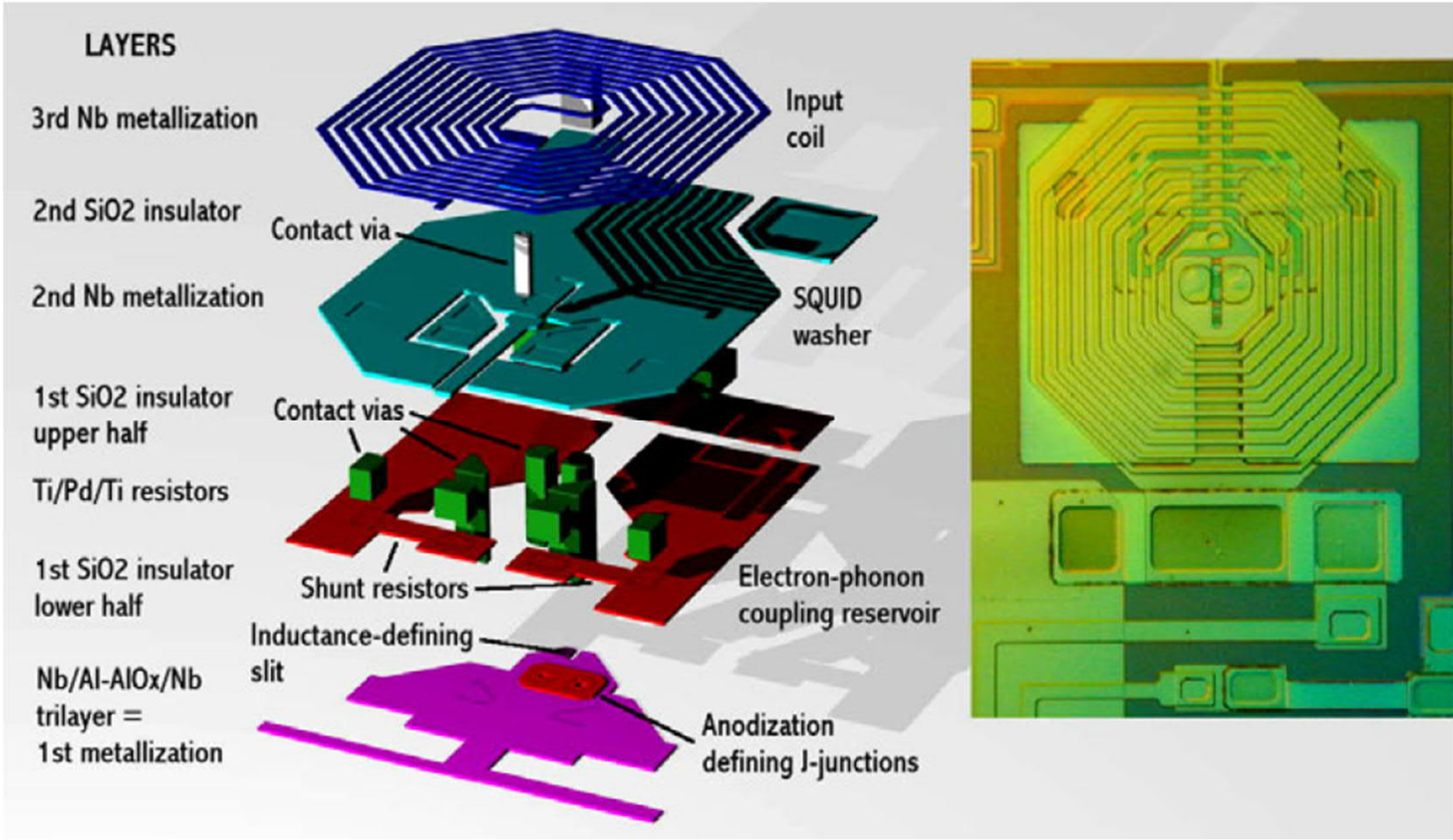

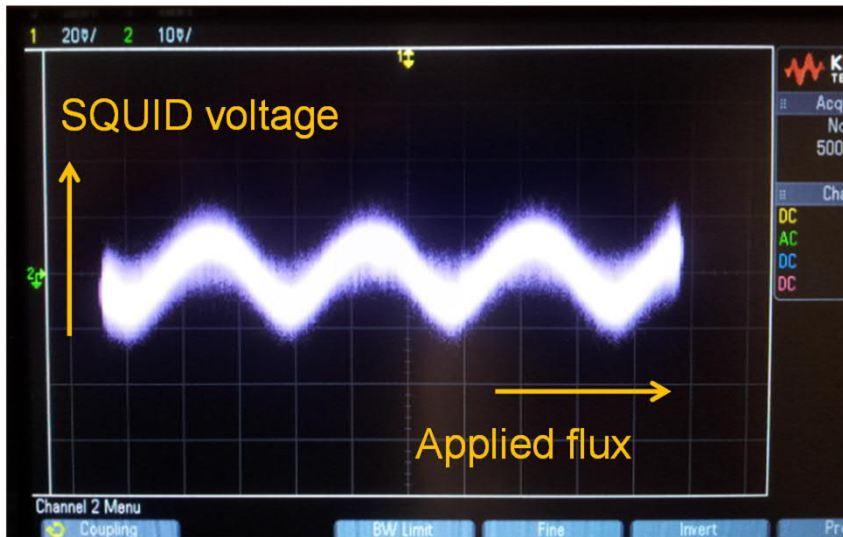
# SQUID readout in practice


What a SQUID flux characteristics may look like in a real experiment




20151214\_132039.jpg

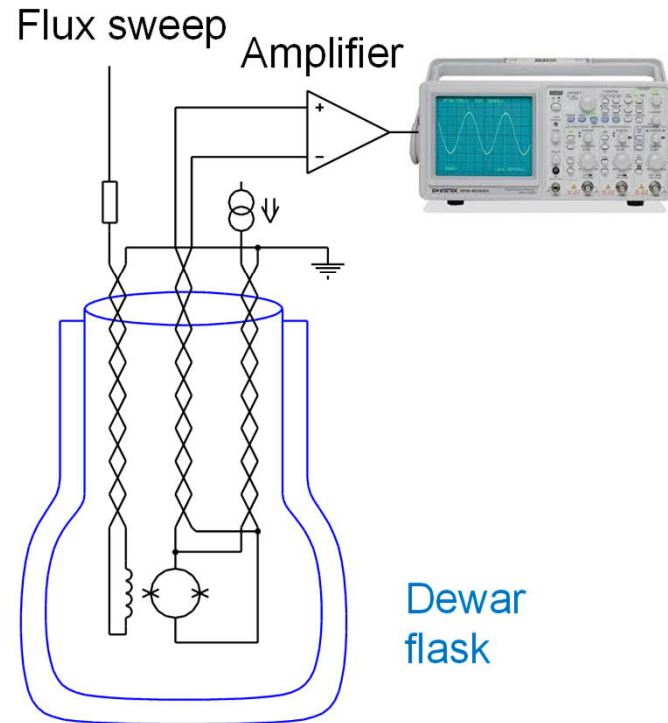



# Dc SQUID readout in practice

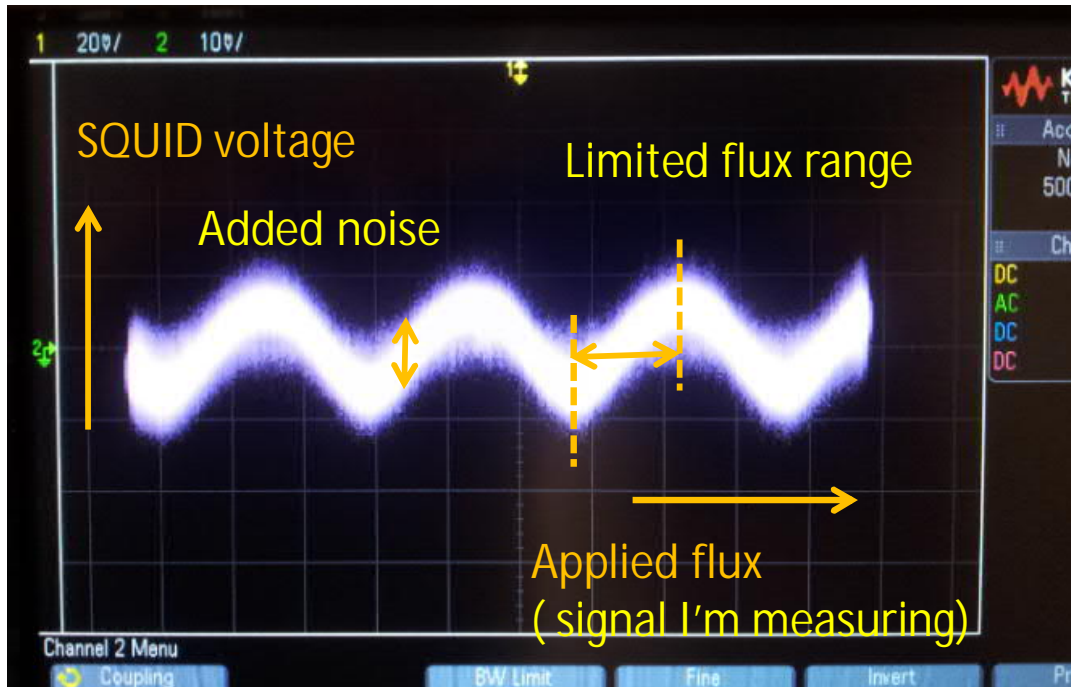

# Low Noise Amplifier (LNA) noise

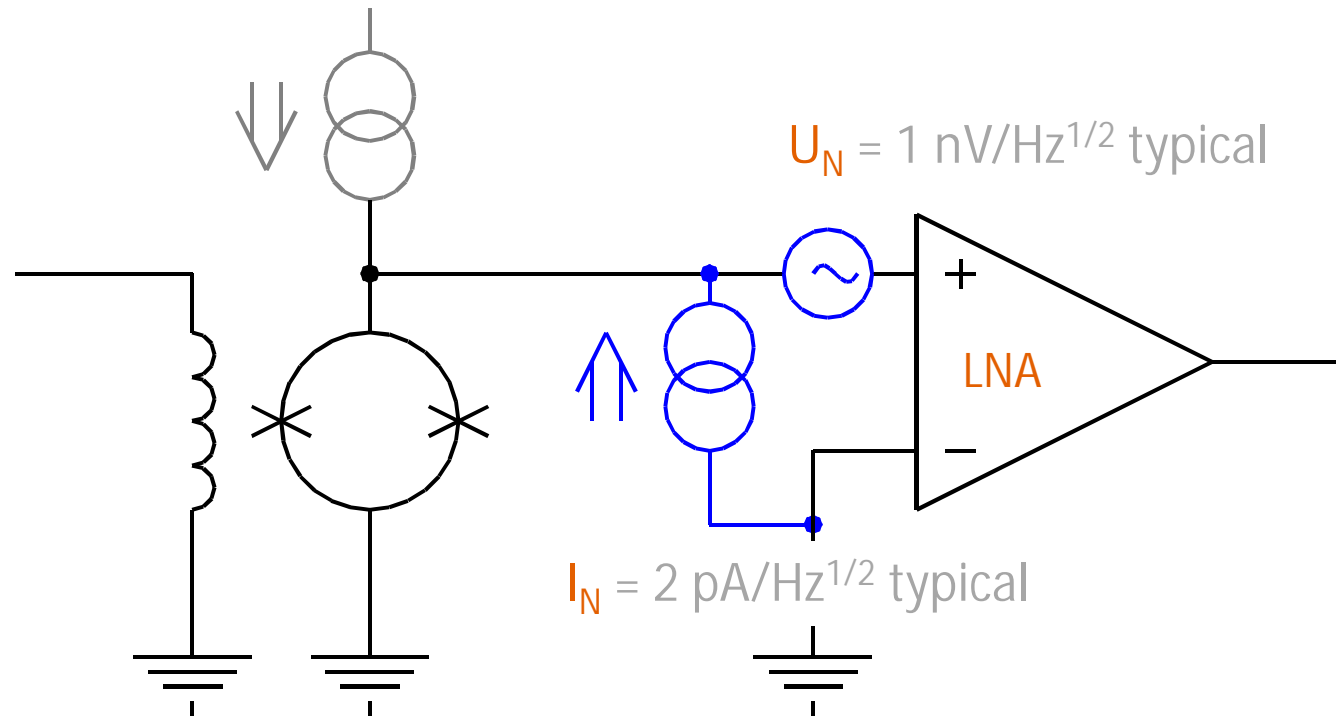


# Voltage noise at SQUID output

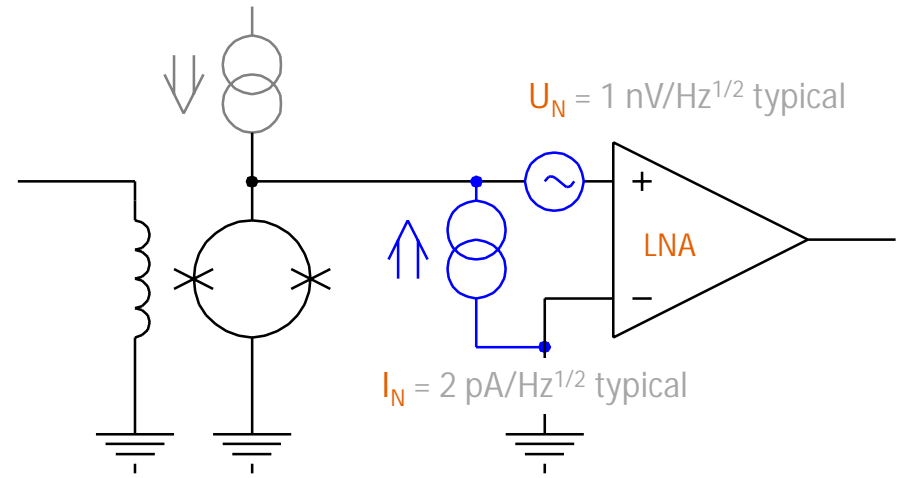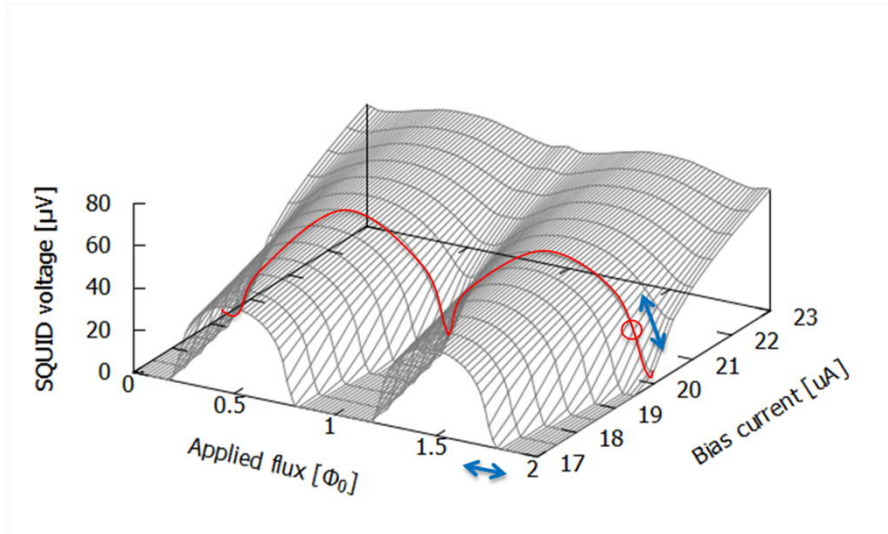


- SQUID  $\Delta V \approx 60 \mu V$
- $dV/d\Phi \approx 200 \mu V/\Phi_0$
- SQUID flux noise  $\Phi_N \approx 0.5 \mu\Phi_0 / \text{Hz}^{1/2}$
- $\Rightarrow$  Voltage noise at SQUID output  $0.1 \text{ nV} / \text{Hz}^{1/2}$
- $\Rightarrow$  LNA noise dominates (always, actually...)
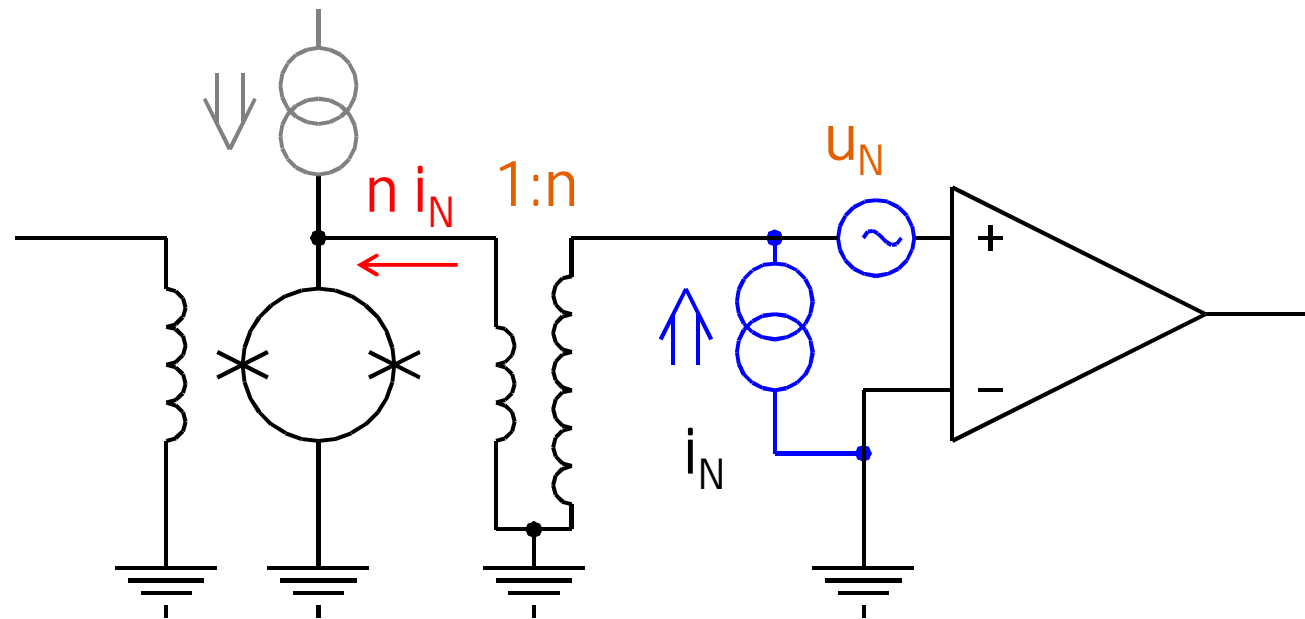
## Use transformer, to increase $dV/d\Phi$ ?




- Must chop SQUID signal (transformer does not pass DC)
- Current noise contribution  $i_N$  increases
- Feasible at low frequency, and using FET LNA.
- Was used in old days, not very practical today


# Positive feedback

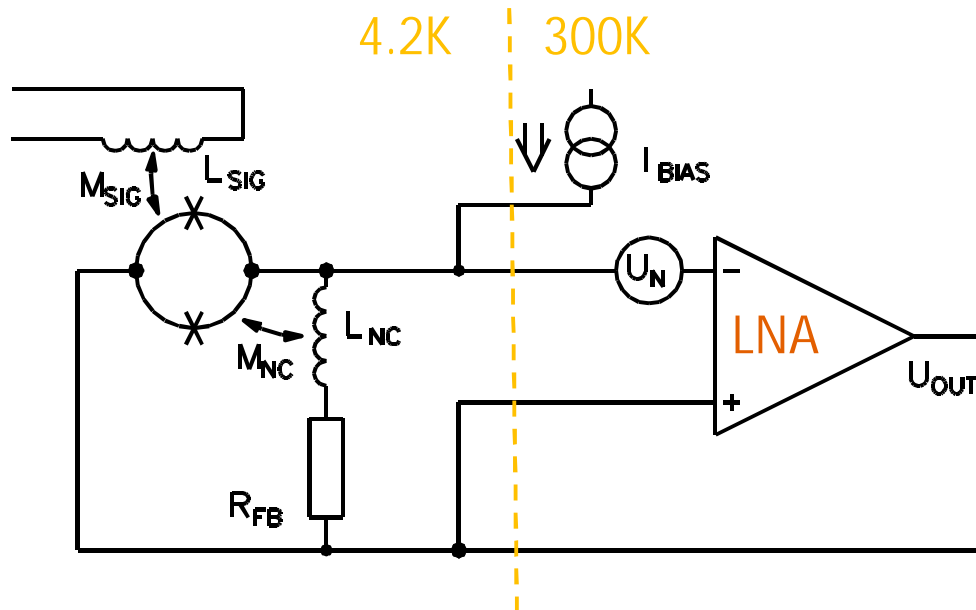

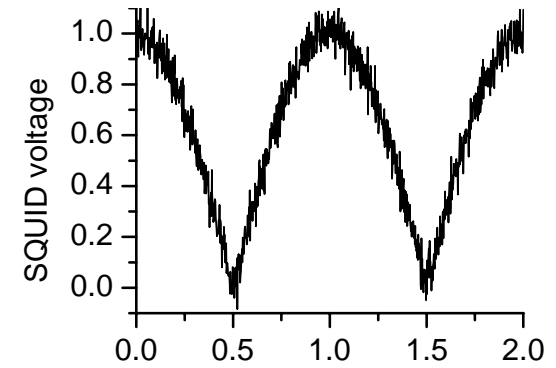- Part of the amplified flux signal is fed back as additional flux
- Narrowed flux operating range, adverse effect on input inductance  $L_{SIG}$  (if  $L_{NC}$  and  $L_{SIG}$  coupled)




Plain current-biased SQUID

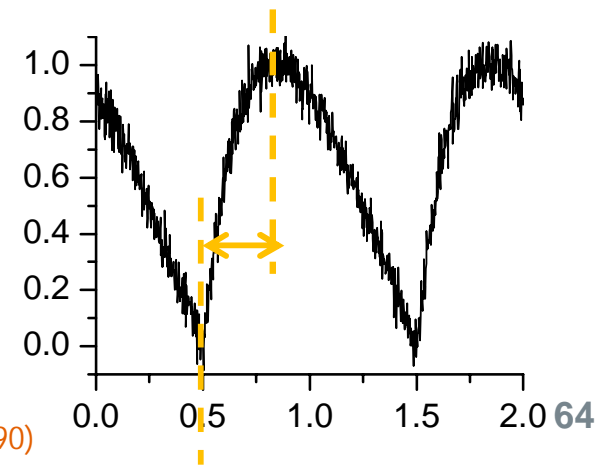

Drung et al, APL 57, 406 (1990)





# SQUID arrays

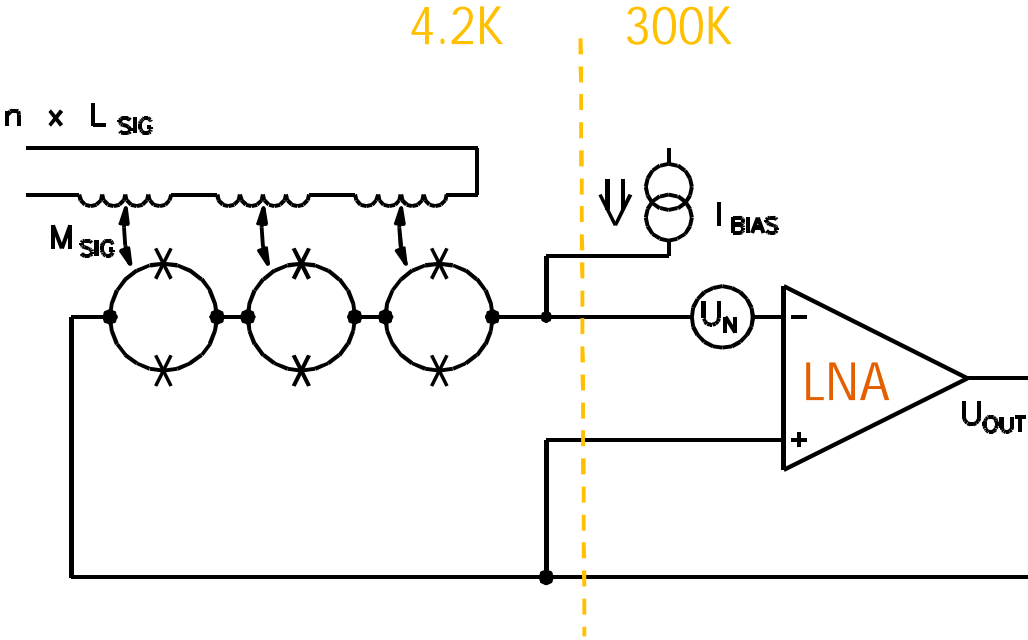

Welty and Martinis, IEEE Tran. Magn. 27 2924 (1991)


- N times the  $dV/d\Phi$  of a single constituent SQUID
- Recall that LNA –limited flux noise  $\Phi_N = u_N / (dV/d\Phi)$   
 $\Rightarrow$  improves  $\sim N$
- SQUID-limited flux noise improves  $\sim \sqrt{N}$   
 $\Rightarrow$  natural dynamic range improves  $\sim \sqrt{N}$   
 (DR: ratio of  $\Phi_N$  to  $\Phi_0/2$ )
- Coherent SQUID operation is a must !

# An example of a SQUID array

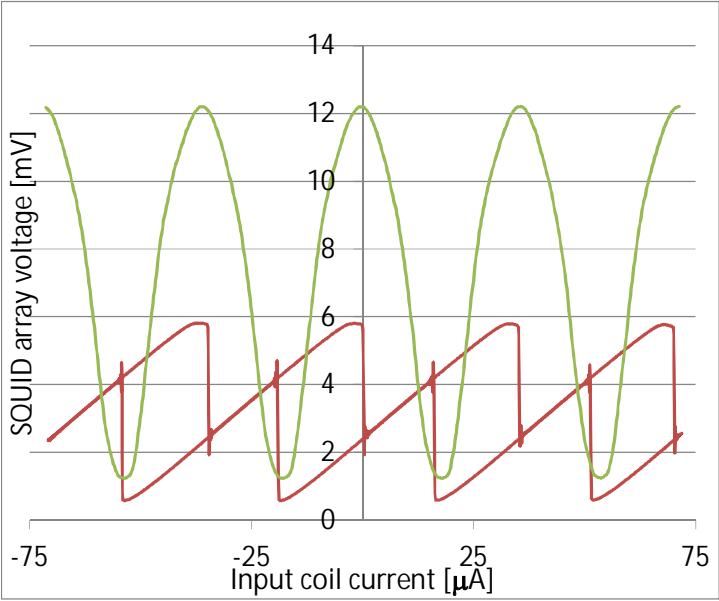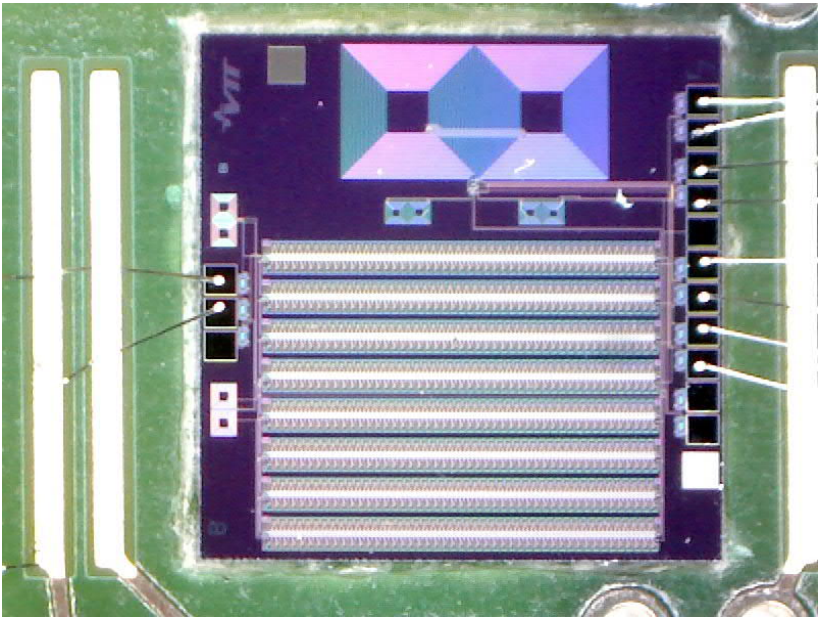





- 184-series 4-parallel SQUID array  
 $\Delta V \approx 11 \text{ mV}$ ,  $dV/d\Phi \approx 20 \text{ mV}/\Phi_0$

## Flux locked loop

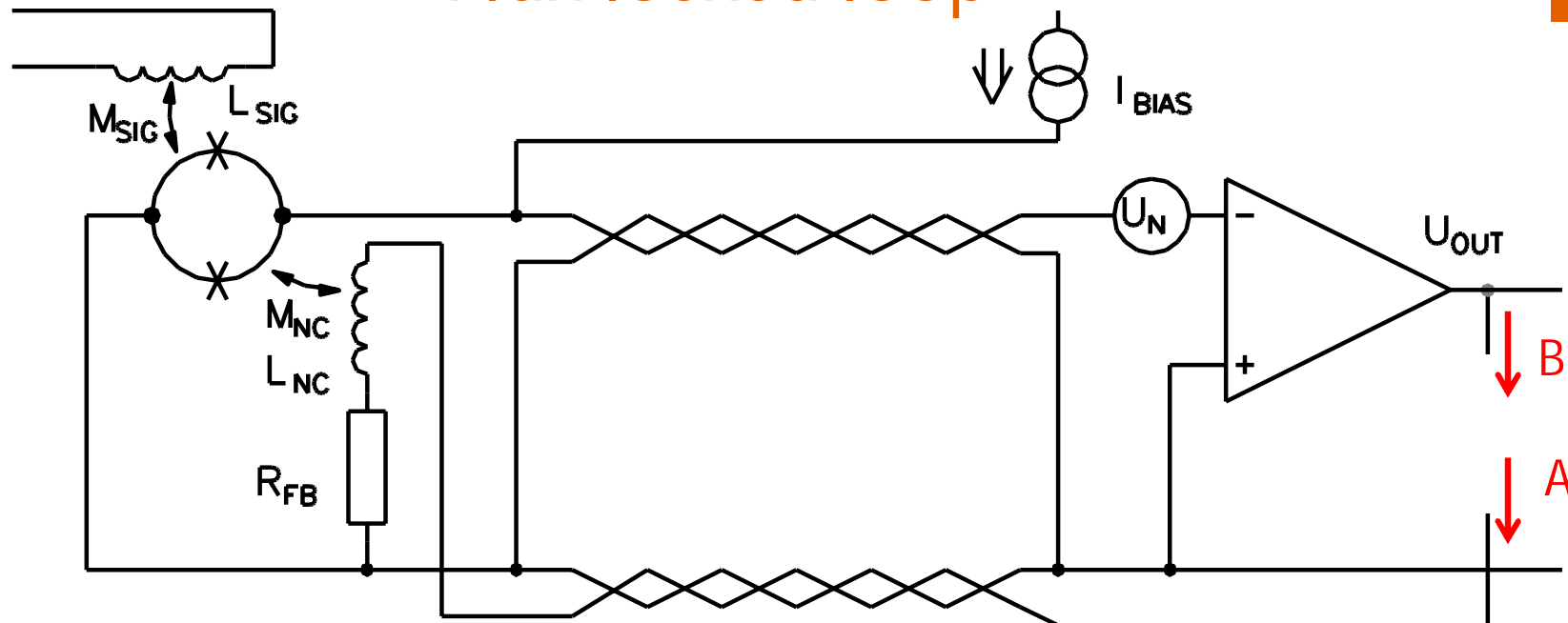


- Cut the loop open (any location will do)
- Inject test signal  $A$
- Measure response  $B$
- The ratio  $B/A$  is the loop gain  $L$
- Needs a loop filter  $A \rightarrow B$  (for stability)
- Just put an integrator there (for more, see <http://stacks.iop.org/SUST/16/1320>)

# Flux locked loop

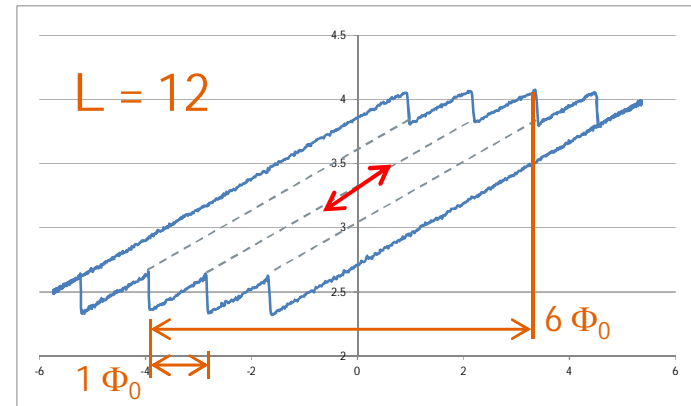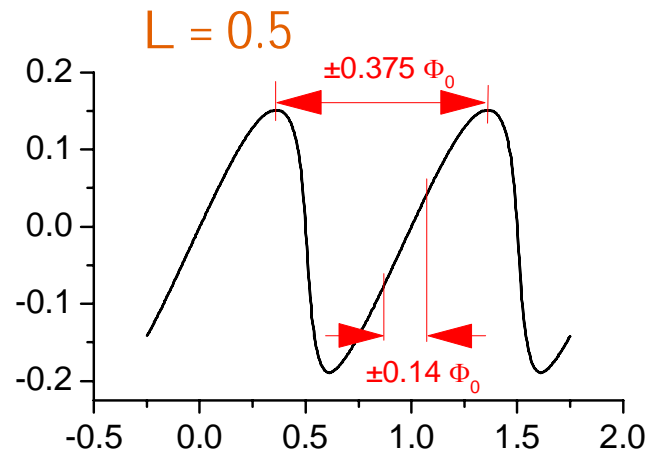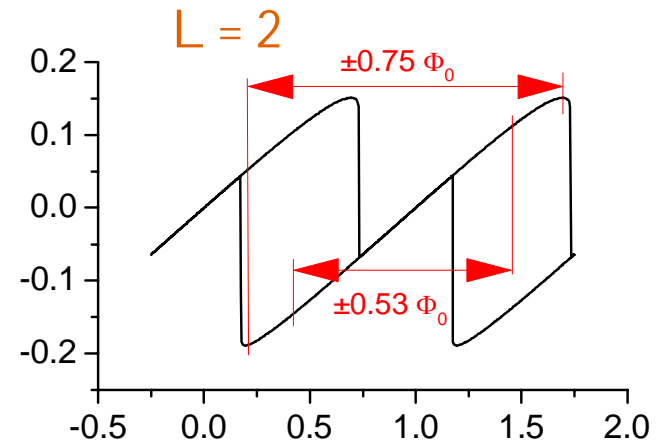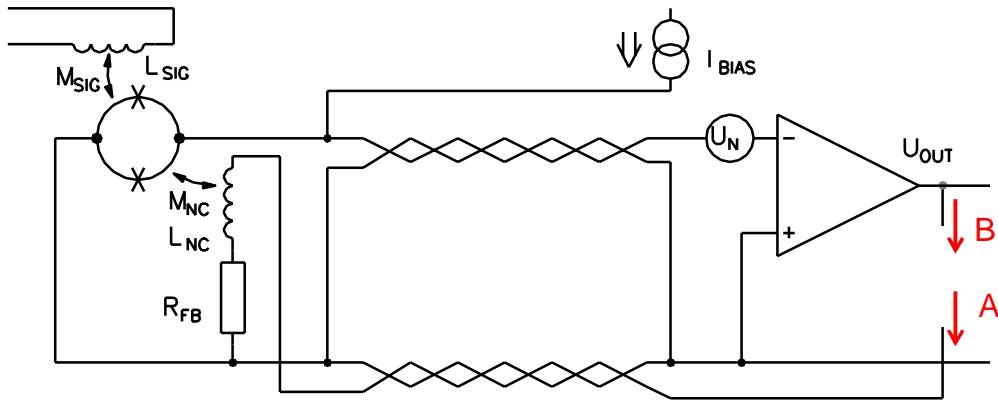

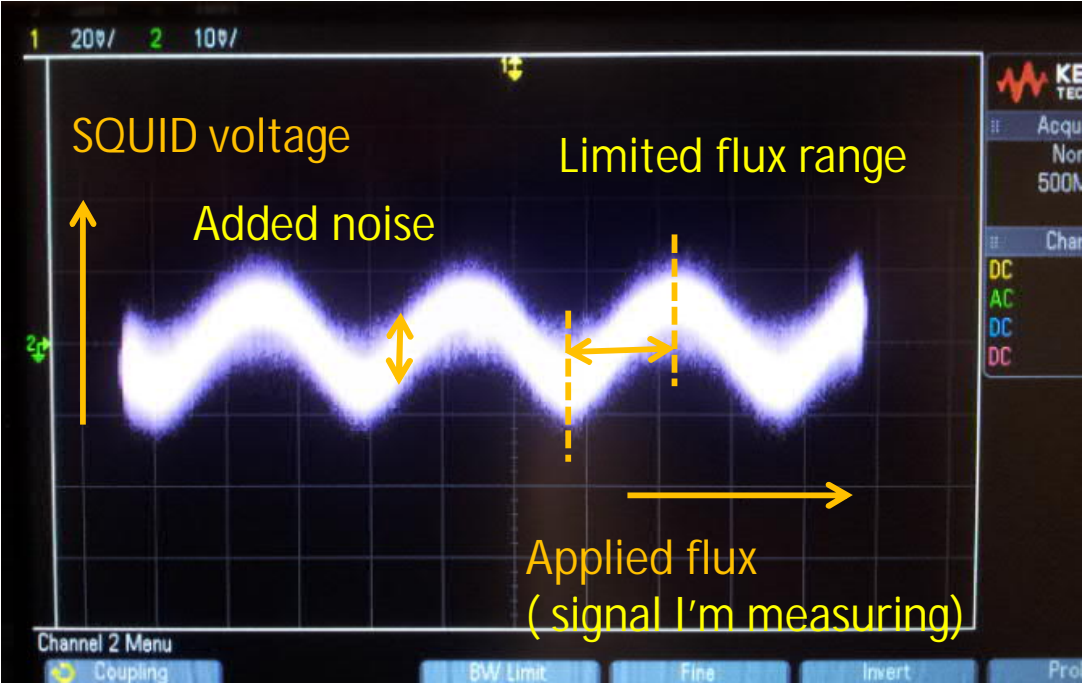With positive feedback (or array SQUID) and FLL we have mitigated the problems



## Thank you for listening

- Kirchoff laws with superconductors
- Weak link - flux quantization
- One-junction rf-SQUID - MISSING
- Two-junction dc-SQUID from SET – SQUID dualism
- Overdamped dc-SQUID, analytic solution
- Realistic dc SQUID characteristics
- A detour to 3-junction interferometer
- Different bias conditions
- Input coil, magnetometers and gradiometers
- SQUID readout, Flux-locked loop