



# **Development of $\mu$ HV (miniature HV supplies) at Nikhef**

Henk Boterenbrood, Harry van der Graaf, Henk Groenstege, Ruud Kluit,  
Fred Hartjes and Jaap Kuijt

RD51 Collaboration workshop  
Freiburg, 25 May 2010


# Why developing HV power supplies?

## ◆ Getting a HV supply that is dedicated for gaseous detectors

- Fast trip in sub  $\mu\text{A}$  region
- Accurate current measurement in nA region
- Small unit, not too expensive
- Fast remote control
- Gently ramping to target voltage
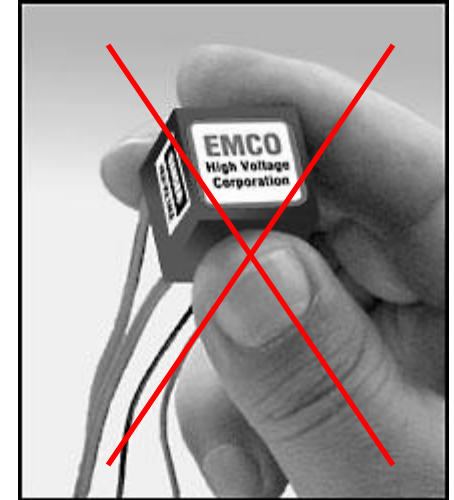
## ◆ In addition, for large scale HEP experiments, one would like having these units close to the detectors in the hot region

- Non-magnetic
- Minimal mass
- Radhard
- Low noise emittance



# Developing two designs

## 1. **Mini HV** for use in the lab, testbeams etc

- Practical in use, relatively small, not completely antimagnetic
  - But **NO** inductors, transformers


## 2. **Micro HV** for use near the detectors in a big experiment

- Very low mass, non-magnetic, radhard (until 1000 Mrad/  $10^7$  Gy)

◆ Presently we are developing **mini HV**

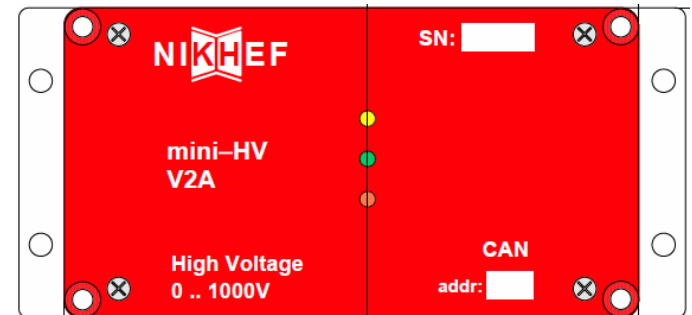
# Preliminary specs of mini HV, version 2

- ◆ Output ~ -3 to -1000V @ 1.8  $\mu$ A max
  - Steps of 73.6 mV
- ◆ Ripple 2 mV p-p @ 1  $\mu$ A expected
- ◆ Ramping: initially linear, followed by exponential approach to target voltage
  - Linear part adjustable in units of 73.6 mV/s
- ◆ Current measurement in 56 pA units
- ◆ Communication by CANopen protocol
- ◆ Single RJ45 cable for CAN communication and supply
  - Can be daisy chained
- ◆ Cast aluminium box 112 x 60 mm, 31 mm high
  - SHV out



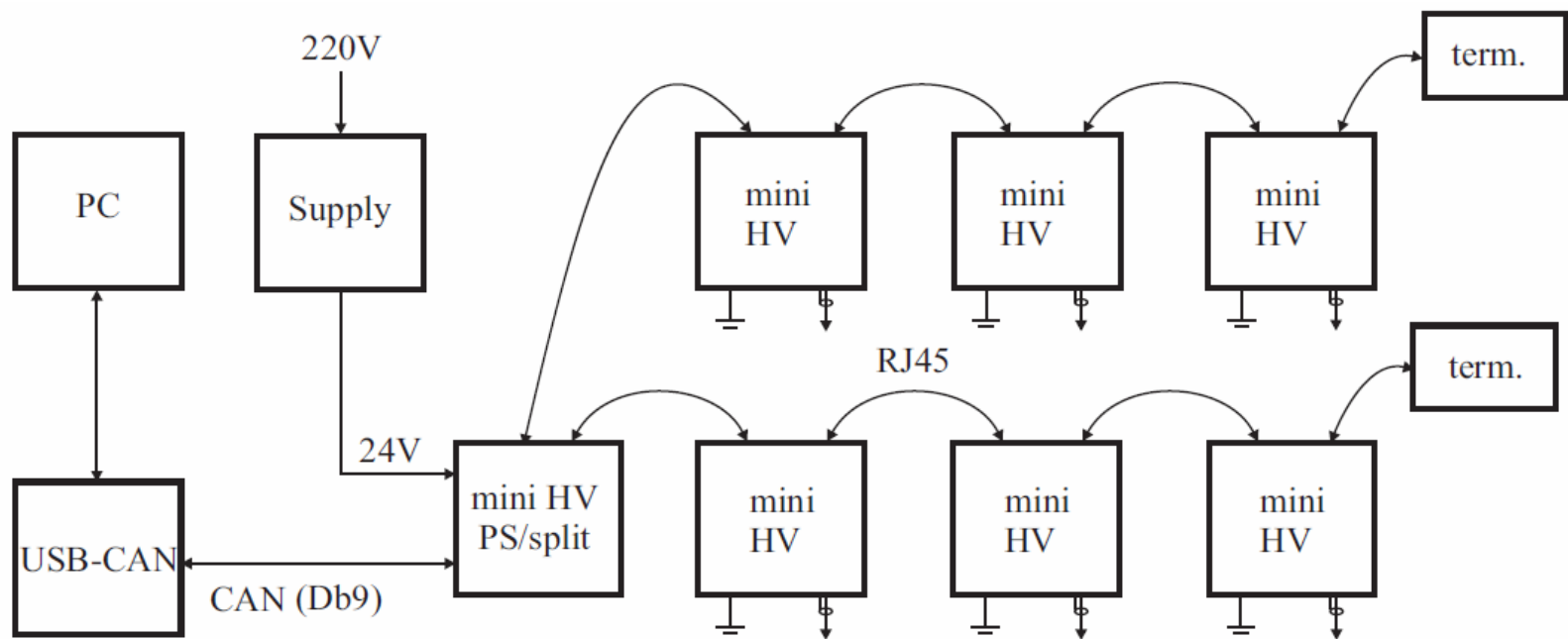
# CANopen communication to multiple mini HVs

- ◆ Single RJ45 cable to supply everything



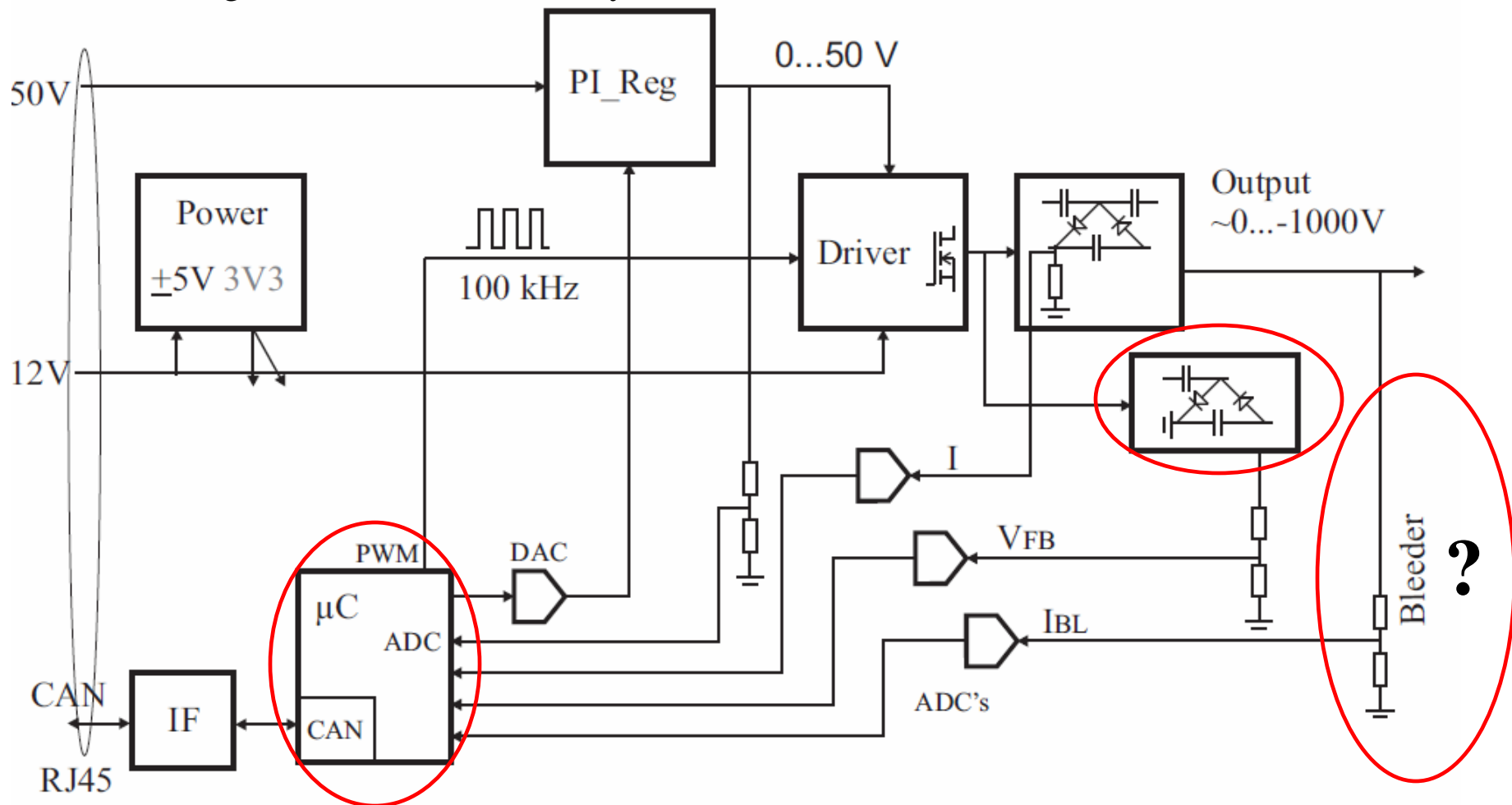
# Block diagram of single mini HV unit

- ◆ Chop frequency may be modified
- ◆ Trip by CAN logic processor, depending on voltage ramp
  - E.g. Trip 5 nA @ ramp 1V/s
- ◆ Voltage feedback from dummy diode circuit


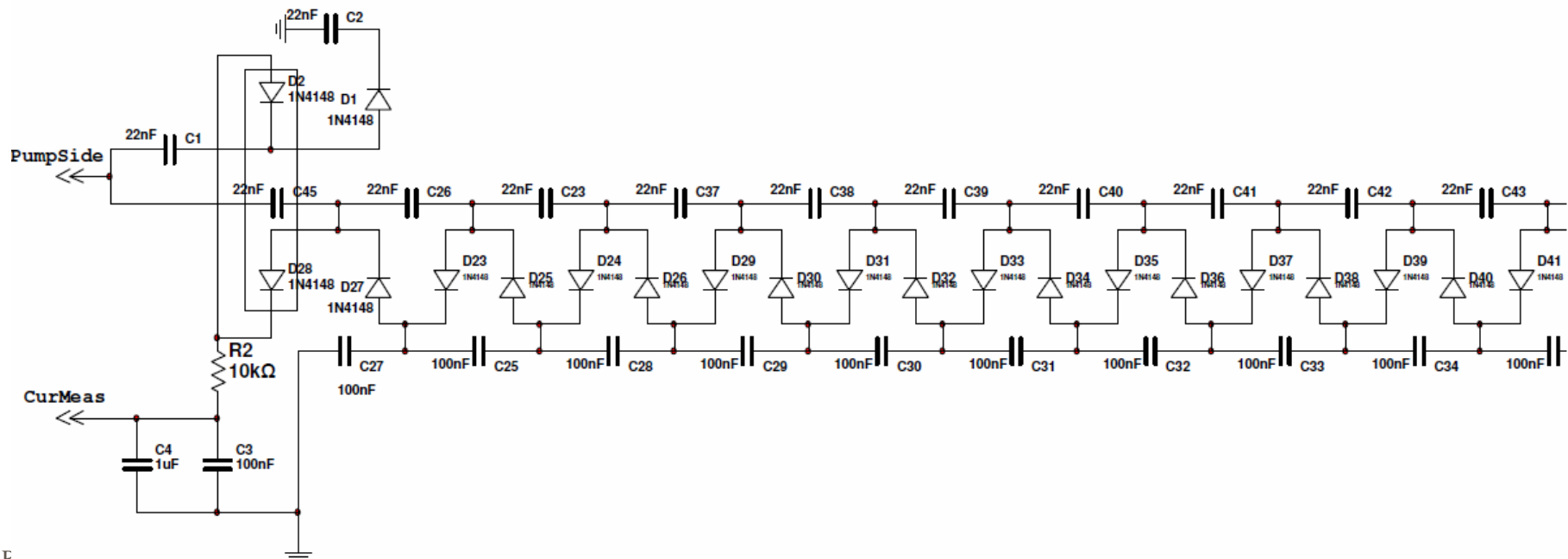
# Cockcroft-Walton circuit


- ◆ In principle no feedback at end of diode chain, only from first diode circuit
- ◆ Advantages
  - Accurate measurement of output current in nA region
  - Sensitive trip possible
- ◆ Disadvantage
  - Regulation less direct, depending on diode characteristics
- ◆ Output capacitance  $\sim 5$  nF



# Fast ramping possible

- ◆ Measured rise time without slope adjustment ~ 100 ms (from 0 to -480V)
  - No overshoot


Saved: 14 APR 2010 13:59:12

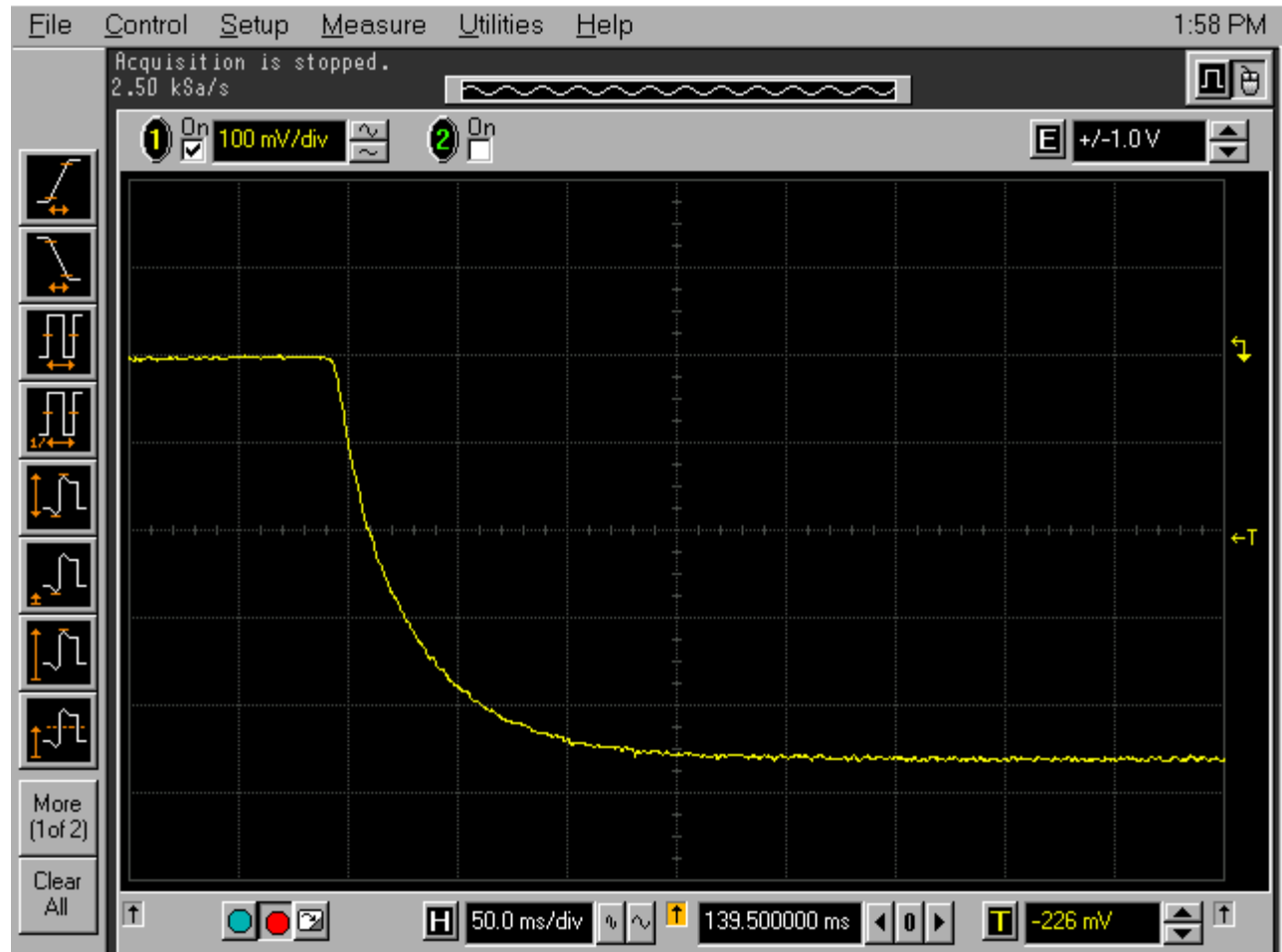


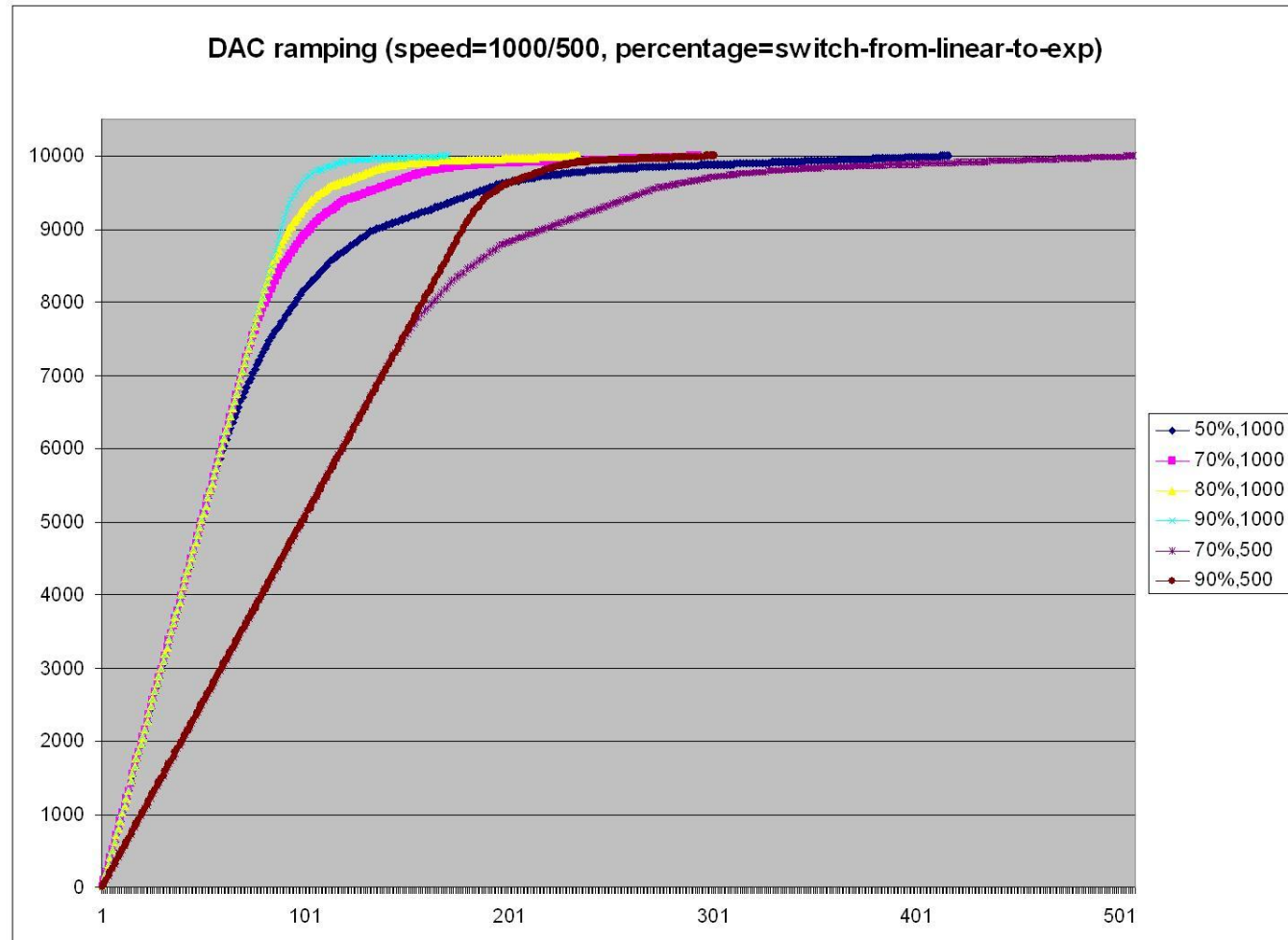
# Simulation of smooth ramping

- ◆ Linear rise adjustable in steps of  $-73.6$  mV/s
- ◆ Followed by exponential approach to target voltage
- ◆ Slope parameters controlled by CANopen commands
  - Linear slope
  - Start exponential part



# CANopen Object Dictionary prepared

MicroHV software

v0.1 3-Feb-2009

*MicroHV*

CANopen application software  
for the

'Micro' High-Voltage Powersupply Controller

Henk Boterenbrood  
NIKHEF, Amsterdam  
3 February 2010

*Version 0.1*

Manufacturer-Specific Profile Area (continued...)						
Index (hex)	Sub Index	Name	Data/Object	Attr	Default	Comment
2500		DAC configuration	Record			
	0	Number of entries	U8	RO	2	
*	1	SPI SCLK signal high period (opto-coupler delay)	U8	RW	10	in $\mu\text{s}$ , $10 \leq \text{value} \leq 255$
*	2	Ramp speed	U16	RW	0	If $\neq 0$ ramp speed is taken into account; in DAC-counts per sec
	3	Ramping pause/continue	Bool	RW		Ramping in progress or not (read), pause/continue ramping (write)
*	4	Percentage to switch from linear to exponential ramping	U8	RW	90	The percentage of the requested DAC end-value at which up-ramping (not down) switches from linear to exponential, taking the set ramp speed into account
2600		PWM configuration	Record			PWM waveforms on AT90CAN64 outputs OC3B/C
	0	Number of entries	U8	RO	4	
*	1	Start at power-up	Bool	RW	0	Start at power-up or not
*	2	Frequency	U8	RW	3	1 = 25KHz, 2 = 50KHz, 3 = 100KHz, 4 = 200KHz
*	3	Gap size	U8	RW	1	Gap between waveforms positive pulses, in units of system clock period (4 MHz, i.e. 250 ns)
	4	PWM stop/start	Bool	RW	0	PWM running or not (read), start or stop the PWM (write)


# Test results of two prototypes of mini HV version 1

◆ **Note: version 2 (in development) may have different performance**
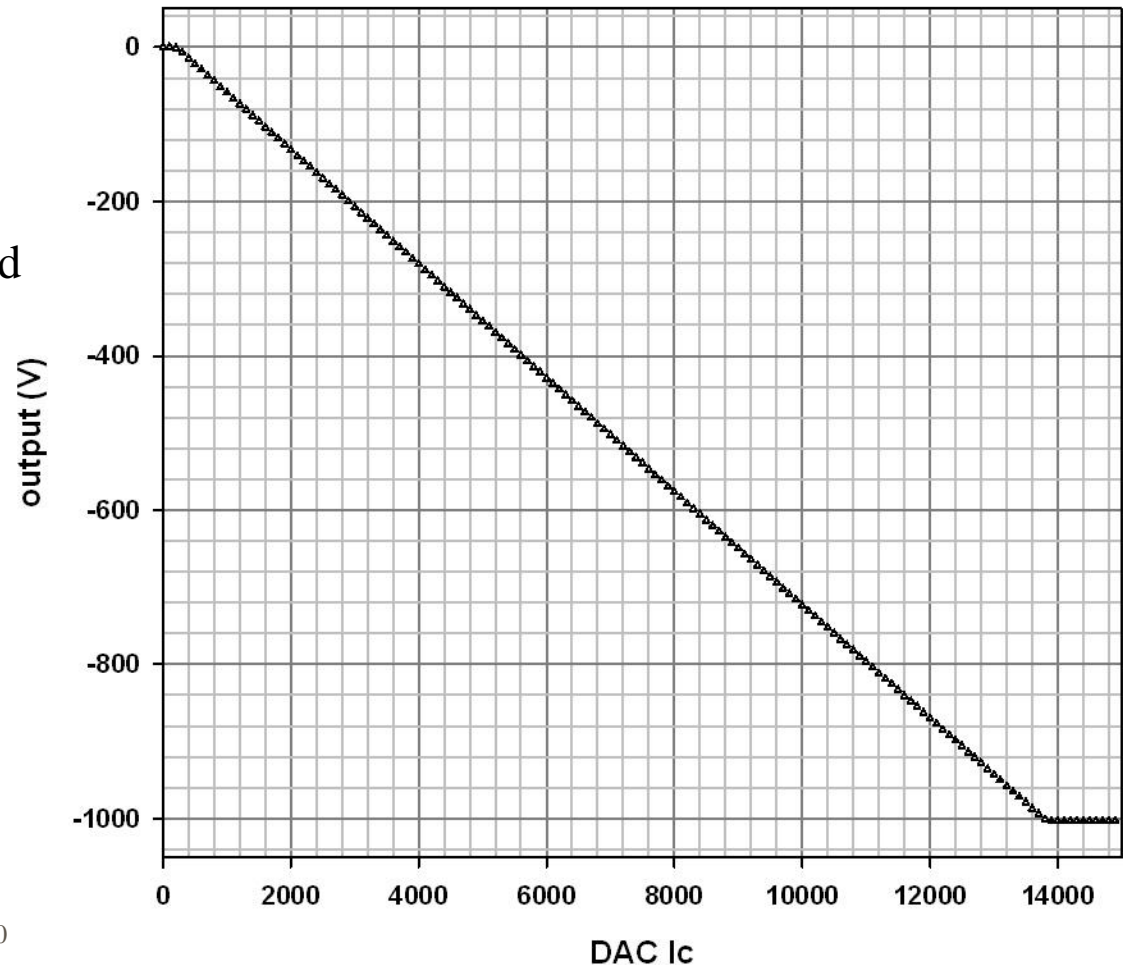
# Output voltage vs DAC value

Output voltage vs applied DAC value


- ◆ Unit 1.2
- ◆ Good linear behaviour over full range
- ◆ Voltage can be regulated in steps of 73.6 mV



# Detail at low voltage

Output voltage vs applied DAC value

- ◆ Starting from  $\sim -3\text{V}$  on

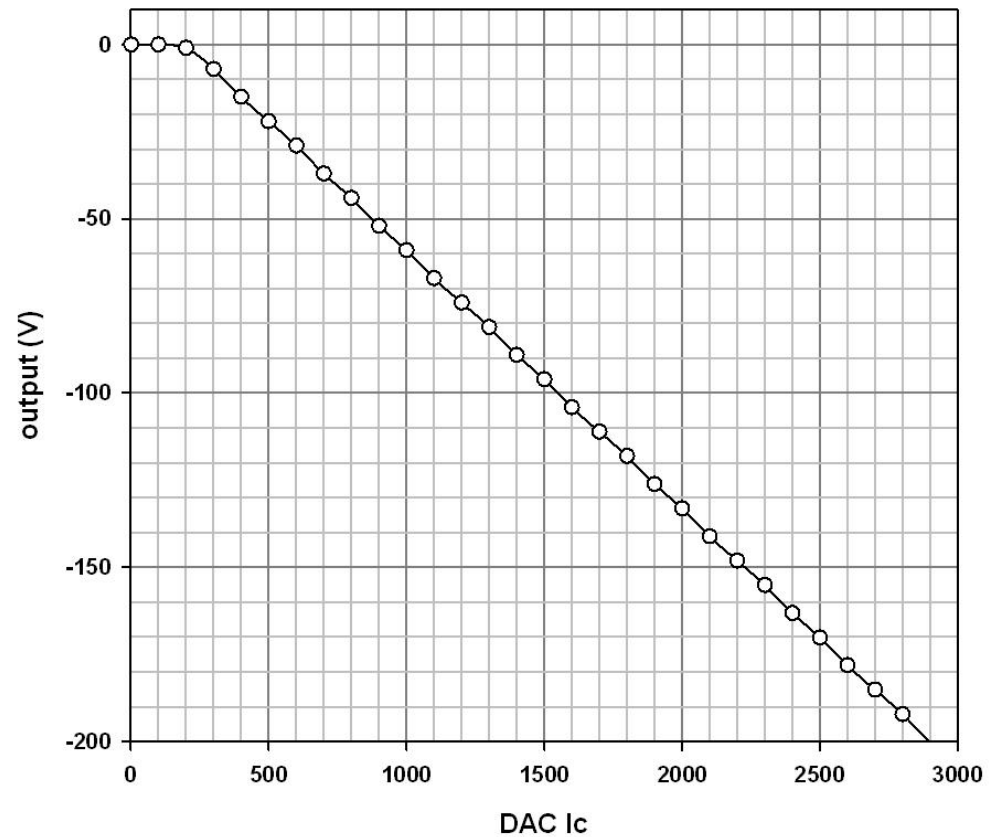


# Current measurement

- ◆ Unit 1.2
- ◆ Steps of  $\sim 56$  pA
- ◆ Certain deviation from linear response
- ◆ RMS  $\sim 50$  pA
  - Measured at  $-500$  V and  $500$  nA

Measured output current vs actual output current  
 $f = 606.8 - 18.18 * x$

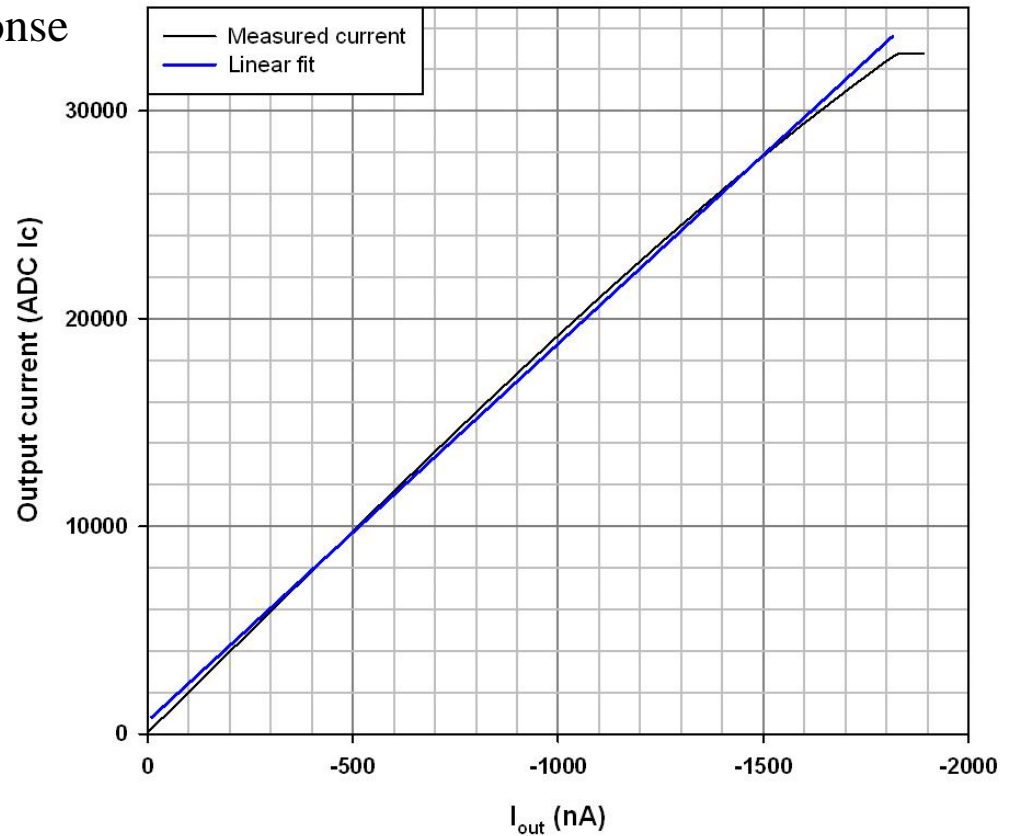HV unit 1.2  
13-14/4/2010  
Fred Hartjes



# Voltage regulation

Output voltage vs output current

HV  
22/  
Fre  
DA


◆ Unit 1.2

◆ Output impedance  $\sim 10$  M $\Omega$  for currents  $> 200$  nA

◆  $\sim 10$  V higher output voltage for currents in few nA range compared to 200 nA

● Using two different types of diodes

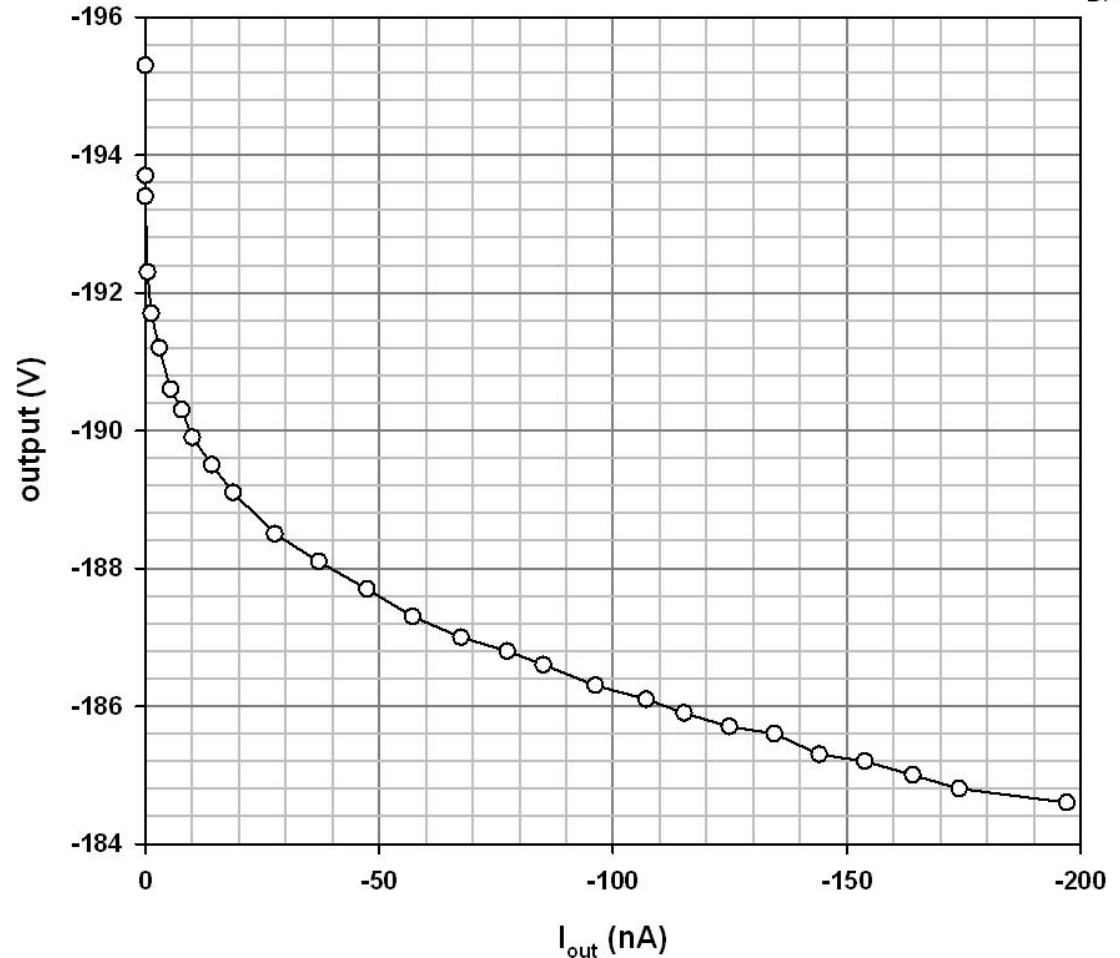●  $\Rightarrow$  Mismatch of diode characteristics



# Voltage regulation for Unit 1.1

## ◆ Basically no mismatch of diode characteristics

- => output impedance zero for currents  $> 150$  nA

- =>  $\sim 2$ V higher output voltage for currents in few nA range

## ◆ Remaining inaccuracy might be partly cured


- by adding bleeder resistors like  $50$  G $\Omega$  per cascade stage
- Making correction in CAN processor

## ◆ Alternative: voltage feedback

- But resistor may be less stable
- Regulation pretty slow


Output voltage vs output current

HV unit 1.1  
19-5-2010  
Fred Hartjes

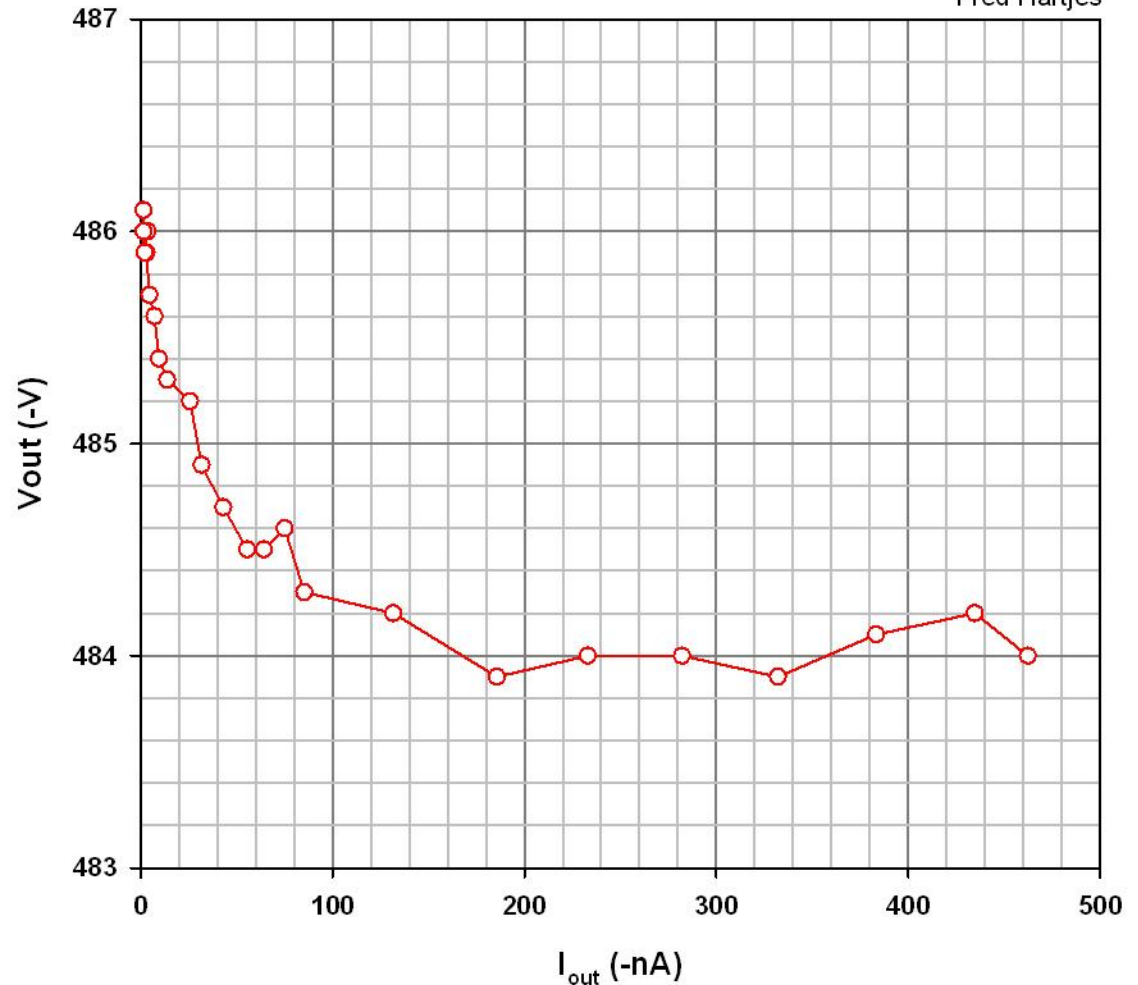



# Assembly in cast aluminium box

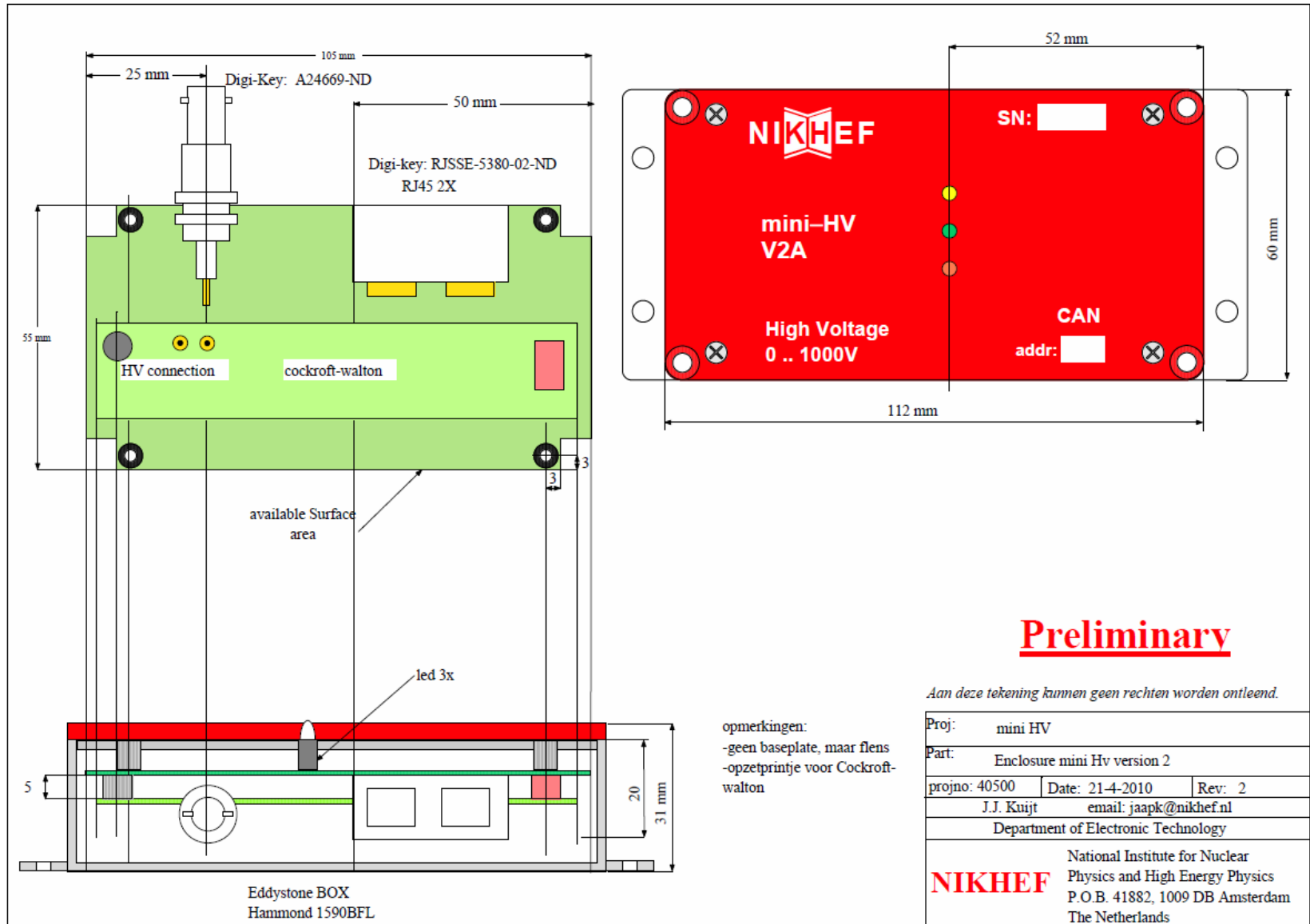

# Planned time schedule mini HV unit

- ◆ Version 1 ready
  - 2 prototypes (-500 and -1000V)
  - Not suited for series production
  
- ◆ Version 2 in development
  - Schematic to be finished
  - Layout PCB to be made
  - Production and assembly PCB
  - Assembly HV box
  
- ◆ Starting with producing **5** prototypes
  - Planned to be ready mid October
  - Production setup for 25 units

# Conclusions

- ◆ Global design for mini HV now settled
  - But still quite some detailing to be done
  
- ◆ Stabilize voltage
  - By individual calibration curve
  - By using voltage feedback from bleeder resistor
  
- ◆ Could start in autumn with some series production (~20 units)
  
- ◆ We might consider also more outputs
  - Like for GEM grids, omitting resistor chain
  - => bit larger housing
  
- ◆ Plan starting producing series of 20 in October 2010